

## Chapter 13

## Exercise Solutions

E13.3

$$V_{iN}(\max) = V^+ - V_{BE}(\text{on}) = 15 - 0.6 = 14.4 \text{ V}$$

$$V_{iN}(\min) \approx 4V_{BE}(\text{on}) + V^+$$

$$= 4(0.6) - 15 = -12.6 \text{ V}$$

$$\underline{-12.6 \leq V_{iN}(\text{cm}) \leq 14.4 \text{ V}}$$

E13.4

$$\text{a. } V_0(\max) \approx V^+ - 2V_{BE}(\text{on}) = 15 - 2(0.6)$$

$$V_0(\max) = 13.8 \text{ V}$$

$$V_0(\min) = 3V_{BE}(\text{on}) + V^- = 3(0.6) - 15$$

$$V_0(\min) \approx -13.2 \text{ V}$$

$$\underline{-13.2 \leq V_0 \leq 13.8 \text{ V}}$$

$$\text{b. } V_0(\max) = 5 - 1.2 = 3.8 \text{ V}$$

$$V_0(\min) \approx 3V_{BE} + V^- = 3(0.6) - 5 = -3.2 \text{ V}$$

$$\underline{-3.2 \leq V_0 \leq 3.8 \text{ V}}$$

E13.5

$$I_{C1} = I_{C2} \approx 9.5 \mu\text{A}$$

$$I_{B1} = I_{B2} = \frac{9.5 \mu\text{A}}{200} = 0.0475 \mu\text{A}$$

$$\Rightarrow \underline{I_{B1} = I_{B2} = 47.5 \text{ nA}}$$

E13.6

$$I_{REF} \approx \frac{15 - 2(0.6) - (-15)}{40} = 0.72 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) = (0.026) \ln \left( \frac{0.72 \times 10^{-3}}{10^{-14}} \right)$$

$$= 0.650 \text{ V}$$

So

$$I_{REF} = \frac{30 - 2(0.65)}{40} \Rightarrow \underline{I_{REF} = 0.718 \text{ mA}}$$

$$\underline{V_{BE11} = 0.650 \text{ V}}$$

$$I_{C10}R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.718}{I_{C10}} \right)$$

$$\text{By trial and error: } I_{C10} = 18.9 \mu\text{A}$$

$$V_{BE10} = V_{BE11} - I_{C10}R_4 = 0.650 - (0.0189)(5)$$


$$\Rightarrow \underline{V_{BE10} \approx 0.556 \text{ V}}$$

$$I_{C6} \approx \frac{I_{C10}}{2} = \frac{18.9}{2} = 9.45 \mu\text{A}$$

$$V_{BE6} = V_T \ln \left( \frac{I_{C6}}{I_S} \right) = (0.026) \ln \left( \frac{9.45 \times 10^{-6}}{10^{-14}} \right)$$

$$\Rightarrow \underline{V_{BE6} = 0.537 \text{ V}}$$

E13.7

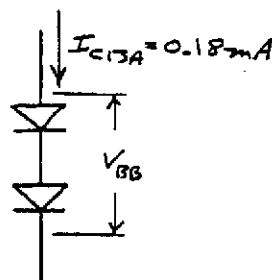

$$0.18 \times 10^{-3} = 10^{-14} \exp \left( \frac{V_D}{V_T} \right)$$

$$V_D = V_T \ln \left( \frac{0.18 \times 10^{-3}}{10^{-14}} \right)$$

$$= (0.026) \ln \left( \frac{0.18 \times 10^{-3}}{10^{-14}} \right)$$

$$V_D = 0.6140$$

$$\underline{V_{BB} = 2V_{DD} \approx 1.228 \text{ V}}$$

$$I_{C14} = I_{C20} = I_S \exp \left( \frac{V_{BB}/2}{V_T} \right)$$

$$= 3 \times 10^{-14} \exp \left( \frac{0.6140}{0.026} \right)$$

$$\underline{I_{C14} = I_{C20} = 0.541 \text{ mA}}$$

E13.8

$$I_{REF} = \frac{10 - 0.6 - 0.6 - (-10)}{40}$$

$$\Rightarrow \underline{I_{REF} = 0.47 \text{ mA}}$$

$$I_{C10}R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.47}{I_{C10}} \right)$$

By trial and error:

$$\Rightarrow \underline{I_{C10} \approx 17.2 \mu\text{A}}$$

$$I_{C6} \approx \frac{I_{C10}}{2} \Rightarrow \underline{I_{C6} = 8.6 \mu\text{A}}$$

$$I_{C13B} = (0.75)I_{REF} \Rightarrow \underline{I_{C13B} = 0.353 \text{ mA}}$$

$$I_{C13A} = (0.25)I_{REF} \Rightarrow \underline{I_{C13A} = 0.118 \text{ mA}}$$



E13.12

(a) For  $M_1$ ,  $K_{p1} = 125 \mu A/V^2$

$$K_{p1}(V_{SG1} + V_{TP})^2 = \frac{V^+ - V^- - V_{SG1}}{R_{out}}$$

$$0.125(V_{SG1} - 0.5)^2 = \frac{5 + 5 - V_{SG1}}{100}$$

$$12.5(V_{SG1}^2 - V_{SG1} + 0.25) = 10 - V_{SG1}$$

$$12.5V_{SG1}^2 - 11.5V_{SG1} - 6.875 = 0$$

$$V_{SG1} = \frac{11.5 \pm \sqrt{(11.5)^2 + 4(12.5)(6.875)}}{2(12.5)}$$

$$V_{SG1} = 1.33 \text{ V}$$

Then

$$I_{REF} = I_Q = I_{D8} = I_{D7} = \frac{10 - 1.33}{100} \Rightarrow 86.7 \mu A$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I_Q}{2} = 43.35 \mu A$$

(b)  $K_{p1} = K_{p2} = 125 \mu A/V^2$

$$r_{o2} = r_{o4} = \frac{1}{\lambda_D} = \frac{1}{(0.02)(0.04335)} = 1153 \text{ k}\Omega$$

Input stage gain

$$\begin{aligned} A_d &= \sqrt{2K_{p1}I_{D1}} \cdot (r_{o2} \parallel r_{o4}) \\ &= \sqrt{2(0.125)(0.0867)} \cdot (1153 \parallel 1153) \Rightarrow \\ A_d &= 84.9 \end{aligned}$$

Transconductance of  $M_7$

$$\begin{aligned} g_{m7} &= 2\sqrt{K_{p1}I_{D7}} = 2\sqrt{(0.125)(0.0867)} \\ &= 0.294 \text{ mA/V} \end{aligned}$$

$$r_{o7} = r_{o8} = \frac{1}{\lambda_{D7}} = \frac{1}{(0.02)(0.0867)} = 577 \text{ k}\Omega$$

Second stage gain

$$\begin{aligned} A_{v2} &= g_{m7}(r_{o7} \parallel r_{o8}) = (0.294)(577 \parallel 577) \Rightarrow \\ A_{v2} &= 84.8 \end{aligned}$$

$$\begin{aligned} \text{Overall gain} &= A_d \cdot A_{v2} = (84.9)(84.8) \Rightarrow \\ A &= 7,200 \end{aligned}$$

E13.13

$$I_{D1} = I_{D2} = 25 \mu A$$

$$g_{m1} = g_{m2} = 2\sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)I_{D2}} = 2\sqrt{\left(\frac{40}{2}\right)(25)(25)} \Rightarrow$$

$$g_{m1} = g_{m2} = 224 \mu A/V$$

$$g_{m6} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D2}} = 2\sqrt{\left(\frac{80}{2}\right)(25)(25)} \Rightarrow$$

$$g_{m6} = 316 \mu A/V$$

$$r_{o1} = r_{o6} = r_{o4} = r_{o10} = \frac{1}{\lambda_D} = \frac{1}{(0.02)(25)} = 2 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_{D4}} = \frac{1}{(0.02)(50)} = 1 \text{ M}\Omega$$

$$R_{o4} = g_{m6}(r_{o6} \parallel r_{o10}) = (224)(2)(2) = 896 \text{ M}\Omega$$

$$R_{o6} = g_{m2}(r_{o2} \parallel r_{o1}) = 316(2)(1 \parallel 2) = 421 \text{ M}\Omega$$

Then

$$A_d = g_{m1}(R_{o4} \parallel R_{o6}) = 224(421 \parallel 896) \Rightarrow$$

$$A_d = 64,158$$

E13.14

$$(a) A_d = Bg_{m1}(r_{o6} \parallel r_{o8})$$

$$g_{m1} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D1}} = 2\sqrt{\left(\frac{80}{2}\right)(20)(50)}$$

$$g_{m1} = 400 \mu A/V$$

$$r_{o6} = \frac{1}{\lambda_p I_{D6}} = \frac{1}{(0.02)(150)} = 0.333 \text{ M}\Omega$$

$$r_{o8} = \frac{1}{\lambda_n I_{D8}} = \frac{1}{(0.02)(150)} = 0.333 \text{ M}\Omega$$

$$A_d = 3(400)(0.333 \parallel 0.333) \Rightarrow A_d = 200$$

$$(b) f_{PD} = \frac{1}{2\pi R_o(C_L + C_p)}$$

$$\text{where } R_o = r_{o6} \parallel r_{o8} = 0.333 \parallel 0.333 \text{ M}\Omega$$

$$f_{PD} = \frac{1}{2\pi(0.333 \parallel 0.333) \times 10^6 \times 2 \times 10^{-12}} \Rightarrow$$

$$f_{PD} = 477 \text{ kHz}$$

$$f_{PD} \cdot A_d = (477 \times 10^3)(200) \Rightarrow 95.4 \text{ MHz}$$

E13.15

(a) From Exercise 13.14,  $g_{m1} = 400 \mu A/V$

$$r_{o6} = r_{o8} = r_{o10} = r_{o12} = 0.333 \text{ M}\Omega$$

$$g_{m10} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D10}} = 2\sqrt{\left(\frac{40}{2}\right)(20)(150)} \Rightarrow$$

$$g_{m10} = 490 \mu A/V$$

$$g_{m12} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D12}} = 2\sqrt{\left(\frac{80}{2}\right)(20)(150)} \Rightarrow$$

$$g_{m12} = 693 \mu A/V$$

$$R_{o10} = g_{m10}(r_{o10} \parallel r_{o6}) = (490)(0.333 \parallel 0.333) = 54.3 \text{ M}\Omega$$

$$R_{o12} = g_{m12}(r_{o12} \parallel r_{o8}) = (693)(0.333 \parallel 0.333) = 76.8 \text{ M}\Omega$$

$$A_d = Bg_{m1}(R_{o10} \parallel R_{o12}) = 3(400)(54.3 \parallel 76.8) \Rightarrow$$

$$A_d = 38,172$$

$$(b) R_o = R_{o10} \parallel R_{o12} = 54.3 \parallel 76.8 = 31.8 \text{ M}\Omega$$

$$f_{PD} = \frac{1}{2\pi(31.8 \times 10^6)(2 \times 10^{-12})} = 2.50 \text{ kHz}$$

$$f_{PD} \cdot A_d = (2.5 \times 10^3)(38,172) \Rightarrow 95.4 \text{ MHz}$$

## E13.16

$$(a) A_d = g_m(R_{os} \parallel R_{os})$$

From Example 13.10,

$$g_m = 316 \mu A/V, R_{os} = 316 M\Omega$$

Now

$$R_{os} = g_{m6}(r_{os} \parallel r_{o1})$$

$$r_{o1} = 1 M\Omega, r_{o4} = 0.5 M\Omega$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{50}{0.026} \Rightarrow 1.923 mA/V$$

$$r_{o4} = \frac{V_{A6}}{I_{C6}} = \frac{80}{50} = 1.6 M\Omega$$

Then

$$R_{os} = (1.923)(1600)(0.5 \parallel 1) = 1026 M\Omega$$

$$A_d = (316)(1026 \parallel 316) \Rightarrow A_d = 76,343$$

$$(b) f_{PD} = \frac{1}{2\pi(316 \parallel 1026) \times 10^6 \times 2 \times 10^{-12}} \Rightarrow$$

$$f_{PD} = 329 Hz$$

$$f_{PD} \cdot A_d = (329)(76,343) \Rightarrow 25.1 MHz$$

## E13.17

$$V^+ - V^- = V_{BE1} + V_{BE6} + V_{BE7} + I_1 R_1$$

$$= 0.6 + 0.6 + 0.6 + (0.24)(8) = 3.72 V$$

So

$$V^+ = -V^- = 1.86 V$$

## E13.18

For  $Q_7$  and  $R_1$

$$V_{SG} = V_{BE7} + I_1 R_1 = 0.6 + I_1(5)$$

For  $M_8$ :

$$I_1 = K_p(V_{SG} + V_{TP})^2$$


$$I_1 = 0.3(V_{SG} - 1.4)^2$$

By trial and error:

$$V_{SG} = 2.54 V$$

$$I_1 = I_2 = 0.388 mA$$

## E13.19

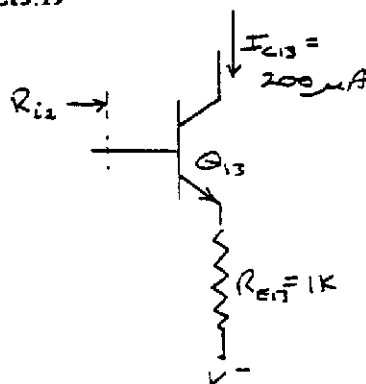

$$r_{\pi 13} = \frac{\beta V_T}{I_{C13}} = \frac{(200)(0.026)}{0.20}$$

$$= 26 k\Omega$$

$$R_{i2} = r_{\pi 13} + (1 + \beta)R_{E13} = 26 + 201(1)$$

$$= 227 k\Omega$$

$$r_{o10} = \frac{1}{\lambda I_{D10}} = \frac{1}{(0.02)(0.1)} = 500 k\Omega$$

$$r_{o12} = \frac{V_A}{I_{C12}} = \frac{50}{0.1} = 500 k\Omega$$

$$g_{m12} = \frac{I_{C12}}{V_T} = \frac{0.1}{0.026} = 3.85 mA/V$$

$$r_{\pi 12} = \frac{\beta V_T}{I_{C12}} = \frac{(200)(0.026)}{0.1} = 52 k\Omega$$

$$R_{accl} = r_{o12}[1 + g_{m12}(r_{\pi 12} \parallel R_5)]$$

$$= 500[1 + (3.85)(52 \parallel 0.5)] = 1453 k\Omega$$

$$A_d = \sqrt{2K_p I_{D5}} \cdot (r_{o10} \parallel R_{accl} \parallel R_{i2})$$

$$= \sqrt{2(0.6)(0.2)} \cdot (500 \parallel 1453 \parallel 227)$$

$$= (0.490)(141) \Rightarrow A_d = 69.1$$

## E13.20

For  $J_6$  biased in the saturation region

$$\Rightarrow I_{C3} = I_{D55} = 300 \mu A$$

$Q_1, Q_2, Q_3$  are matched

$$\Rightarrow I_{C1} = I_{C2} = I_{C3} = 300 \mu A$$

## Chapter 13

## Problem Solutions

13.3

$$(a) A_d = g_{m1}(r_{o2} \| r_{o4} \| R_{L6})$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{20}{0.026} \Rightarrow 0.769 \text{ mA/V}$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{80}{20} = 4 \text{ M}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C2}} = \frac{80}{20} = 4 \text{ M}\Omega$$

$$R_{L6} = r_{o6} + (1 + \beta_n)(R_1 \| r_{e7})$$

$$r_{e7} = \frac{(120)(0.026)}{0.2} = 15.6 \text{ k}\Omega$$

$$I_{C6} = \frac{V_{BE(on)}}{R_1} = \frac{0.6}{20} = 0.030 \text{ mA}$$

$$r_{o6} = \frac{(120)(0.026)}{0.030} = 104 \text{ k}\Omega$$

Then

$$R_{L6} = 104 + (121)[20 \| 15.6] \Rightarrow 1.16 \text{ M}\Omega$$

Then

$$A_d = 769(4 \| 4 \| 1.16) \Rightarrow A_d = 565$$

Now

$$V_o = -I_{e7}r_{o7} = -(\beta_n I_{b7})r_{o7} = -\beta_n I_{e7} \left( \frac{R_1}{R_1 + r_{e7}} \right) I_{e6}$$

$$= -\beta_n(1 + \beta_n)r_{o7} \left( \frac{R_1}{R_1 + r_{e7}} \right) I_{b6} \text{ and } I_{b6} = \frac{V_{o1}}{R_{L6}}$$

Then

$$A_{v2} = \frac{V_o}{V_{o1}} = \frac{-\beta_n(1 + \beta_n)r_{o7} \left( \frac{R_1}{R_1 + r_{e7}} \right)}{R_{L6}}$$

$$r_{e7} = \frac{V_A}{I_{C7}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

So

$$A_{v2} = \frac{-(120)(121)(400) \left( \frac{20}{20 + 15.6} \right)}{1160} \Rightarrow$$

$$A_{v2} = -2813$$

$$\text{Overall gain} = A_d \cdot A_{v2} = (565)(-2813) \Rightarrow$$

$$A = -1.59 \times 10^6$$

$$(b) R_{e4} = 2r_{e1} \text{ and } r_{e1} = \frac{(80)(0.026)}{0.020} = 104 \text{ k}\Omega$$

$$R_{e4} = 208 \text{ k}\Omega$$

$$(c) f_{PD} = \frac{1}{2\pi R_{eq} C_M} \text{ and}$$

$$C_M = (10)(1 + 2813) = 28,140 \text{ pF}$$

$$R_{eq} = r_{o2} \| r_{o4} \| R_{L6} = 4 \| 4 \| 1.16 = 0.734 \text{ M}\Omega$$

$$f_{PD} = \frac{1}{2\pi(0.734 \times 10^6)(28,140 \times 10^{-12})} = 7.71 \text{ Hz}$$

$$\text{Gain-Bandwidth Product} = (7.71)(1.59 \times 10^6) \Rightarrow$$

$$12.3 \text{ MHz}$$

13.4

- $Q_3$  acts as the protection device.
- Same as part (a).

13.5

If we assume  $V_{BE(on)} = 0.7 \text{ V}$ , then

$$V_{in} = 0.7 + 0.7 + 50 + 5$$

So breakdown voltage  $\approx 56.4 \text{ V}$ .

13.6

$$(a) I_{REF} = \frac{15 - 0.6 - 0.6 - (-15)}{R_5} = 0.50$$

$$\Rightarrow R_5 = 57.6 \text{ k}\Omega$$

$$I_{C10}R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$R_4 = \frac{0.026}{0.030} \ln \left( \frac{0.50}{0.030} \right) \Rightarrow R_4 = 2.44 \text{ k}\Omega$$

$$(b) I_{REF} = \frac{5 - 0.6 - 0.6 - (-5)}{57.6} \Rightarrow I_{REF} = 0.153 \text{ mA}$$

$$I_{C10}(2.44) = (0.026) \ln \left( \frac{0.153}{I_{C10}} \right)$$

$$\text{By trial and error, } I_{C10} \approx 21.1 \mu\text{A}$$

13.7

$$(a) I_{REF} \approx 0.50 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) = (0.026) \ln \left( \frac{0.50 \times 10^{-3}}{10^{-14}} \right) \Rightarrow$$

$$V_{BE11} = 0.641 \text{ V} = V_{BE12}$$

Then

$$R_5 = \frac{15 - 0.641 - 0.641 - (-15)}{0.50} \Rightarrow R_5 = 57.4 \text{ k}\Omega$$

$$R_4 = \frac{0.026}{0.030} \ln \left( \frac{0.50}{0.030} \right) \Rightarrow R_4 = 2.44 \text{ k}\Omega$$

$$V_{BE10} = 0.026 \ln \left( \frac{0.030 \times 10^{-3}}{10^{-14}} \right) \Rightarrow V_{BE10} = 0.567 \text{ V}$$

(b) From Problem 13.6,  $I_{REF} \cong 0.15 \text{ mA}$

$$V_{BE11} = V_{BE12} = 0.026 \ln \left( \frac{0.15 \times 10^{-3}}{10^{-14}} \right) = 0.609 \text{ V}$$

$$\text{Then } I_{REF} = \frac{5 - 0.609 - 0.609 - (-5)}{57.4} \Rightarrow$$

$$I_{REF} = 0.153 \text{ mA}$$

Then  $I_{C10} \cong 21.1 \mu\text{A}$  from Problem 13.6

13.8

$$\text{a. } I_{REF} = \frac{5 - 0.6 - 0.6 - (-5)}{40}$$

$$\Rightarrow I_{REF} = 0.22 \text{ mA}$$

$$I_{C10} R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.22}{I_{C10}} \right)$$

By trial and error;

$$I_{C10} \cong 14.2 \mu\text{A}$$

$$I_{C8} \cong \frac{I_{C10}}{2} \Rightarrow I_{C8} = 7.10 \mu\text{A}$$

$$I_{C17} = 0.75 I_{REF} \Rightarrow I_{C17} = 0.165 \text{ mA}$$

$$I_{C13A} = 0.25 I_{REF} \Rightarrow I_{C13A} = 0.055 \text{ mA}$$

b. Using Example 13.4

$$r_{\pi 17} = 31.5 \text{ k}\Omega$$

$$R'_E = 50 \parallel [31.5 + (201)(0.1)] = 50 \parallel 51.6$$

$$= 25.4 \text{ k}\Omega$$

$$r_{\pi 16} = \frac{\beta_n V_T}{I_{C16}} \text{ and}$$

$$I_{C16} = \frac{0.165}{200} + \frac{(0.165)(0.1) + 0.6}{50} = 0.0132 \text{ mA}$$

$$r_{\pi 16} = 394 \text{ k}\Omega$$

Then

$$R_{12} = 394 + (201)(25.4) \Rightarrow 5.5 \text{ M}\Omega$$

$$r_{\pi 6} = 732 \text{ k}\Omega$$

$$g_{m6} = \frac{0.00710}{0.026} = 0.273 \text{ mA/V}$$

$$r_{o6} = \frac{50}{0.0071} = 7.04 \text{ M}\Omega$$

Then

$$R_{ac11} = 7.04[1 + (0.273)(1 \parallel 732)] = 8.96 \text{ M}\Omega$$

$$r_{o4} = \frac{50}{0.0071} = 7.04 \text{ M}\Omega$$

Then

$$A_d = - \left( \frac{7.1}{0.026} \right) (7.04 \parallel 8.96 \parallel 5.5)$$

or

$$A_d = -627 \text{ Gain of differential amp stage}$$

Using Example 13.5, and neglecting the input resistance to the output stage:

$$R_{ac12} = \frac{V_A}{I_{C13B}} = \frac{50}{0.165} = 303 \text{ k}\Omega$$

$$A_{v2} = \frac{-(200)(201)(50)(303)}{(5500)[50 + 31.5 + (201)(0.1)]}$$

or

$$A_{v2} = -1090 \text{ Gain of second stage}$$

13.9

$$I_{C10} = 19 \mu\text{A}$$

From Equation (13.6)

$$I_{C10} = 2I \left[ \frac{\beta_P^2 + 2\beta_P + 2}{\beta_P^2 + 3\beta_P + 2} \right] = 2I \left[ \frac{(10)^2 + 2(10) + 2}{(10)^2 + 3(10) + 2} \right]$$

$$= 2I \left[ \frac{122}{132} \right]$$

So

$$2I = (19) \left( \frac{132}{122} \right) = 20.56 \mu\text{A}$$

$$I_{C2} = I = 10.28 \mu\text{A}$$

$$I_{C9} = \frac{2I}{\left(1 + \frac{2}{\beta_P}\right)} = \frac{20.56}{\left(1 + \frac{2}{10}\right)} \Rightarrow I_{C9} = 17.13 \mu\text{A}$$

$$I_{B9} = \frac{I_{C9}}{\beta_P} = \frac{17.13}{10} \Rightarrow I_{B9} = 1.713 \mu\text{A}$$

$$I_{B4} = \frac{I}{(1 + \beta_P)} = \frac{10.28}{11} \Rightarrow I_{B4} = 0.9345 \mu\text{A}$$

$$I_{C4} = I \left( \frac{\beta_P}{1 + \beta_P} \right) = (10.28) \left( \frac{10}{11} \right)$$

$$\Rightarrow I_{C4} = 9.345 \mu\text{A}$$

13.10

$$V_{B5} - V^- = V_{BE(on)} + I_{C5}(1)$$

$$= 0.6 + (0.0095)(1) = 0.6095$$

$$I_{C7} = \frac{0.6095}{50} \Rightarrow I_{C7} = 12.2 \mu\text{A}$$

$$I_{C8} = I_{C9} = 19 \mu\text{A}$$

$$I_{REF} = 0.72 \text{ mA}$$

$$I_{E13} = I_{REF} = 0.72 \text{ mA}$$

$$I_{C14} = 138 \mu\text{A}$$

$$\begin{aligned} \text{Power} &= (V^+ - V^-)[I_{C7} + I_{C8} + I_{C9} \\ &\quad + I_{REF} + I_{E13} + I_{C14}] \\ &= 30[0.0122 + 0.019 + 0.019 \\ &\quad + 0.72 + 0.72 + 0.138] \\ &\Rightarrow \text{Power} = 48.8 \text{ mW} \end{aligned}$$

Current supplied by  $V^+$  and  $V^-$

$$\begin{aligned} &= I_{C7} + I_{C8} + I_{C9} + I_{REF} + I_{E13} + I_{C14} \\ &= 1.63 \text{ mA} \end{aligned}$$

13.11

$$(a) v_{cm}(\min) = -15 + 0.6 + 0.6 + 0.6 + 0.6 = -12.6 \text{ V}$$

$$v_{cm}(\max) = +15 - 0.6 = 14.4 \text{ V}$$

$$\text{So } -12.6 \leq v_{cm} \leq 14.4 \text{ V}$$

$$(b) v_{cm}(\min) = -5 + 4(0.6) = -2.6 \text{ V}$$

$$v_{cm}(\max) = 5 - 0.6 = 4.4 \text{ V}$$

$$\text{So } -2.6 \leq v_{cm} \leq 4.4 \text{ V}$$

13.12

If  $v_0 = V^- = -15 \text{ V}$ , the base voltage of  $Q_{14}$  is pulled low, and  $Q_{18}$  and  $Q_{19}$  are effectively cut off. As a first approximation

$$I_{C14} = \frac{0.6}{0.027} = 22.2 \text{ mA}$$

$$I_{B14} = \frac{22.2}{200} = 0.111 \text{ mA}$$

Then

$$I_{C15} = I_{C13A} - I_{B14} = 0.18 - 0.111 = 0.069 \text{ mA}$$

Now

$$\begin{aligned} V_{BE15} &= V_T \ln \left( \frac{I_{C15}}{I_S} \right) \\ &= (0.026) \ln \left( \frac{0.069 \times 10^{-3}}{10^{-14}} \right) \\ &= 0.589 \text{ V} \end{aligned}$$

As a second approximation

$$I_{C14} = \frac{0.589}{0.027} \Rightarrow I_{C14} = 21.8 \text{ mA}$$

$$I_{B14} = \frac{21.8}{200} = 0.109 \text{ mA}$$

and

$$I_{C15} = 0.18 - 0.109 \Rightarrow I_{C15} = 0.071 \text{ mA}$$

13.13

a. Neglecting base currents:

$$I_D = I_{BIAS}$$

Then

$$\begin{aligned} V_{BB} &= 2V_D = 2V_T \ln \left( \frac{I_D}{I_S} \right) \\ &= 2(0.026) \ln \left( \frac{0.25 \times 10^{-3}}{2 \times 10^{-14}} \right) \end{aligned}$$

or

$$\begin{aligned} V_{BB} &= 1.2089 \text{ V} \\ I_{CN} = I_{CP} &= I_S \exp \left( \frac{V_{BB}/2}{V_T} \right) \\ &= 5 \times 10^{-14} \exp \left( \frac{1.2089}{2(0.026)} \right) \end{aligned}$$

So

$$I_{CN} = I_{CP} = 0.625 \text{ mA}$$

b. For  $v_I = 5 \text{ V}$ ,  $v_O \approx 5 \text{ V}$

$$i_L = \frac{5}{4} = 1.25 \text{ mA}$$

As a first approximation

$$I_{CN} \approx i_L = 1.25 \text{ mA}$$

$$V_{BE15} = (0.026) \ln \left( \frac{1.25 \times 10^{-3}}{5 \times 10^{-14}} \right) = 0.6225 \text{ V}$$

Neglecting base currents,

$$V_{BB} = 1.2089 \text{ V}$$

$$\text{Then } V_{EBP} = 1.2089 - 0.6225 = 0.5864 \text{ V}$$

$$I_{CP} = 5 \times 10^{-14} \exp \left( \frac{0.5864}{0.026} \right) \Rightarrow I_{CP} = 0.312 \text{ mA}$$

As a second approximation,

$$I_{CN} = i_L + I_{CP} = 1.25 + 0.31 \Rightarrow I_{CN} \approx 1.56 \text{ mA}$$

$$V_{BE15} = (0.026) \ln \left( \frac{1.56 \times 10^{-3}}{5 \times 10^{-14}} \right) = 0.62826 \text{ V}$$

$$V_{EBP} = 1.2089 - 0.62826 = 0.5806 \text{ V}$$

$$I_{CP} = 5 \times 10^{-14} \exp \left( \frac{0.5806}{0.026} \right) \Rightarrow I_{CP} = 0.25 \text{ mA}$$

13.14

$$R_1 + R_2 = \frac{V_{BB}}{(0.1)I_{BIAS}} = \frac{1.157}{0.018} = 64.28 \text{ k}\Omega$$

$$\begin{aligned} V_{BE} &= V_T \ln \left( \frac{I_C}{I_S} \right) = (0.026) \ln \left( \frac{(0.9)I_{BIAS}}{I_S} \right) \\ &= (0.026) \ln \left( \frac{0.162 \times 10^{-3}}{10^{-14}} \right) \end{aligned}$$

$$V_{BE} = 0.6112 \text{ V}$$

$$V_{BE} = \left( \frac{R_2}{R_1 + R_2} \right) V_{BB}$$

$$0.6112 = \left( \frac{R_2}{64.28} \right) (1.157)$$

So

$$R_2 = 33.96 \text{ k}\Omega$$

Then

$$R_1 = 30.32 \text{ k}\Omega$$

13.15

$$(a) A_d = -g_m(r_{o4} \| r_{o6} \| R_2)$$

From example 13.4

$$g_m = \frac{9.5}{0.026} = 365 \mu\text{A/V}, \quad r_{o4} = 5.26 \text{ M}\Omega$$

Now

$$r_{o6} = r_{o4} = 5.26 \text{ M}\Omega$$

Assuming  $R_s = 0$ , we find

$$R_{i2} = r_{o16} + (1 + \beta_n)R'_s \\ = 329 + (201)(50 \| 9.63) \Rightarrow 1.95 \text{ M}\Omega$$

Then

$$A_d = -(365)(5.26 \| 5.26 \| 1.95) \Rightarrow A_d = -409$$

(b) From Equation (13.20),

$$A_{v2} = \frac{-\beta_n(1 + \beta_n)R_9(R_{o2} \| R_{i3} \| R_{o17})}{R_{i2}\{R_9 + [r_{o17} + (1 + \beta_n)R_4]\}}$$

For  $R_9 = 0$ ,  $R_{i2} = 1.95 \text{ M}\Omega$

Using the results of Example 13.5

$$A_{v2} = \frac{-200(201)(50)(92.6 \| 4050 \| 92.6)}{(1950)(50 + 9.63)} \Rightarrow$$

$$A_{v2} = -792$$

13.16

Let  $I_{C10} = 40 \mu\text{A}$ , then  $I_{C1} = I_{C2} = 20 \mu\text{A}$ . Using Example 13.5,

$$R_{i2} = 4.07 \text{ M}\Omega$$

$$r_{o6} = \frac{(200)(0.026)}{0.020} = 260 \text{ k}\Omega$$

$$g_{m6} = \frac{0.020}{0.026} = 0.769 \text{ mA/V}$$

$$r_{o6} = \frac{50}{0.02} \Rightarrow 2.5 \text{ M}\Omega$$

Then

$$R_{o4} = 2.5[1 + (0.769)(1 \| 260)] = 4.42 \text{ M}\Omega$$

$$r_{o6} = \frac{50}{0.02} \Rightarrow 2.5 \text{ M}\Omega$$

Then

$$A_d = -\left( \frac{I_{CQ}}{V_T} \right) (r_{o4} \| R_{o4} \| R_{i2}) \\ = -\left( \frac{20}{0.026} \right) (2.5 \| 4.42 \| 4.07)$$

So

$$A_d = -882$$

13.17

Now

$$R_{e14} = \frac{r_{\pi14} + R_{o1}}{1 + \beta_P} \text{ and } R_o = R_6 + R_{e14}$$

Assume series resistance of  $Q_{18}$  and  $Q_{19}$  is small. Then

$$R_{o1} = r_{o13A} \| R_{e22}$$

$$\text{where } R_{e22} = \frac{r_{\pi22} + R_{o17} \| r_{o13B}}{1 + \beta_P}$$

$$\text{and } R_{o17} = r_{o17}[1 + g_{m17}(R_8 \| r_{\pi17})]$$

Using results from Example 13.6,

$$r_{\pi17} = 9.63 \text{ k}\Omega \quad r_{\pi22} = 7.22 \text{ k}\Omega$$

$$g_{m17} = 20.8 \text{ mA/V} \quad r_{o17} = 92.6 \text{ k}\Omega$$

Then

$$R_{o17} = 92.6[1 + (20.8)(0.1 \| 9.63)] = 283 \text{ k}\Omega$$

$$r_{o13B} = \frac{50}{0.54} = 92.6 \text{ k}\Omega$$

Then

$$R_{e22} = \frac{7.22 + 283 \| 92.6}{51} = 1.51 \text{ k}\Omega$$

$$R_{o1} = r_{o13A} \| R_{e22} = 278 \| 1.51 = 1.50 \text{ k}\Omega$$

$$r_{\pi14} = \frac{(50)(0.026)}{2} = 0.65 \text{ k}\Omega$$

Then

$$R_{e14} = \frac{0.65 + 1.50}{51} = 0.0422 \text{ k}\Omega$$

or

$$R_{e14} = 42.2 \Omega$$

Then

$$R_o = 42.2 + 27 \Rightarrow R_o = 69.2 \Omega$$



13.18

$$R_{id} = 2 \left[ r_{\pi 1} + (1 + \beta_n) \left( \frac{r_{\pi 3}}{1 + \beta_P} \right) \right]$$

Assume  $\beta_n = 200$  and  $\beta_P = 10$ 

Then

$$r_{\pi 1} = \frac{(200)(0.026)}{0.0095} = 547 \text{ k}\Omega$$

$$r_{\pi 3} = \frac{(10)(0.026)}{0.0095} = 27.4 \text{ k}\Omega$$

Then

$$R_{id} = 2 \left[ 547 + \frac{(201)(27.4)}{11} \right]$$

or

$$R_{id} = 2.095 \text{ M}\Omega$$

13.19

We can write

$$\begin{aligned} A(f) &= \frac{A_0}{\left(1 + j \frac{f}{f_{PD}}\right) \left(1 + j \frac{f}{f_1}\right)} \\ &= \frac{356,796}{\left(1 + j \frac{f}{5.43}\right) \left(1 + j \frac{f}{f_1}\right)} \end{aligned}$$

Phase:

$$\phi = -\tan^{-1} \left( \frac{f}{5.43} \right) - \tan^{-1} \left( \frac{f}{f_1} \right)$$

For a phase margin =  $70^\circ$ ,  $\phi = -110^\circ$ 

So

$$-110^\circ = -\tan^{-1} \left( \frac{f}{5.43} \right) - \tan^{-1} \left( \frac{f}{f_1} \right)$$

Assuming  $f \gg 5.43$ , we have

$$\tan^{-1} \left( \frac{f}{f_1} \right) = 20^\circ \Rightarrow \frac{f}{f_1} = 0.364$$

At this frequency,  $|A(f)| = 1$ , so

$$\begin{aligned} 1 &= \frac{356,796}{\sqrt{1 + \left(\frac{f}{5.43}\right)^2} \cdot \sqrt{1 + (0.364)^2}} \\ &= \frac{335,275}{\sqrt{1 + \left(\frac{f}{5.43}\right)^2}} \end{aligned}$$

$$\text{or } \frac{f}{5.43} = 335,275 \Rightarrow f = 1.82 \text{ MHz}$$

Then, second pole at

$$f_1 = \frac{f}{0.364} \Rightarrow f_1 = 5 \text{ MHz}$$

13.20

a. Original  $g_{m1}$  and  $g_{m2}$ 

$$\begin{aligned} K_{p1} = K_{p2} &= \left( \frac{W}{L} \right) \left( \frac{\mu_p C_{ox}}{2} \right) = (12.5)(10) \\ &= 125 \mu\text{A}/V^2 \end{aligned}$$

So

$$\begin{aligned} g_{m1} = g_{m2} &= 2 \sqrt{K_{p1} \left( \frac{I_Q}{2} \right)} = 2 \sqrt{(0.125)(10)} \\ &= 0.09975 \text{ mA}/V \end{aligned}$$

If  $\left( \frac{W}{L} \right)$  is increased to 50, then

$$K_{p1} = K_{p2} = (50)(10) = 500 \mu\text{A}/V^2$$

So

$$g_{m1} = g_{m2} = 2 \sqrt{(0.5)(0.0199)} = 0.1995 \text{ mA}/V$$

b. Gain of first stage

$$A_d = g_{m1} (r_{o2} \parallel r_{o4}) = (0.1995)(5025 \parallel 5025)$$

or

$$A_d = 501$$

Voltage gain of second stage remains the same, or

$$A_{v2} = 251$$

$$\text{Then } A_v = A_d \cdot A_{v2} = (501)(251)$$

or

$$A_d = 125,751$$

13.22

$$\text{a. } K_p = (10)(20) = 200 \mu\text{A}/V^2 = 0.2 \text{ mA}/V^2$$

$$I_{REF} = I_{SET} = \frac{10 - V_{SG} - (-10)}{200}$$

$$= k_P (V_{SG} - 1.5)^2$$

$$20 - V_{SG} = (0.2)(200)(V_{SG}^2 - 3V_{SG} + 2.25)$$

$$40V_{SG}^2 - 119V_{SG} + 70 = 0$$

$$V_{SG} = \frac{119 \pm \sqrt{(119)^2 - 4(40)(70)}}{2(40)}$$

$$\Rightarrow V_{SG} = 2.17 \text{ V}$$

Then

$$I_{REF} = \frac{20 - 2.17}{200} \Rightarrow I_{REF} = 89.2 \mu\text{A}$$

 $M_1$ ,  $M_2$ ,  $M_3$  matched transistors so that

$$I_Q = I_{D1} = I_{REF} = 89.2 \mu\text{A}$$

b. Small-signal voltage gain of input stage:

$$A_d = \sqrt{2K_{p1}I_Q} \cdot (r_{o2} \| r_{o4})$$

$$r_{o2} = \frac{1}{\lambda_P I_D} = \frac{1}{(0.02) \left( \frac{89.2}{2} \right)} = 1.12 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.01) \left( \frac{89.2}{2} \right)} = 2.24 \text{ M}\Omega$$

Then

$$A_d = \sqrt{2(200)(89.2)} \cdot (1.12 \| 2.24)$$

or

$$\underline{A_d = 141}$$

Small-signal voltage gain of second stage:

$$A_{v2} = g_{m7}(r_{o7} \| r_{o8})$$

$$K_{n7} = (20)(20) = 400 \mu\text{A}/\text{V}^2$$

So

$$g_{m7} = 2\sqrt{K_{n7}I_{D7}} = 2\sqrt{(0.4)(0.0892)}$$

$$= 0.378 \text{ mA/V}$$

$$r_{o8} = \frac{1}{\lambda_P I_{D7}} = \frac{1}{(0.02)(0.0892)} = 561 \text{ k}\Omega$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{(0.01)(0.0892)} = 1121 \text{ k}\Omega$$

So

$$A_{v2} = (0.378)(1121 \| 561) \Rightarrow \underline{A_{v2} = 141}$$

Then overall voltage gain

$$A_v = A_d \cdot A_{v2} = (141)(141) \Rightarrow \underline{A_v = 19,881}$$

13.23

Small-signal voltage gain of input stage:

$$A_d = \sqrt{2K_{p1}I_Q} \cdot (r_{o2} \| r_{o4})$$

$$K_{p1} = (10)(10) = 100 \mu\text{A}/\text{V}^2$$

$$r_{o2} = \frac{1}{\lambda_P \left( \frac{I_Q}{2} \right)} = \frac{1}{(0.01) \left( \frac{0.2}{2} \right)} = 1000 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n \left( \frac{I_Q}{2} \right)} = \frac{1}{(0.005) \left( \frac{0.2}{2} \right)} = 2000 \text{ k}\Omega$$

Then

$$A_d = \sqrt{2(0.1)(0.2)} \cdot (1000 \| 2000)$$

or

$$\underline{A_d = 133}$$

Small-signal voltage gain of second stage:

$$A_{v2} = g_{m7}(r_{o7} \| r_{o8})$$

$$K_{n7} = (20)(20) = 400 \mu\text{A}/\text{V}^2$$

So

$$g_{m7} = 2\sqrt{K_{n7}I_{D7}} = 2\sqrt{(0.4)(0.2)}$$

$$= 0.566 \text{ mA/V}$$

$$r_{o8} = \frac{1}{\lambda_P I_{D7}} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{(0.005)(0.2)} = 1000 \text{ k}\Omega$$

So

$$A_{v2} = (0.566)(1000 \| 500) \Rightarrow \underline{A_{v2} = 189}$$

Then overall voltage gain is

$$A_v = A_d \cdot A_{v2} = (133)(189) \Rightarrow \underline{A_v = 25,137}$$

13.24

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

where  $R_{eq} = r_{o4} \| r_{o2}$  and  $C_i = C_1(1 + |A_{v2}|)$

We can find that

$$A_{v2} = 251 \text{ and } r_{o4} = r_{o2} = 5.025 \text{ M}\Omega$$

Now

$$R_{eq} = 5.025 \| 5.025 = 2.51 \text{ M}\Omega$$

and

$$C_i = 12(1 + 251) = 3024 \text{ pF}$$

So

$$f_{PD} = \frac{1}{2\pi(2.51 \times 10^6)(3024 \times 10^{-12})}$$

or

$$\underline{f_{PD} = 21.0 \text{ Hz}}$$

13.25

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

where  $R_{eq} = r_{o4} \| r_{o2}$

From Problem 13.22,

$$r_{o2} = 1.12 \text{ M}\Omega, r_{o4} = 2.24 \text{ M}\Omega \text{ and } A_{v2} = 141$$

So

$$\beta = \frac{1}{2\pi(1.12)(2.24) \times 10^8 \times C_1}$$

or

$$C_1 = 2.66 \times 10^{-8} = C_1(1 + |A_{v2}|) = C_1(142)$$

or

$$C_1 = 188 \text{ pF}$$

13.26

$$R_0 = r_{o7} \parallel r_{o8}$$

We can find that

$$r_{o7} = r_{o8} = 2.52 \text{ M}\Omega$$

Then


$$R_0 = 2.52 \parallel 2.52$$

or

$$R_0 = 1.26 \text{ M}\Omega$$

13.27

a.

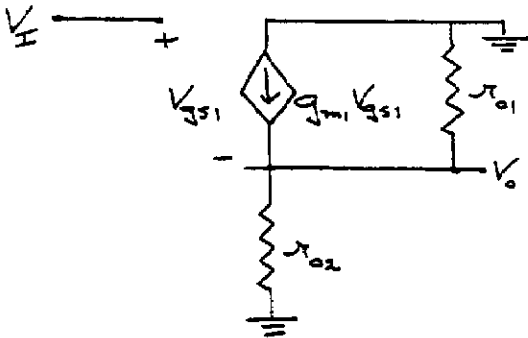

$$V_O = (g_{m1}V_{gs1})(r_{o1} \parallel r_{o2})$$

$$V_I = V_{gs1} + V_O$$

$$\text{Then } V_O = g_{m1}(r_{o1} \parallel r_{o2})(V_I - V_O)$$

or

$$A_v = \frac{g_{m1}(r_{o1} \parallel r_{o2})}{1 + g_{m1}(r_{o1} \parallel r_{o2})}$$

$$\text{b. } I_X + g_{m1}V_{gs1} = \frac{V_X}{r_{o2}} + \frac{V_X}{r_{o1}} \text{ and } V_{gs1} = -V_X$$

$$R_0 = \frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o2}$$

13.28

$$\text{(a) } A_v = g_{m1}(R_{o6} \parallel R_{o4})$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.025)} \Rightarrow 224 \mu\text{A/V}$$

$$g_{m1} = g_{m6}$$

$$g_{m6} = 2\sqrt{(0.5)(0.025)} \Rightarrow 224 \mu\text{A/V}$$

$$r_{o1} = r_{o6} = r_{o4} = r_{o10} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(25)} = 2.67 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda I_{D4}} = \frac{1}{(0.015)(50)} \Rightarrow 1.33 \text{ M}\Omega$$

Now

$$R_{o4} = g_{m6}(r_{o4}r_{o10}) = (224)(2.67)(2.67) = 1597 \text{ M}\Omega$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \parallel r_{o1}) = (224)(2.67)(2.67 \parallel 1.33) \Rightarrow$$

$$R_{o6} = 531 \text{ M}\Omega$$

Then

$$A_v = (224)(531 \parallel 1597) \Rightarrow A_v = 89,264$$

$$\text{(b) } R_o = R_{o6} \parallel R_{o4} = 531 \parallel 1597 \Rightarrow R_o = 398 \text{ M}\Omega$$

$$\text{(c) } f_{PD} = \frac{1}{2\pi R_o C_L} = \frac{1}{2\pi(398 \times 10^6)(5 \times 10^{-12})} \Rightarrow$$

$$f_{PD} = 80 \text{ Hz}$$

$$GBW = (89,264)(80) \Rightarrow GBW = 7.14 \text{ MHz}$$

13.29

$$\text{(a) } r_{o1} = r_{o4} = r_{o10} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.02)(25)} = 2 \text{ M}\Omega$$

$$r_{o6} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.015)(25)} = 2.67 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(50)} = 1.33 \text{ M}\Omega$$

$$g_{m1} = 2\sqrt{\left(\frac{35}{2}\right)\left(\frac{W}{L}\right)_1(25)} = 418\sqrt{\left(\frac{W}{L}\right)_1} = g_{m6}$$

$$g_{m6} = 2\sqrt{\left(\frac{80}{2}\right)\left(\frac{W}{L}\right)_6(25)} = 632\sqrt{\left(\frac{W}{L}\right)_6}$$

$$R_o = R_{o6} \parallel R_{o4} = [g_{m6}(r_{o6})(r_{o4} \parallel r_{o1})] \parallel [g_{m6}(r_{o6}r_{o10})]$$

$$\text{Define } X_1 = \sqrt{\left(\frac{W}{L}\right)_1} \text{ and } X_6 = \sqrt{\left(\frac{W}{L}\right)_6}$$

$$\text{Then } R_o = [632X_6(2.67)(1.33 \parallel 2)] \parallel [418X_1(2)(2)]$$

$$= 134.8X_6 \parallel 167.2X_1 = \frac{22,539X_1X_6}{134.8X_6 + 167.2X_1}$$

$$A_v = g_{m1}R_o = (418X_1)\left(\frac{22,539X_1X_6}{134.8X_6 + 167.2X_1}\right)$$

$$= 10,000$$

$$\text{Now } X_6 = \sqrt{\left(\frac{W}{L}\right)_6} = \sqrt{\frac{1}{2.2}\left(\frac{W}{L}\right)_1} = 0.674X_1$$

We then find

$$X_1^2 = \left(\frac{W}{L}\right)_1 = 4.06 = \left(\frac{W}{L}\right)_1$$

and

$$\left(\frac{W}{L}\right)_n = 1.85$$

13.30

Let  $V^+ = 5V$ ,  $V^- = -5V$

$$P = I_T(10) = 3 \Rightarrow I_T = 0.3 \text{ mA}$$

$$\Rightarrow I_{REF} = 0.1 \text{ mA} = 100 \mu\text{A}$$

$$r_{o1} = r_{o2} = r_{o10} = \frac{1}{(0.02)(50)} = 1 \text{ M}\Omega$$

$$r_{o2} = \frac{1}{(0.015)(50)} = 1.33 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{(0.015)(100)} = 0.667 \text{ M}\Omega$$

$$g_{m1} = 2\sqrt{\left(\frac{35}{2}\right)\left(\frac{W}{L}\right)_1(50)} = 59.2 X_1 = g_{m4}$$

$$\text{where } X_1 = \sqrt{\left(\frac{W}{L}\right)_1}$$

Assume all width-to-length ratios are the same.

$$g_{m6} = 2\sqrt{\left(\frac{80}{2}\right)\left(\frac{W}{L}\right)(50)} = 89.4 X_1$$

Now

$$\begin{aligned} R_o &= R_{o2} \| R_{o4} = [g_{m6}(r_{o2})(r_{o4} \| r_{o1})] \| [g_{m4}(r_{o2} r_{o10})] \\ &= [89.4 X_1 (1.33)(0.667 \| 1)] \| [59.2 X_1 (1)(1)] \\ &= [47.6 X_1] \| [59.2 X_1] = \frac{(47.6 X_1)(59.2 X_1)}{47.6 X_1 + 59.2 X_1} \end{aligned}$$

$$\text{So } R_o = 26.4 X_1$$

Now

$$A_d = g_{m1} R_o = (59.2 X_1)(26.4 X_1) = 25,000$$

$$\text{So that } X_1^2 = \frac{W}{L} = 16 \text{ for all transistors}$$

13.31

$$(a) A_d = B g_{m1}(r_{o2} \| r_{o4})$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(90)} = 0.741 \text{ M}\Omega$$

$$g_{m1} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D1}} = 2\sqrt{(500)(30)} = 245 \mu\text{A/V}$$

$$A_d = (3)(245)(0.741 \| 0.741) \Rightarrow A_d = 272$$

$$(b) R_o = r_{o2} \| r_{o4} = 0.741 \| 0.741 \Rightarrow R_o = 371 \text{ k}\Omega$$

$$(c) f_{PD} = \frac{1}{2\pi R_o C} = \frac{1}{2\pi(371 \times 10^3)(5 \times 10^{-12})} \Rightarrow f_{PD} = 85.8 \text{ kHz}$$

$$GBW = (272)(85.8 \times 10^3) \Rightarrow GBW = 23.3 \text{ MHz}$$

13.32

$$(a) r_{o2} = \frac{1}{(0.02)(2.5)(40)} = 0.5 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{(0.015)(2.5)(40)} = 0.667 \text{ M}\Omega$$

$$A_d = B g_{m1}(r_{o2} \| r_{o4})$$

$$400 = (2.5)g_{m1}(0.5 \| 0.667) \Rightarrow g_{m1} = 560 \mu\text{A/V}$$


$$g_{m1} = 560 = 2\sqrt{\left(\frac{80}{2}\right)\left(\frac{W}{L}\right)(40)} \Rightarrow \left(\frac{W}{L}\right) = 49$$

Assume all  $(W/L)$  ratios are the same except for

$$M_5 \text{ and } M_6. \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = 122.5$$

(b) Assume the bias voltages are

$$V^+ = 5V, V^- = -5V$$

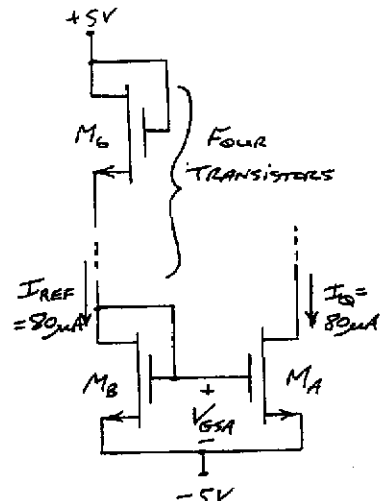

$$\text{Assume } \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_6 = 49$$

$$I_Q = \left(\frac{80}{2}\right)(49)(V_{GS4} - 0.5)^2 = 80 \Rightarrow V_{GS4} = 0.702 \text{ V}$$

Then

$$I_{REF} = 80 = \left(\frac{80}{2}\right)\left(\frac{W}{L}\right)_C (V_{GS4} - 0.5)^2$$

$$V_{asc} = \frac{10 - 0.702}{4} = 2.325V$$

$$80 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_c (2.325 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_c = 0.60$$

$$(c) f_{3-\omega} = \frac{1}{2\pi R_o C} \quad R_o = 0.5 \parallel 0.667 = 0.286 \text{ M}\Omega$$

$$f_{3-\text{dB}} = \frac{1}{2\pi(286 \times 10^3)(3 \times 10^{-12})} = 185 \text{ kHz}$$

$$GBW = (400)(185 \times 10^3) \Rightarrow 74 \text{ MHz}$$

(a) From previous results, we can write

$$R_{o10} = g_{m10}(r_{o10}r_{o6})$$

$$R_{ol2} = g_{ml2}(r_{ol2}, r_{ol1})$$

$$A_d = Bg_{ml}(R_{o10}||R_{o12})$$

$$r_{\text{alo}} = r_{\text{oc}} = \frac{1}{\lambda_p B(I_g/2)} = \frac{1}{(0.02)(2.5)(40)} = 0.5 \text{ M}\Omega$$

$$r_{o12} = r_{os} = \frac{1}{\lambda_n B(I_o/2)} = \frac{1}{(0.015)(2.5)(40)} = 0.667 \text{ M}\Omega$$

Let  $\left(\frac{W}{L}\right) = X^2$

$$g_{10} = 2 \sqrt{\left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_{10} (I_{DQ10})} = 2 \sqrt{\left(\frac{35}{2}\right) X^2 (2.5)(40)} = 83.67 X$$

$$g_{m12} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_{12} (I_{DQ12})} = 2\sqrt{\left(\frac{80}{2}\right)X^2(25)(40)} \\ = 1265X$$


$$g_m = 2\sqrt{\left(\frac{80}{2}\right)X^2(40)} = 80X$$

$$R_{o10} = (83.67 X)(0.5)(0.5) = 20.9 X \text{ } M\Omega$$

$$R_{eq} = (126.5X)(0.667)(0.667) = 56.3X \text{ M}\Omega$$

$$20,000 = (2.5)(80X)[20.9X + 56.3X]$$

$$= 200X \left[ \frac{(20.9X)(56.3X)}{20.9X + 56.3X} \right] = 3048X^2$$
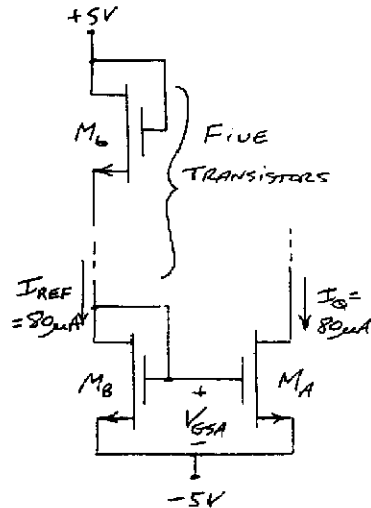
$$X^2 = 656 = \left(\frac{W}{L}\right)$$
$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = (2.5)(6.56) = 16.4$$


Assume  $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 6.56$

$$I_Q = 80 = \left(\frac{80}{2}\right)(6.56)(V_{GS1} - 0.5)^2 \Rightarrow$$

$$V_{GS4} = 1.052 V$$

$$V_{asc} = \frac{10 - 1.052}{5} = 1.79 V$$
$$I_{REF} = 80 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_c (1.79 - 0.5)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right)_c = 1.20$$

$$(c) f_{3-\omega} = \frac{1}{2\pi R_o C} \quad \text{where } R_o = R_{o10} \| R_{o12}$$

$$R_{\text{in}} = 20.9\sqrt{656} = 53.5 \text{ M}\Omega$$

$$R_{in} = 56.3\sqrt{6.56} = 144 \text{ M}\Omega$$

$$R_L = 53.5 \parallel 144 = 39 \text{ M}\Omega$$

$$f_{3-\text{dB}} = \frac{1}{2\pi(39 \times 10^6)(3 \times 10^{-12})} = 136 \text{ kHz}$$

$$GBW = (20,000)(1.36 \times 10^3) \Rightarrow GBW = 27.2 \text{ MHz}$$

13.34

$$A_d = g_m(M_1) \cdot [r_{o2}(M_1) \| r_{o2}(Q_2)]$$

$$g_m(M_1) = 2 \sqrt{\left(\frac{40}{2}\right)(25)(100)} = 447 \mu A/V$$

$$r_{o2}(M_1) = \frac{1}{\lambda_{DQ}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$r_{o2}(Q_2) = \frac{V_A}{I_{CQ}} = \frac{120}{0.1} = 1200 \text{ k}\Omega$$

Then

$$A_d = 447(0.5 \| 1.2) \Rightarrow \underline{A_d = 158}$$

13.35

$$A_d = g_m(M_1) \cdot [r_{o2}(M_1) \| r_{o2}(Q_2)]$$

$$g_m(M_1) = 2 \sqrt{\left(\frac{80}{2}\right)(25)(100)} = 632 \mu A/V$$

$$r_{o2}(M_1) = \frac{1}{\lambda_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$r_{o2}(Q_2) = \frac{V_A}{I_{CQ}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$A_d = (632)(0.667 \| 0.80) \Rightarrow \underline{A_d = 230}$$

13.36

$$I_{REF} = 200 \mu A \quad K_n = K_p = 0.5 \text{ mA/V}^2$$

$$\lambda_n = \lambda_p = 0.015 \text{ V}^{-1}$$

$$A_d = g_{m1}(R_{o6} \| R_{o4})$$

where

$$R_{o4} = g_{m4}(r_{o4} r_{o10})$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \| r_{o1})$$

Now

$$g_{m1} = 2\sqrt{K_n I_{D1}} = 2\sqrt{(0.5)(0.1)} = 0.447 \text{ mA/V}$$

$$r_{o4} = \frac{1}{\lambda_p I_{D4}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$r_{o10} = \frac{1}{\lambda_p I_{D4}} = 667 \text{ k}\Omega$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$r_{o6} = \frac{V_A}{I_{C6}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(0.2)} = 333 \text{ k}\Omega$$

$$r_{o1} = \frac{1}{\lambda_p I_{D1}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$g_{m1} = 2\sqrt{K_n I_{D1}} = 2\sqrt{(0.5)(0.1)} = 0.447 \text{ mA/V}$$

So

$$R_{o4} = (0.447)(667)(667) \Rightarrow 198.9 \text{ M}\Omega$$

$$R_{o6} = (3.846)(800)(333 \| 667) \Rightarrow 683.4 \text{ M}\Omega$$

Then

$$A_d = 447(198.9 \| 683.4) \Rightarrow \underline{A_d = 68,865}$$

13.37

Assume biased at  $V^+ = 10 \text{ V}$ ,  $V^- = -10 \text{ V}$ 

$$P = 3I_{REF}(20) = 10 \Rightarrow I_{REF} = 167 \mu A$$

$$A_d = g_{m1}(R_{o6} \| R_{o4}) = 25,000$$

$$k'_n = 80 \mu A/V^2, k'_p = 35 \mu A/V^2$$

$$\lambda_n = 0.015 \text{ V}^{-1}, \lambda_p = 0.02 \text{ V}^{-1}$$

$$\text{Assume } \left(\frac{W}{L}\right)_p = 2.2 \left(\frac{W}{L}\right)_n$$

$$R_{o4} = g_{m4}(r_{o4} r_{o10})$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \| r_{o1})$$

$$r_{o4} = \frac{1}{\lambda_p I_{D4}} = \frac{1}{(0.02)(83.3)} = 0.60 \text{ M}\Omega$$

$$r_{o10} = \frac{1}{\lambda_p I_{D4}} = 0.60 \text{ M}\Omega$$

$$g_{m1} = 2 \sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_n I_{D1}} = 2 \sqrt{\left(\frac{35}{2}\right) (2.2) X^2 (83.3)} = 113.3 X$$

$$\text{where } X^2 = \left(\frac{W}{L}\right)_n$$

$$r_{o6} = \frac{V_A}{I_{C6}} = \frac{80}{83.3} = 0.960 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(167)} = 0.40 \text{ M}\Omega$$

$$r_{o1} = \frac{1}{\lambda_p I_{D1}} = \frac{1}{(0.02)(83.3)} = 0.60 \text{ M}\Omega$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{83.3}{0.026} = 3204 \mu A/V$$

$$g_{m1} = 2 \sqrt{\left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_p I_{D1}} = 2 \sqrt{\left(\frac{35}{2}\right) (2.2) X^2 (83.3)} = 113.3 X$$

Now

$$R_{o6} = (3204)(0.960)[0.40 \| 0.60] = 738 \text{ M}\Omega$$

$$R_{o4} = (113.3 X)(0.60)(0.60) = 40.8 X \text{ M}\Omega$$

Then

$$A_d = 25,000 = (113.3 X)[738 \| 40.8 X] \\ = (113.3 X) \left[ \frac{30,110 X}{738 + 40.8 X} \right]$$

which yields  $X = 2.48$ 

or

$$X^2 = 6.16 = \left(\frac{W}{L}\right)_n$$

and

$$\left(\frac{W}{L}\right)_p = (2.2)(6.16) = 12.3$$

13.38

For  $v_{cm}(\max)$ , assume  $V_{CB}(Q_5) = 0$ . Then

$$V_S = 15 - 0.6 - 0.6 = 13.8 \text{ V}$$

$$I_{D9} = I_{D10} = \frac{0.236}{2} = 0.118 \text{ mA}$$

Using parameters given in Example 13.11

$$V_{SD} = \sqrt{\frac{I_{D9}}{K_p}} - V_{TP} = \sqrt{\frac{0.118}{0.20}} + 1.4 = 2.17 \text{ V}$$

Then

$$v_{cm}(\max) = 13.8 - 2.17 \Rightarrow v_{cm}(\max) = 11.6 \text{ V}$$

For

 $v_{cm}(\min)$ , assume

$$V_{SD}(M_2) = V_{SD}(\text{sat}) = V_{SD} + V_{TP} \\ = 2.17 - 1.4 = 0.77 \text{ V}$$

Now

$$V_{D10} = I_{D10}(0.5) + 0.6 + I_{D10}(0.5) - 15 \\ = 0.118 + 0.6 - 15 \Rightarrow V_{D10} = -14.28 \text{ V}$$

Then

$$v_{cm}(\min) = -14.28 + V_{SD}(\text{sat}) - V_{SG} \\ = -14.28 + 0.77 - 2.17 = -15.68 \text{ V}$$

Then, common-mode voltage range

$$\underline{-15.68 \leq v_{cm} \leq 11.6}$$

Or, assuming the input is limited to  $\pm 15 \text{ V}$ , then

$$\underline{-15 \leq v_{cm} \leq 11.6 \text{ V}}$$

13.39

For  $I_1 = I_2 = 300 \mu\text{A}$ ,

$$V_{SG} = V_{BE} + (0.3)(8) = 0.6 + 2.4 = 3.0 \text{ V}$$

Then

$$I_1 = K_p(V_{SD} + V_{TP})^2 \\ 0.3 = K_p(3 - 1.4)^2 \\ \Rightarrow K_p = 0.117 \text{ mA/V}^2$$

13.40

For  $V_{CB} = 0$  for both  $Q_6$  and  $Q_7$ , then

$$V_S = 0.6 + 0.6 + V_{SG} + (-V_S)$$

$$\text{So } 2V_S = 1.2 + V_{SG}$$

Now

$$0.6 + I_2 R_1 = V_{SD} = \sqrt{\frac{I_1}{K_p}} + V_{TP} \text{ and } I_1 = I_2$$

$$\text{Also } I_1 = I_2 = K_p(V_{SD} + V_{TP})^2 \text{ so}$$

$$0.6 + (0.25)(8)(V_{SG} - 1.4)^2 = V_{SG}$$

$$0.6 + 2(V_{SG}^2 - 2.8V_{SG} + 1.96) = V_{SG}$$

$$2V_{SG}^2 - 6.6V_{SG} + 4.52 = 0$$

$$V_{SG} = \frac{6.6 \pm \sqrt{(6.6)^2 - 4(2)(4.52)}}{2(2)} = 2.33 \text{ V}$$

$$\text{Then } 2V_S = 1.2 + 2.33 = 3.53 \text{ and}$$

$$\underline{V_S = 1.765 \text{ V}}$$

13.41

$$I_{C3} = I_{C4} = 300 \mu\text{A}$$

Using the parameters from Examples 13.12 and 13.13, we have

$$R_{12} = r_{\pi 12} = \frac{\beta_n V_T}{I_{C12}} = \frac{(200)(0.026)}{0.3} = 17.3 \text{ k}\Omega$$

$$A_d = \sqrt{2K_n I_{D5}} \cdot (R_{12}) = \sqrt{2(0.6)(0.3)} \cdot (17.3)$$

or

$$\underline{A_d = 10.38}$$

Now

$$g_{m13} = \frac{I_{C13}}{V_T} = \frac{0.3}{0.026} = 11.5 \text{ mA/V}$$

$$r_{O13} = \frac{V_A}{I_{C13}} = \frac{50}{0.3} = 167 \text{ k}\Omega$$

Then

$$|A_{v2}| = g_{m13} \cdot r_{O13} = (11.5)(167)$$

or

$$\underline{|A_{v2}| = 1917}$$

Overall gain:

$$\underline{|A_v| = (10.38)(1917) = 19,895}$$

13.42

Assuming the resistances looking into  $Q_4$  and into the output stage are very large, we have

$$|A_{v2}| = \frac{\beta R_{O13}}{r_{\pi 13} + (1 + \beta) R_{E13}}$$

$$\text{where } R_{O13} = r_{O13} [1 + g_{m13} (R_{E13} || r_{\pi 13})]$$

$$I_{C13} = 300 \mu\text{A}, r_{o13} = \frac{50}{0.3} = 167 \text{ k}\Omega$$

$$g_{m13} = \frac{0.3}{0.026} = 11.5 \text{ mA/V}$$

$$r_{\pi13} = \frac{(200)(0.026)}{0.3} = 17.3 \text{ k}\Omega$$

So

$$R_{o13} = (167)[1 + (11.5)(1||17.3)] \Rightarrow 1.98 \text{ M}\Omega$$

Then

$$|A_{v2}| = \frac{(200)(1980)}{17.3 + (201)(1)} = 1814$$

Now

$$C_i = C_1(1 + |A_{v2}|) = 12[1 + 1814] \\ \Rightarrow C_i = 21,780 \text{ pF}$$

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

$$R_{eq} = R_{i2} || r_{o12} || r_{o10}$$

Neglecting  $R_3$ ,

$$r_{o10} = \frac{1}{\lambda I_{D10}} = \frac{1}{(0.02)(0.15)} = 333 \text{ k}\Omega$$

Neglecting  $R_5$ ,

$$r_{o12} = \frac{50}{0.15} = 333 \text{ k}\Omega$$

$$R_{i2} = r_{\pi13} + (1 + \beta)R_{E13} = 17.3 + (201)(1) \\ = 218 \text{ k}\Omega$$

Then

$$f_{PD} = \frac{1}{2\pi[218||333||333] \times 10^3 \times (21,780) \times 10^{-12}}$$

or

$$\underline{f_{PD} = 77.4 \text{ Hz}}$$

Unity-Gain Bandwidth

Gain of first stage:

$$A_d = \sqrt{2K_n I_{Q1}} \cdot (R_{i2} || r_{o12} || r_{o10}) \\ = \sqrt{2(0.6)(0.3)} \cdot (218||333||333) \\ = (0.6)(218||333||333)$$

or  $A_d = 56.6$

Overall gain:

$$A_v = (56.6)(1814) = 102,672$$

Then unity-gain bandwidth =  $(77.4)(102,672)$

$$\Rightarrow \underline{7.95 \text{ MHz}}$$

13.43

Since  $V_{GS} = 0$  in  $J_6$ ,  $I_{REF} = I_{DSS}$

$$\Rightarrow \underline{I_{DSS} = 0.8 \text{ mA}}$$

13.44

a.  $R_{i2} = r_{\pi5} + (1 + \beta)[r_{\pi6} + (1 + \beta)R_E]$

$$r_{\pi6} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$I_{C5} \approx \frac{I_{C6}}{\beta} = \frac{200 \mu\text{A}}{100} = 2 \mu\text{A}$$

So

$$r_{\pi5} = \frac{(100)(0.026)}{0.002} = 1300 \text{ k}\Omega$$

Then

$$R_{i2} = 1300 + (101)[13 + (101)(0.3)]$$

or

$$\underline{R_{i2} = 5.67 \text{ M}\Omega}$$

b.  $A_v = g_{m2}(r_{o2} || r_{o4} || R_{i2})$

$$g_{m2} = \frac{2}{V_P} \cdot \sqrt{I_D \cdot I_{DSS}} = \frac{2}{3} \cdot \sqrt{(0.1)(0.2)} \\ = 0.0943 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$r_{o4} = \frac{V_A}{I_{C4}} = \frac{5.0}{0.1} = 500 \text{ k}\Omega$$

Then

$$A_v = (0.0943)[500||500||5670]$$

or

$$\underline{A_v = 22.6}$$

13.45

a. Need  $V_{SD}(Q_E) \geq V_{SD}(\text{sat}) = V_P$   
For minimum bias  $\pm 3 \text{ V}$

Set  $V_P = 3 \text{ V}$  and  $V_{ZK} = 3 \text{ V}$

$$I_{REF2} = \frac{V_{ZK} - V_{D1}}{R_3}$$

so that  $R_3 = \frac{3 - 0.6}{0.1} \Rightarrow \underline{R_3 = 24 \text{ k}\Omega}$

Set bias in  $Q_E = I_{REF2} + I_{Z2} = 0.1 + 0.1 = 0.2 \text{ mA}$

Therefore,

$$\underline{I_{DSS} = 0.2 \text{ mA}}$$



b. Neglecting base currents

$$I_{O1} = I_{REF1} = 0.5 \text{ mA} = \frac{12 - 0.6}{R_4}$$

so that

$$\underline{R_4 = 22.8 \text{ k}\Omega}$$

13.46

a. We have

$$g_{m2} = \frac{2}{|V_P|} \cdot \sqrt{I_D \cdot I_{DSS}} = \frac{2}{4} \cdot \sqrt{(0.5)(1)} \\ = 0.354 \text{ mA/V}$$

$$r_{02} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.5)} = 100 \text{ k}\Omega$$

$$r_{04} = \frac{V_A}{I_D} = \frac{100}{0.5} = 200 \text{ k}\Omega$$

$$g_{m4} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi4} = \frac{(200)(0.026)}{0.5} = 10.4 \text{ k}\Omega$$

So

$$R_{04} = r_{04}[1 + g_{m4}(r_{\pi4} \parallel R_2)] \\ = 200[1 + (19.23)(10.4 \parallel 0.5)] \\ = 2035 \text{ k}\Omega$$

$$|A_d| = g_{m2}(r_{02} \parallel R_{04} \parallel R_L)$$

For  $R_L \rightarrow \infty$

$$|A_d| = 0.354(100 \parallel 2035) = 33.7$$

With these parameter values, gain can never reach 500.

b. Similarly for this part, gain can never reach 700.