

Chapter 1

Exercise Solutions

E1.1

$$n_i = BT^{3/2} \exp\left(-\frac{E_g}{2kT}\right)$$

GaAs:

$$n_i = (2.1 \times 10^{14})(300)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(300)}\right)$$

$$\underline{n_i = 1.8 \times 10^6 \text{ cm}^{-3}}$$

Ge:

$$n_i = (1.66 \times 10^{15})(300)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(300)}\right)$$

$$\underline{n_i = 2.40 \times 10^{13} \text{ cm}^{-3}}$$

E1.2

Si:

$$n_i = (5.23 \times 10^{15})(400)^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 4.76 \times 10^{12} \text{ cm}^{-3}}$$

GaAs:

$$n_i = (2.1 \times 10^{14})(400)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 2.44 \times 10^3 \text{ cm}^{-3}}$$

Ge:

$$n_i = (1.66 \times 10^{15})(400)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 9.06 \times 10^{14} \text{ cm}^{-3}}$$

E1.3

- a. majority carrier: $p_0 = 10^{17} \text{ cm}^{-3}$
minority carrier:

$$\underline{n_0 = \frac{n_i^2}{N_a} = \frac{(1.5 \times 10^{10})^2}{10^{17}} = 2.25 \times 10^2 \text{ cm}^{-3}}$$

- b. $n_0 = N_d - N_a = 5 \times 10^{15}$

majority carrier: $\underline{n_0 = 5 \times 10^{15} \text{ cm}^{-3}}$

minority carrier:

$$\underline{p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} = 4.5 \times 10^4 \text{ cm}^{-3}}$$

E1.4

- (a) $n_0 = 5 \times 10^{16} \text{ cm}^{-3}$, $p_0 \ll n_0$

$$\sigma \equiv e\mu_n n_0 = (1.6 \times 10^{-19})(1350)(5 \times 10^{16}) \Rightarrow$$

$$\underline{\sigma = 108 (\Omega \cdot \text{cm})^{-1}}$$

- (b) $p_0 = 5 \times 10^{16} \text{ cm}^{-3}$, $n_0 \ll p_0$

$$\sigma \equiv e\mu_p p_0 = (1.6 \times 10^{-19})(480)(5 \times 10^{16}) \Rightarrow$$

$$\underline{\sigma = 384 (\Omega \cdot \text{cm})^{-1}}$$

E1.5

- a. $n_0 = N_d = 8 \times 10^{15} \text{ cm}^{-3}$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{8 \times 10^{15}} \Rightarrow$$

$$\underline{p_0 = 2.81 \times 10^4 \text{ cm}^{-3}}$$

- b. $n = n_0 + \delta n = 8 \times 10^{15} + 0.1 \times 10^{15} \Rightarrow$

$$\underline{n = 8.1 \times 10^{15} \text{ cm}^{-3}}$$

$$p = p_0 + \delta p \Rightarrow$$

$$\underline{p \approx 10^{14} \text{ cm}^{-3}}$$

E1.6

$$J = \sigma E = (10)(15) \Rightarrow$$

$$\underline{J = 150 \text{ A/cm}^2}$$

E1.7

$$\text{a. } V_{bi} = V_T \ln\left(\frac{N_a N_d}{n_i^2}\right)$$

$$V_{bi} = (0.026) \ln\left[\frac{(10^{15})(10^{17})}{(1.5 \times 10^{10})^2}\right]$$

$$\underline{V_{bi} = 0.697 \text{ V}}$$

$$\text{b. } V_{bi} = (0.026) \ln\left[\frac{(10^{17})(10^{17})}{(1.5 \times 10^{10})^2}\right]$$

$$\underline{V_{bi} = 0.817 \text{ V}}$$

E1.8

$$V_{bi} = V_T \ln \left[\frac{N_a N_d}{n_i^2} \right] = (0.026) \ln \left[\frac{(10^6)(10^{17})}{(1.8 \times 10^6)^2} \right]$$

$$\underline{V_{bi} = 1.23 \text{ V}}$$

E1.9

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$$

$$V_{bi} = V_T \ln \left[\frac{N_a N_d}{n_i^2} \right]$$

$$= (0.026) \ln \left[\frac{(10^{17})(10^{18})}{(1.5 \times 10^{10})^2} \right] = 0.757 \text{ V}$$

$$0.8 = C_{j0} \left(1 + \frac{5}{0.757} \right)^{-1/2} = C_{j0} (7.61)^{-1/2}$$

$$= C_{j0} (0.362)$$

$$\underline{C_{j0} = 2.21 \text{ pF}}$$

E1.10

a. $I = I_S \left[\exp \left(\frac{V_D}{V_T} \right) - 1 \right]$

For $V_D = 0.5$: $I \approx 10^{-14} \exp \left(\frac{0.5}{0.026} \right)$

For $V_D = 0.6$: $I = 10^{-14} \exp \left(\frac{0.6}{0.026} \right)$

For $V_D = 0.7$: $I = 10^{-14} \exp \left(\frac{0.7}{0.026} \right)$

So we have

V_D	I
0.5	2.25 μA
0.6	0.105 mA
0.7	4.93 mA

b. 10^{-14} A both cases

E1.11

$$I = I_S \left[\exp \left(\frac{V_D}{V_T} \right) - 1 \right]$$

$$10^{-3} = (10^{-13}) \left[\exp \left(\frac{V_D}{0.026} \right) - 1 \right]$$

$$(0.026) \ln (10^{10}) \approx V_D$$

$$\underline{V_D = 0.599 \text{ V}}$$

E1.12


$$\Delta T = 100^\circ\text{C}$$

$$\Delta V_D \approx 2 \times 100 = 200 \text{ mV}$$

$$\Rightarrow V_D = 0.650 - 0.2$$

$$\Rightarrow \underline{V_D = 0.450 \text{ V}}$$

E1.13

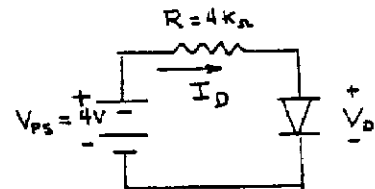

$$I_S = 10^{-12} \text{ A}$$

$$V_{PS} = I_D R + V_D \text{ and } I_D \approx I_S \exp \left(\frac{V_D}{V_T} \right)$$

So

$$4 = I_D (4) + V_D \Rightarrow I_D = (4 - V_D) / 4 \text{ mA}$$


and

$$I_D \approx I_S \exp \left(\frac{V_D}{V_T} \right) \Rightarrow I_D = 10^{-9} \exp \left(\frac{V_D}{0.026} \right) \text{ mA}$$

By trial and error:


$$I_D = 0.864 \text{ mA and } V_D = 0.535 \text{ V}$$

E1.14

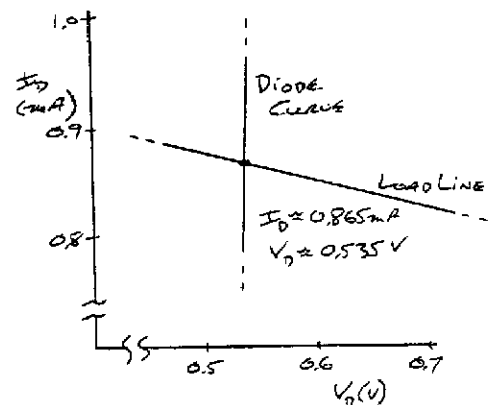

E1.15

a.

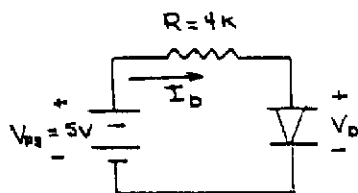


$$I_D = \frac{V_{PS} - V_T}{R} = \frac{5 - 0.7}{4} \Rightarrow I_D = 1.08 \text{ mA}$$


$$\text{b. } I_D = \frac{V_{PS} - V_T}{R} \Rightarrow R = \frac{V_{PS} - V_T}{I_D}$$

$$R = \frac{8 - 0.7}{1.075} \Rightarrow R = 6.79 \text{ k}\Omega$$

c.

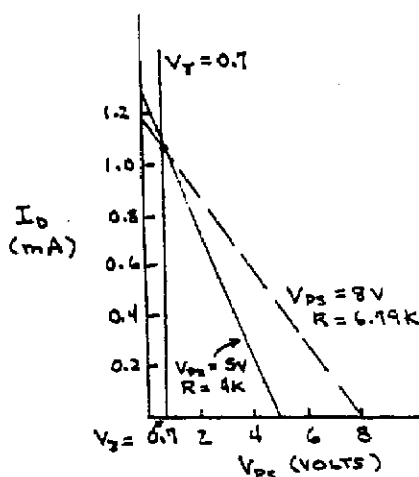

E1.16

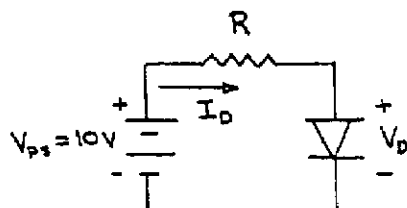

Power dissipation in diode = $I_D V_D$

$$1.05 \text{ mW} = I_D (0.7) \Rightarrow I_D = 1.5 \text{ mA}$$

$$R = \frac{V_{PS} - V_T}{I_D} = \frac{10 - 0.7}{1.5} \Rightarrow R = 6.2 \text{ k}\Omega$$

E1.17

$$g_d = \frac{I_D}{V_T} = \frac{0.8}{0.026} = 30.8 \text{ mS}$$

E1.18

$$r_d = \frac{V_T}{I_D} \Rightarrow 50 = \frac{0.026}{I_D} \Rightarrow I_D = \frac{0.026}{50}$$

$$I_D = 0.52 \text{ mA}$$

E1.19

$$I_D \approx I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$\text{pn junction: } V_D = (0.026) \ln\left(\frac{10^{-3}}{10^{-12}}\right)$$

$$V_D = 0.539 \text{ V}$$

$$\text{Schottky Diode: } V_D = (0.026) \ln\left(\frac{10^{-3}}{10^{-8}}\right)$$

$$V_D = 0.299 \text{ V}$$

E1.20

For the pn junction diode

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right) = (0.026) \ln\left(\frac{1.2 \times 10^{-3}}{4 \times 10^{-15}}\right)$$

$$V_D = 0.6871 \text{ V}$$

Schottky diode voltage will be smaller

$$\Rightarrow V_D = 0.6871 - 0.265 = 0.4221 \text{ V}$$

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$I_S = \frac{1.2 \times 10^{-3}}{\exp\left(\frac{0.4221}{0.026}\right)} \Rightarrow I_S = 1.07 \times 10^{-10} \text{ A}$$

E1.21


$$\text{Power} = I \cdot V_Z$$

$$10 = I(5.6) \Rightarrow I = 1.79 \text{ mA}$$

$$I = \frac{10 - 5.6}{R} = 1.79$$

$$R = \frac{10 - 5.6}{1.79} \Rightarrow \underline{R = 2.46 \text{ k}\Omega}$$

E1.22

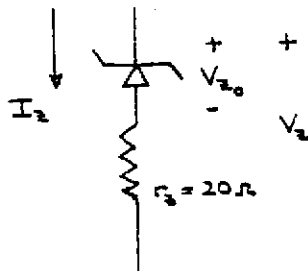

$$V_Z = V_{Z0} + I_Z r_z$$

$$\text{So } V_{Z0} = V_Z - I_Z r_z$$

$$V_{Z0} = 5.20 - (10^{-3})(20) = 5.20 - 0.02 = 5.18$$

Then

$$V_Z = 5.18 + (10 \times 10^{-3})(20) \Rightarrow \underline{V_Z = 5.38 \text{ V}}$$

Chapter 1

Problem Solutions

1.1

(a) $n_i = BT^{3/2} e^{-E_i/2kT}$

(i) Silicon, $T=275\text{K}$

$$n_i = (5.23 \times 10^{15}) (275)^{3/2} e^{-1.4/2(86 \times 10^{-6})(275)}$$

$$n_i = 1.90 \times 10^9 \text{ cm}^{-3}$$

(ii) $T=325\text{K}$

$$n_i = (5.23 \times 10^{15}) (325)^{3/2} e^{-1.4/2(86 \times 10^{-6})(325)}$$

$$n_i = 8.71 \times 10^{10} \text{ cm}^{-3}$$

(b) GaAs

(i) $T=275\text{K}$

$$n_i = (2.1 \times 10^{14}) (275)^{3/2} e^{-1.4/2(86 \times 10^{-6})(275)}$$

$$n_i = 1.34 \times 10^5 \text{ cm}^{-3}$$

(ii) $T=325\text{K}$

$$n_i = (2.10 \times 10^{14}) (325)^{3/2} e^{-1.4/2(86 \times 10^{-6})(325)}$$

$$n_i = 1.63 \times 10^7 \text{ cm}^{-3}$$

1.2

a. $n_i = BT^{3/2} \exp\left(\frac{-E_g}{2kT}\right)$

$$10^{12} = 5.23 \times 10^{15} T^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(T)}\right)$$

$$1.91 \times 10^{-4} = T^{3/2} \exp\left(\frac{-6.40 \times 10^3}{T}\right)$$

By trial and error, $T \approx 367^\circ \text{K}$

b. $n_i = 10^9 \text{ cm}^{-3}$

$$10^9 = 5.23 \times 10^{15} T^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(T)}\right)$$

$$1.91 \times 10^{-7} = T^{3/2} \exp\left(\frac{-6.40 \times 10^3}{T}\right)$$

By trial and error, $T \approx 268^\circ \text{K}$

1.3

a. $N_d = 5 \times 10^{15} \text{ cm}^{-3} \Rightarrow \underline{n\text{-type}}$

$$n_0 = N_d = 5 \times 10^{15} \text{ cm}^{-3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} \Rightarrow \underline{p_0 = 4.5 \times 10^4 \text{ cm}^{-3}}$$

b. $N_d = 5 \times 10^{15} \text{ cm}^{-3} \Rightarrow \underline{n\text{-type}}$

$$n_0 = N_d = 5 \times 10^{15} \text{ cm}^{-3}$$

$$n_i = (2.10 \times 10^{14}) (300)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(300)}\right)$$

$$= (2.10 \times 10^{14}) (300)^{3/2} (1.65 \times 10^{-12})$$

$$= 1.80 \times 10^6 \text{ cm}^{-3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.8 \times 10^6)^2}{5 \times 10^{15}} \Rightarrow \underline{p_0 = 6.48 \times 10^{-4} \text{ cm}^{-3}}$$

1.4

a. $N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$

$$p_0 = N_a = 10^{16} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(1.5 \times 10^{10})^2}{10^{16}} \Rightarrow \underline{n_0 = 2.25 \times 10^4 \text{ cm}^{-3}}$$

b. Germanium

$$N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$$

$$p_0 = N_a = 10^{16} \text{ cm}^{-3}$$

$$n_i = (1.66 \times 10^{15}) (300)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(300)}\right)$$

$$= (1.66 \times 10^{15}) (300)^{3/2} (2.79 \times 10^{-6})$$

$$= 2.4 \times 10^{13} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(2.4 \times 10^{13})^2}{10^{16}} \Rightarrow \underline{n_0 = 5.76 \times 10^{10} \text{ cm}^{-3}}$$

1.5

(a) $n_0 = 5 \times 10^{15} \text{ cm}^{-3}$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} \Rightarrow \underline{p_0 = 4.5 \times 10^4 \text{ cm}^{-3}}$$

(b) $n_0 \gg p_0 \Rightarrow \underline{n\text{-type}}$

(c) $n_0 \approx N_d = 5 \times 10^{15} \text{ cm}^{-3}$

1.6

a. Add Donors

$$N_d = 7 \times 10^{15} \text{ cm}^{-3}$$

b. Want $p_0 = 10^6 \text{ cm}^{-3} = n_i^2/N_d$

$$\text{So } n_i^2 = (10^6)(7 \times 10^{15}) = 7 \times 10^{21}$$

$$= B^2 T^3 \exp\left(\frac{-E_g}{kT}\right)$$

$$7 \times 10^{21} = (5.23 \times 10^{15})^2 T^3 \exp\left(\frac{-1.1}{(86 \times 10^{-6})(T)}\right)$$

By trial and error, $T \approx 324^\circ \text{K}$

1.7

$$I = J \cdot A = \sigma EA$$

$$I = (2.2)(15)(10^{-4}) \Rightarrow I = 3.3 \text{ mA}$$

1.8

$$J = \sigma E \Rightarrow \sigma = \frac{J}{E} = \frac{85}{12}$$

$$\sigma = 7.08 \text{ (ohm-cm)}^{-1}$$

1.9

(a) For n-type,

$$\sigma \cong e\mu_n N_d = (1.5 \times 10^{-19})(8500)N_d$$

$$\text{For } 10^{15} \leq N_d \leq 10^{19} \text{ cm}^{-3} \Rightarrow$$

$$1.36 \leq \sigma \leq 1.36 \times 10^4 \text{ (}\Omega\text{-cm)}^{-1}$$

$$(b) J = \sigma E = \sigma(0.1) \Rightarrow$$

$$0.136 \leq J \leq 1.36 \times 10^3 \text{ A/cm}^2$$

1.10

$$a. N_a = 10^{17} \text{ cm}^{-3} \Rightarrow p_0 = 10^{17} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(1.8 \times 10^6)^2}{10^{17}} \Rightarrow n_0 = 3.24 \times 10^{-5} \text{ cm}^{-3}$$

$$b. n = n_0 + \delta n = 3.24 \times 10^{-5} + 10^{15} \Rightarrow n = 10^{15} \text{ cm}^{-3}$$

$$p = p_0 + \delta p = 10^{17} + 10^{15} \Rightarrow p = 1.01 \times 10^{17} \text{ cm}^{-3}$$

1.11

$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right)$$

$$a. V_{bi} = (0.026) \ln \left[\frac{(10^{15})(10^{15})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.578 \text{ V}$$

$$b. V_{bi} = (0.026) \ln \left[\frac{(10^{15})(10^{18})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.757 \text{ V}$$

$$c. V_{bi} = (0.026) \ln \left[\frac{(10^{18})(10^{18})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.937 \text{ V}$$

1.12

$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right)$$

$$a. V_{bi} = (0.026) \ln \left[\frac{(10^{15})(10^{15})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.05 \text{ V}$$

$$b. V_{bi} = (0.026) \ln \left[\frac{(10^{15})(10^{18})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.23 \text{ V}$$


$$c. V_{bi} = (0.026) \ln \left[\frac{(10^{18})(10^{18})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.41 \text{ V}$$

1.13

$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right) = (0.026) \ln \left[\frac{N_a (10^{16})}{(15 \times 10^{10})^2} \right]$$

$$\text{For } N_a = 10^{15} \text{ cm}^{-3}, V_{bi} = 0.637 \text{ V}$$
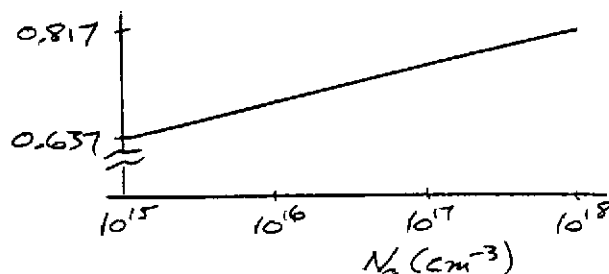
$$\text{For } N_a = 10^{18} \text{ cm}^{-3}, V_{bi} = 0.817 \text{ V}$$



1.14


$$kT = (0.026) \left(\frac{T}{300} \right)$$

T	kT	$(T)^{3/2}$
200	0.01733	2828.4
250	0.02167	3952.8
300	0.026	5196.2
350	0.03033	6547.9
400	0.03467	8000.0
450	0.0390	9545.9
500	0.04333	11180.3

$$n_i = (2.1 \times 10^{14}) (T^{3/2}) \exp \left(\frac{-1.4}{2(86 \times 10^{-6})(T)} \right)$$

$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right)$$

T	n_i	V_{bi}
200	1.256	1.405
250	6.02×10^3	1.389
300	1.80×10^6	1.370
350	1.09×10^8	1.349
400	2.44×10^9	1.327
450	2.80×10^{10}	1.302
500	2.00×10^{11}	1.277

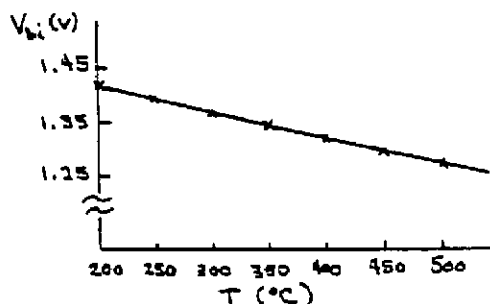

1.15

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$$

$$V_{bi} = (0.026) \ln \left[\frac{(2 \times 10^{18})(2 \times 10^{15})}{(1.5 \times 10^{10})^2} \right] = 0.673 \text{ V}$$

a. $V_R = 1 \text{ V}$

$$C_j = (1) \left(1 + \frac{1}{0.673} \right)^{-1/2} \Rightarrow \underline{C_j = 0.634 \text{ pF}}$$

b. $V_R = 5 \text{ V}$

$$C_j = (1) \left(1 + \frac{5}{0.673} \right)^{-1/2} \Rightarrow \underline{C_j = 0.344 \text{ pF}}$$

1.16

(a) $C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$

For $V_R = 5 \text{ V}$,

$$C_j = (0.02) \left(1 + \frac{5}{0.8} \right)^{-1/2} = 0.00743 \text{ pF}$$

For $V_R = 15 \text{ V}$,

$$C_j = (0.02) \left(1 + \frac{15}{0.8} \right)^{-1/2} = 0.0118 \text{ pF}$$

$$C_j(\text{avg}) = \frac{0.00743 + 0.0118}{2} = 0.00962 \text{ pF}$$

$$v_c(t) = v_c(\text{final}) + (v_c(\text{initial}) - v_c(\text{final}))e^{-t/\tau}$$

where

$$\tau = RC = RC_j(\text{avg}) = (47 \times 10^3)(0.00962 \times 10^{-12})$$

or

$$\tau = 4.52 \times 10^{-10} \text{ s}$$

Then

$$v_c(t) = 1.5 = 0 + (5 - 0)e^{-t/\tau}$$

$$\frac{5}{1.5} = e^{+t/\tau} \Rightarrow t_1 = \tau \ln \left(\frac{5}{1.5} \right)$$

$$\underline{t_1 = 5.44 \times 10^{-10} \text{ s}}$$

(b) For $V_R = 0 \text{ V}$,

$$C_j = C_{j0} = 0.02 \text{ pF}$$

For $V_R = 3.5 \text{ V}$,

$$C_j = (0.02) \left(1 + \frac{3.5}{0.8} \right)^{-1/2} = 0.00863 \text{ pF}$$

$$C_j(\text{avg}) = \frac{0.02 + 0.00863}{2} = 0.0143 \text{ pF}$$

$$\tau = RC_j(\text{avg}) = 6.72 \times 10^{-10} \text{ s}$$

$$v_c(t) = v_c(\text{final}) + (v_c(\text{initial}) - v_c(\text{final}))e^{-t/\tau}$$

$$3.5 = 5 + (0 - 5)e^{-t/\tau} = 5(1 - e^{-t/\tau})$$

so that $\underline{t_2 = 8.09 \times 10^{-10} \text{ s}}$

1.17

$$V_{bi} = (0.026) \ln \left[\frac{(10^{18})(10^{15})}{(1.5 \times 10^{10})^2} \right] = 0.757 \text{ V}$$

a. $V_R = 1 \text{ V}$

$$C_j = (0.25) \left(1 + \frac{1}{0.757} \right)^{-1/2} = 0.164 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(2.2 \times 10^{-3})(0.164 \times 10^{-12})}}$$

$$\underline{f_0 = 8.38 \text{ MHz}}$$

b. $V_R = 10 \text{ V}$

$$C_j = (0.25) \left(1 + \frac{10}{0.757} \right)^{-1/2} = 0.0663 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{(2.2 \times 10^{-3})(0.0663 \times 10^{-12})}}$$

$$f_0 = 13.2 \text{ MHz}$$

1.18

a. $I = I_S \left[\exp \left(\frac{V_D}{V_T} \right) - 1 \right]$

$$-0.90 = \exp \left(\frac{V_D}{V_T} \right) - 1$$

$$\exp \left(\frac{V_D}{V_T} \right) = 1 - 0.90 = 0.10$$

$$V_D = V_T \ln(0.10) \Rightarrow \underline{V_D = -0.0599 \text{ V}}$$

b.

$$\left| \frac{I_F}{I_R} \right| = \frac{I_S}{I_S} \cdot \frac{\left[\exp \left(\frac{V_F}{V_T} \right) - 1 \right]}{\left[\exp \left(\frac{V_R}{V_T} \right) - 1 \right]} = \left| \frac{\exp \left(\frac{0.2}{0.026} \right) - 1}{\exp \left(\frac{-0.2}{0.026} \right) - 1} \right|$$

$$= \left| \frac{2190}{-1} \right|$$

$$\underline{\frac{I_F}{I_R} = 2190}$$

1.19

a.

$$I \approx (10^{-11}) \exp \left(\frac{0.5}{0.026} \right) \Rightarrow \underline{I = 2.25 \text{ mA}}$$

$$I = (10^{-11}) \exp \left(\frac{0.6}{0.026} \right) \Rightarrow \underline{I = 0.105 \text{ A}}$$

$$I = (10^{-11}) \exp \left(\frac{0.7}{0.026} \right) \Rightarrow \underline{I = 4.93 \text{ A}}$$

b.

$$I \approx (10^{-13}) \exp \left(\frac{0.5}{0.026} \right) \Rightarrow \underline{I = 22.5 \text{ } \mu\text{A}}$$

$$I = (10^{-13}) \exp \left(\frac{0.6}{0.026} \right) \Rightarrow \underline{I = 1.05 \text{ mA}}$$

$$I = (10^{-13}) \exp \left(\frac{0.7}{0.026} \right) \Rightarrow \underline{I = 49.3 \text{ mA}}$$

1.20

(a) $I = I_S (e^{V_D/V_T} - 1)$

$$150 \times 10^{-6} = 10^{-11} (e^{V_D/V_T} - 1) \approx 10^{-11} e^{V_D/V_T}$$

Then

$$V_D = V_T \ln \left(\frac{150 \times 10^{-6}}{10^{-11}} \right) = (0.026) \ln \left(\frac{150 \times 10^{-6}}{10^{-11}} \right)$$

Or

$$\underline{V_D = 0.430 \text{ V}}$$

(b)

$$V_D = V_T \ln \left(\frac{150 \times 10^{-6}}{10^{-13}} \right)$$

Or

$$\underline{V_D = 0.549 \text{ V}}$$

1.21

a. $I_D \approx I_S \exp \left(\frac{V_D}{nV_T} \right)$

$$10^{-3} = I_S \exp \left(\frac{0.7}{2(0.026)} \right) \Rightarrow \underline{I_S = 1.42 \times 10^{-9} \text{ A}}$$

b. $I_D = (1.42 \times 10^{-9}) \exp \left(\frac{0.8}{2(0.026)} \right)$

$$\underline{I_D = 6.82 \text{ mA}}$$

c. $10^{-3} = I_S \exp \left(\frac{0.7}{0.026} \right)$

$$\underline{I_S = 2.03 \times 10^{-15} \text{ A}}$$

$$I_D = (2.03 \times 10^{-15}) \exp \left(\frac{0.8}{0.026} \right)$$

$$\underline{I_D = 46.8 \text{ mA}}$$

1.22

I_S doubles for every 5C increase in temperature.

$$I_S = 10^{-12} \text{ A at } T = 300\text{K}$$

$$\text{For } I_S = 0.5 \times 10^{-12} \text{ A} \Rightarrow \underline{T = 295\text{K}}$$

$$\text{For } I_S = 50 \times 10^{-12} \text{ A}, \quad (2)^n = 50 \Rightarrow n = 5.64$$

Where n equals number of 5C increases.

Then

$$\Delta T = (5.64)(5) = 28.2\text{K}$$

So

$$\underline{295 \leq T \leq 328.2\text{K}}$$

1.23

$$\frac{I_S(T)}{I_S(-55)} = 2^{\Delta T/5}, \quad \Delta T = 155^\circ\text{C}$$

$$\frac{I_S(100)}{I_S(-55)} = 2^{155/5} = 2.147 \times 10^9$$

$$V_T @ 100^\circ\text{C} \Rightarrow 373^\circ\text{K} \Rightarrow V_T = 0.03220$$

$$V_T @ -55^\circ\text{C} \Rightarrow 216^\circ\text{K} \Rightarrow V_T = 0.01865$$

$$\frac{I_D(100)}{I_D(-55)} = (2.147 \times 10^9) \times \frac{\exp\left(\frac{0.6}{0.0322}\right)}{\exp\left(\frac{0.6}{0.01865}\right)}$$

$$= \frac{(2.147 \times 10^9)(1.237 \times 10^8)}{(9.374 \times 10^{13})}$$

$$\frac{I_D(100)}{I_D(-55)} = 2.83 \times 10^3$$

1.24


$$\text{a. } \frac{I_{D2}}{I_{D1}} = 10 = \exp\left(\frac{V_{D2} - V_{D1}}{V_T}\right)$$

$$\Delta V_D = V_T \ln(10) \Rightarrow \Delta V_D = 59.9 \text{ mV} \approx 60 \text{ mV}$$

$$\text{b. } \Delta V_D = V_T \ln(100) \Rightarrow \Delta V_D = 119.7 \text{ mV} \approx 120 \text{ mV}$$

1.25

a.

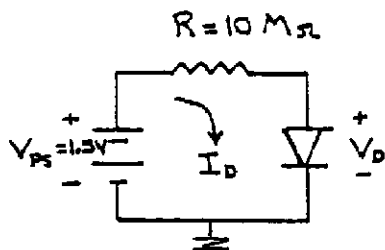

$$1.5 = I_D(10 \times 10^6) + V_D \text{ and}$$

$$I_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

$$1.5 = (10 \times 10^6)(30 \times 10^{-9}) \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D$$

$$= 0.3 \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D$$

By trial and error, $V_D = 0.046 \text{ V}$

$$\text{Then } I_D = \frac{1.5 - 0.046}{10} \Rightarrow I_D = 0.145 \mu\text{A}$$

b. Reverse-Bias


$$I = I_S = 30 \text{ nA}$$

$$V_R = (30 \times 10^{-9})(10 \times 10^6) = 0.30 \text{ V}$$


$$V_D = -1.5 + 0.3 \Rightarrow V_D = -1.2 \text{ V}$$

1.26

$$I_S = 5 \times 10^{-13} \text{ A}$$

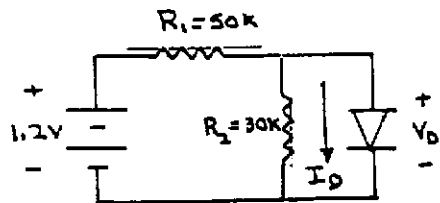
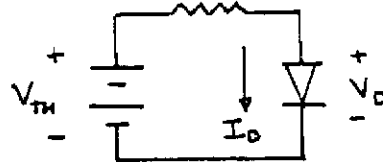
$$R_{TH} = R_1 \parallel R_2 = 18.75 \text{ k}\Omega$$




$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (1.2) = \left(\frac{30}{80} \right) (1.2) = 0.45 \text{ V}$$

$$0.45 = I_D R_{TH} + V_D, \quad V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

By trial and error:

$$I_D = 2.6 \mu\text{A}, \quad V_D = 0.402 \text{ V}$$

1.27

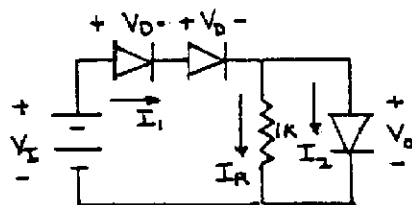

$$I_S = 2 \times 10^{-13} \text{ A}$$

$$V_0 = 0.60 \text{ V}$$

$$I_2 = I_S \exp\left(\frac{V_0}{V_T}\right) = (2 \times 10^{-13}) \exp\left(\frac{0.60}{0.026}\right)$$

$$= 2.105 \text{ mA}$$

$$I_R = \frac{0.6}{1 \text{ k}} = 0.60 \text{ mA}$$


$$I_1 = I_2 + I_R = 2.705 \text{ mA}$$

$$V_D = V_T \ln\left(\frac{I_1}{I_S}\right) = (0.026) \ln\left(\frac{2.705 \times 10^{-3}}{2 \times 10^{-13}}\right)$$

$$= 0.6065$$

$$V_I = 2V_D + V_0 \Rightarrow V_I = 1.81 \text{ V}$$

1.28

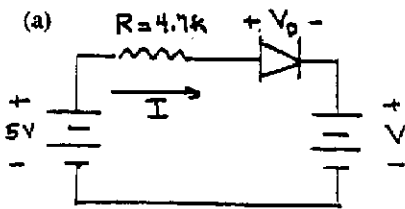

$$I_S = 5 \times 10^{-12} \text{ A}$$

$$I = 0.50 \text{ mA}$$

$$V_D = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{5 \times 10^{-12}} \right)$$

$$\underline{V_D = 0.479 \text{ V}}$$

$$5 = IR + V_D + V$$

$$= (0.5 \times 10^{-3})(4.7 \times 10^3) + 0.479 + V$$

$$\underline{V = 2.17 \text{ V}}$$

$$(b) P = I_D V_D = (0.5)(0.479)$$

or

$$\underline{P = 0.24 \text{ mW}}$$

1.29

(a) Assume diode is conducting.

$$\text{Then, } V_D = V_f = 0.7 \text{ V}$$

$$\text{So that } I_{R2} = \frac{0.7}{30} \Rightarrow 23.3 \mu\text{A}$$

$$I_{R1} = \frac{12 - 0.7}{10} \Rightarrow 50 \mu\text{A}$$

$$\text{Then } I_D = I_{R1} - I_{R2} = 50 - 23.3$$

Or

$$\underline{I_D = 26.7 \mu\text{A}}$$

(b) Let $R_1 = 50 \text{ k}\Omega$ Diode is cutoff.

$$V_D = \frac{30}{30 + 50} \cdot (12) = 0.45 \text{ V}$$

$$\text{Since } V_D < V_f, \quad I_D = 0$$

1.30

(a) Diode is conducting

$$5 = I_D(10) + V_f - 5$$

or

$$I_D = \frac{10 - 0.6}{10} \Rightarrow \underline{I_D = 0.94 \text{ mA}}$$

$$V_o = V_f - 5 = 0.6 - 5 \Rightarrow \underline{V_o = -4.4 \text{ V}}$$

(b) Diode is conducting

$$5 = V_f + I_D(10) - 5$$

or

$$I_D = \frac{10 - 0.6}{10} \Rightarrow \underline{I_D = 0.94 \text{ mA}}$$

$$V_o = I_D R - 5 = (0.94)(10) - 5 \Rightarrow \underline{V_o = 4.4 \text{ V}}$$

(c) Diode is reverse biased

$$\underline{I_D = 0} \quad \underline{V_D = -10 \text{ V}}$$

1.31

Minimum diode current for $V_{PS}(\text{min})$

$$I_D(\text{min}) = 2 \text{ mA}, \quad V_D = 0.7 \text{ V}$$

$$I_2 = \frac{0.7}{R_2}, \quad I_1 = \frac{5 - 0.7}{R_1} = \frac{4.3}{R_1}$$

We have

$$I_1 = I_2 + I_D$$

so

$$(1) \quad \frac{4.3}{R_1} = \frac{0.7}{R_2} + 2$$

Maximum diode current for $V_{PS}(\text{max})$

$$P = I_D V_D \quad 10 = I_D(0.7) \Rightarrow I_D = 14.3 \text{ mA}$$

$$I_1 = I_2 + I_D$$

or

$$(2) \quad \frac{9.3}{R_1} = \frac{0.7}{R_2} + 14.3$$


Using Eq. (1),

$$\frac{9.3}{R_1} = \frac{4.3}{R_1} - 2 + 14.3 \Rightarrow \underline{R_1 = 0.41 \text{ k}\Omega}$$

Then

$$\underline{R_2 = 82.5 \Omega}$$

1.32

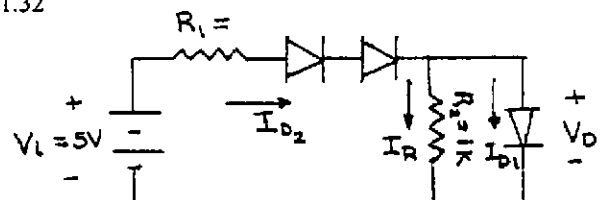


$$I_{D1} = \frac{1}{2} I_{D2} \Rightarrow I_{D1} = I_R = \frac{0.65}{1} = 0.65 \text{ mA}$$

$$I_{D2} = 1.3 \text{ mA} = \frac{5 - 3(0.65)}{R_1}$$

$$\underline{R_1 = 2.35 \text{ k}\Omega}, \quad \underline{I_{D1} = 0.65 \text{ mA}}, \quad \underline{I_{D2} = 1.30 \text{ mA}}$$

1.33

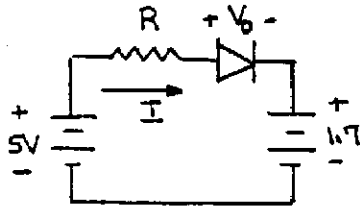

$$V_D = 0.65 \text{ V}$$

$$\text{Power} = I \cdot V_D = 0.2 \text{ mW} = I(0.65)$$

$$\Rightarrow I = 0.308 \text{ mA}$$

$$I = \frac{5 - 0.65 - 1.7}{R} = 0.308$$

$$\Rightarrow R = \frac{2.65}{0.308} \Rightarrow R = 8.60 \text{ k}\Omega$$

1.34

For forward bias

$$I_D = \frac{15 - 0.7}{10 \text{ M}\Omega} = 0.08 \mu\text{A}$$

For reverse bias

$$I_D = 0, V_D = -15 \text{ V}$$

1.35

$$a. r_d = \frac{V_T}{I_{DQ}} = \frac{(0.026)}{1} = 0.026 \text{ k}\Omega = 26 \Omega$$

$$i_d = 0.05 I_{DQ} = 50 \mu\text{A} \text{ peak-to-peak}$$

$$v_d = i_d r_d = (26)(50) \mu\text{V}$$

$$\Rightarrow v_d = 1.30 \text{ mV peak-to-peak}$$


$$b. \text{ For } I_{DQ} = 0.1 \text{ mA} \Rightarrow r_d = \frac{(0.026)}{0.1} = 260 \Omega$$

$$i_d = 0.05 I_{DQ} = 5 \mu\text{A} \text{ peak-to-peak}$$

$$v_d = i_d r_d = (260)(5) \mu\text{V}$$

$$\Rightarrow v_d = 1.30 \text{ mV peak-to-peak}$$

1.36

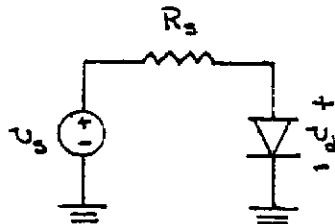

ac equivalent circuit

$$a. \text{ diode resistance } r_d = V_T / I$$

$$v_d = \left(\frac{r_d}{r_d + R_s} \right) v_s = \left(\frac{V_T / I}{V_T / I + R_s} \right) v_s$$

$$v_d = \left(\frac{V_T}{V_T + I R_s} \right) v_s = v_o$$

$$b. R_s = 260 \Omega$$

$$I = 1 \text{ mA}, \frac{v_o}{v_s} = \left(\frac{V_T}{V_T + I R_s} \right) = \frac{0.026}{0.026 + (1)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.0909$$

$$I = 0.1 \text{ mA}, \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.1)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.50$$

$$I = 0.01 \text{ mA}, \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.01)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.909$$

1.37

$$I \approx I_S \exp \left(\frac{V_a}{V_T} \right), V_a = V_T \ln \left(\frac{I}{I_S} \right)$$


$$\text{pn junction, } V_a = (0.026) \ln \left(\frac{100 \times 10^{-6}}{10^{-14}} \right)$$

$$V_a = 0.599 \text{ V}$$

$$\text{Schottky diode, } V_a = (0.026) \ln \left(\frac{100 \times 10^{-6}}{10^{-9}} \right)$$

$$V_a = 0.299 \text{ V}$$

1.38

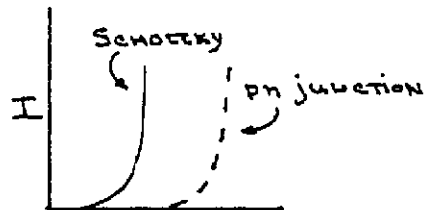

$$\text{Schottky: } I \approx I_S \exp \left(\frac{V_a}{V_T} \right)$$

$$V_a = V_T \ln \left(\frac{I}{I_S} \right) = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{5 \times 10^{-7}} \right)$$

$$= 0.1796 \text{ V}$$

Then

$$V_a \text{ of pn junction} = 0.1796 + 0.30$$

$$= 0.4796$$

$$I_S = \frac{I}{\exp \left(\frac{V_a}{V_T} \right)} = \frac{0.5 \times 10^{-3}}{\exp \left(\frac{0.4796}{0.026} \right)}$$

$$I_S = 4.87 \times 10^{-12} \text{ A}$$

1.39

pn junction $I_D = 0.5 \text{ mA}$

$$I_D \cong I_s e^{V_D/V_T} \Rightarrow V_D = V_T \ln \left(\frac{I_D}{I_s} \right)$$

Then

$$V_D = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{10^{-12}} \right) = 0.521 \text{ V}$$

Schottky diode

$$V_D = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{10^{-8}} \right) = 0.281 \text{ V}$$


Then

$$R = \frac{V_D(\text{pn}) - V_D(\text{S})}{0.5} = \frac{0.521 - 0.281}{0.5} \Rightarrow$$

$$R = 480 \Omega$$

1.40

(a)

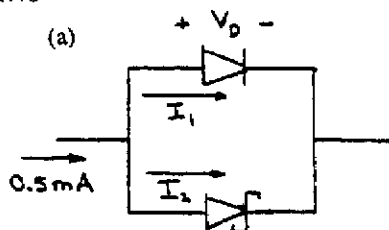

$$I_1 + I_2 = 0.5 \times 10^{-3}$$


$$5 \times 10^{-8} \exp \left(\frac{V_D}{V_T} \right) + 10^{-12} \exp \left(\frac{V_D}{V_T} \right) = 0.5 \times 10^{-3}$$

$$5.001 \times 10^{-8} \exp \left(\frac{V_D}{V_T} \right) = 0.5 \times 10^{-3}$$

$$V_D = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{5.001 \times 10^{-8}} \right) \Rightarrow \underline{V_D = 0.2395}$$

Schottky diode, $I_2 = 0.49999 \text{ mA}$ pn junction, $I_1 = 0.00001 \text{ mA}$

(b)

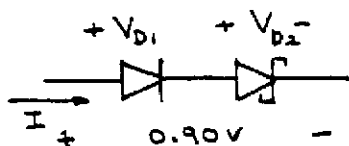

$$I = 10^{-12} \exp \left(\frac{V_{D1}}{V_T} \right) = 5 \times 10^{-8} \exp \left(\frac{V_{D2}}{V_T} \right)$$

$$V_{D1} + V_{D2} = 0.9$$

$$10^{-12} \exp \left(\frac{V_{D1}}{V_T} \right) = 5 \times 10^{-8} \exp \left(\frac{0.9 - V_{D1}}{V_T} \right)$$

$$= 5 \times 10^{-8} \exp \left(\frac{0.9}{V_T} \right) \cdot \exp \left(\frac{-V_{D1}}{V_T} \right)$$

$$\exp \left(\frac{2V_{D1}}{V_T} \right) = \left(\frac{5 \times 10^{-8}}{10^{-12}} \right) \exp \left(\frac{0.9}{0.026} \right)$$


$$2V_{D1} = V_T \ln \left(\frac{5 \times 10^{-8}}{10^{-12}} \right) + 0.9 = 1.1813$$

$$\underline{V_{D1} = 0.591} \text{ pn junction}$$

$$\underline{V_{D2} = 0.309} \text{ Schottky diode}$$

$$I = 10^{-12} \exp \left(\frac{0.5907}{0.026} \right) \Rightarrow \underline{I = 7.36 \text{ mA}}$$

1.41

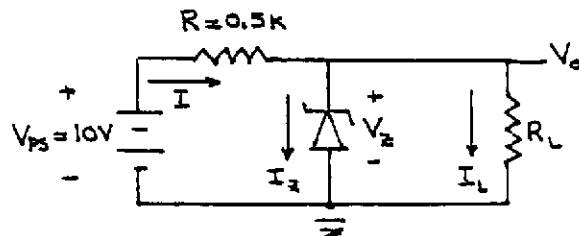

$$V_Z = V_{Z0} = 5.6 \text{ V at } I_Z = 0.1 \text{ mA}$$

$$r_Z = 10 \Omega$$

$$I_Z r_Z = (0.1)(10) = 1 \text{ mV}$$

$$V_{Z0} = 5.599$$

$$\text{a. } R_L \rightarrow \infty \Rightarrow$$

$$I_Z = \frac{10 - 5.599}{R + r_Z} = \frac{4.401}{0.50 + 0.01} = 8.63 \text{ mA}$$

$$V_Z = V_{Z0} + I_Z r_Z = 5.599 + (0.00863)(10)$$

$$\underline{V_Z = V_O = 5.685 \text{ V}}$$

$$\text{b. } V_{PS} = 11 \text{ V} \Rightarrow I_Z = \frac{11 - 5.599}{0.51} = 10.59 \text{ mA}$$

$$V_Z = V_O = 5.599 + (0.01059)(10) = 5.705 \text{ V}$$

$$V_{PS} = 9 \text{ V} \Rightarrow I_Z = \frac{9 - 5.599}{0.51} = 6.669 \text{ mA}$$

$$V_Z = V_O = 5.599 + (0.006669)(10) = 5.666 \text{ V}$$

$$\Delta V_O = 5.705 - 5.666 \Rightarrow \underline{\Delta V_O = 0.039 \text{ V}}$$

$$c. \quad I = I_Z + I_L$$

$$I_L = \frac{V_0}{R_L}, \quad I = \frac{V_{PS} - V_0}{R}, \quad I_Z = \frac{V_0 - V_{Z0}}{r_Z}$$

$$\frac{10 - V_0}{0.50} = \frac{V_0 - 5.599}{0.010} + \frac{V_0}{2}$$

$$\frac{10}{0.50} + \frac{5.599}{0.010} = V_0 \left[\frac{1}{0.50} + \frac{1}{0.010} + \frac{1}{2} \right]$$

$$20.0 + 559.9 = V_0(102.5)$$

$$\underline{V_0 = 5.658 \text{ V}}$$

1.42

$$a. \quad I_Z = \frac{9 - 6.8}{0.2} \Rightarrow \underline{I_Z = 11 \text{ mA}}$$

$$P_Z = (11)(5.8) \Rightarrow \underline{P_Z = 74.8 \text{ mW}}$$

$$b. \quad I_Z = \frac{12 - 6.8}{0.2} \Rightarrow \underline{I_Z = 26 \text{ mA}}$$

$$\% = \frac{26 - 11}{11} \times 100 \Rightarrow \underline{136\%}$$

$$P_Z = (26)(6.8) = 176.8 \text{ mW}$$

$$\% = \frac{176.8 - 74.8}{74.8} \times 100 = \underline{136\%}$$

1.43

$$I_Z r_Z = (0.1)(20) = 2 \text{ mV}$$

$$V_{Z0} = 6.8 - 0.002 = 6.798 \text{ V}$$

$$a. \quad R_L = \infty$$

$$I_Z = \frac{10 - 6.798}{0.5 + 0.02} \Rightarrow I_Z = 6.158 \text{ mA}$$

$$V_0 = V_Z = V_{Z0} + I_Z r_Z = 6.798 + (0.006158)(20)$$

$$\underline{V_0 = 6.921 \text{ V}}$$

$$b. \quad I = I_Z + I_L$$

$$\frac{10 - V_0}{0.50} = \frac{V_0 - 6.798}{0.020} + \frac{V_0}{1}$$

$$\frac{10}{0.50} + \frac{6.798}{0.020} = V_0 \left[\frac{1}{0.50} + \frac{1}{0.020} + \frac{1}{1} \right]$$

$$359.9 = V_0(53)$$

$$V_0 = 6.791 \text{ V}$$

$$\Delta V_0 = 6.791 - 6.921$$

$$\underline{\Delta V_0 = -0.13 \text{ V}}$$