

## Chapter 7

## Exercise Solutions

E7.1

$$a. \quad R_S = R_P = 4 \text{ k}\Omega$$

$$\omega = \frac{1}{r_S} = \frac{1}{(R_S + R_P)C_S}$$

$$C_S = \frac{1}{2\pi f(R_S + R_P)} = \frac{1}{2\pi(20)(4 + 4) \times 10^3}$$

$$C_S = 0.995 \text{ }\mu\text{F}$$

$$b. \quad |T(j\omega)| = \left( \frac{R_P}{R_S + R_P} \right) \frac{\omega r_S}{\sqrt{1 + \omega^2 r_S^2}}$$

$$r_S = (R_S + R_P)C_S = 7.96 \times 10^{-3}$$

$$\frac{R_P}{R_S + R_P} = \frac{4}{4 + 4} = 0.5$$

$$f = 40 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(40)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(40)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.447$$

$$f = 80 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(80)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(80)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.485$$

$$f = 200 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(200)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(200)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.498$$

E7.2

$$\omega = \frac{1}{\tau_P} = \frac{1}{(R_S \| R_P)C_P}$$

$$C_P = \frac{1}{2\pi f(R_S \| R_P)}$$

$$= \frac{1}{2\pi(500 \times 10^3)(10 \| 10) \times 10^3}$$

$$C_P = 63.7 \text{ pF}$$

E7.3

$$a. \quad V_0 = -(g_m V_\pi) R_L$$

$$V_\pi = \frac{r_\pi}{r_\pi + \frac{1}{sC_C} + R_S} \times V_i$$

$$T(s) = \frac{V_0(s)}{V_i(s)} = \frac{-g_m r_\pi R_L}{r_\pi + R_S + (1/sC_C)}$$

$$= \frac{-g_m r_\pi R_L (sC_C)}{1 + s(r_\pi + R_S)C_C}$$

$$g_m r_\pi = \beta$$

$$T(s) = \frac{-\beta R_L}{r_\pi + R_S} \times \left( \frac{s(r_\pi + R_S)C_C}{1 + s(r_\pi + R_S)C_C} \right)$$

$$b. \quad f_{3-dB} = \frac{1}{2\pi(r_\pi + R_S)C_C}$$


$$f_{3-dB} = \frac{1}{2\pi[2 \times 10^3 + 1 \times 10^3][10^{-6}]}$$

$$\Rightarrow f_{3-dB} = 53.1 \text{ Hz}$$

$$|T(j\omega)|_{\max} = \frac{r_\pi g_m R_L}{r_\pi + R_S} = \frac{(2)(50)(4)}{2 + 1}$$

$$|T(j\omega)|_{\max} = 133$$

c.

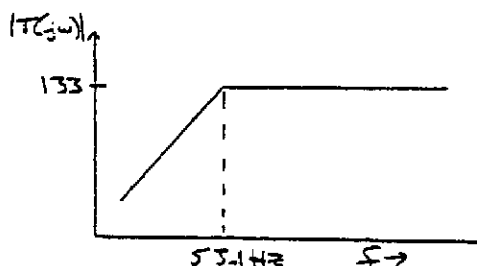

E7.4

$$a. \quad V_0 = -g_m V_\pi \left( R_L \| \frac{1}{sC_L} \right)$$

$$V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) \times V_i$$

$$T(s) = \frac{V_0(s)}{V_i(s)} = -g_m \frac{r_\pi}{r_\pi + R_S} \left( \frac{R_L \times \frac{1}{sC_L}}{R_L + \frac{1}{sC_L}} \right)$$

$$T(s) = \frac{-\beta R_L}{r_\pi + R_S} \times \left( \frac{1}{1 + sR_L C_L} \right)$$


$$b. \quad f_{3-dB} = \frac{1}{2\pi R_L C_L} = \frac{1}{2\pi(5 \times 10^3)(10 \times 10^{-12})}$$

$$\Rightarrow f_{3dB} = 3.18 \text{ MHz}$$

$$|T(j\omega)| = \frac{g_m r_\pi R_L}{r_\pi + R_S} = \frac{(75)(1.5)(5)}{1.5 + 0.5}$$

$$|T(j\omega)|_{\max} = 281$$

c.

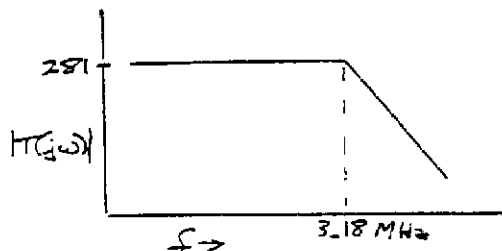

E7.5

$$a. \quad 20 \log_{10} \left( \frac{R_P}{R_P + R_S} \right) = -1$$

$$\Rightarrow \frac{R_P}{R_P + R_S} = 0.891 = \frac{R_P}{R_P + 1}$$

$$\Rightarrow (1 - 0.891)R_P = 0.891 \Rightarrow \underline{R_P = 8.17 \text{ k}\Omega}$$

$$f_L = \frac{1}{2\pi(R_S + R_P)C_S}$$

$$\Rightarrow C_S = \frac{1}{2\pi(100)(1 + 8.17) \times 10^3}$$

$$\underline{C_S = 0.174 \text{ }\mu\text{F}}$$

$$f_H = \frac{1}{2\pi(R_S \| R_P)C_P}$$

$$\Rightarrow C_P = \frac{1}{2\pi(10^6)(1 \| 8.17) \times 10^3}$$

$$\underline{C_P = 179 \text{ pF}}$$

$$b. \quad \tau_S = (R_S + R_P)C_S$$

$$\tau_S = (1 \times 10^3 + 8.17 \times 10^3)(0.174 \times 10^{-6})$$

$$\underline{\tau_S = 1.60 \text{ ms open-circuit time-constant}}$$

$$\tau_P = (R_S \| R_P)C_P$$

$$\tau_P = (1 \| 8.17) \times 10^3 (179 \times 10^{-12})$$

$$\underline{\tau_P = 0.160 \text{ }\mu\text{s short-circuit time-constant}}$$

E7.6

$$a. \quad \text{Open-circuit time constant } (C_L \rightarrow \text{open})$$

$$\tau_S = (R_S + r_\pi)C_C$$

$$= (0.25 + 2) \times 10^3 (2 \times 10^{-6}) = 4.5 \text{ ms}$$

$$\text{Short-circuit time constant } (C_C \rightarrow \text{short})$$

$$\tau_P = R_L C_L = (4 \times 10^3)(50 \times 10^{-12})$$

$$\underline{\tau_P = 0.2 \text{ }\mu\text{s}}$$

$$b. \quad \text{Midband gain}$$

$$V_o = -g_m V_\pi R_L, \quad V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) V_i$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m r_\pi R_L}{r_\pi + R_S} = \frac{-(65)(2)(4)}{2 + 0.25}$$

$$\underline{A_v = -231}$$

$$c. \quad f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(4.5 \times 10^{-3})} \Rightarrow \underline{f_L = 35.4 \text{ Hz}}$$

$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(0.2 \times 10^{-6})} \Rightarrow \underline{f_H = 0.796 \text{ MHz}}$$

E7.7

$$a. \quad \tau_S = (R_1 + R_S)C_C$$

$$b. \quad f = \frac{1}{2\pi\tau_S}$$

$$R_{TH} = R_1 \| R_2 = 2.2 \| 20 = 1.98 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{2.2}{2.2 + 20} \right) (10) = 0.991 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{0.991 - 0.7}{1.98 + (201)(0.1)} = 0.0132 \text{ mA}$$

$$I_{CQ} = 2.64 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(200)(0.026)}{2.64} = 1.97 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.64}{0.026} = 102 \text{ mA/V}$$

$$R_{ib} = r_\pi + (1 + \beta)R_E = 1.97 + (201)(0.1) = 22.1 \text{ k}\Omega$$

$$R_B = R_1 \| R_2 = 1.98 \text{ k}\Omega$$

$$R_i = R_B \| R_{ib} = 1.98 \| 22.1 = 1.82 \text{ k}\Omega$$

$$\tau_S = (R_i + R_S)C_C$$

$$= (1.82 + 0.1)(\times 10^3)(47 \times 10^{-6})$$

$$= 90.24 \text{ ms}$$

$$f = \frac{1}{2\pi(90.24 \times 10^{-3})} \Rightarrow \underline{f = 1.76 \text{ Hz}}$$

Midband Gain

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} \cdot \frac{R_i}{R_i + R_S} = \frac{-(200)(2)}{1.97 + (201)(0.1)} \cdot \frac{1.82}{1.82 + 0.1}$$

$$\underline{A_v = -17.2}$$

E7.8

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2$$

$$a. \quad \sqrt{\frac{0.8}{0.5}} + 2 = V_{GS} \Rightarrow V_{GS} = 3.26 \text{ V}$$

$$V_S = -3.26 \Rightarrow I_{DQ} = \frac{V_S - (-5)}{R_S}$$

$$R_S = \frac{-3.26 + 5}{0.8} \Rightarrow \underline{R_S = 2.18 \text{ k}\Omega}$$

$$V_D = 0 \Rightarrow R_D = \frac{5}{0.8} \Rightarrow \underline{R_D = 6.25 \text{ k}\Omega}$$

$$b. \quad \tau_S = (R_D + R_L)C_C = (10 + 6.25) \times 10^3 \times C_C$$

$$f = \frac{1}{2\pi\tau_S} \Rightarrow C_C = \frac{1}{2\pi f(16.25 \times 10^3)}$$

$$C_C = \frac{1}{2\pi(20)(16.25 \times 10^3)}$$

$$\Rightarrow \underline{C_C = 0.49 \text{ }\mu\text{F}}$$

E7.9

$$\tau_S = (R_L + R_E \parallel R_0)C_{C2}$$

$$f = \frac{1}{2\pi\tau_S} \Rightarrow C_{C2} = \frac{1}{2\pi f(R_L + R_E \parallel R_0)}$$

$$R_0 = r_o \parallel \left\{ \frac{r_\pi + (R_S \parallel R_B)}{1 + \beta} \right\}$$

From Example 7-5,  $R_0 = 35.6 \text{ }\Omega$

$$R_0 \parallel R_E = 0.0356 \parallel 10 \approx 0.0356 \text{ k}\Omega$$

$$C_{C2} = \frac{1}{2\pi(10)(10 \times 10^3 + 35.6)}$$

$$\underline{C_{C2} = 1.59 \text{ }\mu\text{F}}$$

E7.10

$$a. \quad I_{DQ} = K_p (V_{SG} + V_{TP})^2$$

$$\sqrt{\frac{1}{0.5}} - (-2) = V_{SG} \Rightarrow V_{SG} = 3.41 \text{ V}$$

$$V_S = 3.41$$

$$R_S = \frac{5 - 3.41}{1} \Rightarrow \underline{R_S = 1.59 \text{ k}\Omega}$$

For  $V_{SDG} = V_{SGQ} \Rightarrow V_D = 0$

$$\Rightarrow R_D = \frac{5}{1} \Rightarrow \underline{R_D = 5 \text{ k}\Omega}$$

$$b. \quad \tau_P = (R_D \parallel R_L)C_L$$

$$f = \frac{1}{2\pi\tau_P} \Rightarrow C_L = \frac{1}{2\pi f(R_D \parallel R_L)}$$

$$C_L = \frac{1}{2\pi(10^6)(5 \parallel 10) \times 10^3}$$

$$\Rightarrow \underline{C_L = 47.7 \text{ pF}}$$

E7.11

$$a. \quad I_{BQ} = \frac{0 - 0.7 - (-10)}{0.5 + (101)(4)} = 0.0230 \text{ mA}$$

$$I_{CQ} = 2.30 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{2.30} = 1.13 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.30}{0.026} = 88.5 \text{ mA/V}$$

$$\tau_B = \frac{R_E(R_S + r_\pi)C_E}{R_S + r_\pi + (1 + \beta)R_E}$$

$$= \frac{(4 \times 10^3)(0.5 + 1.13)C_E}{0.5 + 1.13 + (101)(4)}$$

$$\tau_B = \frac{1}{2\pi f_B} = \frac{1}{2\pi(200)} = 0.796 \text{ ms}$$

$$\tau_B = 16.07 C_E \Rightarrow C_E = \frac{0.796 \times 10^{-3}}{16.07}$$

$$\Rightarrow \underline{C_E = 49.5 \text{ }\mu\text{F}}$$

$$b. \quad \tau_A = R_E C_E = (4 \times 10^3)(49.5 \times 10^{-6})$$

$$\Rightarrow \tau_A = 0.198 \text{ s}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(0.198)} \Rightarrow \underline{f_A = 0.80 \text{ Hz}}$$

E7.14

$$r_\pi = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(150)(0.026)}{0.5} = 7.8 \text{ k}\Omega$$

$$f_B = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$= \frac{1}{2\pi(7.8 \times 10^3)(2 + 0.3) \times 10^{-12}}$$

$$\Rightarrow \underline{f_B = 8.87 \text{ MHz}}$$

E7.15

$$r_\pi = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$f_B = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{1}{2\pi f_B r_\pi} = \frac{1}{2\pi(11.5 \times 10^6)(10.4 \times 10^3)}$$

$$C_\pi + C_\mu = 1.33 \text{ pF}$$

$$C_\mu = 0.1 \text{ pF}$$

$$\Rightarrow \underline{C_\pi = 1.23 \text{ pF}}$$

E7.16

$$h_{fe} = \frac{\beta_0}{1 + j(f/f_B)}$$

$$f_B = 5 \text{ MHz}, \beta_0 = 100$$

At  $f = 50 \text{ MHz}$

$$|h_{fe}| = \frac{100}{\sqrt{1 + \left(\frac{50}{5}\right)^2}} \Rightarrow |h_{fe}| = 9.95$$

$$\text{Phase} = -\tan^{-1}\left(\frac{50}{5}\right) \Rightarrow \underline{\text{Phase} = -84.3^\circ}$$

E7.17

$$f_s = \frac{f_T}{\beta_0} = \frac{500}{120} \Rightarrow f_s = 4.17 \text{ MHz}$$

$$f_s = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{1}{2\pi f_s r_\pi} = \frac{1}{2\pi (4.17 \times 10^6)(5 \times 10^3)}$$

$$C_\pi + C_\mu = 7.63 \text{ pF}$$

$$C_\mu = 0.2 \text{ pF}$$

$$\Rightarrow C_\pi = 7.43 \text{ pF}$$

E7.18

$$r_\pi = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(150)(0.026)}{1} \Rightarrow r_\pi = 3.9 \text{ k}\Omega$$

$$f_s = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$= \frac{1}{2\pi (3.9 \times 10^3)(4 + 0.5)(10^{-12})}$$

$$\Rightarrow f_s = 9.07 \text{ MHz}$$

$$f_T = \beta_0 f_s = (150)(9.07)$$

$$\Rightarrow f_T = 1.36 \text{ GHz}$$

E7.19

$$R_{TH} = R_1 \parallel R_2 = 200 \parallel 220 = 105 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{220}{200 + 220} \right) (5)$$

$$= 2.62 \text{ V}$$

$$I_{BQ} = \frac{2.62 - 0.7}{105 + (101)(1)} = 0.00932 \text{ mA}$$

$$I_{CQ} = 0.932 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.932}{0.026} \Rightarrow g_m = 35.8 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.932} \Rightarrow r_\pi = 2.79 \text{ k}\Omega$$

$$a. \quad C_M = C_\mu [1 + g_m (R_C \parallel R_L)]$$

$$C_M = (2)[1 + (35.8)(2.2 \parallel 4.7)]$$

$$\Rightarrow C_M = 109 \text{ pF}$$

$$b. \quad R_B = r_s \parallel R_1 \parallel R_2 = 100 \parallel 200 \parallel 220 = 51.2 \text{ k}\Omega$$

$$f_{3dB} = \frac{1}{2\pi (R_B \parallel r_\pi) (C_\pi + C_\mu)}$$

$$= \frac{1}{2\pi [51.2 \parallel 2.79] \times 10^3 \times (10 + 109) \times 10^{-12}}$$

$$\Rightarrow f_{3dB} = 0.595 \text{ MHz}$$

E7.20

$$(a) \quad g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.4)(3 - 1)$$

$$\Rightarrow g_m = 1.6 \text{ mA/V}$$

$$g'_m = 80\% \text{ of } g_m = 1.28 \text{ mA/V}$$

$$g'_m = \frac{g_m}{1 + g_m r_s}$$

$$1 + g_m r_s = \frac{g_m}{g'_m}$$

$$r_s = \frac{1}{g_m} \left( \frac{g_m}{g'_m} - 1 \right) = \frac{1}{1.6} \left( \frac{1.6}{1.28} - 1 \right)$$

$$r_s = 0.156 \text{ k}\Omega \Rightarrow r_s = 156 \text{ ohms}$$

$$(b) \quad g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.4)(5 - 1)$$

$$\Rightarrow g_m = 3.2 \text{ mA/V}$$

$$g'_m = \frac{g_m}{1 + g_m r_s} = \frac{3.2}{1 + (3.2)(0.156)} = 2.13$$

$$\frac{\Delta g_m}{g_m} = \frac{3.2 - 2.13}{3.2} \Rightarrow \Delta 33.4\% \text{ reduction}$$

E7.21

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2$$

$$0.4 = 0.2(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.41 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.2)(2.41 - 1)$$

$$= 0.564 \text{ mA/V}$$

$$f_T = \frac{0.564 \times 10^{-3}}{2\pi (0.25 + 0.02) \times 10^{-12}} \Rightarrow$$

$$f_T = 332 \text{ MHz}$$

E7.22

$$f_T = \frac{g_m}{2\pi (C_{gsT} + C_{gdT})}$$

$$= \frac{g_m}{2\pi (C_{gs} + C_{gsp} + C_{gdp})}$$

$$C_{gs} = \frac{g_m}{2\pi f_T} - C_{gsp} - C_{gdp}$$

$$= \frac{0.5 \times 10^{-3}}{2\pi (500 \times 10^6)} - (0.01 + 0.01) \times 10^{-12}$$

$$\Rightarrow C_{gs} = 0.139 \text{ pF}$$

E7.23

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gsp} + C_{gdp})}$$

$$C_{gsp} = C_{gdp}$$

$$2C_{gsp} = \frac{g_m}{2\pi f_T} - C_{gs} = \frac{1 \times 10^{-3}}{2\pi(350 \times 10^6)} - 0.4 \times 10^{-12}$$

$$2C_{gsp} = 0.0547 \text{ pF}$$

$$\Rightarrow C_{gsp} = C_{gdp} = 0.0274 \text{ pF}$$

E7.24

dc analysis

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{166}{166 + 234} \right) (10) = 4.15 \text{ V}$$

$$I_D = \frac{V_S}{R_S} \text{ and } V_S = V_G - V_{GS}$$

$$K_n(V_{GS} - V_{TN})^2 = \frac{V_G - V_{GS}}{R_S}$$


$$(0.5)(0.5)(V_{GS}^2 - 4V_{GS} + 4) = 4.15 - V_{GS}$$

$$0.25V_{GS}^2 - 3.15 = 0 \Rightarrow V_{GS} = 3.55 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2.55 - 2)$$

$$= 1.55 \text{ mA/V}$$

Small-signal equivalent circuit.

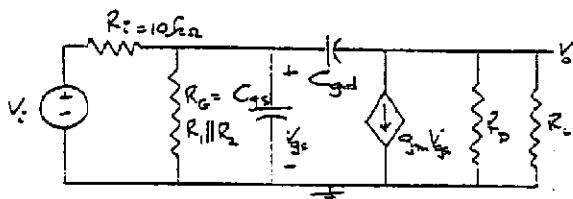

$$a. C_M = C_{gs}(1 + g_m(R_D \parallel R_L))$$

$$C_M = (0.1)[1 + (1.55)(4 \parallel 20)]$$

$$\Rightarrow C_M = 0.617 \text{ pF}$$

$$b. f_H = \frac{1}{2\pi\tau_P}$$

$$\tau_P = (R_G \parallel R_L)(C_{gs} + C_M)$$

$$R_G = R_1 \parallel R_2 = 234 \parallel 166 = 97.1 \text{ kΩ}$$

$$R_G \parallel R_L = 97.1 \parallel 10 = 9.07 \text{ kΩ}$$

$$\tau_P = (9.07 \times 10^3)(1 + 0.617) \times 10^{-12} = 14.7 \text{ ns}$$

$$f_H = \frac{1}{2\pi(14.7 \times 10^{-9})} \Rightarrow f_H = 10.9 \text{ MHz}$$

E7.25

dc analysis

$$V_{TH} = 0, R_{TH} = 10 \text{ kΩ}$$

$$I_{BQ} = \frac{0 - 0.7 - (-5)}{10 + (126)(5)} = 0.00672 \text{ mA}$$


$$I_{CQ} = 0.840 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(125)(0.026)}{0.840} = 3.87 \text{ kΩ}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.840}{0.026} = 32.3 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ kΩ}$$

High-frequency equivalent circuit

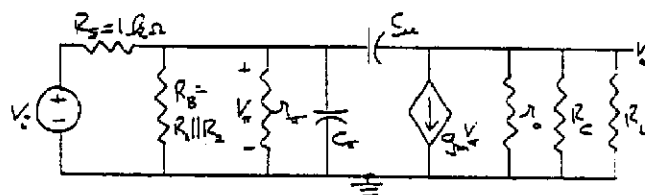

a. Miller capacitance

$$C_M = C_\mu(1 + g_m R'_L)$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$R'_L = 238 \parallel 2.3 \parallel 5 = 1.57 \text{ kΩ}$$

$$C_M = (3)[1 + (32.3)(1.57)] \Rightarrow C_M = 153 \text{ pF}$$

$$b. R_{eq} = R_S \parallel R_B \parallel r_\pi = R_S \parallel R_1 \parallel R_2 \parallel r_\pi$$

$$R_{eq} = 1 \parallel 20 \parallel 20 \parallel 3.87 = 0.736 \text{ kΩ}$$

$$\tau_P = R_{eq}(C_\pi + C_M)$$

$$= (0.736 \times 10^3)(24 + 153) \times 10^{-12}$$

$$= 1.32 \times 10^{-7}$$

$$f_H = \frac{1}{2\pi(1.32 \times 10^{-7})} \Rightarrow f_H = 1.21 \text{ MHz}$$

$$c. (A_v)_M = -g_m R'_L \left[ \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_S} \right]$$

$$(A_v)_M = -(32.3)(1.57) \left[ \frac{10 \parallel 3.87}{10 \parallel 3.87 + 1} \right]$$

$$\Rightarrow (A_v)_M = -37.3$$

## E7.26

dc analysis

$$V_G = \left( \frac{50}{50 + 150} \right) (10) - 5 = -2.5$$

$$V_S = V_G - V_{GS}. \quad I_D = \frac{V_S - (-5)}{R_S}$$

$$K_n (V_{GS} - V_{TN})^2 = \frac{V_G - V_{GS} + 5}{R_S}$$

$$(1)(2)[V_{GS}^2 - 1.6V_{GS} + 0.64] = -2.5 - V_{GS} + 5$$


$$2V_{GS}^2 - 2.2V_{GS} - 1.22 = 0$$

$$V_{GS} = \frac{2.2 \pm \sqrt{(2.2)^2 + 4(2)(1.22)}}{2(2)}$$

$$\Rightarrow V_{GS} = 1.51 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1)(1.51 - 0.8) \\ = 1.42 \text{ mA/V}$$

Equivalent circuit

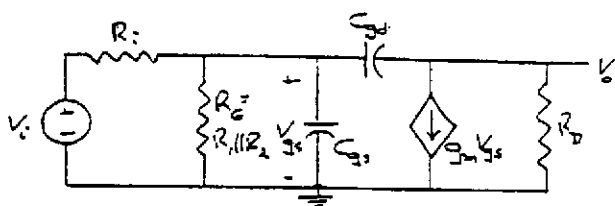

$$(a) \quad C_M = C_{gs}(1 + g_m R_D) = (0.2)[1 + (1.42)(5)] \Rightarrow \\ C_M = 1.62 \text{ pF}$$

$$(b) \quad \tau_P = (R_S \parallel R_G)(C_{gs} + C_M)$$

$$\tau_P = [20 \parallel 50 \parallel 150] \times 10^3 \times (2 + 1.62) \times 10^{-12} \\ = (13 \times 10^3)(3.62 \times 10^{-12}) = 4.71 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(4.7 \times 10^{-8})}$$

$$\Rightarrow \underline{f_H = 3.38 \text{ MHz}}$$

$$(c) \quad (A_v)_M = -g_m R_D \left( \frac{R_G}{R_G + R_S} \right)$$

$$(A_v)_M = -(1.42)(5) \left( \frac{37.5}{37.5 + 20} \right)$$

$$\Rightarrow \underline{(A_v)_M = -4.63}$$

## E7.27

The dc analysis

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)(10)} = 0.00838 \text{ mA}$$

$$I_{CQ} = 0.838 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.838} = 3.10 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 32.2 \text{ mA/V}$$

For the input

$$\tau_{P\pi} = \left[ \left( \frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right] C_\pi \\ = \left[ \frac{3.10}{101} \parallel 10 \parallel 1 \right] \times 10^3 \times 24 \times 10^{-12} \\ = 7.13 \times 10^{-10} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi\tau_{P\pi}} = \frac{1}{2\pi(7.13 \times 10^{-10})} \\ \Rightarrow \underline{f_{H\pi} = 223 \text{ MHz}}$$

For the output

$$\tau_{P\mu} = [R_C \parallel R_L] C_\mu = (10 \parallel 1) \times 10^3 \times 3 \times 10^{-12} \\ = 2.73 \times 10^{-9} \text{ s}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{P\mu}} = \frac{1}{2\pi(2.73 \times 10^{-9})} \\ \Rightarrow \underline{f_{H\mu} = 58.3 \text{ MHz}}$$

$$(A_v)_M = g_m (R_C \parallel R_L) \left[ \frac{R_E \parallel \left( \frac{r_\pi}{1 + \beta} \right)}{R_E \parallel \left( \frac{r_\pi}{1 + \beta} \right) + R_S} \right] \\ = (32.2)(10 \parallel 1) \left[ \frac{10 \parallel \left( \frac{3.1}{101} \right)}{10 \parallel \left( \frac{3.1}{101} \right) + 1} \right]$$

$$\Rightarrow \underline{(A_v)_M = 0.869}$$

## Chapter 7


## Problem Solutions

7.1

$$a. \quad T(s) = \frac{V_o(s)}{V_i(s)} = \frac{1/(sC_1)}{[1/(sC_1)] + R_1}$$

$$T(s) = \frac{1}{1 + sR_1C_1}$$

b.

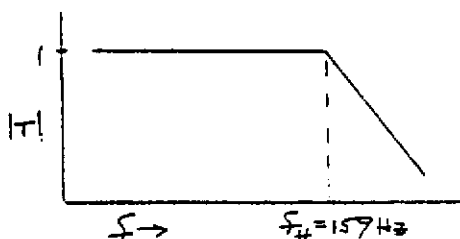

$$f_H = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(10^3)(10^{-6})}$$

$$\Rightarrow f_H = 159 \text{ Hz}$$

$$c. \quad V_o(s) = V_i(s) \cdot \frac{1}{1 + sR_1C_1}$$

$$\text{For a step function } V_i(s) = \frac{1}{s}$$

$$V_o(s) = \frac{1}{s} \cdot \frac{1}{1 + sR_1C_1} = \frac{K_1}{s} + \frac{K_2}{1 + sR_1C_1}$$

$$= \frac{K_1(1 + sR_1C_1) + K_2s}{s(1 + sR_1C_1)}$$

$$= \frac{K_1 + s(K_1R_1C_1 + K_2)}{s(1 + sR_1C_1)}$$

$$K_2 = -K_1R_1C_1 \text{ and } K_1 = 1$$

$$V_o(s) = \frac{1}{s} + \frac{-R_1C_1}{1 + sR_1C_1}$$

$$= \frac{1}{s} - \frac{1}{\frac{1}{R_1C_1} + s}$$


$$v_o(t) = 1 - e^{-t/R_1C_1}$$

7.2

$$a. \quad T(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_2 + [1/(sC_2)]}$$

$$T(s) = \frac{sR_2C_2}{1 + sR_2C_2}$$

b.

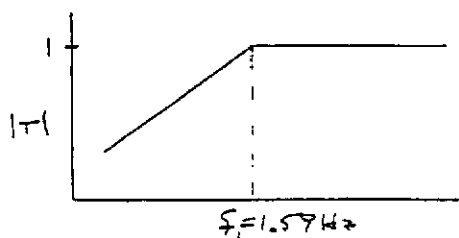

$$f_L = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi(10^4)(10 \times 10^{-6})}$$

$$\Rightarrow f_L = 1.59 \text{ Hz}$$

$$c. \quad V_o(s) = V_i(s) \cdot \frac{sR_2C_2}{1 + sR_2C_2}$$

$$V_i(s) = \frac{1}{s}$$

$$V_o(s) = \frac{R_2C_2}{1 + sR_2C_2} = \frac{1}{s + \frac{1}{R_2C_2}}$$

$$v_o(t) = e^{-t/R_2C_2}$$

7.3

$$a. \quad T(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_P \parallel \frac{1}{sC_P}}{R_P \parallel \frac{1}{sC_P} + \left(R_S + \frac{1}{sC_S}\right)}$$

$$R_P \parallel \frac{1}{sC_P} = \frac{R_P \cdot \frac{1}{sC_P}}{R_P + \frac{1}{sC_P}} = \frac{R_P}{1 + sR_P C_P}$$

Then

$$T(s) = \frac{R_P}{R_P + \left(R_S + \frac{1}{sC_S}\right)(1 + sR_P C_P)}$$

$$= \frac{R_P}{R_P + R_S + \frac{R_P C_P}{C_S} + \frac{1}{sC_S} + sR_S R_P C_P}$$

 $T(s)$ 

$$= \left(\frac{R_P}{R_P + R_S}\right) \times \left(1 / \left[1 + \frac{R_P}{R_P + R_S} \cdot \frac{C_P}{C_S} + \frac{1}{s(R_S + R_P)C_S} + \frac{sR_P R_S}{R_S + R_P} \cdot C_P\right]\right)$$

b.

$$\begin{aligned}
 T(s) &= \left( \frac{10}{10 + 10} \right) \\
 &\quad \times \left( 1 / \left[ 1 + \frac{10}{20} \cdot \frac{10^{-11}}{10^{-6}} + \frac{1}{s(2 \times 10^4) \cdot 10^{-6}} \right. \right. \\
 &\quad \left. \left. + s(5 \times 10^3) \cdot 10^{-11} \right] \right) \\
 &\approx \frac{1}{2} \cdot \frac{1}{1 + \frac{1}{s(0.02)} + s(5 \times 10^{-8})}
 \end{aligned}$$

 $s = j\omega$ 

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + j \left[ \omega(5 \times 10^{-8}) - \frac{1}{\omega(0.02)} \right]}$$

$$\text{For } \omega_L = \frac{1}{(R_S + R_P)C_S} = \frac{1}{(2 \times 10^4)(10^{-6})} = 50$$

$$\begin{aligned}
 T(j\omega) &= \frac{1}{2} \cdot \frac{1}{1 + j \left[ (50)(5 \times 10^{-8}) - \frac{1}{(50)(0.02)} \right]} \\
 &\approx \frac{1}{2} \cdot \frac{1}{1 - j} \Rightarrow |T(j\omega)| = \frac{1}{2} \cdot \frac{1}{\sqrt{2}}
 \end{aligned}$$

For

$$\omega_H = \frac{1}{(R_S \| R_P)C_P} = \frac{1}{(5 \times 10^3)(10^{-11})} = 2 \times 10^7$$

$$\begin{aligned}
 T(j\omega) &= \frac{1}{2} \cdot \frac{1}{1 + j \left[ (2 \times 10^7)(5 \times 10^{-8}) - \frac{1}{(2 \times 10^7)(0.02)} \right]} \\
 T(j\omega) &\approx \frac{1}{2} \cdot \frac{1}{1 + j} \Rightarrow |T(j\omega)| = \frac{1}{2} \cdot \frac{1}{\sqrt{2}}
 \end{aligned}$$

$$T(j\omega) \approx \frac{1}{2} \cdot \frac{1}{1 + j} \Rightarrow |T(j\omega)| = \frac{1}{2} \cdot \frac{1}{\sqrt{2}}$$

$$\text{In each case, } |T(j\omega)| = \frac{1}{\sqrt{2}} \cdot \frac{R_P}{R_P + R_S}$$

$$\text{c. } R_S = R_P = 10 \text{ k}\Omega, \quad C_S = C_P = 0.1 \text{ }\mu\text{F}$$

$$\begin{aligned}
 T(s) &= \frac{1}{2} \cdot \left( 1 / \left[ 1 + \frac{1}{2} \cdot \frac{1}{s} + \frac{1}{s(2 \times 10^4)(10^{-7})} \right. \right. \\
 &\quad \left. \left. + s(5 \times 10^3)(10^{-7}) \right] \right)
 \end{aligned}$$

 $s = j\omega$ 

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + \frac{1}{2} + j \left[ \omega(5 \times 10^{-4}) - \frac{1}{\omega(2 \times 10^{-3})} \right]}$$

$$\text{For } \omega = \frac{1}{(2 \times 10^4)(10^{-7})} = 500$$

$$\begin{aligned}
 T(j\omega) &= \frac{1}{2} \cdot \frac{1}{1.5 + j \left[ (500)(5 \times 10^{-4}) - \frac{1}{(500)(2 \times 10^{-3})} \right]} \\
 &= \frac{1}{2} \cdot \frac{1}{1.5 - j(0.75)} \Rightarrow |T(j\omega)| = 0.298
 \end{aligned}$$

$$\text{For } \omega = \frac{1}{(5 \times 10^3)(10^{-7})} = 2 \times 10^3$$

$$\begin{aligned}
 T(j\omega) &= \frac{1}{2} \cdot \left\{ 1 / \left( 1.5 + j \left[ (2 \times 10^3)(5 \times 10^{-4}) \right. \right. \right. \\
 &\quad \left. \left. \left. - \frac{1}{(2 \times 10^3)(2 \times 10^{-3})} \right] \right) \right\} \\
 &= \frac{1}{2} \cdot \frac{1}{1.5 + j(0.75)} \Rightarrow |T(j\omega)| = 0.298
 \end{aligned}$$

$$\text{In each case, } |T(j\omega)| < \frac{1}{\sqrt{2}} \cdot \frac{R_P}{R_P + R_S}$$

7.4

Circuit (a):

$$\begin{aligned}
 T = \frac{V_o}{V_i} &= \frac{R_2}{R_2 + R_1 \left\| \frac{1}{sC_1} \right\|} = \frac{R_2}{R_2 + \frac{R_1(1/sC_1)}{R_1 + (1/sC_1)}} \\
 &= \frac{R_2}{R_2 + \frac{R_1}{1 + sR_1C_1}} = \frac{R_2(1 + sR_1C_1)}{R_2 + sR_1R_2C_1 + R_1}
 \end{aligned}$$

or

$$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{(1 + sR_1C_1)}{1 + sR_1 \| R_2 C_1}$$

Low frequency:

$$\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1 + R_2} = \frac{20}{10 + 20} = \frac{2}{3}$$

High frequency:

$$\left| \frac{V_o}{V_i} \right| = 1$$


$$\tau_1 = R_1 C_1 = (10^4)(10 \times 10^{-6}) = 0.10 \Rightarrow$$

$$f_1 = \frac{1}{2\pi\tau_1} = 159 \text{ Hz}$$

$$\tau_2 = (R_1 \| R_2) C_1 = (10 \| 20) \times 10^3 \times (10 \times 10^{-6}) \Rightarrow$$

$$\tau_2 = 0.0667 \Rightarrow$$
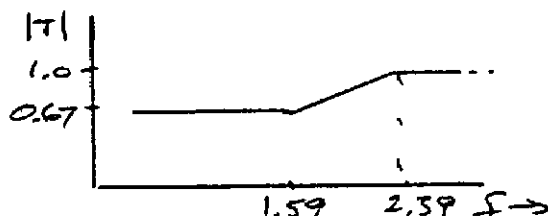
$$f_2 = \frac{1}{2\pi\tau_2} = 239 \text{ Hz}$$



Circuit (b):

$$T = \frac{V_o}{V_i} = \frac{R_2 \parallel \frac{1}{sC_2}}{R_2 \parallel \frac{1}{sC_2} + R_1} = \frac{\frac{R_2}{1+sR_2C_2}}{\frac{R_2}{1+sR_2C_2} + R_1}$$


$$= \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{1}{1 + s(R_1 \parallel R_2)C_2} \right)$$

Low frequency:

$$\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1 + R_2} = \frac{20}{20 + 10} = \frac{2}{3}$$

$$\tau = (R_1 \parallel R_2)C_2 = (10 \parallel 20) \times 10^3 \times 10 \times 10^{-6} = 0.0667$$
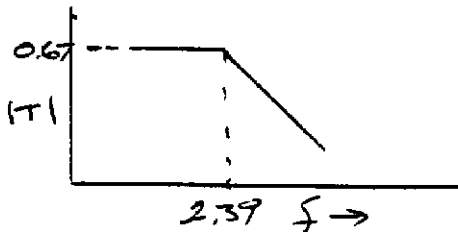
$$f = \frac{1}{2\pi\tau} = 2.39 \text{ Hz}$$



7.5

$$a. \quad \tau_S = (R_i + R_P)C_S = [30 + 10] \times 10^3 \times 10 \times 10^{-6}$$

$$\Rightarrow \tau_S = 0.40 \text{ s}$$

$$\tau_P = (R_i \parallel R_P)C_P = [30 \parallel 10] \times 10^3 \times 50 \times 10^{-12}$$

$$\Rightarrow \tau_P = 0.375 \mu\text{s}$$

$$b. \quad f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(0.4)} \Rightarrow f_L = 0.398 \text{ Hz}$$


$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(0.375 \times 10^{-6})} \Rightarrow f_H = 424 \text{ kHz}$$

 At midband,  $C_S \rightarrow$  short,  $C_P \rightarrow$  open

$$V_o = I_i(R_i \parallel R_P)$$

$$T(s) = R_i \parallel R_P = 30 \parallel 10 \Rightarrow T(s) = 7.5 \text{ k}\Omega$$

c.

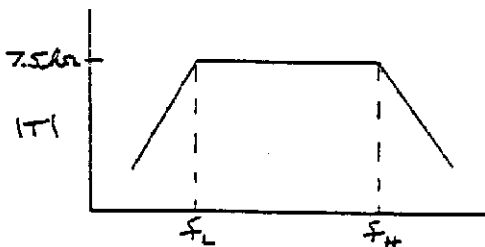

7.6

$$(a) \quad T = \frac{1}{(1 + j2\pi f\tau)^2} \Rightarrow$$

$$|T| = \frac{1}{(\sqrt{1 + (2\pi f\tau)^2})^2} = \frac{1}{1 + (2\pi f\tau)^2}$$

$$|T|_{\max} = 1$$

$$\text{At } f = \frac{1}{2\pi\tau} \Rightarrow |T| = \frac{1}{1 + (1)^2} = \frac{1}{2}$$

$$|T|_{dB} = 20 \log_{10} \left( \frac{1}{2} \right) \Rightarrow |T|_{dB} \approx -6 \text{ dB}$$

$$\text{Phase} = 2 \tan^{-1}(2\pi f\tau) = -2 \tan^{-1}(1) = -2(45^\circ) \Rightarrow$$

$$\text{Phase} = -90^\circ$$

(b) Slope

$$= -2(6 \text{ dB/oct}) =$$

$$-12 \text{ dB/oct} = -40 \text{ dB/decade}$$


$$\text{Phase} = -2(90^\circ) \Rightarrow \text{Phase} = -180^\circ$$

7.7

$$(a) \quad T(j\omega) = \frac{-10(j\omega)}{20 \left( 1 + \frac{j\omega}{20} \right) (2000) \left( 1 + \frac{j\omega}{2000} \right)}$$


$$= \frac{2.5 \times 10^{-4}(j\omega)}{\left( 1 + \frac{j\omega}{20} \right) \left( 1 + \frac{j\omega}{2000} \right)}$$

$$|T| = \frac{2.5 \times 10^{-4}(\omega)}{\sqrt{1 + \left( \frac{\omega}{20} \right)^2} \cdot \sqrt{1 + \left( \frac{\omega}{2000} \right)^2}}$$

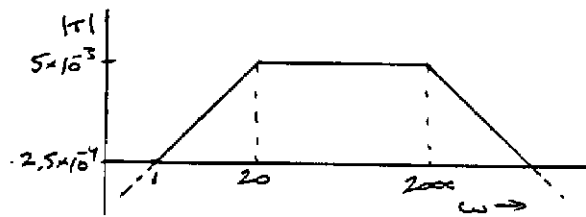

$$(b) \quad T(j\omega) = \frac{(10)(10) \left( 1 + \frac{j\omega}{10} \right)}{1000 \left( 1 + \frac{j\omega}{1000} \right)}$$

$$|T| = \frac{(0.10) \sqrt{1 + \left( \frac{\omega}{10} \right)^2}}{\sqrt{1 + \left( \frac{\omega}{1000} \right)^2}}$$

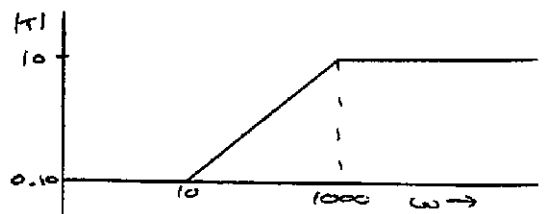

7.8

$$\begin{aligned} \text{a. } V_0 &= -g_m V_\pi R_L \quad V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) V_i \\ |T| &= g_m R_L \left( \frac{r_\pi}{r_\pi + R_S} \right) = (29)(6) \left( \frac{5.2}{5.2 + 0.5} \right) \\ |T_{\text{midband}}| &= 159 \end{aligned}$$

$$\text{b. } r_S = (R_S + r_\pi) C_C$$

$$f_L = \frac{1}{2\pi r_S} \Rightarrow r_S = \frac{1}{2\pi f_L} = \frac{1}{2\pi(30)}$$

$$\Rightarrow r_S = 5.31 \text{ ms} \quad \text{Open-circuit}$$

$$r_P = \frac{1}{2\pi f_H} = \frac{1}{2\pi(480 \times 10^3)}$$

$$\Rightarrow r_P = 0.332 \text{ } \mu\text{s} \quad \text{Short-circuit}$$

$$\text{c. } C_C = \frac{r_S}{(R_S + r_\pi)} = \frac{5.31 \times 10^{-3}}{(0.5 + 5.2) \times 10^3}$$

$$\Rightarrow C_C = 0.932 \text{ } \mu\text{F}$$

$$r_P = R_L C_L$$

$$C_L = \frac{r_P}{R_L} = \frac{0.332 \times 10^{-6}}{6 \times 10^3} \Rightarrow C_L = 55.3 \text{ pF}$$

7.11

$$\text{a. } R_{TH} = R_1 \parallel R_2 = 10 \parallel 1.5 = 1.30 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{1.5}{1.5 + 10} \right) (12) = 1.565 \text{ V}$$

$$I_{BQ} = \frac{1.565 - 0.7}{1.30 + (101)(0.1)} = 0.0759 \text{ mA}$$

$$I_{CQ} = 7.59 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{7.59} = 0.343 \text{ k}\Omega$$

$$g_m = \frac{7.59}{0.026} = 292 \text{ mA/V}$$


$$\begin{aligned} R_i &= R_1 \parallel R_2 \parallel [r_\pi + (1 + \beta) R_E] \\ &= 10 \parallel 1.5 \parallel [0.343 + (101)(0.1)] \\ &= 1.30 \parallel 10.4 \Rightarrow R_i = 1.16 \text{ k}\Omega \end{aligned}$$

$$\tau = (R_S + R_i) C_C = [0.5 + 1.16] \times 10^3 \times 0.1 \times 10^{-6}$$

$$\tau = 1.66 \times 10^{-4}$$

$$f_L = \frac{1}{2\pi\tau} = \frac{1}{2\pi(1.66 \times 10^{-4})} \Rightarrow f_L = 959 \text{ Hz}$$

b.

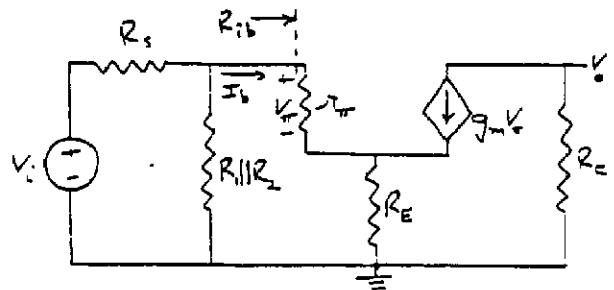

$$V_0 = -(\beta I_B) R_C$$

$$\begin{aligned} R_{ib} &= r_\pi + (1 + \beta) R_E \\ &= 0.343 + (101)(0.1) = 10.4 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} I_b &= \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) I_i \\ &= \left( \frac{1.30}{1.30 + 10.4} \right) I_i = (0.111) I_i \end{aligned}$$


$$\begin{aligned} I_i &= \frac{V_i}{R_S + R_1 \parallel R_2 \parallel R_{ib}} \\ &= \frac{V_i}{0.5 + (1.3) \parallel (10.4)} \end{aligned}$$

$$\begin{aligned} I_i &= \frac{V_i}{1.656} \\ \left| \frac{V_0}{V_i} \right| &= \frac{\beta R_C (0.111)}{1.656} \end{aligned}$$

$$\Rightarrow \left| \frac{V_0}{V_i} \right|_{\text{midband}} = \frac{(100)(1)(0.111)}{1.656}$$

$$\Rightarrow \left| \frac{V_0}{V_i} \right|_{\text{midband}} = 6.70$$

c.

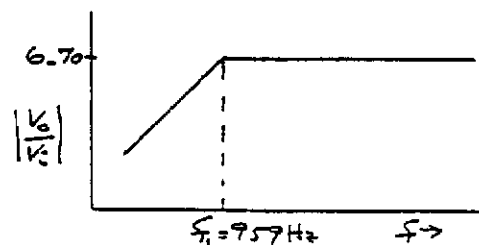

7.12

$$I_{DQ} = 0.5 \text{ mA} \Rightarrow V_S = (0.5)(0.5) = 0.25 \text{ V}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2$$

$$\Rightarrow V_{GS} = \sqrt{\frac{0.5}{0.2}} + 1.5 = 3.08 \text{ V}$$

$$V_G = V_{GS} + V_S = 3.08 + 0.25 \Rightarrow V_G = 3.33 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} \Rightarrow 3.33 = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$3.33 = \frac{1}{R_1}(200)(9) \Rightarrow R_1 = 541 \text{ k}\Omega$$

$$\frac{541R_2}{541 + R_2} = 200 \Rightarrow R_2 = 317 \text{ k}\Omega$$

$$V_D = V_{DSQ} + V_S = 4.5 + 0.25 = 4.75$$

$$R_D = \frac{9 - 4.75}{0.5} \Rightarrow R_D = 8.5 \text{ k}\Omega$$

$$f_L = \frac{1}{2\pi\tau_L} \Rightarrow \tau_L = \frac{1}{2\pi f_L} = \frac{1}{2\pi(20)} = 7.96 \text{ ms}$$



$$\tau_L = R_{in} \cdot C_C \Rightarrow C_C = \frac{\tau_L}{R_{in}} = \frac{7.96 \times 10^{-3}}{200 \times 10^3}$$

$$\Rightarrow C_C = 0.0398 \text{ }\mu\text{F}$$

$$g_m = 2(0.2)(3.08 - 1.5) = 0.632 \text{ mA/V}$$

$$|A_v|_{\text{midband}} = \frac{g_m R_D}{1 + g_m R_S} = \frac{(0.632)(8.5)}{1 + (0.632)(0.5)}$$

$$\Rightarrow |A_v| = 4.08$$

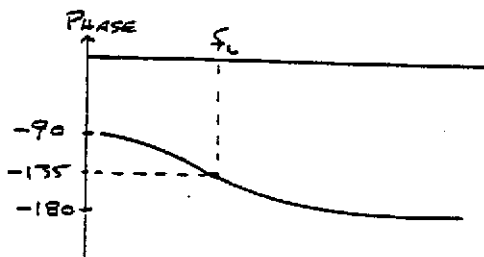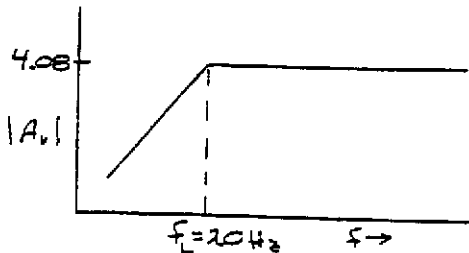

7.13

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$\Rightarrow V_{GS} = \sqrt{\frac{I_{DQ}}{K_n}} + V_{TN} = \sqrt{\frac{1}{0.5}} + 1 = 2.41 \text{ V}$$


$$V_S = -2.41 \text{ V}$$

$$R_S = \frac{-2.41 - (-5)}{1} \Rightarrow R_S = 2.59 \text{ k}\Omega$$

$$V_D = V_{DSQ} + V_S = 3 - 2.41 = 0.59 \text{ V}$$

$$R_D = \frac{5 - 0.59}{1} \Rightarrow R_D = 4.4 \text{ k}\Omega$$

b.

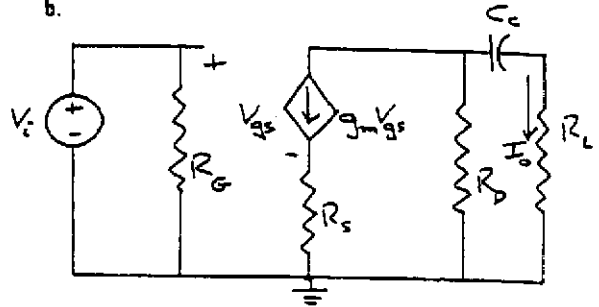

$$I_o = -(g_m V_{gs}) \left( \frac{R_D}{R_D + R_L + \frac{1}{sC_C}} \right)$$

$$V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$\frac{I_o(s)}{V_i(s)} = \frac{-g_m}{1 + g_m R_S} \cdot R_D \left[ \frac{sC_C}{1 + s(R_D + R_L)C_C} \right]$$

$$T(s) = \frac{I_o(s)}{V_i(s)}$$

$$= \frac{-g_m R_D}{1 + g_m R_S} \cdot \frac{1}{R_D + R_L} \cdot \frac{s(R_D + R_L)C_C}{1 + s(R_D + R_L)C_C}$$

$$c. \quad f_L = \frac{1}{2\pi\tau_L} \Rightarrow \tau_L = \frac{1}{2\pi f_L} = \frac{1}{2\pi(10)} = 15.9 \text{ ms}$$

$$\tau_L = (R_D + R_L)C_C$$

$$\Rightarrow C_C = \frac{\tau_L}{R_D + R_L} = \frac{15.9 \times 10^{-3}}{(4.41 + 4) \times 10^3}$$

$$\Rightarrow C_C = 1.89 \text{ }\mu\text{F}$$

7.14

$$a. \quad \frac{9 - V_{SG}}{R_S} = I_D = K_p(V_{SG} + V_{TP})^2$$

$$9 - V_{SG} = (0.5)(12)(V_{SG}^2 - 4V_{SG} + 4)$$

$$6V_{SG}^2 - 23V_{SG} + 15 = 0$$

$$V_{SG} = \frac{23 \pm \sqrt{(23)^2 - 4(6)(15)}}{2(6)} \Rightarrow V_{SG} = 3 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(0.5)(3 - 2)$$

$$\Rightarrow g_m = 1 \text{ mA/V}$$

$$R_o = \frac{1}{g_m} \parallel R_S = 1 \parallel 12 \Rightarrow R_o = 0.923 \text{ k}\Omega$$

$$b. \quad \tau = (R_o + R_L)C_C$$

$$c. \quad f_L = \frac{1}{2\pi\tau} \Rightarrow \tau = \frac{1}{2\pi f_L} = \frac{1}{2\pi(20)} = 7.96 \text{ ms}$$

$$C_C = \frac{\tau}{R_o + R_L} = \frac{7.96 \times 10^{-3}}{(0.923 + 10) \times 10^3}$$

$$\Rightarrow C_C = 0.729 \text{ }\mu\text{F}$$

7.15

$$a. \quad I_{CQ} = 1 \text{ mA}, \quad I_{BQ} = \frac{1}{120} = 0.00833 \text{ mA}$$

$$R_1 \parallel R_2 = (0.1)(1 + \beta)(R_E)$$

$$= (0.1)(121)(4) = 48.4 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(\text{on})} + (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$= (0.00833)(48.4) + 0.7 + (121)(0.00833)(4)$$

$$\frac{1}{R_1}(48.4)(12) = 5.13$$

$$R_1 = 113 \text{ k}\Omega$$

$$\frac{113R_2}{113 + R_2} = 48.4 \Rightarrow R_2 = 84.7 \text{ k}\Omega$$

$$b. \quad R_0 = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o$$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$r_o = \frac{80}{1} = 80 \text{ k}\Omega$$

$$R_0 = \frac{3.12}{121} \parallel 4 \parallel 80 = 0.0258 \parallel 4 \parallel 80$$

$$\Rightarrow R_0 = 25.6 \Omega$$

$$c. \quad \tau = (R_0 + R_L)C_{C2}$$

$$\tau = (0.0256 + 4) \times 10^3 \times 2 \times 10^{-8} = 8.05 \times 10^{-5} \text{ s}$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi(8.05 \times 10^{-5})} \Rightarrow f = 19.8 \text{ Hz}$$

7.16

$$(a) \quad \frac{5 - V_{SG}}{R_1} = K_p(V_{SG} + V_{TP})^2$$

$$5 - V_{SG} = (1)(1.2)(V_{SG} - 1.5)^2 = (1.2)(V_{SG}^2 - 3V_{SG} + 2.25)$$

$$1.2V_{SG}^2 - 2.6V_{SG} - 2.3 = 0 \Rightarrow V_{SG} = 2.84 \text{ V}$$

$$I_{DQ} = 1.8 \text{ mA}$$

$$V_{SDQ} = 10 - (1.8)(1.2 + 1.2) \Rightarrow V_{SDQ} = 5.68 \text{ V}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(1.8)} = 2.68 \text{ mA/V}$$

$$r_o = \infty$$

$$(b) \quad R_k = \frac{1}{g_m} = \frac{1}{2.68} = 0.373 \text{ k}\Omega$$

$$R_1 = 1.2 \parallel 0.373 = 0.285 \text{ k}\Omega$$

$$\text{For } C_{C1}, \quad \tau_{s1} = (285 + 200)(4.7 \times 10^{-6}) = 2.28 \text{ ms}$$

$$\text{For } C_{C2}, \quad \tau_{s2} = (1.2 \times 10^3 + 50 \times 10^3)(10^{-6}) = 51.2 \text{ ms}$$

$$(c) \quad C_{C2} \text{ dominates,}$$

$$f_{z-AB} = \frac{1}{2\pi\tau_{s2}} = \frac{1}{2\pi(51.2 \times 10^{-3})} = 3.1 \text{ Hz}$$

7.17

$$\text{Assume } V_{TN} = 1 \text{ V}, \quad k'_n = 80 \mu\text{A/V}^2, \quad \lambda = 0$$

Neglecting  $R_{S1} = 200 \Omega$ , Midband gain is:

$$|A_v| = g_m R_D$$

$$\text{Let } I_{DQ} = 0.2 \text{ mA}, \quad V_{DSQ} = 5 \text{ V}$$

$$\text{Then } R_D = \frac{9 - 5}{0.2} \Rightarrow R_D = 20 \text{ k}\Omega$$

We need

$$g_m = \frac{|A_v|}{R_D} = \frac{10}{20} = 0.5 \text{ mA/V}^2$$

and

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{DQ}}$$

or

$$0.5 = 2\sqrt{\left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.2)} \Rightarrow \frac{W}{L} = 7.81$$

$$\text{Let } R_1 + R_2 = \frac{9}{(0.2)I_{DQ}} = \frac{9}{(0.2)(0.2)} = 225 \text{ k}\Omega$$

$$I_{DQ} = 0.2 = \left(\frac{0.080}{2}\right)(7.81)(V_{GS} - 1)^2$$

$$\Rightarrow V_{GS} = 1.80 = \left(\frac{R_2}{R_1 + R_2}\right)(9) = \left(\frac{R_2}{225}\right)(9) \Rightarrow$$

$$R_2 = 45 \text{ k}\Omega, \quad R_1 = 180 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 180 \parallel 45 = 36 \text{ k}\Omega$$

$$\tau_1 = \frac{1}{2\pi f_1} = \frac{1}{-2\pi(200)} = 7.96 \times 10^{-4} \text{ s} = (R_{S1} + R_{TH})C_C$$

or

$$C_C = \frac{7.96 \times 10^{-4}}{(200 + 36 \times 10^3)} \Rightarrow C_C = 220 \mu\text{F}$$

$$\tau_2 = \frac{1}{2\pi f_2} = \frac{1}{2\pi(3 \times 10^3)} = 5.31 \times 10^{-5} \text{ s} = R_D C_L$$

or

$$C_L = \frac{5.31 \times 10^{-5}}{20 \times 10^3} \Rightarrow C_L = 2.66 \text{ nF}$$


7.18

$$a. \quad T(s) = \frac{R_2 + (1/s)C}{R_2 + (1/s)C + R_1}$$

$$T(s) = \frac{1 + sR_2C}{1 + s(R_1 + R_2)C}$$

$$\tau_A = R_2C, \quad \tau_B = (R_1 + R_2)C$$

b.

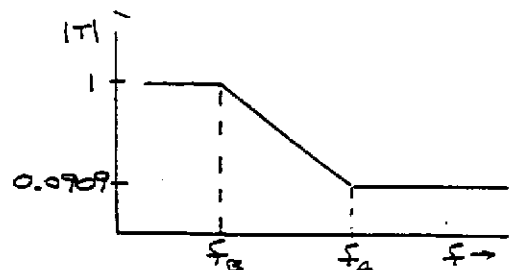

$$c. \quad \tau_A = R_2 C = (10^3)(100 \times 10^{-12}) = 10^{-7} \text{ s} = \tau_A$$

$$\tau_B = (R_1 + R_2)C = [10 + 1] \times 10^3 \times 100 \times 10^{-12}$$

$$= 1.1 \times 10^{-6} \text{ s} = \tau_B$$

$$f_A \approx \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(10^{-7})} \Rightarrow f_A = 1.59 \text{ MHz}$$

$$f_B \approx \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(1.1 \times 10^{-6})}$$

$$\Rightarrow f_B = 0.145 \text{ MHz}$$

7.19

$$I_{BQ} = \frac{10 - 0.7}{430 + (201)(2.5)} = 0.00997 \text{ mA}$$

$$I_{CQ} = (200)I_{BQ} = 1.99 \text{ mA}$$

$$r_\pi = \frac{(200)(0.026)}{1.99} = 2.61 \text{ k}\Omega$$

$$R_{ib} = 2.61 + (201)(2.5) = 505 \text{ k}\Omega$$

$$\tau_s = \frac{1}{2\pi f_L} = \frac{1}{2\pi(15)} = 0.0106 \text{ s}$$

$$= R_{eq} C_C = (0.5 + 505 \parallel 430) \times 10^3 C_C = 232.7 \times 10^3 C_C$$

Or

$$C_C = 4.56 \times 10^{-8} \text{ F} \Rightarrow 45.6 \text{ nF}$$

7.20

$$R_{TH} = R_1 \parallel R_2 = 1.2 \parallel 1.2 = 0.6 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \left( \frac{1.2}{1.2 + 1.2} \right) (5) = 2.5 \text{ V}$$

$$I_{BQ} = \frac{2.5 - 0.7}{0.6 + (101)(0.05)} = 0.319 \text{ mA}$$

$$I_{CQ} = 31.9 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{31.9} = 0.0815 \text{ k}\Omega$$

$$\tau_{C_{C1}} \gg \tau_{C_{C2}} \text{ and } f = \frac{1}{2\pi\tau} \text{ so that}$$

$$f_{3-dB}(C_{C1}) \ll f_{3-dB}(C_{C2})$$

Then, for  $f_{3-dB}(C_{C1}) \Rightarrow C_{C2}$  acts as an open and for $f_{3-dB}(C_{C2}) \Rightarrow C_{C1}$  acts as a short circuit.

$$f_{3-dB}(C_{C2}) = 25 \text{ Hz} = \frac{1}{2\pi\tau_2}, \text{ so that}$$

$$\tau_2 = \frac{1}{2\pi(25)} = 0.00637 \text{ s} = R_{eq} C_{C2}$$

$$\text{where } R_{eq} = R_L + R_E \left( \frac{r_\pi + R_1 \parallel R_2 \parallel R_S}{1 + \beta} \right)$$

$$= 10 + 50 \left( \frac{81.5 + 600 \parallel 300}{101} \right) = 10 + 50 \parallel 2.79 \Rightarrow$$

$$R_{eq} = 12.6 \Omega \Rightarrow C_{C2} = \frac{0.00637}{12.6} \Rightarrow C_{C2} = 506 \mu\text{F}$$

$$R_{ib} = r_\pi + (1 + \beta)R_E \text{ Assume } C_{C2} \text{ an open}$$

$$R_{ib} = 81.5 + (101)(50) = 5132 \Omega$$

$$\tau_1 = (100)\tau_2 = (100)(0.00637) = 0.637 \text{ s} = R_{eq1} C_{C1}$$

$$R_{eq1} = R_S + R_{TH} \parallel R_{ib} = 300 + 600 \parallel 5132 = 837 \Omega$$

$$\text{So } C_{C1} = \frac{0.637}{837} \Rightarrow C_{C1} = 761 \mu\text{F}$$

7.21

$$a. \quad I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.5}{0.5}} + 0.8 = 1.8 \text{ V}$$

$$R_S = \frac{-V_{GS} - (-5)}{0.5} = \frac{5 - 1.8}{0.5} \Rightarrow R_S = 6.4 \text{ k}\Omega$$

$$V_D = V_{DSQ} + V_S = 4 - 1.8 = 2.2 \text{ V}$$

$$R_D = \frac{5 - 2.2}{0.5} \Rightarrow R_D = 5.6 \text{ k}\Omega$$

$$(b) \quad g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$$

From Problem 7.20,

$$\tau_A = R_S C_S = (6.4 \times 10^3)(5 \times 10^{-6})$$

$$= 3.2 \times 10^{-2} \text{ s}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(3.2 \times 10^{-2})} \Rightarrow f_A = 4.97 \text{ Hz}$$

$$\tau_B = \left( \frac{R_S}{1 + g_m R_S} \right) C_S = \left[ \frac{6.4 \times 10^3}{1 + (1)(6.4)} \right] (5 \times 10^{-6})$$

$$= 4.32 \times 10^{-3} \text{ s}$$

$$f_B = \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(4.32 \times 10^{-3})} \Rightarrow f_B = 36.8 \text{ Hz}$$

c.

$$|A_v| = \frac{g_m R_D (1 + s R_S C_S)}{(1 + g_m R_S) \left[ 1 + s \left( \frac{R_S}{1 + g_m R_S} \right) C_S \right]}$$

As  $R_S$  becomes large

$$|A_v| \rightarrow \frac{g_m R_D (s R_S C_S)}{(g_m R_S) \left[ 1 + s \left( \frac{R_S}{g_m R_S} \right) C_S \right]}$$

$$A_v = \frac{(g_m R_D) \left[ s \left( \frac{1}{g_m} \right) C_S \right]}{1 + s \left( \frac{1}{g_m} \right) C_S}$$

The corner frequency  $f_B = \frac{1}{2\pi(1/g_m)C_S}$  and the corresponding  $f_A \rightarrow 0$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$$

$$f_B = \frac{1}{2\pi\left(\frac{1}{10^{-3}}\right)(5 \times 10^{-8})} \Rightarrow \underline{f_B = 31.8 \text{ Hz}}$$

7.22

$$a. \quad f_B = \frac{1}{2\pi\tau_B}$$

$$\text{and } \tau_B = \frac{R_E(R_S + r_\pi)C_E}{R_S + r_\pi + (1 + \beta)R_E}$$

$$\text{For } R_S = 0 \quad \tau_B = \frac{R_E r_\pi C_E}{r_\pi + (1 + \beta)R_E}$$

$$I_{EQ} = \frac{-0.7 - (-10)}{5} = 1.86 \text{ mA}$$

$$\beta = 75 \Rightarrow I_{CQ} = 1.84 \text{ mA}$$

$$\beta = 125 \Rightarrow I_{CQ} = 1.85 \text{ mA}$$

For  $f_B \leq 200 \text{ Hz}$

$$\Rightarrow \tau_B \geq \frac{1}{2\pi(200)} = 0.796 \text{ ms}$$

$r_\pi \propto \beta$  so smallest  $\tau_B$  will occur for smallest  $\beta$ .

$$\beta = 75; \quad r_\pi = \frac{(75)(0.026)}{1.84} = 1.06 \text{ k}\Omega$$

$$0.796 \times 10^{-3} = \frac{(5 \times 10^3)(1.06)C_E}{1.06 + (76)(5)}$$

$$\Rightarrow \underline{C_E = 57.2 \text{ }\mu\text{F}}$$

$$b. \quad \text{For } \beta = 125; \quad r_\pi = \frac{(125)(0.026)}{1.85} = 1.76 \text{ k}\Omega$$

$$\tau_B = \frac{(5 \times 10^3)(1.76)(57.2 \times 10^{-6})}{1.76 + (126)(5)} = 0.797 \text{ ms}$$

$$f_B = \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(0.797 \times 10^{-3})}$$

$$\Rightarrow \underline{f_B = 199.7 \text{ Hz}} \text{ Essentially independent of } \beta.$$

$$\tau_A = R_E C_E = (5 \times 10^3)(57.2 \times 10^{-6}) = 0.286 \text{ sec}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(0.286)}$$

$$\Rightarrow \underline{f_A = 0.556 \text{ Hz}} \text{ Independent of } \beta.$$

7.23

a. Expression for the voltage gain is the same as Equation (7.58) with  $R_S = 0$ .

$$b. \quad \tau_A = R_E C_E$$

$$\tau_B = \frac{R_E r_\pi C_E}{r_\pi + (1 + \beta)R_E}$$

7.24

$$\tau_H = (R_L \parallel R_C)C_L = (10 \parallel 5) \times 10^3 \times 15 \times 10^{-12}$$

$$\tau_H = 5 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi(5 \times 10^{-8})} \Rightarrow \underline{f_H = 3.18 \text{ MHz}}$$

$$I_{EQ} = \frac{10 - 0.7}{10} = 0.93 \text{ mA}, \quad I_{CQ} = 0.921 \text{ mA}$$

$$g_m = \frac{0.921}{0.026} = 35.4 \text{ mA/V}$$

$$A_v = g_m(R_C \parallel R_L) = 35.4(5 \parallel 10) \Rightarrow \underline{A_v = 118}$$

7.25

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{166}{166 + 234}\right)(10) = 4.15 \text{ V}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n(V_{GS} - V_{TN})^2$$

$$4.15 - V_{GS} = (0.5)(0.5)(V_{GS}^2 - 4V_{GS} + 4)$$

$$0.25V_{GS}^2 - 3.15 = 0 \Rightarrow V_{GS} = 3.55 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(3.55 - 2)$$

$$g_m = 1.55 \text{ mA/V}$$

$$R_0 = R_S \parallel \frac{1}{g_m} = 0.5 \parallel \frac{1}{1.55} = 0.5 \parallel 0.645$$

$$R_0 = 0.282 \text{ k}\Omega$$

$$\tau = (R_0 \parallel R_L)C_L \text{ and } f_H = \frac{1}{2\pi\tau}$$

$$\beta\omega \approx f_H = 5 \text{ MHz}$$


$$\Rightarrow \tau = \frac{1}{2\pi(5 \times 10^6)} = 3.18 \times 10^{-8} \text{ s}$$

$$C_L = \frac{\tau}{R_0 \parallel R_L} = \frac{3.18 \times 10^{-8}}{(0.282 \parallel 4) \times 10^3}$$


$$\Rightarrow \underline{C_L = 121 \text{ pF}}$$

7.26


(a) Low-frequency

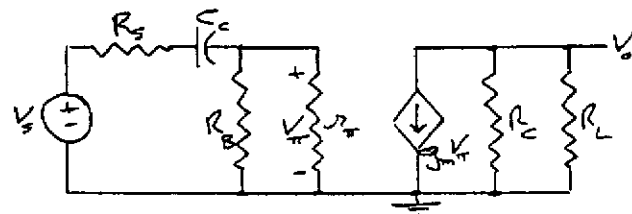


Mid-Band

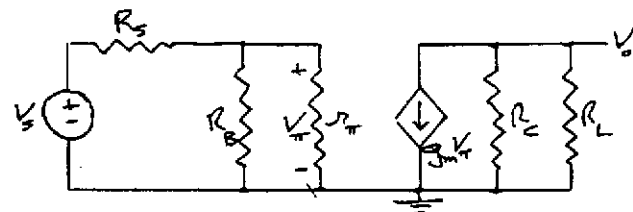

High-frequency

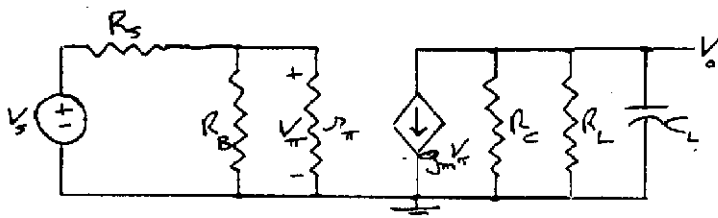

(b)

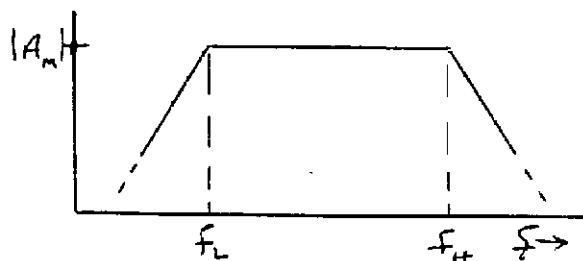

$$(c) I_{BQ} = \frac{12 - 0.7}{1 \text{ M}\Omega} = 11.3 \mu\text{A}$$

$$I_{CQ} = 11.3 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{1.13} = 2.3 \text{ k}\Omega$$

$$g_m = \frac{1.13}{0.026} = 43.46 \text{ mA/V}$$

$$A_m = \frac{V_o}{V_i}(\text{midband}) = -g_m(R_C \parallel R_L) \left( \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s} \right)$$

$$= -(43.46)(5.1 \parallel 500) \left( \frac{1000 \parallel 2.3}{1000 \parallel 2.3 + 1} \right)$$

$$= -(43.46)(5.05) \left( \frac{2.29}{2.29 + 1} \right) \Rightarrow |A_m| = 153$$

$$|A_m|_{dB} = 43.7 \text{ dB}$$

$$f_L = \frac{1}{2\pi\tau_L}, \quad \tau_L = (R_s + R_B \parallel r_\pi)C_C$$

or

$$\tau_L = (1 + 1000 \parallel 2.3) \times 10^3 (10 \times 10^{-6}) \Rightarrow$$


$$\tau_L = 3.29 \times 10^{-2} \text{ s} \Rightarrow f_L = 4.84 \text{ Hz}$$

$$f_H = \frac{1}{2\pi\tau_H}, \quad \tau_H = (R_C \parallel R_L)C_L \Rightarrow$$

$$\tau_H = (5.1 \parallel 500) \times 10^3 (10 \times 10^{-12}) = 5.05 \times 10^{-8} \text{ s}$$

$$\Rightarrow f_H = 3.15 \text{ MHz}$$

7.27

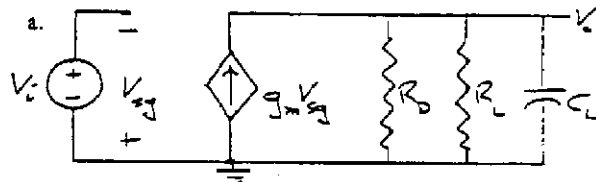

$$V_o = (g_m V_{sg}) \left( R_D \parallel R_L \parallel \frac{1}{sC_L} \right)$$

$$V_{sg} = -V_i$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = -g_m \left( R_D \parallel R_L \parallel \frac{1}{sC_L} \right)$$

$$= -g_m \left[ \frac{R_D \parallel R_L \cdot \frac{1}{sC_L}}{R_D \parallel R_L + \frac{1}{sC_L}} \right]$$

$$A_v(s) = -g_m(R_D \parallel R_L) \cdot \frac{1}{1 + s(R_D \parallel R_L)C_L}$$

$$b. \quad \tau = (R_D \parallel R_L)C_L$$

$$c. \quad \tau = (10 \parallel 20) \times 10^3 \times 10 \times 10^{-12}$$

$$\Rightarrow \tau = 6.67 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(6.67 \times 10^{-8})}$$

$$\Rightarrow f_H = 2.39 \text{ MHz}$$

From Example 7.6,  $g_m = 0.705 \text{ mA/V}$ 

$$|A_v| = g_m(R_D \parallel R_L) = (0.705)(10 \parallel 20)$$

$$\Rightarrow |A_v| = 4.7$$

7.31

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1}{0.026} = 38.5 \text{ mA/V}$$

$$f_T = \frac{38.5 \times 10^{-3}}{2\pi(10 + 2) \times 10^{-12}}$$

$$f_T = 511 \text{ MHz}$$

$$f_B = \frac{f_T}{\beta} = \frac{511}{120} \Rightarrow f_B = 4.26 \text{ MHz}$$

7.32

$$f_\beta = \frac{f_T}{\beta} = \frac{5000 \text{ MHz}}{150} \Rightarrow \underline{f_\beta = 33.3 \text{ MHz}}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{0.5}{0.026} = 19.2 \text{ mA/V}$$

$$5 \times 10^9 = \frac{19.2 \times 10^3}{2\pi(C_\pi + 0.15) \times 10^{-12}}$$

$$C_\pi + 0.15 = \frac{19.2 \times 10^3}{2\pi(10^{-12})(5 \times 10^9)} = 0.611 \text{ pF}$$

$$\underline{C_\pi = 0.461 \text{ pF}}$$

7.33

$$\text{a. } f_\beta = \frac{f_T}{\beta} = \frac{2000 \text{ MHz}}{150} = 13.3 \text{ MHz} = f_\beta$$

$$\text{b. } h_{fe} = \frac{150}{1 + j(f/f_\beta)}$$

$$|h_{fe}| = \frac{150}{\sqrt{1 + (f/f_\beta)^2}} = 10$$

$$1 + \left(\frac{f}{f_\beta}\right)^2 = \left(\frac{150}{10}\right)^2 = 225$$

$$f = f_\beta \cdot \sqrt{224} = (13.3) \cdot \sqrt{224}$$

$$\Rightarrow \underline{f = 199 \text{ MHz}}$$

7.34

(a)  $V_o = -g_m V_\pi R_L$  where

$$V_\pi = \frac{r_\pi \parallel \frac{1}{sC_1}}{r_\pi \parallel \frac{1}{sC_1} + r_b} \cdot V_i = \frac{\frac{r_\pi}{1 + s\tau_\pi C_1}}{\frac{r_\pi}{1 + s\tau_\pi C_1} + r_b} \cdot V_i$$

$$= \frac{r_\pi}{r_\pi + r_b + s\tau_\pi r_b C_1} \cdot V_i = \left(\frac{r_\pi}{r_\pi + r_b}\right) \left(\frac{1}{1 + s(r_b \parallel r_\pi)C_1}\right) \cdot V_i$$

So

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = -g_m R_L \left(\frac{r_\pi}{r_\pi + r_b}\right) \left(\frac{1}{1 + s(r_b \parallel r_\pi)C_1}\right)$$

(b) Midband gain:

$$r_\pi = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

(i) For  $r_b = 100 \Omega$ 

$$A_{v1} = -(38.46)(4) \left(\frac{2.6}{2.6 + 0.1}\right) \Rightarrow \underline{A_{v1} = -148.1}$$

(ii) For  $r_b = 500 \Omega$ 

$$A_{v2} = -(38.46)(4) \left(\frac{2.6}{2.6 + 0.5}\right) \Rightarrow \underline{A_{v2} = -129.0}$$

$$\text{(c) } f_{3-dB} = \frac{1}{2\pi\tau}, \quad \tau = (r_b \parallel r_\pi)C_1$$

(i) For  $r_b = 100 \Omega$ 

$$\tau_1 = (0.1 \parallel 2.6) \times 10^3 (2.2 \times 10^{-12}) = 2.12 \times 10^{-10} \text{ s}$$

$$\Rightarrow \underline{f_{3-dB} = 751 \text{ MHz}}$$

(ii) For  $r_b = 500 \Omega$ 


$$\tau_2 = (0.5 \parallel 2.3) \times 10^3 (2.2 \times 10^{-12}) = 9.04 \times 10^{-10} \text{ s}$$

$$\underline{f_{3-dB} = 176 \text{ MHz}}$$

7.35

$$\text{a. } C_M = C_\pi(1 + g_m R_L)$$

b.

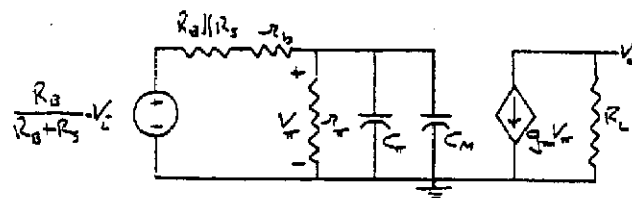

$$V_o = -g_m V_\pi R_L \quad \text{Let } C_\pi + C_M = C_i$$

$$V_\pi = \frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi \parallel \frac{1}{sC_i} + R_B \parallel R_S + r_b} \cdot \left(\frac{R_B}{R_B + R_S}\right) V_i$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)}$$

$$= -g_m R_L \left(\frac{R_B}{R_B + R_S}\right) \left[ \frac{\frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi + \frac{1}{sC_i}}}{\frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi + \frac{1}{sC_i}} + R_B \parallel R_S + r_b} \right]$$

$$= -g_m R_L \left(\frac{R_B}{R_B + R_S}\right) \times \left[ \frac{r_\pi}{r_\pi + (1 + s\tau_\pi C_i)(R_B \parallel R_S + r_b)} \right]$$

$$\text{Let } R_{eq} = (R_B \parallel R_S + r_b)$$


$$A_v(s) = -\beta R_L \left(\frac{R_B}{R_B + R_S}\right)$$

$$\times \left[ \frac{1}{(r_\pi + R_{eq})[1 + s(r_\pi \parallel R_{eq})C_i]} \right]$$

$$A_v(s) = \frac{-\beta R_L}{r_\pi + R_{eq}} \cdot \left(\frac{R_B}{R_B + R_S}\right) \cdot \frac{1}{1 + s(r_\pi \parallel R_{eq})C_i}$$

$$\text{c. } \underline{f_H = \frac{1}{2\pi(r_\pi \parallel R_{eq})C_i}}$$

7.36

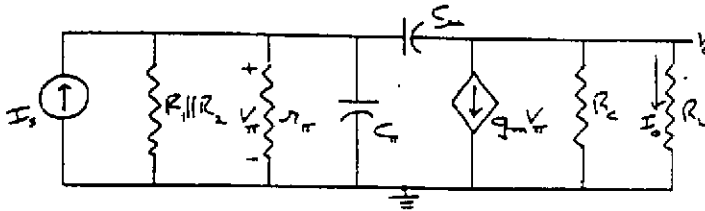High Freq.  $\Rightarrow C_{C1}, C_{C2}, C_E \rightarrow$  short circuits

$$g_m = \frac{I_{CQ}}{V_T} = \frac{5}{0.026} = 192 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow 250 \times 10^6 = \frac{192 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = 122 \text{ pF} \Rightarrow C_\mu = 5 \text{ pF}, C_\pi = 117 \text{ pF}$$

$$C_M = C_\mu(1 + g_m(R_C || R_L))$$

$$= 5[1 + (192)(1 || 1)] \Rightarrow C_M = 485 \text{ pF}$$

$$C_i = C_\pi + C_M = 117 + 485 = 602 \text{ pF}$$

$$r_\pi = \frac{(200)(0.026)}{5} = 1.04 \text{ k}\Omega$$

$$R_{eq} = R_1 || R_2 || r_\pi = 5 || 1.04 = 0.861 \text{ k}\Omega$$

$$r = R_{eq} \cdot C_i = (0.861 \times 10^3)(602 \times 10^{-12})$$

$$= 5.18 \times 10^{-7} \text{ s}$$

$$f = \frac{1}{2\pi r} = \frac{1}{2\pi(5.18 \times 10^{-7})} \Rightarrow f = 307 \text{ kHz}$$

7.37

$$R_{TH} = R_1 || R_2 = 60 || 5.5 = 5.04 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5.5}{5.5 + 60} \right) (15) = 1.26 \text{ V}$$

$$I_{BQ} = \frac{1.26 - 0.7}{5.04 + (101)(0.2)} = 0.0222 \text{ mA}$$

$$I_{CQ} = 2.22 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{2.22} = 1.17 \text{ k}\Omega$$

$$g_m = \frac{2.22}{0.026} = 85.4 \text{ mA/V}$$

Lower 3 - dB frequency:

$$r_L = R_{eq} \cdot C_{C1}$$

$$R_{eq} = R_S + R_1 || R_2 || r_\pi$$

$$= 2 + 60 || 5.5 || 1.17 = 2.95 \text{ k}\Omega$$

$$r_L = (2.95 \times 10^3)(0.1 \times 10^{-6}) = 2.95 \times 10^{-4} \text{ s}$$

$$f_L = \frac{1}{2\pi r_L} = \frac{1}{2\pi(2.95 \times 10^{-4})} \Rightarrow f_L = 540 \text{ Hz}$$

Upper 3 - dB frequency:

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow 400 \times 10^6 = \frac{85.4 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = 34 \text{ pF}; C_\mu = 2 \text{ pF} \Rightarrow C_\pi = 32 \text{ pF}$$

$$C_M = C_\mu(1 + g_m R_C) = 2(1 + (85.4)(4))$$

$$\Rightarrow C_M = 685 \text{ pF}$$

$$C_i = C_\pi + C_M = 32 + 685 = 717 \text{ pF}$$

$$R_{eq} = R_S || R_1 || R_2 || r_\pi = 2 || 60 || 5.5 || 1.17$$

$$= 0.644 \text{ k}\Omega$$

$$r = R_{eq} \cdot C_i = (0.644 \times 10^3)(717 \times 10^{-12})$$

$$= 4.62 \times 10^{-7} \text{ s}$$

$$f_H = \frac{1}{2\pi r} \Rightarrow f_H = 344 \text{ kHz}$$

7.38

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$g_m = 2\sqrt{K_n I_D}, K_n = (15)\left(\frac{40}{10}\right) = 60 \mu\text{A/V}^2$$

$$g_m = 2\sqrt{(60)(100)} = 155 \mu\text{A/V}^2$$

$$f_T = \frac{155 \times 10^{-6}}{2\pi(0.5 + 0.05) \times 10^{-12}} \Rightarrow f_T = 44.9 \text{ MHz}$$

7.39

$$a. C_M = C_{gs}(1 + g_m(r_o || R_D))$$

$$C_M = 5[1 + (3)(15 || 10)] \Rightarrow C_M = 95 \text{ pF}$$

$$b. r = (r_o)(C_{gs} + C_M)$$

$$r = (10 \times 10^3)(50 + 95) \times 10^{-12} = 1.45 \times 10^{-6} \text{ s}$$

$$f = \frac{1}{2\pi r} = \frac{1}{2\pi(1.45 \times 10^{-6})}$$

$$\Rightarrow f = 110 \text{ kHz}$$

7.40

$$f_T = \frac{g_m}{2\pi(C_{gs,T} + C_{gd,T})} \quad (\text{Eq. 7.90})$$

$$\text{Let } C_{gd,T} = 0 \text{ and } C_{gs,T} = \left(\frac{2}{3}\right)(WLC_{ox})$$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{\left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$\text{So } f_T = \frac{2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_D}}{2\pi\left(\frac{2}{3}\right)(WLC_{ox})}$$

$$= \frac{3}{2\pi L} \cdot \frac{\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_D}}{WC_{ox}}$$

$$f_T = \frac{3}{2\pi L} \cdot \sqrt{\frac{\mu_n I_D}{2WC_{ox}L}}$$

7.41

(a)  $g'_m = \frac{g_m}{1 + g_m r_s}$

$$g_m = 2K_n(V_{GS} - V_{TN})$$

$$K_n = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right) = \left(\frac{(400)(7.25 \times 10^{-9})}{2}\right) (10)$$

$$K_n = 1.45 \times 10^{-4} \text{ mA/V}^2$$

For  $V_{GS} = 5 \text{ V}$ 

$$g_m = 2(1.45 \times 10^{-4})(5 - 0.65) = 1.26 \times 10^{-3}$$

$$g'_m = (0.80)g_m = 1.01 \times 10^{-3}$$

$$1.01 \times 10^{-3} = \frac{1.26 \times 10^{-3}}{1 + (1.26 \times 10^{-3})r_s}$$

$$1 + (1.26 \times 10^{-3})r_s = 1.25$$

$$\Rightarrow r_s = 198 \Omega$$

b. For  $V_{GS} = 3 \text{ V}$ 

$$g_m = 2(1.45 \times 10^{-4})(3 - 0.65) = 0.6815 \times 10^{-3}$$


$$g'_m = \frac{0.6815 \times 10^{-3}}{1 + (0.6815 \times 10^{-3})(198)}$$

$$g'_m = 0.60 \times 10^{-3} \text{ A/V}$$

Reduced by  $\approx 12\%$ 

7.42

a.

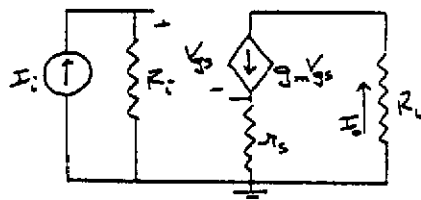


$$I_0 = g_m V_{gs} \text{ and } V_{gs} = I_i R_i - g_m V_{gs} r_s$$

$$\text{so } V_{gs} = \frac{I_i R_i}{1 + g_m r_s}$$

$$\text{Then } A_i = \frac{I_0}{I_i} = \frac{g_m R_i}{1 + g_m r_s}$$

b. As an approximation, consider

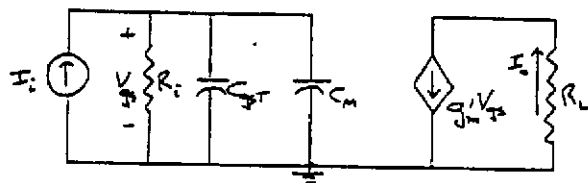

In this case

$$A_i = \frac{I_0}{I_i} = g'_m R_i \cdot \frac{1}{1 + s R_i (C_{gsT} + C_M)}$$

$$\text{where } C_M = C_{gsT}(1 + g'_m R_L) \text{ and } g'_m = \frac{g_m}{1 + g_m r_s}$$

c. As  $r_s$  increases,  $C_M$  decreases, so the bandwidth increases, but the current gain magnitude decreases.

7.43


$$V_{GS} = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{225}{225 + 500}\right)(10)$$

$$V_{GS} = 3.10 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1)(3.10 - 2)$$

$$g_m = 2.2 \text{ mA/V}$$

a.

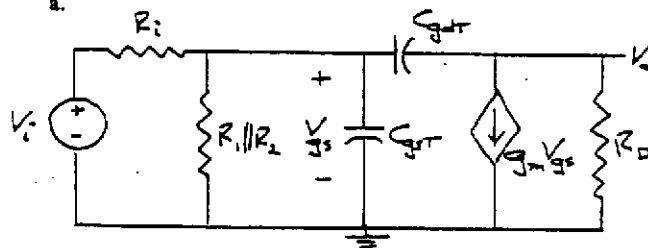

$$b. \quad C_M = C_{gsT}(1 + g_m R_D) = (1)[1 + (2.2)(5)]$$

$$C_M = 12 \text{ pF}$$

$$c. \quad \tau = (R_i \parallel R_1 \parallel R_2)(C_{gsT} + C_M)$$

$$R_i \parallel R_1 \parallel R_2 = 1 \parallel 500 \parallel 225 = 1 \parallel 155 = 0.994 \text{ k}\Omega$$

$$\tau = (0.994 \times 10^3)(5 + 12) \times 10^{-12} = 1.69 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(1.69 \times 10^{-8})} \Rightarrow f_H = 9.42 \text{ MHz}$$

$$A_v = \frac{-g_m V_{gs} R_D}{V_i} \text{ and}$$

$$V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \cdot V_i = \frac{155}{155 + 1} \cdot V_i = 0.994 V_i$$

$$A_v = -(2.2)(5)(0.994) \Rightarrow A_v = -10.9$$

7.44

$$R_{TH} = R_1 \parallel R_2 = 33 \parallel 22 = 13.2 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (5) = \left( \frac{22}{22 + 33} \right) (5) = 2 \text{ V}$$

$$I_{BQ} = \frac{2 - 0.7}{13.2 + (121)(4)} = 0.00261 \text{ mA}$$

$$I_{CQ} = 0.314 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{0.314} = 9.94 \text{ k}\Omega$$

$$g_m = \frac{0.314}{0.026} = 12.1 \text{ mA/V}$$

$$r_o = \frac{100}{0.314} = 318 \text{ k}\Omega$$

$$a. \quad f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{12.1 \times 10^{-3}}{2\pi(600 \times 10^3)}$$

$$C_\pi + C_\mu = 3.21 \text{ pF}; C_\mu = 1 \text{ pF} \Rightarrow C_\pi = 2.21 \text{ pF}$$

$$C_M = C_\mu[1 + g_m(r_o \parallel R_C \parallel R_L)]$$

$$= (1)[1 + (12.1)(318 \parallel 4 \parallel 5)]$$

$$C_M = 27.7 \text{ pF}$$

$$b. \quad \tau = R_{eq}(C_\pi + C_M)$$

$$R_{eq} = R_1 \parallel R_2 \parallel R_S \parallel r_\pi = 33 \parallel 22 \parallel 2 \parallel r_\pi$$

$$= 1.74 \parallel 9.94 \text{ k}\Omega \Rightarrow R_{eq} = 1.48 \text{ k}\Omega$$

$$\tau = (1.48 \times 10^3)(2.21 + 27.7) \times 10^{-12}$$

$$\tau = 4.43 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(4.43 \times 10^{-8})}$$

$$\Rightarrow f_H = 3.59 \text{ MHz}$$

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_\pi = \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) V_i$$

$$R_1 \parallel R_2 \parallel r_\pi = 33 \parallel 22 \parallel 9.94 = 5.67 \text{ k}\Omega$$

$$V_\pi = \left( \frac{5.67}{5.67 + 2} \right) V_i = 0.739 V_i$$

$$r_o \parallel R_C \parallel R_L = 318 \parallel 4 \parallel 5 = 2.18 \text{ k}\Omega$$

$$A_v = -(12.1)(0.739)(2.18)$$

$$\underline{A_v = -19.5}$$

7.45

$$R_{TH} = R_1 \parallel R_2 = 40 \parallel 5 = 4.44 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5}{5 + 40} \right) (10) = 1.11 \text{ V}$$

$$I_{BQ} = \frac{1.11 - 0.7}{4.44 + (121)(0.5)} = 0.00631 \text{ mA}$$

$$I_{CQ} = 0.758 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{0.758} = 4.12 \text{ k}\Omega$$

$$g_m = \frac{0.758}{0.026} = 29.2 \text{ mA/V}$$

$$r_o = \infty$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{29.2 \times 10^{-3}}{2\pi(250 \times 10^3)}$$

$$C_\pi + C_\mu = 18.6 \text{ pF}; C_\mu = 3 \text{ pF} \Rightarrow C_\pi = 15.6 \text{ pF}$$

$$a. \quad C_M = C_\mu[1 + g_m(R_C \parallel R_L)]$$

$$C_M = 3[1 + (29.2)(5 \parallel 2.5)] \Rightarrow C_M = 149 \text{ pF}$$

For upper frequency:

$$\tau_H = R_{eq}(C_\pi + C_M)$$

$$R_{eq} = r_\pi \parallel R_1 \parallel R_2 \parallel R_S = 4.12 \parallel 40 \parallel 5 \parallel 0.5$$

$$R_{eq} = 0.405 \text{ k}\Omega$$

$$\tau_H = (0.405 \times 10^3)(15.6 + 149) \times 10^{-12}$$

$$= 6.67 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} \Rightarrow f_H = 2.39 \text{ MHz}$$

For lower frequency:

$$\tau_L = R_{eq}C_{C1}$$


$$R_{eq} = R_S \parallel R_1 \parallel R_2 \parallel r_\pi = 0.5 + 40 \parallel 5 \parallel 4.12$$

$$R_{eq} = 2.64 \text{ k}\Omega$$

$$\tau_L = (2.64 \times 10^3)(4.7 \times 10^{-8}) = 1.24 \times 10^{-2} \text{ s}$$

$$f_L = \frac{1}{2\pi\tau_L} \Rightarrow f_L = 12.8 \text{ Hz}$$

b.

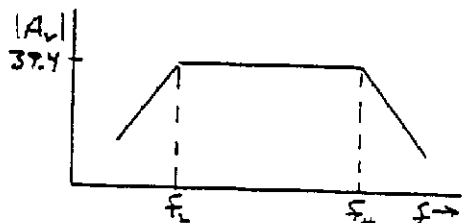

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_\pi = \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) V_i$$

$$V_\pi = \left( \frac{2.14}{2.14 + 0.5} \right) V_i = 0.8106 V_i$$

$$|A_v| = (29.2)(0.8106)(5 \parallel 2.5)$$

$$\underline{|A_v| = 39.4}$$

7.46

$$I_D = K_p(V_{SG} + V_{TP})^2 = \frac{9 - V_{SG}}{R_S}$$

$$(2)(1.2)(V_{SG}^2 - 4V_{SG} + 4) = 9 - V_{SG}$$

$$2.4V_{SG}^2 - 8.6V_{SG} + 0.6 = 0$$

$$V_{SG} = \frac{8.6 \pm \sqrt{(8.6)^2 - 4(2.4)(0.6)}}{2(2.4)}$$

$$V_{SG} = 3.51 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(2)(3.51 - 2)$$

$$g_m = 6.04 \text{ mA/V}$$

$$I_D = (2)(3.51 - 2)^2 = 4.56 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(4.56)} \Rightarrow r_o = 21.9 \text{ k}\Omega$$

$$a. \quad C_M = C_{gsT}(1 + g_m(r_o \parallel R_D))$$

$$C_M = (1)[1 + (6.04)(21.9 \parallel 1)] \Rightarrow C_M = 6.78 \text{ pF}$$

$$b. \quad \tau_H = (R_i \parallel R_G)(C_{gsT} + C_M)$$

$$\tau_H = (2 \parallel 100) \times 10^3 (10 + 6.78) \times 10^{-12}$$

$$\tau_H = 3.29 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} \Rightarrow f_H = 4.84 \text{ MHz}$$

$$V_o = -g_m(r_o \parallel R_D) \cdot V_{gs}$$

$$V_{gs} = \left( \frac{R_G}{R_G + R_i} \right) V_i = \left( \frac{100}{102} \right) V_i$$

$$A_v = -(6.04) \left( \frac{100}{102} \right) (21.9 \parallel 1)$$

$$A_v = -5.66$$

7.47

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left( \frac{22}{22 + 8} \right) (20) - 10$$

$$V_G = 4.67 \text{ V}$$

$$I_D = \frac{10 - V_{SG} - 4.67}{R_S} = K_p(V_{SG} + V_{TP})^2$$

$$5.33 - V_{SG} = (1)(0.5)(V_{SG}^2 - 4V_{SG} + 4)$$

$$0.5V_{SG}^2 - V_{SG} - 3.33 = 0$$

$$V_{SG} = \frac{1 \pm \sqrt{1 + 4(0.5)(3.33)}}{2(0.5)} \Rightarrow V_{SG} = 3.77 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(3.77 - 2)$$

$$g_m = 3.54 \text{ mA/V}$$

$$b. \quad C_M = C_{gsT}(1 + g_m(R_D \parallel R_L))$$

$$C_M = (3)[1 + (3.54)(2 \parallel 5)] \Rightarrow C_M = 18.2 \text{ pF}$$

$$a. \quad \tau = R_{eq}(C_{gsT} + C_M)$$

$$R_{eq} = R_i \parallel R_1 \parallel R_2 = 0.5 \parallel 8 \parallel 22 = 0.461 \text{ k}\Omega$$

$$\tau = (0.461 \times 10^3)(15 + 18.2) \times 10^{-12}$$

$$= 1.53 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} \Rightarrow f_H = 10.4 \text{ MHz}$$

$$c. \quad V_o = -g_m V_{gs}(R_D \parallel R_L)$$

$$V_{gs} = \left( \frac{R_i \parallel R_2}{R_i \parallel R_2 + R_i} \right) V_i = \left( \frac{5.87}{5.87 + 0.5} \right) V_i$$

$$\Rightarrow V_{gs} = (0.9215) V_i$$

$$A_v = -(3.54)(0.9215)(2 \parallel 5)$$

$$\Rightarrow A_v = -4.66$$

7.48

$$I_E = 0.5 \text{ mA} \Rightarrow I_{CQ} = \left( \frac{100}{101} \right) (0.5) = 0.495 \text{ mA}$$

$$g_m = \frac{0.495}{0.026} = 19.0 \text{ mA/V}$$

$$\tau_r = \frac{(100)(0.026)}{0.495} = 5.25 \text{ k}\Omega$$

$$a. \quad \text{Input: From Eq. 7.107b}$$

$$\begin{aligned} \tau_{Pr} &= \left[ \frac{r_\pi}{1 + \beta} \parallel R_E \parallel R_S \right] C_r \\ &= \left[ \frac{5.25}{101} \parallel 0.5 \parallel 0.05 \right] \times 10^3 \times 10 \times 10^{-12} \\ &= 2.43 \times 10^{-10} \text{ s} \end{aligned}$$


$$f_{Hr} = \frac{1}{2\pi\tau_{Pr}} \Rightarrow f_{Hr} = 656 \text{ MHz}$$

$$\text{Output: From Eq. 7.108b}$$

$$\begin{aligned} \tau_{P\mu} &= (R_B \parallel R_L) C_\mu = (100 \parallel 1) \times 10^3 \times 10^{-12} \\ &= 9.90 \times 10^{-10} \text{ s} \end{aligned}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{P\mu}} \Rightarrow f_{H\mu} = 161 \text{ MHz}$$

b.

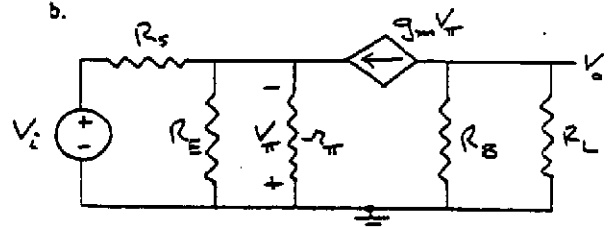

$$V_0 = -g_m V_\pi (R_E \parallel R_L)$$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{R_E} + \frac{V_i - (-V_\pi)}{R_S} = 0$$

$$V_\pi \left[ g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{R_S} \right] = \frac{-V_i}{R_S}$$

$$V_\pi \left[ 19 + \frac{1}{5.25} + \frac{1}{0.5} + \frac{1}{0.05} \right] = \frac{-V_i}{0.05}$$

$$V_\pi (41.19) = -V_i (20)$$

$$V_\pi = -(0.4856) V_i$$

$$\frac{V_0}{V_i} = -(19)(-0.4856)(100 \parallel 1)$$

$$A_v = 9.14$$

$$c. \quad \tau = C_L (R_L \parallel R_B) = (15 \times 10^{-12})(1 \parallel 100) \times 10^3$$

$$\tau = 1.485 \times 10^{-8} \text{ s}$$

$$f = \frac{1}{2\pi\tau} \rightarrow f = 10.7 \text{ MHz}$$

Since  $f < f_{H\mu} \Rightarrow 3\text{dB freq. dominated by } C_L$ .

7.49

$$I_{EQ} = \frac{20 - 0.7}{10} = 1.93 \text{ mA}$$

$$I_{CQ} = \left( \frac{100}{101} \right) (1.93) = 1.91 \text{ mA}$$

$$g_m = \frac{1.91}{0.026} = 73.5 \text{ mA/V}$$

$$r_\pi = \frac{(100)(0.026)}{1.91} = 1.36 \text{ k}\Omega$$

a. Input:

$$\tau_{P\pi} = \left[ \frac{r_\pi}{1 + \beta} \parallel R_E \parallel R_S \right] \cdot C_\pi$$

$$= \left[ \frac{1.36}{101} \parallel 10 \parallel 1 \right] \times 10^3 \times 10 \times 10^{-12}$$

$$\tau_{P\pi} = 1.327 \times 10^{-10} \text{ s}$$

$$f_{P\pi} = \frac{1}{2\pi\tau_{P\pi}} \rightarrow f_{P\pi} = 1.20 \text{ GHz}$$

output:

$$\tau_{P\mu} = (R_C \parallel R_L) C_\mu = (6.5 \parallel 5) \times 10^3 \times 10^{-12}$$

$$\tau_{P\mu} = 2.826 \times 10^{-9} \text{ s}$$

$$f_{P\mu} = \frac{1}{2\pi\tau_{P\mu}} \rightarrow f_{P\mu} = 56.3 \text{ MHz}$$

$$b. \quad V_0 = -g_m V_\pi (R_C \parallel R_L)$$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{R_E} + \frac{V_i - (-V_\pi)}{R_S} = 0$$

$$V_\pi \left( g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{R_S} \right) = -\frac{V_i}{R_S}$$

$$V_\pi \left[ 73.5 + \frac{1}{1.36} + \frac{1}{10} + \frac{1}{1} \right] = \frac{-V_i}{(1)}$$

$$V_\pi (75.34) = -V_i \Rightarrow V_\pi = -(0.01327) V_i$$

$$V_0 = -(73.5)(-0.01327)(6.5 \parallel 5) V_i$$

$$A_v = 2.76$$

$$c. \quad \tau = C_L (R_L \parallel R_C) = (15 \times 10^{-12})(6.5 \parallel 5) \times 10^3$$

$$\tau = 4.24 \times 10^{-8} \text{ s}$$

$$f = \frac{1}{2\pi\tau} \rightarrow f = 3.75 \text{ MHz}$$

Since  $f < f_{P\mu}$ , 3dB frequency is dominated by  $C_L$ .

7.50

$$V_{GS} + I_D R_S = 5$$

$$I_D = \frac{5 - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$5 - V_{GS} = (3)(10)(V_{GS}^2 - 2V_{GS} + 1)$$

$$30V_{GS}^2 - 59V_{GS} + 25 = 0$$

$$V_{GS} = \frac{59 \pm \sqrt{(59)^2 - 4(30)(25)}}{2(30)} \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(3)(1.35 - 1)$$


$$g_m = 2.1 \text{ mA/V}$$

On the output:

$$\tau_{P\mu} = (R_D \parallel R_L) C_{gdT} = (5 \parallel 4) \times 10^3 \times 4 \times 10^{-12}$$

$$\tau_{P\mu} = 8.89 \times 10^{-9} \text{ s}$$
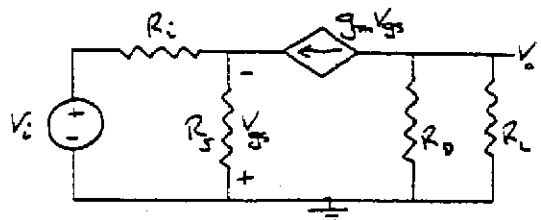
$$f_{P\mu} = \frac{1}{2\pi\tau_{P\mu}} \rightarrow f_{P\mu} = 17.9 \text{ MHz}$$



$$V_0 = -g_m V_{gs} (R_D \parallel R_L)$$

$$g_m V_{gs} + \frac{V_{gs}}{R_S} + \frac{V_i - (-V_{gs})}{R_i} = 0$$

$$V_{gs} \left( g_m + \frac{1}{R_S} + \frac{1}{R_i} \right) = -\frac{V_i}{R_i}$$

$$V_{gs} \left( 2.1 + \frac{1}{10} + \frac{1}{2} \right) = -\frac{V_i}{2}$$

$$V_{gs} = -(0.185) V_i$$

$$A_v = \frac{V_0}{V_i} = (2.1)(0.185)(5 \parallel 4)$$

$$A_v = 0.863$$

7.51

dc analysis

$$I_D = \frac{V^+ - V_{SG}}{R_S} = K_p (V_{SG} + V_{TP})^2$$

$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2$$


$$= 4(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(4)(2.44)}}{2(4)} = 1.707$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(1.707 - 0.8)$$

$$g_m = 1.81 \text{ mA/V}$$

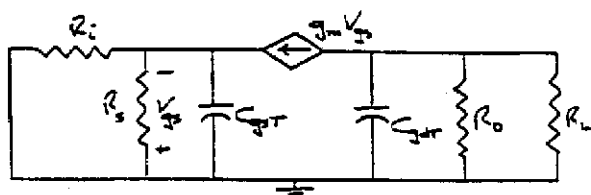

3-dB frequency due to  $C_{gs}$ :  $R_{eq} = \frac{1}{g_m} \parallel R_S \parallel R_i$

$$f_A = \frac{1}{2\pi R_{eq} C_{gs}}$$

$$R_{eq} = \frac{1}{1.81} \parallel 4 \parallel 0.5 = 0.246 \text{ k}\Omega$$

$$f_A = \frac{1}{2\pi(0.246)(4 \times 10^{-12})} = 162 \text{ MHz}$$


3-dB frequency due to  $C_{gd}$

$$f_B = \frac{1}{2\pi(R_D \parallel R_L)C_{gd}}$$

$$= \frac{1}{2\pi(2 \parallel 4) \times 10^3 \times 10^{-12}}$$

$$f = 119 \text{ MHz}$$

Midband gain

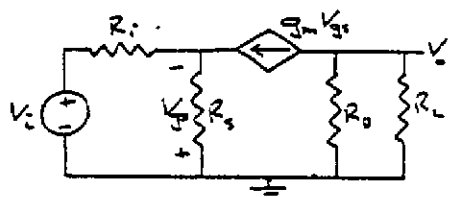

$$V_{gs} = \frac{-\frac{1}{g_m} \parallel R_S}{\frac{1}{g_m} \parallel R_S + R_i} \cdot V_i = \frac{-\frac{1}{1.81} \parallel 4}{\frac{1}{1.81} \parallel 4 + 0.5} \cdot V_i$$

$$= -0.492V_i$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$A_v = (0.492)(1.81)(4 \parallel 2) \Rightarrow A_v = 1.19$$

7.52

$$r_\pi = \frac{(120)(0.026)}{1.02} = 3.06 \text{ k}\Omega$$

$$g_m = 39.2 \text{ mA/V}$$

a. Input:  $f_{H\pi} = \frac{1}{2\pi\tau_\pi}$

$$\tau_\pi = [R_S \parallel R_2 \parallel R_3 \parallel r_\pi](C_\pi + 2C_\mu)$$

$$= 0.1 \parallel 20.5 \parallel 28.3 \parallel 3.06 = 0.096 \text{ k}\Omega$$

$$\tau_\pi = (96)(12 + 2(2)) \times 10^{-12} = 1.536 \times 10^{-9} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi(1.536 \times 10^{-9})} = 103.6 \text{ MHz}$$

Output:  $f_{H\mu} = \frac{1}{2\pi\tau_\mu}$

$$\tau_\mu = (R_C \parallel R_L)C_\mu$$

$$= (5 \parallel 10) \times 10^3 \times 2 \times 10^{-12}$$

$$= 6.67 \times 10^{-9}$$

$$f_{H\mu} = \frac{1}{2\pi(6.67 \times 10^{-9})} = 23.9 \text{ MHz}$$

b.  $A = g_m(R_C \parallel R_L) \left[ \frac{R_2 \parallel R_3 \parallel r_\pi}{R_2 \parallel R_3 \parallel r_\pi + R_S} \right]$

$$R_2 \parallel R_3 \parallel r_\pi = 20.5 \parallel 28.3 \parallel 3.06 = 2.43 \text{ k}\Omega$$

$$A = (39.2)(5 \parallel 10) \left[ \frac{2.43}{2.43 + 0.1} \right] \Rightarrow A = 125.5$$

c.  $C_L = 15 \text{ pF} > C_\mu \Rightarrow C_L$  dominates frequency response.