

Chapter 4

Exercise Solutions

E4.1

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.25}{0.026} \Rightarrow g_m = 9.62 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(120)}{0.25} \Rightarrow r_\pi = 12.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{0.25} \Rightarrow r_o = 600 \text{ k}\Omega$$

E4.2

$$r_o = \frac{V_A}{I_{CQ}} \Rightarrow I_{CQ} = \frac{V_A}{r_o} = \frac{75}{200 \text{ k}\Omega}$$

$$\Rightarrow I_{CQ} = 0.375 \text{ mA}$$

E4.3

$$I_{BQ} = \frac{V_{BB} - V_{BE(\text{on})}}{R_B} = \frac{0.92 - 0.7}{100}$$

$$\Rightarrow I_{BQ} = 0.0022 \text{ mA}$$

$$I_{CQ} = (150)(0.0022) = 0.33 \text{ mA}$$

$$\text{a. } g_m = \frac{I_{CQ}}{V_T} = \frac{0.33}{0.026} \Rightarrow g_m = 12.7 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.0026)(150)}{0.33} \Rightarrow r_\pi = 11.8 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.33} \Rightarrow r_o = 606 \text{ k}\Omega$$

$$\text{b. } v_o = -g_m v_\pi (r_o \parallel R_C), \quad v_\pi = \left(\frac{r_\pi}{r_\pi + R_B} \right) v_s$$

$$A_v = \frac{v_o}{v_s} = -g_m \left(\frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C)$$

$$= -(12.7) \left(\frac{11.8}{11.8 + 100} \right) (606 \parallel 15)$$

$$= -(12.7)(0.1055)(14.64)$$

$$\Rightarrow A_v = -19.6$$

E4.4

$$g_m = \frac{I_{CQ}}{V_T}$$

$$\text{a. } I_{BQ} = \frac{V_{BB} - V_{EB(\text{on})}}{R_B} = \frac{1.145 - 0.70}{50}$$

$$\Rightarrow I_{BQ} = 0.0089 \text{ mA}$$

$$I_{CQ} = (90)(0.0089) \Rightarrow I_{CQ} = 0.801 \text{ mA}$$

$$g_m = \frac{0.801}{0.026} \Rightarrow g_m = 30.8 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.0026)(90)}{0.801} \Rightarrow r_\pi = 2.92 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{120}{0.801} \Rightarrow r_o = 150 \text{ k}\Omega$$

$$\text{b. } v_o = g_m v_\pi (r_o \parallel R_C), \quad v_\pi = - \left(\frac{r_\pi}{r_\pi + R_B} \right) v_s$$

$$A_v = \frac{v_o}{v_s} = -g_m \left(\frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C)$$

$$= -(30.8) \left(\frac{2.92}{2.92 + 50} \right) (150 \parallel 2.5)$$

$$= -(30.8)(0.055)(2.46)$$

$$\Rightarrow A_v = -4.17$$

E4.5

$$R_{TH} = 250 \parallel 75 = 57.7 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (5) = \left(\frac{75}{75 + 250} \right) (5) = 1.154$$

$$I_{BQ} = \frac{1.154 - 0.7}{57.7 + (121)(0.6)} = 3.48 \text{ }\mu\text{A}$$

$$I_{CQ} = 0.418 \text{ mA}$$

$$\text{a. } r_\pi = \frac{(120)(0.026)}{0.418} = 7.46 \text{ k}\Omega$$

$$g_m = \frac{0.418}{0.026} = 16.08 \text{ mA/V}$$

$$V_o = -g_m V_\pi R_C$$

$$R_{ib} = r_\pi + (1 + \beta) R_E = 7.46 + (121)(0.6) = 80.1 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 250 \parallel 75 = 57.7 \text{ k}\Omega$$

$$R_1 \parallel R_2 \parallel R_{ib} = 57.7 \parallel 80.1 = 33.54 \text{ k}\Omega$$

$$V_s' = \left(\frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right) V_s = \left(\frac{33.54}{33.54 + 0.5} \right) V_s$$

$$V_s' = (0.985) V_s$$

$$V_s' = V_\pi \left[1 + \left(\frac{1 + \beta}{r_\pi} \right) R_E \right]$$

Then

$$A_v = (0.985)(-8.39) = -8.27$$

$$\text{b. } R_{ib} = r_\pi + (1 + \beta)(R_E) = 7.46 + (121)(0.6)$$

$$\Rightarrow R_{ib} = 80.1 \text{ k}\Omega$$

E4.6

As a first approximation,

$$A_v \approx - \frac{R_C}{R_E}$$

Resulting gain is always smaller than this value.
The effect of R_s is very small.

$$\text{Set } \frac{R_C}{R_E} = 10$$

$$5 \cong I_C(R_C + R_E) + V_{CEQ}$$

$$5 = 0.5(R_C + R_E) + 2.5$$

$$\text{So that } R_E = 0.454 \text{ k}\Omega \text{ and } R_C = 4.54 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.5}{100} = 0.005 \text{ mA}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(0.454) = 4.59 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} R_{TH} V_{CC} = \frac{1}{R_1} (4.59)(5)$$

$$\text{or } V_{TH} = \frac{23}{R_1}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE}(on) + (1 + \beta) I_{BQ} R_E$$

$$\frac{23}{R_1} = (0.005)(4.59) + 0.7 + (101)(0.005)(0.454)$$

$$\text{which yields, } R_1 = 24.1 \text{ k}\Omega \text{ and } R_2 = 5.67 \text{ k}\Omega$$

E4.7

dc analysis

$$R_{TH} = R_1 \parallel R_2 = 15 \parallel 85 = 12.75$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{85}{85 + 15} \right) (12)$$

$$V_{TH} = 10.2 \text{ V}$$

$$I_{BQ} = \frac{12 - 0.7 - V_{TH}}{R_{TH} + (1 + \beta)R_E}$$

$$= \frac{12 - 0.7 - 10.2}{12.75 + (101)(0.5)} = \frac{1.1}{63.25} = 0.0174$$

$$I_{CQ} = 1.74 \text{ mA}$$

ac analysis

$$V_o = h_{fe} I_b (R_C \parallel R_L)$$

$$I_b = \frac{-V_s}{h_{ie} + (1 + h_{fe})R_E}$$

$$A_v = \frac{-h_{fe}(R_C \parallel R_L)}{h_{ie} + (1 + h_{fe})R_E}$$

$$\text{For } I_{CQ} = 1.7 \text{ mA}$$

$$h_{fe}(\text{max}) = 110 \quad h_{fe}(\text{min}) = 70$$

$$h_{ie}(\text{max}) = 2 \text{ k}\Omega \quad h_{ie}(\text{min}) = 1.1 \text{ k}\Omega$$

$$A_v(\text{max}) = \frac{-110(4 \parallel 2)}{2 + (111)(0.5)} = -2.54$$

$$A_v(\text{min}) = \frac{-70(4 \parallel 2)}{1.1 + (71)(0.5)} = -2.54$$

E4.8

First approximation, $A_v = -\frac{R_C}{R_E}$ which predicts a

low value. Set $\frac{R_C}{R_E} = 9$. Now

$$V_{CC} \cong I_{CQ}(R_C + R_E) + V_{ECQ}$$

$$7.5 = (0.6)(9R_E + R_E) + 3.75$$

$$\text{So } R_E = 0.625 \text{ k}\Omega \text{ and } R_C = 5.62 \text{ k}\Omega$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(0.625) = 6.31 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} R_{TH} V_{CC} = \frac{1}{R_1} (6.31)(7.5)$$

$$V_{CC} = (1 + \beta)I_{BQ}R_E + V_{EB}(on) + I_{BQ}R_{TH} + V_{TH}$$

$$I_{BQ} = \frac{0.6}{100} = 0.006 \text{ mA}$$

$$7.5 = (101)(0.006)(0.625) + 0.7 + (0.006)(6.31) + \frac{1}{R_1} (6.31)(7.5)$$

$$\text{Then } R_1 = 7.40 \text{ k}\Omega \text{ and } R_2 = 42.8 \text{ k}\Omega$$

E4.9

dc analysis

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)(20)} = 0.00439 \text{ mA}$$

$$I_{CQ} = 0.439 \text{ mA}, I_{EQ} = 0.443 \text{ mA}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.439} = 5.92 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.439}{0.026} = 16.88 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.439} = 228 \text{ k}\Omega$$

$$(a) V_o = -g_m V_\pi (r_o \parallel R_C)$$

$$V_\pi = V_i = \left(\frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s} \right) V_i$$

$$R_B \parallel r_\pi = 100 \parallel 5.92 = 5.59 \text{ k}\Omega$$

Then

$$V_\pi = \left(\frac{5.59}{5.59 + 0.5} \right) V_i = 0.918 V_i$$

Then

$$A_v = -(161.7)(0.918) = -148$$

$$b. R_{in} = R_B \parallel r_\pi = (100) \parallel (5.92)$$

$$\Rightarrow R_{in} = 5.59 \text{ k}\Omega$$

$$R_o = R_C \parallel r_o = 10 \parallel 228 \Rightarrow R_o = 9.58 \text{ k}\Omega$$

E4.10

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} = -(0.95) \left(\frac{R_C}{R_E} \right) = -(0.95) \left(\frac{2}{0.4} \right)$$

$$\text{or } A_v = -4.75$$

Assume $r_\pi = 1.2 \text{ k}\Omega$ from Example 4.5. Then

$$\frac{-\beta(2)}{1.2 + (1 + \beta)(0.4)} = -4.75$$

$$\text{which yields } \beta = 76$$

E4.11

dc analysis: $V_{TH} = 0, R_{TH} = R_1 \parallel R_2 = 10 \text{ k}\Omega$

$$I_{BQ} = \frac{5 - 0.7}{10 + (126)(5)} = 0.00672$$

$$I_{CQ} = 0.84 \text{ mA}$$

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(125)}{0.84} = 3.87 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.84}{0.026} = 32.3 \text{ mA/V}$$


$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ k}\Omega$$

a. $v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L), v_{\pi} = v_s$

$$A_v = -g_m (r_o \parallel R_C \parallel R_L) = -(32.3)(238 \parallel 2.3 \parallel 5)$$

$$A_v = -(32.3)(1.56) \Rightarrow \underline{A_v = -50.4}$$

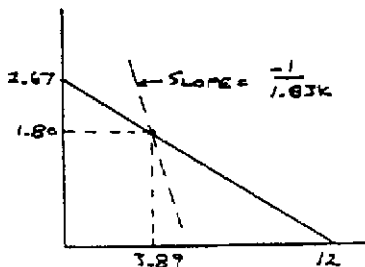b. $R_o = r_o \parallel R_C \Rightarrow \underline{R_o = 2.28 \text{ k}\Omega}$



$$I_{BQ} = \frac{12 - 0.7 - 10.2}{12.75 + (121)(0.5)} = \frac{1.1}{73.25}$$

$$I_{BQ} = 0.0150$$

$$I_{CQ} = 1.80, I_{EQ} = 1.82$$

$$\Rightarrow V_{ECQ} = 3.89$$


b. For $\Delta i_C = 1.8 \Rightarrow \Delta v_{EC} = (1.8)(1.83) = 3.29$

For $\Delta v_{EC} = -3.29 \Rightarrow \Delta v_{CE} = 3.89 - 3.29 = 0.6$

$$\Rightarrow \text{Max. symmetrical swing}$$

$$= 2 \times (3.29) = \underline{6.58 \text{ V peak-to-peak}}$$

E4.12

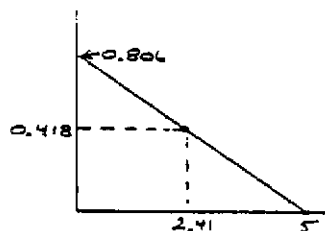

$$V_{CEQ} = 5 - (0.418)(5.6) - \left(\frac{121}{120}\right)(0.418)(0.6)$$

$$= 5 - 2.34 - 0.253$$

$$V_{CEQ} = 2.41$$

$$\Delta V_{CE} \text{ variation } (2.41 - 0.5)2 = 3.82 \text{ V}$$

peak-to-peak

E4.13

a. dc load line:

$$V_{EC} = V_{CC} - I_E R_E - I_C R_C$$

$$V_{EC} = 12 - I_C (R_E + R_C) = 12 - I_C (4.5)$$

ac load line:

$$v_{ec} \approx -i_C (R_E + R_C \parallel R_L)$$

$$v_{ec} = -i_C (0.5 + 4 \parallel 2) = -i_C (1.83)$$

E4.14


dc load line:

$$V_{CE} \approx (10 + 10) - I_C (R_C + R_E)$$

$$V_{CE} = 20 - I_C (10 + R_E)$$

$$v_{ce} = -i_C R_C = -i_C (10)$$

ac load line:

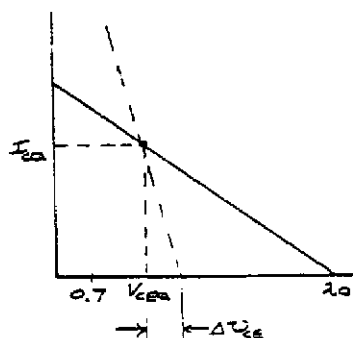

$$\Delta v_{ce} = V_{CEQ} - 0.7 = \Delta i_C (10) = I_{CQ} (10)$$

$$\text{So } V_{CEQ} - 0.7 = I_{CQ} (10)$$

We have

$$V_{CEQ} = 20 - I_{CQ} (10 + R_E)$$

$$I_{CQ} (10) + 0.7 = 20 - I_{CQ} (10 + R_E)$$

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)R_E} \Rightarrow I_{CQ} = \frac{(100)(9.3)}{100 + (101)R_E} \quad (2)$$

From (1)

$$I_{CQ}[10 + 10 + R_E] = 20 - 0.7$$

Substitute (2)

$$\left[\frac{(100)(9.3)}{100 + (101)R_E} \right] (20 + R_E) = 19.3$$

$$930(20 + R_E) = 19.3[100 + (101)R_E]$$

$$18,600 + 930R_E = 1930 + 1949.3R_E$$

$$16,670 = 1019.3R_E \Rightarrow R_E = 16.35 \text{ k}\Omega$$

So

$$I_{CQ} = \frac{(100)(9.3)}{100 + (101)(16.35)} \Rightarrow I_{CQ} = 0.531 \text{ mA}$$

$$V_{CEQ} = 20 - (0.531)(10 + 16.35) \Rightarrow V_{CEQ} = 6.0 \text{ V}$$

$$\Delta v_{CE} = V_{CEQ} - 0.7 = 6 - 0.7 = 5.3$$

Max symmetrical swing

$$2 \times (5.3) = 10.6 \text{ V peak-to-peak}$$

E4.15

$$\text{a. } I_{BQ} = \frac{5 - 0.7}{10 + (126)(5)} = 0.00672$$


$$I_{CQ} = 0.84 \text{ mA}, I_{EQ} = 0.847 \text{ mA}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ k}\Omega$$

$$V_{CEQ} = 10 - (0.84)(2.3) - (0.847)(5)$$

$$= 10 - 1.932 - 4.235$$

$$V_{CEQ} = 3.83 \text{ V}$$

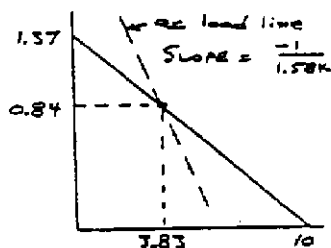

dc load line

$$V_{CE} \approx 10 - I_C(7.3)$$

ac load line

$$v_{ce} = -i_c(R_C \parallel R_L) = -i_c(2.3 \parallel 5) = -i_c(1.58)$$

(neglecting r_o)

$$\text{b. } \Delta i_C = 0.84$$

$$\Rightarrow \Delta v_{CE} = (0.84)(1.58) = 1.33 \text{ V}$$

$$V_{CE(\min)} = 3.83 - 1.33 = 2.5 \text{ V}$$

$$V_{CE(\max)} = 3.83 + 1.33 = 5.16 \text{ V}$$

So max symmetrical swing

$$= 2 \times (1.33) = 2.66 \text{ V peak-to-peak}$$

E4.16

$$\text{a. } V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (12). \quad V_{TH} = \frac{1}{R_1} (R_{TH})(12)$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(121)R_E$$

$$= 12.1 R_E = 12.1 \text{ k}\Omega$$

$$I_{BQ} = \frac{12 - 0.7 - V_{TH}}{R_{TH} + (1 + \beta)R_E} = \frac{11.3 - \frac{1}{R_1}(12.1)(12)}{12.1 + (121)(1)}$$

$$I_{CQ} = 1.6 \Rightarrow I_{BQ} = \frac{1.6}{120} = 0.01333 \text{ mA}$$

$$0.01333 = \frac{11.3 - \frac{1}{R_1}(145.2)}{133.1}$$

$$\frac{1}{R_1}(145.2) = 11.3 - (0.01333)(133.1)$$

$$\Rightarrow R_1 = 15.24 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 12.1 = \frac{15.24 R_2}{15.24 + R_2}$$

$$(12.1)(15.24) = (15.24 - 12.1)R_2$$


$$\Rightarrow R_2 = 58.7 \text{ k}\Omega$$

$$V_{CEQ} = 12 - (16)(4) - (1.61)(1) \Rightarrow V_{CEQ} = 3.99 \text{ V}$$

$$\text{b. } v_o = g_m v_{\pi}(R_C \parallel R_L) = -g_m(R_C \parallel R_L) = -v_{ec}$$

$$i_C = g_m v_{\pi} = -g_m v_{\pi}$$
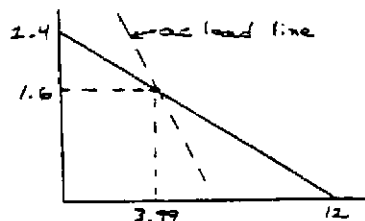
$$\text{or } -v_{ec} = i_C(R_C \parallel R_L)$$



$$\text{Want } \Delta i_C = 1.6 - 0.1 = 1.5$$

$$\Delta v_{ec} = 3.99 - 0.5 = 3.49$$

$$\frac{\Delta v_{ec}}{\Delta i_C} = \frac{3.49}{1.5} = 2.327 \text{ k}\Omega = R_C \parallel R_L$$

$$\frac{R_C R_L}{R_C + R_L} = \frac{4 R_L}{4 + R_L} = 2.327$$

$$(4 - 2.327)R_L = (4)(2.327) \Rightarrow R_L = 5.56 \text{ k}\Omega$$

E4.17

$$R_{TH} = R_1 \parallel R_2 = 25 \parallel 50 = 16.7 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{50}{50 + 25} \right) (5)$$

$$V_{TH} = 3.33 \text{ V}$$

$$I_{BQ} = \frac{V_{BB} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_E} = \frac{3.33 - 0.70}{16.7 + (121)(1)}$$

$$= \frac{2.63}{137.7}$$

$$\Rightarrow I_{BQ} = 0.0191$$

$$I_{CQ} = 2.29 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.29}{0.026} = 88.1 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(120)}{2.29} = 1.36 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{2.29} = 43.7 \text{ k}\Omega$$

a.

$$V_s' = \left(\frac{R_1 \| R_2 \| R_{ib}}{R_1 \| R_2 \| R_{ib} + R_s} \right) \cdot V_s$$

$$R_{ib} = r_\pi + (1 + \beta)(R_E \| r_o) = (1.36) + (121)(1 \| 43.7) \Rightarrow$$

$$R_{ib} = 120 \text{ k}\Omega \text{ and } R_1 \| R_2 = 16.7 \text{ k}\Omega$$

$$\text{Then } R_1 \| R_2 \| R_{ib} = 16.7 \| 120 = 14.7 \text{ k}\Omega$$

Then

$$V_s' = \left(\frac{14.7}{14.7 + 0.5} \right) \cdot V_s = (0.967)V_s$$

Now

$$V_o = \left(\frac{V_s}{r_\pi} + g_m V_s' \right) (R_E \| r_o) = V_s \left(\frac{1 + \beta}{r_\pi} \right) R_E \| r_o$$

$$V_s = \frac{V_s'}{1 + \left(\frac{1 + \beta}{r_\pi} \right) R_E \| r_o} = \frac{(0.967)V_s}{1 + \left(\frac{1 + \beta}{r_\pi} \right) R_E \| r_o}$$

So

$$\frac{V_o}{V_s} = \frac{(0.967) \left(\frac{1 + \beta}{r_\pi} \right) R_E \| r_o}{1 + \left(\frac{1 + \beta}{r_\pi} \right) R_E \| r_o} = \frac{(0.967)(1 + \beta) R_E \| r_o}{r_\pi + (1 + \beta) R_E \| r_o}$$

$$R_E \| r_o = 1 \| 43.7 = 0.978 \text{ k}\Omega$$

Then

$$A_v = \frac{(0.967)(121)(0.978)}{1.36 + (121)(0.978)} \Rightarrow A_v = 0.956$$

$$\text{b. } R_{ib} = r_\pi + (1 + \beta) R_E \| r_o = 1.36 + (121)(0.978)$$

$$\Rightarrow R_{ib} = 120 \text{ k}\Omega$$

(c)

$$R_o = R_E \| r_o \left\| \frac{r_\pi + R_1 \| R_2 \| R_s}{1 + \beta} \right\| = 1 \| 43.7 \left\| \frac{1.36 + 16.7 \| 0.5}{121} \right\|$$

which yields

$$R_o = 15.1 \Omega$$

E4.18

$$V_{CEQ} = 5 \text{ V} \Rightarrow I_{EQ} = \frac{5}{2} = 2.5 \text{ mA}$$

$$I_{BQ} = \frac{2.5}{101} = 0.0248 \text{ mA}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1 + \beta) I_{BQ} R_E$$

$$R_{in} = R_{TH} \| [r_\pi + (1 + \beta) R_E]$$

$$r_\pi = 1.05 \text{ k}\Omega$$

$$65 = R_{TH} \| 203 = \frac{R_{TH} \cdot 203}{R_{TH} + 203}$$

$$\Rightarrow R_{TH} = 95.6 \text{ k}\Omega$$

$$\frac{1}{R_1} (95.6)(10) = (0.0248)(95.6) + 0.7 + 2.5(2)$$

$$= 8.07$$

$$R_1 = 118 \text{ k}\Omega, \quad \frac{118 R_2}{118 + R_2} = 95.6$$

$$R_2 = 504 \text{ k}\Omega$$

$$R_{in} = 65 \text{ k}\Omega$$

$$V_i' = \left(\frac{R_{in}}{R_{in} + R_s} \right) \cdot V_s = \left(\frac{65}{65 + 0.5} \right) \cdot V_s = 0.992 V_s$$

Then

$$A_v = \frac{(0.992)(1 + \beta) R_E}{r_\pi + (1 + \beta) R_E} = \frac{(0.992)(101)(2)}{1.05 + (101)(2)} \Rightarrow$$

$$A_v = 0.987$$

$$\text{Neglecting } R_s, \quad A_v = 0.995$$

$$R_o = R_E \left\| \frac{r_\pi + R_1 \| R_2 \| R_s}{1 + \beta} \right\| = 2 \left\| \frac{1.05 + 95.6 \| 0.5}{101} \right\|$$

or

$$R_o = 15.2 \Omega$$

$$\text{Neglecting } R_s, \quad R_o = 2 \left\| \frac{1.05}{102} \right\| \Rightarrow R_o = 10.3 \Omega$$

E4.19

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$\beta = 100, \quad V_A = 125 \text{ V}, \quad V_{BE(on)} = 0.7 \text{ V}$$


$$I_{CQ} = 0.75 \text{ mA}$$

$$\text{Then } r_o = \frac{125}{0.75} = 167 \text{ k}\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.75} \Rightarrow r_\pi = 3.47 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - (-5)}{R_{TH} + (1 + \beta) R_E}$$

$$I_{CQ} = \beta I_{BQ}$$

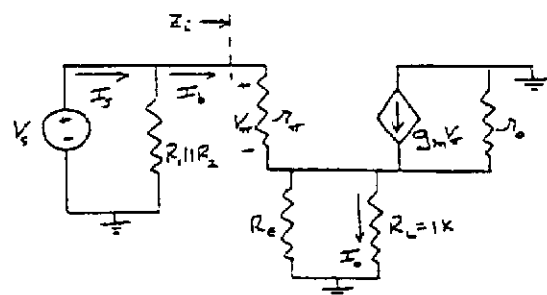

$$Z_i = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$$

$$I_o = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) I_b$$

$$I_b = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right)$$

Assume that $R_E \parallel r_o \approx R_E$

$$R_1 \parallel R_2 = (0.1)(1 + \beta)R_E$$

$$= (0.1)(101)R_E = 10.1R_E$$

Assume $R_L = 1 \text{ k}\Omega$

Then

$$A_I = 15 = \left(\frac{R_E}{R_E + 1} \right) (101) \times \left(\frac{10.1R_E}{10.1R_E + 3.47 + (101)(R_E \parallel 1 \text{ k}\Omega)} \right)$$

where $R_E \parallel R_L \parallel r_o \approx R_E \parallel R_L = R_E \parallel 1 \text{ k}\Omega$

$$15 = \frac{(101)(10.1)R_E^2}{R_E + 1} \times$$

$$\frac{1}{\left[10.1R_E + 3.47 + \frac{10.1R_E}{1 + R_E} \right]}$$

$$15 = \frac{(101)(10.1)R_E^2}{R_E + 1}$$

$$\times \frac{1}{\frac{(1 + R_E)(10.1R_E + 3.47) + 10.1R_E}{1 + R_E}}$$

$$15 = \frac{(101)(10.1)R_E^2}{10.1R_E + 3.47 + 10.1R_E^2 + 3.47R_E + 10.1R_E}$$

$$15 = \frac{(101)(10.1)R_E^2}{10.1R_E^2 + 114.57R_E + 3.47}$$

$$(101)(10.1)R_E^2 = 15[10.1R_E^2 + 114.57R_E + 3.47]$$

$$1020.1R_E^2 = 151.3R_E^2 + 1718.55R_E + 52.05$$

$$868.6R_E^2 - 1718.55R_E - 52.05 = 0$$

$$16.7R_E^2 - 33.0R_E - 1 = 0$$

$$R_E = \frac{33 \pm \sqrt{(33)^2 + 4(16.7)}}{2(16.7)}$$

Must use + sign $\Rightarrow R_E = 2.0 \text{ k}\Omega$

$$\text{Then } R_1 \parallel R_2 = 10.1R_E = 20.2 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \frac{1}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \frac{1}{R_1} (20.2)(10) - 5$$

$$I_{CQ} = 0.75$$

$$= (100) \left\{ \frac{\frac{1}{R_1} (20.2)(10) - 5 - 0.7 + 5}{20.2 + (101)(2)} \right\}$$

$$1.67 = \frac{1}{R_1} (202) - 0.7 \Rightarrow R_1 = 85.2 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 20.2 = \frac{85.2 R_2}{85.2 + R_2} \Rightarrow R_2 = 26.5 \text{ k}\Omega$$

E4.20

$$\text{a. } \beta = 100, V_{BE(\text{on})} = 0.7, I_{CQ} = 1.25 \text{ mA}$$

$$I_{EQ} = 1.26 \text{ mA}, I_{BQ} = 0.0125 \text{ mA}$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$V_{TH} = \frac{1}{R_1} (R_1 \parallel R_2) (10) - 5$$

$$I_{BQ} = \frac{V_{TH} - 0.7 - (-5)}{R_{TH} + (1 + \beta)R_E}$$

$$V_{CEQ} = 10 - I_{EQ}R_E = 4$$

$$I_{EQ}R_E = 6 \Rightarrow I_{EQ} = \frac{6}{R_E} \Rightarrow R_E = \frac{6}{1.26} = 4.76 \text{ k}\Omega$$

$$\Rightarrow R_E = 4.76 \text{ k}\Omega$$

$$R_{TH} = (0.1)(1 + \beta)R_E = 10.1R_E$$

Then

$$I_{BQ} = \frac{I_{EQ}}{101} = \frac{\frac{1}{R_1} (101)R_E (10) - 5 - 0.7 + 5}{10.1R_E + (101)R_E}$$

$$0.0125 = \frac{\frac{1}{R_1} (101)(4.76) - 0.7}{(111.1)(4.76)} \Rightarrow R_1 = 65.8 \text{ k}\Omega$$


$$\frac{R_1 R_2}{R_1 + R_2} = (10.1)R_E = (10.1)(4.76) = 48.1 \text{ k}\Omega$$

$$(65.8)R_2 = (48.1)(65.8) + (48.1)R_2$$

$$(65.8 - 48.1)R_2 = (48.1)(65.8)$$

$$\Rightarrow R_2 = 178.8 \text{ k}\Omega$$

b.

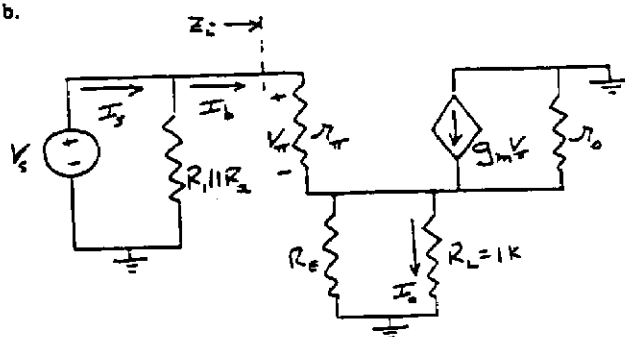

$$r_o = \frac{V_A}{I_{CQ}} = \frac{125}{1.25} = 100 \text{ k}\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.25} = 2.08 \text{ k}\Omega$$

$$g_m V_\pi = g_m (i_b r_\pi) = \beta i_b$$

$$Z_i = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$$

$$= 2.08 + (101)[4.76 \parallel 1 \parallel 100]$$

$$= 2.08 + (101)[0.826 \parallel 100]$$

$$= 2.08 + (101)(0.819)$$

$$Z_i = 84.8 \text{ k}\Omega$$

Assume $R_L = 1 \text{ k}\Omega$

$$I_o = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) I_b$$

$$I_b = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right) I_s$$

$$A_I = \frac{I_o}{I_s} = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right)$$

$$R_E \parallel r_o = 4.76 \parallel 100 = 4.54$$

$$A_I = \left(\frac{4.54}{4.54 + 1} \right) (101) \left(\frac{48.1}{48.1 + 84.8} \right)$$


$$= \left(\frac{4.54}{5.54} \right) (101) \left(\frac{48.1}{132.9} \right)$$

$$\Rightarrow A_I = 30.0$$

$$c. \quad R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o = \frac{2.08}{101} \parallel 4.76 \parallel 100$$

$$\Rightarrow R_o = 20.4 \Omega$$

d.

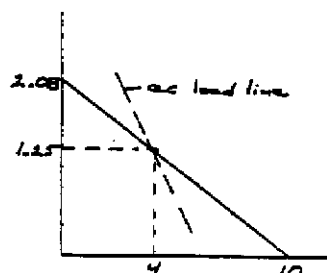

$$v_o = v_{ce} = (1 + \beta) i_b (R_E \parallel R_L \parallel r_o)$$

$$i_b = \frac{i_c}{\beta}$$

$$v_{ce} = i_c \left(\frac{1 + \beta}{\beta} \right) (R_E \parallel R_L \parallel r_o)$$

$$= i_c \left(\frac{101}{100} \right) (4.76 \parallel 1 \parallel 100)$$

$$= i_c (0.828)$$

$$\text{If } \Delta i_c = 1.25 \text{ mA, } -\Delta v_{ce} = 1.035 \text{ V}$$

Maximum symmetrical swing in output voltage

$$i_s = 2\Delta v_{ce} = 2.07 \text{ V peak-to-peak}$$

E4.21

For $\beta = 130$

$$I_{BQ} = \frac{10 - 0.7}{100 + (131)(10)} \Rightarrow 6.596 \mu\text{A}$$

$$I_{CQ} = 0.857 \text{ mA}$$

From Figure 4.21

$$3 < h_{ie} < 5 \text{ k}\Omega \quad \text{Let } h_{re} = 0$$

$$98 < h_{fe} < 170$$

$$8 < h_{oe} < 16 \mu\text{S}$$

$$h_{ie} = 4 \text{ k}\Omega$$

$$h_{fe} = 134$$

$$h_{oe} = 12 \mu\text{S} \Rightarrow \frac{1}{h_{oe}} = 83.3 \text{ k}\Omega$$

$$a. \quad R_E = R_L = 10 \text{ k}\Omega$$

$$R_{ib} = h_{ie} + (1 + h_{fe}) \left(R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)$$

$$= 4 + (135)(10 \parallel 10 \parallel 83.3)$$

$$\Rightarrow R_{ib} = 641 \text{ k}\Omega$$

$$A_v = \left(\frac{R_E \parallel R_{ib}}{R_E + R_{ib}} \right) \times$$

$$\left(\frac{(1 + h_{fe}) \left(R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)}{h_{ie} + (1 + h_{fe}) \left(R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)} \right)$$

$$A_v = \left(\frac{100 \parallel 641}{10 + 100 \parallel 641} \right) \left[\frac{(135)(10 \parallel 10 \parallel 83.3)}{4 + (135)(10 \parallel 10 \parallel 83.3)} \right]$$

$$= \left(\frac{86.5}{10 + 86.5} \right) \left[\frac{637}{641} \right]$$

$$\Rightarrow A_v = 0.891$$

$$A_i = \left(\frac{R_E \parallel \frac{1}{h_{oe}}}{R_E \parallel \frac{1}{h_{oe}} + R_L} \right) (1 + h_{fe}) \left(\frac{R_E}{R_E + R_{ib}} \right)$$

$$= \left(\frac{10 \parallel 83.3}{10 \parallel 83.3 + 10} \right) (135) \left(\frac{100}{100 + 641} \right)$$

$$\Rightarrow A_i = 8.59$$

$$R_o = R_E \parallel \frac{1}{h_{oe}} \parallel \frac{h_{ie} + R_E \parallel R_L}{1 + h_{fe}}$$

$$= 10 \parallel 83.3 \parallel \frac{4 + 10 \parallel 100}{135} = 8.93 \parallel 0.0970$$

$$\Rightarrow R_o = 96.0 \Omega$$

$$b. \quad R_E = 1 \text{ k}\Omega, \quad R_{ib} = 641 \text{ k}\Omega, \quad A_i = 8.59$$

$$A_v = \left(\frac{86.5}{1 + 86.5} \right) \left(\frac{637}{641} \right) \Rightarrow A_v = 0.982$$

$$R_o = 10 \parallel 8.33 \parallel \left[\frac{4 + 1 \parallel 100}{135} \right]$$

$$= 8.93 \parallel 0.03696 \Rightarrow R_o = 36.8 \Omega$$

E4.22

$$V_{TH} = 2.5 \text{ V}, R_{TH} = 25 \text{ k}\Omega$$

$$I_{BQ} = \frac{5 - 0.7 - 2.5}{25 + (101)(2)} = \frac{1.8}{227} = 0.00793 \text{ mA}$$

$$I_{CQ} = 0.793 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.793}{0.026} = 30.5 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.793} = 3.28 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{125}{0.793} = 158 \text{ k}\Omega$$

$$\text{a. } R_E \parallel R_L \parallel r_o = 2 \parallel 0.5 \parallel 158 = 0.4 \parallel 158 \approx 0.4$$

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L \parallel r_o)}{r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)}$$

$$= \frac{(101)(0.4)}{3.28 + (101)(0.4)} \Rightarrow A_v = 0.925$$

$$\text{b. } R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$$

$$R_{ib} = 3.28 + (101)(0.4)$$

$$\Rightarrow R_{ib} = 43.7 \text{ k}\Omega$$

$$R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o = \frac{3.28}{101} \parallel 2 \parallel 98.3$$

$$\Rightarrow R_o = 32.0 \Omega$$

$$\text{c. } I_B(\text{max}) =$$

$$R_E(\text{min}) = 1.9 \text{ k}\Omega$$

$$R_2(\text{min}) = 47.5 \text{ k}\Omega$$

$$R_1(\text{max}) = 52.5 \text{ k}\Omega$$

$$R_{TH} = 24.9 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{47.5}{100} \right) (5) = 2.375$$

$$I_{BQ} = \frac{5 - 0.7 - 2.375}{24.9 + (101)(1.9)} = \frac{1.925}{216.8}$$

$$I_{CQ} = 0.888 \text{ mA}$$

$$R_E(\text{max}) = 2.1 \text{ k}\Omega$$

$$R_2(\text{max}) = 52.5 \text{ k}\Omega$$

$$R_1(\text{min}) = 47.5 \text{ k}\Omega$$

$$R_{TH} = 24.9 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{52.5}{100} \right) (5) = 2.625$$

$$I_{CQ} = (100) \left[\frac{5 - 0.7 - 2.625}{24.9 + (101)(2.1)} \right] = \frac{(100)(1.675)}{237}$$

$$I_{CQ} = 0.707 \text{ mA}$$

$$r_\pi(\text{max}) = \frac{(100)(0.026)}{0.707} = 3.68 \text{ k}\Omega$$


$$R_o = 1.96 \parallel \frac{3.68}{101} = 1.96 \parallel 0.0364 = 35.7 \Omega$$

$$r_\pi(\text{min}) = 2.93 \text{ k}\Omega$$

$$R_o = 1.96 \parallel \frac{2.93}{101} = 1.96 \parallel 0.0290 = 28.6 \Omega$$

$$\Rightarrow 28.6 \leq R_o \leq 35.7 \Omega$$

E4.23

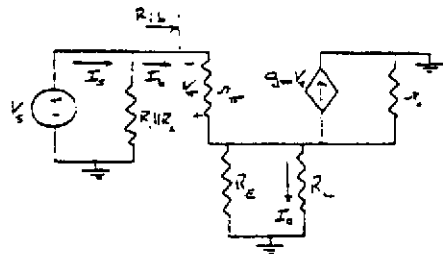For $V_{ECQ} = 2.5 \text{ V}$,

$$I_{EQ} = \frac{5 - 2.5}{R_E} = \frac{5 - 2.5}{0.5} = 5 \text{ mA}$$

$$I_{CQ} = \left(\frac{75}{76} \right) (5) = 4.93 \text{ mA} \Rightarrow I_{BQ} = 0.0658 \text{ mA}$$

$$V_\pi = -I_B r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(75)(0.026)}{4.93} = 0.396 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{75}{4.93} = 15.2 \text{ k}\Omega$$

$$g_m V_\pi = g_m (-I_B r_\pi) = -\beta I_B$$

$$I_o = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) \times (1 + \beta) I_B$$

$$I_o = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_{ib}} \right) I_s$$

$$A_I = \frac{I_o}{I_s} = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_{ib}} \right)$$

$$\text{a. } R_E = R_L = 0.5 \text{ k}\Omega$$

$$R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$$

$$= 0.396 + (76)(0.5 \parallel 0.5 \parallel 15.2)$$

$$= 0.396 + (76)(0.246)$$

$$\Rightarrow R_{ib} = 19.1 \text{ k}\Omega$$

$$R_E \parallel r_o = 0.5 \parallel 15.2 = 0.484 \text{ k}\Omega$$

$$A_I = 10 = \left(\frac{0.484}{0.484 + 0.5} \right) (76) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 19.1} \right)$$

$$10 = 37.38 \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 19.1} \right)$$

$$0.2673(R_1 \parallel R_2 + 19.1) = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 6.975 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} (R_1 \parallel R_2) V_{CC}$$

$$= \frac{1}{R_1} (6.975)(5)$$

$$I_{BQ} = \frac{5 - V_{EB(\text{on})} - V_{TH}}{R_{TH} + (1 + \beta)R_E}$$

$$0.0658 = \frac{5 - 0.7 - V_{TH}}{6.975 + (76)(0.5)}$$

$$2.96 = 4.3 - V_{TH} \Rightarrow V_{TH} = 1.34 = \frac{1}{R_1}(6.975)(5)$$

$$\Rightarrow R_1 = 26.0 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 6.975 = \frac{26 R_2}{26 + R_2}$$

$$6.975(26 + R_2) = 26 R_2$$

$$\Rightarrow R_2 = 9.53 \text{ k}\Omega$$

b. For $R_E = 4R_L = 4(0.5) \Rightarrow R_E = 2 \text{ k}\Omega$

$$I_{EQ} = \frac{5 - 2.5}{2} = 1.25 \text{ mA} \rightarrow I_{CQ} = 1.23 \text{ mA}$$

$$\rightarrow I_{BQ} = 0.0164 \text{ mA}$$

$$r_\pi = \frac{(75)(0.026)}{1.23} = 1.59 \text{ k}\Omega$$

$$r_o = \frac{75}{1.23} = 60.9 \text{ k}\Omega$$

$$Z_{ib} = r_\pi + (1 + \beta)[R_E \parallel R_L \parallel r_o]$$

$$= 1.59 + (76)[2 \parallel 0.5 \parallel 60.9]$$

$$\Rightarrow Z_{ib} = 31.8 \text{ k}\Omega$$

$$R_E \parallel r_o = 2 \parallel 60.9 = 1.94 \text{ k}\Omega$$

$$A_I = \left(\frac{1.94}{1.94 + 0.5} \right) (76) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 31.8} \right) = 10$$

$$10 = 60.4 \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 31.8} \right)$$

$$0.166(R_1 \parallel R_2 + 31.8) = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 6.33 \text{ k}\Omega$$

$$\text{Then } I_{BQ} = 0.0164 = \frac{4.3 - V_{TH}}{6.33 + (76)(2)}$$

$$V_{TH} = 1.70 = \frac{1}{R_1}(R_1 \parallel R_2)V_{CC} = \frac{1}{R_1}(6.33)(5)$$

$$\Rightarrow R_1 = 18.6 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 6.33 = \frac{(18.6)R_2}{18.6 + R_2}$$

$$6.33(18.6 + R_2) = (18.6)R_2$$

$$\Rightarrow R_2 = 9.6 \text{ k}\Omega$$

E4.24

a. $I_{EQ} = \frac{10 - 0.7}{10} = 0.93 \text{ mA}$

$$I_{CQ} = \left(\frac{\beta}{1 + \beta} \right) I_{EQ} = \left(\frac{100}{101} \right) (0.93)$$

$$\Rightarrow I_{CQ} = 0.921 \text{ mA}$$

$$V_{ECQ} = 10 + 10 - I_{CQ}R_C - I_{EQ}R_E$$

$$V_{ECQ} = 20 - (0.921)(5) - (0.93)(10)$$

$$\Rightarrow V_{ECQ} = 6.1 \text{ V}$$

b. $r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.921} = 2.82 \text{ k}\Omega$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.921}{0.026} = 35.42 \text{ mA/V}$$

$$i_o = g_m V_\pi \text{ and } V_\pi = v_s$$

$$i_i = \frac{v_s}{R_E \parallel r_\pi} + g_m V_\pi = v_s \left(\frac{1}{R_E \parallel r_\pi} + g_m \right)$$

$$A_I = \frac{i_o}{i_i} = \frac{g_m v_s}{v_s \left(\frac{1}{R_E \parallel r_\pi} + g_m \right)} = \frac{g_m (R_E \parallel r_\pi)}{1 + g_m (R_E \parallel r_\pi)}$$

$$= \frac{(35.42)(10 \text{ k}\Omega \parallel 2.82 \text{ k}\Omega)}{1 + (35.42)(10 \text{ k}\Omega \parallel 2.82 \text{ k}\Omega)}$$

$$\Rightarrow A_I = 0.987$$

$$A_v = \frac{v_o}{v_s} \text{ and } v_o = g_m V_\pi R_C = g_m v_s R_C$$

$$A_v = g_m R_C = (35.42)(5) \Rightarrow A_v = 177.1$$

c. $V_{ECQ} = 6.1 \text{ V} \Rightarrow V_{ECQ} = V_E - V_C$

$$V_C = V_E - V_{ECQ} = 0.7 - 6.1 = -5.4 \text{ V}$$

$$v_C = V_C + i_o R_C$$

$$\text{For } v_{EC} = 0.5 \Rightarrow v_C = +0.2$$

$$+0.2 = -5.4 + i_o R_C$$

$$i_o = \frac{0.2 + 5.4}{5} = 1.12 \text{ mA}$$

$$\Rightarrow \text{Current limited}$$

$$i_o(\text{max}) = 0.921$$

$$\Rightarrow v_o(\text{peak}) = (0.921)(5) = 4.61$$

$$\Rightarrow 9.21 \text{ V peak-to-peak}$$

E4.25

a. $I_{BQ} = \frac{V_{EE} - V_{BE(\text{on})}}{R_B + (1 + \beta)R_E} = \frac{10 - 0.7}{100 + (101)(10)}$


$$\Rightarrow I_{BQ} = 8.38 \text{ }\mu\text{A}, I_{CQ} = 0.838 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.838} \Rightarrow r_\pi = 3.10 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.838}{0.026} \Rightarrow g_m = 32.23 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.838} \Rightarrow r_o = \infty$$

b.

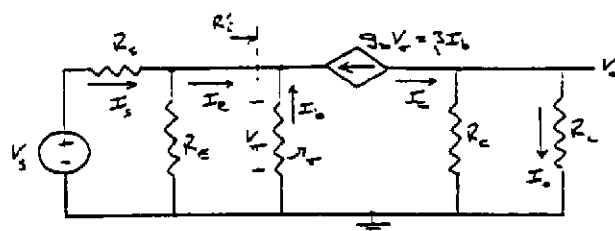

$$g_m V_\pi + \frac{V_\pi}{r_\pi} = \left(\frac{-V_\pi}{R_E} \right) + \frac{(-V_\pi - V_S)}{R_S}$$

$$V_\pi \left[\left(\frac{1+\beta}{r_\pi} \right) + \frac{1}{R_E} + \frac{1}{R_S} \right] = -\frac{V_S}{R_S}$$

$$V_\pi = -\frac{V_S}{R_S} \left[\left(\frac{1+\beta}{r_\pi} \right) \parallel R_E \parallel R_S \right]$$

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$A_v = \frac{V_o}{V_S} = g_m \frac{(R_C \parallel R_L)}{R_S} \left[\left(\frac{r_\pi}{1+\beta} \right) \parallel R_E \parallel R_S \right]$$

$$= \frac{(32.23)(10 \parallel 1)}{(1)} \left\{ \frac{3.10}{101} \parallel 10 \parallel 1 \right\}$$

$$= (32.23)(0.909)(0.0297) \Rightarrow \underline{A_v = 0.870}$$

$$R'_i = \frac{r_\pi}{1+\beta} = \frac{3.10}{101} = 0.0307 \text{ k}\Omega$$

$$I_e = \left(\frac{R_E}{R_E + R_i} \right) I_S \approx I_S$$

$$I_C = \left(\frac{\beta}{1+\beta} \right) I_e, \quad I_o = \left(\frac{R_C}{R_C + R_L} \right) I_C$$

$$I_e = \left(\frac{R_C}{R_C + R_L} \right) \left(\frac{\beta}{1+\beta} \right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left(\frac{10}{10+1} \right) \left(\frac{100}{101} \right) \Rightarrow \underline{A_I = 0.900}$$

c. $R_i = R_E \parallel R'_i = 10 \parallel 0.0307$

$$\Rightarrow \underline{R_i \approx 30.7 \Omega}$$

$$\underline{R_o = R_C = 10 \text{ k}\Omega}$$

E4.26

$$5 = I_B R_B + V_{BE(\text{on})} + I_E R_E$$

$$I_B = \frac{5 - 0.7}{R_B + (101)R_E} = \frac{4.3}{R_B + (101)R_E}$$

$$I_C = \frac{(100)(4.3)}{R_B + (101)R_E}$$

$$5 = I_C R_C + V_{CE} + I_E R_E - 5$$

$$V_{CE} = 10 - I_C \left(R_C + \left(\frac{101}{100} \right) R_E \right)$$

ac analysis

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_S = -V_\pi - \frac{V_\pi}{r_\pi} \cdot R_B = -V_\pi \left(1 + \frac{R_B}{r_\pi} \right)$$

$$\text{or } V_\pi = -\left(\frac{r_\pi}{r_\pi + R_B} \right) V_S$$

$$\frac{V_o}{V_S} = -g_m \left[-\left(\frac{r_\pi}{r_\pi + R_B} \right) \right] (R_C \parallel R_L)$$

$$A_v = \frac{V_o}{V_S} = \frac{\beta}{r_\pi + R_B} (R_C \parallel R_L)$$

For $I_C = 1 \text{ mA}$,

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$A_v = 20 = \frac{(100)(1)}{2.6 + R_B}$$

$$R_B = \frac{(100)(1)}{20} - 2.6 \Rightarrow \underline{R_B = 2.4 \text{ k}\Omega}$$

$$I_C = 1 = \frac{(100)(4.3)}{2.4 + (101)R_E}$$

$$R_E = \frac{(100)(4.3) - 2.4}{(101)} \Rightarrow \underline{R_E = 4.23 \text{ k}\Omega}$$

E4.27

a. $R_{TH} = 70 \parallel 6 = 5.526 \text{ k}\Omega$

$$V_{TH} = \left(\frac{6}{6+70} \right) (10) - 5 = -4.21 \text{ V}$$

$$I_{B1} = \frac{5 - 4.21 - 0.70}{5.526 + (126)(0.2)} = \frac{0.090}{30.726}$$

$$\Rightarrow I_{B1} = 2.93 \mu\text{A}, \quad I_{CQ1} = 0.366 \text{ mA}$$

$$\frac{5 - V_{C1}}{5} = I_{C1} + \frac{(V_{C1} - 0.7) - (-5)}{(1+\beta)1.5}$$

$$\frac{6 - V_{C1}}{5} = 0.366 + \frac{V_{C1}}{(126)(1.5)} + \frac{4.3}{(126)(1.5)}$$

$$1 - 0.366 - \frac{4.3}{(126)(1.5)} = \frac{V_{C1}}{5} + \frac{V_{C1}}{(126)(1.5)}$$

$$0.6112 = V_{C1}(0.2053) \Rightarrow V_{C1} = 2.977 \text{ V}$$

$$I_{E1} = 0.369 \text{ mA}$$

$$V_{E1} = (0.369)(0.2) - 5 \Rightarrow V_{E1} = -4.926 \text{ V}$$

$$\Rightarrow V_{CE1} = V_{C1} - V_{E1} = 2.977 - (-4.926)$$

$$\Rightarrow \underline{V_{CE1} = 7.90 \text{ V}}$$


$$I_{E2} = \frac{(V_{C1} - 0.7) - (-5)}{1.5} = \frac{5 + 2.98 - 0.7}{1.5}$$

$$= 4.85 \text{ mA}$$

$$I_{CQ2} = \left(\frac{\beta}{1+\beta} \right) I_{E2} \Rightarrow \underline{I_{CQ2} = 4.81 \text{ mA}}$$

$$V_{E2} = V_{C1} - 0.7 = 2.98 - 0.7 = 2.28$$
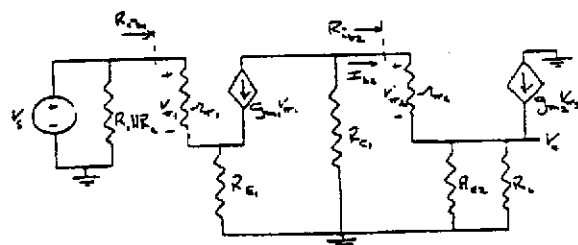
$$V_{CE2} = 5 - V_{E2} = 5 - 2.28 \Rightarrow \underline{V_{CE2} = 2.72 \text{ V}}$$



$$r_{\pi 1} = \frac{\beta V_T}{I_{CQ1}} = \frac{(125)(0.026)}{0.366} = 8.88 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ2}} = \frac{(125)(0.026)}{4.81} = 0.676 \text{ k}\Omega$$

$$g_{m1} = \frac{I_{CQ1}}{V_T} = \frac{0.366}{0.026} = 14.1 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ2}}{V_T} = \frac{4.81}{0.026} = 185 \text{ mA/V}$$

$$R_{ib1} = r_{\pi1} + (1 + \beta)R_{E1} = 8.88 + (126)(0.2) \\ = 34.08 \text{ k}\Omega$$

$$R_{ib2} = r_{\pi2} + (1 + \beta)(R_{E2} \parallel R_L) \\ = 0.676 + (126)(1.5 \parallel 10) = 165 \text{ k}\Omega$$

$$V_0 = (1 + \beta)I_{b2}(R_{E2} \parallel R_L)$$

$$I_{b2} = \left(\frac{R_{C1}}{R_{C1} + R_{ib2}} \right) (-g_{m1} V_{\pi1})$$

$$V_{\pi1} = \frac{V_S}{Z_1} \cdot r_{\pi1}$$

$$A_v = (1 + \beta)(R_{E2} \parallel R_L) \left(\frac{R_{C1}}{R_{C1} + R_{ib2}} \right) \left(\frac{-g_{m1} r_{\pi1}}{R_{ib1}} \right)$$

$$A_v = \frac{V_0}{V_S}$$

$$= -(126)(125)(1.5 \parallel 10) \left(\frac{5}{5 + 165} \right) \left(\frac{1}{34.08} \right)$$

$$= -(126)(125)(1.30) \left(\frac{5}{170} \right) \left(\frac{1}{34.08} \right)$$

$$A_v = -17.7$$

$$c. \quad R_i = R_1 \parallel R_2 \parallel R_{ib1} = (5.53) \parallel (34.1)$$

$$\Rightarrow R_i = 4.76 \text{ k}\Omega$$

$$R_0 = \left(\frac{r_{\pi2} + R_{C1}}{1 + \beta} \right) \parallel R_{E2} = \left(\frac{0.676 + 5}{126} \right) \parallel 1.5$$

$$= 0.0450 \parallel 1.5$$

$$\Rightarrow R_0 = 43.7 \Omega$$

E4.28

$$a. \quad I_{CQ2} = \left(\frac{100}{101} \right) (1 \text{ mA}) \Rightarrow I_{CQ2} = 0.990 \text{ mA}$$

$$I_{EQ1} = \frac{I_{EQ2}}{1 + \beta} = \frac{1}{101} \Rightarrow I_{EQ1} = 0.0099 \text{ mA}$$

$$I_{BQ1} = \frac{I_{EQ1}}{1 + \beta} = \frac{0.0099}{101}$$

$$\Rightarrow I_{BQ1} = 0.000098 \text{ mA}, \quad I_{CQ1} = 0.0098 \text{ mA}$$

$$V_{B1} = -I_{BQ1} R_B = -(0.000098)(10)$$

$$= -0.00098 \text{ V} \approx 0$$

$$V_{E1} = -0.7 \text{ V}, \quad V_{E2} = -1.4 \text{ V}$$

$$I_1 = I_{CQ2} + I_{CQ1} = 0.990 + 0.0098$$

$$I_1 \approx 1 \text{ mA} \Rightarrow V_0 = 5 - (1)(4) = 1 \text{ V}$$

$$V_{CEQ2} = 1 - (-1.4) = 2.4$$

$$\Rightarrow V_{CEQ2} = 2.4 \text{ V}, \quad I_{CQ2} = 0.990 \text{ mA}$$

$$V_{CEQ1} = 1 - (-0.7) = 1.7$$

$$\Rightarrow V_{CEQ1} = 1.7 \text{ V}, \quad I_{CQ1} = 0.0098 \text{ mA}$$

$$b. \quad r_{\pi} = \frac{\beta V_T}{I_{CQ}} \text{ and } g_m = \frac{I_{CQ}}{V_T}$$

For Q_1 :

$$r_{\pi1} = \frac{(100)(0.026)}{0.0098} \Rightarrow r_{\pi1} = 265 \text{ k}\Omega$$

$$g_{m1} = \frac{0.0098}{0.026} \Rightarrow g_{m1} = 0.377 \text{ mA/V}$$


For Q_2 :

$$r_{\pi2} = \frac{(100)(0.026)}{0.990} \Rightarrow r_{\pi2} = 2.63 \text{ k}\Omega$$

$$g_{m2} = \frac{0.99}{0.026} \Rightarrow g_{m2} = 38.1 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

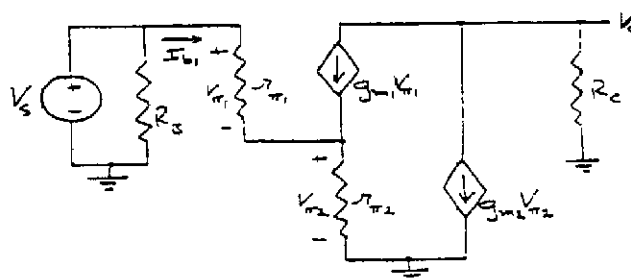

$$V_0 = -(g_{m1} V_{\pi1} + g_{m2} V_{\pi2}) R_C$$

$$V_S = V_{\pi1} + V_{\pi2}$$

$$V_{\pi2} = \left(\frac{V_{\pi1}}{r_{\pi1}} + g_{m1} V_{\pi1} \right) r_{\pi2} = \frac{(1 + \beta)}{r_{\pi1}} V_{\pi1} r_{\pi2}$$

Then

$$V_0 = - \left[g_{m1} V_{\pi1} + g_{m2} \left(\frac{(1 + \beta) r_{\pi2}}{r_{\pi1}} V_{\pi1} \right) \right] R_C$$

Also

$$V_S = V_{\pi1} + \left(\frac{1 + \beta}{r_{\pi1}} \right) V_{\pi1} r_{\pi2}$$

$$= V_{\pi1} \left[1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right) \right]$$

$$V_{\pi1} = \frac{V_S}{1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)}$$

$$V_0 = - \left[g_{m1} + g_{m2} (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right) \right] R_C$$

$$+ \frac{V_S}{1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)}$$

$$A_v = - \frac{\left[g_{m1} + g_{m2} (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right) \right] R_C}{1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)}$$

$$A_v = - \frac{\left[0.377 + (38.08)(101) \left(\frac{2.626}{265.3} \right) \right] (4)}{1 + (101) \left(\frac{2.626}{265.3} \right)}$$

$$A_v = - \frac{153.8}{1.9997} \Rightarrow A_v = -76.9$$

$$d. \quad R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$

$$R_i = 265.3 + (101)(2.626)$$

$$\Rightarrow R_i = 531 \text{ k}\Omega$$

E4.29

$$a. \quad I_{E1} = \frac{V_{E1} - (-10)}{20} + \frac{(V_{E1} - 0.7) - (-10)}{(1 + \beta)(10)}$$

$$-I_{B1} R_B - V_{BE(\text{on})} = V_{E1}$$

So

$$(1 + \beta) I_{B1} = \frac{10 - I_{B1} R_B - 0.7}{20} + \frac{10 - 0.7 - I_{B1} R_B - 0.7}{(101)(10)}$$

$$(101) I_{B1} + I_{B1} \left(\frac{20}{20} \right) + I_{B1} \cdot \frac{20}{(101)(10)} = \frac{9.3}{20} + \frac{8.6}{(101)(10)}$$

$$(102) I_{B1} = 0.465 + 0.00851$$

$$I_{B1} = 0.00464 \text{ mA} \Rightarrow V_{B1} = -0.09281$$

$$\Rightarrow V_{E1} = -0.793 \text{ V} \Rightarrow V_{E2} = -1.493 \text{ V}$$

$$I_{C1} = 0.464 \text{ mA}, \quad I_{E1} = 0.469 \text{ mA}$$

$$I_1 = \frac{10 - 0.793}{20} = 0.46035 \text{ mA}$$

$$\Rightarrow I_{B2} = I_{E1} - I_1$$

$$I_{B2} = 0.00855 \text{ mA} \Rightarrow I_{C2} = 0.865 \text{ mA}$$

$$\text{or } I_{E2} = \frac{10 - 1.493}{10} = 0.851 \Rightarrow I_{C2} = 0.842 \text{ mA}$$

$$I_C = I_{C1} + I_{C2} = 0.464 + 0.842$$

$$= 1.306 \text{ mA}$$

$$V_0 = 10 - (1.306)(2) = 7.39 \text{ V}$$

$$V_{CEQ2} = 7.39 - (-1.493)$$

$$\Rightarrow V_{CEQ2} = 8.88 \text{ V}, \quad I_{CQ2} = 0.842 \text{ mA}$$

$$V_{CEQ1} = 7.39 - (-0.793)$$

$$\Rightarrow V_{CEQ1} = 8.18 \text{ V}, \quad I_{CQ1} = 0.464 \text{ mA}$$

$$b. \quad r_{\pi} = \frac{\beta V_T}{I_{CQ}}, \quad g_m = \frac{I_{CQ}}{V_T}$$

For Q_1 :

$$r_{\pi 1} = \frac{(100)(0.026)}{0.464} \Rightarrow r_{\pi 1} = 5.60 \text{ k}\Omega$$


$$g_{m1} = \frac{0.464}{0.026} \Rightarrow g_{m1} = 17.8 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{0.842} \Rightarrow r_{\pi 2} = 3.09 \text{ k}\Omega$$

$$g_{m2} = \frac{0.842}{0.026} \Rightarrow g_{m2} = 32.4 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

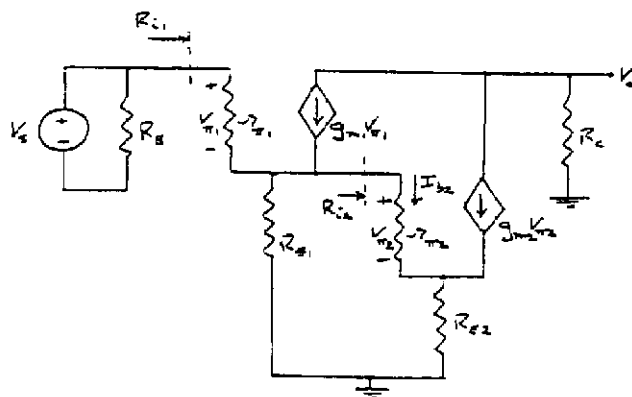

$$R_{i2} = r_{\pi 2} + (1 + \beta) R_{E2} = 3.09 + (101)(10) = 1013.1 \text{ k}\Omega$$

$$R_{i1} = r_{\pi 1} + (1 + \beta) [R_{E1} \parallel R_{i2}] = 5.60 + (101)[20 \parallel 1013.1]$$

$$d. \quad R_{i1} = 1.986 \text{ M}\Omega$$

Note that $g_{m1} V_{\pi 1} = \beta I_{b1}$ and $g_{m2} V_{\pi 2} = \beta I_{b2}$ So $V_0 = -[\beta I_{b1} + \beta I_{b2}] R_C$

$$I_{b1} = \frac{V_S}{R_{i1}} \text{ and } I_{b2} = \left(\frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta) I_{b1}$$

So

$$V_0 = -[I_{b1} + I_{b2}] \beta R_C$$

$$= - \left\{ I_{b1} + \left(\frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta) I_{b1} \right\} \beta R_C$$

$$A_v = \frac{V_0}{V_S} = - \left[1 + \left(\frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta) \right] \frac{\beta R_C}{R_{i1}}$$

$$= - \left[1 + \left(\frac{20}{20 + 1013.1} \right) (101) \right] \frac{(100)(2)}{1986}$$

$$A_v = -0.298$$

E4.30

a. dc analysis

$$\beta = 100, \quad V_{BE(\text{on})} = 0.7 \text{ V}, \quad V_A = \infty$$

$$\text{Want: } I_{CQ2} = 0.5 \text{ mA}, \quad V_{CE1} = V_{CE2} = 4 \text{ V}$$

$$R_1 + R_2 + R_3 = 100 \text{ k}\Omega$$

Neglecting base currents:

$$I_1 = \frac{12}{100} = 0.12 \text{ mA}$$

$$V_{E1} = I_{CQ2} R_E = (0.5)(0.5) = 0.25 \text{ V}$$

$$V_{C1} = V_{CEQ1} + V_{E1} = 4 + 0.25 = 4.25$$

So

$$V_{C2} = V_{C1} + V_{CEQ2} = 4.25 + 4 = 8.25 \text{ V}$$

$$R_C = \frac{V_{CC} - V_{C2}}{I_{CQ}} = \frac{12 - 8.25}{0.5} \Rightarrow R_C = 7.5 \text{ k}\Omega$$

$$V_{B1} = V_{E1} + 0.7 = 0.25 + 0.7 = 0.95 \text{ V}$$

$$V_{B1} = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) (12) \Rightarrow 0.95 = \frac{R_3}{100} (12)$$

$$\Rightarrow R_3 = 7.92 \text{ k}\Omega$$

$$V_{B2} = V_{C1} + 0.7 = 4.25 + 0.7 = 4.95$$

$$V_{B2} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (12)$$

$$\Rightarrow 4.95 = \frac{R_2 + 7.92}{100} (12)$$

$$R_2 = \frac{(4.95)(100)}{12} - 7.92 \Rightarrow R_2 = 33.3 \text{ k}\Omega$$

$$R_1 = 100 - R_2 - R_3 = 100 - 33.3 - 7.92$$

$$\Rightarrow R_1 = 58.8 \text{ k}\Omega$$

b. For both Q_1 and Q_2

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5}$$


$$\Rightarrow r_{\pi1} = r_{\pi2} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026}$$

$$\Rightarrow g_{m1} = g_{m2} = 19.23 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

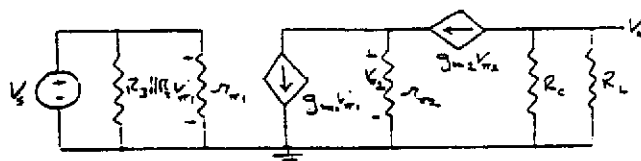

$$v_O = -g_{m2} V_{\pi2} (R_C \parallel R_L)$$

$$\frac{V_{\pi2}}{r_{\pi2}} + g_{m2} V_{\pi2} = g_{m1} V_{\pi1}$$

$$V_{\pi2} \left(\frac{1 + \beta}{r_{\pi2}} \right) = g_{m1} V_{\pi1}$$

$$V_{\pi2} = g_{m1} V_{\pi1} \left(\frac{r_{\pi2}}{1 + \beta} \right) \text{ and } V_{\pi1} = v_{\pi}$$

So

$$A_v = \frac{v_O}{v_{\pi}} = -g_{m2} (R_C \parallel R_L) \cdot g_{m1} \left(\frac{r_{\pi2}}{1 + \beta} \right)$$

$$= -g_{m2} (R_C \parallel R_L) \left(\frac{\beta}{1 + \beta} \right)$$

$$A_v = - \left(\frac{100}{101} \right) (19.23)(7.5 \parallel 2) \Rightarrow A_v = -30.1$$

E4.31

a. dc analysis

$$\beta = 80, V_{BE}(\text{on}) = 0.7, V_A = \infty$$

$$I_{BQ} = \frac{2.32 - 0.7}{24.2 + (81)(0.5)} = \frac{1.62}{64.7}$$

$$I_{BQ} = 0.0250 \text{ mA}, I_{CQ} = 2.00 \text{ mA}$$

$$\text{Power dissipated in } R_C = I_{CQ}^2 R_C = (2.0)^2 (2)$$

$$\Rightarrow P_C = 8.0 \text{ mW}$$

$$\text{Power dissipated in } R_L = 0, P_L = 0$$

$$V_{CE} = V_{CC} - I_C \left[R_C + \left(\frac{1 + \beta}{\beta} \right) R_E \right]$$

$$= 12 - 2 \left[2 + \left(\frac{81}{80} \right) (0.5) \right]$$

$$V_{CE} = 6.99 \text{ V}$$

$$P_T = I_B V_{BE} + I_C V_{CE} = (0.0259)(0.7) + (2)(6.99)$$

$$\Rightarrow P_T = 14.0 \text{ mW}$$

$$b. r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(80)(0.026)}{2.0} \Rightarrow r_{\pi} = 1.04 \text{ k}\Omega$$

$$\text{For } v_s = 18 \cos \omega t \text{ mV}$$

From the text, power dissipation in the transistor

$$P_T = V_{CEQ} I_{CQ} - \left(\frac{\beta}{r_{\pi}} \right)^2 \left(\frac{V_P}{\sqrt{2}} \right)^2 (R_C \parallel R_L)$$

$$= (6.99)(2 \times 10^{-3})$$

$$- \left(\frac{80}{1.04 \times 10^3} \right)^2 \left(\frac{0.018}{\sqrt{2}} \right)^2 (2 \times 10^3 \parallel 2 \times 10^3)$$

$$P_T = (14 - 0.96) \text{ mW} \Rightarrow P_T = 13.0 \text{ mW}$$

From notes

$$|v_{ce}| = \frac{\beta}{r_{\pi}} (R_C \parallel R_L) V_P \cos \omega t$$

Power dissipated in R_L

$$P_L = \frac{|v_{ce}|^2}{R_L} \Big|_{\text{rms}} = \left[\frac{\beta}{r_{\pi}} (R_C \parallel R_L) \right]^2 \times \frac{1}{R_L} \times \frac{V_P^2}{2}$$

$$= \left[\frac{80}{1.04} (1.0) \right]^2 \times \frac{1}{2 \times 10^3} \times \left(\frac{0.018}{2} \right)^2$$

$$\Rightarrow P_L = 0.479 \text{ mW}$$

$$R_C = 2 \text{ k}\Omega \text{ also so } P_C = 8.0 + 0.479$$

$$\Rightarrow P_C = 8.48 \text{ mW}$$

E4.32

$$\beta = 100, V_{BE(on)} = 0.7 \text{ V}, V_A = \infty$$

$$\text{a. } R_{TH} = R_1 || R_2 = 10 || 53.8 = 8.43 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (5) = \left(\frac{10}{10 + 53.8} \right) (5)$$

$$V_{TH} = 0.7837$$

$$I_{BQ} = \frac{0.7837 - 0.7}{8.43} = 0.00993 \text{ mA}$$

$$I_{CQ} = 0.993 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C$$

$$2.5 = 5 - (0.993) R_C \Rightarrow \underline{R_C = 2.52 \text{ k}\Omega}$$

$$\text{b. Power in } R_C = P_R = I_C^2 R_C = (0.993)^2 (2.52)$$

$$\Rightarrow \underline{P_R = 2.48 \text{ mW}}$$

$$\text{Power in } Q \approx P_Q \approx I_{CQ} V_{CEQ} = (0.993)(2.5)$$

$$\Rightarrow \underline{P_Q = 2.48 \text{ mW}}$$

$$\text{c. } i_C = 0.993 \cos \omega t$$

$$\text{ac power} = \frac{1}{2} \times (0.993)^2 \times R_C = 1.24 \text{ mW}$$

$$\text{in } R_C$$

$$\frac{1.24}{2.48 + 2.48} = \underline{0.25}$$

Chapter 4

Problem Solutions

4.1

$$a. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{2}{0.026} \Rightarrow g_m = 76.9 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(180)(0.026)}{2} \Rightarrow r_\pi = 2.34 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{2} \Rightarrow r_o = 75 \text{ k}\Omega$$

$$b. \quad g_m = \frac{0.5}{0.026} \Rightarrow g_m = 19.2 \text{ mA/V}$$

$$r_\pi = \frac{(180)(0.026)}{0.5} \Rightarrow r_\pi = 9.36 \text{ k}\Omega$$

$$r_o = \frac{150}{0.5} \Rightarrow r_o = 300 \text{ k}\Omega$$

4.2

$$g_m = \frac{I_{CQ}}{V_T} \Rightarrow 200 = \frac{I_{CQ}}{0.026} \Rightarrow I_{CQ} = 5.2 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(125)(0.026)}{5.2} \Rightarrow r_\pi = 0.625 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{5.2} \Rightarrow r_o = 38.5 \text{ k}\Omega$$

4.3

$$(a) \quad I_{BQ} = \frac{2-0.7}{250} = 0.0052 \text{ mA}$$

$$I_C = (120)(0.0052) = 0.624 \text{ mA}$$

$$g_m = \frac{0.624}{0.026} \Rightarrow g_m = 24 \text{ mA/V}$$

$$r_\pi = \frac{(120)(0.026)}{0.624} \Rightarrow r_\pi = 5 \text{ k}\Omega$$

$$r_o = \infty$$

$$(b) \quad A_v = -g_m R_C \left(\frac{r_\pi}{r_\pi + R_B} \right) = -(24)(4) \left(\frac{5}{5+250} \right) \Rightarrow$$

$$A_v = -1.88$$

$$(c) \quad v_s = \frac{v_o}{A_v} = \frac{v_o}{-1.88} \Rightarrow$$

$$v_s = -0.426 \sin 100t \text{ V}$$

4.4

$$g_m = \frac{I_{CQ}}{V_T}, \quad 1.08 \leq I_{CQ} \leq 1.32 \text{ mA}$$

$$\frac{1.08}{0.026} \leq g_m \leq \frac{1.32}{0.026} \Rightarrow 41.5 \leq g_m \leq 50.8 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}; \quad r_\pi(\text{max}) = \frac{(120)(0.026)}{1.08} = 2.89 \text{ k}\Omega$$

$$r_\pi(\text{min}) = \frac{(80)(0.026)}{1.32} = 1.58 \text{ k}\Omega$$

$$1.58 \leq r_\pi \leq 2.89 \text{ k}\Omega$$

4.5

$$a. \quad r_\pi = 5.4 = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{I_{CQ}}$$

$$\Rightarrow I_{CQ} = 0.578 \text{ mA}$$

$$V_{CEQ} = \frac{1}{2} V_{CC} = \frac{1}{2}(5) = 2.5 \text{ V}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C \Rightarrow 2.5 = 5.0 - (0.578) R_C$$

$$\Rightarrow R_C = 4.33 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.578}{120} = 0.00482 \text{ mA}$$

$$V_{BB} = I_{BQ} R_B + V_{BE(\text{on})}$$

$$= (0.00482)(25) + 0.70$$

$$\Rightarrow V_{BB} = 0.821$$

$$b. \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{0.578} = 5.40 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.578}{0.026} = 22.2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.578} = 173 \text{ k}\Omega$$

$$V_o = -g_m(r_o \parallel R_C) V_\pi, \quad V_\pi = \left(\frac{r_\pi}{r_\pi + R_B} \right) V_s$$

$$A_v = -g_m \left(\frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C) = -\frac{\beta(r_o \parallel R_C)}{r_\pi + R_B}$$

$$A_v = -\frac{(120)[173 \parallel 4.33]}{5.40 + 25} = -\frac{(120)(4.22)}{30.4}$$

$$\Rightarrow A_v = -16.7$$

4.6

$$a. \quad V_{ECQ} = \frac{1}{2} V_{CC} = 5 \text{ V}$$

$$V_{ECQ} = 10 - I_{CQ} R_C \Rightarrow 5 = 10 - (0.5) R_C$$

$$\Rightarrow R_C = 10 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.5}{100} = 0.005$$

$$V_{EB(\text{on})} + I_{BQ} R_B = V_{BB} = (0.70) + (0.005)(50)$$

$$\Rightarrow V_{BB} = 0.95 \text{ V}$$

$$b. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} \Rightarrow g_m = 19.2 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5} \Rightarrow r_\pi = 5.2 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.5} \Rightarrow r_o = \infty$$

$$c. \quad A_v = -\frac{\beta R_C}{r_\pi + R_B} = -\frac{(100)(10)}{5.2 + 50} \Rightarrow A_v = -18.1$$

4.7 a. $I_E = 0.35 \text{ mA}$, $I_B = \frac{0.35}{101} = 0.00347 \text{ mA}$

$$V_B = -I_B R_B = -(0.00347)(10)$$

$$\Rightarrow V_B = -0.0347 \text{ V}$$

$$V_E = V_B - V_{BE(\text{on})} \Rightarrow V_E = -0.735 \text{ V}$$

b. $V_C = V_{CEQ} + V_E = 3.5 - 0.735 = 2.77 \text{ V}$

$$I_C = \left(\frac{\beta}{1 + \beta} \right) I_E = \left(\frac{100}{101} \right) (0.35) = 0.347 \text{ mA}$$

$$R_C = \frac{V^+ - V_C}{I_C} = \frac{5 - 2.77}{0.347} \Rightarrow R_C = 6.43 \text{ k}\Omega$$

(c) $A_v = -g_m \left(\frac{R_B \| r_\pi}{R_B \| r_\pi + R_S} \right) (R_C \| r_o)$

$$g_m = \frac{0.347}{0.026} = 13.3 \text{ mA/V}, \quad r_o = \frac{100}{0.347} = 288 \text{ k}\Omega$$

$$r_\pi = \frac{(100)(0.026)}{0.347} = 7.49 \text{ k}\Omega$$

$$R_B \| r_\pi = 10 \| 7.49 = 4.28 \text{ k}\Omega$$

$$A_v = -(13.3) \left(\frac{4.28}{4.28 + 0.1} \right) (6.43 \| 288) \Rightarrow$$

$$A_v = -81.7$$

d. $A_v = -g_m \left(\frac{R_B \| r_\pi}{R_B \| r_\pi + R_S} \right) (R_C \| r_o)$

$$R_B \| r_\pi = 10 \| 7.49 = 4.28 \text{ k}\Omega$$

$$A_v = -(13.3) \left(\frac{4.28}{4.28 + 0.5} \right) (6.43 \| 288)$$

$$\Rightarrow A_v = -74.9$$

4.8

a. $R_{TH} = R_1 \| R_2 = 6 \| 1.5 = 1.2 \text{ k}\Omega$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V^+ = \left(\frac{1.5}{1.5 + 6} \right) (5) = 1.0 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_E} = \frac{1.0 - 0.7}{1.2 + (101)(0.1)} = 0.0155 \text{ mA}$$

$$I_{CQ} = 2.80 \text{ mA}, \quad I_{EQ} = 2.81$$

$$V_{CEQ} = V^+ - I_{CQ}R_C - I_{EQ}R_E = 5 - (2.8)(1) - (2.81)(0.1)$$

$$\Rightarrow V_{CEQ} = 1.92 \text{ V}$$

b. $r_\pi = \frac{(100)(0.026)}{2.80} \Rightarrow r_\pi = 1.67 \text{ k}\Omega$

$$g_m = \frac{2.80}{0.026} \Rightarrow g_m = 108 \text{ mA/V}, \quad r_o = \infty$$

(c) $A_v = -g_m \left(\frac{R_1 \| R_2 \| r_\pi}{R_1 \| R_2 \| r_\pi + R_S} \right) (R_C \| R_L)$

$$R_1 \| R_2 \| r_\pi = 6 \| 1.5 \| 1.67 = 0.698 \text{ k}\Omega$$

$$A_v = -(108) \left(\frac{0.698}{0.698 + 0.2} \right) (1 \| 1.2) \Rightarrow$$

$$A_v = -45.8$$

4.9

a. $I_{CQ} \approx I_{EQ}$

$$V_{CEQ} = 5 = 10 - I_{CQ}(R_C + R_E)$$

$$= 10 - I_{CQ}(1.2 + 0.2)$$

$$I_{CQ} = 3.57 \text{ mA}$$

$$I_{BQ} = \frac{3.57}{150} = 0.0238 \text{ mA}$$

$$R_1 \| R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(151)(0.2) = 3.02 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot (10) - 5$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(\text{on})} + (1 + \beta)I_{BQ}R_E - 5$$

$$\frac{1}{R_1}(3.02)(10) - 5 = (0.0238)(3.02) + 0.7$$


$$+ (151)(0.0238)(0.2) - 5$$

$$\frac{1}{R_1}(30.2) = 1.49 \Rightarrow R_1 = 20.3 \text{ k}\Omega$$

$$\frac{20.3R_2}{20.3 + R_2} = 3.02 \Rightarrow R_2 = 3.55 \text{ k}\Omega$$

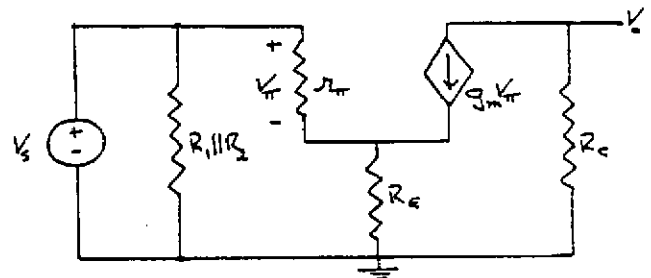b. $r_\pi = \frac{(150)(0.026)}{3.57} = 1.09 \text{ k}\Omega$

$$g_m = \frac{3.57}{0.026} = 137 \text{ mA/V}$$



$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} = -\frac{(150)(1.2)}{1.09 + (151)(0.2)}$$

$$\Rightarrow A_v = -5.75$$

4.10

$$a. \quad V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{50}{50 + 10} \right) (12) = 10 \text{ V}$$


$$R_{TH} = R_1 || R_2 = 50 || 10 = 8.33 \text{ k}\Omega$$

$$I_{BQ} = \frac{12 - 0.7 - 10}{8.33 + (101)(1)} = 0.0119 \text{ mA}$$


$$I_{CQ} = 1.19 \text{ mA}, \quad I_{EQ} = 1.20 \text{ mA}$$

$$V_{ECQ} = 12 - (1.20)(1) - (1.19)(2)$$

$$V_{ECQ} = 8.42 \text{ V}$$

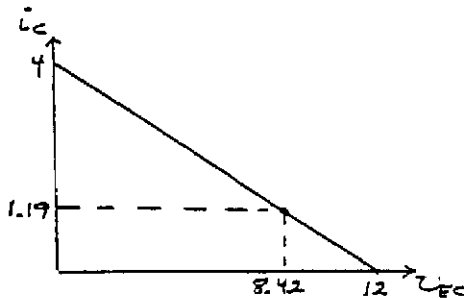

b.

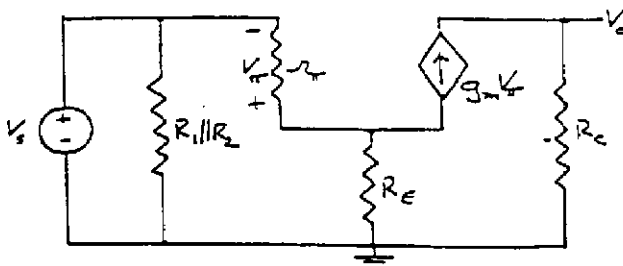

$$r_\pi = \frac{(100)(0.026)}{1.19} = 2.18 \text{ k}\Omega$$

$$V_o = g_m V_\pi R_C$$

$$V_s = -V_\pi - \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) R_E$$

$$= -V_\pi \left[\frac{r_\pi + (1 + \beta) R_E}{r_\pi} \right]$$

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E} = \frac{-(100)(2)}{2.18 + (101)(1)}$$

$$\Rightarrow A_v = -1.94$$

 c. Approximation: Assume r_π does not vary significantly.

$$R_C = 2 \text{ k}\Omega \pm 5\% = 2.1 \text{ k}\Omega \text{ or } 1.9 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega \pm 5\% = 1.05 \text{ k}\Omega \text{ or } 0.95 \text{ k}\Omega$$

 For $R_C(\text{max}) = 2.1 \text{ k}\Omega$ and $R_E(\text{min})$

$$A_v = \frac{-(100)(2.1)}{2.18 + (101)(0.95)} = -2.14$$

 For $R_C(\text{min}) = 1.9 \text{ k}\Omega$ and $R_E(\text{max}) = 1.05 \text{ k}\Omega$

$$A_v = \frac{-(100)(1.9)}{2.18 + (101)(1.05)} = -1.76$$

 So $1.76 \leq |A_v| \leq 2.14$

4.11

$$(a) \quad V_{CC} = \left(\frac{1 + \beta}{\beta} \right) I_{CQ} R_E + V_{ECQ} + I_{CQ} R_C$$

$$12 = \left(\frac{101}{100} \right) I_{CQ}(1) + 6 + I_{CQ}(2)$$

 so that $I_{CQ} = 1.99 \text{ mA}$

$$I_{BQ} = \frac{1.99}{100} = 0.0199 \text{ mA}$$

$$R_{TH} = (0.1)(1 + \beta) R_E = (0.1)(101)(1) = 10.1 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} R_{TH} V_{CC} = \frac{1}{R_1} (10.1)(12)$$

$$V_{CC} = (1 + \beta) I_{BQ} R_E + V_{EB}(\text{on}) + I_{BQ} R_{TH} + V_{TH}$$

$$12 = (101)(0.0199)(1) + 0.7 + (0.0199)(10.1) + \frac{121.2}{R_1}$$

 which yields $R_1 = 13.3 \text{ k}\Omega$ and $R_2 = 42 \text{ k}\Omega$

$$(b) \quad A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E} = \frac{-(100)(2)}{1.31 + (101)(1)}$$

$$A_v = -1.95$$

4.12

$$I_{CQ} = 0.25 \text{ mA}, \quad I_{EQ} = 0.2525 \text{ mA}$$

$$I_{BQ} = 0.0025 \text{ mA}$$

$$I_{BQ} R_B + V_{BE}(\text{on}) + I_{EQ} (R_S + R_E) - 5 = 0$$

$$(0.0025)(50) + 0.7 + (0.2525)(0.1 + R_E) = 5$$

$$R_E = 16.4 \text{ k}\Omega$$

$$V_E = -(0.0025)(50) - 0.7 = -0.825 \text{ V}$$

$$V_C = V_{CEQ} + V_E = 3 - 0.825 = 2.175 \text{ V}$$

$$R_C = \frac{5 - 2.175}{0.25} \Rightarrow R_C = 11.3 \text{ k}\Omega$$

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E}$$

$$r_\pi = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$A_v = \frac{-(100)(11.3)}{10.4 + (101)(0.1)} \Rightarrow A_v = -55.1$$

$$R_1 = R_B || [r_\pi + (1 + \beta) R_S]$$

$$= 50 || [10.4 + (101)(0.1)]$$

$$R_1 = 50 || 20.5 \Rightarrow R_1 = 14.5 \text{ k}\Omega$$

4.13

$$a. \quad 9 = I_{EQ} R_E + V_{EB(on)} + I_{BQ} R_S$$

$$I_{EQ} = 0.75 \text{ mA}, \quad I_{BQ} = \frac{0.75}{81} = 0.00926 \text{ mA}$$

$$I_{CQ} = 0.741 \text{ mA}$$

$$9 = (0.75)R_E + 0.7 + (0.00926)(2)$$

$$\Rightarrow \underline{R_E = 11.0 \text{ k}\Omega}$$

$$b. \quad V_E = 9 - (0.75)(11) = 0.75 \text{ V}$$

$$V_C = V_E - V_{ECQ} = 0.75 - 7 = -6.25 \text{ V}$$

$$R_C = \frac{V_C - (-9)}{I_{CQ}} = \frac{9 - 6.25}{0.741} \Rightarrow \underline{R_C = 3.71 \text{ k}\Omega}$$

$$c. \quad A_v = -g_m \left(\frac{r_\pi}{r_\pi + R_S} \right) (R_C \parallel R_L \parallel r_o)$$

$$r_\pi = \frac{(80)(0.026)}{0.741} = 2.81 \text{ k}\Omega$$

$$r_o = \frac{80}{0.741} = 108 \text{ k}\Omega$$

$$A_v = \frac{-80}{2.81 + 2} (3.71 \parallel 10 \parallel 108)$$

$$\underline{A_v = -43.9}$$

$$d. \quad R_i = R_S + r_\pi = 2 + 2.81 \Rightarrow \underline{R_i = 4.81 \text{ k}\Omega}$$

4.14

$$(a) \quad V_{CC} \cong I_{CQ}(R_C + R_E) + V_{CEQ}$$

$$9 = I_{CQ}(2.2 + 2) + 3.75 \text{ So that}$$

$$\underline{I_{CQ} = 1.25 \text{ mA}}$$


$$(b) \quad g_m = \frac{1.25}{0.026} = 48.1 \text{ mA/V}$$

$$r_\pi = \frac{(120)(0.026)}{1.25} = 2.50 \text{ k}\Omega$$

$$r_o = \frac{100}{1.25} = 80 \text{ k}\Omega$$

Assume circuit is to be designed to be bias stable.
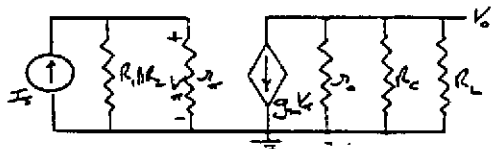
$$R_{TH} = R_1 \parallel R_2 = (0.1)(1 + \beta)R_E = (0.1)(121)(2) = 24.2 \text{ k}\Omega$$



$$V_o = -g_m V_x (r_o \parallel R_C \parallel R_L)$$

$$V_x = I_s (R_1 \parallel R_2 \parallel r_\pi)$$

Then

$$R_m = \frac{V_o}{I_s} = -g_m (R_1 \parallel R_2 \parallel r_\pi) (r_o \parallel R_C \parallel R_L)$$

$$R_m = -48.1(24.2 \parallel 2.5)(80 \parallel 2.2 \parallel 1) = -48.1(2.27)(0.682)$$

or

$$R_m = \frac{V_o}{I_s} = -74.5 \text{ k}\Omega = -74.5 \text{ V/mA}$$

4.15

$$a. \quad I_{EQ} = 0.80 \text{ mA}, \quad I_{BQ} = \frac{0.80}{66} = 0.0121 \text{ mA}$$

$$I_{CQ} = 0.788 \text{ mA}$$

$$V_B = I_{BQ} R_B \Rightarrow R_B = \frac{0.3}{0.0121} \Rightarrow \underline{R_B = 24.8 \text{ k}\Omega}$$

$$R_C = \frac{V_C - (-5)}{I_{CQ}} = \frac{5 - 3}{0.788} \Rightarrow \underline{R_C = 2.54 \text{ k}\Omega}$$

$$b. \quad g_m = \frac{0.788}{0.026} = 30.3 \text{ mA/V}$$

$$r_\pi = \frac{(65)(0.026)}{0.788} = 2.14 \text{ k}\Omega$$

$$r_o = \frac{75}{0.788} = 95.2 \text{ k}\Omega$$

$$i_o = \left(\frac{R_C \parallel r_o}{R_C \parallel r_o + R_L} \right) g_m V_\pi, \quad V_\pi = -v_s$$

$$G_f = \frac{i_o}{v_s} = -g_m \left(\frac{R_C \parallel r_o}{R_C \parallel r_o + R_L} \right) = -(30.3) \left(\frac{2.54 \parallel 95.2}{2.54 \parallel 95.2 + 4} \right)$$

$$\underline{G_f = -11.6 \text{ mA/V}}$$


4.16

$$I_{BQ} = \frac{4 - 0.7}{5 + (101)(5)} = 0.00647$$

$$I_{CQ} = 0.647 \text{ mA}$$

$$a. \quad 80 \leq h_{fe} \leq 120, \quad 10 \leq h_{oe} \leq 20 \text{ }\mu\text{S}$$
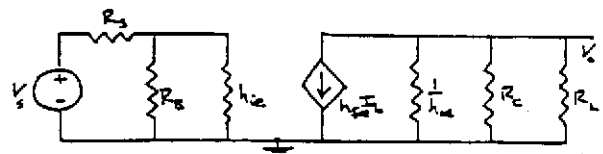
$$\underbrace{2.45 \text{ k}\Omega}_{\text{low gain}} \leq h_{ie} \leq \underbrace{3.7 \text{ k}\Omega}_{\text{high gain}}$$



$$V_o = -h_{fe} I_b \left(\frac{1}{h_{oe}} \parallel R_C \parallel R_L \right)$$

$$I_b = \frac{R_B}{R_{TH} + R_B} \cdot V_s$$

$$R_{TH} = R_B \parallel R_S = 5 \parallel 1 = 0.833 \text{ k}\Omega$$

High-gain

$$I_b = \frac{\left(\frac{5}{5+1}\right)V_S}{0.833 + 3.7} = 0.1938V_S$$

Low-gain

$$I_b = \frac{\left(\frac{5}{5+1}\right)V_S}{0.833 + 2.45} = 0.2538V_S$$

For

$$h_{oe} = 10 \Rightarrow \frac{1}{h_{oe}} \parallel R_C \parallel R_L = \frac{1}{0.010} \parallel 4 \parallel 4$$

$$= 100 \parallel 2 = 1.96 \text{ k}\Omega$$

For

$$h_{oe} = 20 \Rightarrow \frac{1}{0.020} \parallel 4 \parallel 4 = 50 \parallel 2 = 1.92 \text{ k}\Omega$$

$$|A_v|_{\max} = (120)(0.1938)(1.96) = 43.2$$

$$|A_v|_{\min} = (80)(0.2538)(1.92) = 39.0$$

$$39.0 \leq |A_v| \leq 43.2$$

$$\text{b. } R_1 = R_B \parallel h_{ie} = 5 \parallel 3.7 = 2.13 \text{ k}\Omega$$

$$\text{or } R_1 = 5 \parallel 2.45 = 1.64 \text{ k}\Omega$$


$$1.64 < R_1 < 2.13 \text{ k}\Omega$$

$$R_0 = \frac{1}{h_{oe}} \parallel R_C = \frac{1}{0.010} \parallel 4 = 100 \parallel 4 = 3.85 \text{ k}\Omega$$

$$\text{or } R_0 = \frac{1}{0.020} \parallel 4 = 50 \parallel 4 = 3.70 \text{ k}\Omega$$

$$3.70 < R_0 < 3.85 \text{ k}\Omega$$

4.17

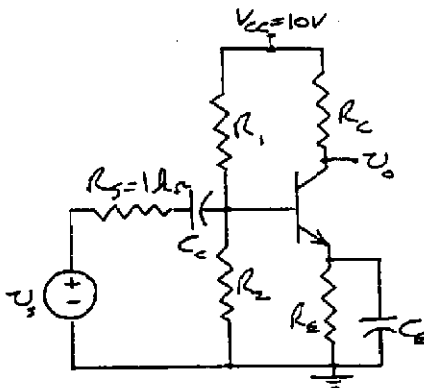

Assume an npn transistor with $\beta = 100$ and $V_A = \infty$. Let $V_{CC} = 10 \text{ V}$.

$$|A_v| = \frac{0.5}{0.01} = 50$$

Bias at $I_{CQ} = 1 \text{ mA}$ and let $R_E = 1 \text{ k}\Omega$

For a bias stable circuit

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(1) = 10.1 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (10.1)(10) = \frac{101}{R_1}$$

$$I_{BQ} = \frac{1}{100} = 0.01 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$$

$$\frac{101}{R_1} = (0.01)(10.1) + 0.7 + (101)(0.01)(1)$$

which yields $R_1 = 55.8 \text{ k}\Omega$ and $R_2 = 12.3 \text{ k}\Omega$

Now

$$r_\pi = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

$$V_o = -g_m V_\pi R_C$$

where

$$V_\pi = \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) \cdot V_s = \left(\frac{10.1 \parallel 2.6}{10.1 \parallel 2.6 + 1} \right) \cdot V_s$$

or

$$V_\pi = 0.674V_s$$

Then

$$A_v = \frac{V_o}{V_s} = -(0.674)g_m R_C = -(0.674)(38.46)R_C = -50$$

which yields $R_C = 1.93 \text{ k}\Omega$

With this R_C , the dc bias is OK.

4.18

$$\text{a. } I_{BQ} = \frac{6 - 0.7}{10 + (101)(3)} = 0.0169 \text{ mA}$$

$$I_{CQ} = 1.69 \text{ mA}, I_{EQ} = 1.71 \text{ mA}$$

$$V_{CEQ} = (16 + 6) - (1.69)(6.8) - (1.71)(3)$$

$$V_{CEQ} = 5.38 \text{ V}$$

$$\text{b. } g_m = \frac{1.69}{0.026} \Rightarrow g_m = 65 \text{ mA/V}$$

$$r_\pi = \frac{(100)(0.026)}{1.69} \Rightarrow r_\pi = 1.54 \text{ k}\Omega, r_o = \infty$$

$$\text{(c) } A_v = \frac{-\beta(R_C \parallel R_L)}{r_\pi + (1 + \beta)R_E} \cdot \frac{R_B \parallel R_b}{R_B \parallel R_b + R_s}$$

$$R_b = r_\pi + (1 + \beta)R_E = 1.54 + (101)(3) = 304.5 \text{ k}\Omega$$

$$R_B \parallel R_b = 10 \parallel 304.5 = 9.68 \text{ k}\Omega$$

Then

$$A_v = \frac{-(100)(6.8 \parallel 6.8)}{1.54 + (101)(3)} \cdot \left(\frac{9.68}{9.68 + 0.5} \right) \Rightarrow$$

$$A_v = -1.06$$

$$i_o = \left(\frac{R_C}{R_C + R_L} \right) (-\beta i_b)$$

$$i_b = \left(\frac{R_B}{R_B + r_\pi + (1 + \beta)R_E} \right) i_s$$

$$A_v = -(\beta) \left(\frac{R_C}{R_C + R_L} \right) \left(\frac{R_B}{R_B + r_\pi + (1 + \beta)R_E} \right)$$

$$= -(100) \left(\frac{6.8}{6.8 + 6.8} \right) \left(\frac{10}{10 + 1.54 + (101)(3)} \right)$$

$$\Rightarrow A_v = -1.59$$

$$(d) R_u = R_s + R_b \parallel R_b = 0.5 + 10 \parallel 304.5 = 10.2 \text{ k}\Omega$$


$$(e) A_v = \frac{-\beta(R_c \parallel R_L)}{r_x + (1 + \beta)R_E} \cdot \frac{R_b \parallel R_b}{R_b \parallel R_b + R_s}$$

$$A_v = \frac{-(100)(6.8 \parallel 6.8)}{154 + (101)(3)} \cdot \left(\frac{9.68}{9.68 + 1} \right) \Rightarrow$$

$$A_v = -1.01$$

$$A_i = \text{same as (c)} \Rightarrow A_i = -1.59$$

4.19

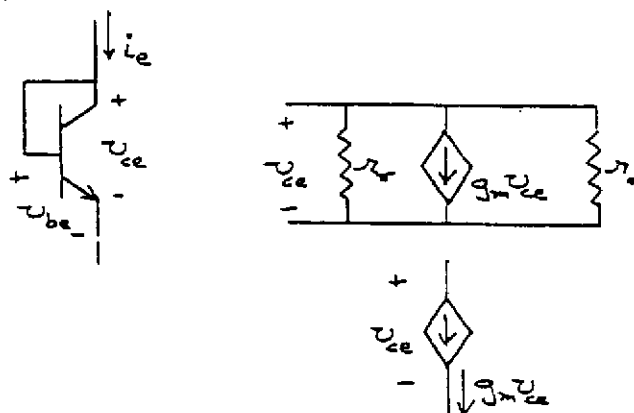


$$r = \frac{v_{ce}}{g_m v_{ce}} = \frac{1}{g_m}$$

$$\text{So } r_e = r_x \parallel \left(\frac{1}{g_m} \right) \parallel r_o$$

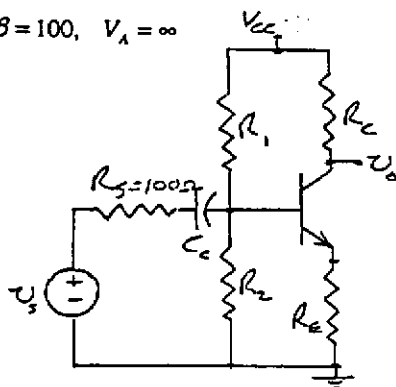4.20

$$\text{Let } \beta = 100, V_A = \infty$$



$$\text{Let } V_{cc} = 2.5 \text{ V}$$

$$P = (I_R + I_C)V_{cc} \Rightarrow 0.12 = (I_R + I_C)(2.5) \Rightarrow$$

$$I_R + I_C = 48 \mu\text{A}, \text{ Let } I_R = 8 \mu\text{A}, I_C = 40 \mu\text{A}$$

$$R_1 + R_2 = \frac{V_{cc}}{I_R} = \frac{2.5}{8} \Rightarrow 312.5 \text{ k}\Omega$$

$$I_{BQ} = \frac{40}{100} = 0.4 \mu\text{A}$$

Let $R_E = 2 \text{ k}\Omega$. For a bias stable circuit

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(2) = 20.2 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1} (20.2)(2.5) = (0.0004)(20.2) + 0.7$$

$$+ (101)(0.0004)(2)$$

which yields $R_1 = 64 \text{ k}\Omega$ and $R_2 = 29.5 \text{ k}\Omega$

$$r_x = \frac{(100)(0.026)}{0.04} = 65 \text{ k}\Omega \quad \text{Neglect } R_s$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta R_C}{r_x + (1 + \beta)R_E}$$

$$-10 = \frac{-100R_C}{65 + (101)(2)} \Rightarrow R_C = 26.7 \text{ k}\Omega$$

With this R_C , dc biasing is OK.

4.21

$$\text{Need a voltage gain of } \frac{100}{5} = 20.$$

Assume a sign inversion from a common-emitter is not important. Use the configuration for Figure 4.28. Need an input resistance of

$$R_i = \frac{5 \times 10^{-3}}{0.2 \times 10^{-6}} = 25 \times 10^3 = 25 \text{ k}\Omega$$

$$R_i = R_{TH} \parallel R_b. \text{ Let } R_{TH} = 50 \text{ k}\Omega, R_b = 50 \text{ k}\Omega$$

$$R_b = r_x + (1 + \beta)R_E \approx (1 + \beta)R_E$$

$$\text{For } \beta = 100, R_E = \frac{R_b}{1 + \beta} = \frac{50}{101} = 0.495 \text{ k}\Omega$$

$$\text{Let } R_E = 0.5 \text{ k}\Omega, V_{CC} = 10 \text{ V}, I_{CQ} = 0.2 \text{ mA}$$

$$\text{Then } I_{BQ} = \frac{0.2}{100} = 0.002 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (50)(10) = (0.002)(50) + 0.7$$

$$+ (101)(0.002)(0.5)$$

which yields $R_1 = 555 \text{ k}\Omega$ and $R_2 = 55 \text{ k}\Omega$

Now


$$A_v = \frac{-\beta R_C}{r_x + (1 + \beta)R_E}, \quad r_x = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

so

$$-20 = \frac{-(100)R_C}{13 + (101)(0.5)} \Rightarrow R_C = 12.7 \text{ k}\Omega$$

[Note: $I_{CQ}R_C = (0.2)(12.7) = 2.54 \text{ V}$. So dc biasing is OK.]

4.22

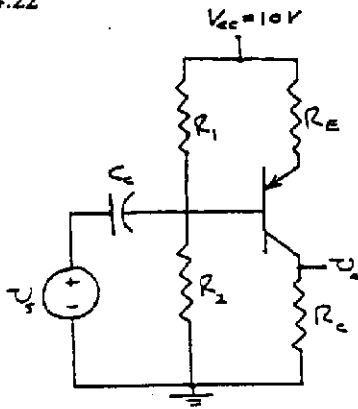

$$\beta = 80, A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E}$$

First approximation:

$$(A_v) \approx \frac{R_C}{R_E} = 10 \Rightarrow R_C = 10R_E$$

$$\text{Set } R_C = 12R_E$$

$$V_{EC} \approx V_{CC} - I_C(R_C + R_E) = 10 - I_C(13R_E)$$

$$\text{For } V_{EC} = \frac{1}{2}V_{CC} = 5$$

$$5 = 10 - I_C(13R_E)$$

$$\text{For } I_C = 0.7 \text{ mA}$$

$$I_E = 0.709, I_B = 0.00875 \text{ mA}$$

$$\Rightarrow R_E = 0.55 \text{ k}\Omega - R_C = 6.6 \text{ k}\Omega$$

Bias stable \Rightarrow

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(81)(0.55) = 4.46 \text{ k}\Omega$$

$$10 = (0.709)(0.35) + 0.7 + (0.00875)(4.46)$$

$$+ \frac{1}{R_1}(4.46)(10)$$

$$8.87 = \frac{1}{R_1}(4.46) \Rightarrow R_1 = 5.03 \text{ k}\Omega$$

$$\frac{5.03R_2}{5.03 + R_2} = 4.46 \Rightarrow R_2 = 39.4 \text{ k}\Omega$$


$$\frac{10}{R_1 + R_2} = \frac{10}{5.03 + 39.4} = 0.225 \text{ mA}$$

$$0.7 + 0.225 \approx 0.925 \text{ mA from } V_{CC} \text{ source.}$$

$$\text{Now } r_\pi = \frac{(80)(0.026)}{0.7} = 2.97 \text{ k}\Omega$$

$$|A_v| = \frac{(80)(6.6)}{2.97 + (81)(0.55)} = 11.1$$

4.23

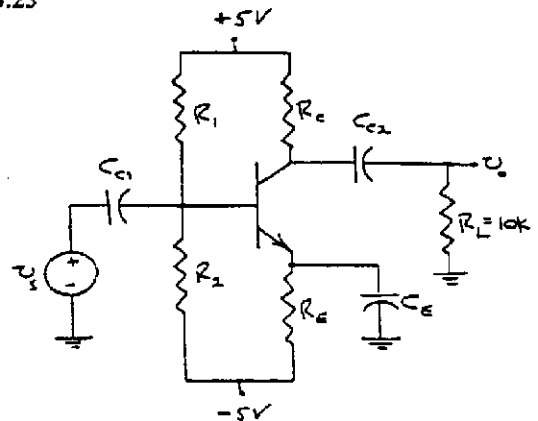

$$\beta = 120$$

$$\text{Let } I_{CQ} = 0.35 \text{ mA, } I_{EQ} = 0.353 \text{ mA}$$

$$I_{BQ} = 0.00292 \text{ mA}$$

$$\text{Let } R_E = 2 \text{ k}\Omega. \text{ For } V_{CEQ} = 4 \text{ V} \Rightarrow$$

$$10 = 4 + (0.35)R_C + (0.353)(2)$$

$$R_C = 15.1 \text{ k}\Omega, r_\pi = \frac{(120)(0.026)}{0.35} = 8.91 \text{ k}\Omega$$

$$A_v = \frac{-\beta(R_C \parallel R_L)}{r_\pi} = -\frac{(120)(15.1 \parallel 10)}{8.91}$$

$$A_v = -81.0$$

For bias stable circuit:

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(121)(2) = 24.2 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right)(10) - 5 = \frac{1}{R_1} \cdot R_{TH} \cdot (10) - 5$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 5$$

$$\frac{1}{R_1}(24.2)(10) - 5 = (0.00292)(24.2) + 0.7$$

$$+ (121)(0.00292)(2) - 5$$

$$\frac{1}{R_1}(242) = 1.477, R_1 = 164 \text{ k}\Omega$$

$$\frac{164R_2}{164 + R_2} = 24.2 \Rightarrow R_2 = 28.4 \text{ k}\Omega$$

$$\frac{10}{164 + 28.4} = 0.052, 0.35 + 0.052 = 0.402 \text{ mA}$$

4.24

From Prob. 4-10:

$$R_{TH} = R_1 \parallel R_2 = 10 \parallel 50 = 8.33 \text{ k}\Omega$$


$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right)(12) = \left(\frac{50}{50 + 10} \right)(12) = 10 \text{ V}$$

$$I_{BQ} = \frac{12 - 0.7 - 10}{8.33 + (101)(1)} = 0.0119 \text{ mA}$$

$$I_{CQ} = 1.19 \text{ mA, } I_{EQ} = 1.20 \text{ mA}$$

$$V_{ECQ} = 12 - (1.19)(2) - (120)(1) = 8.42 \text{ V}$$

4.22

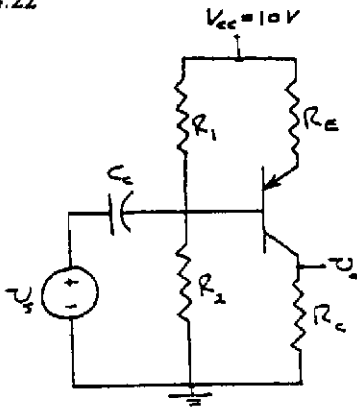

$$\beta = 80, A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E}$$

First approximation:

$$(A_v) \approx \frac{R_C}{R_E} = 10 \Rightarrow R_C = 10R_E$$

$$\text{Set } R_C = 12R_E$$

$$V_{EC} \approx V_{CC} - I_C(R_C + R_E) = 10 - I_C(13R_E)$$

$$\text{For } V_{EC} = \frac{1}{2}V_{CC} = 5$$

$$5 = 10 - I_C(13R_E)$$

$$\text{For } I_C = 0.7 \text{ mA}$$

$$I_E = 0.709, I_B = 0.00875 \text{ mA}$$

$$\Rightarrow R_E = 0.55 \text{ k}\Omega \rightarrow R_C = 6.6 \text{ k}\Omega$$

Bias stable \Rightarrow

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(81)(0.55) = 4.46 \text{ k}\Omega$$

$$10 = (0.709)(0.55) + 0.7 + (0.00875)(4.46)$$

$$+ \frac{1}{R_1}(4.46)(10)$$

$$8.87 = \frac{1}{R_1}(4.46) \Rightarrow R_1 = 5.03 \text{ k}\Omega$$

$$\frac{5.03R_2}{5.03 + R_2} = 4.46 \Rightarrow R_2 = 39.4 \text{ k}\Omega$$


$$\frac{10}{R_1 + R_2} = \frac{10}{5.03 + 39.4} = 0.225 \text{ mA}$$

$$0.7 + 0.225 \approx 0.925 \text{ mA from } V_{CC} \text{ source.}$$

$$\text{Now } r_\pi = \frac{(80)(0.026)}{0.7} = 2.97 \text{ k}\Omega$$

$$|A_v| = \frac{(80)(6.6)}{2.97 + (81)(0.55)} = 11.1$$

4.23

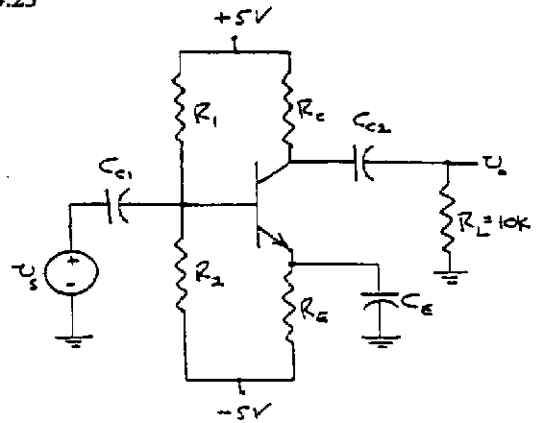

$$\beta = 120$$

$$\text{Let } I_{CQ} = 0.35 \text{ mA}, I_{EQ} = 0.353 \text{ mA}$$

$$I_{BQ} = 0.00292 \text{ mA}$$

$$\text{Let } R_E = 2 \text{ k}\Omega. \text{ For } V_{CEQ} = 4 \text{ V} \Rightarrow$$

$$10 = 4 + (0.35)R_C + (0.353)(2)$$

$$R_C = 15.1 \text{ k}\Omega, r_\pi = \frac{(120)(0.026)}{0.35} = 8.91 \text{ k}\Omega$$

$$A_v = \frac{-\beta(R_C \parallel R_L)}{r_\pi} = -\frac{(120)(15.1 \parallel 10)}{8.91}$$

$$A_v = -81.0$$

For bias stable circuit:

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(121)(2) = 24.2 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right)(10) - 5 = \frac{1}{R_1} \cdot R_{TH} \cdot (10) - 5$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 5$$

$$\frac{1}{R_1}(24.2)(10) - 5 = (0.00292)(24.2) + 0.7$$

$$+ (121)(0.00292)(2) - 5$$

$$\frac{1}{R_1}(242) = 1.477, R_1 = 164 \text{ k}\Omega$$

$$\frac{164R_2}{164 + R_2} = 24.2 \Rightarrow R_2 = 28.4 \text{ k}\Omega$$

$$\frac{10}{164 + 28.4} = 0.052, 0.35 + 0.052 = 0.402 \text{ mA}$$

4.24

From Prob. 4-10:


$$R_{TH} = R_1 \parallel R_2 = 10 \parallel 50 = 8.33 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right)(12) = \left(\frac{50}{50 + 10} \right)(12) = 10 \text{ V}$$

$$I_{BQ} = \frac{12 - 0.7 - 10}{8.33 + (101)(1)} = 0.0119 \text{ mA}$$

$$I_{CQ} = 1.19 \text{ mA}, I_{EQ} = 1.20 \text{ mA}$$
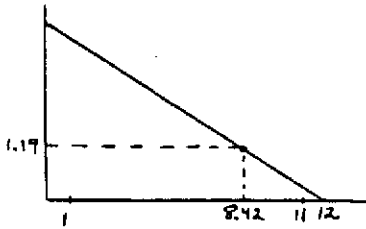
$$V_{ECQ} = 12 - (1.19)(2) - (120)(1) = 8.42 \text{ V}$$



For $1 \leq v_{EC} \leq 11$

$$\Delta v_{EC} = 11 - 8.42 = 2.58$$

\Rightarrow Output voltage swing = 5.16 V
(peak-to-peak)


4.25

$$I_{BQ} = \frac{5 - 0.7}{50 + (101)(0.1 + 12.9)} = 0.00315 \text{ mA}$$

$$I_{CQ} = 0.315 \text{ mA}, I_{EQ} = 0.319 \text{ mA}$$

$$V_{CEQ} = (5 + 5) - (0.315)(6) - (0.319)(13)$$

$$V_{CEQ} = 3.96 \text{ V}$$

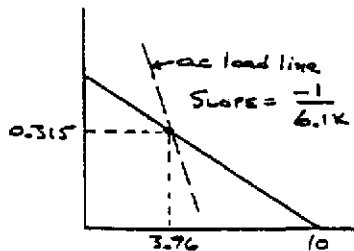

$$\Delta i_C = -\frac{1}{6.1} \Delta v_{ec}$$

$$\text{For } \Delta i_C = 0.315 - 0.05 = 0.265$$

$$\Rightarrow |\Delta v_{EC}| = 1.62$$

$$v_{EC}(\min) = 3.96 - 1.62 = 2.34$$

Output signal swing determined by current:

Max. output swing = 3.24 V peak-to-peak

4.26

$$\text{For } R_C = 6 \text{ k}\Omega, V_C = 5 - \left(\frac{100}{101}\right)(0.35)(6) = 2.92 \text{ V}$$

$$V_E = -I_{BQ}R_B - V_{BE(on)} = -\frac{0.35}{100}(10) - 0.7 = -0.735 \text{ V}$$

$$\text{Then } V_{CE} = V_C - V_E = 2.92 - (-0.735) = 3.66 \text{ V}$$

$$\Delta v_{CE} = \Delta i_C \cdot R_C \Rightarrow (4.5 - 3.66) = \Delta i_C(6)$$

so that $\Delta i_C = 0.14 \text{ mA}$

$$(a) \text{ Total } \Delta v_{CE} = 2(4.5 - 3.66) = 1.68 \text{ V peak-to-peak}$$

$$(b) \text{ Total } \Delta i_C = 2(0.14) = 0.28 \text{ mA peak-to-peak}$$

4.27

$$I_{BQ} = 0.80 \text{ mA}, I_{CQ} = 0.792 \text{ mA}$$


$$I_{BQ} = 0.008 \text{ mA}$$

$$V_E = 0.7 + (0.008)(10) = 0.78 \text{ V}$$

$$V_C = I_{CQ}R_C - 5 = (0.792)(4) - 5 = -1.83 \text{ V}$$

$$V_{ECQ} = 0.78 - (-1.83) = 2.61 \text{ V}$$

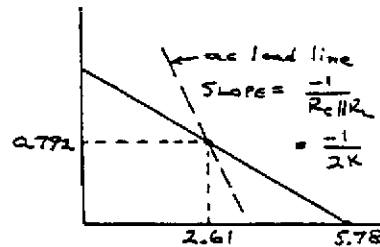Load line: Assume V_E remains constant at $\approx 0.78 \text{ V}$



$$\Delta i_C = \frac{-1}{2 \text{ k}\Omega} \cdot v_{ec}$$

$$\text{Collector current swing} = 0.792 - 0.08$$

$$= 0.712 \text{ mA}$$

$$|\Delta v_{ec}| = (0.712)(2) = 1.42 \text{ V}$$

Output swing determined by current.

Max. output swing = 2.84 V peak-to-peak

$$\text{Swing in } i_C \text{ current} = \frac{2.84}{4}$$

$$= \underline{0.71 \text{ mA peak-to-peak}}$$


4.28

$$I_{BQ} = \frac{6 - 0.7}{10 + (101)(3)} = 0.0169 \text{ mA}$$

$$I_{CQ} = 1.69 \text{ mA}, I_{EQ} = 1.71 \text{ mA}$$

$$V_{CEQ} = (16 + 6) - (1.69)(6.8) - (1.71)(3)$$

$$V_{CEQ} = 5.38 \text{ V}$$

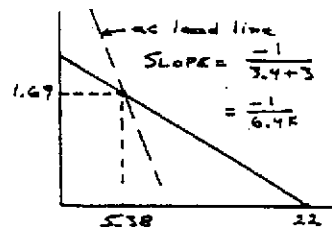

$$\Delta i_C = -\frac{1}{6.4} \Delta v_{ce}$$

$$\text{For } v_{ce}(\min) = 1 \text{ V, } \Delta v_{ce} = 5.38 - 1 = 4.38 \text{ V}$$

$$\Rightarrow |\Delta i_C| = \frac{4.38}{6.4} = 0.684 \text{ mA}$$

Output swing limited by voltage:


$$\Delta v_{ce} = \text{Max. swing in output voltage}$$

$$= 8.76 \text{ V peak-to-peak}$$

$$\Delta i_0 = \frac{1}{2} \Delta i_C \Rightarrow \Delta i_0 = 0.342 \text{ mA}$$

(peak-to-peak)

4.29

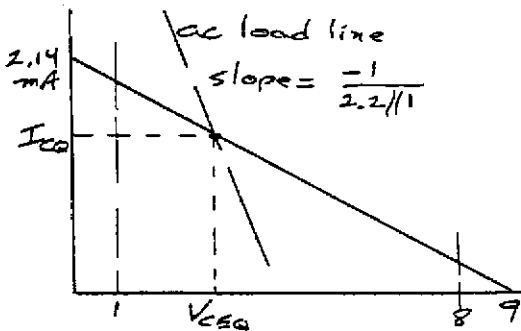

$$\Delta v_{ce}(\max) = V_{CEQ} - 1, \Delta i_C(\max) = I_{CQ}$$

$$\Delta v_{ce} = \Delta i_C(0.6875). \text{ So}$$

$$V_{CEQ} - 1 = I_{CQ}(0.6875) \text{ and}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) \Rightarrow V_{CEQ} = 9 - I_{CQ}(4.2)$$

Then

$$9 - I_{CQ}(4.2) - 1 = I_{CQ}(0.6875)$$

$$\text{So } I_{CQ} = 1.64 \text{ mA and } V_{CEQ} = 2.11 \text{ V}$$

$$V_{TH} = \frac{1}{R_1} R_{TH} V_{CC} \text{ and } R_{TH} = (0.1)(1 + \beta)R_E$$

$$R_{TH} = (0.1)(151)(2) = 30.2 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(\text{on}) + (1 + \beta)I_{BQ}R_E$$


$$I_{BQ} = \frac{1.64}{150} = 0.0109 \text{ mA}$$

$$\frac{1}{R_1}(30.2)(9) = (0.0109)(30.2) + 0.7 + (151)(0.0109)(2)$$

$$\text{which yields } R_1 = 62.9 \text{ k}\Omega \text{ and } R_2 = 58.1 \text{ k}\Omega$$

4.30

dc load line

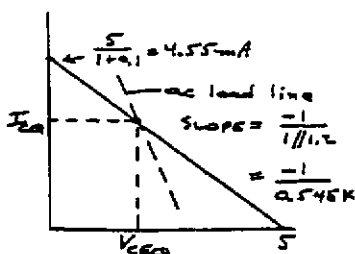

For maximum symmetrical swing

$$\Delta i_C = I_{CQ} - 0.25$$

$$\Delta v_{CE} = V_{CEQ} - 0.5$$

$$\text{and } |\Delta i_C| = \frac{1}{0.545 \text{ k}\Omega} |\Delta v_{CE}|$$

$$I_{CQ} - 0.25 = \frac{V_{CEQ} - 0.5}{0.545}$$

$$V_{CEQ} = 5 - I_{CQ}(1.1)$$

$$0.545(I_{CQ} - 0.25) = [5 - I_{CQ}(1.1)] - 0.5$$

$$(0.545 + 1.1)I_{CQ} = 5 - 0.5 + 0.136$$

$$I_{CQ} = 2.82 \text{ mA, } I_{BQ} = 0.0157 \text{ mA}$$

$$R_{TH} = R_1 \parallel R_2 = (0.1)(1 + \beta)R_E$$

$$= (0.1)(181)(0.1) = 1.81 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} R_{TH} V^+ = I_{BQ}R_{TH} + V_{BE}(\text{on})$$

$$+ (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1}(1.81)(5) = (0.0157)(1.81) + 0.7$$

$$+ (181)(0.0157)(0.1)$$

$$\frac{1}{R_1}(9.05) = 1.01 \Rightarrow R_1 = 8.96 \text{ k}\Omega$$

$$\frac{8.96 R_2}{8.96 + R_2} = 1.81 \Rightarrow R_2 = 2.27 \text{ k}\Omega$$

4.31

$$I_{CQ} = 0.647 \text{ mA, } V_{CEQ} = 10 - (0.647)(9) = 4.18 \text{ V}$$

$$\Delta i_C = I_{CQ} = 0.647 \text{ mA}$$

$$\text{So } \Delta v_{ce} = \Delta i_C(4 \parallel 4) = (0.647)(2) = 1.294 \text{ V}$$

Voltage swing is well within the voltage specification. Then

$$\Delta v_{ce} = 2(1.294) = 2.59 \text{ V peak-to-peak}$$

4.32

$$\text{a. } R_{TH} = R_1 \parallel R_2 = 10 \parallel 10 = 5 \text{ k}\Omega$$


$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (18) - 9 = \left(\frac{10}{10 + 10} \right) (18) - 9 = 0$$

$$I_{BQ} = \frac{0 - 0.7 - (-9)}{5 + (181)(0.5)} = 0.0869 \text{ mA}$$

$$I_{CQ} = 15.6 \text{ mA, } I_{EQ} = 15.7 \text{ mA}$$

$$V_{CEQ} = 18 - (15.7)(0.5) \Rightarrow V_{CEQ} = 10.1 \text{ V}$$

b.

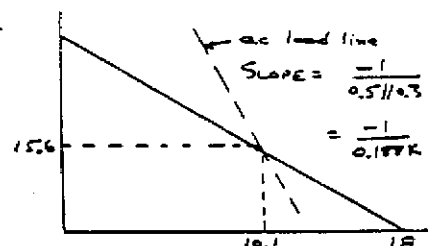

$$c. \quad r_{\pi} = \frac{(180)(0.026)}{15.6} = 0.30 \text{ k}\Omega$$

$$A_v = \frac{(1+\beta)(R_E \parallel R_L)}{r_{\pi} + (1+\beta)(R_E \parallel R_L)} \cdot \left(\frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L) = 0.30 + (181)(0.5 \parallel 0.3)$$

$$\text{or } R_{ib} = 34.2 \text{ k}\Omega$$

$$R_1 \parallel R_2 \parallel R_{ib} = 5 \parallel 34.2 = 4.36 \text{ k}\Omega$$

$$A_v = \frac{(181)(0.5 \parallel 0.3)}{0.3 + (181)(0.5 \parallel 0.3)} \cdot \left(\frac{4.36}{4.36 + 1} \right) \Rightarrow A_v = 0.806$$

$$d. \quad R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$$

$$R_{ib} = 0.30 + (181)(0.188) \Rightarrow R_{ib} = 34.3 \text{ k}\Omega$$

$$R_o = R_E \parallel \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{1+\beta} = 0.5 \parallel \frac{0.3 + 5 \parallel 1}{181} \Rightarrow$$

$$R_o = 6.18 \Omega$$

4.33

$$a. \quad R_{TH} = R_1 \parallel R_2 = 10 \parallel 10 = 5 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (-10) = -5 \text{ V}$$


$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1+\beta) I_{BQ} R_E - 10$$

$$I_{BQ} = \frac{-5 - 0.7 - (-10)}{5 + (121)(2)} = 0.0174 \text{ mA}$$

$$I_{CQ} = 2.09 \text{ mA}, \quad I_{SQ} = 2.11 \text{ mA}$$

$$V_{CEQ} = 10 - (2.09)(1) - (2.11)(2)$$

$$\Rightarrow V_{CEQ} = 3.69 \text{ V}$$

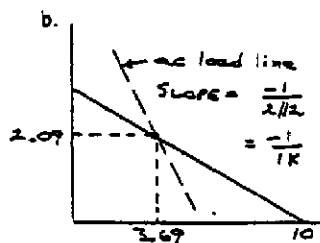

$$c. \quad r_{\pi} = \frac{(120)(0.026)}{2.09} = 1.49 \text{ k}\Omega$$

$$A_v = \frac{(1+\beta)(R_E \parallel R_L)}{r_{\pi} + (1+\beta)(R_E \parallel R_L)} \cdot \left(\frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L) = 1.49 + (121)(2 \parallel 2)$$

$$R_{ib} = 122.5 \text{ k}\Omega, \quad R_1 \parallel R_2 \parallel R_{ib} = 5 \parallel 122.5 = 4.80 \text{ k}\Omega$$

$$A_v = \frac{(121)(2 \parallel 2)}{1.49 + (121)(2 \parallel 2)} \cdot \left(\frac{4.80}{4.80 + 5} \right) \Rightarrow$$

$$A_v = 0.484$$


$$d. \quad R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$$

$$R_{ib} = 1.49 + (121)(2 \parallel 2) \Rightarrow R_{ib} = 122 \text{ k}\Omega$$

$$R_o = R_E \parallel \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{1+\beta} = 2 \parallel \frac{1.49 + 5 \parallel 5}{121} \Rightarrow$$

$$R_o = 32.5 \Omega$$

4.34

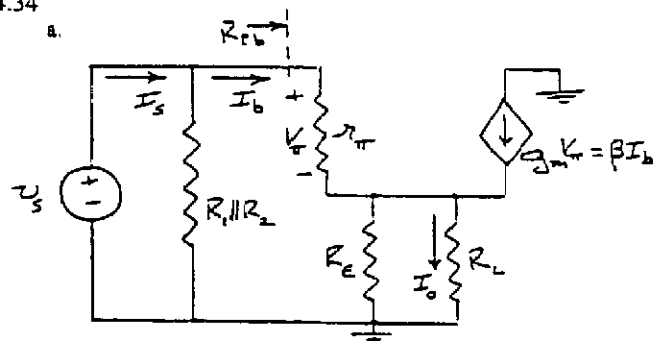

$$I_o = (1+\beta) I_b \left(\frac{R_E}{R_E + R_L} \right)$$

$$I_b = I_s \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$$

$$V_{CC} = 10 \text{ V}, \quad \text{For } V_{CEQ} = 5 \text{ V}$$

$$5 = 10 - \left(\frac{1+\beta}{\beta} \right) I_{CQ} R_E$$

$$\beta = 80, \quad \text{For } R_E = 0.5 \text{ k}\Omega$$

$$I_{CQ} = 9.88 \text{ mA}, \quad I_{EQ} = 10 \text{ mA}, \quad I_{BQ} = 0.123 \text{ mA}$$

$$r_{\pi} = \frac{(80)(0.026)}{9.88} = 0.211 \text{ k}\Omega$$

$$R_{ib} = 0.211 + (81)(0.5 \parallel 0.5) \Rightarrow R_{ib} = 20.46 \text{ k}\Omega$$

$$A_i = \frac{I_o}{I_s} = (1+\beta) \left(\frac{R_E}{R_E + R_L} \right) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right)$$

$$8 = (81) \left(\frac{1}{2} \right) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 20.46} \right)$$

$$0.1975(R_1 \parallel R_2 + 20.46) = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 5.04 \text{ k}\Omega$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1+\beta) I_{BQ} R_E$$

$$\frac{1}{R_1} (5.04)(10) = (0.123)(5.04) + 0.7 + (10)(0.5)$$

$$\Rightarrow R_1 = 7.97 \text{ k}\Omega$$

$$\frac{7.97 R_2}{7.97 + R_2} = 5.04 \Rightarrow R_2 = 13.7 \text{ k}\Omega$$

$$(b) R_b = 0.211 + (81)(0.5 \parallel 2) = 32.6 \text{ k}\Omega$$

$$A_v = (81) \left(\frac{0.5}{0.5 + 2} \right) \left(\frac{5.04}{5.04 + 32.6} \right) = (81)(0.2)(0.134)$$

$$A_v = 2.17$$

4.35

$$R_i = R_{TH} \parallel R_b \text{ where } R_b = r_\pi + (1 + \beta)R_E$$

$$V_{CEQ} = 3.5, \quad I_{CQ} = \frac{5 - 3.5}{2} = 0.75 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{0.75} = 4.16 \text{ k}\Omega$$

$$R_b = 4.16 + (121)(2) = 246 \text{ k}\Omega$$

$$\text{Then } R_i = 120 = R_{TH} \parallel 245 \Rightarrow R_{TH} = 235 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.75}{120} = 0.00625 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_i} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_i} (235)(5) = (0.00625)(235) + 0.7 + (121)(0.00625)(2)$$

$$\text{which yields } R_1 = 319 \text{ k}\Omega \text{ and } R_2 = 892 \text{ k}\Omega$$


4.36

$$a. \text{ Let } R_E = 24 \text{ }\Omega \text{ and } V_{CEQ} = \frac{1}{2}V_{CC} = 12 \text{ V}$$

$$\Rightarrow I_{BQ} = \frac{12}{24} = 0.5 \text{ A}$$

$$I_{CQ} = 0.493 \text{ A}, \quad I_{BQ} = 6.58 \text{ mA}$$
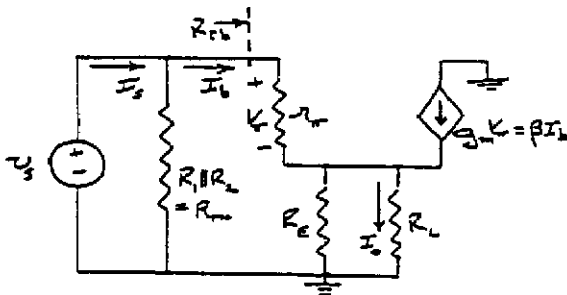
$$r_\pi = \frac{(75)(0.026)}{0.493} = 3.96 \text{ }\Omega$$



$$I_o = (1 + \beta)I_b \left(\frac{R_E}{R_E + R_L} \right)$$

$$I_b = I_s \left(\frac{R_{TH}}{R_{TH} + R_{ib}} \right)$$

$$R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L)$$

$$= 3.96 + (76)(24 \parallel 8) \Rightarrow R_{ib} = 460 \text{ }\Omega$$

$$A_v = \frac{I_o}{I_s} = (1 + \beta) \left(\frac{R_E}{R_E + R_L} \right) \left(\frac{R_{TH}}{R_{TH} + R_{ib}} \right)$$

$$8 = (76) \left(\frac{24}{24 + 8} \right) \left(\frac{R_{TH}}{R_{TH} + 460} \right)$$

$$0.140 = \frac{R_{TH}}{R_{TH} + 460}$$

$$\Rightarrow R_{TH} = 74.9 \text{ }\Omega \text{ (Minimum value)}$$

dc analysis:


$$V_{TH} = \frac{1}{R_i} \cdot R_{TH} \cdot V_{CC}$$

$$= I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

$$\frac{1}{R_i} (74.9)(24) = (0.00658)(74.9) + 0.70 + (0.5)(24)$$

$$= 12.75$$
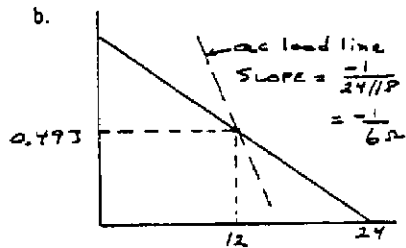
$$R_1 = 136 \text{ }\Omega, \quad \frac{136 R_2}{136 + R_2} = 74.9 \Rightarrow R_2 = 167 \text{ }\Omega$$



$$\Delta i_C = -\frac{1}{6} \Delta v_{ce}$$

$$\text{For } \Delta i_C = 0.493$$

$$\Rightarrow |\Delta v_{ce}| = (0.493)(6)$$

$$\Rightarrow \text{Max. swing in output voltage for this design}$$

$$= 5.92 \text{ V peak-to-peak}$$

$$c. \quad R_o = \frac{r_\pi}{1 + \beta} \parallel R_E = \frac{3.96}{76} \parallel 24 = 0.0521 \parallel 24$$

$$\Rightarrow R_o = 52 \text{ m}\Omega$$

4.37

$$a. \quad R_{TH} = R_1 \parallel R_2 = 60 \parallel 40 = 24 \text{ k}\Omega$$


$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{40}{40 + 60} \right) (5) = 2 \text{ V}$$

$$I_{BQ} = \frac{5 - 0.7 - 2}{24 + (51)(3)} = 0.0130 \text{ mA}$$

$$I_{CQ} = 0.650 \text{ mA}, \quad I_{BQ} = 0.663 \text{ mA}$$

$$V_{CEQ} = 5 - I_{CQ}R_E = 5 - (0.663)(3)$$

$$\Rightarrow V_{CEQ} = 3.01 \text{ V}$$

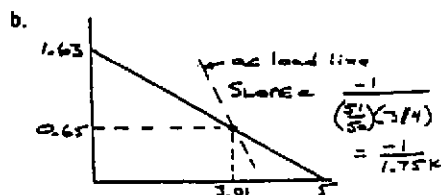

c. $r_{\pi} = \frac{(50)(0.026)}{0.650} = 2 \text{ k}\Omega$, $r_o = \frac{80}{0.65} = 123 \text{ k}\Omega$

Define $R'_L = R_E \parallel R_L \parallel r_o = 3 \parallel 4 \parallel 123 = 1.69 \text{ k}\Omega$

$A_v = \frac{(1 + \beta)R'_L}{r_{\pi} + (1 + \beta)R'_L} = \frac{(51)(1.69)}{2 + (51)(1.69)}$

$\Rightarrow A_v = 0.977$

$A_i = (1 + \beta)I_b \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right)$

$I_b = I_S \left(\frac{R_{TH}}{R_{TH} + R_{i,b}} \right)$

$R_{i,b} = r_{\pi} + (1 + \beta)R'_L = 2 + (51)(1.69) = 88.2$

$R_E \parallel r_o = 3 \parallel 123 = 2.93$

$A_i = (51) \left(\frac{2.93}{2.93 + 4} \right) \left(\frac{24}{24 + 88.2} \right)$

$\Rightarrow A_i = 4.61$

d. $R_{i,b} = r_{\pi} + (1 + \beta)R_E \parallel R_L \parallel r_o = 2 + (51)(1.69)$

$\Rightarrow R_{i,b} = 88.2 \text{ k}\Omega$

$R_o = \frac{r_{\pi}}{1 + \beta} \parallel R_E = \left(\frac{2}{51} \right) \parallel 3 = 0.0392 \parallel 3$

$R_o = 38.7 \Omega$

e. Assume variations in r_{π} and r_o have negligible effects

$R_1 = 60 \pm 5\% \rightarrow R_1 = 63 \text{ k}\Omega, R_1 = 57 \text{ k}\Omega$

$R_2 = 40 \pm 5\% \rightarrow R_2 = 42 \text{ k}\Omega, R_2 = 38 \text{ k}\Omega$

$R_E = 3 \pm 5\% \rightarrow R_E = 3.15 \text{ k}\Omega, R_E = 2.85 \text{ k}\Omega$

$R_L = 4 \pm 5\% \rightarrow R_L = 4.2 \text{ k}\Omega, R_L = 3.8 \text{ k}\Omega$

$A_i = (1 + \beta) \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) \left(\frac{R_{TH}}{R_{TH} + R_{i,b}} \right)$

$R_{i,b} = r_{\pi} + (1 + \beta)(R_E \parallel R_L \parallel r_o)$

$R_{TH}(\text{max}) = 25.2 \text{ k}\Omega, R_{TH}(\text{min}) = 22.8 \text{ k}\Omega$

$R_{i,b}(\text{max}) = 92.5 \text{ k}\Omega, R_{i,b}(\text{min}) = 84.0 \text{ k}\Omega$

$R_E(\text{max}), R_L(\text{min}), R_{i,b} = 88.6 \text{ k}\Omega$

$R_E(\text{min}), R_L(\text{max}), R_{i,b} = 87.4 \text{ k}\Omega$

$R_E(\text{max}) \parallel r_o = 3.07 \text{ k}\Omega$

$R_E(\text{min}) \parallel r_o = 2.79 \text{ k}\Omega$

For $R_E(\text{min}), R_L(\text{max}), R_{TH}(\text{min})$

$A_i = (51) \left(\frac{2.79}{2.79 + 4.2} \right) \left(\frac{22.8}{22.8 + 87.4} \right)$

$\Rightarrow A_i = 4.21$

For $R_E(\text{max}), R_L(\text{min}), R_{TH}(\text{max})$


$A_i = (51) \left(\frac{3.07}{3.07 + 3.8} \right) \left(\frac{25.2}{25.2 + 88.6} \right)$

$\Rightarrow A_i = 5.05$

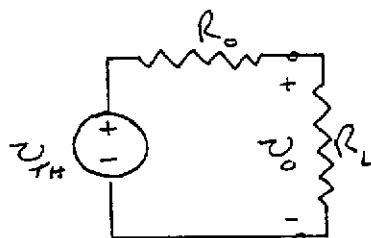4.38

The output of the emitter follower is

$v_o = \left(\frac{R_L}{R_L + R_o} \right) \cdot v_{TH}$



For v_o to be within 5% for a range of R_L , we have

$\frac{R_L(\text{min})}{R_L(\text{min}) + R_o} = (0.95) \frac{R_L(\text{max})}{R_L(\text{max}) + R_o}$

$\frac{4}{4 + R_o} = (0.95) \frac{10}{10 + R_o}$ which yields

$R_o = 0.364 \text{ k}\Omega$

We have $R_o = \left(\frac{r_{\pi} + R_1 \parallel R_2 \parallel R_E}{1 + \beta} \right) \parallel R_E \parallel r_o$

The first term dominates

Let $R_1 \parallel R_2 \parallel R_E \equiv R_S$, then

$R_o \equiv \frac{r_{\pi} + R_S}{1 + \beta} \Rightarrow 0.364 = \frac{r_{\pi} + 4}{1 + \beta}$

or

$0.364 = \frac{r_{\pi}}{1 + \beta} + \frac{4}{1 + \beta} = \frac{\beta V_T}{I_{CQ}(1 + \beta)} + \frac{4}{1 + \beta}$

$0.364 \equiv \frac{V_T}{I_{CQ}} + \frac{4}{1 + \beta}$

The factor $\frac{4}{1 + \beta}$ is in the range of $\frac{4}{91} = 0.044$ to

$\frac{4}{131} = 0.0305$. We can set $R_o \equiv 0.32 = \frac{V_T}{I_{CQ}}$

Or $I_{CQ} = 0.08125 \text{ mA}$. To take into account other

factors, set $I_{CQ} = 0.15 \text{ mA}$,

$I_{BQ} = \frac{0.15}{110} = 0.00136 \text{ mA}$

For $V_{CEQ} \equiv 5 \text{ V}$, set $R_E = \frac{5}{0.15} = 33.3 \text{ k}\Omega$

Design a bias stable circuit.

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5 = \frac{1}{R_1} (R_{TH})(10) - 5$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(111)(33.3) = 370 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 5$$

$$\text{So } \frac{1}{R_1}(370)(10) - 5 = (0.00136)(370) + 0.7$$

$$+ (111)(0.00136)(33.3) - 5$$

which yields $R_1 = 594 \text{ k}\Omega$ and $R_2 = 981 \text{ k}\Omega$

Now

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L)}{r_\pi + (1 + \beta)(R_E \parallel R_L)} \cdot \left(\frac{R_{TH} \parallel R_b}{R_{TH} \parallel R_b + R_s} \right)$$

$$R_b = r_\pi + (1 + \beta)(R_E \parallel R_L) \text{ and } r_\pi = \frac{\beta V_T}{I_{CQ}}$$

For $\beta = 90$, $R_L = 4 \text{ k}\Omega$,

$$r_\pi = 15.6 \text{ k}\Omega, R_b = 340.6 \text{ k}\Omega$$

$$A_v = \frac{(91)(33.3 \parallel 4)}{15.6 + (91)(33.3 \parallel 4)} \cdot \frac{370 \parallel 340.6}{370 \parallel 340.6 + 4} \Rightarrow$$

$$A_v = 0.9332$$

For $\beta = 90$, $R_L = 10 \text{ k}\Omega$

$$R_b = 715.4 \text{ k}\Omega$$

$$A_v = \frac{(91)(33.3 \parallel 10)}{15.6 + (91)(33.3 \parallel 10)} \cdot \frac{370 \parallel 715.4}{370 \parallel 715.4 + 4} \Rightarrow$$

$$A_v = 0.9625$$

For $\beta = 130$, $R_L = 4 \text{ k}\Omega$

$$r_\pi = 22.5 \text{ k}\Omega, R_b = 490 \text{ k}\Omega$$

$$A_v = \frac{(131)(33.3 \parallel 4)}{22.5 + (131)(33.3 \parallel 4)} \cdot \frac{370 \parallel 490}{370 \parallel 490 + 4} \Rightarrow$$

$$A_v = 0.9360$$

For $\beta = 130$, $R_L = 10 \text{ k}\Omega$

$$R_b = 1030 \text{ k}\Omega$$

$$A_v = \frac{(131)(33.3 \parallel 10)}{22.5 + (131)(33.3 \parallel 10)} \cdot \frac{370 \parallel 1030}{370 \parallel 1030 + 4} \Rightarrow$$

$$A_v = 0.9645$$

Now $v_o(\min) = |A_v(\min)| \cdot v_s = 3.73 \sin \alpha$

$$v_o(\max) = |A_v(\max)| \cdot v_s = 3.86 \sin \alpha$$

$$\frac{\Delta v_o}{v_o} = 3.5\%$$

4.39

a. $R_{TH} = R_1 \parallel R_2 = 40 \parallel 60 = 24 \text{ k}\Omega$

$$V_{TH} = \left(\frac{60}{60 + 40} \right) (10) = 6 \text{ V}$$

$$\beta = 75$$

$$I_{BQ} = \frac{6 - 0.7}{24 + (75)(5)} = 0.0131 \text{ mA}$$

$$I_{CQ} = 0.984 \text{ mA}$$

$$\beta = 150$$

$$I_{BQ} = \frac{6 - 0.7}{24 + (151)(5)} = 0.00680 \text{ mA}$$

$$I_{CQ} = 1.02 \text{ mA}$$

$$\beta = 75$$

$$r_\pi = \frac{(75)(0.026)}{0.984} = 1.98 \text{ k}\Omega$$

$$\beta = 150$$

$$r_\pi = 3.82 \text{ k}\Omega$$

$$\beta = 75$$

$$R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L) = 65.3 \text{ k}\Omega$$

$$\beta = 150$$

$$R_{ib} = 130 \text{ k}\Omega$$

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L)}{r_\pi + (1 + \beta)(R_E \parallel R_L)} \cdot \frac{R_1 \parallel R_2 \parallel R_b}{R_1 \parallel R_2 \parallel R_b + R_s}$$

For $\beta = 75$, $R_1 \parallel R_2 \parallel R_b = 40 \parallel 60 \parallel 65.3 = 17.5 \text{ k}\Omega$

$$A_v = \frac{(76)(0.833)}{1.98 + (76)(0.833)} \cdot \frac{17.5}{17.5 + 4} \Rightarrow$$

$$A_v = 0.789$$

For $\beta = 150$, $R_1 \parallel R_2 \parallel R_b = 40 \parallel 60 \parallel 130 = 20.3 \text{ k}\Omega$

$$A_v = \frac{(151)(0.833)}{3.82 + (151)(0.833)} \cdot \frac{20.3}{20.3 + 4} \Rightarrow$$

$$A_v = 0.811$$

$$A_i = (1 + \beta) \left(\frac{R_E}{R_E + R_L} \right) \left(\frac{R_{TH}}{R_{TH} + R_{ib}} \right)$$

$$\beta = 75$$

$$A_i = (76) \left(\frac{5}{5 + 1} \right) \left(\frac{24}{24 + 65.3} \right) \Rightarrow A_i = 17.0$$

$$\beta = 150$$

$$A_i = (151) \left(\frac{5}{6} \right) \left(\frac{24}{24 + 130} \right) \Rightarrow A_i = 19.6$$

$$17.0 < A_i < 19.6$$

b. Current gain is the same as part (a)

(b) For $R_s = 5 \text{ k}\Omega$

$$\beta = 75 \Rightarrow A_v = 0.754$$

$$\beta = 150 \Rightarrow A_v = 0.779$$

4.40

(a) $I_{BQ} = \frac{0.5}{81} = 0.00617 \text{ mA}$

$$V_B = I_{BQ}R_B = (0.00617)(10) \Rightarrow V_B = 0.0617 \text{ V}$$

$$V_E = V_B + 0.7 \Rightarrow V_E = 0.7617 \text{ V}$$


$$(b) I_{CQ} = (0.5) \left(\frac{80}{81} \right) = 0.494 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.494}{0.026} \Rightarrow g_m = 19 \text{ mA/V}$$

$$r_x = \frac{\beta V_T}{I_{CQ}} = \frac{(80)(0.026)}{0.494} \Rightarrow r_x = 4.21 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{0.494} \Rightarrow r_o = 304 \text{ k}\Omega$$

(c)

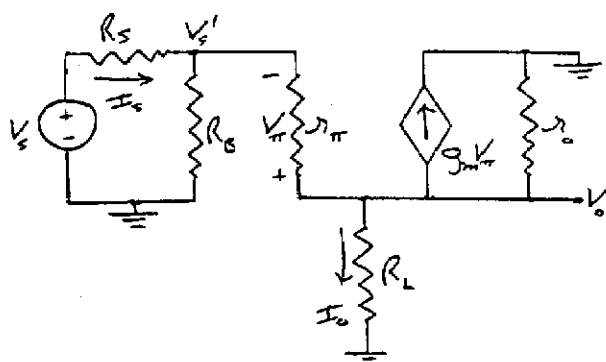For $R_s = 0$

$$V_o = - \left(\frac{V_s}{r_x} + g_m V_s \right) (R_L \parallel r_o)$$

so that

$$V_x = \frac{-V_o}{\left(\frac{1+\beta}{r_x} \right) (R_L \parallel r_o)}$$

Now

$$V_s + V_x = V_o$$

or

$$V_s = V_o - V_x = V_o + \frac{V_o}{\left(\frac{1+\beta}{r_x} \right) (R_L \parallel r_o)}$$

We find

$$A_v = \frac{V_o}{V_s} = \frac{(1+\beta)(R_L \parallel r_o)}{r_x + (1+\beta)(R_L \parallel r_o)} = \frac{(81)(0.5 \parallel 304)}{4.21 + (81)(0.5 \parallel 304)} \\ \approx \frac{(81)(0.5)}{4.21 + (81)(0.5)} \Rightarrow A_v = 0.906$$

$$R_{ib} = r_x + (1+\beta)(R_L \parallel r_o) \approx 4.21 + (81)(0.5) = 44.7 \text{ k}\Omega$$

$$I_b = \left(\frac{R_s}{R_s + R_{ib}} \right) \cdot I_s \text{ and } I_o = \left(\frac{r_o}{r_o + R_L} \right) (1+\beta) I_b$$

Then

$$A_i = \frac{I_o}{I_s} = (1+\beta) \left(\frac{R_s}{R_s + R_{ib}} \right) \left(\frac{r_o}{r_o + R_L} \right)$$

$$A_i \approx (81) \left(\frac{10}{10 + 44.7} \right) (1) \Rightarrow A_i = 14.8$$

(d)

$$V_s' = \left(\frac{R_2 \parallel R_b}{R_s \parallel R_b + R_s} \right) \cdot V_s = \left(\frac{10 \parallel 44.7}{10 \parallel 44.7 + 2} \right) \cdot V_s = (0.803) V_s$$

Then

$$A_v = (0.803)(0.906) \Rightarrow A_v = 0.728$$

$$A_i = 14.8 \text{ (Unchanged)}$$

4.41

$$V_o = (1+\beta) I_b R_L$$

$$I_b = \frac{V_s}{r_x + (1+\beta) R_L}$$

$$\text{so } A_v = \frac{(1+\beta) R_L}{r_x + (1+\beta) R_L}$$

$$\text{For } \beta = 100, R_L = 0.5 \text{ k}\Omega$$

$$r_x = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$\text{Then } A_v(\text{min}) = \frac{(101)(0.5)}{5.2 + (101)(0.5)} = 0.9066$$

$$\text{For } \beta = 180, R_L = 500 \text{ k}\Omega$$

$$r_x = \frac{(180)(0.026)}{0.5} = 9.36 \text{ k}\Omega$$

$$\text{Then } A_v(\text{max}) = \frac{(181)(500)}{9.36 + (181)(500)} = 0.9999$$

4.42

$$a. I_{BQ} = 1 \text{ mA}, V_{CEQ} = V_{CC} - I_{BQ} R_E$$

$$5 = 10 - (1)(R_E) \Rightarrow R_E = 5 \text{ k}\Omega$$


$$I_{BQ} = \frac{1}{101} = 0.0099$$

$$10 = I_{BQ} R_B + V_{BE}(\text{on}) + I_{BQ} R_E$$

$$10 = (0.0099) R_B + 0.7 + (1)(5)$$

$$\Rightarrow R_B = 434 \text{ k}\Omega$$

b.

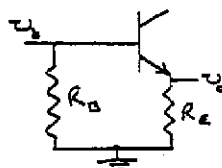


$$r_x = \frac{(100)(0.026)}{0.99} = 2.63 \text{ k}\Omega$$

$$\frac{v_o}{v_b} = \frac{(1+\beta) R_E}{r_x + (1+\beta) R_E} = \frac{(101)(5)}{2.63 + (101)(5)} = 0.995$$

$$\Rightarrow v_b = \frac{v_o}{0.995} = \frac{4}{0.995}$$
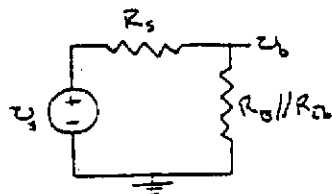
$$\Rightarrow v_b = 4.02 \text{ V peak-to-peak at base}$$



$$R_{ib} = r_\pi + (1 + \beta)R_E = 508 \text{ k}\Omega$$

$$R_B \parallel R_{ib} = 434 \parallel 508 = 234 \text{ k}\Omega$$

$$\nu_o = \frac{R_B \parallel R_{ib}}{R_B \parallel R_{ib} + R_s} \nu_s = \frac{234 \nu_s}{234 + 0.7} = \frac{234}{234.7} \nu_s$$

$$\nu_o = 0.997 \nu_s$$

$$\Rightarrow \nu_s = \frac{4.02}{0.997} \Rightarrow \nu_s = 4.03 \text{ V peak-to-peak}$$

$$c. \quad R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L)$$

$$R_{ib} = 2.63 + (101)(5 \parallel 1) = 86.8 \text{ k}\Omega$$

$$R_B \parallel R_{ib} = 434 \parallel 86.8 = 72.3 \text{ k}\Omega$$

$$\nu_o = \left(\frac{72.3}{72.3 + 0.7} \right) \nu_s = 0.99 \nu_s = (0.99)(4.03)$$

$$\nu_o = 3.99 \text{ V peak-to-peak}$$

$$\nu_o = \frac{(1 + \beta)(R_E \parallel R_L)}{r_\pi + (1 + \beta)(R_E \parallel R_L)} \nu_b$$

$$= \frac{(101)(0.833)}{2.63 + (101)(0.833)} (3.99)$$

$$\nu_o = 3.87 \text{ V peak-to-peak}$$

4.43

$$P_{AVG} = i_L^2(rms) R_L \Rightarrow 1 = i_L^2(rms)(12)$$

$$\text{so } i_L(rms) = 0.289 \text{ A} \Rightarrow i_L(peak) = \sqrt{2}(0.289)$$

$$i_L(peak) = 0.409 \text{ A}$$

$$\nu_L(peak) = i_L(peak) \cdot R_L = (0.409)(12) = 4.91 \text{ V}$$

$$\text{Need a gain of } \frac{4.91}{5} = 0.982$$

With $R_s = 10 \text{ k}\Omega$, we will not be able to meet this voltage gain requirement. Need to insert a buffer or an op-amp voltage follower (see Chapter 9) between R_s and C_{in} .

$$\text{Set } I_{EQ} = 0.5 \text{ A}, \quad V_{CEQ} = \frac{1}{3}(12 - (-12)) = 8 \text{ V}$$

$$24 = I_{EQ}R_E + V_{CEQ} = (0.5)R_E + 8 \Rightarrow R_E = 32 \text{ }\Omega$$

$$\text{Let } \beta = 50, \quad I_{CQ} = \frac{50}{51}(0.5) = 0.49 \text{ A}$$

$$r_x = \frac{\beta V_T}{I_{CQ}} = \frac{(50)(0.026)}{0.49} = 2.65 \text{ }\Omega$$

$$R_{ib} = r_x + (1 + \beta)(R_E \parallel R_L) = 2.65 + (51)(32 \parallel 12)$$

$$R_{ib} = 448 \text{ }\Omega$$

$$I_{BQ} = \frac{0.49}{50} = 0.0098 \text{ A} = 9.8 \text{ mA}$$

$$\text{Let } I_R = \frac{24}{R_1 + R_2} \approx 10 I_B = 98 \text{ mA}$$

$$\text{So that } R_1 + R_2 = 245 \text{ }\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2}(24) - 12 = I_{BQ}R_{TH} + V_{BE}(on)$$

$$+ I_{EQ}R_E - 12$$

$$\left(\frac{R_2}{245} \right)(24) = \frac{(0.0098)R_1R_2}{245} + 0.7 + (0.5)(32)$$

$$\text{Now } R_1 = 245 - R_2$$

So we obtain

$$4 \times 10^{-5} R_2^2 + 0.0882 R_2 - 16.7 = 0$$

$$\text{which yields } R_2 = 175 \text{ }\Omega \text{ and } R_1 = 70 \text{ }\Omega$$

4.44

$$(a) \quad R_{TH} = R_1 \parallel R_2 = 25.6 \parallel 10.4 = 7.40 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \left(\frac{10.4}{10.4 + 25.6} \right) (18) = 5.2 \text{ V}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$$

$$I_{BQ} = \frac{5.2 - 0.7}{7.40 + (126)(3)} = 0.0117 \text{ mA}$$

$$\text{Then } I_{CQ} = 1.46 \text{ mA and } I_{EQ} = 1.47 \text{ mA}$$


$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E$$

$$V_{CEQ} = 18 - (1.46)(4) - (1.47)(3) \Rightarrow V_{CEQ} = 7.75 \text{ V}$$

(b)

$$r_x = \frac{(125)(0.026)}{1.46} = 2.23 \text{ k}\Omega$$
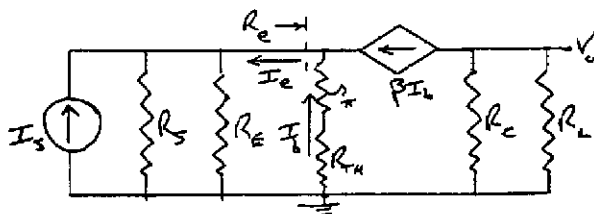
$$g_m = \frac{1.46}{0.026} = 56.2 \text{ mA/V}$$



$$R_x = \frac{r_x + R_{TH}}{1 + \beta} = \frac{2.23 + 7.40}{126} = 0.0764 \text{ k}\Omega$$

$$I_e = \frac{-(R_s \parallel R_E)}{(R_s \parallel R_E) + R_x} I_s = \frac{-(100 \parallel 3)}{(100 \parallel 3) + 0.0764} I_s$$

$$\text{or } I_e = -(0.974) I_s$$

$$V_o = -I_e(R_C \parallel R_L) = -\left(\frac{\beta}{1 + \beta} \right) I_s(R_C \parallel R_L)$$

Then

$$\frac{V_o}{I_s} = -\left(\frac{\beta}{1+\beta}\right)(-0.974)(R_C \parallel R_L) = \left(\frac{125}{126}\right)(0.974)(4 \parallel 4)$$

Then

$$R_m = \frac{V_o}{I_s} = 1.93 \text{ k}\Omega = 1.93 \text{ V/mA}$$

(c)

$$V_s = I_s(R_S \parallel R_E \parallel R_r) = I_s(100 \parallel 3 \parallel 0.0764) = I_s(0.0744)$$

$$\text{or } I_s = \frac{V_s}{0.0744}$$

$$\text{which yields } \frac{V_o}{I_s} = \frac{V_o}{V_s}(0.0744) = 1.93$$

$$\text{or } A_v = \frac{V_o}{V_s} = 25.9$$

4.45

$$(a) A_v = \frac{\beta(R_C \parallel R_L)}{r_\pi + R_1 \parallel R_2}, \quad R_L = 12 \text{ k}\Omega, \quad \beta = 100$$

$$\text{Let } R_1 \parallel R_2 = 50 \text{ k}\Omega, \quad I_{CQ} = 0.5 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1+\beta)I_{BQ}R_E$$

$$I_{BQ} = \frac{0.5}{100} = 0.005 \text{ mA}, \quad r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(50)(12) = (0.005)(50) + 0.7 + (101)(0.005)(0.5)$$

$$\text{which yields } R_1 = 500 \text{ k}\Omega \text{ and } R_2 = 55.6 \text{ k}\Omega$$

$$A_v = \frac{(100)(12 \parallel 12)}{5.2 + 50} = 10.7, \text{ Design criterion is met.}$$

(b)

$$I_{CQ} = 0.5 \text{ mA}, \quad I_{EQ} = 0.505 \text{ mA}$$

$$V_{CEQ} = 12 - (0.5)(12) - (0.505)(0.5) \Rightarrow$$

$$V_{CEQ} = 5.75 \text{ V}$$

$$A_v = g_m(R_C \parallel R_L), \quad g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$A_v = (19.23)(12 \parallel 12) \Rightarrow A_v = 115$$

4.46

$$i_s(\text{peak}) = 2.5 \mu\text{A}, \quad v_o(\text{peak}) = 5 \text{ mV}$$

$$\text{So we need } R_m = \frac{v_o}{i_s} = \frac{5 \times 10^{-3}}{2.5 \times 10^{-6}} = 2 \times 10^3 = 2 \text{ k}\Omega$$

From Problem 4.44

$$\frac{V_o}{I_s} = \left(\frac{\beta}{1+\beta}\right)(R_C \parallel R_L) \left(\frac{R_S \parallel R_E}{R_S \parallel R_E + R_r}\right)$$

$$\text{Let } R_C = 4 \text{ k}\Omega, \quad R_L = 5 \text{ k}\Omega, \quad R_E = 2 \text{ k}\Omega$$

Now $\beta = 120$, so we have

$$2 = \left(\frac{120}{121}\right)(4 \parallel 5) \left(\frac{R_S \parallel R_E}{R_S \parallel R_E + R_r}\right) = 2.20 \left(\frac{R_S \parallel R_E}{R_S \parallel R_E + R_r}\right)$$

$$\text{Then } \frac{R_S \parallel R_E}{R_S \parallel R_E + R_r} = 0.909$$

$$R_S \parallel R_E = 50 \parallel 2 = 1.92 \text{ k}\Omega, \text{ so that } R_r = 0.192 \text{ k}\Omega$$

Assume $V_{CEQ} = 6 \text{ V}$

$$V_{CC} \equiv I_{CQ}(R_C + R_E) + V_{CEQ}$$

$$12 = I_{CQ}(4 + 2) + 6 \Rightarrow I_{CQ} = 1 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$R_r = \frac{r_\pi + R_{TH}}{1 + \beta} \Rightarrow 0.192 = \frac{3.12 + R_{TH}}{121}$$

$$\text{which yields } R_{TH} = 20.1 \text{ k}\Omega$$

$$\text{Now } V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

$$I_{BQ} = \frac{1}{120} = 0.00833 \text{ mA}, \quad I_{EQ} = \left(\frac{121}{120}\right)(1) = 1.008 \text{ mA}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(20.1)(5) = (0.00833)(20.1) + 0.7 + (1.008)(2)$$

$$\text{which yields } R_1 = 34.9 \text{ k}\Omega \text{ and } R_2 = 47.4 \text{ k}\Omega$$

4.47

a. Emitter current

$$I_{EQ} = I_{CC} = 0.5 \text{ mA}$$

$$I_{BQ} = \frac{0.5}{101} = 0.00495 \text{ mA}$$

$$V_E = I_{EQ}R_E = (0.5)(1) \Rightarrow V_E = 0.5 \text{ V}$$


$$V_B = V_E + V_{BE(on)} = 0.5 + 0.7 \Rightarrow V_B = 1.20 \text{ V}$$

$$V_C = V_B + I_{BQ}R_B = 1.20 + (0.00495)(100)$$

$$\Rightarrow V_C = 1.7 \text{ V}$$

$$b. \quad r_\pi = \frac{(100)(0.026)}{(100)(0.00495)} = 5.25 \text{ k}\Omega$$
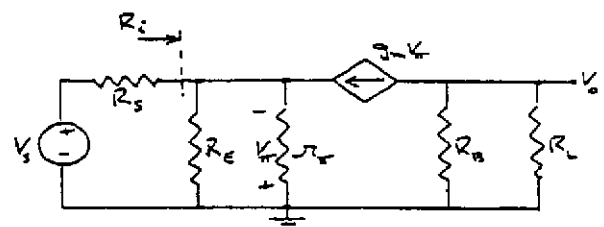
$$g_m = \frac{(100)(0.00495)}{0.026} = 19.0 \text{ mA/V}$$



$$V_o = -g_m V_\pi (R_B \parallel R_L)$$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{\left(\frac{R_E}{R_E + R_S}\right) V_S - (-V_\pi)}{R_S \parallel R_E} = 0$$

$$V_\pi \left[g_m + \frac{1}{r_\pi} + \frac{1}{R_S \parallel R_E} \right] = \frac{-\left(\frac{R_E}{R_E + R_S}\right) V_S}{R_S \parallel R_E}$$


$$V_\pi \left[19.0 + \frac{1}{5.25} + \frac{1}{0.05 \parallel 1} \right] = \frac{-\left(\frac{1}{1 + 0.05}\right) V_S}{0.05 \parallel 1}$$

$$V_\pi (40.19) = -20 V_S \Rightarrow V_\pi = -(0.4976) V_S$$

$$V_o = (19)(0.4976) V_S (100 \parallel 1)$$

$$A_v = 9.36$$

c.

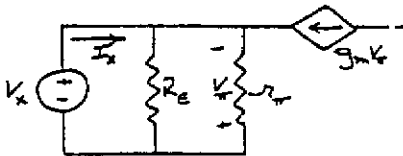

$$I_X = \frac{V_X}{R_E} + \frac{V_X}{r_\pi} - g_m V_\pi, \quad V_\pi = -V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_i} = \frac{1}{R_E} + \frac{1}{r_\pi} + g_m$$

$$\text{or } R_i = R_E \parallel r_\pi \parallel \frac{1}{g_m} = 1 \parallel 5.25 \parallel \frac{1}{19}$$

$$R_i = 0.84 \parallel 0.0526$$

$$\Rightarrow R_i = 49.5 \Omega$$

4.48

$$a. \quad I_{EQ} = \frac{20 - 0.7}{10} = 1.93 \text{ mA}$$


$$I_{CQ} = 1.91 \text{ mA}$$

$$V_{ECQ} = V_{CC} + V_{EB(\text{on})} - I_C R_C$$

$$= 25 + 0.7 - (1.91)(6.5)$$

$$\Rightarrow V_{ECQ} = 13.3 \text{ V}$$

b.

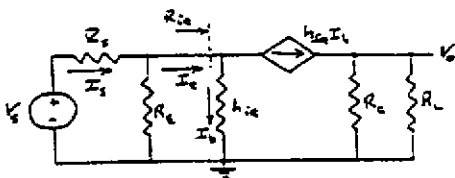

Neglect effect of h_{oe} .

From Problem 4-16, assume

$$2.45 \leq h_{ie} \leq 3.7 \text{ k}\Omega$$

$$80 \leq h_{fe} \leq 120$$

$$V_o = (h_{fe} I_b)(R_C \parallel R_L)$$

$$R_{ie} = \frac{h_{ie}}{1 + h_{fe}}, \quad I_e = \left(\frac{R_E}{R_E + R_{ie}}\right) I_S$$

$$I_b = \left(\frac{I_e}{1 + h_{fe}}\right), \quad I_S = \frac{V_S}{R_S + R_E \parallel R_{ie}}$$

$$A_v = \left(\frac{h_{fe}}{1 + h_{fe}}\right)(R_C \parallel R_L) \left(\frac{R_E}{R_E + R_{ie}}\right) \times \left(\frac{1}{R_S + R_E \parallel R_{ie}}\right)$$

High gain device: $h_{ie} = 3.7 \text{ k}\Omega$, $h_{fe} = 120$

$$R_{ie} = \frac{3.7}{121} = 0.0306 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.0306 = 0.0305$$

$$A_v = \left(\frac{120}{121}\right)(6.5 \parallel 5) \left(\frac{10}{10 + 0.0306}\right) \left(\frac{1}{1 + 0.0305}\right)$$

$$\Rightarrow A_v = 2.711$$

Low gain device: $h_{ie} = 2.45 \text{ k}\Omega$, $h_{fe} = 80$

$$R_{ie} = \frac{2.45}{81} = 0.03025 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.03025 = 0.0302$$

$$A_v = \left(\frac{80}{81}\right)(6.5 \parallel 5) \left(\frac{10}{10 + 0.03025}\right) \left(\frac{1}{1 + 0.0302}\right)$$

$$\Rightarrow A_v = 2.70 \text{ So } A_v \approx \text{constant}$$

$$2.70 < A_v < 2.71$$

$$c. \quad R_i = R_E \parallel R_{ie}$$

$$\text{We found } 0.0302 < R_i < 0.0305 \text{ k}\Omega$$

$$\text{Neglecting } h_{oe}, \quad R_o = R_C = 6.5 \text{ k}\Omega$$

4.49

a. Small-signal voltage gain

$$A_v = g_m(R_C \parallel R_L) \Rightarrow 25 = g_m(R_C \parallel 1)$$

$$\text{For } V_{ECQ} = 3 \text{ V}$$

$$\Rightarrow V_C = -V_{ECQ} + V_{EB(\text{on})} = -3 + 0.7$$

$$\Rightarrow V_C = -2.3$$

$$V_{CC} - I_{CQ} R_C + V_C = 0$$

$$\Rightarrow I_{CQ} = \frac{5 - 2.3}{R_C} = \frac{2.7}{R_C} = I_{CQ}$$

$$\text{For } I_{CQ} = 1 \text{ mA}, \quad R_C = 2.7 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.5 \text{ mA/V}$$

$$A_v = (38.5)(2.7 \parallel 1) = 28.1$$

Design criterion satisfied and V_{ECQ} satisfied.

$$I_E = \left(\frac{101}{100} \right) (1) = 1.01 \text{ mA}$$

$$V_{EE} = I_E R_E + V_{EB}(\text{on})$$

$$\Rightarrow R_E = \frac{5 - 0.7}{1.01} \Rightarrow R_E = 4.26 \text{ k}\Omega$$

$$\text{b. } r_e = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1}$$

$$\Rightarrow r_e = 2.6 \text{ k}\Omega, \quad g_m = 38.5 \text{ mA/V}, \quad r_o = \infty$$

4.50

$$\text{a. } V_{TH1} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{20}{20 + 80} \right) (10)$$

$$\Rightarrow V_{TH1} = 2.0 \text{ V}$$

$$R_{TH1} = R_1 \parallel R_2 = 20 \parallel 80 = 16 \text{ k}\Omega$$

$$I_{B1} = \frac{2 - 0.7}{16 + (101)(1)} = 0.0111 \text{ mA}$$

$$I_{C1} = 1.11 \text{ mA}$$

$$\Rightarrow g_{m1} = \frac{1.11}{0.026} \Rightarrow g_{m1} = 42.7 \text{ mA/V}$$

$$r_{\pi 1} = \frac{(100)(0.026)}{1.11} \Rightarrow r_{\pi 1} = 2.34 \text{ k}\Omega$$

$$r_{o1} = \frac{\infty}{1.11} \Rightarrow r_{o1} = \infty$$

$$V_{TH2} = \left(\frac{R_4}{R_3 + R_4} \right) V_{CC} = \left(\frac{15}{15 + 85} \right) (10) = 1.50 \text{ V}$$

$$R_{TH2} = R_3 \parallel R_4 = 15 \parallel 85 = 12.75 \text{ k}\Omega$$

$$I_{B2} = \frac{1.50 - 0.70}{12.75 + (101)(0.5)} = 0.0126 \text{ mA}$$

$$I_{C2} = 1.26 \text{ mA}$$

$$\Rightarrow g_{m2} = \frac{1.26}{0.026} \Rightarrow g_{m2} = 48.5 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{1.26} \Rightarrow r_{\pi 2} = 2.06 \text{ k}\Omega$$

$$r_{o2} = \infty$$

$$\text{b. } A_{v1} = -g_{m1} R_{C1} = -(42.7)(2)$$

$$\Rightarrow A_{v1} = -85.4$$

$$A_{v2} = -g_{m2} (R_{C2} \parallel R_L) = -(48.5)(4 \parallel 4)$$

$$\Rightarrow A_{v2} = -97$$

c. Input resistance of 2nd stage

$$R_{i2} = R_3 \parallel R_4 \parallel r_{\pi 2} = 15 \parallel 85 \parallel 2.06$$

$$= 12.75 \parallel 2.06 \Rightarrow R_{i2} = 1.77 \text{ k}\Omega$$

$$A'_{v1} = -g_{m1} (R_{C1} \parallel R_{i2}) = -(42.7)(2 \parallel 1.77)$$

$$A'_{v1} = -40.1$$

$$\text{Overall gain: } A_v = (-40.1)(-97) \Rightarrow A_v = 3890$$

$$\text{If we had } A_{v1} \cdot A_{v2} = (-85.4)(-97) = 8284$$

Loading effect reduces overall gain

4.51

$$\text{a. } V_{TH1} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{12.7}{12.7 + 67.3} \right) (12)$$

$$\Rightarrow V_{TH1} = 1.905 \text{ V}$$

$$R_{TH1} = R_1 \parallel R_2 = 12.7 \parallel 67.3 = 10.68 \text{ k}\Omega$$

$$I_{B1} = \frac{1.905 - 0.70}{10.68 + (121)(2)} = 0.00477 \text{ mA}$$

$$I_{C1} = 0.572 \text{ mA}$$

$$g_{m1} = \frac{0.572}{0.026} \Rightarrow g_{m1} = 22 \text{ mA/V}$$

$$r_{\pi 1} = \frac{(120)(0.026)}{0.572} \Rightarrow r_{\pi 1} = 5.45 \text{ k}\Omega$$

$$r_{o1} = \frac{\infty}{0.572} \Rightarrow r_{o1} = \infty$$

$$V_{TH2} = \left(\frac{R_4}{R_3 + R_4} \right) V_{CC} = \left(\frac{45}{45 + 15} \right) (12)$$

$$\Rightarrow V_{TH2} = 9.0 \text{ V}$$

$$R_{TH2} = R_3 \parallel R_4 = 15 \parallel 45 = 11.25 \text{ k}\Omega$$

$$I_{B2} = \frac{9.0 - 0.70}{11.25 + (121)(1.6)} = 0.0405 \text{ mA}$$

$$I_{C2} = 4.86 \text{ mA}$$

$$g_{m2} = \frac{4.86}{0.026} \Rightarrow g_{m2} = 187 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(120)(0.026)}{4.86} \Rightarrow r_{\pi 2} = 0.642 \text{ k}\Omega$$

$$r_{o2} = \infty$$



$$\text{b. } I_{E1} = 0.577 \text{ mA}$$

$$V_{CEQ1} = 12 - (0.572)(10) - (0.577)(2)$$

$$\Rightarrow V_{CEQ1} = 5.13 \text{ V}$$

$$I_{E2} = 4.90$$
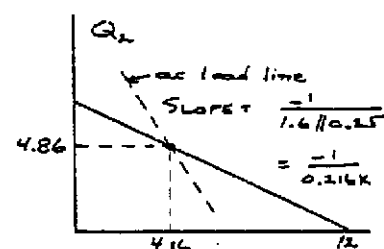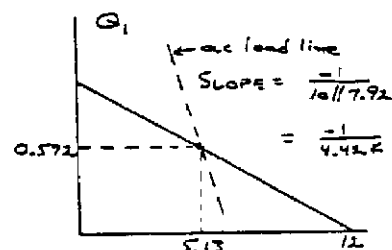
$$V_{CEQ2} = 12 - (4.90)(1.6) \Rightarrow V_{CEQ2} = 4.16 \text{ V}$$



$$R_{i2} = R_3 \parallel R_4 \parallel R_{i3}$$

$$R_{i3} = r_{\pi 2} + (1 + \beta)(R_{E2} \parallel R_L)$$

$$= 0.642 + (121)(1.6 \parallel 0.25)$$

$$R_{i3} = 26.8$$

$$R_{i2} = 15 \parallel 45 \parallel 26.8$$

$$R_{i2} = 7.92 \text{ k}\Omega$$

c. $A_{v1} = -g_{m1}(R_{C1} \parallel R_{i2}) = -(22)(10 \parallel 7.92)$

$$\Rightarrow A_{v1} = -97.2$$

$$A_{v2} = \frac{(1 + \beta)(R_{E2} \parallel R_L)}{r_{\pi 2} + (1 + \beta)(R_{E2} \parallel R_L)}$$

$$= \frac{(121)(0.216)}{0.642 + (121)(0.216)} = 0.976$$

$$\text{Overall gain} = (-97.2)(0.976) = \underline{-94.9}$$

d. $R_{i5} = R_1 \parallel R_2 \parallel r_{\pi 1} = 67.3 \parallel 12.7 \parallel 5.45$

$$\Rightarrow R_{i5} = 3.61 \text{ k}\Omega$$

$$R_0 = \frac{r_{\pi 2} + R_S}{1 + \beta} \parallel R_{E2} \text{ where}$$

$$R_S = R_3 \parallel R_4 \parallel R_{C1}$$

$$= 15 \parallel 45 \parallel 10 \Rightarrow R_S = 5.29 \text{ k}\Omega$$

$$R_0 = \frac{0.642 + 5.29}{121} \parallel 1.6 \Rightarrow 0.049 \parallel 1.6$$

$$\Rightarrow R_0 = \underline{47.5 \Omega}$$

e. $\Delta i_C = \frac{-1}{0.216 \text{ k}\Omega} \cdot \Delta v_{ce}$. $\Delta i_C = 4.86$

$$|\Delta v_{ce}| = (4.86)(0.216) = 1.05 \text{ V}$$

Max. output voltage swing

$$= \underline{2.10 \text{ V peak-to-peak}}$$

4.52

(a) $I_{R1} = \frac{5 - 2(0.7)}{0.050} = 72 \text{ mA}$


$$I_{R2} = \frac{0.7}{0.5} = 1.4 \text{ mA}$$

$$I_{C2} = \left(\frac{\beta}{1 + \beta} \right) (72 - 1.4) \Rightarrow I_{C2} = 69.9 \text{ mA}$$

$$I_{E2} = \frac{69.9}{100} = 0.699 \text{ mA}$$

$$I_{C1} = \left(\frac{\beta}{1 + \beta} \right) (1.4 + 0.699) \Rightarrow I_{C1} = 2.08 \text{ mA}$$

(b)

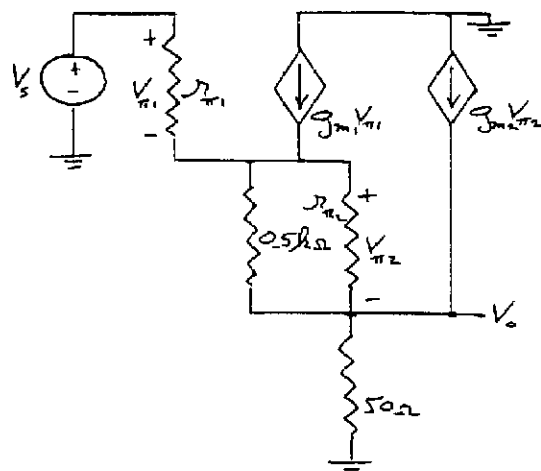

$$V_s = V_{\pi 1} + V_{\pi 2} + V_o$$

$$(1) V_o = \left(\frac{V_{\pi 2}}{0.5} + \frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} \right) (0.05)$$

$$r_{\pi 2} = \frac{(100)(0.026)}{69.9} = 0.0372 \text{ k}\Omega$$

$$g_{m2} = \frac{69.9}{0.026} = 2688 \text{ mA/V}$$

$$V_o = V_{\pi 2} \left(\frac{1}{0.05} + \frac{1}{0.0372} + 2688 \right) (0.05)$$

$$\text{so that } (1) V_{\pi 2} = \frac{V_o}{136.7}$$

$$(2) \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{\pi 2}}{0.5} + \frac{V_{\pi 2}}{r_{\pi 2}}$$

$$r_{\pi 1} = \frac{(100)(0.026)}{2.08} = 1.25 \text{ k}\Omega$$

$$g_{m1} = \frac{2.08}{0.026} = 80 \text{ mA/V}$$

$$V_{\pi 1} \left(\frac{1}{1.25} + 80 \right) = V_{\pi 2} \left(\frac{1}{0.5} + \frac{1}{0.0372} \right)$$

$$V_{\pi 1} (80.8) = V_{\pi 2} (28.88) = \left(\frac{V_o}{136.7} \right) (28.88)$$

$$\text{or } (2) V_{\pi 1} = V_o (0.00261)$$


Then

$$V_s = V_o (0.00261) + \frac{V_o}{136.7} + V_o = V_o (1.00993)$$

$$\text{or } A_v = \frac{V_o}{V_s} = 0.990$$

(c)
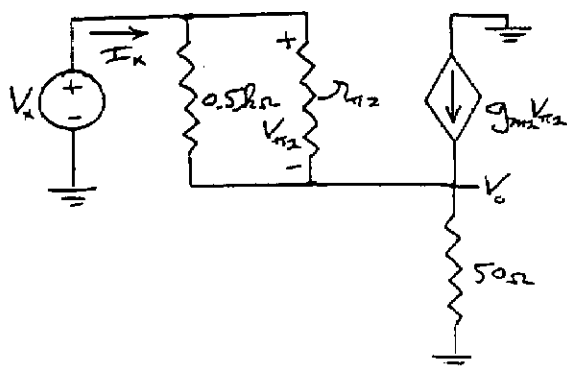
$$R_{ib} = r_{\pi 1} + (1 + \beta)[R_s]$$




$$I_x = \frac{V_{x2}}{0.5} + \frac{V_{x2}}{r_{x2}} = V_{x2} \left(\frac{1}{0.5} + \frac{1}{r_{x2}} \right)$$

$$\frac{V_o}{0.05} = \frac{V_x - V_{x2}}{0.05} = I_x + g_{m2} V_{x2}$$

$$\frac{V_x}{0.05} - I_x = V_{x2} \left(\frac{1}{0.05} + g_{m2} \right) = \frac{I_x \left(\frac{1}{0.05} + g_{m2} \right)}{\left(\frac{1}{0.05} + \frac{1}{r_{x2}} \right)}$$

We find $\frac{V_o}{I_x} = R_o = 2.89 \text{ k}\Omega$

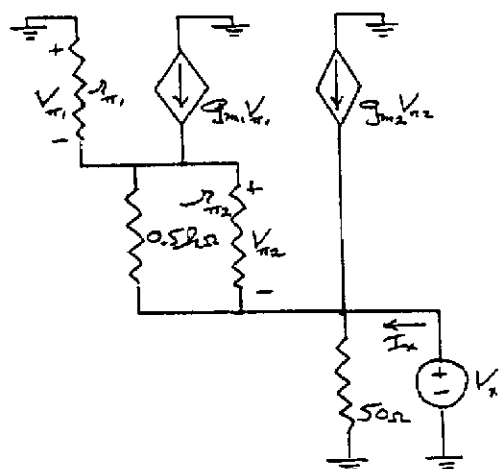Then $R_{ib} = 1.25 + (101)(2.89) \Rightarrow \underline{R_{ib} = 293 \text{ k}\Omega}$



To find R_o :

$$(1) I_x = \frac{V_x}{0.05} - g_{m2} V_{x2} - \frac{V_{x2}}{0.05 \parallel r_{x2}}$$

$$(2) V_{x2} = \left(\frac{V_{x1}}{r_{x1}} + g_{m1} V_{x1} \right) (0.05 \parallel r_{x2})$$

$$= V_{x1} \left(\frac{1}{1.25} + 80 \right) (0.05 \parallel 0.0372)$$

or $V_{x2} = (1.72) V_{x1}$

$$(3) V_{x1} + V_{x2} + V_x = 0 \Rightarrow V_{x1} + (1.72) V_{x1} + V_x = 0$$

so that $V_{x1} = -(0.368) V_x$

and $V_{x2} = (1.72) [-(0.368) V_x] = -(0.633) V_x$

Now $I_x = \frac{V_x}{0.05} - V_{x2} \left(g_{m2} + \frac{1}{0.05 \parallel r_{x2}} \right)$

So that

$$I_x = \frac{V_x}{0.05} + (0.633) V_x \left[2688 + \frac{1}{0.05 \parallel 0.0372} \right]$$

which yields

$$R_o = \frac{V_x}{I_x} = 0.583 \Omega$$

4.53

a. $R_{TH} = R_1 \parallel R_2 = 335 \parallel 125 = 91.0 \text{ k}\Omega$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$= \left(\frac{125}{125 + 335} \right) (10) = 2.717 \text{ V}$$

$$V_{TH} = I_{B1} R_{TH} + V_{BE1} + V_{BE2} + I_{E2} R_{E2}$$

$$I_{E2} = (1 + \beta) I_{E1} = (1 + \beta)^2 I_{B1}$$

$$I_{B1} = \frac{2.717 - 1.40}{91.0 + (101)^2 (1)} \Rightarrow I_{B1} = 0.128 \mu\text{A}$$

$$I_{C1} = 12.8 \mu\text{A}$$

$$I_{C2} = \beta I_{E1} = \beta (1 + \beta) I_{B1} = (100)(101)(0.128 \mu\text{A})$$

$$I_{C2} = 1.29 \text{ mA}, \quad I_{E2} = 1.31 \text{ mA}$$

$$I_{RC} = I_{C2} + I_{C1} = 1.29 + 0.0128 = 1.31 \text{ mA}$$

$$V_C = 10 - I_{RC} R_C = 10 - (1.31)(2.2) = 7.12 \text{ V}$$

$$V_E = I_{E2} R_{E2} = (1.31)(1) = 1.31 \text{ V}$$

$$V_{CE2} = 7.12 - 1.31 = 5.81 \text{ V}$$

$$V_{CE1} = V_{CE2} - V_{BE2} = 5.81 - 0.7$$

$$V_{CE1} = 5.11 \text{ V}$$


Summary:

$$I_{C1} = 12.8 \mu\text{A} \quad I_{C2} = 1.29 \text{ mA}$$

$$V_{CE1} = 5.11 \text{ V} \quad V_{CE2} = 5.81 \text{ V}$$

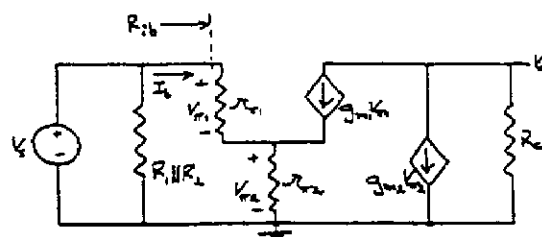b. $g_{m1} = \frac{0.0128}{0.026} = 0.492 \text{ mA/V}$

$$g_{m2} = \frac{1.29}{0.026} = 49.6 \text{ mA/V}$$



$$V_0 = -(g_{m1}V_{\pi1} + g_{m2}V_{\pi2})R_C$$

$$V_S = V_{\pi1} + V_{\pi2}, \quad V_{\pi1} = V_S - V_{\pi2}$$

$$V_{\pi2} = \left(\frac{V_{\pi1}}{r_{\pi1}} + g_{m1}V_{\pi1} \right) r_{\pi2}$$

$$V_{\pi2} = V_{\pi1} \left(\frac{1 + \beta}{r_{\pi1}} \right) r_{\pi2}$$

$$r_{\pi1} = \frac{(100)(0.026)}{0.0128} = 203 \text{ k}\Omega$$

$$r_{\pi2} = \frac{(100)(0.026)}{1.29} = 2.02 \text{ k}\Omega$$

$$V_0 = -[g_{m1}(V_S - V_{\pi2}) + g_{m2}V_{\pi2}]R_C$$

$$V_0 = -[g_{m1}V_S + (g_{m2} - g_{m1})V_{\pi2}]R_C$$

$$V_{\pi2} = (V_S - V_{\pi2})(1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)$$

$$V_{\pi2} \left[1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right) \right] = V_S(1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)$$

$$V_0 = - \left\{ g_{m1}V_S + (g_{m2} - g_{m1}) \cdot \frac{V_S(1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)}{1 + (1 + \beta) \left(\frac{r_{\pi2}}{r_{\pi1}} \right)} \right\} R_C$$

$$A_v = \frac{V_0}{V_S}$$

$$= - \left\{ (0.492) + \frac{(49.6 - 0.492)(101) \left(\frac{2.02}{203} \right)}{1 + (101) \left(\frac{2.02}{203} \right)} \right\} 2.2$$

$$A_v = -55.2$$

c. $R_{i_s} = R_1 \parallel R_2 \parallel R_{i_b}$


$$R_{i_b} = r_{\pi1} + (1 + \beta)r_{\pi2}$$

$$= 203 + (101)(2.02) = 407 \text{ k}\Omega$$

$$R_{i_s} = 91 \parallel 407 = 74.4 \text{ k}\Omega = R_{i_s}$$

$$R_0 = R_C = 2.2 \text{ k}\Omega$$

4.54

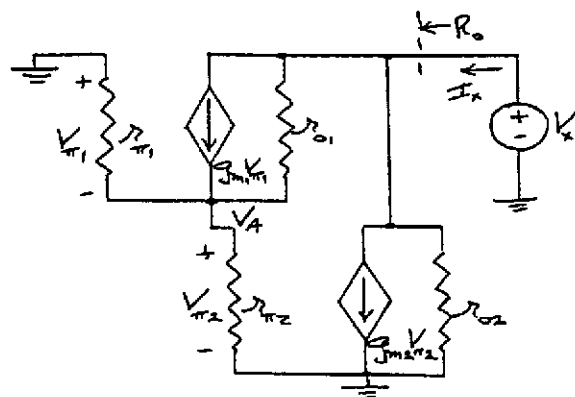

$$(1) I_x = g_{m2}V_{\pi2} + \frac{V_x}{r_{o2}} + \frac{V_x - V_A}{r_{o1}} + g_{m1}V_{\pi1}$$

$$(2) \frac{V_x - V_A}{r_{o1}} + g_{m1}V_{\pi1} = \frac{V_A}{r_{\pi1} \parallel r_{\pi2}}$$

$$(3) V_{\pi2} = V_A = -V_{\pi1}$$

Then from (2)

$$\frac{V_x}{r_{o1}} = V_A \left(\frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}} \right)$$

$$(1) I_x = g_{m2}V_A + \frac{V_x}{r_{o2}} + \frac{V_x}{r_{o1}} - \frac{V_A}{r_{o1}} - g_{m1}V_A$$

$$\text{or } I_x = V_x \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) + V_A \left(g_{m2} - \frac{1}{r_{o1}} - g_{m1} \right)$$

Solving for V_A from Equation (2) and substituting into Equation (1), we find

$$R_o = \frac{V_x}{I_x} = \frac{\frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}}}{\frac{1}{r_{o2}} \left(\frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}} \right) + \frac{1}{r_{o1}} \left(\frac{1}{r_{\pi1} \parallel r_{\pi2}} + g_{m2} \right)}$$

For $\beta = 100$, $V_A = 100 \text{ V}$, $I_{C1} = I_{Bias} = 1 \text{ mA}$

$$r_{o1} = r_{o2} = \frac{100}{1} = 100 \text{ k}\Omega$$

$$r_{\pi1} = r_{\pi2} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Then

$$R_o = \frac{\frac{1}{100} + 38.46 + \frac{1}{2.6 \parallel 2.6}}{\frac{1}{100} \left(\frac{1}{100} + 38.46 + \frac{1}{2.6 \parallel 2.6} \right) + \frac{1}{100} \left(\frac{1}{2.6 \parallel 2.6} + 38.46 \right)}$$

or

$$R_o = 50.0 \text{ k}\Omega$$

Now

$$I_{C2} = 1 \text{ mA}, I_{Bias} = 0$$

$$\text{Replace } I_{Bias} \text{ by } \frac{I_{C2}}{\beta} \cdot \frac{\beta}{1 + \beta} = \frac{I_{C2}}{1 + \beta}, \quad I_{C1} \cong 0.01 \text{ mA}$$

$$r_{o2} = \frac{100}{1} = 100 \text{ k}\Omega, \quad r_{o1} = \frac{100}{0.01} = 10,000 \text{ k}\Omega$$

$$g_{m2} = \frac{1}{0.026} = 38.46 \text{ mA/V}, \quad g_{m1} = 0.3846 \text{ mA/V}$$

$$r_{\pi2} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega, \quad r_{\pi1} = 260 \text{ k}\Omega$$

Then

$$R_o = 66.4 \text{ k}\Omega$$

4.55

$$a. \quad R_{TH} = R_1 \| R_2 = 93.7 \| 6.3 = 5.90 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$= \left(\frac{6.3}{6.3 + 93.7} \right) (12) = 0.756 \text{ V}$$

$$I_{BQ} = \frac{0.756 - 0.70}{5.90} = 0.00949 \text{ mA}$$

$$I_{CQ} = 0.949 \text{ mA}$$

$$V_{CEQ} = 12 - (0.949)(6) \Rightarrow V_{CEQ} = 6.31 \text{ V}$$

Transistor:


$$P_Q \approx I_{CQ} V_{CEQ} = (0.949)(6.31)$$

$$\Rightarrow \underline{P_Q = 5.99 \text{ mW}}$$

$$R_C: \quad P_R = I_{CQ}^2 R_C = (0.949)^2 (6)$$

$$\Rightarrow \underline{P_R = 5.40 \text{ mW}}$$

b.

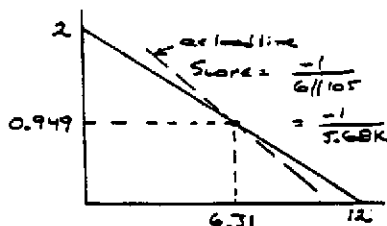

$$r_o = \frac{100}{0.949} = 105 \text{ k}\Omega$$

$$\text{Peak signal current} = 0.949 \text{ mA}$$

$$|V_o(\text{max})| = (5.68)(0.949) = 5.39 \text{ V}$$

$$P_{RC} = \frac{1}{2} \cdot \frac{V_o^2(\text{max})}{R_C} = \frac{1}{2} \left[\frac{(5.39)^2}{6} \right]$$

$$\Rightarrow \underline{P_{RC} = 2.42 \text{ mW}}$$

4.56

$$(a) \quad 10 = I_{BQ} R_B + V_{BE}(\text{on}) + (1 + \beta) I_{BQ} R_E$$

$$I_{BQ} = \frac{10 - 0.7}{100 + (121)(20)} = 0.00369 \text{ mA}$$

$$I_{CQ} = 0.443 \text{ mA}, \quad I_{EQ} = 0.447 \text{ mA}$$

$$\text{For } R_C: \quad P_{RC} = (0.443)^2 (10) \Rightarrow \underline{P_{RC} = 1.96 \text{ mW}}$$

$$\text{For } R_E: \quad P_{RE} = (0.447)^2 (20) \Rightarrow \underline{P_{RE} = 4.0 \text{ mW}}$$

(b)

$$\Delta i_C = 0.443 \text{ mA}, \quad \Delta v_{CE} = (0.443)(10) = 4.43 \text{ V}$$

Then

$$\overline{P_{RC}} = \frac{1}{2} (\Delta i_C)^2 R_C = \frac{1}{2} (0.443)^2 (10)$$

$$\underline{\overline{P_{RC}} = 0.981 \text{ mW}}$$

4.57

$$a. \quad I_{BQ} = \frac{10 - 0.7}{50 + (151)(10)} = 0.00596 \text{ mA}$$

$$I_{CQ} = 0.894 \text{ mA}, \quad I_{EQ} = 0.90 \text{ mA}$$

$$V_{ECQ} = 20 - (0.894)(5) - (0.90)(10)$$


$$\Rightarrow \underline{V_{ECQ} = 6.53 \text{ V}}$$

$$P_Q \approx I_{CQ} V_{ECQ} = (0.894)(6.53) \Rightarrow \underline{P_Q = 5.84 \text{ mW}}$$

$$P_{RC} \approx I_{CQ}^2 R_C = (0.894)^2 (5) \Rightarrow \underline{P_{RC} = 4.0 \text{ mW}}$$

$$P_{RE} \approx I_{EQ}^2 R_E = (0.90)^2 (10) \Rightarrow \underline{P_{RE} = 8.1 \text{ mW}}$$

b.

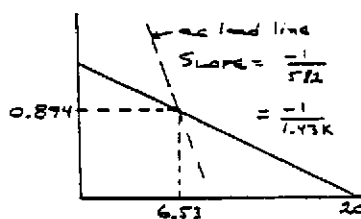

$$\Delta i_C = \frac{-1}{1.43 \text{ k}\Omega} \cdot \Delta v_{ec}$$

$$\Delta i_C = 0.894 \Rightarrow |\Delta v_{ec}| = (0.894)(1.43) = 1.28 \text{ V}$$

$$\Delta i_o = \left(\frac{5}{5 + 2} \right) \Delta i_C = 0.639 \text{ mA}$$

$$\overline{P_{RL}} = \frac{1}{2} (0.639)^2 (2) \Rightarrow \underline{\overline{P_{RL}} = 0.408 \text{ mW}}$$

$$\overline{P_{RC}} = \frac{1}{2} \cdot (0.894 - 0.639)^2 (5) \Rightarrow \underline{\overline{P_{RC}} = 0.163 \text{ mW}}$$

$$\underline{\overline{P_{RE}} = 0}$$

$$\underline{\overline{P_Q} = 5.84 - 0.408 - 0.163 \Rightarrow \overline{P_Q} = 5.27 \text{ mW}}$$


4.58

$$I_{BQ} = \frac{10 - 0.70}{100 + (101)(10)} = 0.00838 \text{ mA}$$

$$I_{CQ} = 0.838 \text{ mA}, \quad I_{EQ} = 0.846 \text{ mA}$$

$$V_{CEQ} = 20 - (0.838)(10) - (0.846)(10)$$

$$\Rightarrow V_{CEQ} = 3.16 \text{ V}$$

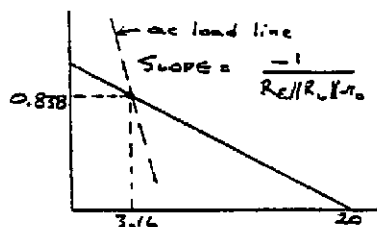

$$r_o = \frac{100}{0.838} = 119 \text{ k}\Omega$$

Neglecting base currents:

a. $R_L = 1 \text{ k}\Omega$

$$\text{slope} = \frac{-1}{10 \parallel 1 \parallel 119} = \frac{-1}{0.902 \text{ k}\Omega}$$

$$\Delta i_C = \frac{-1}{0.902 \text{ k}\Omega} \cdot \Delta v_{ce}$$

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.902)(0.838)$$

$$= 0.756 \text{ V}$$

$$\overline{P_{RL}} = \frac{1}{2} \frac{(0.756)^2}{1} \Rightarrow \overline{P_{RL}} = 0.286 \text{ mW}$$

b. $R_L = 10 \text{ k}\Omega$

$$\text{slope} = \frac{-1}{10 \parallel 10 \parallel 119} = \frac{-1}{4.80}$$

For

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.838)(4.80) = 4.02$$

Max. swing determined by voltage

$$\overline{P_{RL}} = \frac{1}{2} \frac{(3.16)^2}{10} \Rightarrow \overline{P_{RL}} = 0.499 \text{ mW}$$

4.59

a. $I_{BQ} = \frac{10 - 0.7}{100 + (101)(10)} = 0.00838 \text{ mA}$

$$I_{CQ} = 0.838 \text{ mA}, \quad I_{EQ} = 0.846 \text{ mA}$$


$$V_{CEQ} = 20 - (0.838)(10) - (0.846)(10)$$

$$\Rightarrow V_{CEQ} = 3.16 \text{ V}$$

$$P_Q \approx I_{CQ} V_{CEQ} = (0.838)(3.16) \Rightarrow \underline{P_Q = 2.65 \text{ mW}}$$

$$P_{RC} \approx I_{CQ}^2 R_C = (0.838)^2 (10) \Rightarrow \underline{P_{RC} = 7.02 \text{ mW}}$$

b.

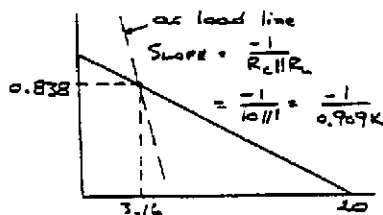

$$\Delta i_C = \frac{-1}{0.909 \text{ k}\Omega} \cdot \Delta v_{ce}$$

For

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.909)(0.838) = 0.762 \text{ V}$$

$$\Delta i_o = \left(\frac{R_C}{R_C + R_L} \right) \Delta i_C = \left(\frac{10}{10 + 1} \right) \Delta i_C = 0.762 \text{ mA}$$

$$\overline{P_{RL}} = \frac{1}{2} (0.762)^2 (1) \Rightarrow \underline{\overline{P_{RL}} = 0.290 \text{ mW}}$$

$$\overline{P_{RC}} = \frac{1}{2} \cdot (0.838 - 0.762)^2 (10) \Rightarrow \underline{\overline{P_{RC}} = 0.0289 \text{ mW}}$$

$$\overline{P_Q} = 2.65 - 0.290 - 0.0289 \Rightarrow \underline{\overline{P_Q} = 2.33 \text{ mW}}$$