

Chapter 6

Exercise Solutions

E6.1

$$\begin{aligned}
 g_m &= 2K_n(V_{GS} - V_{TN}) \text{ and} \\
 I_D &= K_n(V_{GS} - V_{TN})^2 \\
 0.75 &= 0.5(V_{GS} - 0.8)^2 \Rightarrow V_{GS} = 2.025 \text{ V} \\
 g_m &= 2(0.5)(2.025 - 0.8) \Rightarrow \underline{g_m = 1.22 \text{ mA/V}} \\
 r_o &= [\lambda K_n(V_{GS} - V_{TN})^2]^{-1} \\
 &= [(0.01)(0.5)(2.025 - 0.8)^2]^{-1} \Rightarrow \\
 \underline{r_o = 133 \text{ k}\Omega}
 \end{aligned}$$

E6.2

$$\begin{aligned}
 g_m &= 2K_n(V_{GS} - V_{TN}) \text{ and } I_D = K_n(V_{GS} - V_{TN})^2 \\
 \Rightarrow V_{GS} - V_{TN} &= \sqrt{\frac{I_{DQ}}{K_n}} \text{ and} \\
 g_m &= 2K_n \sqrt{\frac{I_{DQ}}{K_n}} = 2\sqrt{K_n I_{DQ}} \\
 K_n &= \frac{g_m^2}{4I_{DQ}} = \frac{(3.4)^2}{4(2)} = 1.45 \text{ mA/V} \\
 K_n &= \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \\
 1.45 &= (0.018) \left(\frac{W}{L} \right) \Rightarrow \underline{\frac{W}{L} = 80.6} \\
 r_o &= [\lambda K_n(V_{GS} - V_{TN})^2]^{-1} = [\lambda I_{DQ}]^{-1} \\
 r_o &= [(0.015)(2)]^{-1} \Rightarrow \underline{r_o = 33.3 \text{ k}\Omega}
 \end{aligned}$$

E6.3

$$\begin{aligned}
 \text{a. } I_{DQ} &= K_n(V_{GS} - V_{TN})^2 \\
 0.4 &= 0.5(V_{GS} - 2)^2 \Rightarrow \underline{V_{GS} = 2.89 \text{ V}} \\
 V_{DSQ} &= V_{DD} - I_{DQ}R_D = 10 - (0.4)(10) \\
 &\Rightarrow \underline{V_{DSQ} = 6 \text{ V}} \\
 \text{b. } g_m &= 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2.89 - 2) \\
 &\Rightarrow \underline{g_m = 0.89 \text{ mA/V}} \\
 r_o &= [\lambda I_{DQ}]^{-1}, \lambda = 0 \Rightarrow \underline{r_o = \infty} \\
 A_v &= \frac{v_o}{v_i} = -g_m R_D = -(0.89)(10) \\
 &\Rightarrow \underline{A_v = -8.9}
 \end{aligned}$$

$$\text{c. } v_i = 0.4 \sin \omega t \Rightarrow v_{ds} = -(8.9)(0.4) \sin \omega t$$

$$v_{ds} = -3.56 \sin \omega t$$

$$\text{At } V_{DS1} = 6 - 3.56 = 2.44$$

$$V_{GS1} = 2.89 + 0.4 = 3.29$$

$$V_{GS1} - V_{TN} = 3.29 - 2 = 1.29$$

$$\text{So } V_{DS1} > V_{GS1} - V_{TN} \Rightarrow \underline{\text{Biased in saturation region}}$$

E6.4

$$\text{a. } V_{SDQ} = V_{DD} - I_{DQ}R_D$$


$$7 = 12 - I_{DQ}(6) \Rightarrow I_{DQ} = 0.833 \text{ mA}$$

$$I_{DQ} = K_p(V_{SG} - |V_{TP}|)^2$$

$$0.833 = 2(V_{SG} - 1)^2 \Rightarrow \underline{V_{SG} = 1.65 \text{ V}}$$

$$\text{b. } g_m = 2K_p(V_{SG} - |V_{TP}|) = 2(2)(1.65 - 1)$$
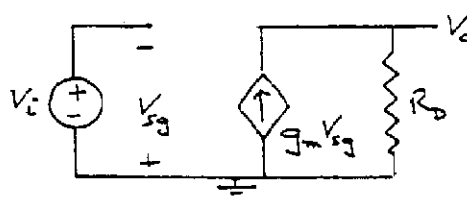
$$\Rightarrow \underline{g_m = 2.6 \text{ mA/V}}, \quad \underline{r_o = \infty}$$



$$A_v = \frac{v_o}{v_i} = -g_m R_D = -(2.6)(6)$$

$$\Rightarrow \underline{A_v = -15.6}$$

E6.5

$$\begin{aligned}
 I_{DQ} &= K_n(V_{GS} - V_{TN})^2 \Rightarrow V_{GS} - V_{TN} = \sqrt{\frac{I_{DQ}}{K_n}} \\
 g_m &= 2K_n(V_{GS} - V_{TN}) = 2K_n \sqrt{\frac{I_{DQ}}{K_n}} \\
 \text{So } g_m &= 2\sqrt{K_n I_{DQ}}
 \end{aligned}$$

E6.6

$$\eta = \frac{\gamma}{2\sqrt{2\phi_f + v_{ss}}}$$

$$\text{(a) } \eta = \frac{0.40}{2\sqrt{2(0.35) + 1}} \Rightarrow \underline{\eta = 0.153}$$

$$(b) \eta = \frac{0.40}{2\sqrt{2(0.35)+3}} \Rightarrow \eta = 0.104$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.75)} = 1.22 \text{ mA/V}$$

$$\text{For (a), } g_{mb} = g_m \eta = (1.22)(0.153) \Rightarrow$$

$$g_{mb} = 0.187 \text{ mA/V}$$

$$\text{For (b), } g_{mb} = (1.22)(0.104) \Rightarrow g_{mb} = 0.127 \text{ mA/V}$$

E6.7

$$a. \quad I_{DQ} = K_n (V_{GS} - V_{TN})^2 = (0.25)(2 - 0.8)^2$$

$$\Rightarrow I_{DQ} = 0.36 \text{ mA}$$

$$V_{DSQ} = V_{DD} - I_{DQ} R_D = 5 - (0.36)(5)$$

$$\Rightarrow V_{DSQ} = 3.2 \text{ V}$$

$$b. \quad g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.25)(2 - 0.8)$$

$$\Rightarrow g_m = 0.6 \text{ mA/V}, \quad r_o = \infty$$

$$c. \quad A_v = \frac{v_o}{v_i} = -g_m R_D = -(0.6)(5)$$

$$\Rightarrow A_v = -3.0$$

E6.8

$$v_i = v_{gs} = 0.1 \sin \omega t$$

$$i_d = g_m v_{gs} = (0.6)(0.1) \sin \omega t$$

$$i_d = 0.06 \sin \omega t \text{ mA}$$

$$v_{ds} = (-3)(0.1) \sin \omega t = -0.3 \sin \omega t$$

$$\text{Then } i_D = I_{DQ} + i_d = 0.36 + 0.06 \sin \omega t$$

$$= i_D \text{ mA}$$

$$v_{DS} = V_{DSQ} + v_{ds} = 3.2 - 0.3 \sin \omega t = v_{DS}$$

E6.9

$$V_{SDQ} = 3 \text{ V and } I_{DQ} = 0.5 \text{ mA}$$

$$\Rightarrow R_D = \frac{5 - 3}{0.5} \Rightarrow R_D = 4 \text{ k}\Omega$$

$$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$$

$$0.5 = 1(V_{SG} - 1)^2 \Rightarrow V_{SG} = 1.71 \text{ V}$$

$$\Rightarrow V_{GG} = 5 - 1.71 \Rightarrow V_{GG} = 3.29 \text{ V}$$

$$A_v = -g_m R_D$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.5)}$$

$$g_m = 1.41 \text{ mA/V}$$

$$A_v = -(1.41)(4) \Rightarrow A_v = -5.64$$

$$A_v = \frac{v_o}{v_i} = \frac{-v_{sd}}{v_i} = -\frac{0.46 \sin \omega t}{v_i} = -5.64$$

$$\Rightarrow v_i = 0.0816 \sin \omega t$$

E6.10

$$a. \quad V_{SG} = 9 - I_{DQ} R_S, \quad I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$$

$$V_{SG} = 9 - (2)(1.2)(V_{SG} - 2)^2$$

$$= 9 - 2.4(V_{SG}^2 - 4V_{SG} + 4)$$

$$2.4V_{SG}^2 - 8.6V_{SG} + 0.6 = 0$$

$$V_{SG} = \frac{8.6 \pm \sqrt{(8.6)^2 - 4(2.4)(0.6)}}{2(2.4)}$$


$$V_{SG} = 3.51 \text{ V}, \quad I_{DQ} = 2(3.51 - 2)^2$$

$$\Rightarrow I_{DQ} = 4.56 \text{ mA}$$

$$V_{SDQ} = 9 + 9 - I_{DQ}(1.2 + 1) = 18 - (4.56)(2.2)$$

$$\Rightarrow V_{SDQ} = 7.97 \text{ V}$$

b.

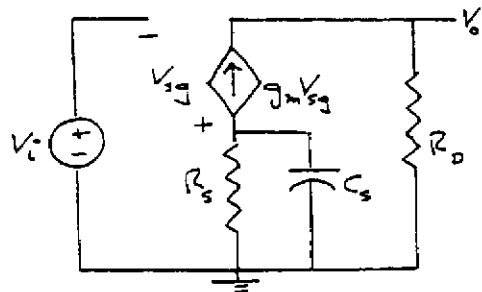

$$V_o = g_m V_{SG} R_D$$

$$A_v = -g_m R_D = -(6.04)(1) \Rightarrow A_v = -6.04$$

E6.11

$$I_{DQ} = I_Q = 0.5 \text{ mA}$$

$$\text{Let } \frac{W}{L} = 25$$

$$K_n = (20)(25) = 500 \mu\text{A/V}^2$$

$$V_{GS} = \sqrt{\frac{0.5}{0.5}} + 1.5 = 2.5 \text{ V} \Rightarrow V_S = -2.5 \text{ V}$$

$$A_v = -g_m R_D$$

$$g_m = 2(0.5)(2.5 - 1.5) = 1 \text{ mA/V}$$

$$\text{For } A_v = -4.0 \Rightarrow R_D = 4 \text{ k}\Omega$$

$$V_D = 5 - (0.5)(4) = 3 \text{ V}$$

$$\Rightarrow V_{DSQ} = 3 - (-2.5) = 5.5 \text{ V}$$

E6.12

$$a. \quad \text{With } R_G \Rightarrow V_{GS} = V_{DS} \Rightarrow \text{transistor biased in sat. region}$$

$$I_D = K_n (V_{GS} - V_{TN})^2 = K_n (V_{DS} - V_{TN})^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$= V_{DD} - K_n R_D (V_{DS} - V_{TN})^2$$

$$\begin{aligned}
 V_{DS} &= 15 - (0.15)(10)(V_{DS} - 1.8)^2 \\
 &= 15 - 1.5(V_{DS}^2 - 3.6V_{DS} + 3.24) \\
 1.5V_{DS}^2 - 4.4V_{DS} - 10.14 &= 0 \\
 V_{DS} &= \frac{4.4 \pm \sqrt{(4.4)^2 + (4)(1.5)(10.14)}}{2(1.5)} \\
 &\Rightarrow \underline{V_{DSQ} = 4.45 \text{ V}} \\
 I_{DQ} &= (0.15)(4.45 - 1.8)^2 \Rightarrow \underline{I_{DQ} = 1.05 \text{ mA}}
 \end{aligned}$$

b. Neglecting effect of R_G :

$$\begin{aligned}
 A_v &= -g_m(R_D \parallel R_L) \\
 g_m &= 2K_n(V_{GS} - V_{TN}) = 2(0.15)(4.45 - 1.8) \\
 &\Rightarrow g_m = 0.795 \text{ mA/V} \\
 A_v &= -(0.795)(10 \parallel 5) \Rightarrow \underline{A_v = -2.65}
 \end{aligned}$$


c. $R_G \Rightarrow$ establishes $V_{GS} = V_{DS} \Rightarrow$ essentially no effect on small-signal voltage gain.

E6.13

$$\begin{aligned}
 \text{a. } I_{DQ} &= K_n(V_{GS} - V_{TN})^2 \\
 I_{DQ} &= 0.8(2 - V_{SG})^2 = \frac{V_{SG}}{R_S} = \frac{V_{SG}}{4} \\
 3.2(4 - 4V_{SG} + V_{SG}^2) &= V_{SG} \\
 3.2V_{SG}^2 - 13.8V_{SG} + 12.8 &= 0 \\
 V_{SG} &= \frac{13.8 \pm \sqrt{(13.8)^2 - 4(3.2)(12.8)}}{2(3.2)} \\
 V_{SG} &= 1.35 \text{ V} \Rightarrow I_{DQ} = 0.8(2 - 1.35)^2 \\
 &\Rightarrow \underline{I_{DQ} = 0.338 \text{ mA}}
 \end{aligned}$$

$$\begin{aligned}
 \text{b. } V_{DSQ} &= V_{DD} - I_{DQ}(R_D + R_S) \\
 6 &= 10 - (0.338)(R_D + 4) \\
 R_D &= \frac{10 - (0.338)(4) - 6}{0.338} \Rightarrow \underline{R_D = 7.83 \text{ k}\Omega}
 \end{aligned}$$

c.

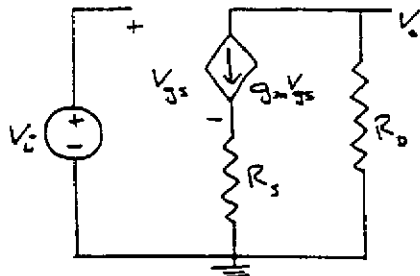


$$\begin{aligned}
 V_i &= V_{gs} + g_m V_{gs} R_S \Rightarrow V_{gs} = \frac{V_i}{1 + g_m R_S} \\
 V_o &= -g_m V_{gs} R_D \\
 g_m &= 2K_n(V_{GS} - V_{TN}) = 2(0.8)(-1.35 + 2) \\
 &= 1.04 \text{ mA/V} \\
 A_v &= \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-(1.04)(7.83)}{1 + (1.04)(4)} \\
 &\Rightarrow \underline{A_v = -1.58}
 \end{aligned}$$

E6.14

$$\begin{aligned}
 \text{a. } 5 &= I_{DQ} R_S + V_{SG} \text{ and } \\
 I_{DQ} &= K_p(V_{SG} + V_{TP})^2 \\
 0.8 &= 0.5(V_{SG} + 0.8)^2 \Rightarrow V_{SG} = 0.465 \text{ V} \\
 5 &= (0.8)R_S + 0.465 \Rightarrow \underline{R_S = 5.67 \text{ k}\Omega} \\
 V_{SDQ} &= 10 - I_{DQ}(R_S + R_D) \\
 3 &= 10 - (0.8)(5.67 + R_D) \\
 R_D &= \frac{10 - (0.8)(5.67) - 3}{0.8} \Rightarrow \underline{R_D = 3.08 \text{ k}\Omega}
 \end{aligned}$$


b.

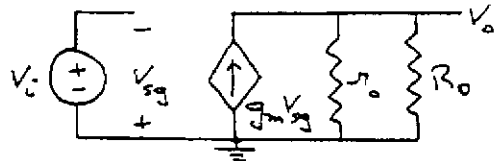

$$\begin{aligned}
 V_o &= g_m V_{gs}(R_D \parallel r_o) = -g_m V_i(R_D \parallel r_o) \\
 A_v &= \frac{V_o}{V_i} = -g_m(R_D \parallel r_o) \\
 g_m &= 2K_p(V_{SG} + V_{TP}) = 2(0.5)(0.465 + 0.8) \\
 &= 1.27 \text{ mA/V} \\
 r_o &= \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.8)} = 62.5 \text{ k}\Omega \\
 A_v &= -(1.27)(3.08 \parallel 62.5) \Rightarrow \underline{A_v = -3.73}
 \end{aligned}$$

E6.15
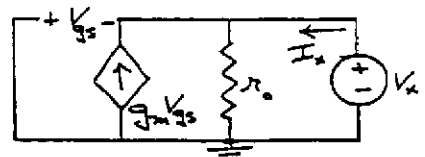
$$\begin{aligned}
 V_o &= g_m V_{gs} r_o \\
 V_i &= V_{gs} + V_o \Rightarrow V_{gs} = V_i - V_o \\
 \text{So } V_o &= g_m r_o (V_i - V_o) \\
 A_v &= \frac{V_o}{V_i} = \frac{g_m r_o}{1 + g_m r_o} = \frac{(4)(50)}{1 + (4)(50)} \\
 &\Rightarrow \underline{A_v = 0.995}
 \end{aligned}$$



$$I_x + g_m V_{gs} = \frac{V_x}{r_o} \text{ and } V_{gs} = -V_x$$

$$I_x = g_m V_x + \frac{V_x}{r_o} \Rightarrow R_o = r_o \parallel \frac{1}{g_m} = 50 \parallel \frac{1}{4}$$

$$\Rightarrow \underline{R_o \approx 0.25 \text{ k}\Omega}$$

$$\text{With } R_S = 4 \text{ k}\Omega \Rightarrow A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)}$$

$$r_o \parallel R_S = 50 \parallel 4 = 3.7 \text{ k}\Omega \Rightarrow A_v = \frac{(4)(3.7)}{1 + (4)(3.7)}$$

$$\Rightarrow \underline{A_v = 0.937}$$

E6.16

$$V_{DSQ} = V_{DD} - I_{DQ} R_S$$

$$5 = 10 - (1.5) R_S \Rightarrow \underline{R_S = 3.33 \text{ k}\Omega}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2 \Rightarrow 1.5 = (1)(V_{GS} - 0.8)^2$$

$$V_{GS} = 2.02 \text{ V} = V_G - V_S = V_G - 5$$

$$\Rightarrow V_G = 7.02 \text{ V} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{R_2}{400} \cdot 10$$

$$\text{So } \underline{R_2 = 280.8 \text{ k}\Omega}, \quad \underline{R_1 = 119.2 \text{ k}\Omega}$$

Neglecting R_{Si} ,

$$A_v = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$

$$r_o = [\lambda I_{DQ}]^{-1} = [(0.015)(1.5)]^{-1} = 44.4 \text{ k}\Omega$$

$$R_S \parallel r_o = 3.33 \parallel 44.4 = 3.1 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1)(1.5)} = 2.45 \text{ mA/V}$$

$$A_v = \frac{(2.45)(3.1)}{1 + (2.45)(3.1)} \Rightarrow \underline{A_v = 0.884}$$

$$R_o = \frac{1}{g_m} \parallel R_S \parallel r_o = \frac{1}{2.45} \parallel 3.33 \parallel 44.4$$

$$= 0.408 \parallel 3.1$$

$$\Rightarrow \underline{R_o = 0.36 \text{ k}\Omega}$$

E6.17

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{9.3}{70.7 + 9.3} \right) (5)$$

$$= 0.581 \text{ V}$$

$$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2 = K_p (V_S - V_G - |V_{TP}|)^2$$

$$= \frac{5 - V_S}{R_S}$$

$$\text{Then } (0.4)(5)(V_S - 0.581 - 0.8)^2 = 5 - V_S$$

$$2(V_S - 1.381)^2 = 5 - V_S$$

$$2(V_S^2 - 2.762V_S + 1.907) = 5 - V_S$$

$$2V_S^2 - 4.52V_S - 1.19 = 0$$

$$V_S = \frac{4.52 \pm \sqrt{(4.52)^2 + 4(2)(1.19)}}{2(2)}$$

$$V_S = 2.50 \text{ V} \Rightarrow I_{DQ} = \frac{5 - 2.5}{5} = 0.5 \text{ mA}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.4)(0.5)} = 0.894 \text{ mA/V}$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S}$$

$$= \frac{(0.894)(5)}{1 + (0.894)(5)} \cdot \frac{70.7 \parallel 9.3}{70.7 \parallel 9.3 + 0.5} \Rightarrow \underline{A_v = 0.770}$$

Neglecting R_{Si} , $A_v = 0.817$

$$R_o = R_S \parallel \frac{1}{g_m} = 5 \parallel \frac{1}{0.894} = 5 \parallel 1.12$$

$$\Rightarrow \underline{R_o = 0.915 \text{ k}\Omega}$$

E6.18

$$(a) \quad g_m = 2\sqrt{K_n I_{DQ}} \Rightarrow 2 = 2\sqrt{K_n(0.8)} \Rightarrow$$

$$K_n = 1.25 \text{ mA/V}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \Rightarrow 1.25 = (0.020) \left(\frac{W}{L} \right)$$

$$\text{So } \underline{\frac{W}{L} = 62.5}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2 \Rightarrow 0.8 = 1.25 (V_{GS} - 2)^2$$

$$\Rightarrow \underline{V_{GS} = 2.8 \text{ V}}$$

$$b. \quad r_o = [\lambda I_{DQ}]^{-1} = [(0.01)(0.8)]^{-1} = 125 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_L)}{1 + g_m(r_o \parallel R_L)}$$

$$r_o \parallel R_L = 125 \parallel 4 = 3.88$$

$$A_v = \frac{(2)(3.88)}{1 + (2)(3.88)} \Rightarrow \underline{A_v = 0.886}$$

$$R_o = \frac{1}{g_m} \parallel r_o = \frac{1}{2} \parallel 125 \Rightarrow \underline{R_o \approx 0.5 \text{ k}\Omega}$$

E6.19

$$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$$

$$3 = 2(V_{SG} - 2)^2 \Rightarrow V_{SG} = 3.22 \text{ V}$$

$$I_{DQ} = \frac{5 - V_{SG}}{R_S} \Rightarrow 3 = \frac{5 - 3.22}{R_S}$$

$$\Rightarrow \underline{R_S = 0.593 \text{ k}\Omega}$$

$$r_o = [\lambda I_{DQ}]^{-1} = [(0.02)(3)]^{-1} = 16.7 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(3)} = 4.9 \text{ mA/V}$$

$$\text{For } R_L = \infty, \quad A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)}$$

$$r_o \parallel R_S = 16.7 \parallel 0.593 = 0.573 \text{ k}\Omega$$

$$A_v = \frac{(4.9)(0.573)}{1 + (4.9)(0.573)} \Rightarrow \underline{A_v = 0.737}$$

If A_v is reduced by 10%

$$\Rightarrow A_v = 0.737 - 0.0737 = 0.663$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$\text{Let } r_o \parallel R_S \parallel R_L = r$$

$$0.563 = \frac{(4.9)r}{1 + (4.9)r} \Rightarrow 0.563 = 4.9r(1 - 0.563)$$

$$r = 0.402 = 0.573 \parallel R_L$$

$$\frac{0.573 R_L}{R_L + 0.573} = 0.402$$

$$\Rightarrow (0.573 - 0.402)R_L = (0.402)(0.573)$$

$$\Rightarrow R_L = 1.35 \text{ k}\Omega$$

E6.20

$$R_{in} = \frac{1}{g_m} = 0.35 \text{ k}\Omega \Rightarrow g_m = 2.86 \text{ mA/V}$$

$$\frac{V_o}{I_i} = R_D \parallel R_L = 2.4 = R_D \parallel 4 = \frac{4R_D}{4 + R_D}$$

$$(4 - 2.4)R_D = (2.4)(4) \Rightarrow R_D = 6 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$2.86 = 2\sqrt{K_n(0.5)} \Rightarrow K_n = 4.09 \text{ mA/V}^2$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$0.5 = 4.09(V_{GS} - 1)^2 \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$\Rightarrow V_S = -1.35 \text{ V}, \quad V_D = 5 - (0.5)(6) = 2 \text{ V}$$


$$V_{DS} = V_D - V_S = 2 - (-1.35) = 3.35 \text{ V}$$

We have

$$V_{DS} = 3.35 > V_{GS} - V_{TN} = 1.35 - 1 = 0.35 \text{ V}$$

\Rightarrow Biased in the saturation region

E6.21

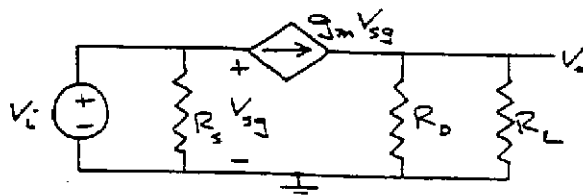

$$V_o = g_m V_{sg}(R_D \parallel R_L) \text{ and } V_{sg} = V_i$$

$$A_v = g_m(R_D \parallel R_L)$$

$$I_{DQ} = \frac{5 - V_{SG}}{R_S} = K_p(V_{SG} - |V_{TP}|)^2$$

$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2$$

$$5 - V_{SG} = 4[V_{SG}^2 - 1.6V_{SG} + 0.64]$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + (4)(4)(2.44)}}{2(4)}$$

$$V_{SG} = 1.71 \text{ V}$$

$$I_{DQ} = \frac{5 - 1.71}{4} = 0.822 \text{ mA}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.822)} = 1.81 \text{ mA/V}$$

$$A_v = (1.81)(2 \parallel 4) = (1.81)(1.33) \Rightarrow A_v = 2.41$$

$$R_{in} = R_S \parallel \frac{1}{g_m} = 4 \parallel \frac{1}{1.81} = 4 \parallel 0.552$$

$$\Rightarrow R_{in} = 0.485 \text{ k}\Omega$$

E6.22

$$K_{n1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_1 = (0.020)(80) = 1.6 \text{ mA/V}^2$$

$$K_{n2} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_2 = (0.020)(1) = 0.020 \text{ mA/V}^2$$

$$A_v = -\sqrt{\frac{K_{n1}}{K_{n2}}} = -\sqrt{\frac{1.6}{0.020}} \Rightarrow A_v = -8.94$$

The transition point is determined from

$$V_{GS1} - V_{TND} = V_{DD} - V_{TNL} - \sqrt{\frac{K_{n1}}{K_{n2}}}(V_{GS1} - V_{TND})$$

$$V_{GS1} - 0.8 = (5 - 0.8) - (8.94)(V_{GS1} - 0.8)$$

$$V_{GS1} = \frac{(5 - 0.8) + (8.94)(0.8) + 0.8}{1 + 8.94}$$

$$V_{GS1} = 1.22 \text{ V}$$

For Q-point in middle of saturation region

$$V_{GS} = \frac{1.22 - 0.8}{2} + 0.8 \Rightarrow V_{GS} = 1.01 \text{ V}$$

E6.23

$$K_{n2} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_2 = (0.015)(2) = 0.030 \text{ mA/V}^2$$

$$A_v = -\sqrt{\frac{K_{n1}}{K_{n2}}} = -6 \Rightarrow \frac{K_{n1}}{K_{n2}} = 36$$

$$K_{n1} = (36)(0.030) = 1.08 \text{ mA/V}^2$$

$$1.08 = (0.015) \left(\frac{W}{L} \right)_1 \Rightarrow \left(\frac{W}{L} \right)_1 = 72$$

The transition point is found from

$$V_{GS1} - 1 = (10 - 1) - (6)(V_{GS1} - 1)$$

$$V_{GS1} = \frac{10 - 1 + 6 + 1}{1 + 6} = 2.29 \text{ V}$$

For Q-point in middle of saturation region

$$V_{GS} = \frac{2.29 - 1}{2} + 1 \Rightarrow V_{GS} = 1.645 \text{ V}$$

E6.24

(a) Transition points:

$$\text{For } M_2: v_{os} = V_{DD} - |V_{TNL}| = 5 - 1.2 = 3.8 \text{ V}$$

For M_1 :

$$K_{n1}[(v_{os})^2(1 + \lambda v_{os})] = K_{n2}[(V_{TNL})^2(1 + \lambda_2[V_{DD} - v_{os}])]$$

$$250[v_{os}^2 + (0.01)v_{os}^3] = 25[(1.2)^2(1 + (0.01)(5) - (0.01)v_{os})]$$

$$10[v_{\alpha\alpha}^2 + (0.01)v_{\alpha\alpha}^3] = 1512 - 0.0144v_{\alpha\alpha}$$

$$(0.01)v_{\alpha\alpha}^3 + v_{\alpha\alpha}^2 + 0.00144v_{\alpha\alpha} - 0.512 = 0$$

which yields $v_{\alpha\alpha} \approx 0.388 \text{ V}$

Then middle of saturation region

$$v_{oQ} = \frac{3.3 - 0.388}{2} + 0.388 \Rightarrow V_{DSQ1} = 2.094 \text{ V}$$

$$K_{n1}[(V_{GS1} - V_{TND})^2(1 + \lambda_1 v_o)]$$

$$= K_{n2}[(V_{TNL})^2(1 + \lambda_2[V_{DD} - v_o])]$$

$$250[(V_{GS1} - 0.8)^2(1 + [0.01][2.094])]$$

$$= 25[(1.2)^2(1 + [0.01][5 - 2.094])]$$

$$10[(V_{GS1} - 0.8)^2(1.0209)] = 1.482$$

$$(V_{GS1} - 0.8)^2 = 0.145 \Rightarrow \underline{V_{GS1} = 1.18 \text{ V}}$$

$$b. \quad I_{DQ} = K_{n1}[(V_{GS1} - 0.8)^2(1 + (0.01)(2.094))]$$

$$I_{DQ} = (0.25)[(0.145)^2(1.02094)]$$

$$\Rightarrow \underline{I_{DQ} = 37.0 \mu\text{A}}$$

$$c. \quad A_v = \frac{-g_{m1}}{I_{DQ}(\lambda_1 + \lambda_2)} = -g_{m1}(r_{o1} \| r_{o2})$$

$$g_{m1} = 2K_{n1}(V_{GS1} - V_{TND})$$

$$= 2(0.25)(1.18 - 0.8) = 0.19 \text{ mA/V}$$

$$A_v = \frac{-0.19}{(0.037)(0.01 + 0.01)} \Rightarrow \underline{A_v = -257}$$

E6.25

$$R_o = R_{S2} \parallel \frac{1}{g_{m2}}$$

$$g_{m2} = 0.632 \text{ mA/V}, \quad R_{S2} = 8 \text{ k}\Omega$$

$$R_o = 8 \parallel \frac{1}{0.632} = 8 \parallel 1.58 \Rightarrow \underline{R_o = 1.32 \text{ k}\Omega}$$

E6.26

$$a. \quad I_{DQ2} = 2 \text{ mA}, \quad V_{SDQ2} = 10 \text{ V}$$

$$I_{DQ2} \cdot R_{S2} = 10 = 2R_{S2} \Rightarrow \underline{R_{S2} = 5 \text{ k}\Omega}$$

$$I_{DQ2} = K_{n2}(V_{GS2} - V_{TN2})^2$$

$$2 = 1(V_{GS2} - 2)^2 \Rightarrow V_{GS2} = 3.41 \text{ V}$$

$$\Rightarrow V_{G2} = 3.41 \text{ V}$$

$$\text{Then } R_{D1} = \frac{10 - 3.41}{2} \Rightarrow \underline{R_{D1} = 3.3 \text{ k}\Omega}$$

$$\text{For } V_{DSQ1} = 10 \text{ V} = V_{S1} = 3.41 - 10 = -6.59 \text{ V}$$

$$\text{Then } R_{S1} = \frac{-6.59 - (-10)}{2} \Rightarrow \underline{R_{S1} = 1.71 \text{ k}\Omega}$$

$$I_{D1} = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$2 = 1(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 3.41 \text{ V}$$

$$V_{GS1} = \left(\frac{R_2}{R_1 + R_2} \right) (20) - I_{DQ1} R_{S1}$$

$$\frac{R_2}{R_1 + R_2} = \frac{1}{R_1} \cdot R_{1n}$$

$$3.41 = \frac{1}{R_1} (200)(20) - (2)(1.71)$$

$$\Rightarrow \underline{R_1 = 586 \text{ k}\Omega}$$

$$\frac{586 R_2}{586 + R_2} = 200 \Rightarrow (586 - 200) R_2 = (200)(586)$$

$$\Rightarrow \underline{R_2 = 304 \text{ k}\Omega}$$

$$b. \quad g_{m1} = 2\sqrt{K_{n1} I_{DQ1}} = 2\sqrt{(1)(2)}$$

$$\Rightarrow g_{m1} = g_{m2} = 2.83 \text{ mA/V}$$

From Example 6-16

$$A_v = \frac{-g_{m1} g_{m2} R_{D1} (R_{S2} \parallel R_L)}{1 + g_{m2} (R_{S2} \parallel R_L)}$$

$$R_{S2} \parallel R_L = 5 \parallel 4 = 2.22 \text{ k}\Omega$$

$$A_v = \frac{-(2.83)(2.83)(3.3)(2.22)}{1 + (2.83)(2.22)}$$

$$\Rightarrow \underline{A_v = -8.06}$$

$$R_o = \frac{1}{g_{m2}} \parallel R_{S2} = \frac{1}{2.83} \parallel 5 = 0.353 \parallel 5$$

$$\Rightarrow \underline{R_o = 0.330 \text{ k}\Omega}$$

E6.27

$$a. \quad I_{DQ1} = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$1 = 1.2(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = V_{GS2} = 2.91 \text{ V}$$

$$R_S = 10 \text{ k}\Omega \Rightarrow V_{S1} = I_{DQ} R_S = 10$$

$$= (1)(10) - 10 = 0$$

$$V_{G1} = 2.91 = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) (10)$$

$$= \left(\frac{R_3}{500} \right) (10)$$

$$\Rightarrow \underline{R_3 = 145.5 \text{ k}\Omega}$$

$$V_{DSQ1} = 3.5 \Rightarrow V_{S2} = 3.5 \text{ V} \Rightarrow 3.5 + 2.91$$

$$\Rightarrow V_{G2} = 6.41$$

$$V_{G2} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (10) = 6.41$$

$$= \left(\frac{R_2 + R_3}{500} \right) (10)$$

$$R_2 + R_3 = 320.5 = R_2 + 145.5 \Rightarrow \underline{R_2 = 175 \text{ k}\Omega}$$

$$\text{Then } R_1 + R_2 + R_3 = 500 = R_1 + 175 + 145.5$$

$$\Rightarrow \underline{R_1 = 179.5 \text{ k}\Omega}$$

$$\text{Now } V_{S2} = 3.5 \Rightarrow V_{D2} = V_{S2} + V_{SDQ2}$$

$$= 3.5 + 3.5 = 7 \text{ V}$$

$$\text{So } R_D = \frac{10 - 7}{1} \Rightarrow \underline{R_D = 3 \text{ k}\Omega}$$

b. From Example 6-18:

$$A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_{n1} I_{DQ}} = 2\sqrt{(1.2)(1)} = 2.19 \text{ mA/V}$$

$$A_v = -(2.19)(3) \Rightarrow \underline{A_v = -6.57}$$

E6.28

From Example 6-18:

$$g_m = 2.98 \text{ mA/V}, \quad r_o = 42.1 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 420 \parallel 180 = 126 \text{ k}\Omega$$

$$\begin{aligned} V_{gs} &= \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \right) V_i \\ &= \left(\frac{126}{126 + 20} \right) V_i = 0.863 V_i \end{aligned}$$

$$\begin{aligned} A_v &= \frac{-g_m V_{gs} (r_o \parallel R_D \parallel R_L)}{V_i} \\ &= -(2.98)(0.863)(42.1 \parallel 2.7 \parallel 4) \\ &= -(2.57)(42.1 \parallel 1.61) = -(2.57)(1.55) \\ &\Rightarrow \underline{A_v = -3.98} \end{aligned}$$

E6.29

$$V_S = I_{DQ} R_S = (1.2)(2.7) = 3.24 \text{ V}$$

$$V_D = V_S + V_{DSQ} = 3.24 + 12 = 15.24$$

$$R_D = \frac{20 - 15.24}{1.2} \Rightarrow \underline{R_D = 3.97 \text{ k}\Omega}$$

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ 1.2 &= 4 \left(1 - \frac{V_{GS}}{V_P} \right)^2 \Rightarrow \frac{V_{GS}}{V_P} = 0.452 \end{aligned}$$

$$V_{GS} = (0.452)(-3) = -1.356$$

$$V_G = V_S + V_{GS} = 3.24 - 1.356 = 1.88 \text{ V}$$

$$\begin{aligned} V_G &= \left(\frac{R_2}{R_1 + R_2} \right) (20) = \left(\frac{R_2}{500} \right) (20) = 1.88 \\ &\Rightarrow \underline{R_2 = 47 \text{ k}\Omega}, \quad \underline{R_1 = 453 \text{ k}\Omega} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.005)(1.2)} = 167 \text{ k}\Omega \\ g_m &= \frac{2I_{DSS}}{(-V_P)} \left(1 - \frac{V_{GS}}{V_P} \right) = \frac{2(4)}{3} \left(1 - \frac{1.356}{3} \right) \\ &= 1.46 \text{ mA/V} \\ A_v &= -g_m (r_o \parallel R_D \parallel R_L) = -(1.46)(167 \parallel 3.97 \parallel 4) \\ &\Rightarrow \underline{A_v = -2.87} \end{aligned}$$

E6.30

$$\begin{aligned} \text{a. } V_{G1} &= \left(\frac{R_2}{R_1 + R_2} \right) (V_{DD}) \\ V_{G1} &= \left(\frac{430}{430 + 70} \right) (20) = 17.2 \text{ V} \end{aligned}$$

$$\begin{aligned} I_{DQ1} &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 6 \left(1 - \frac{V_{G1} - V_{S1}}{2} \right)^2 \\ &= 6 \left(1 - \frac{17.2}{2} + \frac{V_{S1}}{2} \right)^2 = 6 \left(\frac{V_{S1}}{2} - 7.6 \right)^2 \\ \text{and } I_{DQ1} &= \frac{20 - V_{S1}}{4} \end{aligned}$$

$$\text{Then } \frac{20 - V_{S1}}{4} = 6 \left(\frac{V_{S1}}{2} - 7.6 \right)^2$$

$$\begin{aligned} 20 - V_{S1} &= 24 \left(\frac{V_{S1}^2}{4} - 7.6 V_{S1} + 57.76 \right) \\ &= 6 V_{S1}^2 - 182.4 V_{S1} + 1386.24 \end{aligned}$$

$$6 V_{S1}^2 - 181.4 V_{S1} + 1366.24 = 0$$

$$V_{S1} = \frac{181.4 \pm \sqrt{(181.4)^2 - 4(6)(1366.24)}}{2(6)}$$

$$\begin{aligned} V_{S1} &= 14.2 \text{ V} \Rightarrow V_{GS1} = 17.2 - 14.2 \\ &= 3 \text{ V} > V_P \end{aligned}$$

$$\begin{aligned} \text{So } V_{S1} &= 16.0 \Rightarrow V_{GS1} = 17.2 - 16 \\ &= 1.2 < V_P - Q \end{aligned}$$

$$\text{on } I_{DQ1} = \frac{20 - 16}{4} \Rightarrow \underline{I_{DQ1} = 1 \text{ mA}}$$

$$\begin{aligned} V_{SDQ1} &= 20 - I_{DQ1}(R_{S1} + R_{D1}) \\ &= 20 - (1)(8) \\ &\Rightarrow \underline{V_{SDQ1} = 12 \text{ V}} \end{aligned}$$

$$V_{D1} = I_{DQ1} R_{D1} = (1)(4) = 4 \text{ V} = V_{GS2}$$

$$\begin{aligned} I_{DQ2} &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 6 \left(1 - \frac{V_{G2} - V_{S2}}{(-2)} \right)^2 \\ &= 6 \left(1 + \frac{4}{2} - \frac{V_{S2}}{2} \right)^2 = 6 \left(3 - \frac{V_{S2}}{2} \right)^2 \end{aligned}$$

$$\text{and } I_{DQ2} = \frac{V_{S2}}{R_{S2}} = \frac{V_{S2}}{4}$$

Then

$$\begin{aligned} \frac{V_{S2}}{4} &= 6 \left(3 - \frac{V_{S2}}{2} \right)^2 \\ V_{S2} &= 24 \left(9 - 3 V_{S2} + \frac{V_{S2}^2}{4} \right) \end{aligned}$$

$$6 V_{S2}^2 - 73 V_{S2} + 216 = 0$$

$$V_{S2} = \frac{73 \pm \sqrt{(73)^2 - 4(6)(216)}}{2(6)}$$

$$\Rightarrow V_{S2} = 7.09 \text{ V or } 5.08 \text{ V}$$


$$\text{For } V_{S2} = 5.08 \text{ V}$$

$$\Rightarrow V_{GS2} = 4 - 5.08 = -1.08 \text{ transistor biased ON}$$

$$I_{DQ2} = \frac{5.08}{4} \Rightarrow I_{DQ2} = 1.27 \text{ mA}$$

$$V_{DS2} = 20 - V_{S2} = 20 - 5.08 \Rightarrow V_{DS2} = 14.9 \text{ V}$$

b.

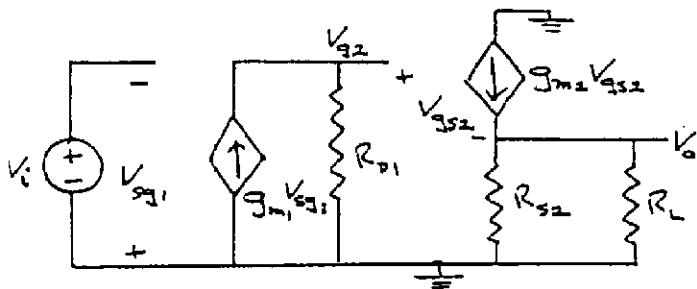

$$V_{g2} = g_{m1}V_{gs1}R_{D1} = -g_{m1}V_iR_{D1}$$

$$V_o = g_{m2}V_{gs2}(R_{S2} \parallel R_L)$$

$$V_{g2} = V_{gs2} + V_o \Rightarrow V_{gs2} = \frac{V_{g2}}{1 + g_{m2}(R_{S2} \parallel R_L)}$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_{m1}R_{D1}}{1 + g_{m2}(R_{S2} \parallel R_L)}$$


$$g_{m1} = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2(6)}{2} \left(1 - \frac{1.2}{2}\right) = 2.4 \text{ mA/V}$$

$$g_{m2} = \frac{2(5)}{2} \left(1 - \frac{1.08}{2}\right) = 2.76 \text{ mA/V}$$

$$\text{Then } A_v = \frac{-(2.4)(4)}{1 + (2.76)(4)(2)} = \underline{\underline{-2.05 = A_v}}$$

b.

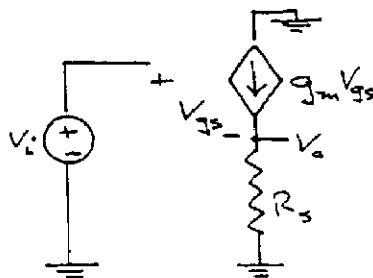

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(8)}{3.5} \left(1 - \frac{1.75}{3.5}\right) = 2.29 \text{ mA/V}$$

$$r_o = \frac{1}{(0.01)(2)} = 50 \text{ k}\Omega$$

$$V_i = V_{gs} + g_m R_S V_{gs} \Rightarrow V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S \parallel r_o}{1 + g_m R_S \parallel r_o} = \frac{(2.29)[5.88 \parallel 50]}{1 + (2.29)[5.88 \parallel 50]} \Rightarrow \underline{\underline{A_v = 0.923}}$$

$$c. \quad A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = 0.931 - 0.186 = 0.745$$

$$\frac{(2.29)(R_S \parallel R_L)}{1 + (2.29)(R_S \parallel R_L)} = 0.745$$

$$(2.29)(R_S \parallel R_L)(1 - 0.745) = 0.745$$

$$\Rightarrow R_S \parallel R_L = 1.28 \text{ k}\Omega$$

$$\frac{5.88 R_L}{5.88 + R_L} = 1.28$$

$$\Rightarrow (5.88 - 1.28)R_L = (1.28)(5.88)$$

$$\Rightarrow \underline{\underline{R_L = 1.54 \text{ k}\Omega}}$$

E6.31

$$a. \quad I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2 = 8 \left(1 - \frac{V_{GS}}{V_P}\right)^2 \Rightarrow \frac{V_{GS}}{V_P} = 0.5$$

$$V_{GS} = (0.5)(-3.5) \Rightarrow V_{GS} = -1.75$$

$$\text{Also } I_{DQ} = \frac{-V_{GS} - (-10)}{R_S}$$

$$2 = \frac{1.75 + 10}{R_S} \Rightarrow \underline{\underline{R_S = 5.88 \text{ k}\Omega}}$$

Chapter 6

Problem Solutions

6.1

$$(a) \quad g_m = 2\sqrt{K_n I_D} = 2\sqrt{\left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$0.5 = 2\sqrt{(0.020)\left(\frac{W}{L}\right)(0.5)} \Rightarrow \frac{W}{L} = 12.5$$

$$(b) \quad I_D = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{GS} - V_{TN})^2$$

$$0.5 = (0.02)(12.5)(V_{GS} - 0.8)^2$$

$$\Rightarrow \underline{V_{GS} = 2.21 \text{ V}}$$

6.2

$$(a) \quad g_m = 2\sqrt{K_p I_D} = 2\sqrt{\left(\frac{\mu_p C_{ox}}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$\left(\frac{50}{2}\right)^2 = (10)\left(\frac{W}{L}\right)(100) \Rightarrow \frac{W}{L} = 0.625$$

$$(b) \quad I_D = \left(\frac{\mu_p C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{SG} + V_{TP})^2$$

$$100 = (10)(0.625)(V_{SG} - 1.2)^2$$

$$\Rightarrow \underline{V_{SG} = 4.2 \text{ V}}$$

6.3

$$I_D = K_n(V_{GS} - V_{TN})^2(1 + \lambda V_{DS})$$

$$\frac{I_{D1}}{I_{D2}} = \frac{1 + \lambda V_{DS1}}{1 + \lambda V_{DS2}} \Rightarrow \frac{3.4}{3.0} = \frac{1 + \lambda(10)}{1 + \lambda(5)}$$

$$3.4[1 + 5\lambda] = 3.0[1 + 10\lambda]$$

$$3.4 - 3.0 = \lambda(3 \cdot 10 - (3.4) \cdot 5)$$

$$\Rightarrow \underline{\lambda = 0.0308}$$

$$r_o \approx \frac{1}{\lambda I_D} = \frac{1}{(0.0308)(3)} \Rightarrow \underline{r_o = 10.8 \text{ k}\Omega}$$

6.4

$$r_o = \frac{1}{\lambda I_D}$$

$$I_D = \frac{1}{\lambda r_o} = \frac{1}{(0.012)(100)} \Rightarrow \underline{I_D = 0.833 \text{ mA}}$$

6.5

$$A_v = -g_m(r_o \parallel R_D) = -(1)(50 \parallel 10)$$

$$\Rightarrow \underline{A_v = -8.33}$$

6.6

$$a. \quad R_D = \frac{V_{DD} - V_{DSQ}}{I_{DQ}} = \frac{10 - 6}{0.5} \Rightarrow \underline{R_D = 8 \text{ k}\Omega}$$

For $V_{GSQ} = 2 \text{ V}$, for example,

$$I_{DQ} = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{GSQ} - V_{TN})^2$$

$$0.5 = (0.030)\left(\frac{W}{L}\right)(2 - 0.8)^2$$

$$\Rightarrow \underline{\frac{W}{L} = 11.6}$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2K_n(V_{GSQ} - V_{TN})$$

$$g_m = 2(0.030)(11.6)(2 - 0.8)$$

$$\Rightarrow \underline{g_m = 0.835 \text{ mA/V}}$$

$$I_{DQ} = (0.030)(11.6)(2 - 0.8)^2 = 0.501 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(0.501)} \Rightarrow \underline{r_o = 133 \text{ k}\Omega}$$

$$c. \quad A_v = -g_m(r_o \parallel R_D) = -(0.835)(133 \parallel 8)$$

$$\Rightarrow \underline{A_v = -6.30}$$

6.7

$$K_n v_{gs}^2 = K_n [V_{gs} \sin \omega x]^2 = K_n V_{gs}^2 \sin^2 \omega x$$

$$\sin^2 \omega x = \frac{1}{2}[1 - \cos 2\omega x]$$

$$\text{So } K_n v_{gs}^2 = \frac{K_n V_{gs}^2}{2}[1 - \cos 2\omega x]$$

Ratio of signal at 2ω to that at ω :

$$\frac{\frac{K_n V_{gs}^2}{2} \cdot \cos 2\omega x}{2K_n(V_{GSQ} - V_{TN})V_{gs} \cdot \sin \omega x}$$

The coefficient of this expression is then:

$$\frac{V_{gs}}{4(V_{GSQ} - V_{TN})}$$

6.8

$$0.01 = \frac{V_{gs}}{4(V_{GSQ} - V_{TN})}$$

$$\text{So } V_{gs} = (0.01)(4)(3 - 1)$$

$$\Rightarrow \underline{V_{gs} = 0.08 \text{ V}}$$

6.9

$$V_o = -g_m V_{gs}(r_o \parallel R_D)$$

$$V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot V_i = \left(\frac{50}{50 + 2}\right) \cdot V_i = (0.962)V_i$$

$$A_v = -g_m(0.962)(r_o \parallel R_D) = -(1)(0.962)(50 \parallel 10) \Rightarrow$$

$$\underline{A_v = -8.02}$$

6.10

$$A_v = -g_m(r_o \parallel R_D)$$

$$-10 = -g_m(100 \parallel 5)$$

$$\Rightarrow \underline{g_m = 2.1 \text{ mA/V}}$$

6.11

$$\text{a. } V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$V_G = \left(\frac{200}{200 + 300} \right) (12) = 4.8 \text{ V}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$4.8 - V_{GS} = (1)(2)(V_{GS}^2 - 4V_{GS} + 4)$$

$$2V_{GS}^2 - 7V_{GS} + 3.2 = 0$$

$$V_{GS} = \frac{7 \pm \sqrt{(7)^2 - 4(2)(3.2)}}{2(2)} = 2.96 \text{ V}$$

$$I_D = (1)(2.96 - 2)^2 \Rightarrow \underline{I_D = 0.920 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 12 - (0.92)(3 + 2)$$

$$\Rightarrow \underline{V_{DS} = 7.4 \text{ V}}$$

$$\text{(b) } V_o = \frac{-g_m V_{gs} (R_D \parallel R_L)}{1 + g_m R_S}$$

$$\text{where } V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{si}} \cdot V_i = \frac{300 \parallel 200}{300 \parallel 200 + 2} \cdot V_i$$

$$= \frac{120}{120 + 2} \cdot V_i = (0.984) V_i$$


Then

$$A_v = \frac{-g_m (0.984) (R_D \parallel R_L)}{1 + g_m R_S}$$

$$g_m = 2(1)(2.96 - 2) = 1.92 \text{ mA/V}$$

$$\text{So } A_v = \frac{-(1.92)(0.984)(3 \parallel 3)}{1 + (1.92)(2)} \Rightarrow \underline{A_v = -0.586}$$

c.

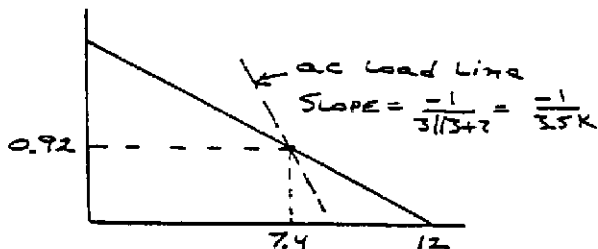

$$\Delta i_D = \frac{-1}{3.5 \text{ k}\Omega} \cdot \Delta v_{ds}$$

$$\Delta i_D = 0.92 \text{ mA}$$

$$\Rightarrow |\Delta v_{ds}| = (0.92)(3.5) = 3.22$$

$$\Rightarrow \underline{6.44 \text{ V peak-to-peak}}$$

6.12

$$\text{a. } I_{DQ} = 3 \text{ mA} \Rightarrow V_S = I_{DQ} R_S = (3)(0.5) = 1.5 \text{ V}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2$$

$$3 = (2)(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.22 \text{ V}$$

$$V_G = V_{GS} + V_S = 3.22 + 1.5 = 4.72 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$4.72 = \frac{1}{R_1} (200)(15) \Rightarrow \underline{R_1 = 636 \text{ k}\Omega}$$

$$\frac{636 R_2}{636 + R_2} = 200 \Rightarrow \underline{R_2 = 292 \text{ k}\Omega}$$

$$\text{b. } A_v = \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_S}$$

$$g_m = 2(2)(3.22 - 2) = 4.88 \text{ mA/V}$$

$$A_v = \frac{-(4.88)(2 \parallel 5)}{1 + (4.88)(0.5)} \Rightarrow \underline{A_v = -2.03}$$

6.13

From Problem 6-11: $I_D = 0.920 \text{ mA}$


$$V_{DS} = 7.4 \text{ V}$$

$$g_m = 1.92 \text{ mA/V}$$

$$A_v = -g_m (R_D \parallel R_L) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{si}} \right)$$

$$= -(1.92)(3 \parallel 3) \left(\frac{200 \parallel 300}{200 \parallel 300 + 2} \right) = -(2.88)(0.984)$$

$$\underline{A_v = -2.83}$$

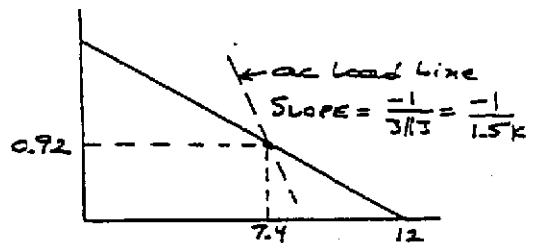


$$\Delta i_D = \frac{-1}{1.5 \text{ k}\Omega} \cdot \Delta v_{DS}, \quad \Delta i_D = 0.92 \text{ mA}$$

$$\Rightarrow |\Delta v_{DS}| = (0.92)(1.5) = 1.38$$

$$\Rightarrow \underline{2.76 \text{ V peak-to-peak output voltage swing}}$$

6.14

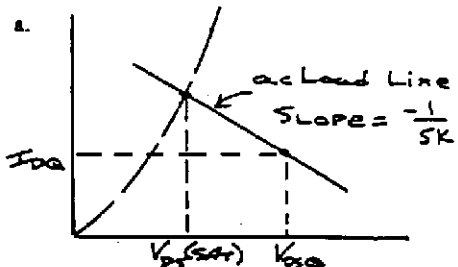

$$V_{DSQ} = V^+ - I_{DQ}R_D - (-V_{GSQ})$$

$$\text{Output Voltage Swing} = V_{DSQ} - V_{DS}(\text{sat})$$

$$= [V^+ - I_{DQ}R_D + V_{GSQ}] - (V_{GSQ} - V_{TN})$$

$$= V^+ - I_{DQ}R_D + V_{TN}$$

$$\text{So } |\Delta I_D| = I_{DQ} = \frac{1}{5 \text{ k}\Omega} |\Delta V_{DS}|$$

$$= \frac{1}{5 \text{ k}\Omega} [V^+ - I_{DQ}R_D + V_{TN}]$$

$$I_{DQ} = \frac{1}{5 \text{ k}\Omega} [5 - I_{DQ}(10) + 1]$$

$$= 1.2 - 2I_{DQ} = I_{DQ}$$

$$\Rightarrow I_{DQ} = 0.4 \text{ mA} = I_Q$$

$$\text{b. } g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.4)} = 0.894 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(0.4)} = 250 \text{ k}\Omega$$

$$A_v = -g_m(R_D \| R_L \| r_o)$$

$$= -(0.894)(10 \| 10 \| 250)$$

$$\Rightarrow A_v = -4.38$$

6.15

$$\text{a. } I_D = K_n(V_{GS} - V_{TN})^2$$

$$2 = 4(V_{GS} - (-1))^2$$

$$V_{GS} = -0.293 \text{ V}$$

$$\Rightarrow V_S = 0.293 \text{ V} = I_D R_S = (2)R_S$$

$$\Rightarrow R_S = 0.146 \text{ k}\Omega$$

$$V_D = V_{DS} + V_S = 6 + 0.293 = 6.293$$

$$R_D = \frac{10 - 6.293}{2} \Rightarrow R_D = 1.85 \text{ k}\Omega$$


$$\text{b. } A_v = \frac{-g_m(R_D \| R_L)}{1 + g_m R_S}$$

$$g_m = 2K_n(V_{GS} - V_{TN})$$

$$g_m = 2(4)(-0.293 + 1) = 5.66 \text{ mA/V}$$

$$A_v = \frac{-(5.66)(1.85 \| 2)}{1 + (5.66)(0.146)} \Rightarrow A_v = -2.98$$

c.

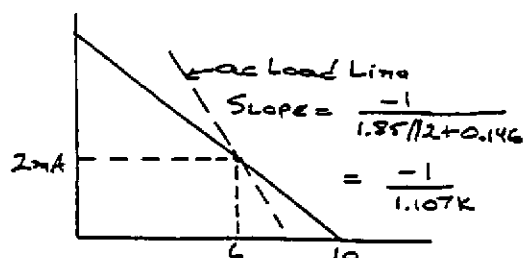

$$\Delta v_o = (\Delta i_D)(1.85 \| 2) = (2)(1.85 \| 2)$$

$$= 1.92 \text{ V}$$

$$\Delta v_i = \frac{1.92}{2.98} = 0.645 \Rightarrow V_i = 0.645 \text{ V}$$

6.16

$$\text{a. } V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S)$$

$$2.5 = 5 - I_{DQ}(2 + R_S)$$

$$I_{DQ} = \frac{2.5}{2 + R_S}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2 = \frac{-V_{GS}}{R_S}$$

$$\Rightarrow V_{GS} = -I_{DQ}R_S = \frac{-2.5R_S}{2 + R_S}$$

$$K_n \left[\frac{-2.5R_S}{2 + R_S} - V_{TN} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \left[1 - \frac{2.5R_S}{2 + R_S} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \left[\frac{2 + R_S - 2.5R_S}{2 + R_S} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \frac{(2 - 1.5R_S)^2}{2 + R_S} = 2.5$$

$$4(4 - 6R_S + 2.25R_S^2) = 2.5(2 + R_S)$$

$$9R_S^2 - 26.5R_S + 11 = 0$$

$$R_S = \frac{26.5 \pm \sqrt{(26.5)^2 - 4(9)(11)}}{2(9)}$$

$$R_S = 0.5 \text{ k}\Omega \text{ or } 2.44 \text{ k}\Omega$$

$$\text{But } R_S = 2.44 \text{ k}\Omega \Rightarrow V_{GS} = -1.37 \text{ Cut off.}$$

$$\Rightarrow R_S = 0.5 \text{ k}\Omega, I_{DQ} = 1.0 \text{ mA}$$

$$\text{b. } A_v = \frac{-g_m(R_D \| R_L)}{1 + g_m R_S}$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(1)} = 4 \text{ mA/V}$$

$$A_v = \frac{-(4)(2 \| 2)}{1 + (4)(0.5)} \Rightarrow A_v = -1.33$$

6.17

$$\text{a. } 5 = I_{DQ}R_S + V_{SDQ} + I_{DQ}R_D - 5$$

$$5 = I_{DQ}R_S + 6 + I_{DQ}(10) - 5$$

$$1. I_{DQ} = \frac{4}{R_S + 10}$$

$$V_S = V_{SDQ} + I_{DQ}R_D - 5 = V_{SGQ}$$

$$2. 1 + I_{DQ}(10) = V_{SGQ}$$

$$3. I_{DQ} = K_n(V_{SGQ} - 2)^2$$

Choose $R_S = 10 \text{ k}\Omega \Rightarrow I_{DQ} = \frac{4}{20} = 0.20 \text{ mA}$

$$V_{SGQ} = 1 + (0.2)(10) = 3 \text{ V}$$

$$0.20 = K_p(3 - 2)^2 \Rightarrow K_p = 0.20 \text{ mA/V}^2$$

b. $I_{DQ} = (0.20)(3 - 2)^2 = 0.20 \text{ mA}$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.2)(0.2)} = 0.4 \text{ mA/V}$$

$$A_v = -g_m(R_D \parallel R_L) = -(0.4)(10 \parallel 10)$$

$$\Rightarrow A_v = -2.0$$

c. Choose $R_S = 20 \text{ k}\Omega \Rightarrow I_{DQ} = \frac{4}{30} = 0.133 \text{ mA}$

$$V_{SGQ} = 1 + (0.133)(10) = 2.33 \text{ V}$$

$$0.133 = K_p(2.33 - 2)^2 \Rightarrow K_p = 1.22 \text{ mA/V}^2$$

$$g_m = 2\sqrt{(1.22)(0.133)} = 0.806 \text{ mA/V}$$

$$A_v = -(0.806)(10 \parallel 10) \Rightarrow A_v = -4.03$$

A larger gain can be achieved.

6.18

a. $I_{DQ} = 1 = K_p(V_{SGQ} + V_{TP})^2$

$$1 = 5(V_{SGQ} - 1.5)^2 \Rightarrow V_{SGQ} = 1.95 \text{ V}$$

$$R_S = \frac{5 - 1.95}{1} \Rightarrow R_S = 3.05 \text{ k}\Omega$$

$$V_{SDQ} = 10 - I_{DQ}(R_S + R_D)$$


$$5 = 10 - (1)(3.05 + R_D) \Rightarrow R_D = 1.95 \text{ k}\Omega$$

b. $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(5)(1)} = 4.47 \text{ mA/V}$

$$A_v = -g_m(R_D \parallel R_L) = -(4.47)(1.95 \parallel 2)$$

$$\Rightarrow A_v = -4.41$$

c.

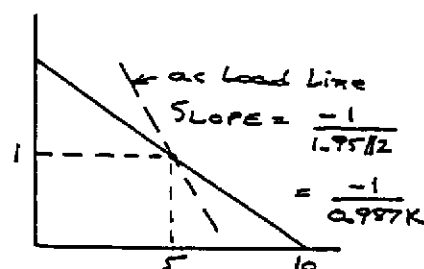

$$\Delta i_D = -\frac{1}{0.987 \text{ k}\Omega} \cdot \Delta v_{DS}$$

$$\Rightarrow |\Delta v_{DS}| = (1)(0.987) = 0.987 \text{ V}$$

Swing in output voltage = 1.97 V peak-to-peak

6.19

$$I_{DQ} = K_n(V_{GSQ} - V_{TN})^2$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$2.2 = 2\sqrt{K_n(6)} \Rightarrow K_n = 0.202 \text{ mA/V}^2$$

$$6 = 0.202(2.8 - V_{TN})^2 \Rightarrow V_{TN} = -2.65 \text{ V}$$

$$V_{DSQ} = 18 - I_{DQ}(R_S + R_D)$$

$$R_S + R_D = \frac{18 - 10}{6} = 1.33 \text{ k}\Omega \Rightarrow R_S = 1.33 - R_D$$

$$A_v = -\frac{g_m(R_D \parallel R_L)}{1 + g_m R_S}$$

$$-1 = \frac{-2.2 \left(\frac{R_D \cdot 1}{R_D + 1} \right)}{1 + (2.2)(1.33 - R_D)}$$

$$1 + 2.93 - 2.2R_D = \frac{2.2R_D}{1 + R_D}$$

$$(3.93 - 2.2R_D)(1 + R_D) = 2.2R_D$$

$$3.93 + 1.73R_D - 2.2R_D^2 = 2.2R_D$$

$$2.2R_D^2 + 0.47R_D - 3.93 = 0$$

$$R_D = \frac{-0.47 + \sqrt{(0.47)^2 + 4(2.2)(3.93)}}{2(2.2)}$$

$$\Rightarrow R_D = 1.23 \text{ k}\Omega, R_S = 0.10 \text{ k}\Omega$$


$$V_G = V_{GS} + V_S = 2.8 + (6)(0.1) = 3.4 \text{ V}$$

$$V_G = \frac{1}{R_1} \cdot R_n \cdot V_{DD} = \frac{1}{R_1}(100)(18) = 3.4$$

$$\Rightarrow R_1 = 529 \text{ k}\Omega$$

$$\frac{529 R_2}{529 + R_2} = 100 \Rightarrow R_2 = 123 \text{ k}\Omega$$

6.20

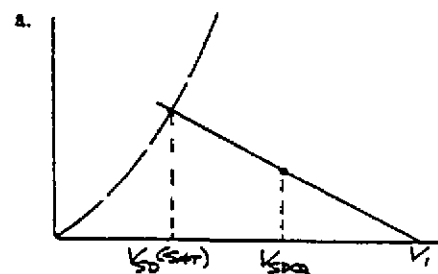

$$V_1 = 9 + V_{SG}, V_{SD}(\text{sat}) = V_{SG} + V_{TP}$$

$$V_{SDQ} = \frac{V_1 - V_{SD}(\text{sat})}{2} + V_{SD}(\text{sat})$$

$$= \frac{(9 + V_{SG}) - (V_{SG} + V_{TP})}{2} + (V_{SG} + V_{TP})$$

$$= \frac{9 + 1.5}{2} + V_{SG} - 1.5$$

$$V_{SDQ} = 3.75 + V_{SG} = 9 + V_{SG} - I_{DQ} R_D$$

$$I_{DQ} = K_p(V_{SG} + V_{TP})^2$$

Set $R_D = 0.1 R_L = 2 \text{ k}\Omega$

$3.75 = 9 - I_{DQ}(2) \Rightarrow I_{DQ} = 2.625 \text{ mA}$

b. $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(2.625)} = 4.58 \text{ mA/V}$

$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(2.625)} = 38.1 \text{ k}\Omega$

Open circuit.

$A_v = -g_m(R_D \parallel r_o)$

$A_v = -4.58(2 \parallel 38.1) \Rightarrow A_v = -8.70$

c. With R_L

$A_v = -4.58(2 \parallel 20 \parallel 38.1) \Rightarrow A_v = -7.95$

$\Rightarrow \text{Change} = 8.62\%$

6.21

a. $I_{DQ} = K_p(V_{SG} + V_{TP})^2$

$2 = (0.5)(V_{SG} + 2)^2 \Rightarrow V_{SG} = 0 \text{ V}$

$R_S = \frac{10 - 0}{2} \Rightarrow R_S = 5 \text{ k}\Omega$

$V_D = 0 - V_{SDQ} = 0 - 6 \Rightarrow R_D = \frac{-6 - (-10)}{2}$

$\Rightarrow R_D = 2 \text{ k}\Omega$

$A_v = -g_m R_D$

b. $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.5)(2)} = 2 \text{ mA/V}$

$A_v = -(2)(2) \Rightarrow A_v = -4.0$

6.22

$A_v = -g_m(R_D \parallel R_L)$

$V_{DSQ} = V_{DD} - I_{DQ}(R_S + R_D)$

$10 = 20 - (1)(R_S + R_D) \Rightarrow R_S + R_D = 10 \text{ k}\Omega$

Let $R_D = 8 \text{ k}\Omega$. $R_S = 2 \text{ k}\Omega$

$A_v = -10 = -g_m(8 \parallel 20)$

$g_m = 1.75 \text{ mA/V} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{K_n(1)} \Rightarrow$

$K_n = 0.766 \text{ mA/V}^2$

$V_S = I_{DQ} R_S = (1)(2) = 2 \text{ V}$

$I_{DQ} = K_n(V_{GS} - V_{TN})^2 \Rightarrow 1 = 0.766(V_{GS} - 2)^2$

$\Rightarrow V_{GS} = 3.31 \text{ V}$

$V_G = V_{GS} + V_S = 3.31 + 2 = 5.31$

$V_G = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$

$\Rightarrow \frac{1}{R_1}(200)(20) = 5.31 \Rightarrow R_1 = 753 \text{ k}\Omega$

$\frac{753 R_2}{753 + R_2} = 200 \Rightarrow R_2 = 272 \text{ k}\Omega$

6.23

$A_v = \frac{g_m r_o}{1 + g_m r_o} = \frac{(4)(50)}{1 + (4)(50)} \Rightarrow A_v = 0.995$

$R_0 = \frac{1}{g_m} \parallel r_o = \frac{1}{4} \parallel 50 \Rightarrow R_0 = 0.249 \text{ k}\Omega$

$A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)} = \frac{4(50 \parallel 2.5)}{1 + 4(50 \parallel 2.5)}$

$= \frac{4(2.38)}{1 + 4(2.38)} \Rightarrow A_v = 0.905$

$R_0 = \frac{1}{g_m} \parallel r_o \parallel R_S = \frac{1}{4} \parallel 50 \parallel 2.5$

$\Rightarrow R_0 = 0.226 \text{ k}\Omega$

6.24

a. $V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \left(\frac{396}{396 + 1240}\right)(10)$

$\Rightarrow V_G = 2.42 \text{ V}$

$I_{DQ} = \frac{10 - (V_{SG} + 2.42)}{R_S} = K_p(V_{SG} + V_{TP})^2$

$7.58 - V_{SG} = (2)(4)(V_{SG}^2 - 4V_{SG} + 4)$

$8V_{SG}^2 - 31V_{SG} + 24.4 = 0$

$V_{SG} = \frac{31 \pm \sqrt{(31)^2 - 4(8)(24.4)}}{2(8)}$

$\Rightarrow V_{SG} = 2.78 \text{ V}$

$I_{DQ} = (2)(2.78 - 2)^2 \Rightarrow I_{DQ} = 1.21 \text{ mA}$

$V_{SDQ} = 10 - I_{DQ} R_S = 10 - (1.21)(4)$


$\Rightarrow V_{SDQ} = 5.16 \text{ V}$

b. $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(1.21)} = 3.11 \text{ mA/V}$

$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(1.21)} = 41.3 \text{ k}\Omega$

$A_v = \frac{g_m(R_S \parallel R_L \parallel r_o)}{1 + g_m(R_S \parallel R_L \parallel r_o)}$

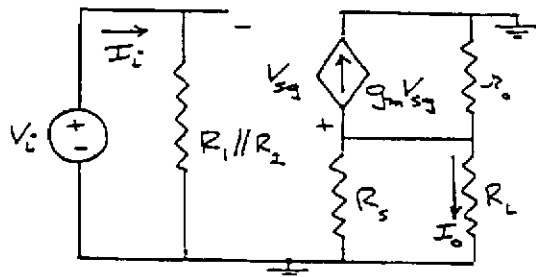$= \frac{3.11(4 \parallel 4 \parallel 41.3)}{1 + (3.11)(4 \parallel 4 \parallel 41.3)} \Rightarrow A_v = 0.886$



$I_o = -(g_m V_{gs}) \left(\frac{R_S \parallel r_o}{R_S \parallel r_o + R_L} \right)$

$V_{gs} = \frac{-V_i}{1 + g_m(R_S \parallel R_L \parallel r_o)}$

$V_i = I_i(R_1 \parallel R_2)$

$$A_i = \frac{I_o}{I_i} = \frac{g_m(R_1 \parallel R_2)}{1 + g_m(R_S \parallel R_L \parallel r_o)} \cdot \frac{R_S \parallel r_o}{R_S \parallel r_o + R_L}$$

$$= \frac{(3.11)(396 \parallel 1240)}{1 + (3.11)(4 \parallel 4 \parallel 41.3)} \cdot \frac{4 \parallel 41.3}{4 \parallel 41.3 + 4}$$

$$= \frac{(3.11)(300)}{1 + (3.11)(1.908)} \cdot \frac{3.647}{3.647 + 4}$$

$$\Rightarrow A_v = 64.2$$

$$R_o = \frac{1}{g_m} \parallel R_S \parallel R_L \parallel r_o = \frac{1}{3.11} \parallel 4 \parallel 4 \parallel 41.3$$

$$\Rightarrow R_o = 0.275 \text{ k}\Omega$$

6.25

$$g_m = 2\sqrt{K_n I_Q} = 2\sqrt{(1)(1)} = 2 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(1)} = 100 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_L)}{1 + g_m(r_o \parallel R_L)} = \frac{2(100 \parallel 4)}{1 + 2(100 \parallel 4)}$$

$$\Rightarrow A_v = 0.885$$

$$R_o = \frac{1}{g_m} \parallel r_o = \frac{1}{2} \parallel 100 \Rightarrow R_o = 0.490 \text{ k}\Omega$$

6.26

$$a. \quad A_v = \frac{g_m R_L}{1 + g_m R_L} \Rightarrow 0.95 = \frac{g_m(4)}{1 + g_m(4)}$$

$$0.95 = 4(1 - 0.95)g_m \Rightarrow g_m = 4.75 \text{ mA/V}$$

$$g_m = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_Q}$$

$$4.75 = 2\sqrt{(0.030)\left(\frac{W}{L}\right)(4)} \Rightarrow \frac{W}{L} = 47.0$$

$$b. \quad g_m = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_Q}$$

$$4.75 = 2\sqrt{(0.030)(60)I_Q} \Rightarrow I_Q = 3.13 \text{ mA}$$

6.27

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$5 = 5(V_{GS} + 2)^2 \Rightarrow V_{GS} = -1 \text{ V}$$

$$\Rightarrow V_S = -V_{GS} = 1 \text{ V}$$

$$I_{DQ} = \frac{V_S - (-5)}{R_S} \Rightarrow R_S = \frac{1 + 5}{5} \Rightarrow R_S = 1.2 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(5)(5)} = 10 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(5)} = 20 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$= \frac{(10)(20 \parallel 1.2 \parallel 2)}{1 + (10)(20 \parallel 1.2 \parallel 2)} \Rightarrow A_v = 0.878$$

$$R_o = \frac{1}{g_m} \parallel r_o \parallel R_S = \frac{1}{10} \parallel 20 \parallel 1.2$$

$$\Rightarrow R_o = 91.9 \Omega$$

6.28

$$A_v = \frac{g_m R_S}{1 + g_m R_S} \Rightarrow 0.90 = \frac{g_m(10)}{1 + g_m(10)}$$

$$0.90 = 10(1 - 0.90)g_m \Rightarrow g_m = 0.90 \text{ mA/V}$$

$$R_o = \frac{1}{g_m} \parallel R_S = \frac{1}{0.90} \parallel 10 \Rightarrow R_o = 1 \text{ k}\Omega$$

With R_L :

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{(0.90)(10 \parallel 2)}{1 + (0.90)(10 \parallel 2)}$$

$$\Rightarrow A_v = 0.60$$

6.29

$$R_o = \frac{1}{g_m} \parallel R_S$$

Output resistance determined primarily by g_m

$$\text{Set } \frac{1}{g_m} = 0.2 \text{ k}\Omega \Rightarrow g_m = 5 \text{ mA/V}$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$\Rightarrow 5 = 2\sqrt{(4)I_{DQ}} \Rightarrow I_{DQ} = 1.56 \text{ mA}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$1.56 = 4(V_{GS} + 2)^2$$

$$V_{GS} = -1.38 \text{ V}, \quad V_S = -V_{GS} = 1.38 \text{ V}$$

$$R_S = \frac{1.38 - (-5)}{1.56} \Rightarrow R_S = 4.09 \text{ k}\Omega$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{5(4.09 \parallel 2)}{1 + 5(4.09 \parallel 2)}$$

$$\Rightarrow A_v = 0.870$$

6.30

$$a. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(5)(5)} = 10 \text{ mA/V}$$

$$R_o = \frac{1}{g_m} = \frac{1}{10} \Rightarrow R_o = 100 \Omega$$

b. Open-circuit gain

$$A_v = \frac{g_m r_o}{1 + g_m r_o} \quad \text{But } r_o = \infty \text{ so } A_v = 1.0$$

With R_L :

$$A_v = \frac{g_m R_L}{1 + g_m R_L}$$

$$0.50 = \frac{10 R_L}{1 + 10 R_L} \Rightarrow 0.50 = 10(1 - 0.5)R_L$$

$$\Rightarrow R_L = 0.1 \text{ k}\Omega$$

6.31

$$|\Delta i_D| = I_{DQ} = \frac{-1}{R_S \parallel R_L} \cdot \Delta v_o$$

$$\Delta v_o = -I_{DQ} \cdot R_S \parallel R_L = -\frac{I_{DQ} \cdot R_S R_L}{R_S + R_L}$$

$$v_o(\min) = -\frac{I_{DQ} R_S}{1 + \frac{R_S}{R_L}}$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{v_o}{v_i}$$

$$v_i = \frac{-I_{DQ}(R_S \parallel R_L)[1 + g_m(R_S \parallel R_L)]}{g_m(R_S \parallel R_L)}$$

$$v_i(\min) = -\frac{I_{DQ}}{g_m}[1 + g_m(R_S \parallel R_L)]$$

6.32

$$a. \quad V_{DSQ} = V_{DD} - I_{DQ} R_S$$

$$3 = 5 - (1.7) R_S \Rightarrow R_S = 1.18 \text{ k}\Omega$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$1.7 = (1)(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.30 \text{ V}$$

$$V_S = V_{DD} - V_{DSQ} = 5 - 3 = 2 \text{ V}$$

$$V_G = V_S + V_{GS} = 2 + 2.30 = 4.30 \text{ V}$$

$$V_G = \frac{1}{R_1} \cdot R_1 \cdot V_{DD} = \frac{1}{R_1}(300)(5) = 4.30$$

$$\Rightarrow R_1 = 349 \text{ k}\Omega$$

$$\frac{349 R_2}{349 + R_2} = 300 \Rightarrow R_2 = 2.14 \text{ M}\Omega$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1)(1.7)} = 2.61 \text{ mA/V}$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} = \frac{2.61(1.18)}{1 + (2.61)(1.18)}$$

$$\Rightarrow A_v = 0.755$$

$$R_0 = \frac{1}{g_m} \parallel R_S = \frac{1}{2.61} \parallel 1.18 = 0.383 \parallel 1.18$$

$$\Rightarrow R_0 = 0.289 \text{ k}\Omega$$

6.33

$$a. \quad V_{GS} + I_{DQ} R_S = 5$$

$$I_{DQ} = \frac{5 - V_{GS}}{R_S} = K_n(V_{GS} - V_{TN})^2$$

$$5 - V_{GS} = (10)(3)(V_{GS}^2 - 2V_{GS} + 1)$$

$$30V_{GS}^2 - 59V_{GS} + 25 = 0$$

$$V_{GS} = \frac{59 \pm \sqrt{(59)^2 - 4(30)(25)}}{2(30)} \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$I_{DQ} = (3)(1.35 - 1)^2 \Rightarrow I_{DQ} = 0.365 \text{ mA}$$

$$V_{DSQ} = 10 - (0.365)(5 + 10) \Rightarrow V_{DSQ} = 4.53 \text{ V}$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(3)(0.365)} \Rightarrow$$

$$g_m = 2.09 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0)(0.365)} \Rightarrow r_o = \infty$$

$$c. \quad A_v = g_m(R_D \parallel R_L) = (2.09)(5 \parallel 4)$$

$$\Rightarrow A_v = 4.64$$

6.34

$$a. \quad I_{DQ} = K_p(V_{SG} + V_{TP})^2$$

$$0.75 = (0.5)(V_{SG} - 1)^2 \Rightarrow V_{SG} = 2.22 \text{ V}$$

$$5 = I_{DQ} R_S + V_{SG} \Rightarrow R_S = \frac{5 - 2.22}{0.75}$$

$$\Rightarrow R_S = 3.71 \text{ k}\Omega$$

$$V_{SDQ} = 10 - I_{DQ}(R_S + R_D)$$

$$6 = 10 - (0.75)(3.71 + R_D) \Rightarrow R_D = 1.62 \text{ k}\Omega$$

$$b. \quad R_i = \frac{1}{g_m}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.5)(0.75)} = 1.22 \text{ mA/V}$$

$$R_i = \frac{1}{1.22} \Rightarrow R_i = 0.816 \text{ k}\Omega$$

$$R_0 = R_D \Rightarrow R_0 = 1.62 \text{ k}\Omega$$

$$c. \quad i_o = \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{R_S}{R_S + [1/g_m]} \right) \cdot i_i$$

$$i_o = \left(\frac{1.62}{1.62 + 2} \right) \left(\frac{3.71}{3.71 + 0.816} \right) i_i$$

$$i_o = 0.367 i_i \Rightarrow i_o = 1.84 \sin \omega t \text{ (}\mu\text{A)}$$

$$v_o = i_o R_L = (1.84)(2) \sin \omega t$$

$$\Rightarrow v_o = 3.68 \sin \omega t \text{ (mV)}$$

6.35

$$a. \quad I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$5 = 4(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.12 \text{ V}$$

$$V^+ = I_{DQ} R_D + V_{DSQ} - V_{GS}$$

$$10 = (5)R_D + 12 - 3.12 \Rightarrow R_D = 0.224 \text{ k}\Omega$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(5)} \Rightarrow g_m = 8.94 \text{ mA/V}$$

$$R_i = \frac{1}{g_m} = \frac{1}{8.94} \Rightarrow R_i = 0.112 \text{ k}\Omega$$

$$c. \quad A_v = g_m(R_D \parallel R_L) = (8.94)(0.224 \parallel 2)$$

$$\Rightarrow A_v = 1.80$$

6.36


$$\begin{aligned}
 \text{a. } I_{DQ} &= K_p (V_{SG} + V_{TP})^2 \\
 3 &= 2(V_{SG} - 2)^2 \Rightarrow V_{SG} = 3.22 \text{ V} \\
 V^+ &= I_{DQ} R_S + V_{SG} \\
 R_S &= \frac{10 - 3.22}{3} \Rightarrow R_S = 2.26 \text{ k}\Omega \\
 V_{SDQ} &= 20 - I_{DQ}(R_S + R_D) \\
 10 &= 20 - (3)(2.26 + R_D) \Rightarrow R_D = 1.07 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{b. } A_v &= g_m (R_D \parallel R_L) \\
 g_m &= 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(3)} = 4.90 \text{ mA/V} \\
 A_v &= (4.90)(1.07 \parallel 10) \Rightarrow A_v = 4.74
 \end{aligned}$$

6.37

$$\begin{aligned}
 \text{a. } |A_v| &= \sqrt{\frac{(W/L)_D}{(W/L)_L}} = 5 \\
 \Rightarrow (W/L)_D &= 25(0.5) \Rightarrow (W/L)_D = 12.5 \\
 K_D &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_D = (30)(12.5) = 375 \mu\text{A/V}^2 \\
 K_L &= (30)(0.5) = 15 \mu\text{A/V}^2 \\
 \text{Transition point:}
 \end{aligned}$$
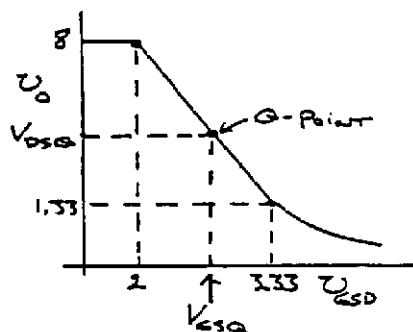
$$\begin{aligned}
 V_{GSD} - V_{TND} &= (V_{DD} - V_{TNL}) - \sqrt{\frac{K_D}{K_L}} (V_{GSD} - V_{TND}) \\
 V_{GSD} - 2 &= (10 - 2) - \sqrt{\frac{375}{15}} (V_{GSD} - 2) \\
 V_{GSD}(1 + 5) &= (10 - 2) + 2 + 5(2) \\
 V_{GSD} &= 3.33 \text{ V and } V_{DSQ} = 1.33 \text{ V}
 \end{aligned}$$



$$V_{GSQ} = \frac{3.33 - 2}{2} + 2 \Rightarrow V_{GSQ} = 2.67 \text{ V}$$

$$\begin{aligned}
 \text{b. } I_{DQ} &= K_D (V_{GSQ} - V_{TND})^2 \\
 I_{DQ} &= 0.375(2.67 - 2)^2 \Rightarrow I_{DQ} = 0.167 \text{ mA} \\
 V_{DSQ} &= \frac{8 - 1.33}{2} + 1.33 \Rightarrow V_{DSQ} = 4.67 \text{ V}
 \end{aligned}$$

6.38

$$\begin{aligned}
 \text{(a) Transition point: Load:} \\
 v_{oB} &= V_{DD} - |V_{TNL}| = 10 - 2 = 8 \text{ V} \\
 \text{Driver:} \\
 K_D [v_{oA}]^2 (1 + \lambda_D v_{oA}) &= K_L [(-V_{TNL})^2 (1 + \lambda_L (V_{DD} - v_{oA}))] \\
 0.5 [v_{oA}^2 + (0.02)v_{oA}^3] &= 0.1 [(4)(1 + 0.02(10 - v_{oA}))]
 \end{aligned}$$

We have

$$0.01 v_{oA}^3 + 0.5 v_{oA}^2 + 0.008 v_{oA} - 0.48 = 0$$

Therefore $v_{oA} = 0.963 \text{ V}$

Now

$$v_{oQ} = \frac{8 - 0.963}{2} + 0.963 = 4.48 \text{ V} = V_{DSQ}$$

Then

$$\begin{aligned}
 K_D [(V_{GSD} - V_{TND})^2 (1 + \lambda_D v_{oQ})] &= K_L [(-V_{TNL})^2 (1 + \lambda_L (V_{DD} - v_{oQ}))] \\
 0.5 [(V_{GSD} - 1.2)^2 (1 + (0.02)(4.48))] &= 0.1 [(4)(1 + 0.02(10 - 4.48))]
 \end{aligned}$$

which yields $V_{GSD} = 2.103 \text{ V}$

$$\begin{aligned}
 \text{b. } I_{DQ} &= K_D (V_{GSD} - V_{TND})^2 (1 + \lambda_D v_{oQ}) \\
 I_{DQ} &= 0.5 [(2.103 - 1.2)^2 (1 + (0.02)(4.48))] \\
 \text{So } I_{DQ} &= 0.444 \text{ mA}
 \end{aligned}$$

$$\text{c. } r_{oD} = r_{oL} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(0.444)} = 113 \text{ k}\Omega$$

$$\begin{aligned}
 g_{mD} &= 2K_D (V_{GSD} - V_{TND}) = 2(0.5)(2.103 - 1.2) \Rightarrow \\
 g_{mD} &= 0.903 \text{ mA/V}
 \end{aligned}$$

Then

$$\begin{aligned}
 A_v &= -g_{mD} (r_{oD} \parallel r_{oL}) = -(0.903)(113 \parallel 113) \\
 \text{or } A_v &= -51.0
 \end{aligned}$$

6.39

$$\begin{aligned}
 I_D &= K_n(V_{GS} - V_{TN})^2, \quad V_{DS} = V_{GS} \\
 I_D &= 0 \quad \text{when} \quad V_{DS} = 1.5 \text{ V} \Rightarrow V_{TN} = 1.5 \text{ V} \\
 0.8 &= K_n(3 - 1.5)^2 \Rightarrow K_n = 0.356 \text{ mA/V}^2 \\
 g_m &= \frac{dI_D}{dV_{DS}} = \frac{1}{R_o} = 2K_n(V_{DS} - V_{TN}) \\
 &= 2(0.356)(3 - 1.5) \\
 \Rightarrow R_o &= 0.936 \text{ k}\Omega
 \end{aligned}$$

6.40

a.

$$\begin{aligned}
 I_{DQ} &= K_{nD}(V_{GS} - V_{TND})^2 = (0.5)(0 - (-1))^2 \\
 I_{DQ} &= 0.5 \text{ mA} \\
 I_{DQ} &= K_{nL}(V_{GSL} - V_{TNL})^2 = K_{nL}(V_{DD} - V_o - V_{TNL})^2 \\
 0.5 &= 0.030(10 - V_o - 1)^2 \\
 \sqrt{\frac{0.5}{0.030}} &= 9 - V_o \Rightarrow V_o = 4.92 \text{ V}
 \end{aligned}$$

$$b. \quad I_{DD} = I_{DL}$$

$$\begin{aligned}
 K_{nD}(V_i - V_{TND})^2 &= K_{nL}(V_{DD} - V_o - V_{TNL})^2 \\
 \sqrt{\frac{K_{nD}}{K_{nL}}}(V_i - V_{TND}) &= V_{DD} - V_o - V_{TNL} \\
 V_o &= V_{DD} - V_{TNL} - \sqrt{\frac{K_{nD}}{K_{nL}}}(V_i - V_{TND}) \\
 A_v &= \frac{dV_o}{dV_i} = -\sqrt{\frac{K_{nD}}{K_{nL}}} = -\sqrt{\frac{(W/L)_D}{(W/L)_L}} \\
 A_v &= -\sqrt{\frac{500}{30}} \Rightarrow A_v = -4.08
 \end{aligned}$$

6.41

$$\begin{aligned}
 (a) \quad I_{DQ} &= K_L(V_{GSL} - V_{TNL})^2 = K_L(V_{DSL} - V_{TNL})^2 \\
 I_D &= (0.1)(4 - 1)^2 = 0.9 \text{ mA} \\
 I_{DQ} &= K_D(V_{GSD} - V_{TND})^2 \\
 0.9 &= (1)(V_{GSD} - 1)^2 \Rightarrow V_{GSD} = 1.95 \text{ V} \\
 V_{GG} &= V_{GSD} + V_{DSL} = 1.95 + 4 \\
 \Rightarrow V_{GG} &= 5.95 \text{ V}
 \end{aligned}$$

$$b. \quad I_{DD} = I_{DL}$$

$$\begin{aligned}
 K_D(V_{GSD} - V_{TND})^2 &= K_L(V_{GSL} - V_{TNL})^2 \\
 \sqrt{\frac{K_D}{K_L}}(V_{GG} + V_i - V_o - V_{TND}) &= V_o - V_{TNL} \\
 V_o \left(1 + \sqrt{\frac{K_D}{K_L}}\right) &= \sqrt{\frac{K_D}{K_L}}(V_{GG} + V_i - V_{TND}) + V_{TNL} \\
 A_v &= \frac{dV_o}{dV_i} = \frac{\sqrt{K_D/K_L}}{1 + \sqrt{K_D/K_L}} \Rightarrow A_v = \frac{1}{1 + \sqrt{K_L/K_D}}
 \end{aligned}$$

(c) From Problem 6.39:

$$\begin{aligned}
 R_{LD} &= \frac{1}{2K_L(V_{DSL} - V_{TNL})} \\
 &= \frac{1}{2(0.1)(4 - 1)} = 1.67 \text{ k}\Omega \\
 g_m &= 2\sqrt{K_D I_{DQ}} = 2\sqrt{(1)(0.9)} = 1.90 \text{ mA/V} \\
 A_v &= \frac{g_m(R_{LD} \parallel R_L)}{1 + g_m(R_{LD} \parallel R_L)} = \frac{(1.90)(1.67 \parallel 4)}{1 + (1.90)(1.67 \parallel 4)} \\
 \Rightarrow A_v &= 0.691
 \end{aligned}$$

6.42

a. From Problem 6-41:

$$\begin{aligned}
 A_v &= \frac{g_m(R_{LD} \parallel R_L)}{1 + g_m(R_{LD} \parallel R_L)} = \frac{(1.90)(1.67 \parallel 10)}{1 + (1.90)(1.67 \parallel 10)} \\
 A_v &= 0.731
 \end{aligned}$$


$$\begin{aligned}
 b. \quad R_o &= \frac{1}{g_m} \parallel R_{LD} = \frac{1}{1.90} \parallel 1.67 = 0.526 \parallel 1.67 \\
 R_o &= 0.40 \text{ k}\Omega
 \end{aligned}$$

6.43

$$\begin{aligned}
 a. \quad I_{D1} &= K_1(V_{GS1} - V_{TN1})^2 \\
 0.4 &= 0.1(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 4 \text{ V} \\
 V_{S1} &= I_{D1}R_{S1} = (0.4)(4) = 1.6 \text{ V} \\
 V_{G1} &= V_{S1} + V_{GS1} = 1.6 + 4 = 5.6 \text{ V} \\
 V_{G1} &= \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}
 \end{aligned}$$

$$\begin{aligned}
 5.6 &= \frac{1}{R_1}(200)(10) \Rightarrow R_1 = 357 \text{ k}\Omega \\
 \frac{357R_2}{357 + R_2} &= 200 \Rightarrow R_2 = 455 \text{ k}\Omega \\
 V_{DS1} &= V_{DD} - I_{D1}(R_{S1} + R_{D1}) \\
 4 &= 10 - (0.4)(4 + R_{D1}) \Rightarrow R_{D1} = 11 \text{ k}\Omega \\
 V_{D1} &= 10 - (0.4)(11) = 5.6 \text{ V}
 \end{aligned}$$
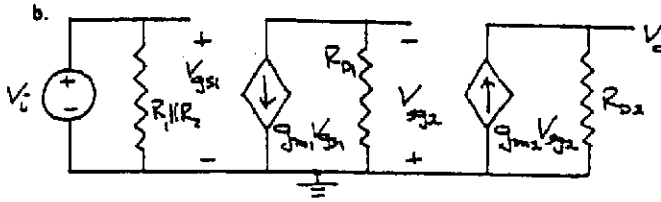
$$\begin{aligned}
 I_{D2} &= K_2(V_{SG2} + V_{TN2})^2 \\
 2 &= 1(V_{SG2} - 2)^2 \Rightarrow V_{SG2} = 3.41 \text{ V} \\
 V_{S2} &= V_{D1} + V_{SG2} = 5.6 + 3.41 = 9.01 \\
 R_{S2} &= \frac{10 - 9.01}{2} \Rightarrow R_{S2} = 0.495 \text{ k}\Omega \\
 V_{SD2} &= V_{DD} - I_{D2}(R_{S2} + R_{D2}) \\
 5 &= 10 - (2)(0.495 + R_{D2}) \Rightarrow R_{D2} = 2.01 \text{ k}\Omega
 \end{aligned}$$



$$V_o = g_{m2} V_{gs2} R_{D2} = (g_{m2} R_{D2})(g_{m1} V_{gs1} R_{D1})$$

$$V_{gs1} = V_i$$


$$A_v = \frac{V_o}{V_i} = g_{m1} g_{m2} R_{D1} R_{D2}$$

$$g_{m1} = 2\sqrt{K_1 I_{D1}} = 2\sqrt{(0.1)(0.4)} = 0.4 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_2 I_{D2}} = 2\sqrt{(1)(2)} = 2.83 \text{ mA/V}$$

$$A_v = (0.4)(2.83)(11)(2.01) \Rightarrow \underline{A_v = 25.0}$$

c.

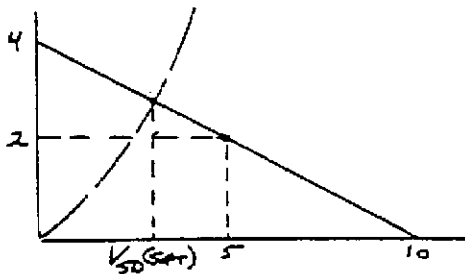

$$V_{SD}(\text{sat}) = V_{SG} + V_{TN}$$

$$= V_{DD} - I_{D2}(R_{D2} + R_{S2})$$

$$= V_{DD} - k_{p2}(R_{D2} + R_{S2})V_{SD}^2(\text{sat})$$

So

$$(1)(2.01 + 0.495)V_{SD}^2(\text{sat}) + V_{SD}(\text{sat}) - V_{DD} = 0$$

$$2.505V_{SD}^2(\text{sat}) + V_{SD}(\text{sat}) - 10 = 0$$

$$V_{SD}(\text{sat}) = \frac{-1 \pm \sqrt{1 + 4(2.505)(10)}}{2(2.505)}$$


$$V_{SD}(\text{sat}) = 1.81 \text{ V}$$

$$5 - 1.81 = 3.19$$

$$\Rightarrow \text{Max. output swing} = 6.38 \text{ V peak-to-peak}$$

6.44

a.

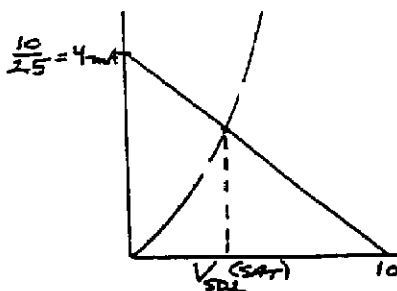

$$V_{SD2}(\text{sat}) = V_{DD} - I_{D2}(R_{D2} + R_{S2})$$

$$= V_{DD} - K_{p2}(R_{D2} + R_{S2})V_{SD2}^2(\text{sat})$$

$$(1)(2 + 0.5)V_{SD2}^2(\text{sat}) + V_{SD2}(\text{sat}) - 10 = 0$$

$$2.5V_{SD2}^2(\text{sat}) + V_{SD2}(\text{sat}) - 10 = 0$$

$$V_{SD2}(\text{sat}) = \frac{-1 \pm \sqrt{1 + 4(2.5)(10)}}{2(2.5)} = 1.81 \text{ V}$$

$$V_{SDQ2} = \frac{10 - 1.81}{2} + 1.81 \Rightarrow V_{SDQ2} = 5.91 \text{ V}$$

$$V_{SDQ2} = V_{DD} - I_{DQ2}(R_{D2} + R_{S2})$$

$$5.91 = 10 - I_{DQ2}(2 + 0.5) \Rightarrow I_{DQ2} = 1.64 \text{ mA}$$

$$V_{S2} = 10 - (1.64)(0.5) = 9.18 \text{ V}$$

$$I_{DQ2} = K_{p2}(V_{GS2} + V_{TP2})^2$$

$$1.64 = (1)(V_{GS2} - 2)^2 \Rightarrow V_{GS2} = 3.28 \text{ V}$$

$$V_{D1} = V_{S2} - V_{SG2} = 9.18 - 3.28 = 5.90 \text{ V}$$

$$R_{D1} = \frac{10 - 5.90}{0.4} \Rightarrow \underline{R_{D1} = 10.25 \text{ k}\Omega}$$

$$I_{DQ1} = K_{p1}(V_{GS1} - V_{TN1})^2$$

$$0.4 = (0.1)(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 4 \text{ V}$$

$$V_{S1} = (0.4)(1) = 0.4 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = 0.4 + 4 = 4.4 \text{ V}$$

$$V_{G1} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$4.4 = \frac{1}{R_1} \cdot (200)(10) \Rightarrow \underline{R_1 = 455 \text{ k}\Omega}$$

$$\frac{455R_2}{455 + R_2} = 200 \Rightarrow \underline{R_2 = 357 \text{ k}\Omega}$$

b. $\underline{I_{DQ2} = 1.64 \text{ mA}}$

$$V_{SDQ2} = 10 - (1.64)(2 + 0.5) \Rightarrow \underline{V_{SDQ2} = 5.90 \text{ V}}$$

$$V_{DSQ1} = 10 - (0.4)(10.25 + 1) \Rightarrow \underline{V_{DSQ1} = 5.50 \text{ V}}$$

(c) $g_{m1} = 2\sqrt{K_{p1}I_{DQ1}} = 2\sqrt{(0.1)(0.4)} = 0.4 \text{ mA/V}$

$$g_{m2} = 2\sqrt{K_{p2}I_{DQ2}} = 2\sqrt{(1)(1.64)} = 2.56 \text{ mA/V}$$

$$A_v = g_{m1}g_{m2}R_{D1}R_{D2} = (0.4)(2.56)(10.25)(2)$$

$$\Rightarrow \underline{A_v = 21.0}$$

6.45

a. $V_{DSQ2} = 7 = V_{DD} - I_{DQ2}R_{S2} = 10 - I_{DQ2}(6)$

$$I_{DQ2} = 0.5 \text{ mA}$$

$$I_{DQ2} = K_2(V_{GS2} - V_{TN2})^2$$

$$0.5 = (0.2)(V_{GS2} - 0.8)^2 \Rightarrow V_{GS2} = 2.38 \text{ V}$$

$$V_{S1} = V_{S2} + V_{GS2} = 3 + 2.38 = 5.38$$

$$I_{DQ1} = \frac{V_{S1}}{R_{S1}} = \frac{5.38}{20} = 0.269 \text{ mA}$$

$$I_{DQ1} = K_1(V_{GS1} - V_{TN1})^2$$

$$0.269 = (0.2)(V_{GS1} - 0.8)^2 \Rightarrow V_{GS1} = 1.96 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = 5.38 + 1.96 = 7.34 \text{ V}$$

$$V_{G1} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$7.34 = \frac{1}{R_1} (400)(10) \Rightarrow R_1 = 545 \text{ k}\Omega$$

$$\frac{545 R_2}{545 + R_2} = 400 \Rightarrow R_2 = 1.50 \text{ M}\Omega$$

b. $I_{DQ1} = 0.269 \text{ mA}$, $I_{DQ2} = 0.5 \text{ mA}$

$$V_{DSQ1} = 10 - (0.269)(20) \Rightarrow V_{DSQ1} = 4.62 \text{ V}$$

c. $A_v = \frac{g_{m1} R_{S1}}{1 + g_{m1} R_{S1}} \cdot \frac{g_{m2} R_{S2}}{1 + g_{m2} R_{S2}}$


$$g_{m1} = 2\sqrt{K_1 I_{DQ1}} = 2\sqrt{(0.2)(0.269)} = 0.464 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_2 I_{DQ2}} = 2\sqrt{(0.2)(0.5)} = 0.632 \text{ mA/V}$$

$$A_v = \frac{(0.464)(20)}{1 + (0.464)(20)} \cdot \frac{(0.632)(6)}{1 + (0.632)(6)}$$

$$= (0.9027)(0.7913)$$

$$= A_v = 0.714$$

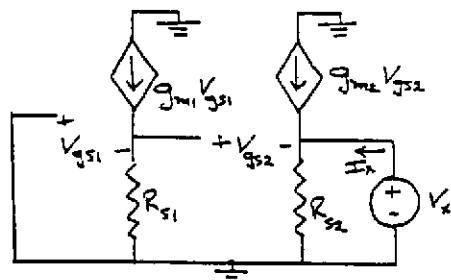

$$R_0 = \frac{1}{g_{m2}} \parallel R_{S2} = \frac{1}{0.632} \parallel 6 = 1.582 \parallel 6$$

$$\Rightarrow R_0 = 1.25 \text{ k}\Omega$$

6.46

(a) $I_{DQ1} = \frac{10 - V_{GS1}}{R_{S2}} = K_{n1}(V_{GS1} - V_{TN1})^2$

$$10 - V_{GS1} = (4)(10)(V_{GS1}^2 - 4V_{GS1} + 4)$$

$$40V_{GS1}^2 - 159V_{GS1} + 150 = 0$$

$$V_{GS1} = \frac{159 \pm \sqrt{(159)^2 - 4(40)(150)}}{2(40)}$$

$$\Rightarrow V_{GS1} = 2.435 \text{ V}$$

$$I_{DQ1} = (4)(2.435 - 2)^2 \Rightarrow I_{DQ1} = 0.757 \text{ mA}$$

$$V_{DSQ1} = 20 - (0.757)(10) \Rightarrow V_{DSQ1} = 12.4 \text{ V}$$


Also $I_{DQ2} = 0.757 \text{ mA}$

$$V_{DSQ2} = 20 - (0.757)(10 + 5) \Rightarrow V_{DSQ2} = 8.65 \text{ V}$$

(b) $g_{m1} = g_{m2} = 2\sqrt{K I_{DQ}} = 2\sqrt{(4)(0.757)} \Rightarrow$

$$g_{m1} = g_{m2} = 3.48 \text{ mA/V}$$

c.

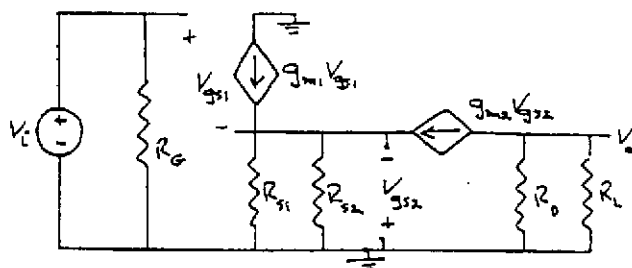

$$V_o = -(g_{m2} V_{gs2})(R_D \parallel R_L)$$

$$V_{gs2} = (-g_{m1} V_{gs1} - g_{m2} V_{gs2})(R_{S1} \parallel R_{S2})$$

$$V_i = V_{gs1} - V_{gs2} \Rightarrow V_{gs1} = V_i + V_{gs2}$$

$$V_{gs2} + g_{m2} V_{gs2}(R_{S1} \parallel R_{S2})$$

$$= -g_{m1}(V_i + V_{gs2})(R_{S1} \parallel R_{S2})$$

$$V_{gs2} + g_{m2} V_{gs2}(R_{S1} \parallel R_{S2}) + g_{m1} V_{gs2}(R_{S1} \parallel R_{S2})$$

$$= -g_{m1} V_i(R_{S1} \parallel R_{S2})$$

$$V_{gs2} = \frac{-g_{m1} V_i(R_{S1} \parallel R_{S2})}{1 + g_{m2}(R_{S1} \parallel R_{S2}) + g_{m1}(R_{S1} \parallel R_{S2})}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_{m1} g_{m2} (R_{S1} \parallel R_{S2})(R_D \parallel R_L)}{1 + (g_{m1} + g_{m2})(R_{S1} \parallel R_{S2})}$$

$$A_v = \frac{(3.48)^2 (10 \parallel 10)(5 \parallel 2)}{1 + (3.48 + 3.48)(10 \parallel 10)}$$

$$\Rightarrow A_v = 2.42$$

6.47

a. $I_{DQ} = 3 \text{ mA}$

$$V_{S1} = I_{DQ} R_S - 5 = (3)(1.2) - 5 = -1.4 \text{ V}$$

$$I_{DQ} = K_1(V_{GS} - V_{TN})^2$$

$$3 = 2(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.22 \text{ V}$$

$$V_{G1} = V_{GS} + V_{S1} = 2.22 - 1.4 = 0.82 \text{ V}$$

$$V_{G1} = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) (5) \Rightarrow 0.82 = \left(\frac{R_3}{500} \right) (5)$$

$$\Rightarrow R_3 = 82 \text{ k}\Omega$$

$$V_{D1} = V_{S1} + V_{DSQ1} = -1.4 + 2.5 = 1.1 \text{ V}$$

$$V_{G2} = V_{D1} + V_{GS} = 1.1 + 2.22 = 3.32 \text{ V}$$

$$V_{G2} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (5)$$

$$\Rightarrow 3.32 = \left(\frac{R_2 + R_3}{500} \right) (5)$$

$$R_2 + R_3 = 332 \Rightarrow R_2 = 250 \text{ k}\Omega$$

$$R_1 = 500 - 250 - 82 \Rightarrow \underline{R_1 = 168 \text{ k}\Omega}$$

$$V_{D2} = V_{D1} + V_{DSQ2} = 1.1 + 2.5 = 3.6 \text{ V}$$

$$R_D = \frac{5 - 3.6}{3} \Rightarrow \underline{R_D = 0.467 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(2)(3)} = 4.90 \text{ mA/V}$$

$$A_v = -(4.90)(0.467) \Rightarrow \underline{A_v = -2.29}$$

6.48

$$\text{a. } V_{S1} = I_{DQ} R_S - 10 = (5)(2) - 10 \Rightarrow V_{S1} = 0$$

$$I_{DQ} = K_1 (V_{GS1} - V_{TN})^2$$

$$5 = 4(V_{GS1} - 1.5)^2 \Rightarrow V_{GS1} = 2.618 \text{ V}$$

$$V_{G1} = V_{GS1} + V_{S1} = 2.618 \text{ V} = I R_3 = (0.1) R_3$$

$$\Rightarrow \underline{R_3 = 26.2 \text{ k}\Omega}$$

$$V_{D1} = V_{S1} + V_{DSQ1} = 0 + 3.5 = 3.5 \text{ V}$$

$$V_{G2} = V_{D1} + V_{GS} = 3.5 + 2.62 = 6.12 \text{ V}$$

$$= (0.1)(R_2 + R_3)$$

$$R_2 + R_3 = 61.2 \text{ k}\Omega \Rightarrow \underline{R_2 = 35 \text{ k}\Omega}$$

$$V_{D2} = V_{D1} + V_{DSQ2} = 3.5 + 3.5 = 7.0 \text{ V}$$

$$R_D = \frac{10 - 7}{5} \Rightarrow \underline{R_D = 0.6 \text{ k}\Omega}$$

$$R_1 = \frac{10 - 6.12}{0.1} \Rightarrow \underline{R_1 = 38.8 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(5)} = 8.94 \text{ mA/V}$$

$$A_v = -(8.94)(0.6) \Rightarrow \underline{A_v = -5.36}$$

6.49

$$\text{a. } I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 6 \left(1 - \frac{V_{GS}}{(-3)}\right)^2$$

$$V_{GS} = (-3) \left[1 - \sqrt{\frac{4}{6}}\right] \Rightarrow \underline{V_{GS} = -0.551 \text{ V}}$$

$$V_{DSQ} = V_{DD} - I_{DQ} R_D$$

$$6 = 10 - (4) R_D \Rightarrow \underline{R_D = 1 \text{ k}\Omega}$$

$$\text{b. } g_m = \frac{2I_{DSS}}{(-V_P)} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(6)}{3} \left(1 - \frac{-0.551}{-3}\right)$$

$$\Rightarrow \underline{g_m = 3.27 \text{ mA/V}}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(4)} \Rightarrow \underline{r_o = 25 \text{ k}\Omega}$$

$$\text{c. } A_v = -g_m (r_o \parallel R_D) = -(3.27)(25 \parallel 1)$$

$$\Rightarrow \underline{A_v = -3.14}$$

6.50

$$V_{GS} + I_{DQ}(R_{S1} + R_{S2}) = 0$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} + I_{DSS}(R_{S1} + R_{S2}) \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0$$

$$V_{GS} + (2)(0.1 + 0.25) \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0$$

$$V_{GS} + 0.7 \left(1 - \frac{2V_{GS}}{(-2)} + \frac{V_{GS}^2}{(-2)^2}\right) = 0$$

$$0.175V_{GS}^2 + 1.7V_{GS} + 0.7 = 0$$

$$V_{GS} = \frac{-1.7 \pm \sqrt{(1.7)^2 - 4(0.175)(0.7)}}{2(0.175)}$$

$$\Rightarrow \underline{V_{GS} = -0.431 \text{ V}}$$

$$g_m = \frac{2I_{DSS}}{-V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(2)}{2} \left(1 - \frac{-0.431}{-2}\right)$$

$$\Rightarrow \underline{g_m = 1.57 \text{ mA/V}}$$

$$A_v = \frac{-g_m(R_D \parallel R_L)}{1 + g_m R_{S1}} = \frac{-(1.57)(8 \parallel 4)}{1 + (1.57)(0.1)}$$

$$\Rightarrow \underline{A_v = -3.62}$$

$$A_i = \frac{i_o}{i_i} = \frac{(v_o/R_L)}{(v_i/R_G)} = \frac{v_o}{v_i} \cdot \frac{R_G}{R_L} = (-3.62) \left(\frac{50}{4}\right)$$

$$\Rightarrow \underline{A_i = -45.3}$$

6.51

$$I_{DQ} = \frac{I_{DSS}}{2} = 4 \text{ mA}$$

$$V_{DSQ} = \frac{V_{DD}}{2} = 10 \text{ V}$$

$$V_{DSQ} = V_{DD} - I_{DQ}(R_S + R_D)$$

$$10 = 20 - (4)(R_S + R_D) \Rightarrow R_S + R_D = 2.5 \text{ k}\Omega$$

$$V_S = 2 \text{ V} = I_{DQ} R_S = 4 R_S$$

$$\Rightarrow \underline{R_S = 0.5 \text{ k}\Omega}, \quad \underline{R_D = 2.0 \text{ k}\Omega}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 8 \left(1 - \frac{V_{GS}}{(-4.2)}\right)^2 \Rightarrow V_{GS} = (-4.2) \left(1 - \sqrt{\frac{4}{8}}\right)$$

$$\Rightarrow \underline{V_{GS} = -1.23 \text{ V}}$$

$$V_G = V_S + V_{GS} = 2 - 1.23$$

$$V_G = 0.77 \text{ V} = \left(\frac{R_2}{R_1 + R_2}\right)(20) = \left(\frac{R_2}{100}\right)(20)$$

$$\Rightarrow \underline{R_2 = 3.85 \text{ k}\Omega}, \quad \underline{R_1 = 95.2 \text{ k}\Omega}$$

6.52

$$a. \quad I_{DQ} = \frac{I_{DSS}}{2} = 5 \text{ mA}$$

$$V_{DSQ} = \frac{V_{DD}}{2} = \frac{12}{2} = 6 \text{ V}$$

$$R_S = \frac{12 - 6}{5} \Rightarrow R_S = 1.2 \text{ k}\Omega$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5 = 10 \left(1 - \frac{V_{GS}}{(-5)}\right)^2 \Rightarrow V_{GS} = (-5) \left(1 - \sqrt{\frac{5}{10}}\right)$$

$$\Rightarrow V_{GS} = -1.46 \text{ V}$$

$$V_G = V_S + V_{GS} = 6 - 1.46 = 4.54 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \frac{1}{R_1} \cdot R_{1n} \cdot V_{DD}$$

$$4.54 = \frac{1}{R_1} (100)(12) \Rightarrow R_1 = 264 \text{ k}\Omega$$

$$\frac{264 R_2}{264 + R_2} = 100 \Rightarrow R_2 = 161 \text{ k}\Omega$$

$$b. \quad g_m = \frac{2I_{DSS}}{(-V_P)} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(10)}{5} \left(1 - \frac{-1.46}{-5}\right)$$

$$\Rightarrow g_m = 2.83 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(5)} = 20 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$A_v = \frac{(2.83)(20 \parallel 1.2 \parallel 0.5)}{1 + (2.83)(20 \parallel 1.2 \parallel 0.5)}$$

$$\Rightarrow A_v = 0.495$$

$$R_o = \frac{1}{g_m} \parallel R_S = \frac{1}{2.83} \parallel 1.2 = 0.353 \parallel 1.2$$

$$\Rightarrow R_o = 0.273 \text{ k}\Omega$$

6.53

$$a. \quad V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \left(\frac{110}{110 + 90}\right)(10) = 5.5 \text{ V}$$

$$I_{DQ} = \frac{10 - (V_G - V_{GS})}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$10 - 5.5 + V_{GS} = (2)(5) \left(1 - \frac{V_{GS}}{1.75}\right)^2$$

$$4.5 + V_{GS} = 10 \left(1 - 1.143 V_{GS} + 0.3265 V_{GS}^2\right)$$

$$3.265 V_{GS}^2 - 12.43 V_{GS} + 5.5 = 0$$

$$V_{GS} = \frac{12.43 \pm \sqrt{(12.43)^2 - 4(3.265)(5.5)}}{2(3.265)}$$

$$\Rightarrow V_{GS} = 0.511 \text{ V}$$

$$I_{DQ} = (2) \left(1 - \frac{0.511}{1.75}\right)^2 \Rightarrow I_{DQ} = 1.42 \text{ mA}$$

$$V_{SDQ} = 10 - (1.42)(5) \Rightarrow V_{SDQ} = 2.9 \text{ V}$$

$$b. \quad g_m = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(2)}{1.75} \left(1 - \frac{0.511}{1.75}\right)$$

$$\Rightarrow g_m = 1.62 \text{ mA/V}$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{(1.62)(5 \parallel 10)}{1 + (1.62)(5 \parallel 10)}$$


$$\Rightarrow A_v = 0.844$$

$$A_i = \frac{i_o}{i_i} = \left(\frac{v_o/R_L}{v_i/R_i}\right) = A_v \cdot \left(\frac{R_i}{R_L}\right)$$

$$R_i = R_1 \parallel R_2 = 90 \parallel 110 = 49.5 \text{ k}\Omega$$

$$A_i = (0.844) \left(\frac{49.5}{10}\right) \Rightarrow A_i = 4.18$$

c.

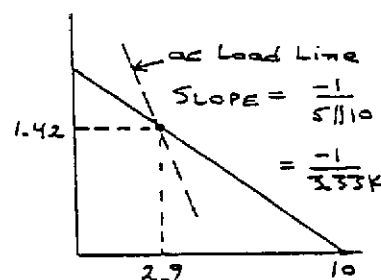

Maximum swing in output voltage
= 3.8 V peak-to-peak

6.54

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 8 \left(1 - \frac{V_{GS}}{4}\right)^2 \Rightarrow V_{GS} = 4 \left(1 - \sqrt{\frac{4}{8}}\right)$$

$$\Rightarrow V_{GS} = 1.17 \text{ V}$$

$$V_{SDQ} = V_{DD} - I_{DQ}(R_S + R_D)$$

$$7.5 = 20 - 4(R_S + R_D) \Rightarrow R_S + R_D = 3.125 \text{ k}\Omega$$

$$g_m = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(8)}{4} \left(1 - \frac{1.17}{4}\right)$$

$$\Rightarrow g_m = 2.83 \text{ mA/V}$$

$$R_S = 3.125 - R_D$$

$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$

$$-3(1 + g_m R_S) = -g_m R_D$$

$$3[1 + (2.83)(3.125 - R_D)] = (2.83)R_D$$

$$9.844 - 2.83R_D = 0.7075R_D \Rightarrow \underline{R_D = 2.78 \text{ k}\Omega}$$

$$\underline{R_S = 0.345 \text{ k}\Omega}$$

$$V_S = 20 - (4)(0.345) \Rightarrow V_S = 18.6 \text{ V}$$

$$V_G = V_S - V_{GS} = 18.6 - 1.17 = 17.4 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{R_2}{400} \right) (20)$$

$$\Rightarrow \underline{R_2 = 348 \text{ k}\Omega}, \quad \underline{R_1 = 52 \text{ k}\Omega}$$