

## Chapter 9

## Exercise Solutions

E9.1

$$A_{CL} = -\frac{R_2}{R_1} = \frac{-100 \text{ k}\Omega}{10 \text{ k}\Omega} \Rightarrow A_{CL} = -10$$

$$v_I = 0.25 \text{ V} \Rightarrow v_O = -2.5 \text{ V}$$

$$i_1 = \frac{v_I}{R_1} = \frac{0.25}{10 \text{ k}\Omega} = 0.025 \text{ mA} \Rightarrow i_1 = 25 \mu\text{A}$$

$$i_2 = i_1 = 25 \mu\text{A}$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

E9.2

$$A_{CL} = -\frac{R_2}{R_1} = -15$$

$$R_1 = \underline{R_1 = 20 \text{ k}\Omega} \Rightarrow R_2 = (15)(20 \text{ k}\Omega)$$

$$R_2 = \underline{300 \text{ k}\Omega}$$

E9.3

$$(a) A_v = \frac{-R_2}{R_1 + R_3}$$

$$A_v(\text{min}) = \frac{-100}{19 + 1.3} = -4.926$$

$$A_v(\text{max}) = \frac{-100}{19 + 0.7} = -5.076$$

$$\text{so } 4.926 \leq |A_v| \leq 5.076$$

$$(b) i_1(\text{max}) = \frac{0.1}{19 + 0.7} = 5.076 \mu\text{A}$$

$$i_1(\text{min}) = \frac{0.1}{19 + 1.3} = 4.926 \mu\text{A}$$

$$\text{so } 4.926 \leq i_1 \leq 5.076 \mu\text{A}$$

(c) Maximum current specification is violated.

E9.4

We can write

$$A_{CL} = -\frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_4} \right) - \frac{R_3}{R_1}$$

$$R_1 = \underline{R_1 = 10 \text{ k}\Omega}$$

$$\text{Want } A_{CL} = -50 \quad \text{Set } \underline{R_2 = R_3 = 50 \text{ k}\Omega}$$


$$A_{CL} = -50 = -5 \left( 1 + \frac{R_3}{R_4} \right) - 5$$

$$1 + \frac{R_3}{R_4} = 9 \Rightarrow \frac{R_3}{R_4} = 8 = \frac{50}{R_4}$$

$$\underline{R_4 = 6.25 \text{ k}\Omega}$$

E9.5
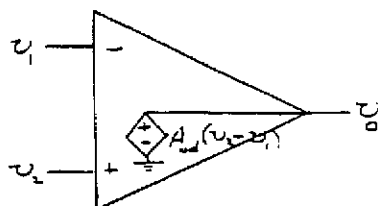
$$v_O = A_d(v_2 - v_1) \quad A_d = 10^3$$



$$a. \quad v_2 = 0, v_O = 5$$

$$v_1 = -\frac{v_O}{A_d} = -\frac{5}{10^3} \Rightarrow \underline{v_1 = -5 \text{ mV}}$$

$$b. \quad v_1 = 5, v_O = -10$$

$$\frac{v_O}{A_d} = v_2 - v_1$$

$$\frac{-10}{10^3} = v_2 - 5 \Rightarrow \underline{v_2 = 4.99 \text{ V}}$$

$$c. \quad v_1 = 0.001, v_2 = -0.001$$

$$v_O = 10^3(-0.001 - 0.001)$$

$$\underline{v_O = -2 \text{ V}}$$

$$d. \quad v_2 = 3, v_O = 3$$

$$v_O = A_d(v_2 - v_1)$$

$$\frac{v_O}{A_d} = v_2 - v_1$$

$$\frac{3}{10^3} = 3 - v_1 \Rightarrow \underline{v_1 = 2.997 \text{ V}}$$

E9.6

We have

$$A_{CL} = -\frac{R_2}{R_1} \cdot \frac{1}{\left[ 1 + \frac{1}{A_d} \left( 1 + \frac{R_2}{R_1} \right) \right]}$$

$$R_1 = R_2 = 25 \text{ k}\Omega \quad \text{Let } \frac{R_2}{R_1} = x$$

$$-12 = -\frac{x}{1 + \frac{1}{5 \times 10^3}(1 + x)}$$

$$= \frac{-x}{1.0002 + \frac{x}{5 \times 10^3}}$$

$$12 \left( 1.0002 + \frac{x}{5 \times 10^3} \right) = x$$

$$12.0024 = x - (2.4 \times 10^{-3})x$$

$$x = \frac{12.0024}{0.9976} = 12.0313 = \frac{R_2}{25 \text{ k}\Omega}$$


$$\underline{R_2 = 300.78 \text{ k}\Omega}$$

E9.7

$$\begin{aligned} v_o &= -\left(\frac{R_4}{R_1}v_{I1} + \frac{R_4}{R_2}v_{I2} + \frac{R_4}{R_3}v_{I3}\right) \\ v_o &= -\left[\left(\frac{40}{10}\right)(250) + \left(\frac{40}{20}\right)(200) + \left(\frac{40}{30}\right)(75)\right] \\ v_o &= -[1000 + 400 + 100] \\ v_o &= -1500 \mu\text{V} = -1.5 \text{ mV} \end{aligned}$$

E9.8
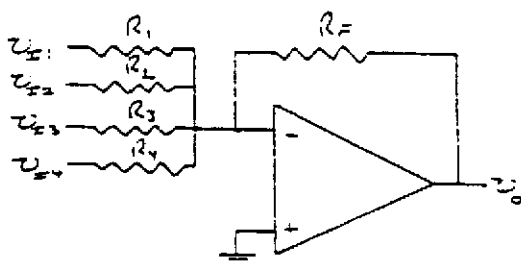
$$v_o = -\left(\frac{R_F}{R_1}v_{I1} + \frac{R_F}{R_2}v_{I2} + \frac{R_F}{R_3}v_{I3} + \frac{R_F}{R_4}v_{I4}\right)$$



We need

$$\frac{R_F}{R_1} = 7, \quad \frac{R_F}{R_2} = 14, \quad \frac{R_F}{R_3} = 3.5, \quad \frac{R_F}{R_4} = 10$$

Set  $R_F = 280 \text{ k}\Omega$ 

$$\text{Then } R_1 = \frac{280}{7} = 40 \text{ k}\Omega$$

$$R_2 = \frac{280}{14} = 20 \text{ k}\Omega$$

$$R_3 = \frac{280}{3.5} = 80 \text{ k}\Omega$$

$$R_4 = \frac{280}{10} = 28 \text{ k}\Omega$$

E9.9

$$|v_o| = \frac{v_{I1} + v_{I2} + v_{I3}}{3} = \frac{R_F}{R}(v_{I1} + v_{I2} + v_{I3})$$

$$\frac{R_F}{R} = \frac{1}{3} \Rightarrow R_1 = R_2 = R_3 = R = 1 \text{ M}\Omega$$

$$\text{Then } R_F = \frac{1}{3} \text{ M}\Omega = 333 \text{ k}\Omega$$

E9.10

$$A_v = \frac{v_o}{v_I} = \left(1 + \frac{R_2}{R_1}\right) = 5$$

$$\text{so that } \frac{R_2}{R_1} = 4$$


$$\text{For } v_o = 10 \text{ V}, v_I = 2 \text{ V}$$

$$\text{Then } i_1 = \frac{2}{R_1} = 50 \mu\text{A} \Rightarrow \underline{R_1 = 40 \text{ k}\Omega}$$

Then  $R_2 = 160 \text{ k}\Omega$  we find

$$i_2 = \frac{v_o - v_I}{R_2} = \frac{10 - 2}{160} = 50 \mu\text{A}$$

E9.11

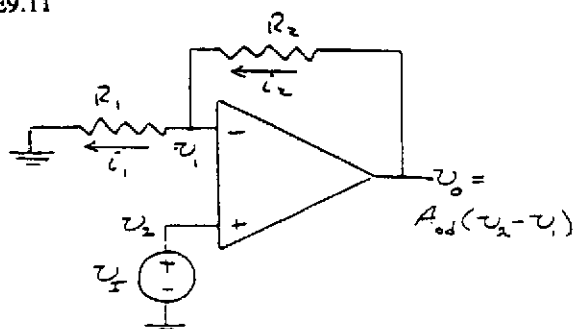

$$v_o = A_{od}(v_{I2} - v_{I1}) = A_{od}(v_{I1} - v_{I1})$$

$$\frac{v_o}{A_{od}} - v_{I1} = -v_{I1} \text{ or } v_{I1} = v_{I1} - \frac{v_o}{A_{od}}$$

$$i_1 = \frac{v_{I1}}{R_1} = i_2 \text{ and } i_2 = \frac{v_o - v_{I1}}{R_2}$$

$$\text{Then } v_{I1} \left(\frac{1}{R_1}\right) = \frac{v_o - v_{I1}}{R_2}$$

$$v_{I1} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) = \frac{v_o}{R_2}$$

$$v_o \left(1 + \frac{R_2}{R_1}\right) v_{I1} = \left(1 + \frac{R_2}{R_1}\right) \left(v_{I1} - \frac{v_o}{A_{od}}\right)$$

$$\text{So } A_v = \frac{v_o}{v_{I1}} = \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)}$$

E9.12

$$\text{For } v_{I2} = 0, v_o = \left(\frac{R_b}{R_b + R_a}\right) v_{I1} \text{ and}$$

$$v_o(v_{I1}) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_b}{R_b + R_a}\right) v_{I1}$$

$$= \left(1 + \frac{70}{5}\right) \left(\frac{50}{50 + 25}\right) v_{I1}$$

$$= 10v_{I1}$$

For  $v_{I1} = 0$ ,

$$v_o = \left(\frac{R_a}{R_b + R_a}\right) v_{I2}$$

$$v_o(v_{I2}) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_a}{R_b + R_a}\right) v_{I2}$$

$$= \left(1 + \frac{70}{5}\right) \left(\frac{25}{25 + 50}\right) v_{I2}$$


$$= 5v_{I2}$$

Then

$$v_o = v_o(v_{I1}) + v_o(v_{I2})$$

$$\underline{v_o = 10v_{I1} + 5v_{I2}}$$

E9.13

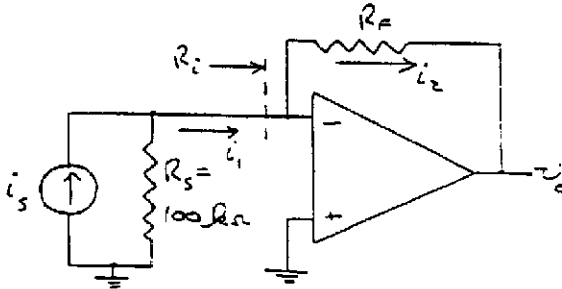

$$R_S \gg R_i \text{ so } i_1 = i_2 = i_s = 100 \mu\text{A}$$

$$v_o = -i_s R_F$$

$$\text{We want } -10 = -(100 \times 10^{-6}) R_F$$

$$\Rightarrow \underline{R_F = 100 \text{ k}\Omega}$$

E9.14

We may note that

$$\frac{R_3}{R_2} = \frac{3}{1.5} = 2 \text{ and } \frac{R_F}{R_1} = \frac{20}{10} = 2$$

so that

$$\frac{R_3}{R_2} = \frac{R_F}{R_1}$$

Then

$$i_L = \frac{-v_I}{R_2} = \frac{-(-3)}{1.5 \text{ k}\Omega}$$

$$\Rightarrow \underline{i_L = 2 \text{ mA}}$$

$$v_L = i_L Z_L = (2 \times 10^{-3})(200) = 0.4 \text{ V}$$

$$i_4 = \frac{v_L}{R_2} = \frac{0.4}{1.5 \text{ k}\Omega} = 0.267 \text{ mA}$$

$$i_3 = i_4 + i_L = 0.267 + 2 = 2.267 \text{ mA}$$

$$v_o = i_3 R_3 + v_L = (2.267 \times 10^{-3})(3 \times 10^3) - 0.4$$

$$\Rightarrow \underline{v_o = 7.2 \text{ V}}$$

E9.15

We want  $i_L = 1 \text{ mA}$  when  $v_I = -5 \text{ V}$

$$i_L = \frac{-v_I}{R_2} \Rightarrow R_2 = \frac{-v_I}{i_L} = \frac{-(-5)}{10^{-3}}$$

$$\Rightarrow \underline{R_2 = 5 \text{ k}\Omega}$$

$$v_L = i_L Z_L = (10^{-3})(500)$$

$$\Rightarrow v_L = 0.5 \text{ V}$$

$$i_4 = \frac{v_L}{R_2} = \frac{0.5}{5 \text{ k}\Omega} \Rightarrow i_4 = 0.1 \text{ mA}$$

$$i_3 = i_4 + i_L = 0.1 + 1 = 1.1 \text{ mA}$$

If op-amp is biased at  $\pm 10 \text{ V}$ , output must be limited to  $\approx 8 \text{ V}$ .

$$\text{So } v_o = i_3 R_3 + v_L$$

$$8 = (1.1 \times 10^{-3}) R_3 + 0.5$$

$$\Rightarrow \underline{R_3 = 6.82 \text{ k}\Omega}$$

$$\text{Let } \underline{R_3 = 7.0 \text{ k}\Omega}$$

Then we want

$$\frac{R_3}{R_2} = \frac{R_F}{R_1} = \frac{7}{5} = 1.4$$

$$\text{Can choose } \underline{R_1 = 10 \text{ k}\Omega} \text{ and } \underline{R_F = 14 \text{ k}\Omega}$$

E9.16

Refer to Fig. 9.24

$$R_1 = 2R_2 = 5 \text{ k}\Omega$$

$$\text{Let } \underline{R_1 = R_3 = 2.5 \text{ k}\Omega}$$

$$\text{Set } R_2 = R_4$$

$$\text{Differential Gain} = \frac{v_o}{v_i} = \frac{R_2}{R_1} = 100 = \frac{R_2}{2.5 \text{ k}\Omega}$$

$$\Rightarrow \underline{R_2 = R_4 = 250 \text{ k}\Omega}$$

E9.17

We have the general relation that

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{[R_4/R_3]}{1 + [R_4/R_3]}\right) v_{I2} - \frac{R_2}{R_1} v_{I1}$$

$$R_1 = R_3 = 10 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega, R_4 = 21 \text{ k}\Omega$$

$$v_o = \left(1 + \frac{20}{10}\right) \left(\frac{[21/10]}{1 + [21/10]}\right) v_{I2} - \left(\frac{20}{10}\right) v_{I1}$$

$$v_o = 2.0323 v_{I2} - 2.0 v_{I1}$$

$$\text{a. } v_{I1} = 1, v_{I2} = -1$$

$$v_o = -2.0323 - 2.0 \Rightarrow \underline{v_o = -4.032 \text{ V}}$$

$$\text{b. } v_{I1} = v_{I2} = 1 \text{ V}$$

$$v_o = 2.0323 - 2.0 \Rightarrow \underline{v_o = 0.0323 \text{ V}}$$

$$\text{c. } v_{cm} = v_{I1} = v_{I2} \text{ so common-mode gain}$$

$$\underline{A_{cm} = \frac{v_o}{v_{cm}} = 0.0323}$$

$$\text{d. } CMRR_{dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}}\right)$$

$$A_d = \frac{2.0323}{2} - (2.0) \left(-\frac{1}{2}\right) = 2.016$$

$$CMRR_{dB} = 20 \log_{10} \left(\frac{2.016}{0.0323}\right) = 35.9 \text{ dB}$$

E9.18

$$v_o = -\frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (v_{I1} - v_{I2})$$

$$\text{Differential gain (magnitude)} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Minimum Gain  $\Rightarrow$  Maximum  $R_1 = 1 + 50 = 51 \text{ k}\Omega$ 

$$\text{So } A_d = \frac{20}{20} \left( 1 + \frac{2(100)}{51} \right) \Rightarrow A_d = 4.92$$

Maximum Gain  $\Rightarrow$  Minimum  $R_1 = 1 \text{ k}\Omega$ 

$$A_d = \frac{20}{20} \left( 1 + \frac{2(100)}{1} \right) \Rightarrow A_d = 201$$

Range of Differential Gain = 4.92–201

E9.19

$$\text{a. } i_1 = \frac{v_{I1} - v_{I2}}{R_1}$$

$$v_{o1} = v_{I1} + i_1 R_2', \quad v_{o2} = v_{I2} - i_1 R_2 \text{ and}$$

$$v_o = \frac{R_4}{R_3} (v_{o2} - v_{o1})$$

$$v_o = \frac{R_4}{R_3} [v_{I2} - i_1 R_2 - v_{I1} - i_1 R_2']$$

$$v_o = \frac{R_4}{R_3} [(v_{I2} - v_{I1}) - i_1 (R_2 + R_2')]$$

$$v_o = \frac{R_4}{R_3} \left[ (v_{I2} - v_{I1}) - \left( \frac{v_{I2} - v_{I1}}{R_1} \right) (R_2 + R_2') \right]$$

For common-mode input  $v_{I2} = v_{I1}$ 

$$\Rightarrow v_o = 0 \Rightarrow \text{Common Gain} = 0, \text{ CMRR} = \infty$$

b.  $A_d(\text{min}) \Rightarrow R_2' \text{ min}, R_1 \text{ max}$ 

$$A_d = \left( \frac{20}{20} \right) \left[ 1 + \frac{100 + 95}{51} \right] = 4.82$$

$$A_d(\text{max}) = \left( \frac{20}{20} \right) \left[ 1 + \frac{100 + 105}{1} \right] = 206$$

$$\text{c. } \text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

$$A_{cm} = 0 \Rightarrow \text{CMRR} = \infty$$

E9.20

$$\text{Differential Gain} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Let  $R_3 = R_4$  so the difference amplifier gain is unity.Minimum Gain  $\Rightarrow$  Maximum  $R_1$ 

$$\text{So } \left( 1 + \frac{2R_2}{R_1(\text{max})} \right) = 2$$

$$\text{We want } 2R_2 = R_1(\text{max})$$

Maximum Gain  $\Rightarrow$  Minimum  $R_1$ 

$$\text{So } \left( 1 + \frac{2R_2}{R_1(\text{min})} \right) = 1000 \text{ or } 2R_2 = 999R_1(\text{min})$$

If  $R_2 = 50 \text{ k}\Omega$ , let  $R_1(\text{min}) = 100 \Omega$  fixed resistorand let  $R_1(\text{max}) = \frac{100 \text{ k}\Omega}{100} + 100 \Omega = 100.1$   
pot

Then actual differential gain is in the range of

$$\underline{1.999 - 1001}$$

E9.21


$$\text{Time constant} = \tau = R_1 C_2 = (10^4)(0.1 \times 10^{-6}) \\ = 1 \text{ m sec}$$

$$0 \leq t \leq 1 \Rightarrow v_o = \frac{-1}{R_1 C_2} \times t$$

$$\text{At } t = 1 \text{ m sec} \Rightarrow v_o = -1 \text{ V}$$

$$0 \leq t \leq 2 \Rightarrow v_o = -1 + \frac{1}{R_1 C_2} \times (t - 1)$$
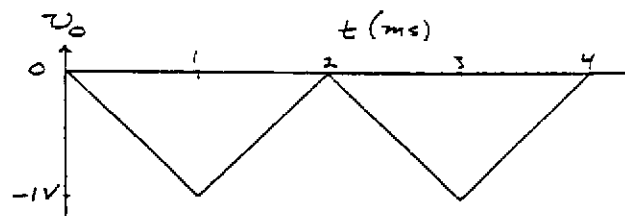
$$\text{At } t = 2 \text{ m sec} \Rightarrow v_o = -1 + \frac{(2 - 1)}{1} = 0$$



E9.22

End of 1st pulse:

$$v_o = \frac{-1}{\tau} \times t \Big|_0^{10 \mu\text{sec}} = \frac{-10 \times 10^{-6}}{\tau}$$

After 10 pulses:

$$v_o = -5 = \frac{-(10)(10 \times 10^{-6})}{\tau}$$

$$\text{So } \tau = \frac{100 \times 10^{-6}}{5} = 20 \mu\text{sec} = \tau$$

$$\tau = R_1 C_2 = 20 \mu\text{sec} = 20 \times 10^{-6}$$

For example,

$$\underline{C_2 = 0.01 \times 10^{-6} = 0.01 \mu\text{F} \Rightarrow R_1 = 2 \text{ k}\Omega}$$

E9.23

$$v_o = v_{I1} + 10v_{I2} - 25v_{I3} - 80v_{I4}$$

From Figure 9.37,  $v_{I3}$  input to  $R_1$ ,  $v_{I4}$  input to  $R_2$ ,  $v_{I1}$  input to  $R_A$ , and  $v_{I2}$  input to  $R_B$ .

From Equation (9.87)

$$\frac{R_F}{R_1} = 25 \text{ and } \frac{R_F}{R_2} = 80$$

Set  $R_F = 500 \text{ k}\Omega$ , then  $R_1 = 20 \text{ k}\Omega$ , and

$$R_2 = 6.25 \text{ k}\Omega.$$

$$\text{Also } \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_F}{R_A}\right) = 1$$

$$\text{and } \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_F}{R_B}\right) = 10$$

where  $R_N = R_1 \parallel R_2 = 20 \parallel 6.25 = 4.76 \text{ k}\Omega$

and  $R_F = R_A \parallel R_B \parallel R_C$

$$\text{We find that } \frac{R_A}{R_B} = 10$$

Let  $R_A = 200 \text{ k}\Omega$ ,  $R_B = 20 \text{ k}\Omega$

$$\text{Now } \left(1 + \frac{500}{4.76}\right) \left(\frac{R_F}{R_A}\right) = 1 = (106) \left(\frac{R_F}{200}\right)$$

Then  $R_F = 1.89 \text{ k}\Omega$

$$R_A \parallel R_B = 200 \parallel 20 = 18.2 \text{ k}\Omega$$

$$\text{So } R_F = 1.89 = \frac{18.2 R_C}{18.2 + R_C} \Rightarrow R_C = 2.11 \text{ k}\Omega$$

E9.25

$$\begin{aligned} v_{o1} &= \left[ \frac{R - \Delta R}{(R - \Delta R) + (R + \Delta R)} - \frac{R + \Delta R}{(R + \Delta R) + (R - \Delta R)} \right] V^+ \\ &= \left[ \frac{R - \Delta R}{2R} - \frac{R + \Delta R}{2R} \right] V^+ \\ &= \left( \frac{R - \Delta R - R - \Delta R}{2R} \right) V^+ \end{aligned}$$

$$v_{o1} = -\left(\frac{\Delta R}{R}\right) V^+$$

For  $V^+ = 3.5 \text{ V}$ ,  $\Delta R = 50$ ,  $R = 10 \times 10^3$

$$v_{o1} = -\left(\frac{50}{10^4}\right)(3.5) = -1.75 \times 10^{-2}$$

Need an amplifier with a gain of

$$A_d = \frac{v_o}{v_i} = \frac{5}{-1.75 \times 10^{-2}} \Rightarrow A_d = -285.7$$

Use instrumentation amplifier, Fig. 9-25.

Connect  $v_{o1}$  to  $v_{I1}$  and  $(-v_{o1})$  to  $v_{I2}$ .

$$|A_d| = \left(\frac{R_4}{R_3}\right) \left(1 + \frac{2R_2}{R_1}\right) = 285.7$$

Let  $R_4 = 150 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$  Then  $\frac{R_2}{R_1} = 9.02$

Let  $R_2 = 100 \text{ k}\Omega$ ,  $R_1 = 11.1 \text{ k}\Omega$

E9.26

$$\begin{aligned} v_{o1} &= \left[ \frac{1}{2} - \frac{R}{R + R(1 + \delta)} \right] V^+ \\ &= \left[ \frac{R + R(1 + \delta) - 2R}{2(R + R(1 + \delta))} \right] V^+ \\ &= \frac{R\delta}{2R(2 + \delta)} \times V^+ \end{aligned}$$

$$v_{o1} \approx \left(\frac{\delta}{4}\right) V^+$$

$$V^+ = 5 \text{ For } \delta = 0.01$$

$$v_{o1} = \left(\frac{0.01}{4}\right)(5) = 0.0125$$

Need a gain

$$A_d = \frac{v_o}{v_{o1}} = \frac{5}{0.0125} = 400$$

Use an instrumentation amplifier

$$A_d = 400 = \left(\frac{R_4}{R_3}\right) \left(1 + \frac{2R_2}{R_1}\right)$$

Let  $R_4 = 150 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , then  $\frac{R_2}{R_1} = 12.8$

Let  $R_2 = 150 \text{ k}\Omega$ ,  $R_1 = 11.7 \text{ k}\Omega$

## Chapter 9

## Problem Solutions

9.1

$$\left. \begin{aligned} A_v &= -\frac{200}{20} = -10 \\ \text{and} \\ R_i &= 20 \text{ k}\Omega \end{aligned} \right\} \text{for each case}$$

9.2

$$\text{a. } A_v = -\frac{100}{10} = -10$$

$$R_i = R_1 = 10 \text{ k}\Omega$$

$$\text{b. } A_v = -\frac{100 \parallel 100}{10} = -5$$

$$R_i = R_1 = 10 \text{ k}\Omega$$

$$\text{c. } A_v = -\frac{100}{10 \parallel 10} = -20$$

$$R_i = 10 \parallel 10 = 5 \text{ k}\Omega$$

9.3

$$A_v = -\frac{R_2}{R_1} = -12 \Rightarrow R_2 = 12R_1$$

$$R_i = R_1 = 25 \text{ k}\Omega$$

$$\Rightarrow R_2 = (12)(25) = 300 \text{ k}\Omega$$

9.4

$$A_v = -\frac{R_2}{R_1} = -8 \Rightarrow R_2 = 8R_1$$

$$\text{For } v_i = -1, i_1 = \frac{1}{R_1} = 15 \mu\text{A} \Rightarrow R_1 = 66.7 \text{ k}\Omega$$

$$\Rightarrow R_2 = 533.3 \text{ k}\Omega$$

9.5

$$A_v = -\frac{R_2}{R_1} = -30 \Rightarrow R_2 = 30R_1$$

$$\text{Set } R_2 = 1 \text{ M}\Omega$$

$$\Rightarrow R_1 = 33.3 \text{ k}\Omega$$

9.6

$$\text{a. } A_v = \frac{R_2}{R_1} \Rightarrow \frac{1.05R_2}{0.95R_1} = 1.105 \left( \frac{R_2}{R_1} \right)$$

$$\frac{0.95R_2}{1.05R_1} = 0.905 \left( \frac{R_2}{R_1} \right)$$

Deviation in gain is +10.5% and -9.5%

$$\text{b. } A_v \Rightarrow \frac{1.01R_2}{0.99R_1} = 1.02 \left( \frac{R_2}{R_1} \right)$$

$$\Rightarrow \frac{0.99R_2}{1.01R_1} = 0.98 \left( \frac{R_2}{R_1} \right)$$

Deviation in gain =  $\pm 2\%$ 

9.7

$$\text{(a) } A_v = \frac{v_o}{v_i} = \frac{-15}{1} = -15$$

$$v_o = -15v_i \Rightarrow v_o = -150 \sin \omega t \text{ (mV)}$$

$$\text{(b) } i_2 = i_1 = \frac{v_i}{R_1} = 10 \sin \omega t \text{ (}\mu\text{A)}$$

$$i_L = \frac{v_o}{R_L} \Rightarrow i_L = -37.5 \sin \omega t \text{ (}\mu\text{A)}$$

$$i_o = i_L - i_2$$

$$i_o = -47.5 \sin \omega t \text{ (}\mu\text{A)}$$

9.8

$$A_v = -\frac{R_2}{R_1 + R_3}$$

$$A_v = -30 \pm 2.5\% \Rightarrow 29.25 \leq |A_v| \leq 30.75$$

$$\text{So } \frac{R_2}{R_1 + 2} = 29.25 \text{ and } \frac{R_2}{R_1 + 1} = 30.75$$

$$\text{We have } 29.25(R_1 + 2) = 30.75(R_1 + 1)$$

$$\text{Which yields } R_1 = 18.5 \text{ k}\Omega \text{ and } R_2 = 599.6 \text{ k}\Omega$$

For  $v_i = 25 \text{ mV}$ , then

$$0.731 \leq |v_o| \leq 0.769 \text{ V}$$

9.9

$$v_{o1} = -\left(\frac{50}{10}\right)v_i = (-5)(0.15) \Rightarrow v_{o1} = -0.75 \text{ V}$$

$$v_o = -\frac{150}{25} \cdot v_{o1} = (-6)(-0.75) \Rightarrow v_o = 4.5 \text{ V}$$

$$i_1 = i_2 = \frac{0.15}{10} \Rightarrow i_1 = i_2 = 15 \mu\text{A}$$

$$i_3 = i_4 = \frac{v_{o1}}{R_3} = -\frac{0.75}{25} \Rightarrow i_3 = i_4 = -30 \mu\text{A}$$

First op-amp must sink  $15 + 30 = 45 \mu\text{A}$

9.10

$$(a) A_v = -\frac{R_2}{R_1} = -\frac{22}{1} \Rightarrow A_v = -22$$

$$(b) A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)\right]}$$

$$= -\frac{22}{1} \cdot \frac{1}{\left[1 + \frac{1}{15 \times 10^5} \left(1 + \frac{22}{1}\right)\right]} = -\frac{22}{1} \cdot \frac{1}{1.000153} \Rightarrow$$

$$A_v = -21.99663$$

$$(c) |A_v| = 22 - 1\% = 22 - 0.22 = 21.78$$

$$\text{Then } 21.78 = \frac{22}{1} \cdot \frac{1}{\left[1 + \frac{1}{A_{od}} (23)\right]} \Rightarrow A_{od} = 2277$$

9.11

$$A_v = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$$

$$a. -10 = -\frac{R_2}{100} \left(1 + \frac{100}{100} + \frac{100}{R_2}\right)$$

$$10 = \frac{2R_2}{100} + 1 \Rightarrow R_2 = 450 \text{ k}\Omega$$

$$b. 100 = \frac{2R_2}{100} + 1 \Rightarrow R_2 = 4.95 \text{ M}\Omega$$

9.12

$$a. A_v = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$$

$$R_1 = 500 \text{ k}\Omega$$

$$80 = \frac{R_2}{500} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$$

$$\text{Set } R_2 = R_3 = 500 \text{ k}\Omega$$

$$80 = 1 \left(1 + \frac{500}{R_4} + 1\right) = 2 + \frac{500}{R_4}$$

$$\Rightarrow R_4 = 6.41 \text{ k}\Omega$$

$$b. \text{ For } v_i = -0.05 \text{ V}$$

$$i_1 = i_2 = \frac{-0.05}{500 \text{ k}\Omega} \Rightarrow i_1 = i_2 = -0.1 \mu\text{A}$$


$$v_x = -i_2 R_2 = -(-0.1 \times 10^{-6})(500 \times 10^3)$$

$$= 0.05$$

$$i_4 = -\frac{v_x}{R_4} = -\frac{0.05}{6.41} \Rightarrow i_4 = -7.80 \mu\text{A}$$

$$i_3 = i_2 + i_4 = -0.1 - 7.80 \Rightarrow i_3 = -7.90 \mu\text{A}$$

9.13

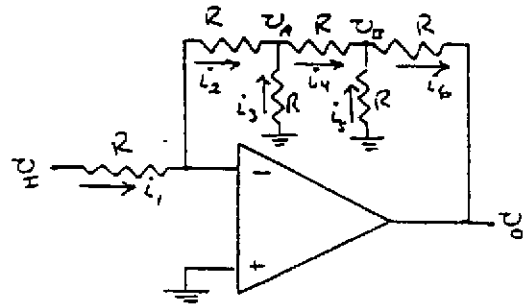

$$i_1 = \frac{v_i}{R} = i_2$$

$$v_A = -i_2 R = -\left(\frac{v_i}{R}\right) R = -v_i$$

$$i_3 = -\frac{v_A}{R} = \frac{v_i}{R}$$

$$i_4 = i_2 + i_3 = -\frac{v_i}{R} - \frac{v_i}{R} = -\frac{2v_i}{R} = \frac{2v_i}{R}$$

$$v_B = v_A - i_4 R = -v_i - \left(\frac{2v_i}{R}\right) R = -3v_i$$

$$i_5 = -\frac{v_B}{R} = -\frac{(-3v_i)}{R} = \frac{3v_i}{R}$$

$$i_6 = i_4 + i_5 = \frac{2v_i}{R} + \frac{3v_i}{R} = \frac{5v_i}{R}$$

$$v_o = v_B - i_6 R = -3v_i - \left(\frac{5v_i}{R}\right) R$$

$$\Rightarrow \frac{v_o}{v_i} = -8$$

$$\text{From Figure 9.11} \Rightarrow A_v = -3$$

9.14

$$(a) A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)\right]}$$

$$= -\frac{50}{10} \cdot \frac{1}{\left[1 + \frac{1}{2 \times 10^5} \left(1 + \frac{50}{10}\right)\right]} \Rightarrow A_v = -4.99985$$

$$(b) v_o = -(4.99985)(100 \times 10^{-3}) \Rightarrow$$

$$v_o = -499.985 \text{ mV}$$

$$(c) \text{ Error} = \frac{0.5 - 0.499985}{0.5} \times 100\% \Rightarrow 0.003\%$$

9.15

a. From Equation (9.23)


$$A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)\right]}$$

$$= -\frac{100}{100} \cdot \frac{1}{\left[1 + \frac{1}{10^3} \left(1 + \frac{100}{100}\right)\right]} = -0.9980$$

Then  $v_o = A_v \cdot v_i = (-0.9980)(2)$ 

$$\Rightarrow \underline{v_o = -1.9960}$$

b.

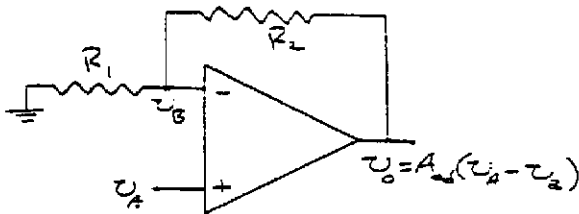

$$v_o = A_{od}(v_A - v_B)$$

$$\frac{v_B}{R_1} = \frac{v_o - v_B}{R_2} \Rightarrow v_B \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}$$

$$v_B = \frac{v_o}{\left(1 + \frac{R_2}{R_1}\right)}$$

$$\text{Then } v_o = A_{od}v_A - \frac{A_{od}v_o}{\left(1 + \frac{R_2}{R_1}\right)}$$

$$v_o \left[ 1 + \frac{A_{od}}{\left(1 + \frac{R_2}{R_1}\right)} \right] = A_{od}v_A$$

$$v_o \left[ \frac{\left(1 + \frac{R_2}{R_1}\right) + A_{od}}{\left(1 + \frac{R_2}{R_1}\right)} \right] = A_{od}v_A$$

$$v_o = \frac{A_{od} \left(1 + \frac{R_2}{R_1}\right) v_A}{A_{od} + \left(1 + \frac{R_2}{R_1}\right)}$$

$$v_o = \frac{\left(1 + \frac{R_2}{R_1}\right) v_A}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)}$$

So

$$v_o = \frac{\left(1 + \frac{10}{10}\right) \left(\frac{v_i}{2}\right)}{1 + \frac{1}{10^3} \left(1 + \frac{10}{10}\right)} = 0.9980 v_i$$

For  $v_i = 2 \text{ V}$ 

$$\underline{v_o = 1.9960 \text{ V}}$$

9.16

$$(a) i_i = \frac{v_i}{R_i} = i_2 = -\frac{v_o}{R_2} \Rightarrow \frac{v_o}{v_i} = -\frac{R_2}{R_i}$$

$$(b) i_2 = i_1 = \frac{v_i}{R_i} = i_3 + \frac{v_o}{R_L} = i_3 + \frac{1}{R_L} \left( -\frac{R_2}{R_i} \cdot v_i \right)$$

$$\text{Then } i_3 = \frac{v_i}{R_i} \left( 1 + \frac{R_2}{R_L} \right)$$

9.17

$$V_{x,\max} = \left( \frac{R_3 \parallel R_i}{R_3 \parallel R_i + R_4} \right) \cdot V^* = \left( \frac{0.1 \parallel 1}{0.1 \parallel 1 + 10} \right) (10) \Rightarrow$$

$$V_{x,\max} = 0.09008 \text{ V}$$

$$|v_o| = \frac{R_2}{R_i} \cdot V_{x,\max}$$

$$10 = \frac{R_2}{R_i} (0.09008) \Rightarrow \frac{R_2}{R_i} = 111$$

$$\text{So } \underline{R_2 = 111 \text{ k}\Omega}$$

9.18

$$v_o = A_{od}(v_2 - v_1)$$

$$a. A_{od} = \frac{1}{[1 - (-1)] \times 10^{-3}} \Rightarrow \underline{A_{od} = 500}$$

$$b. 1 = 500(v_2 - 1 \times 10^{-3}) \Rightarrow \underline{v_2 = 3 \text{ mV}}$$

$$c. 5 = 500(1 - v_1) \Rightarrow \underline{v_1 = 0.99 \text{ V}}$$

$$d. v_o = 500(-1 - (-1)) \Rightarrow \underline{v_o = 0}$$

$$e. -3 = 500(v_2 - (-0.5)) \Rightarrow \underline{v_2 = -0.506 \text{ V}}$$

9.19

$$a. v_o = -\frac{R_F}{R_1} \cdot v_{I1} - \frac{R_F}{R_2} \cdot v_{I2} - \frac{R_F}{R_3} \cdot v_{I3}$$

$$v_o = -\frac{80}{20}(0.5) - \frac{80}{40}(-1) - \frac{80}{60}(2)$$

$$= -4(0.5) - 2(-1) - 1.33(2)$$

$$\underline{v_o = -2.667 \text{ V}}$$

$$b. -5.2 = -4(1) - 2(0.25) - 1.33v_{I3}$$

$$\underline{v_{I3} = 0.525}$$



9.20

$$\begin{aligned} v_o &= -8v_{I1} - 2v_{I2} - 5v_{I3} \\ &= -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} - \frac{R_F}{R_3}v_{I3} \\ \frac{R_F}{R_1} &= 8 \quad \frac{R_F}{R_2} = 2 \quad \frac{R_F}{R_3} = 5 \end{aligned}$$

$$\begin{aligned} \text{Let } R_F &= 500 \text{ k}\Omega \Rightarrow R_1 = 62.5 \text{ k}\Omega \\ R_2 &= 250 \text{ k}\Omega \\ R_3 &= 100 \text{ k}\Omega \end{aligned}$$


9.21

$$\begin{aligned} v_o &= -4v_{I1} - 0.5v_{I2} = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} \\ \frac{R_F}{R_1} &= 4 \quad \frac{R_F}{R_2} = 0.5 \\ \Rightarrow R_1 &\text{ is the smallest resistor} \end{aligned}$$

$$\begin{aligned} |i| &= 100 \mu\text{A} = \frac{v_I}{R_1} = \frac{2}{R_1} \Rightarrow \underline{R_1 = 20 \text{ k}\Omega} \\ &\Rightarrow \underline{R_F = 80 \text{ k}\Omega} \\ &\Rightarrow \underline{R_2 = 160 \text{ k}\Omega} \end{aligned}$$

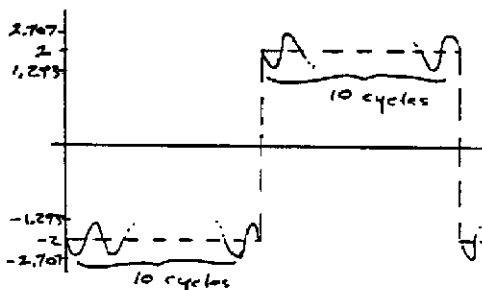9.22

$$\begin{aligned} v_{I1} &= (0.05)\sqrt{2} \sin(2\pi ft) = 0.0707 \sin(2\pi ft) \\ f &= 1 \text{ kHz} \Rightarrow T = \frac{1}{10^3} \Rightarrow 1 \text{ ms} \\ v_{I2} &\Rightarrow T_2 = \frac{1}{100} \Rightarrow 10 \text{ ms} \\ v_o &= -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} = -\frac{10}{1}v_{I1} - \frac{10}{5}v_{I2} \\ v_o &= -(10)(0.0707 \sin(2\pi ft)) - (2)(\pm 1 \text{ V}) \\ v_o &= -0.707 \sin(2\pi ft) - (\pm 2 \text{ V}) \end{aligned}$$



9.23

$$\begin{aligned} v_o &= -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} - \frac{R_F}{R_3}v_{I3} \\ v_o &= -\frac{20}{10}v_{I1} - \frac{20}{5}v_{I2} - \frac{20}{2}v_{I3} \\ K \sin \alpha &= -2v_{I1} - 4[2 + 100 \sin \alpha] - 0 \\ \text{Set } v_{I1} &= -4 \end{aligned}$$

9.24

a.

$$v_o = -\frac{R_F}{R_3} \cdot a_3(-5) - \frac{R_F}{R_2} \cdot a_2(-5) - \frac{R_F}{R_1} \cdot a_1(-5) - \frac{R_F}{R_0} \cdot a_0(-5)$$

$$\text{So } v_o = \frac{R_F}{10} \left[ \frac{a_3}{2} + \frac{a_2}{4} + \frac{a_1}{8} + \frac{a_0}{16} \right] (5)$$

$$\text{b. } v_o = 2.5 = \frac{R_F}{10} \cdot \frac{1}{2} \cdot 5 \Rightarrow \underline{R_F = 10 \text{ k}\Omega}$$

$$\text{c. i. } v_o = \frac{10}{10} \cdot \frac{1}{16} \cdot 5 \Rightarrow v_o = 0.3125 \text{ V}$$

$$\begin{aligned} \text{ii. } v_o &= \frac{10}{10} \left[ \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right] (5) \\ &\Rightarrow \underline{v_o = 4.6875 \text{ V}} \end{aligned}$$

9.25

$$\text{(a) } v_{o1} = -\frac{10}{1}v_{I1}$$

$$\begin{aligned} v_o &= -\frac{20}{1}v_{o1} - \frac{20}{1}v_{I2} = -(20)(-10)v_{I1} - (20)v_{I2} \\ v_o &= 200v_{I1} - 20v_{I2} \end{aligned}$$

$$\text{(b) } v_{I1} = 1 + 2 \sin \alpha \text{ (mV)}$$


$$v_{I2} = -10 \text{ mV}$$

$$\text{Then } v_o = 200(1 + 2 \sin \alpha) - 20(-10)$$

$$\text{So } v_o = 0.4 + 0.4 \sin \alpha \text{ (V)}$$

9.26

For one-input

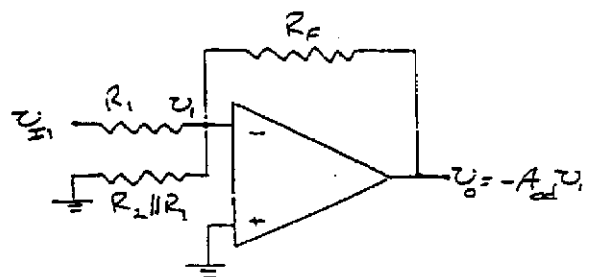

$$v_1 = -\frac{v_o}{A_{od}}$$

$$\frac{v_{I1} - v_1}{R_1} = \frac{v_1}{R_2 \parallel R_3} + \frac{v_1 - v_o}{R_F}$$

$$\begin{aligned} \frac{v_{I1}}{R_1} &= v_1 \left[ \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} + \frac{1}{R_F} \right] - \frac{v_o}{R_F} \\ &= -\frac{v_o}{A_{od}} \left[ \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} + \frac{1}{R_F} \right] - \frac{v_o}{R_F} \\ &= -v_o \left\{ \frac{1}{A_{od} R_F} + \frac{1}{R_F} + \frac{1}{A_{od}} \left( \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} \right) \right\} \\ &= -\frac{v_o}{R_F} \left\{ \frac{1}{A_{od}} + 1 + \frac{1}{A_{od}} \cdot \frac{R_F}{R_1 \parallel R_2 \parallel R_3} \right\} \end{aligned}$$

$$v_o = -\frac{R_F}{R_1} \cdot v_{I1} \cdot \left\{ \frac{1}{1 + \frac{1}{A_{od}} \left( 1 + \frac{R_F}{R_P} \right)} \right\}$$

where  $R_P = R_1 \parallel R_2 \parallel R_3$

Therefore, for three-inputs

$$v_o = \frac{-1}{1 + \frac{1}{A_{od}} \left( 1 + \frac{R_F}{R_P} \right)} \times \left( \frac{R_F}{R_1} \cdot v_{I1} + \frac{R_F}{R_2} \cdot v_{I2} + \frac{R_F}{R_3} \cdot v_{I3} \right)$$

9.27


$$A_v = \left( 1 + \frac{R_2}{R_1} \right) = 10$$

$$\frac{R_2}{R_1} = 9$$

$$|i| = \frac{v_I}{R_1} = \frac{0.8}{R_1} = 100 \mu A$$

$$\Rightarrow R_1 = 8 \text{ k}\Omega, R_2 = 72 \text{ k}\Omega$$

9.28

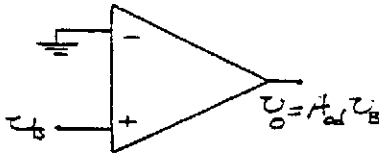

$$v_B = \left( \frac{1}{1 + 500} \right) v_I, \quad v_o = A_{od} \left( \frac{1}{501} \right) v_I$$

$$\text{a. } 2.5 = A_{od} \left( \frac{1}{501} \right) (5) \Rightarrow A_{od} = 250.5$$

$$\text{b. } v_o = 5000 \left( \frac{1}{501} \right) (5) \Rightarrow v_o = 49.9 \text{ V}$$

9.29

$$v_o = \left( 1 + \frac{50}{50} \right) \left[ \left( \frac{20}{20 + 40} \right) v_{I2} + \left( \frac{40}{20 + 40} \right) v_{I1} \right]$$

$$v_o = 1.33 v_{I1} + 0.667 v_{I2}$$


9.30

$$v_o = \left( 1 + \frac{100}{50} \right) \times \left[ \left( \frac{10 \parallel 40}{10 \parallel 40 + 20} \right) v_{I1} + \left( \frac{10 \parallel 20}{10 \parallel 20 + 40} \right) v_{I2} \right]$$

$$v_o = 3 \left[ \left( \frac{8}{8 + 20} \right) v_{I1} + \left( \frac{6.67}{6.67 + 40} \right) v_{I2} \right]$$

$$v_o = 0.857 v_{I1} + 0.429 v_{I2}$$

9.31

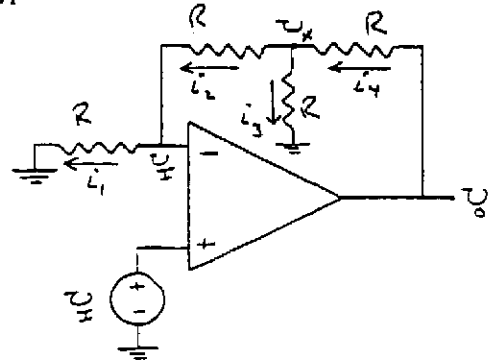

$$i_1 = \frac{v_I}{R} = i_2$$

$$v_X = i_2 R + v_I = \left( \frac{v_I}{R} \right) R + v_I = 2v_I$$

$$i_3 = \frac{v_X}{R} = \frac{2v_I}{R}$$

$$i_4 = i_2 + i_3 = \frac{v_I}{R} + \frac{2v_I}{R} = \frac{3v_I}{R}$$

$$v_o = i_4 R + v_X = \left( \frac{3v_I}{R} \right) R + 2v_I$$

$$\frac{v_o}{v_I} = 5$$

9.32

$$\text{(a) } \frac{v_o}{v_I} = 1$$

(b) From Exercise 9.11


$$\frac{v_o}{v_I} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{\left[ 1 + \frac{1}{A_{od}} \left( 1 + \frac{R_2}{R_1} \right) \right]}$$

But  $R_2 = 0, R_1 = \infty$

$$\frac{v_o}{v_I} = \frac{1}{1 + \frac{1}{A_{od}}} = \frac{1}{1 + \frac{1}{1.5 \times 10^5}} \Rightarrow \frac{v_o}{v_I} = 0.99999$$

$$\text{(b) Want } \frac{v_o}{v_I} = 0.990 = \frac{1}{1 + \frac{1}{A_{od}}} \Rightarrow A_{od} = 99$$

9.33

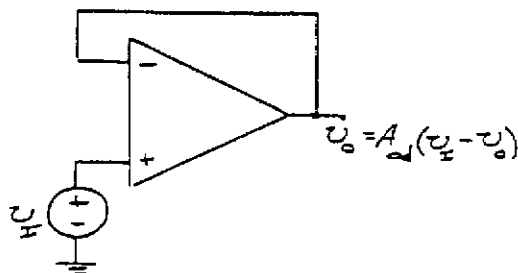

$$v_O = A_{od}(v_I - v_O)$$

$$\left(\frac{1}{A_{od}} + 1\right)v_O = v_I$$

$$v_O = \frac{v_I}{\left(1 + \frac{1}{A_{od}}\right)}$$

$$A_{od} = 10^4; \quad \frac{v_O}{v_I} = 0.99990$$

$$A_{od} = 10^3; \quad \frac{v_O}{v_I} = 0.9990$$

$$A_{od} = 10^2; \quad \frac{v_O}{v_I} = 0.990$$

$$A_{od} = 10; \quad \frac{v_O}{v_I} = 0.909$$

9.34

$$v_{O1} = \left(1 + \frac{R_2}{R_1}\right)v_I$$

$$v_{O1} = \left(1 + \frac{R_2}{R_1}\right)v_I, \quad v_{O2} = -\left(1 + \frac{R_2}{R_1}\right)v_I$$

$$\text{So } v_{O1} = -v_{O2}$$

9.35

$$(a) \quad i_L = \frac{v_I}{R_1}$$

$$(b) \quad v_{O1} = i_L R_L + v_I = i_L R_L + i_L R_1$$

$$v_{O1}(\max) \cong 8V = i_L(1+9) = 10i_L$$

$$\text{So } i_L(\max) \cong 0.8 \text{ mA}$$

$$\text{Then } v_I(\max) \cong i_L R_1 = (0.8)(9) \Rightarrow v_I(\max) \cong 7.2V$$

9.36

$$(a) \quad v_x = \left(\frac{20}{20+40}\right) \cdot v_I = \left(\frac{20}{60}\right)(6) = 2$$

$$v_O = 2V$$

(b) Same as (a)

$$(c) \quad v_x = \left(\frac{6}{6+48}\right)(6) = 0.666V$$

$$v_O = \left(1 + \frac{10}{10}\right) \cdot v_x \Rightarrow v_O = 1.33V$$

9.37

$$a. \quad R_{in} = \frac{v_I}{i_1} \text{ and } \frac{v_I - v_O}{R_F} = i_1 \text{ and } v_O = -A_{od}v_I$$

$$\text{So } i_1 = \frac{v_I - (-A_{od}v_I)}{R_F} = \frac{v_I(1 + A_{od})}{R_F}$$

$$\text{Then } R_{in} = \frac{v_I}{i_1} = \frac{R_F}{1 + A_{od}}$$

$$b. \quad i_1 = \left(\frac{R_S}{R_S + R_{in}}\right)i_S \text{ and } v_O = -A_{od} \cdot \frac{R_F}{1 + A_{od}} \cdot i_1$$

$$\text{So } v_O = -R_F \left(\frac{A_{od}}{1 + A_{od}}\right) \left(\frac{R_S}{R_S + R_{in}}\right)i_S$$


$$R_{in} = \frac{R_F}{1 + A_{od}} = \frac{10}{1001} = 0.009990$$

$$v_O = -R_F \left(\frac{1000}{1001}\right) \left(\frac{R_S}{R_S + 0.009990}\right)i_S$$

$$\text{Want } \left(\frac{1000}{1001}\right) \left(\frac{R_S}{R_S + 0.009990}\right) \geq 0.990$$

$$\text{which yields } R_S \geq 1.099 \text{ k}\Omega$$

9.38

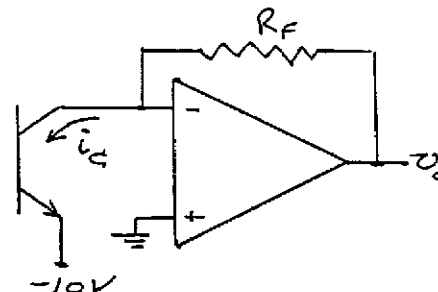

$$v_O = i_C R_F, \quad 0 \leq i_C \leq 8 \text{ mA}$$

$$\text{For } v_O(\max) = 8V, \text{ Then}$$

$$R_F = 1 \text{ k}\Omega$$

9.39

$$i = \frac{v_I}{R} \text{ so } 1 = \frac{10}{R} \Rightarrow R = 10 \text{ k}\Omega$$

In the ideal op-amp,  $R_1$  has no influence.

$$\text{Output voltage: } v_O = \left(1 + \frac{R_2}{R}\right)v_I$$

$v_O$  must remain within the bias voltages of the op-amp; the larger the  $R_2$ , the smaller the range of input voltage  $v_I$  in which the output is valid.

9.40

$$i_L = \frac{-v_I}{R_2} \Rightarrow 10 = -\frac{(-10)}{R_2} \Rightarrow R_2 = 1 \text{ k}\Omega$$

$$i_4 = \frac{v_L}{R_2} \text{ and } v_L = i_L Z_L = (0.010)(100) = 1 \text{ V}$$

$$i_4 = \frac{1}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$i_3 = i_4 + i_L = 1 + 10 = 11 \text{ mA}$$

$$\text{For } v_O(\text{max}) \approx 12 \text{ V} = i_3 R_3 + v_L = (11)R_3 + 1$$

$$\Rightarrow R_3 = 1 \text{ k}\Omega$$

We need

$$\frac{R_3}{R_2} = \frac{R_F}{R_1} = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega} \Rightarrow R_1 = R_F$$

9.41

$$(a) i_1 = i_2 \text{ and } i_2 = \frac{v_x}{R_2} + i_D, \quad v_x = -i_2 R_F$$

$$\text{Then } i_1 = -i_2 \left( \frac{R_F}{R_2} \right) + i_D$$

$$\text{Or } i_D = i_1 \left( 1 + \frac{R_F}{R_2} \right)$$

$$(b) R_1 = \frac{v_I}{i_1} = \frac{5}{1} \Rightarrow R_1 = 5 \text{ k}\Omega$$

$$12 = (1) \left( 1 + \frac{R_F}{R_2} \right) \Rightarrow \frac{R_F}{R_2} = 11$$

$$\text{For example, } R_2 = 5 \text{ k}\Omega, \quad R_F = 55 \text{ k}\Omega$$

9.42

$$(1) I_x = \frac{V_x}{R_2} + \frac{V_x - v_O}{R_3}$$

$$(2) \frac{V_x}{R_1} + \frac{V_x - v_O}{R_F} = 0$$

$$\text{From (2) } v_O = V_x \left( 1 + \frac{R_F}{R_1} \right)$$

$$\text{Then (1) } I_x = V_x \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_3} V_x \left( 1 + \frac{R_F}{R_1} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_2} + \frac{1}{R_3} - \frac{1}{R_3} - \frac{R_F}{R_1 R_3} = \frac{1}{R_2} - \frac{R_F}{R_1 R_3}$$

$$= \frac{R_1 R_3 - R_2 R_F}{R_1 R_2 R_3}$$

or

$$R_o = \frac{R_1 R_2 R_3}{R_1 R_3 - R_2 R_F}$$

$$\text{Note: If } \frac{R_F}{R_1 R_3} = \frac{1}{R_2} \Rightarrow R_2 R_F = R_1 R_3$$

then  $R_o = \infty$ , which corresponds to an ideal current source.

9.43

$$A_d = \frac{R_2}{R_1} = \frac{R_4}{R_3} = 5$$

Minimum resistance seen by  $v_{I1}$  is  $R_1$ .

$$\text{Set } R_1 = R_3 = 25 \text{ k}\Omega \text{ Then } R_2 = R_4 = 125 \text{ k}\Omega$$

$$i_L = \frac{v_O}{R_L} \Rightarrow v_O = i_L R_L = (0.5)(5) = 2.5 \text{ V}$$

$$v_O = 5(v_{I2} - v_{I1})$$

$$2.5 = 5(v_{I2} - 2) \Rightarrow v_{I2} = 2.5 \text{ V}$$

9.44

a. From superposition:

$$v_{O1} = -\frac{R_2}{R_1} v_{I1}$$

$$v_{O2} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) v_{I2}$$

$$\text{Setting } v_{I1} = v_{I2} = v_{cm}$$

$$v_O = v_{O1} + v_{O2} = \left[ \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{1 + \frac{R_3}{R_4}} \right) - \frac{R_2}{R_1} \right] v_{cm}$$

$$A_{cm} = \frac{v_O}{v_{cm}} = \frac{R_4}{R_3} \cdot \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{1 + \frac{R_3}{R_4}} \right) - \frac{R_2}{R_1}$$

$$= \frac{\frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_3} \right)}{\left( 1 + \frac{R_4}{R_3} \right)}$$


$$A_{cm} = \frac{\frac{R_4}{R_3} - \frac{R_2}{R_1}}{\left( 1 + \frac{R_4}{R_3} \right)}$$

$$b. \text{ Max } |A_{cm}| \Rightarrow \text{Min } \frac{R_4}{R_3} \text{ and Max } \frac{R_2}{R_1}$$

$$\text{Max } |A_{cm}| = \frac{\frac{47.5}{10.5} - \frac{52.5}{9.5}}{1 + \frac{47.5}{10.5}} = \frac{4.5238 - 5.5263}{1 + 4.5238}$$

$$\Rightarrow |A_{cm}|_{\text{max}} = 0.1815$$

9.45

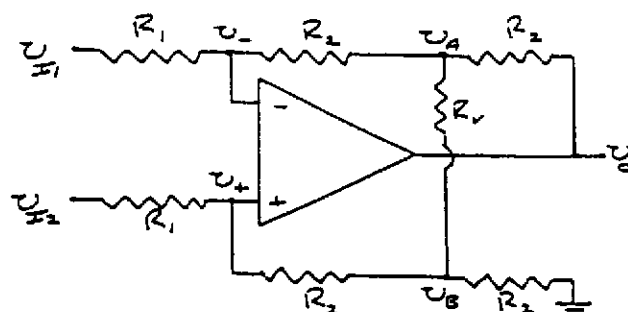

$$\frac{v_{I1} - v_A}{R_1 + R_2} = \frac{v_A - v_B}{R_V} + \frac{v_A - v_0}{R_2} \quad (1) \quad 9.46$$

$$\frac{v_{I2} - v_B}{R_1 + R_2} = \frac{v_B - v_A}{R_V} + \frac{v_B}{R_2} \quad (2)$$

$$v_- = \left( \frac{R_1}{R_1 + R_2} \right) v_A + \left( \frac{R_2}{R_1 + R_2} \right) v_{I1} \quad (3)$$

$$v_+ = \left( \frac{R_1}{R_1 + R_2} \right) v_B + \left( \frac{R_2}{R_1 + R_2} \right) v_{I2} \quad (4)$$

$$\text{Now } v_- = v_+ \Rightarrow R_1 v_A + R_2 v_{I1} = R_1 v_B + R_2 v_{I2}$$

$$\text{So that } v_A = v_B + \frac{R_2}{R_1} (v_{I2} - v_{I1})$$

$$\frac{v_{I1}}{R_1 + R_2} = v_A \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_B}{R_V} - \frac{v_0}{R_2} \quad (1)$$

$$\frac{v_{I2}}{R_1 + R_2} = v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_A}{R_V} \quad (2)$$

Then

$$\frac{v_{I1}}{R_1 + R_2} \quad (1)$$

$$= v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_B}{R_V} - \frac{v_0}{R_2} + \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) (v_{I2} - v_{I1})$$

$$\frac{v_{I1}}{R_1 + R_2} = v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{1}{R_V} \left[ v_B + \frac{R_2}{R_1} (v_{I2} - v_{I1}) \right] \quad (2)$$

Substitute (1)-(2)

$$\begin{aligned} & \frac{1}{R_1 + R_2} (v_{I1} - v_{I2}) \\ &= \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) (v_{I2} - v_{I1}) \\ & \quad - \frac{v_0}{R_2} + \frac{1}{R_V} \cdot \frac{R_2}{R_1} (v_{I2} - v_{I1}) \end{aligned}$$

$$\frac{v_0}{R_2} = (v_{I2} - v_{I1}) \left\{ \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) + \frac{1}{R_1 + R_2} + \frac{1}{R_V} \cdot \frac{R_2}{R_1} \right\}$$

$$v_0 = (v_{I2} - v_{I1}) \left( \frac{R_2}{R_1} \right) \left\{ \frac{R_2}{R_1 + R_2} + \frac{R_2}{R_V} + 1 + \frac{R_1}{R_1 + R_2} + \frac{R_2}{R_V} \right\}$$

$$v_0 = \frac{2R_2}{R_1} \left( 1 + \frac{R_2}{R_V} \right) (v_{I2} - v_{I1})$$

$$\begin{aligned} v_{01} &= \left( 1 + \frac{R_2}{R_1} \right) v_{I1} - \frac{R_2}{R_1} v_{I2} \\ &= \left( 1 + \frac{50}{10} \right) (-25 \sin \omega t) - \frac{50}{10} (25 \sin \omega t) \\ v_{01} &= -275 \sin \omega t \text{ mV} \end{aligned}$$

$$\begin{aligned} v_{02} &= \left( 1 + \frac{R_2}{R_1} \right) v_{I2} - \frac{R_2}{R_1} v_{I1} \\ &= \left( 1 + \frac{50}{10} \right) (25 \sin \omega t) - \frac{50}{10} (-25 \sin \omega t) \\ v_{02} &= 275 \sin \omega t \text{ mV} \end{aligned}$$

$$\begin{aligned} v_0 &= \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1}) \\ &= \frac{30}{20} \left( 1 + 2 \left[ \frac{50}{10} \right] \right) (25 - [-25]) \sin \omega t \\ v_0 &= 825 \sin \omega t \text{ mV} \end{aligned}$$

Current in  $R_1$  and  $R_2$ :

$$\begin{aligned} i_1 &= \frac{v_{I1} - v_{I2}}{R_1} = \frac{(-25 - 25) \sin \omega t \text{ mV}}{10 \text{ k}\Omega} \\ |i_1| &= 5 \sin \omega t \text{ }\mu\text{A} \end{aligned}$$

Current in bottom  $R_3$  and  $R_4$ :

$$\begin{aligned} i_3 &= \frac{v_{02}}{R_3 + R_4} = \frac{275 \sin \omega t \text{ mV}}{(20 + 30) \text{ k}\Omega} \\ |i_3| &= 5.5 \sin \omega t \text{ }\mu\text{A} \end{aligned}$$

Current in top  $R_3$  and  $R_4$ :

$$\begin{aligned} i'_3 &= \frac{v_{01} - \left( \frac{R_4}{R_3 + R_4} \right) v_{02}}{R_3} \\ &= \frac{\left[ -275 - \left( \frac{30}{30 + 20} \right) (275) \right] \sin \omega t \text{ mV}}{20 \text{ k}\Omega} \\ |i'_3| &= 22 \sin \omega t \text{ }\mu\text{A} \end{aligned}$$

9.47

$$\begin{aligned} v_0 &= \frac{30}{20} \left( 1 + \frac{2(50)}{R_1} \right) (25 - (-25)) \sin \omega t \text{ mV} \\ |v_0| &= (1.5)(50) \left( 1 + \frac{100}{R_1} \right) \text{ mV} \end{aligned}$$

For

$$\begin{aligned} |v_0| &= 0.1 \text{ V} = (1.5)(0.050) \left( 1 + \frac{100}{R_1} \right) \\ \Rightarrow R_1 &= 300 \text{ k}\Omega \end{aligned}$$

For

$$|v_o| = 5 \text{ V} = (1.5)(0.050) \left(1 + \frac{100}{R_1}\right)$$

$$\Rightarrow R_1 = 1.52 \text{ k}\Omega$$

$$\text{So } R_{1f} = 1.52 \text{ k}\Omega \Rightarrow \text{Potentiometer} \approx 300 \text{ k}\Omega$$

9.48

$$A_d = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right)$$

$$\text{For } A_d(\text{max}), R_1 = R_1(\text{min}) = R_{1f}$$

$$200 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_{1f}}\right)$$

$$\text{For } A_d(\text{min}), R_1 = R_1(\text{max}) \approx 50 \text{ k}\Omega$$

$$0.5 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{50}\right)$$

$$\text{Let } \frac{R_4}{R_3} = 0.4$$

$$\text{Then } 0.5 = 0.4 \left(1 + \frac{2R_2}{50}\right) \Rightarrow R_2 = 6.25 \text{ k}\Omega$$

and

$$200 = (0.4) \left(1 + \frac{2(6.25)}{R_{1f}}\right) \Rightarrow R_{1f} = 25.05 \text{ }\Omega$$

9.49

For a common-mode gain,  $v_{cm} = v_{I1} = v_{I2}$ 

Then

$$v_{O1} = \left(1 + \frac{R_2}{R_1}\right)v_{cm} - \frac{R_2}{R_1}v_{cm} = v_{cm}$$

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right)v_{cm} - \frac{R_2}{R_1}v_{cm} = v_{cm}$$

From Problem 9.41, we can write

$$A_{cm} = \frac{\frac{R_4}{R_3} - \frac{R_4}{R_3'}}{\left(1 + \frac{R_4}{R_3}\right)}$$

$$R_3 = R_4 = 20 \text{ k}\Omega, R_3' = 20 \text{ k}\Omega \pm 5\%$$

$$A_{cm} = \frac{1 - \frac{20}{R_3'}}{(1 + 1)} = \frac{1}{2} \left(1 - \frac{20}{R_3'}\right)$$

$$\text{For } R_3' = 20 \text{ k}\Omega - 5\% = 19 \text{ k}\Omega$$

$$A_{cm} = \frac{1}{2} \left(1 - \frac{20}{19}\right) = -0.0263$$

$$\text{For } R_3' = 20 \text{ k}\Omega + 5\% = 21 \text{ k}\Omega$$

$$A_{cm} = \frac{1}{2} \left(1 - \frac{20}{21}\right) = 0.0238$$

$$\text{So } |A_{cm}|_{\text{max}} = 0.0263$$

9.50

$$\text{a. } v_o = \frac{1}{R_1 C_2} \int v_I(t') dt'$$

$$\int 0.5 \sin \omega t dt = -\frac{0.5}{\omega} \cos \omega t$$

$$|v_o| = 0.5 = \frac{1}{R_1 C_2} \cdot \frac{(0.5)}{\omega} = \frac{0.5}{2\pi R_1 C_2 f}$$

$$f = \frac{1}{2\pi R_1 C_2} = \frac{1}{2\pi (50 \times 10^3)(0.1 \times 10^{-6})}$$

$$\Rightarrow f = 31.8 \text{ Hz}$$

Output signal lags input signal by  $90^\circ$ 

$$\text{b. i. } f = \frac{0.5}{2\pi (50 \times 10^3)(0.1 \times 10^{-6})} \Rightarrow f = 15.9 \text{ Hz}$$

$$\text{ii. } f = \frac{0.5}{(0.1)(2\pi)(50 \times 10^3)(0.1 \times 10^{-6})}$$

$$\Rightarrow f = 159 \text{ Hz}$$

9.51

$$\text{(a) } v_o = -\frac{1}{RC} \int v_I(t') dt'$$

$$v_o = -\frac{1}{0.2} (0.5)(2) \Rightarrow v_o = -5 \text{ V}$$

$$\text{(b) } -15 = -\frac{1}{0.2} (0.5)t \Rightarrow t = 6 \text{ s}$$

9.52

$$\text{a. } \frac{v_o}{v_I} = \frac{-R_2 \parallel \frac{1}{j\omega C_2}}{R_1} = -\frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_1 \left(R_2 + \frac{1}{j\omega C_2}\right)}$$

$$\frac{v_o}{v_I} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

$$\text{b. } \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

$$\text{c. } f = \frac{1}{2\pi R_2 C_2}$$

9.53

$$\text{a. } \frac{v_o}{v_I} = \frac{-R_2}{R_1 + \frac{1}{j\omega C_1}} = -\frac{R_2(j\omega C_1)}{1 + j\omega R_1 C_1}$$

$$\frac{v_o}{v_I} = -\frac{R_2}{R_1} \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

$$\text{b. } \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

$$\text{c. } f = \frac{1}{2\pi R_1 C_1}$$

9.54

Assuming the Zener diode is in breakdown,

$$v_o = -\frac{R_z}{R_1} V_z = -\frac{1}{1}(6.8) \Rightarrow v_o = -6.8 \text{ V}$$

$$i_z = \frac{0 - v_o}{R_z} = \frac{0 - (-6.8)}{1} \Rightarrow i_z = 6.8 \text{ mA}$$

$$i_z = \frac{10 - V_z}{R_s} - i_2 = \frac{10 - 6.8}{5.6} - 6.8 \Rightarrow i_z = -6.2 \text{ mA!!!}$$

Circuit is not in breakdown. Now

$$\frac{10 - 0}{R_s + R_1} = i_1 = \frac{10}{5.6 + 1} \Rightarrow i_1 = 1.52 \text{ mA}$$

$$v_o = -i_1 R_2 = -(1.52)(1) \Rightarrow v_o = -1.52 \text{ V}$$

$$i_z = 0$$


9.55

$$v_o = -V_T \ln\left(\frac{v_i}{I_s R_1}\right) = -(0.026) \ln\left[\frac{v_i}{(10^{-14})(10^4)}\right] \Rightarrow$$

$$v_o = -0.026 \ln\left(\frac{v_i}{10^{-10}}\right)$$

$$\text{For } v_i = 20 \text{ mV, } |v_o| = 0.497 \text{ V}$$

$$\text{For } v_i = 2 \text{ V, } |v_o| = 0.617 \text{ V}$$

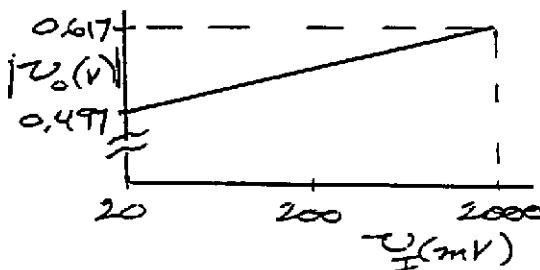

9.56

$$v_o = \left(\frac{333}{20}\right)(v_{o1} - v_{o2}) = 16.65(v_{o1} - v_{o2})$$

$$v_{o1} = -v_{BE1} = -V_T \ln\left(\frac{i_{C1}}{I_s}\right)$$

$$v_{o2} = -v_{BE2} = -V_T \ln\left(\frac{i_{C2}}{I_s}\right)$$

$$v_{o1} - v_{o2} = -V_T \ln\left(\frac{i_{C1}}{i_{C2}}\right) = V_T \ln\left(\frac{i_{C2}}{i_{C1}}\right)$$

$$i_{C2} = \frac{v_2}{R_2}, \quad i_{C1} = \frac{v_1}{R_1}$$

$$\text{So } v_{o1} - v_{o2} = V_T \ln\left(\frac{v_2}{R_2} \cdot \frac{R_1}{v_1}\right)$$

Then

$$v_o = (16.65)(0.026) \ln\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$

$$v_o = 0.4329 \ln\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$

$$\ln(x) = \log_e(x) = [\log_{10}(x)] \cdot [\log_e(10)]$$

$$= 2.3026 \log_{10}(x)$$

Then

$$v_o = (1.0) \log_{10}\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$


9.57

$$v_o = -I_s R(e^{v_i/V_T}) = -(10^{-14})(10^4)e^{v_i/V_T}$$

$$|v_o| = (10^{-10})e^{v_i/0.026}$$

$$\text{For } v_i = 0.30 \text{ V, } |v_o| = 1.03 \times 10^{-5} \text{ V}$$


$$\text{For } v_i = 0.60 \text{ V, } |v_o| = 1.05 \text{ V}$$

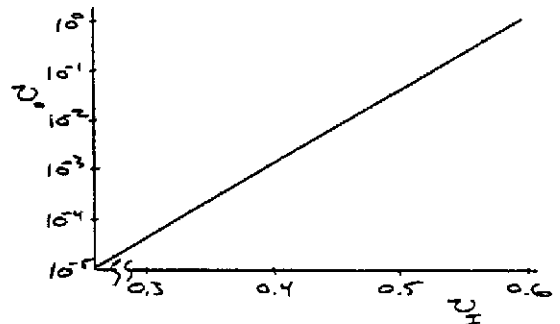

9.58

$$v_o = 2v_{i1} - 10v_{i2} + 3v_{i3} - v_{i4}$$

From Figure 9.37

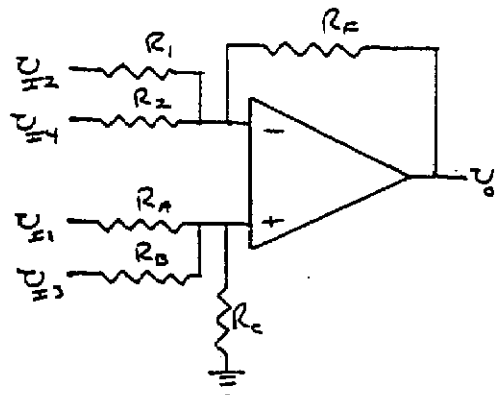

From Equation (9.110), we can write

$$v_o = -\frac{R_F}{R_1} v_{i2} - \frac{R_F}{R_2} v_{i4} + \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_P}{R_A} v_{i1} + \frac{R_P}{R_B} v_{i3}\right]$$

where  $R_N = R_1 \parallel R_2$ ,  $R_P = R_A \parallel R_B \parallel R_C$ 

$$\text{Then } \frac{R_F}{R_1} = 10; \quad \frac{R_F}{R_2} = 1$$

Set  $R_F = 500 \text{ k}\Omega$ , then  $R_1 = 50 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$

Now  $R_N = R_1 \parallel R_2 = 50 \parallel 500 = 45.45 \text{ k}\Omega$

$$\left(1 + \frac{R_F}{R_N}\right) = \left(1 + \frac{500}{45.45}\right) = 12$$

$$\text{Then } (12) \left(\frac{R_F}{R_A}\right) = 2; \quad (12) \left(\frac{R_F}{R_B}\right) = 3$$

$$\text{Now } \frac{12(R_F/R_A)}{12(R_F/R_B)} = \frac{2}{3} = \frac{R_B}{R_A}$$

$R_A$  is the largest resistor

Set  $R_A = 500 \text{ k}\Omega$ , then  $R_B = 333.3 \text{ k}\Omega$

$$\text{Then } \frac{12R_F}{R_A} = 2 = \frac{12R_F}{500} = 2 \Rightarrow R_F = 83.33 \text{ k}\Omega$$


$$R_F = R_A \parallel R_B \parallel R_C \text{ and } R_A \parallel R_B = 500 \parallel 333.3 \\ = 200 \text{ k}\Omega$$

Then  $200 \parallel R_C = 83.33$  so  $R_C = 142.8 \text{ k}\Omega$

9.59

$$v_O = 6v_{I1} + 3v_{I2} + 5v_{I3} - v_{I4} - 2v_{I5}$$

From Figure 9.37

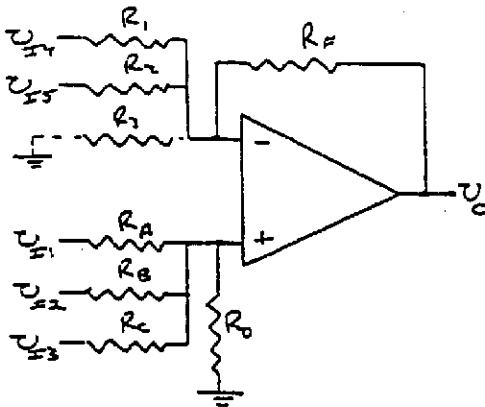

$$v_O = -\frac{R_F}{R_1} \cdot v_{I4} - \frac{R_F}{R_2} \cdot v_{I5} \\ + \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_F}{R_A} \cdot v_{I1} + \frac{R_F}{R_B} \cdot v_{I2} + \frac{R_F}{R_C} \cdot v_{I3}\right]$$

where

$$R_N = R_1 \parallel R_2, \quad R_F = R_A \parallel R_B \parallel R_C \parallel R_D$$

$$\text{Then } \frac{R_F}{R_1} = 1; \quad \frac{R_F}{R_2} = 2$$

Let  $R_F = 250 \text{ k}\Omega$ , then  $R_1 = 250 \text{ k}\Omega$ ,  $R_2 = 125 \text{ k}\Omega$

$$\text{Then } R_N = R_1 \parallel R_2 = 250 \parallel 125 = 83.33 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N}\right) = \left(1 + \frac{250}{83.33}\right) = 4$$

$$\text{Now } 4 \left(\frac{R_F}{R_A}\right) = 6; \quad 4 \left(\frac{R_F}{R_B}\right) = 3; \quad 4 \left(\frac{R_F}{R_C}\right) = 5$$

$$\frac{4(R_F/R_A)}{4(R_F/R_B)} = \frac{6}{3} = 2 = \frac{R_B}{R_A}$$

$$\frac{4(R_F/R_C)}{4(R_F/R_B)} = \frac{5}{3} = 1.667 = \frac{R_B}{R_C}$$

Set  $R_B = 250 \text{ k}\Omega$ , then

$$R_A = 125 \text{ k}\Omega, \quad R_C = 150 \text{ k}\Omega$$

$$\text{Then } \frac{4R_F}{R_A} = 6 = \frac{4R_F}{125} = 6 \Rightarrow R_F = 187.5 \text{ k}\Omega$$

$\Rightarrow$  won't work since

$$R_F = R_A \parallel R_B \parallel R_C \parallel R_D > R_A \text{ and } R_C$$

Add a resistor  $R_3$  in parallel with  $R_1$  and  $R_2$  to decrease  $R_N$  (but with zero input to  $R_3$ ).

$$\text{Set } R_D = \infty \Rightarrow R_F = R_A \parallel R_B \parallel R_C = 53.57 \text{ k}\Omega$$

Then

$$\left(1 + \frac{R_F}{R_N}\right) \cdot \frac{R_F}{R_A} = 6 = \left(1 + \frac{R_F}{R_N}\right) \cdot \left(\frac{53.57}{125}\right) \\ \Rightarrow \frac{R_F}{R_N} = 13.0$$

So


$$R_N = \frac{250}{13} = 19.23 = R_1 \parallel R_2 \parallel R_3 = 83.33 \parallel R_3$$

$$\text{So } R_3 = 25 \text{ k}\Omega$$

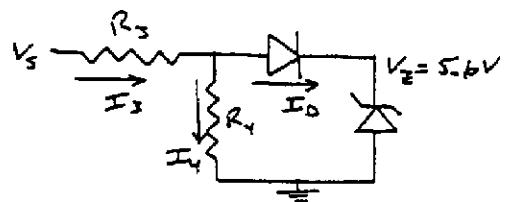9.60

$$\frac{V_O}{V_Z} = \left(1 + \frac{R_2}{R_1}\right) \\ \frac{9}{5.6} = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = 0.607 \\ I_F = \frac{V_O - V_Z}{R_F}$$

$$\text{Set } I_F = 0.8 \text{ mA} = \frac{9 - 5.6}{R_F} \Rightarrow R_F = 4.25 \text{ k}\Omega$$



$$V'_2 = 5.6 + 0.7 = 6.3 \text{ V}$$

$$I_4 = \frac{V'_2}{R_4} = \frac{6.3}{R_4}, \quad I_3 = \frac{V_S - V'_2}{R_3}$$

$$\text{If } V_S = 10 \text{ V}, \quad I_3 = \frac{10 - 6.3}{R_3} = \frac{3.7}{R_3}$$

$$\text{Want } I_{D1} = 0.1 \text{ mA}; \text{ if we set } I_4 = 0.1 \text{ mA} = \frac{6.3}{R_4}$$

$$\Rightarrow R_4 = 63 \text{ k}\Omega$$

$$\text{Then } I_3 = 0.2 \text{ mA} = \frac{3.7}{R_3} \Rightarrow R_3 = 18.5 \text{ k}\Omega$$



9.61

For  $I_Z = 1 \text{ mA}$ 

$$I_Z = \frac{V_0 - V_Z}{R_1} = \frac{10 - 5.6}{R_1} = 1 \text{ mA} \Rightarrow R_1 = 4.4 \text{ k}\Omega$$

$$V_Z = \left( \frac{R_3}{R_2 + R_3} \right) \cdot V_0 \Rightarrow 5.6 = \frac{R_3}{R_2 + R_3} \cdot 10$$

$$= \frac{10}{\left( 1 + \frac{R_2}{R_3} \right)}$$

$$1 + \frac{R_2}{R_3} = \frac{10}{5.6} \Rightarrow \frac{R_2}{R_3} = 0.786$$

$$\text{Let } \frac{V_0}{R_2 + R_3} = 1 \text{ mA} = \frac{10}{R_2 + R_3} = 1 \text{ mA}$$

$$\Rightarrow R_2 + R_3 = 10 \text{ k}\Omega$$

$$R_2 = 0.786 R_3 \Rightarrow 0.786 R_3 + R_3 = 10$$

$$\Rightarrow R_3 = 5.6 \text{ k}\Omega, R_2 = 4.4 \text{ k}\Omega$$

$$\text{Let } \frac{V_{in} - V_0}{R_4} = 2 \text{ mA} = \frac{12 - 10}{R_4} \Rightarrow R_4 = 1 \text{ k}\Omega$$

In this case, the op-amp must supply the load current.

9.62

For  $v_{01} - v_{02} = 0$  at  $T = 250^\circ \text{ K}$ , set

$$R_1 = R_2 = R_3 = R_T @ 250^\circ \text{ K} = 12 \text{ k}\Omega$$

Assuming  $v_{01}$  and  $v_{02}$  look into an open circuit.

$$v_{02} = \left( \frac{R_T}{R_T + R_2} \right) V^+ \text{ and}$$

$$v_{01} = \left( \frac{R_3}{R_1 + R_3} \right) \cdot V^+ = \frac{V^+}{2}$$

As temperature increases,  $R_T$  decreases. Let  $R_T = 12(1 - \delta)$  where  $\delta$  is positive.

$$R_T = 10 \text{ k}\Omega @ 300^\circ \Rightarrow \delta = 0.1667$$

$$v_{02} = \left( \frac{12(1 - \delta)}{12(1 - \delta) + 12} \right) V^+$$

Consider

$$v_{02} - v_{01} = \left( \frac{12(1 - \delta)}{12(1 - \delta) + 12} - \frac{1}{2} \right) (10)$$

$$= \left( \frac{12(1 - \delta) - 6[(1 - \delta) + 1]}{12[(1 - \delta) + 1]} \right) (10)$$

$$= \left( \frac{6(1 - \delta) - 6}{12[(1 - \delta) + 1]} \right) (10) = \frac{60\delta}{12[(1 - \delta) + 1]}$$

$$\text{Now consider } v_{01} - v_{02} = \frac{5\delta}{2 - \delta} \approx \frac{5}{2} \cdot \delta$$

Connect  $v_{01}$  to the  $v_{I2}$  terminal of the instrumentation amplifier and  $v_{02}$  to the  $v_{I1}$  terminal.

$$\text{Now } v_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) \left( \frac{5}{2} \right) \cdot \delta$$

For  $\delta = 0.1667$ ,  $v_0 = 5$ 

$$\frac{5}{0.1667} = 30 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) \left( \frac{5}{2} \right) \text{ or}$$

$$\frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) = 12$$

Set  $\frac{R_4}{R_3} = 4$  Then  $\frac{2R_2}{R_1} = 3$  If  $R_2 = 30 \text{ k}\Omega$

$$R_1 = 20 \text{ k}\Omega$$

Resistor  $R_1$  can be a fixed resistor in series with a potentiometer for more precise control.

9.63

Using the bridge circuit shown in Figure 9.44

$$v_{01} = \left[ \frac{1}{2} - \frac{R}{R + R(1 + \delta)} \right] V^+ = \left[ \frac{1}{2} - \frac{1}{2 + \delta} \right] (10)$$

$$= \left( \frac{2 + \delta - 2}{2(2 + \delta)} \right) (10)$$

$$\Rightarrow v_{01} \approx \frac{10\delta}{4} = 2.5\delta$$

Connect  $v_{01}$  to an instrumentation amplifier.

$$v_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (2.5\delta)$$

When  $\delta = 0.02$ ,  $v_0 = 5$ 

$$\frac{5}{(2.5)(0.02)} = 100 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Set  $\frac{R_4}{R_3} = 10$  Then  $\frac{2R_2}{R_1} = 9$