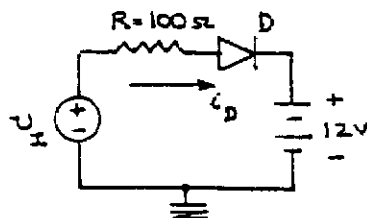



Chapter 2

Exercise Solutions

E2.1



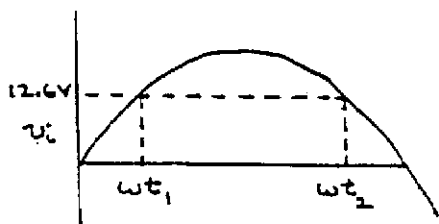- a. $i_D(\text{peak}) = \frac{24 - 12 - 0.6}{0.10} = 114 \text{ mA}$
 b. $V_R(\text{max}) = 24 + 12 = 36 \text{ V}$
 c.




$$v_i = 24 \sin \omega t = 12.6$$

$$\omega t_1 = \sin^{-1} \left(\frac{12.6}{24} \right) = 31.7^\circ$$

$$\text{By symmetry, } \omega t_2 = 180 - 31.7 = 148.3^\circ$$

$$\% = \left(\frac{148.3 - 31.7}{360} \right) \times 100\% \Rightarrow \underline{32.4\%}$$

E2.2

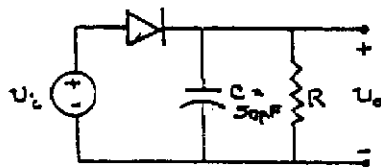

$$v_i = 75 \sin(2\pi 60t)$$

$$V_r = \frac{V_m}{fRC}$$

$$\text{or } R = \frac{V_m}{fCV_r} = \frac{75}{(60)(50 \times 10^{-6})(4)}$$

$$\underline{R = 6.25 \text{ k}\Omega}$$

E2.3

$$v_i = 120 \sin(2\pi 60t), V_r = 0.7, R = 2.5 \text{ k}\Omega$$

Full-wave rectifier

$$\text{Turns ratio } 1:2 \Rightarrow v_s = v_i$$

$$V_M = 120 - 0.7 = 119.3 \text{ V}$$

$$V_r = 119.3 - 100 = 19.3 \text{ V}$$

$$\text{So } C = \frac{V_m}{2fRV_r} = \frac{119.3}{2(60)(2.5 \times 10^3)(19.3)}$$

$$C = 2.06 \times 10^{-5} = 20.6 \times 10^{-6} \Rightarrow C = 20.6 \mu\text{F}$$

E2.4

$$v_i = 50 \sin(2\pi 60t), V_r = 0.7, R = 10 \text{ k}\Omega$$

Full-wave rectifier

$$C = \frac{V_m}{2fRV_r} = \frac{(50 - 1.4)}{2(60)(10 \times 10^3)(2)}$$

$$C = 2.025 \times 10^{-5} = 20.25 \times 10^{-6} \Rightarrow C = 20.3 \mu\text{F}$$

E2.5

Using Eq. (2-10)

$$\text{a. } \omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(4)}{75}} = 0.327$$

$$\% = \left(\frac{0.327}{2\pi} \right) \times 100\% = \underline{5.2\%}$$


$$\text{b. } \omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(19.3)}{119.3}} = 0.569$$

$$\% = \left(\frac{0.569}{\pi} \right) \times 100\% = \underline{18.1\%}$$

$$\text{c. } \omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(2)}{48.6}} = 0.287$$

$$\% = \left(\frac{0.287}{\pi} \right) \times 100\% = \underline{9.14\%}$$

E2.6

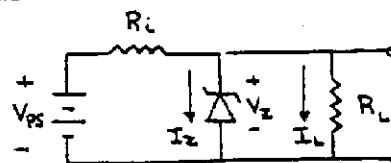

$$10 \leq V_{PS} \leq 14 \text{ V}, V_Z = 5.6$$

$$20 \leq R_L \leq 100$$

$$I_L(\text{max}) = \frac{5.6}{20} = 0.28 \text{ A}, I_L(\text{min}) = \frac{5.6}{100} = 0.056 \text{ A}$$

$$\begin{aligned}
 I_Z(\max) &= \frac{[V_{PS}(\max) - V_Z]I_L(\max)}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)} \\
 &\quad - \frac{[V_{PS}(\min) - V_Z]I_L(\min)}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)} \\
 &= \frac{[14 - 5.6](280) - [10 - 5.6](56)}{10 - (0.9)(5.6) - (0.1)(14)} \\
 &= \frac{2352 - 246.4}{3.56} \\
 &= 591.5 \text{ mA}
 \end{aligned}$$

$$I_Z(\max) = 591.5 \text{ mA}$$

$$\text{Power}(\min) = I_Z(\max) \cdot V_Z = (0.5915)(5.6)$$

$$\text{Power} = 3.31 \text{ W}$$

$$\begin{aligned}
 R_i &= \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)} = \frac{14 - 5.6}{0.5915 + 0.056} \\
 &= \frac{8.4}{0.6475} \\
 R_i &\approx 13\Omega
 \end{aligned}$$

E2.7

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$

For $V_{PS}(\min)$ and $I_L(\max)$, then

$$I_Z(\min) = \frac{11 - 9}{20} - 0.1 = 0$$

(Minimum Zener current is zero.)

For $V_{PS}(\max)$ and $I_L(\min)$, then

$$I_Z(\max) = \frac{13.6 - 9}{20} - 0 \Rightarrow 230 \text{ mA}$$

The characteristic of the minimum Zener current being one-tenth of the maximum value is violated. The proper circuit operation is questionable.

E2.8

$$I_Z(\min) = \frac{V_{PS}(\min) - V_Z}{R_i} - I_L(\max)$$

so

$$30 = \frac{10 - 9}{0.0153} - I_L(\max)$$

Or

$$I_L(\max) = 35.4 \text{ mA}$$

E2.9

$$\% \text{ Regulation} = \frac{V_L(\max) - V_L(\min)}{V_L(\text{nominal})}$$

$$V_L(\text{nominal}) = 5.6$$

$$\begin{aligned}
 V_L(\max) &= V_L(\text{nominal}) + I_Z(\max)r_z \\
 &= 5.6 + (0.5915)(1.5) = 6.487
 \end{aligned}$$

$$V_L(\min) = V_L(\text{nominal}) + I_Z(\min)r_z$$

$$= 5.6 + (I_Z(\min))(1.5)$$


$$I_Z(\min) = \frac{10 - 5.6}{13} - 0.280$$

$$= 0.0585 \text{ A}$$



$$V_L(\min) = 5.6 + (0.0585)(1.5) = 5.688$$

$$\% \text{ Reg} = \frac{6.487 - 5.688}{5.6} = 0.143 \Rightarrow 14.3\%$$

E2.10

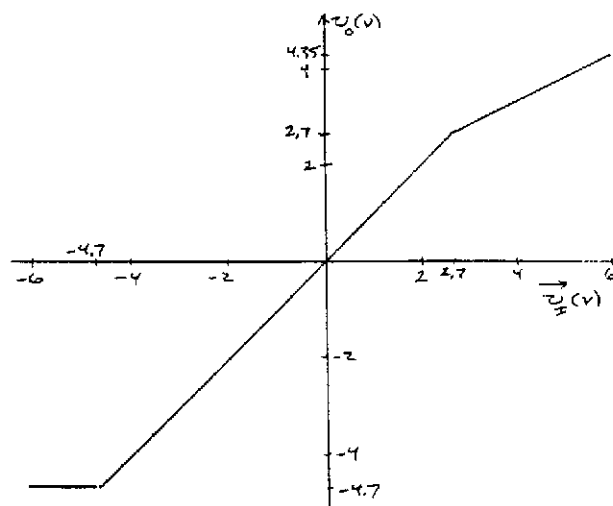

E2.11

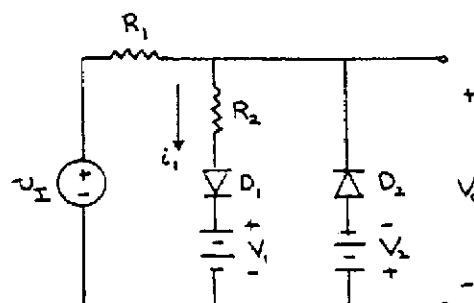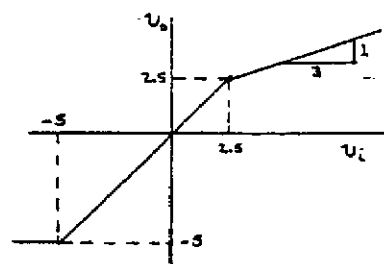

$$V_T = 0.7 \text{ V}$$

$$\text{For } v_I < 5, D_2 \text{ on} \Rightarrow V_O = -5 \text{ V} \Rightarrow V_2 = 4.3 \text{ V}$$

$$D_1 \text{ turns on when } v_I = 2.5 \Rightarrow V_1 = 1.8 \text{ V}$$

$$\text{For } v_I > 2.5, \frac{\Delta v_O}{\Delta v_I} = \frac{1}{3} \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{3}$$

$$\Rightarrow R_1 = 2R_2$$

E2.12

$$\text{For } V_T = 0, v_O(\text{max}) = -2 \text{ V}$$


Now, $\Delta v_O = 8 \text{ V}$, so that

$$v_O(\text{min}) = -10 \text{ V}$$

E2.13

As v_S goes negative, D turns on and $v_O = +5 \text{ V}$.

As v_S goes positive, D turns off.

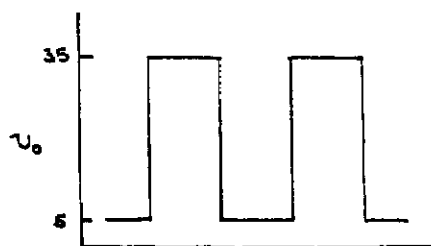

Output, a square wave oscillating between +5 and +35 volts.


E2.14

$$v_O = 4.4, \quad I = \frac{10 - 4.4}{9.5} = 0.5895 \text{ mA}$$

$$\text{Set } I = I_{D1}$$

$$v_I = 4.4 - 0.6 - (0.5895)(0.3)$$

$$v_I = 3.505$$

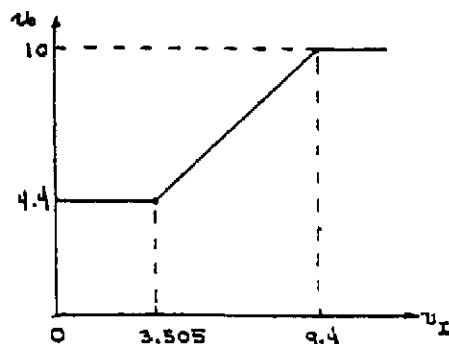

Summary: $0 \leq v_I \leq 3.5, \quad v_O = 4.4$

For $v_I > 3.5$, D_2 turns off and when $v_I \geq 9.4$,

$$v_O = 10$$


E2.15

$$V_O = -0.6 \text{ V}, \quad I_{D1} = 0,$$


$$I_{D2} = I = \frac{-0.6 - (-10)}{2.2} \Rightarrow I_{D2} = I = 4.27 \text{ mA}$$

E2.16

(a)

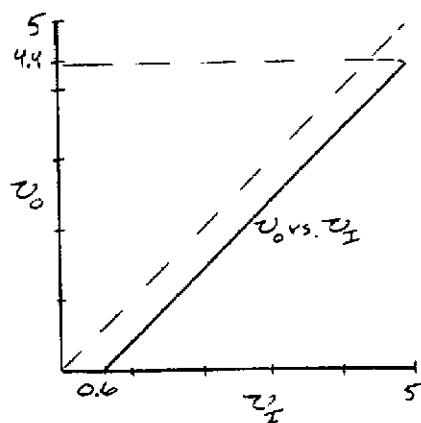


(b)

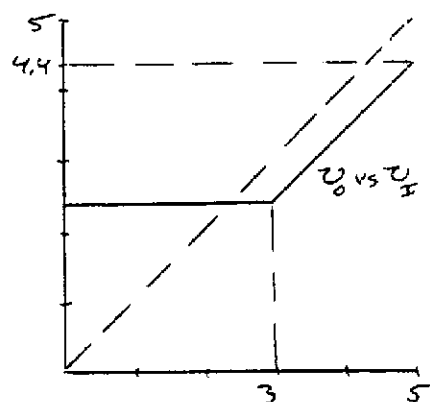

E2.17

a. $V_O = 0.6 \text{ V}$ for all V_I

b.

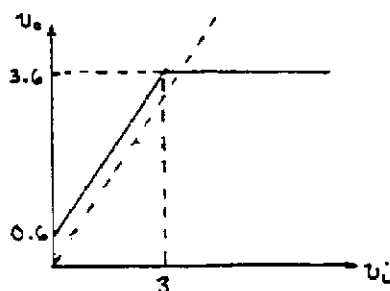

E2.18

a. $I_{Ph} = \eta e \Phi \text{ A}$


$$I_{Ph} = (0.8)(1.6 \times 10^{-19}) \left[\frac{6.4 \times 10^{-2}}{(2)(1.6 \times 10^{-19})} \right] (0.5)$$

$$\underline{I_{Ph} = 12.8 \text{ mA}}$$

- b. We have $v_o = (12.8)(1) = 12.8 \text{ volts}$.
The diode must be reverse biased so that
 $V_{PS} > 12.8 \text{ volts}$.

E2.19

The equivalent circuit is

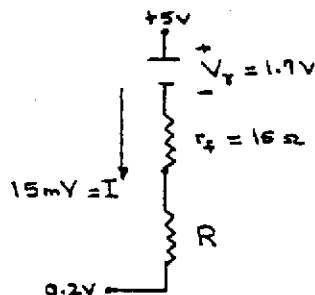

$$I = \frac{5 - 1.7 - 0.2}{r_f + R} = 15 \text{ mA}$$

$$r_f + R = \frac{5 - 1.7 - 0.2}{15} = \frac{3.1}{15} = 0.207 \text{ k}\Omega$$



$$= 207\Omega$$

$$R = 207 - 15 \Rightarrow \underline{R = 192\Omega}$$

Chapter 2

Problem Solutions

2.1

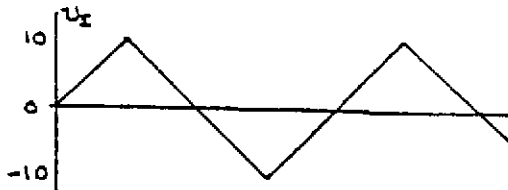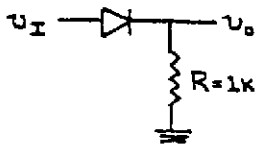


$$V_T = 0.6 \text{ V}, r_f = 20 \Omega$$


$$\text{For } v_I = 10 \text{ V}, v_o = \left(\frac{R}{R + r_f} \right) (10 - 0.6)$$

$$= \left(\frac{1}{1 + 0.02} \right) (9.4)$$

$$v_o = 9.22$$

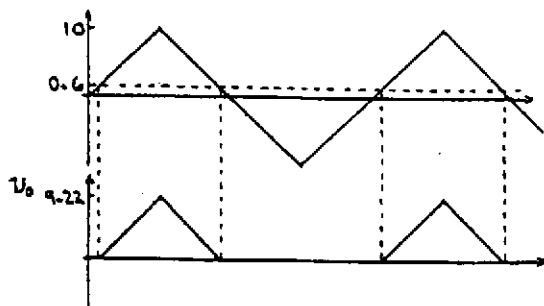

2.2

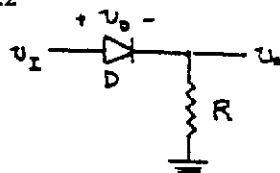

$$v_o = v_I - v_D$$

$$v_D = V_T \ln \left(\frac{i_D}{I_S} \right) \text{ and } i_D = \frac{v_o}{R}$$


$$v_o = v_I - V_T \ln \left(\frac{v_o}{I_S R} \right)$$

2.3

$$(a) v_s(\max) = \frac{160}{4} = 40 \text{ V}$$

$$(b) PIV = |v_s(\max)| = 40 \text{ V}$$

(c)

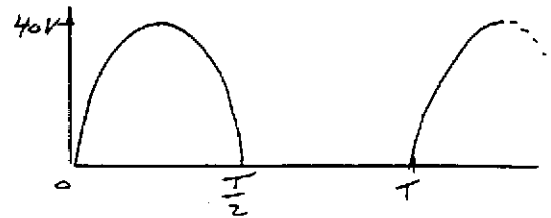

$$v_o(\text{avg}) = \frac{1}{T_o} \int_0^T v_o(t) dt = \frac{1}{2\pi} \int_0^\pi 40 \sin x dx$$

$$= \frac{40}{2\pi} [-\cos x]_0^\pi = \frac{40}{2\pi} [-(-1 - 1)] = \frac{40}{\pi}$$

or

$$v_o(\text{avg}) = 12.7 \text{ V}$$

(d) 50%

2.4

$$v_o = v_s - 2V_T \Rightarrow v_s(\max) = v_o(\max) + 2V_T$$

$$a. \text{ For } v_o(\max) = 25 \text{ V} \Rightarrow v_s(\max) = 25 + 2(0.7)$$

$$= 26.4 \text{ V}$$

$$\frac{N_1}{N_2} = \frac{160}{26.4} \Rightarrow \frac{N_1}{N_2} = 6.06$$

$$b. \text{ For } v_o(\max) = 100 \text{ V} \Rightarrow v_s(\max) = 101.4 \text{ V}$$

$$\frac{N_1}{N_2} = \frac{160}{101.4} \Rightarrow \frac{N_1}{N_2} = 1.58$$

From part (a)

$$PIV = 2v_s(\max) - V_T = 2(26.4) - 0.7$$

or

$$PIV = 52.1 \text{ V}$$

or, from part (b)

$$PIV = 2(101.4) - 0.7$$

or

$$PIV = 202.1 \text{ V}$$

2.5

a. $v_o(\max) = 24 \text{ V} \Rightarrow v_s(\max) = 24 + 2(0.7)$

$$v_s(\max) = 25.4 \text{ V}$$

$$v_s(\text{rms}) = \frac{25.4}{\sqrt{2}} \Rightarrow \underline{v_s(\text{rms}) = 17.96 \text{ V}}$$

b. $V_r = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fV_r R}$

$$C = \frac{24}{2(60)(0.5)(150)} \Rightarrow \underline{C = 2667 \text{ } \mu\text{F}}$$

c. $i_{D,\max} = \frac{V_m}{R} \left(1 + 2\pi \sqrt{\frac{V_M}{2V_r}} \right)$

$$i_{D,\max} = \frac{24}{150} \left(1 + 2\pi \sqrt{\frac{24}{2(0.5)}} \right)$$

$$\underline{i_{D,\max} = 5.08 \text{ A}}$$

2.6

(a) $v_s(\max) = 24 + 0.7 = 24.7 \text{ V}$

$$v_s(\text{rms}) = \frac{v_s(\max)}{\sqrt{2}} \Rightarrow v_s(\text{rms}) = 17.5 \text{ V}$$

(b) $V_r = \frac{V_M}{fRC} \Rightarrow C = \frac{V_M}{fR V_r} = \frac{24}{(60)(150)(0.5)}$


or
 $\underline{C = 5333 \text{ } \mu\text{F}}$

(c) For the half-wave rectifier



$$i_{D,\max} = \frac{V_M}{R} \left(1 + 4\pi \sqrt{\frac{V_M}{2V_r}} \right) = \frac{24}{150} \left(1 + 4\pi \sqrt{\frac{24}{2(0.5)}} \right)$$

or
 $\underline{i_{D,\max} = 10.0 \text{ A}}$

2.7

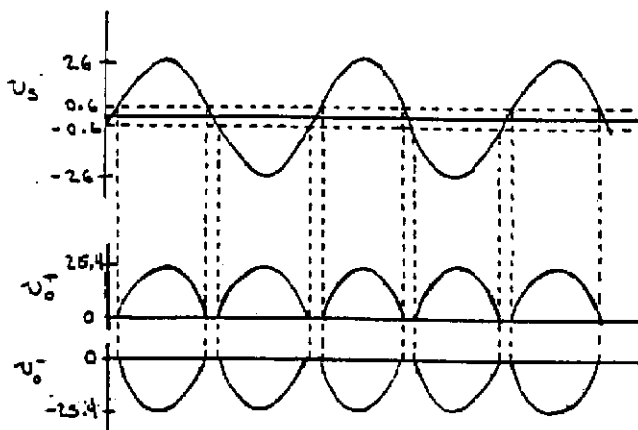

2.8

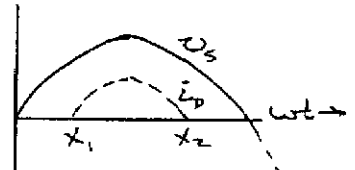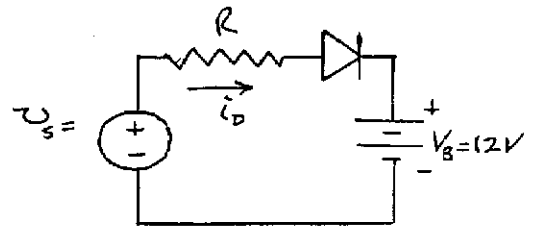

$$v_s(t) = 24 \sin \omega t$$

Now

$$i_D(\text{avg}) = \frac{1}{T} \int_0^T i_D(t) dt$$

We have for $x_1 \leq \omega t \leq x_2$

$$i_D = \frac{24 \sin x - 12.7}{R}$$

To find x_1 and x_2 ,

$$24 \sin x_1 = 12.7$$

$$x_1 = 0.558 \text{ rad}$$

$$x_2 = \pi - 0.558 = 2.584 \text{ rad}$$

Then

$$i_D(\text{avg}) = \frac{1}{2\pi} \int_{x_1}^{x_2} \left[\frac{24 \sin x - 12.7}{R} \right] dx$$

$$= \frac{1}{2\pi} \left(\frac{24}{R} \right) \left(-\cos x \right)_{x_1}^{x_2} - \frac{1}{2\pi} \left(\frac{12.7}{R} \right) x_{x_1}^{x_2}$$

or

$$2 = \frac{6.482}{R} - \frac{4.095}{R} \Rightarrow \underline{R = 1.19 \text{ } \Omega}$$

Fraction of time diode is conducting

$$= \frac{x_2 - x_1}{2\pi} \times 100\% = \frac{2.584 - 0.558}{2\pi} \times 100\%$$

or

$$\underline{\text{Fraction} = 32.2\%}$$

Power rating

$$P_{\text{avg}} = R \cdot i_{\text{rms}}^2 = \frac{R}{T} \int_0^T i_D^2 dt = \frac{R}{2\pi} \int_{x_1}^{x_2} \left[\frac{24 \sin x - 12.7}{R} \right]^2 dx$$

$$= \frac{1}{2\pi R} \int_{x_1}^{x_2} \left[(24)^2 \sin^2 x - 2(12.7)(24) \sin x + (12.7)^2 \right] dx$$

$$= \frac{1}{2\pi R} \left[(24)^2 \left[\frac{x}{2} - \frac{\sin 2x}{4} \right]_{x_1}^{x_2} - 2(12.7)(24)(-\cos x)_{x_1}^{x_2} + (12.7)^2 x_{x_1}^{x_2} \right]$$

For $R = 1.19 \text{ } \Omega$, then

$$\underline{P_{\text{avg}} = 17.9 \text{ W}}$$

2.9

$$R = \frac{15}{0.1} = 150 \Omega$$

$$v_s(\max) = v_o(\max) + V_\gamma = 15 + 0.7$$

or

$$v_s(\max) = 15.7 \text{ V}$$

Then

$$v_s(\text{rms}) = \frac{15.7}{\sqrt{2}} = 11.1 \text{ V}$$

Now

$$\frac{N_1}{N_2} = \frac{120}{11.1} \Rightarrow \frac{N_1}{N_2} = 10.8$$

$$V_r = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fRV_r} = \frac{15}{2(60)(150)(0.4)}$$

or



$$C = 2083 \mu\text{F}$$

$$PIV = 2v_s(\max) - V_\gamma = 2(15.7) - 0.7$$

or

$$PIV = 30.7 \text{ V}$$


2.10

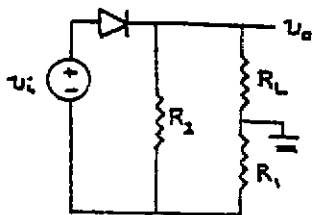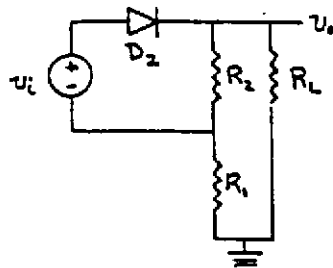For $v_i > 0$ 

$$V_\gamma = 0$$

Voltage across $R_L + R_1 = v_i$

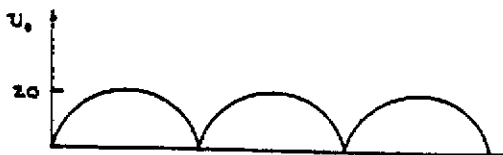
$$\text{Voltage Divider} \Rightarrow v_o = \left(\frac{R_L}{R_L + R_1} \right) v_i = \frac{1}{2} v_i$$



2.11

For $v_i > 0$, ($V_\gamma = 0$)

a.

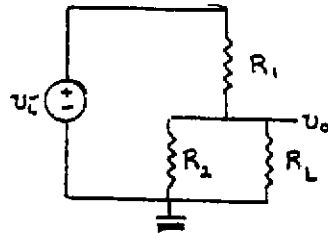

$$v_o = \left(\frac{R_2 \| R_L}{R_2 \| R_L + R_1} \right) v_i$$


$$R_2 \| R_L = 2.2 \| 6.8 = 1.66 \text{ k}\Omega$$

$$v_o = \left(\frac{1.66}{1.66 + 2.2} \right) v_i = 0.43 v_i$$



$$\text{b. } v_o(\text{rms}) = \frac{v_o(\max)}{\sqrt{2}} \Rightarrow \underline{v_o(\text{rms}) = 3.04 \text{ V}}$$

2.12

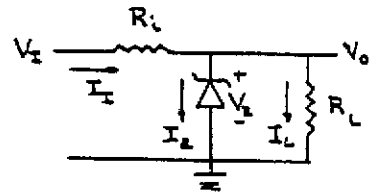

$$V_i = 6.3 \text{ V}, R_i = 12 \Omega, V_Z = 4.8$$

$$\text{a. } I_i = \frac{6.3 - 4.8}{12} \Rightarrow 125 \text{ mA}$$

$$I_L = I_i - I_Z = 125 - I_Z$$

$$25 \leq I_L \leq 120 \text{ mA} \Rightarrow 40 \leq R_L \leq 192 \Omega$$

$$\text{b. } P_Z = I_Z V_Z = (100)(4.8) \Rightarrow \underline{P_Z = 480 \text{ mW}}$$

$$P_L = I_L V_o = (120)(4.8) = \underline{P_L = 576 \text{ mW}}$$

2.13

$$\text{a. } I_i = \frac{20 - 10}{222} \Rightarrow \underline{I_i = 45.0 \text{ mA}}$$

$$I_L = \frac{10}{380} \Rightarrow \underline{I_L = 26.3 \text{ mA}}$$

$$I_Z = I_i - I_L \Rightarrow \underline{I_Z = 18.7 \text{ mA}}$$

$$b. \quad P_Z(\max) = 400 \text{ mW} \Rightarrow I_Z(\max) = \frac{400}{10} = 40 \text{ mA}$$

$$\Rightarrow I_L(\min) = I_I - I_Z(\max) = 45 - 40$$

$$\Rightarrow I_L(\min) = 5 \text{ mA} = \frac{10}{R_L}$$

$$\Rightarrow R_L = 2 \text{ k}\Omega$$

For $R_i = 175 \Omega$

$$I_L = 57.1 \text{ mA} \quad I_L = 26.3 \text{ mA} \quad I_Z = 30.8 \text{ mA}$$

$$I_Z(\max) = 40 \text{ mA} \Rightarrow I_L(\min) = 57.1 - 40 = 17.1 \text{ mA}$$

$$R_L = \frac{10}{17.1} \Rightarrow R_L = 585 \Omega$$

2.14

a. From Eq. (2-23)

$$I_Z(\max) = \frac{500[20 - 10] - 50[15 - 10]}{15 - (0.9)(10) - (0.1)(20)} \\ = \frac{5000 - 250}{4}$$

$$I_Z(\max) = 1.1875 \text{ A}$$

$$I_Z(\min) = 0.11875 \text{ A}$$

From Eq. (2-21(b))

$$R_i = \frac{20 - 10}{1.1875 + 50} \Rightarrow R_i = 8.08 \Omega$$

$$b. \quad P_Z = (1.1875)(10) \Rightarrow P_Z = 11.9 \text{ W} \\ P_L = I_L(\max)V_o = (0.5)(10) \Rightarrow P_L = 5 \text{ W}$$

2.15

(a) As approximation, assume $I_Z(\max)$ and $I_Z(\min)$ are the same as in problem 2-14.

$$V_o(\max) = V_o(\text{nom}) + I_Z(\max)r_z \\ = 20 + (0.453)(2) = 20.906$$

$$V_o(\min) = V_o(\text{nom}) + I_Z(\min)r_z \\ = 20 + (0.0453)(2) = 20.0906$$

$$b. \quad \% \text{ Reg} = \frac{20.906 - 20.0906}{20} \times 100\% \\ \Rightarrow \% \text{ Reg} = 4.08\%$$

2.16

$$\% \text{ Reg} = \frac{V_L(\max) - V_L(\min)}{V_L(\text{nom})} \times 100\% \\ = \frac{V_L(\text{nom}) + I_Z(\max)r_z - (V_L(\text{nom}) + I_Z(\min)r_z)}{V_L(\text{nom})} \\ = \frac{[I_Z(\max) - I_Z(\min)](3)}{6} = 0.05$$

So

$$I_Z(\max) - I_Z(\min) = 0.1 \text{ A}$$

Now

$$I_L(\max) = \frac{6}{500} = 0.012 \text{ A}, \quad I_L(\min) = \frac{6}{1000} = 0.006 \text{ A}$$

Now

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_Z(\min) + I_L(\max)}$$

or

$$280 = \frac{15 - 6}{I_Z(\min) + 0.012} \Rightarrow I_Z(\min) = 0.020 \text{ A}$$

Then

$$I_Z(\max) = 0.1 + 0.02 = 0.12 \text{ A}$$

and

$$R_i = \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)}$$

or

$$280 = \frac{V_{PS}(\max) - 6}{0.12 + 0.006} \Rightarrow V_{PS}(\max) = 41.3 \text{ V}$$

2.17

Using Figure 2.17

$$a. \quad V_{PS} = 20 \pm 25\% \Rightarrow 15 \leq V_{PS} \leq 25 \text{ V}$$

For $V_{PS}(\min)$:

$$I_I = I_Z(\min) + I_L(\max) = 3 + 20 = 25 \text{ mA}$$

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_I} = \frac{15 - 10}{25} \Rightarrow R_i = 200 \Omega$$

b. For $V_{PS}(\max)$

$$\Rightarrow I_I(\max) = \frac{25 - 10}{R_i} \Rightarrow I_I(\max) = 75 \text{ mA}$$

$$\text{For } I_L(\min) = 0 \Rightarrow I_Z(\max) = 75 \text{ mA}$$

$$V_{Z0} = V_Z - I_Z r_z = 10 - (0.025)(5) = 9.875 \text{ V}$$

$$V_o(\max) = 9.875 + (0.075)(5) = 10.25$$

$$V_o(\min) = 9.875 + (0.005)(5) = 9.90$$

$$\Delta V_o = 0.35 \text{ V}$$

$$c. \quad \% \text{ Reg} = \frac{\Delta V_o}{V_o(\text{nom})} \times 100\% \Rightarrow \% \text{ Reg} = 3.5\%$$

2.18

From Equation (2.21(a))

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_Z(\min) + I_L(\max)} = \frac{24 - 16}{40 + 400}$$

or

$$R_i = 18.2 \Omega$$

Also

$$V_r = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fRV_r}$$

$$R \cong R_i + r_i = 18.2 + 2 = 20.2 \Omega$$

Then

$$C = \frac{24}{2(60)(1)(20.2)} \Rightarrow C = 9901 \mu\text{F}$$

2.19

$$V_Z = V_{Z0} + I_Z r_Z \quad V_{Z(\text{nom})} = 8 \text{ V}$$

$$8 = V_{Z0} + (0.1)(0.5) \Rightarrow V_{Z0} = 7.95 \text{ V}$$

$$I_i = \frac{V_S(\text{max}) - V_{Z(\text{nom})}}{R_i} = \frac{12 - 8}{3} = 1.333 \text{ A}$$

$$\text{For } I_L = 0.2 \text{ A} \Rightarrow I_Z = 1.133 \text{ A}$$

$$\text{For } I_L = 1 \text{ A} \Rightarrow I_Z = 0.333 \text{ A}$$

$$V_L(\text{max}) = V_{Z0} + I_Z(\text{max})r_Z \\ = 7.95 + (1.133)(0.5) = 8.5165$$

$$V_L(\text{min}) = V_{Z0} + I_Z(\text{min})r_Z \\ = 7.95 + (0.333)(0.5) = 8.1165$$

$$\Delta V_L = 0.4 \text{ V}$$

$$\% \text{ Reg} = \frac{\Delta V_L}{V_0(\text{nom})} = \frac{0.4}{8} \Rightarrow \% \text{ Reg} = 5.0\%$$

$$V_r = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fRV_r}$$

$$R = R_i + r_i = 3 + 0.5 = 3.5 \Omega$$

Then

$$C = \frac{8}{2(60)(3.5)(0.8)} \Rightarrow C = 0.0238 \text{ F}$$

2.20

(a) For $-10 \leq v_i \leq 0$, both diodes are conducting $\Rightarrow v_o = 0$

For $0 \leq v_i \leq 3$, Zener not in breakdown, so


$$i_i = 0, \quad v_o = 0$$

For $v_i > 3$

$$i_i = \frac{v_i - 3}{20} \text{ mA}$$

$$v_o = \left(\frac{v_i - 3}{20} \right)(10) = \frac{1}{2}v_i - 1.5$$

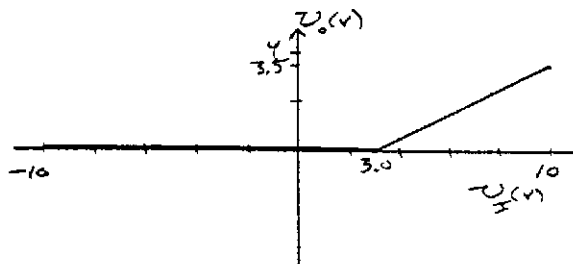
$$\text{At } v_i = 10 \text{ V}, \quad v_o = 3.5 \text{ V}, \quad i_i = 0.35 \text{ mA}$$



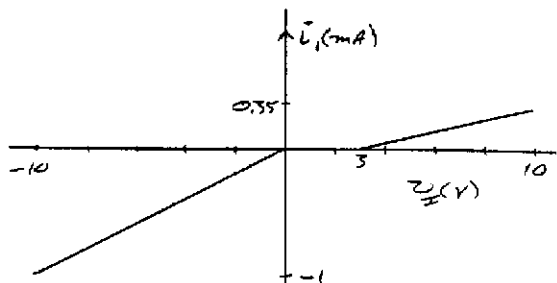(b) For $v_i < 0$, both diodes forward biased


$$-i_i = \frac{0 - v_i}{10}. \quad \text{At } v_i = -10 \text{ V}, \quad i_i = -1 \text{ mA}$$

$$\text{For } v_i > 3, \quad i_i = \frac{v_i - 3}{20}. \quad \text{At } v_i = 10 \text{ V}, \quad i_i = 0.35 \text{ mA}$$



2.21

(a)

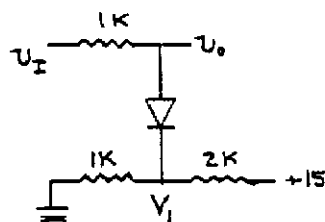

$$V_i = \frac{1}{3} \times 15 = 5 \text{ V} \Rightarrow \text{for } v_i \leq 5.7, \quad v_o = v_i$$

$$\frac{v_i - (V_i + 0.7)}{1} + \frac{15 - V_i}{2} = \frac{V_i}{1}, \quad v_o = V_i + 0.7$$


$$\frac{v_i - v_o}{1} + \frac{15 - (v_o - 0.7)}{2} = \frac{v_o - 0.7}{1}$$

$$\frac{v_i}{1} + \frac{15.7}{2} + \frac{0.7}{1} = v_o \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{1} \right) = v_o(2.5)$$

$$v_i + 8.55 = v_o(2.5) \Rightarrow v_o = \frac{1}{2.5}v_i + 3.42$$

$$v_i = 5.7 \Rightarrow v_o = 5.7$$

$$v_i = 15 \Rightarrow v_o = 9.42$$

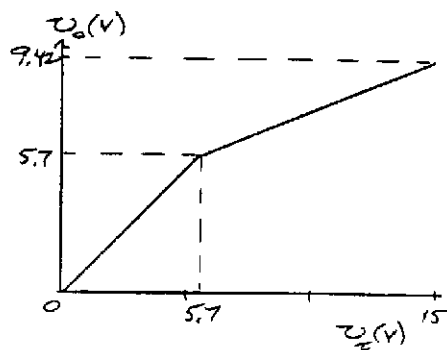


(b) $i_D = 0$ for $0 \leq v_i \leq 5.7$

Then

$$i_D = \frac{v_i - v_o}{1} = \frac{v_i - \left(\frac{v_i}{2.5} + 3.42 \right)}{1}$$


or
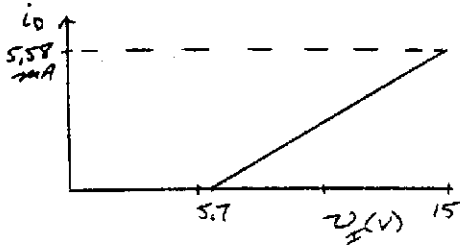
$$i_D = \frac{0.6v_i - 3.42}{1} \quad \text{For } v_i = 15, \quad i_D = 5.58 \text{ mA}$$




2.22

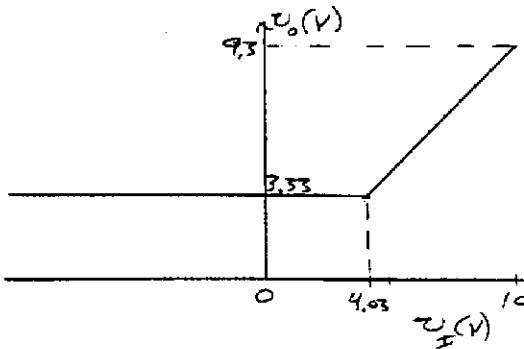(a) For D off, $v_o = \left(\frac{20}{30}\right)(20) - 10 = 3.33$ V
 Then for $v_i \leq 3.33 + 0.7 = 4.03$ V $\Rightarrow v_o = 3.33$ V
 For $v_i > 4.03$, $v_o = v_i - 0.7$;
 For $v_i = 10$, $v_o = 9.3$




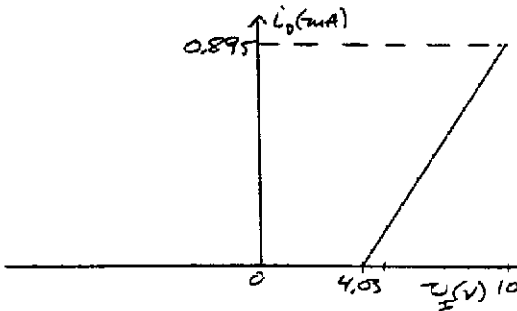(b) For $v_i \leq 4.03$ V, $i_D = 0$
 For $v_i > 4.03$, $i_D + \frac{10 - v_o}{10} = \frac{v_o - (-10)}{20}$
 Which yields $i_D = \frac{3}{20}v_i - 0.605$
 For $v_i = 10$, $i_D = 0.895$ mA




2.23

a.

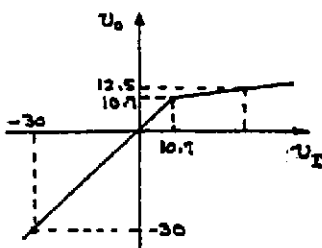


For $v_i = 30$ V, $i = \frac{30 - 10.7}{100 + 10} = 0.175$ A
 $v_o = i(10) + 10.7 = 12.5$ V


b.

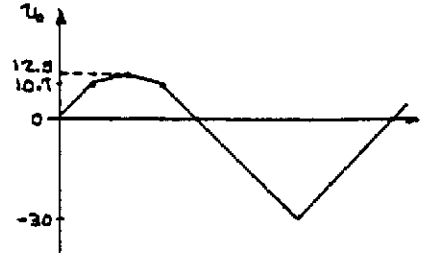

2.24

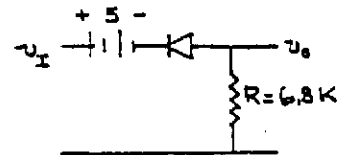


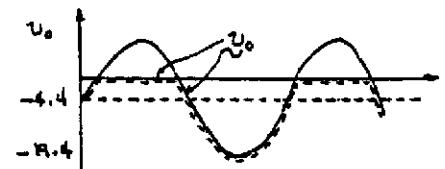$V_\gamma = 0.6$ V
 $v_i = 15 \sin \omega t$




2.25


a. $V_\gamma = 0$

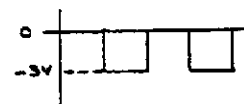


$V_\gamma = 0.6$

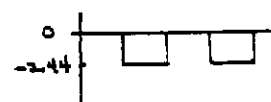

b. $V_T = 0$

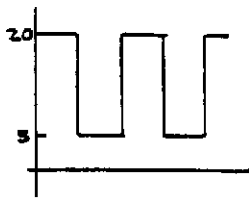


$V_T = 0.6$

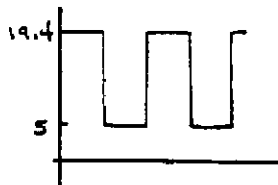

2.26



One possible example is shown.

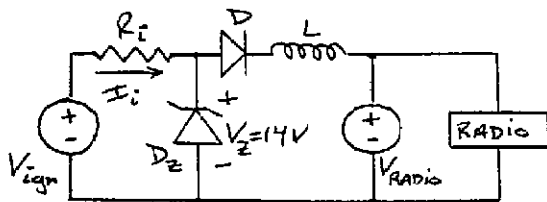


L will tend to block the transient signals
 D_Z will limit the voltage to +14 V and -0.7 V.
 Power ratings depends on number of pulses per second and duration of pulse.

2.27

$V_T = 0$

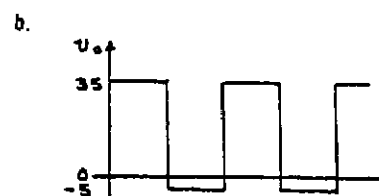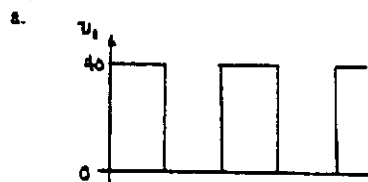


2.28

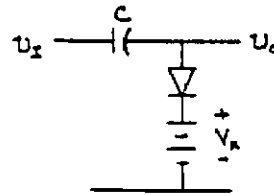

- a. For $V_T = 0 \Rightarrow V_x = 2.7$ V
 b. For $V_T = 0.7$ V $\Rightarrow V_x = 2.0$ V


2.29

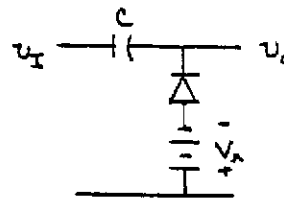

For $V_T = 0$; $V_x = 10$ V


2.30

For circuit in Figure P2.27(a)

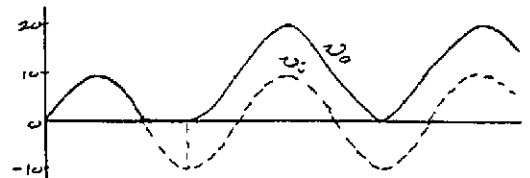


For circuit in Figure P2.27(b)

(i) For $V_B = +3$ V

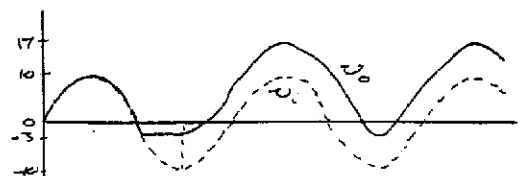


(ii) For $V_B = -3$ V

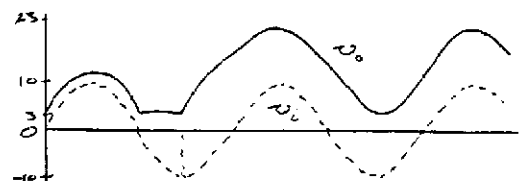

2.31

For Figure P2.27(a)

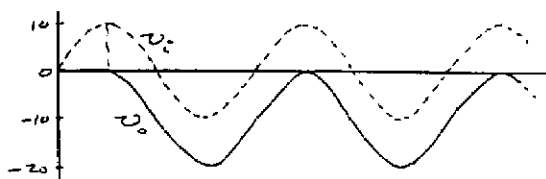

2.32

$$a. \quad I_{D1} = \frac{10 - 0.6}{9.5 + 0.5} \Rightarrow \underline{I_{D1} = 0.94 \text{ mA}} \quad \underline{I_{D2} = 0}$$

$$V_0 = I_{D1}(9.5) \Rightarrow \underline{V_0 = 8.93 \text{ V}}$$

$$b. \quad I_{D1} = \frac{5 - 0.6}{9.5 + 0.5} \Rightarrow \underline{I_{D1} = 0.44 \text{ mA}} \quad \underline{I_{D2} = 0}$$

$$V_0 = I_{D1}(9.5) \Rightarrow \underline{V_0 = 4.18 \text{ V}}$$

c. Same as (a)

$$d. \quad 10 = \frac{(I)}{2}(0.5) + 0.6 + I(9.5) \Rightarrow I = 0.964 \text{ mA}$$

$$V_0 = I(9.5) \Rightarrow \underline{V_0 = 9.16 \text{ V}}$$

$$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow \underline{I_{D1} = I_{D2} = 0.482 \text{ mA}}$$

2.33

$$a. \quad I = I_{D1} = I_{D2} = 0 \quad \underline{V_0 = 10}$$

$$b. \quad 10 = I(9.5) + 0.6 + I(0.5) \Rightarrow$$

$$\underline{I = I_{D2} = 0.94 \text{ mA}} \quad \underline{I_{D1} = 0}$$

$$V_0 = 10 - I(9.5) \Rightarrow \underline{V_0 = 1.07 \text{ V}}$$

$$c. \quad 10 = I(9.5) + 0.6 + I(0.5) + 5 \Rightarrow$$

$$\underline{I = I_{D2} = 0.44 \text{ mA}} \quad \underline{I_{D1} = 0}$$

$$V_0 = 10 - I(9.5) \Rightarrow \underline{V_0 = 5.82 \text{ V}}$$

$$d. \quad 10 = I(9.5) + 0.6 + \frac{I}{2}(0.5) \Rightarrow \underline{I = 0.964 \text{ mA}}$$

$$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow \underline{I_{D1} = I_{D2} = 0.482 \text{ mA}}$$

$$V_0 = 10 - I(9.5) \Rightarrow \underline{V_0 = 0.842 \text{ V}}$$

2.34

$$a. \quad V_1 = V_2 = 0 \Rightarrow D_1, D_2, D_3 \text{ on} \quad \underline{V_0 = 4.4 \text{ V}}$$

$$I = \frac{10 - 4.4}{9.5} \Rightarrow \underline{I = 0.589 \text{ mA}}$$

$$I_{D1} = I_{D2} = \frac{4.4 - 0.6}{0.5} \Rightarrow \underline{I_{D1} = I_{D2} = 7.6 \text{ mA}}$$

$$I_{D3} = I_{D1} + I_{D2} - I = 2(7.6) - 0.589 \Rightarrow$$

$$\underline{I_{D3} = 14.6 \text{ mA}}$$

$$b. \quad V_1 = V_2 = 5 \text{ V} \quad D_1 \text{ and } D_2 \text{ on, } D_3 \text{ off}$$

$$10 = I(9.5) + 0.6 + \frac{I}{2}(0.5) + 5 \Rightarrow \underline{I = 0.451 \text{ mA}}$$

$$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow \underline{I_{D1} = I_{D2} = 0.226 \text{ mA}}$$

$$\underline{I_{D3} = 0}$$

$$V_0 = 10 - I(9.5) = 10 - (0.451)(9.5) \Rightarrow$$

$$\underline{V_0 = 5.72 \text{ V}}$$

$$c. \quad V_1 = 5 \text{ V}, V_2 = 0 \quad D_1 \text{ off, } D_2, D_3 \text{ on}$$

$$\underline{V_0 = 4.4 \text{ V}}$$

$$I = \frac{10 - 4.4}{9.5} \Rightarrow \underline{I = 0.589 \text{ mA}}$$

$$I_{D2} = \frac{4.4 - 0.6}{0.5} \Rightarrow \underline{I_{D2} = 7.6 \text{ mA}}$$

$$\underline{I_{D1} = 0}$$

$$I_{D3} = I_{D2} - I = 7.6 - 0.589 \Rightarrow \underline{I_{D3} = 7.01 \text{ mA}}$$

$$d. \quad V_1 = 5 \text{ V}, V_2 = 2 \text{ V} \quad D_1 \text{ off, } D_2, D_3 \text{ on}$$

$$\underline{V_0 = 4.4 \text{ V}}$$

$$I = \frac{10 - 4.4}{9.5} \Rightarrow \underline{I = 0.589 \text{ mA}}$$

$$I_{D2} = \frac{4.4 - 0.6 - 2}{0.5} \Rightarrow \underline{I_{D2} = 3.6 \text{ mA}}$$

$$\underline{I_{D1} = 0}$$

$$I_{D3} = I_{D2} - I = 3.6 - 0.589 \Rightarrow \underline{I_{D3} = 3.01 \text{ mA}}$$

2.35

$$(a) \quad D_1 \text{ on, } D_2 \text{ off, } D_3 \text{ on}$$

$$\text{So } \underline{I_{D2} = 0}$$

$$\text{Now } \underline{V_1 = -0.6 \text{ V}}, \quad I_{D1} = \frac{10 - 0.6 - (-0.6)}{R_1 + R_2} = \frac{10}{2 + 6} \Rightarrow$$

$$\underline{I_{D1} = 1.25 \text{ mA}}$$

$$V_1 = 10 - 0.6 - (1.25)(2) \Rightarrow \underline{V_1 = 6.9 \text{ V}}$$

$$I_{R3} = \frac{-0.6 - (-5)}{2} = 2.2 \text{ mA}$$

$$I_{D3} = I_{R3} - I_{D1} = 2.2 - 1.25 \Rightarrow \underline{I_{D3} = 0.95 \text{ mA}}$$

$$(b) \quad D_1 \text{ on, } D_2 \text{ on, } D_3 \text{ off}$$

$$\text{So } \underline{I_{D3} = 0}$$

$$\underline{V_1 = 4.4 \text{ V}}, \quad I_{D1} = \frac{10 - 0.6 - 4.4}{R_1} = \frac{5}{6}$$

or

$$\underline{I_{D1} = 0.833 \text{ mA}}$$

$$I_{R2} = \frac{4.4 - (-5)}{R_2 + R_3} = \frac{9.4}{10} = 0.94 \text{ mA}$$

$$I_{D2} = I_{R2} - I_{D1} = 0.94 - 0.833 \Rightarrow \underline{I_{D2} = 0.107 \text{ mA}}$$

$$V_2 = I_{R2}R_3 - 5 = (0.94)(5) - 5 \Rightarrow \underline{V_2 = -0.3 \text{ V}}$$


(c) All diodes are on
 $V_1 = 4.4 \text{ V}$, $V_2 = -0.6 \text{ V}$

$$I_{D1} = 0.5 \text{ mA} = \frac{10 - 0.6 - 4.4}{R_1} \Rightarrow R_1 = 10 \text{ k}\Omega$$

$$I_{R2} = 0.5 + 0.5 = 1 \text{ mA} = \frac{4.4 - (-0.6)}{R_2} \Rightarrow$$

$$R_2 = 5 \text{ k}\Omega$$
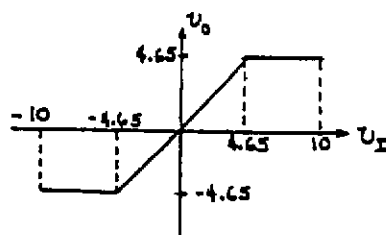
$$I_{R3} = 1.5 \text{ mA} = \frac{-0.6 - (-5)}{R_3} \Rightarrow R_3 = 2.93 \text{ k}\Omega$$



$$v_o = v_i \text{ for } -4.65 \leq v_i \leq 4.65$$

2.36

For v_i small, both diodes off

$$v_o = \left(\frac{0.5}{0.5 + 5} \right) v_i = 0.0909 v_i$$

When $v_i - v_o = 0.6$, D_1 turns on. So we have

$$v_i - 0.0909 v_i = 0.6 \Rightarrow v_i = 0.66, \quad v_o = 0.06$$

For D_1 on

$$\frac{v_i - 0.6 - v_o}{5} + \frac{v_i - v_o}{5} = \frac{v_o}{0.5} \text{ which yields}$$

$$v_o = \frac{2v_i - 0.6}{12}$$

When $v_o = 0.6$, D_2 turns on. Then

$$0.6 = \frac{2v_i - 0.6}{12} \Rightarrow v_i = 3.9 \text{ V}$$


Now for $v_i > 3.9$

$$\frac{v_i - 0.6 - v_o}{5} + \frac{v_i - v_o}{5} = \frac{v_o}{0.5} + \frac{v_o - 0.6}{0.5}$$

Which yields

$$v_o = \frac{2v_i + 5.4}{22}; \text{ For } v_i = 10 \Rightarrow v_o = 1.15 \text{ V}$$

2.37

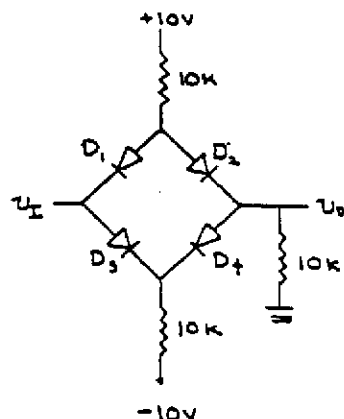


For $v_i > 0$, when D_1 turns off

$$I = \frac{10 - 0.7}{20} = 0.465 \text{ mA}$$

$$v_o = I(10 \text{ k}\Omega) = 4.65 \text{ V}$$

2.38

a.

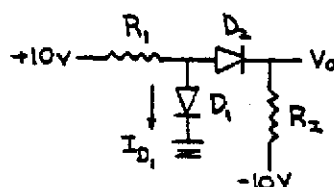

$$R_1 = 5 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega$$

$$D_1 \text{ and } D_2 \text{ on} \Rightarrow v_o = 0$$

$$I_{D1} = \frac{10 - 0.7}{5} - \frac{0 - (-10)}{10} = 1.86 - 1.0$$

$$I_{D1} = 0.86 \text{ mA}$$

b. $R_1 = 10 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, D_1 off, D_2 on

$$I_{D1} = 0$$

$$I = \frac{10 - 0.7 - (-10)}{15} = 1.287$$

$$V_o = IR_2 - 10 \Rightarrow \underline{V_o = -3.57 \text{ V}}$$

2.39


$$\frac{15 - (V_o + 0.7)}{10} = \frac{V_o + 0.7}{20} + \frac{V_o}{20}$$

$$\frac{15}{10} - \frac{0.7}{10} - \frac{0.7}{20} = V_o \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{20} \right) = V_o \left(\frac{4.0}{20} \right)$$

$$V_o = 6.975 \text{ V}$$

$$I_D = \frac{V_o}{20} \Rightarrow \underline{I_D = 0.349 \text{ mA}}$$

2.40

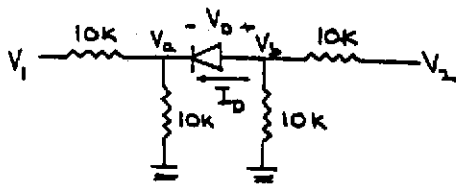

a. $V_1 = 15 \text{ V}$, $V_2 = 10 \text{ V}$ Diode off

$$V_a = 7.5 \text{ V}, V_b = 5 \text{ V} \Rightarrow V_D = -2.5 \text{ V}$$

$$I_D = 0$$

b. $V_1 = 10 \text{ V}$, $V_2 = 15 \text{ V}$ Diode on

$$\frac{V_2 - V_b}{10} = \frac{V_b}{10} + \frac{V_a}{10} + \frac{V_a - V_1}{10} \Rightarrow V_a = V_b - 0.6$$

$$\frac{15}{10} + \frac{10}{10} = V_b \left(\frac{1}{10} + \frac{1}{10} \right) + V_b \left(\frac{1}{10} + \frac{1}{10} \right)$$

$$-0.6 \left(\frac{1}{10} + \frac{1}{10} \right)$$

$$2.62 = V_b \left(\frac{4}{10} \right) \Rightarrow V_b = 6.55 \text{ V}$$

$$I_D = \frac{15 - 6.55}{10} - \frac{6.55}{10} \Rightarrow I_D = 0.19 \text{ mA}$$

$$V_D = 0.6 \text{ V}$$

2.41

$v_I = 0$, D_1 off, D_2 on

$$I = \frac{10 - 2.5}{15} = 0.5 \text{ mA}$$

$$v_o = 10 - (0.5)(5) \Rightarrow v_o = 7.5 \text{ V for } 0 \leq v_I \leq 7.5$$


For $v_I = 30 \text{ V}$, D_2 off, $v_o = 10 \text{ V}$

Determine v_I when $V_x = 10$

$$I = \frac{v_I - 2.5}{25}$$

$$V_x = 10 = I(10) + 2.5 \Rightarrow I = 0.75 \text{ mA}$$

$$v_I = (0.75)(25) + 2.5 = 21.25$$

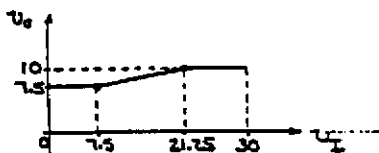

2.42

a. $V_{01} = V_{02} = 0$

b. $V_{01} = 4.4 \text{ V}$, $V_{02} = 3.8 \text{ V}$

c. $V_{01} = 4.4 \text{ V}$, $V_{02} = 3.8 \text{ V}$

Logic "1" level degrades as it goes through additional logic gates.

2.43

a. $V_{01} = V_{02} = 5 \text{ V}$

b. $V_{01} = 0.6 \text{ V}$, $V_{02} = 1.2 \text{ V}$

c. $V_{01} = 0.6 \text{ V}$, $V_{02} = 1.2 \text{ V}$

Logic "0" signal degrades as it goes through additional logic gates.

2.44

$$(V_1 \text{ AND } V_2) \text{ OR } (V_3 \text{ AND } V_4)$$

2.45

$$I = \frac{10 - 1.5 - 0.2}{R + 10} = 12 \text{ mA} = 0.012$$

$$R + 10 = \frac{8.3}{0.012} = 691.7 \Omega$$


$$R = 681.7 \Omega$$

2.46

$$I = \frac{10 - 1.7 - V_I}{0.75} = 8$$

$$V_I = 10 - 1.7 - 8(0.75) \Rightarrow V_I = 2.3 \text{ V}$$

2.47

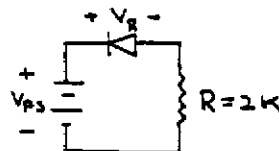

$$V_R = 1 \text{ V}, I = 0.8 \text{ mA}$$

$$V_{PS} = 1 + (0.8)(2)$$

$$V_{PS} = 2.6 \text{ V}$$

2.48

$$I_{ph} = \eta e \Phi A$$

$$0.6 \times 10^{-3} = (1)(1.6 \times 10^{-19})(10^{17}) A$$

$$A = 3.75 \times 10^{-2} \text{ cm}^2$$