

Chapter 14

Exercise Solutions

E14.1

$$v_{ICM}(\max) = V^+ - V_{SD1}(\text{sat}) - V_{SD1}$$

$$v_{ICM}(\min) = V^- + V_{DS4}(\text{sat}) + V_{SD1}(\text{sat}) - V_{SD1}$$

We have:

$$I_{REF} = 100 \mu\text{A}, \quad k'_n = 80 \mu\text{A}/\text{V}^2, \quad k'_p = 40 \mu\text{A}/\text{V}^2,$$

$$\left(\frac{W}{L}\right) = 25$$

For M_1 :

$$I_D = 50 = \left(\frac{40}{2}\right)(25)(V_{SD1} + V_{TP})^2$$

$$\text{So } 50 = 500(V_{SD1} - 0.5)^2 \Rightarrow V_{SD1} = 0.816\text{V}$$

$$V_{SD1}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

Then

$$v_{CM}(\max) = V^+ - 0.316 - 0.816 = V^+ - 1.13\text{V}$$

For M_4 :

$$I_D = 100 = \left(\frac{80}{2}\right)(25)(V_{GS4} - V_{TN})^2$$

$$\text{So } 100 = 1000(V_{GS4} - 0.5)^2 \Rightarrow V_{GS4} = 0.816\text{V}$$

$$V_{DS4}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

$$v_{CM}(\min) = V^- + 0.316 + 0.316 - 0.816 = V^- - 0.184$$

So

$$\underline{V^- - 0.184 \leq v_{CM} \leq V^+ - 1.13\text{V}}$$

E14.2

$$v_o(\max) = V^+ - V_{SD1}(\text{sat}) - V_{SD10}(\text{sat})$$

$$v_o(\min) = V^- + V_{DS4}(\text{sat}) + V_{DS6}(\text{sat})$$

Now

$$V_{SD1} = V_{SD10} = \sqrt{\frac{50}{(40/2)(25)}} + 0.5 = 0.816\text{V}$$

$$V_{SD6}(\text{sat}) = V_{SD10}(\text{sat}) = 0.316\text{V}$$

$$\text{So } v_o(\max) = V^+ - 0.316 - 0.316 = V^+ - 0.632$$

Also

$$V_{GS6} = \sqrt{\frac{50}{(80/2)(25)}} + 0.5 = 0.724\text{V}$$

$$V_{GS4} = \sqrt{\frac{100}{(80/2)(25)}} + 0.5 = 0.816\text{V}$$

$$V_{DS6}(\text{sat}) = 0.724 - 0.5 = 0.224\text{V}$$

$$V_{DS4}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

$$\text{So } v_o(\min) = V^- + 0.316 + 0.224 = V^- + 0.54$$

Then

$$\underline{V^- + 0.54 \leq v_o \leq V^+ - 0.632\text{V}}$$

E14.3

$$\text{a. } A_{CL} = \frac{-50}{1 + \left(\frac{1}{5 \times 10^4}\right)(51)} \Rightarrow \underline{A_{CL} = -49.949}$$

$$\text{b. } \frac{dA_{CL}}{A_{CL}} = 10 \times \frac{51}{5 \times 10^4} \Rightarrow \frac{dA_{CL}}{A_{CL}} = 0.0102\%$$

$$A_{CL} = \frac{-50}{1 + \frac{51}{4.5 \times 10^4}} \Rightarrow \underline{A_{CL} = -49.943}$$

E14.4

$$A_{CL}(\text{ideal}) = -\frac{500}{20} = -25$$

$$\text{Within } 0.1\% \Rightarrow -25 + (0.001)(25)$$

$$\Rightarrow A_{CL} = -24.975$$

$$-24.975 = \frac{-25}{1 + \frac{26}{A_{OL}}}$$

$$\frac{26}{A_{OL}} = \frac{-25}{-24.975} - 1 = 0.0010$$

$$\underline{A_{OL} = 25.974}$$

E14.5

$$\text{a. } A_{CL} = \frac{A_{CL}(\infty)}{1 + \left[\frac{A_{CL}(\infty)}{A_{OL}}\right]}$$

$$A_{CL}(\infty) = 1 + \frac{R_2}{R_1} = 1 + \frac{495}{5} = 100$$

$$A_{CL} = \frac{100}{1 + \frac{100}{10^5}} \Rightarrow \underline{A_{CL} = 99.90}$$

$$\underline{A_{CL}(\infty) = 100}$$

$$\text{b. } \frac{dA_{CL}}{A_{CL}} = 10 \times \frac{100}{10^5} = \underline{0.01\%}$$

$$A_{CL} = 99.90 - (0.0001)(99.90)$$

$$\Rightarrow \underline{A_{CL} = 99.89}$$

E14.6

$$\frac{A_{CL}(\infty) - A_{CL}}{A_{CL}(\infty)} = 1 - \frac{A_{CL}}{A_{CL}(\infty)} = 1 - \frac{1}{1 + \frac{A_{CL}(\infty)}{A_{CL}}}$$

$$\text{So } 0.001 = \frac{1 + \frac{A_{CL}(\infty)}{A_{CL}} - 1}{1 + \frac{A_{CL}(\infty)}{A_{CL}}} = \frac{\frac{A_{CL}(\infty)}{A_{CL}}}{1 + \frac{A_{CL}(\infty)}{A_{CL}}}$$

$$0.001 = 0.999 \cdot \frac{A_{CL}(\infty)}{A_{OL}}$$

$$A_{CL}(\infty) = \frac{0.001}{0.999} \cdot A_{OL} = \frac{0.001}{0.999} \cdot (10^4)$$

$$\Rightarrow \underline{A_{CL}(\infty) = 10.010}$$

or

$$A_{CL} = (1 - 0.001)(10.010)$$

$$\Rightarrow \underline{A_{CL} = 10.0}$$

E14.7

a. For $R_o = 0$

$$\frac{1}{R_{if}} = \frac{1}{10} + \frac{1}{10}(1 + 10^4) = 0.1 + 10^3$$

$$\Rightarrow \underline{R_{if} = 10^{-3} \text{ k}\Omega = 1 \text{ }\Omega}$$

b. For $R_o = 10 \text{ k}\Omega$

$$\frac{1}{R_{if}} = \frac{1}{10} + \frac{1}{10} \times \left[\frac{1 + 10^4 + 1}{1 + 1 + 1} \right] \approx 0.1 + \frac{10^4}{3(10)}$$

$$R_{if} = 3 \times 10^{-3} \text{ k}\Omega$$

$$\Rightarrow \underline{R_{if} = 3 \text{ }\Omega}$$

E14.8

$$\frac{i_f}{i_1} = \left(\frac{R_{if}}{R_i} \right)$$

$$\text{a. } \frac{i_f}{i_1} = \frac{0.1}{10^4} = \underline{1 \times 10^{-5}}$$

$$\text{b. } \frac{i_f}{i_1} = \frac{10}{10^4} = \underline{1 \times 10^{-3}}$$

E14.9

$$R_{if} = \frac{40(1 + 10^4) + 99 \left(1 + \frac{40}{1} \right)}{1 + \frac{99}{1}}$$

$$\approx \frac{4 \times 10^5 + 4.059 \times 10^3}{100}$$

$$R_{if} = 4.04 \times 10^3 \text{ k}\Omega \Rightarrow \underline{R_{if} = 4.04 \text{ M}\Omega}$$

E14.10

Voltage follower $R_2 = 0$, $R_1 = \infty$

$$R_{if} = R_i(1 + A_{OL}) = 10(1 + 5 \times 10^5)$$

$$\approx 5 \times 10^6 \text{ k}\Omega \Rightarrow \underline{R_{if} = 5000 \text{ M}\Omega}$$

E14.11

$$1 + \frac{R_2}{R_1} = 100$$

$$\text{a. } \frac{1}{R_{of}} = \frac{1}{100} \left[\frac{10^5}{100} \right] = 10$$

$$\Rightarrow \underline{R_{of} = 0.1 \text{ }\Omega}$$

$$\text{b. } \frac{1}{R_{of}} = \frac{1}{10} \left[\frac{10^5}{100} \right] = 10^2$$

$$R_{of} = 10^{-2} \text{ k}\Omega \Rightarrow \underline{R_{of} = 10 \text{ }\Omega}$$

E14.12

From Equation (14.43)

$$A_{CL}(f) = \frac{A_{CLo}}{1 + j \cdot \frac{f}{f_{PD}(A_o/A_{CLo})}}$$

$$= \frac{25}{1 + j \cdot \frac{f}{(50)(10^4/25)}} = \frac{25}{1 + j \cdot \frac{f}{2 \times 10^4}}$$

a. For $f = 2 \text{ kHz}$

$$\frac{v_o}{v_i} = 25 \Rightarrow \underline{v_o(\text{peak}) = 1.25 \text{ mV}}$$

b. $f = 20 \text{ kHz}$

$$\frac{v_o}{v_i} = \frac{1}{\sqrt{2}} \cdot 25 \Rightarrow \underline{v_o(\text{peak}) = 0.384 \text{ mV}}$$

c. $f = 100 \text{ kHz}$

$$\frac{v_o}{v_i} = \frac{25}{\sqrt{1 + (100/20)^2}} = \frac{25}{5.099} = 4.90$$

$$\Rightarrow \underline{v_o = 0.245 \text{ mV}}$$

E14.13

Full-scale response = $1 \times 5 = 5 \text{ V}$

$$t = \frac{5}{2} \Rightarrow \underline{t = 2.5 \text{ }\mu\text{s}}$$

E14.14

$$\text{a. } F_{PBW} = \frac{SR}{2\pi V_o(\text{max})} = \frac{0.63 \times 10^6}{2\pi(1)}$$

$$F_{PBW} = 1.0 \times 10^5 \Rightarrow \underline{F_{PBW} = 100 \text{ kHz}}$$

$$\text{b. } F_{PBW} = \frac{0.63 \times 10^6}{2\pi(10)} = 1.0 \times 10^4$$

$$\Rightarrow \underline{F_{PBW} = 10 \text{ kHz}}$$

E14.15

$$f_{3dB} = \frac{f_T}{A_{CL0}} = \frac{(10^5)(10)}{50} \Rightarrow 20 \text{ kHz}$$

$$f_{max} = f_{3dB} = \frac{SR}{2\pi V_0(\max)}$$

$$V_0(\max) = \frac{SR}{2\pi f_{3dB}} = \frac{0.8 \times 10^6}{2\pi(20 \times 10^3)}$$

$$\Rightarrow \underline{V_0(\max) = 6.37 \text{ V}}$$

E14.16

$$|V_{OS}| = \left| V_T \ln \left(\frac{I_{S2}}{I_{S1}} \right) \right| = (0.026) \ln \left(\frac{1.85 \times 10^{-14}}{2 \times 10^{-14}} \right)$$

$$\Rightarrow \underline{V_{OS} = 2.03 \text{ mV}}$$

E14.17

We need

$$i_{C1} = i_{C2}, \nu_{BE3} = \nu_{EC1} = 0.6 \text{ V, and}$$

$$\nu_{CE1} = \nu_{CE2} = 10 \text{ V}$$

By Equation (14.60(a))

$$i_{C1} = I_{S1} \left[\exp \left(\frac{\nu_{BE1}}{V_T} \right) \right] \left(1 + \frac{10}{50} \right)$$

$$= I_{S3} \left[\exp \left(\frac{\nu_{BE3}}{V_T} \right) \right] \left(1 + \frac{0.6}{50} \right)$$

By Equation (14.60(b))

$$i_{C2} = I_{S2} \left[\exp \left(\frac{\nu_{BE2}}{V_T} \right) \right] \left(1 + \frac{10}{50} \right)$$

$$= I_{S4} \left[\exp \left(\frac{\nu_{BE4}}{V_T} \right) \right] \left(1 + \frac{0.6}{50} \right)$$

 $I_{S1} = I_{S2}$, take the ratio:

$$\exp \left(\frac{\nu_{BE1} - \nu_{BE2}}{V_T} \right) = \frac{I_{S3}}{I_{S4}}$$

$$\nu_{BE1} - \nu_{BE2} = V_{OS} = V_T \ln \left(\frac{I_{S3}}{I_{S4}} \right)$$

$$= 0.026 \cdot \ln(1.05)$$

$$\Rightarrow \underline{V_{OS} = 1.27 \text{ mV}}$$

E14.18

$$V_{OS} = \frac{1}{2} \cdot \sqrt{\frac{I_Q}{2K_n}} \cdot \left(\frac{\Delta K_n}{K_n} \right)$$

$$0.020 = \frac{1}{2} \cdot \sqrt{\frac{150}{2(50)}} \cdot \left(\frac{\Delta K_n}{50} \right)$$

$$\Rightarrow \underline{\Delta K_n = 1.63 \mu A/V^2}$$

$$\Rightarrow \frac{\Delta K_n}{K_n} = \frac{1.63}{50} \Rightarrow \underline{3.26 \%}$$

E14.19

$$\text{Want } \left(\frac{R_5}{R_5 + R_4} \right) V^+ = 5 \text{ mV}$$

$$R_5 \ll R_4 \text{ so } \frac{R_5}{R_4} \times V^+ = 0.005$$

$$R_5 = \frac{(0.005)(100)}{10} = 0.05 \text{ k}\Omega$$

$$\Rightarrow \underline{R_5 = 50 \Omega}$$

E14.20

$$R'_1 = 25 \parallel 1 = 0.9615 \text{ k}\Omega$$

$$R'_2 = 75 \parallel 1 = 0.9868 \text{ k}\Omega$$

$$\text{For } I_Q = 100 \mu A \Rightarrow i_{C1} = i_{C2} = 50 \mu A$$

From Equation (14.75)

$$(0.026) \ln \left(\frac{50 \times 10^{-6}}{10^{-14}} \right) + (0.050)(0.9615)$$

$$= (0.026) \ln \left(\frac{i_{C2}}{I_{S4}} \right) + (0.050)(0.9868)$$

$$0.58065 + 0.049075$$

$$= (0.026) \ln \left(\frac{i_{C2}}{I_{S4}} \right) + 0.04934$$

$$\ln \left(\frac{i_{C2}}{I_{S4}} \right) = 22.284$$

$$\frac{50 \times 10^{-6}}{I_{S4}} = 4.7625 \times 10^9$$

$$\underline{I_{S4} = 1.05 \times 10^{-14} \text{ A}}$$

E14.21

From Equation (14.79)

$$v_o = I_{B1} R_2 - I_{B2} R_3 \left(1 + \frac{R_2}{R_1} \right)$$

For $v_o = 0$

$$0 = (1.1 \times 10^{-6})(100 \text{ k}\Omega) - (1.0 \times 10^{-6}) R_3 \left(1 + \frac{100}{10} \right)$$

$$R_3(11) = (1.1)(100 \text{ k}\Omega) \Rightarrow \underline{R_3 = 10 \text{ k}\Omega}$$

E14.22

$$\text{a. } v_o = I_{B1} R_3 = (10^{-6})(200 \times 10^3)$$

$$\Rightarrow \underline{v_o = 0.20 \text{ V}}$$


$$\text{b. } R_4 = R_1 \parallel R_2 \parallel R_3 = 100 \parallel 50 \parallel 200$$

$$\Rightarrow \underline{R_4 = 28.6 \text{ k}\Omega}$$

Chapter 14

Problem Solutions

14.1

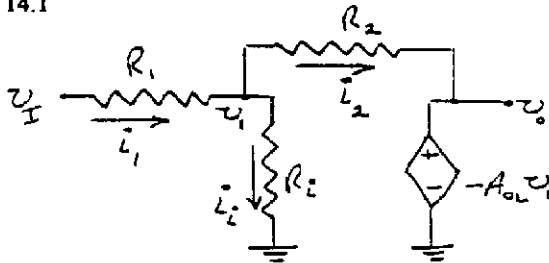

$$\frac{v_I - v_1}{R_1} = \frac{v_1 - v_o}{R_2} + \frac{v_1}{R_i} \text{ and } v_o = -A_{oL}v_1$$

$$\text{so that } v_1 = -\frac{v_o}{A_{oL}}$$

$$\frac{v_I}{R_1} + \frac{v_o}{R_2} = v_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right)$$

So

$$\frac{v_I}{R_1} = -v_o \left[\frac{1}{R_2} + \frac{1}{A_{oL}} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right) \right]$$

Then

$$\frac{v_o}{v_I} = \frac{-(1/R_1)}{\left[\frac{1}{R_2} + \frac{1}{A_{oL}} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right) \right]} = A_{CL}$$

From Equation (14.20) for $R_L = \infty$ and $R_o = 0$

$$\frac{1}{R_{i,f}} = \frac{1}{R_1} + \frac{1}{R_2} \cdot \frac{(1 + A_{oL})}{1}$$

a. For $R_i = 1 \text{ k}\Omega$

$$A_{CL} = \frac{-(1/20)}{\left[\frac{1}{100} + \frac{1}{10^3} \left(\frac{1}{20} + \frac{1}{100} + \frac{1}{1} \right) \right]} = \frac{-0.05}{[0.01 + 1.06 \times 10^{-3}]}$$

or

$$\Rightarrow A_{CL} = -4.52$$

$$\frac{1}{R_{i,f}} = \frac{1}{1} + \frac{1 + 10^3}{100} \Rightarrow R_{i,f} = 90.8 \Omega$$

b. For $R_i = 10 \text{ k}\Omega$

$$A_{CL} = \frac{-(1/20)}{\left[\frac{1}{100} + \frac{1}{10^3} \left(\frac{1}{20} + \frac{1}{100} + \frac{1}{10} \right) \right]} = \frac{-0.05}{[0.01 + 1.6 \times 10^{-4}]}$$

or

$$\Rightarrow A_{CL} = -4.92$$

$$\frac{1}{R_{i,f}} = \frac{1}{10} + \frac{1 + 10^3}{100} \Rightarrow R_{i,f} = 98.9 \Omega$$

c. For $R_i = 100 \text{ k}\Omega$


$$A_{CL} = \frac{-(1/20)}{\left[\frac{1}{100} + \frac{1}{10^3} \left(\frac{1}{20} + \frac{1}{100} + \frac{1}{100} \right) \right]} = \frac{-0.05}{[0.01 + 7 \times 10^{-5}]}$$

or

$$\Rightarrow A_{CL} = -4.965$$

$$\frac{1}{R_{i,f}} = \frac{1}{100} + \frac{1 + 10^3}{100} \Rightarrow R_{i,f} = 99.8 \Omega$$

14.2

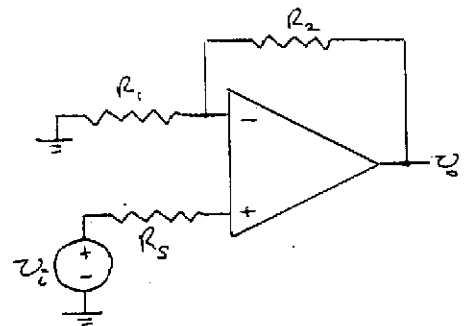

$$A_{CL} = \frac{v_o}{v_i} = \frac{\left(1 + \frac{R_2}{R_1} \right)}{\left[1 + \frac{1}{A_{oL}} \left(1 + \frac{R_2}{R_1} \right) \right]}$$

For the ideal:

$$\left(1 + \frac{R_2}{R_1} \right) = \frac{0.10}{0.002} = 50$$

$$v_o(\text{actual}) = (0.10)(1 - 0.001) = 0.0999$$

So

$$\frac{0.0999}{0.002} = \frac{50}{1 + \frac{1}{A_{oL}}(50)} = 49.95$$

which yields

$$A_{oL} = 1000$$

14.3

$$A_{v,f} = \frac{v_{o,f}}{v_i} = \frac{-\left(\frac{A_{oL}}{R_o} - \frac{1}{R_2} \right)}{\left(\frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2} \right)}$$

Or

$$v_{o1} = -\left(\frac{5 \times 10^3}{1} - \frac{1}{100}\right) \cdot v_i = \frac{-(4.99999 \times 10^3)}{1.11} \cdot v_i$$

$$v_{o1} = -4.504495 \times 10^3 \cdot v_i$$

Now

$$\frac{i_1}{v_i} = \frac{v_i - v_i}{R_1 v_i} = K$$

Then

$$v_i - v_i = KR_1 v_i$$

which yields

$$v_i = \frac{v_i}{KR_1 + 1}$$

Now

$$K = \frac{1}{10} + \frac{1}{100} \left[\frac{1 + 5 \times 10^3 + \frac{1}{10}}{1 + \frac{1}{10} + \frac{1}{100}} \right]$$

$$= (0.1) + (0.01) \left[\frac{5.0011 \times 10^3}{1.11} \right] = 45.15495$$

Then

$$v_i = \frac{v_i}{(45.15495)(10) + 1} = \frac{v_i}{452.5495}$$

We find

$$v_{o1} = -4.504495 \times 10^3 \left[\frac{v_i}{452.5495} \right]$$

Or

$$A_{v1} = \frac{v_{o1}}{v_i} = -9.9536$$

For the second stage, $R_L = \infty$

$$v_{o2} = -\left(\frac{5 \times 10^3}{1} - \frac{1}{100}\right) \cdot v_i' = \frac{-(4.99999 \times 10^3)}{\left(\frac{1}{1} + \frac{1}{100}\right)} \cdot v_i' = -4.950485 \times 10^3 \cdot v_i'$$

$$K = \frac{1}{10} + \frac{1}{100} \left[\frac{1 + 5 \times 10^3}{1 + \frac{1}{100}} \right] = 49.61485$$

$$v_i' = \frac{v_{o1}}{KR_1 + 1} = \frac{v_{o1}}{(49.61485)(10) + 1} = \frac{v_{o1}}{497.1485}$$

Then


$$\frac{v_{o2}}{v_{o1}} = \frac{-4.950485 \times 10^3}{497.1485} = -9.95776$$

So

$$A_v = \frac{v_{o2}}{v_i} = (-9.9536)(-9.95776) \Rightarrow$$

$$A_v = 99.12$$

14.4

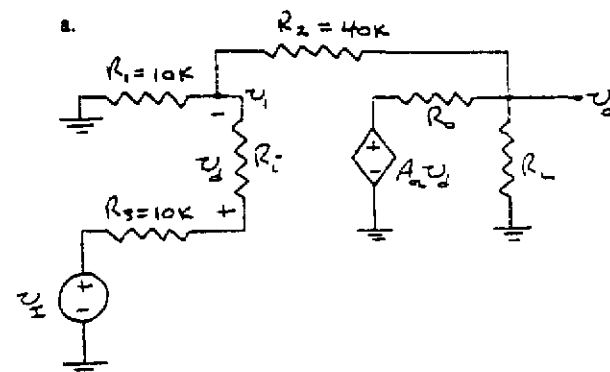

$$\frac{v_1 - v_I}{R_3 + R_4} + \frac{v_1}{R_1} + \frac{v_1 - v_0}{R_2} = 0 \quad (1)$$

$$v_1 \left[\frac{1}{R_3 + R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{v_0}{R_2} + \frac{v_I}{R_3 + R_4}$$

$$\frac{v_0}{R_L} + \frac{v_0 - A_{OL} v_d}{R_0} + \frac{v_0 - v_1}{R_2} = 0 \quad (2)$$

or

$$v_0 \left[\frac{1}{R_L} + \frac{1}{R_0} + \frac{1}{R_2} \right] = \frac{v_1}{R_2} + \frac{A_{OL} v_d}{R_0}$$

$$v_d = \left(\frac{v_I - v_1}{R_3 + R_4} \right) \cdot R_4 \quad (3)$$

So substituting numbers:

$$v_1 \left[\frac{1}{10 + 20} + \frac{1}{10} + \frac{1}{40} \right] = \frac{v_0}{40} + \frac{v_I}{10 + 20} \quad (1)$$

or

$$v_1 [0.15833] = v_0 [0.025] + v_I [0.03333]$$

$$v_0 \left[\frac{1}{1} + \frac{1}{0.5} + \frac{1}{40} \right] = \frac{v_1}{40} + \frac{(10^4) v_d}{0.5} \quad (2)$$

or

$$v_0 [3.025] = v_1 [0.025] + (2 \times 10^4) v_d$$

$$v_d = \left(\frac{v_I - v_1}{10 + 20} \right) \cdot 20 = 0.6667(v_I - v_1) \quad (3)$$

So

$$v_0 [3.025] = v_1 [0.025] + (2 \times 10^4) (0.6667)(v_I - v_1)$$

$$\text{or} \quad (2) \quad v_0 [3.025] = 1.333 \times 10^4 v_I - 1.333 \times 10^4 v_1$$

From (1):

$$v_1 = v_0(0.1579) + v_I(0.2105)$$

Then

$$\begin{aligned} v_0[3.025] &= 1.333 \times 10^4 v_I \\ &\quad - 1.333 \times 10^4 [v_0(0.1579) + v_I(0.2105)] \\ v_0[2.1078 \times 10^3] &= v_I[1.0524 \times 10^4] \end{aligned}$$

or

$$A_{CL} = \frac{v_0}{v_I} = 4.993$$

To find R_{if} : Use Equation (14.27)

$$\begin{aligned} i_I \left(1 + \frac{0.5}{1} + \frac{0.5}{40} \right) \\ = v_1 \left\{ \left(\frac{1}{10} + \frac{1}{40} \right) \left(1 + \frac{0.5}{1} + \frac{0.5}{40} \right) - \frac{0.5}{(40)^2} \right\} \\ \quad - \frac{(10^3)v_d}{40} \end{aligned}$$

$$i_I(1.5125) = v_1 \{ (0.125)(1.5125) - 0.0003125 \} - 25v_d$$

or

$$i_I(1.5125) = v_I \{ 0.18875 \} - 25v_d$$

Now

$$v_d = i_I R_i = i_I(20) \text{ and } v_1 = v_I - i_I(20)$$

So

$$\begin{aligned} i_I(1.5125) &= [v_I - i_I(20)] \cdot [0.18875] - 25i_I(20) \\ i_I[505.3] &= v_I(0.18875) \end{aligned}$$

or

$$\frac{v_I}{i_I} = 2677 \text{ k}\Omega$$

$$\text{Now } R_{if} = 10 + 2677 \Rightarrow \underline{R_{if} = 2.687 \text{ M}\Omega}$$

To determine R_{of} : Using Equation (14.36)

$$\frac{1}{R'_{of}} = \frac{1}{R_o} \cdot \left[\frac{A_{oL}}{1 + \frac{R_2}{R_1 || R_i}} \right] = \frac{1}{0.5} \cdot \left[\frac{10^3}{1 + \frac{40}{10 || 20}} \right]$$

$$\text{or } R'_{of} = 3.5 \Omega$$

$$\text{Then } R_{of} = 1 \text{ k}\Omega || 3.5 \Omega$$


$$\Rightarrow \underline{R_{of} = 3.49 \Omega}$$

b. Using Equation (14.16)

$$\frac{dA_{CL}}{A_{CL}} = (-10) \left(\frac{5}{10^3} \right) \Rightarrow \underline{\frac{dA_{CL}}{A_{CL}} = -(0.05)\%}$$

14.5

a.

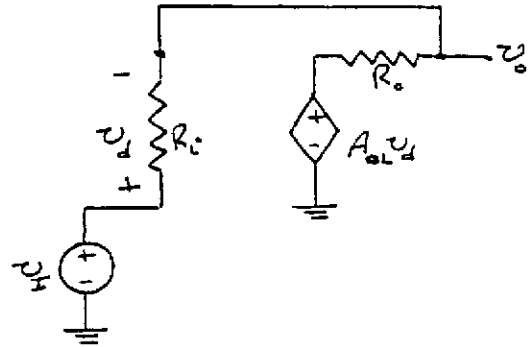

$$\frac{v_0 - A_{oL}v_d}{R_o} + \frac{v_0 - v_I}{R_i} = 0 \text{ and } v_d = v_I - v_0$$

So

$$\frac{v_0}{R_o} - \frac{A_{oL}}{R_o} \cdot (v_I - v_0) + \frac{v_0}{R_i} - \frac{v_I}{R_i} = 0$$

$$\begin{aligned} v_0 \left[\frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i} \right] &= v_I \left[\frac{1}{R_i} + \frac{A_{oL}}{R_o} \right] \\ v_0 \left[\frac{1}{0.2} + \frac{(10^4)}{0.2} + \frac{1}{100} \right] &= v_I \left[\frac{1}{100} + \frac{(10^4)}{0.2} \right] \\ v_0 [5.000501 \times 10^4] &= v_I [5.000001 \times 10^4] \end{aligned}$$

$$\text{So } A_{CL} = \frac{v_0}{v_I} = 0.9999$$

b. Set $v_I = 0$

$$i_o = \frac{v_0 - A_{oL}v_d}{R_o} + \frac{v_0}{R_i} \text{ and } v_d = -v_0$$

$$i_o = v_0 \left[\frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i} \right]$$

Then

$$\frac{1}{R'_{of}} = \frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i}$$


or

$$\frac{1}{R'_{of}} = \frac{1}{0.2} + \frac{(10^4)}{0.2} + \frac{1}{100}$$

which yields

$$\underline{R'_{of} \approx 0.02 \Omega}$$

14.6

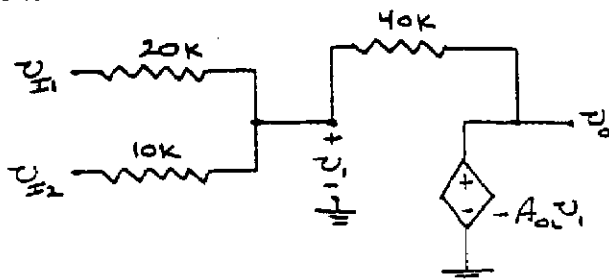

$$\frac{v_{I1} - v_1}{20} + \frac{v_{I2} - v_1}{10} = \frac{v_1 - v_0}{40}$$

$$\frac{v_{I1}}{20} + \frac{v_{I2}}{10} + \frac{v_0}{40} = v_1 \left[\frac{1}{20} + \frac{1}{10} + \frac{1}{40} \right]$$

and $v_0 = -A_{OL} v_1$ so that $v_1 = -\frac{v_0}{A_{OL}}$

Then


$$v_{I1}(0.05) + v_{I2}(0.10) = -v_0 \left\{ \frac{1}{40} + \frac{1}{2 \times 10^3} \cdot \left(\frac{7}{40} \right) \right\}$$

$$= -v_0 [2.50875 \times 10^{-2}]$$

$$\Rightarrow v_0 = -1.993 v_{I1} - 3.986 v_{I2}$$

$$\frac{\Delta v_0}{v_0} = \frac{2 - 1.993}{2} \Rightarrow \frac{\Delta v_0}{v_0} = 0.35\%$$

14.7

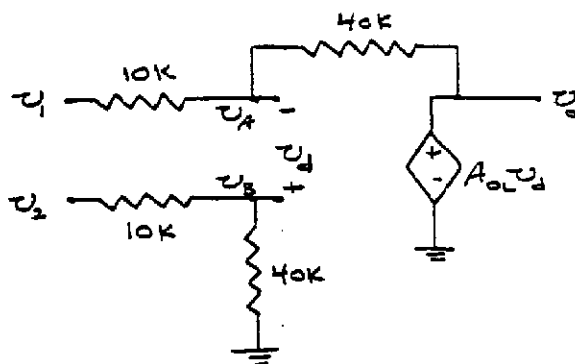

$$v_B = \left(\frac{40}{40 + 10} \right) v_2 = \left(\frac{4}{5} \right) v_2 = 0.8 v_2 \quad (1)$$

$$\frac{v_1 - v_A}{10} = \frac{v_A - v_0}{40}$$

$$\frac{v_1}{10} + \frac{v_0}{40} = v_A \left(\frac{1}{10} + \frac{1}{40} \right)$$

$$v_1(0.1) + v_0(0.025) = v_A(0.125) \quad (2)$$

$$v_0 = A_{OL} v_d = A_{OL} (v_B - v_A) \quad (3)$$

or

$$v_0 = A_{OL} [0.8 v_2 - v_A]$$

$$\frac{v_0}{A_{OL}} - 0.8 v_2 = -v_A$$

$$\Rightarrow v_A = 0.8 v_2 - \frac{v_0}{A_{OL}}$$

Then

$$v_1(0.1) + v_0(0.025) = (0.125) \left[0.8 v_2 - \frac{v_0}{A_{OL}} \right]$$

$$v_1(0.1) - v_2(0.1) = -v_0 \left[0.025 + \frac{0.125}{10^3} \right]$$

$$= -v_0 [2.5125 \times 10^{-2}]$$

$$\Rightarrow A_d = \frac{v_0}{v_2 - v_1} = 3.9801$$

$$\Rightarrow \frac{\Delta A_d}{A_d} = \frac{0.0199}{4} \Rightarrow 0.4975\%$$

14.8

- a. Considering the second op-amp and Equation (14.20), we have

$$\frac{1}{R_{i,f2}} = \frac{1}{10} + \frac{1}{0.1} \cdot \left[\frac{1 + 100}{1 + \frac{1}{0.1}} \right] = 0.10 + \frac{101}{(0.1)(11)}$$

So $R_{i,f2} = 0.0109 \text{ k}\Omega$

The effective load on the first op-amp is then

$$R_{L1} = 0.1 + R_{i,f2} = 0.1109 \text{ k}\Omega$$

Again using Equation (14.20), we have

$$\frac{1}{R_{i,f}} = \frac{1}{10} + \frac{1}{1} \cdot \frac{1 + 100 + \frac{1}{0.1109}}{1 + \frac{1}{0.1109} + \frac{1}{1}} = 0.10 + \frac{110.017}{11.017}$$

so that

$$R_{i,f} = 99.1 \Omega$$

- b. To determine $R_{o,f}$:

For the first op-amp, we can write, using Equation (14.36)

$$\frac{1}{R_{o,f1}} = \frac{1}{R_o} \cdot \left[\frac{A_{OL}}{1 + \frac{R_2}{R_1 \| R_i}} \right] = \frac{1}{1} \cdot \left[\frac{100}{1 + \frac{40}{1 \| 10}} \right]$$

which yields $R_{o,f1} = 0.021 \text{ k}\Omega$


For the second op-amp, then

$$\frac{1}{R_{of}} = \frac{1}{R_o} \cdot \left[\frac{A_{OL}}{1 + \frac{R_2}{(R_1 + R_{of}) \parallel R_i}} \right]$$

$$= \frac{1}{1} \cdot \left[\frac{100}{1 + \frac{0.10}{(0.121) \parallel 10}} \right]$$

or $R_{of} = 18.4 \Omega$

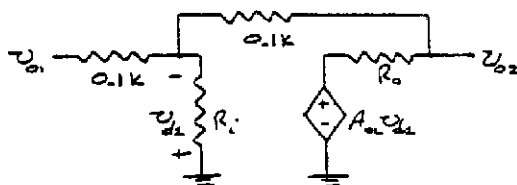c. To find the gain, consider the second op-amp.



$$\frac{v_{o1} - (-v_{o2})}{0.1} + \frac{v_{o2}}{R_i} = \frac{-v_{o2} - v_{o1}}{0.1} \quad (1)$$

$$\frac{v_{o1}}{0.1} + v_{o2} \left(\frac{1}{0.1} + \frac{1}{10} + \frac{1}{0.1} \right) = -\frac{v_{o2}}{0.1}$$

or

$$v_{o1}(10) + v_{o2}(20.1) = -v_{o2}(10)$$

$$\frac{v_{o2} - A_{OL} v_{o2}}{R_o} + \frac{v_{o2} - (-v_{o2})}{0.1} = 0 \quad (2)$$

$$\frac{v_{o2}}{1} - v_{o2} \left(\frac{100}{1} - \frac{1}{0.1} \right) + \frac{v_{o2}}{0.1} = 0$$

$$v_{o2}(11) - v_{o2}(90) = 0$$

or

$$v_{o2} = v_{o2}(0.1222)$$


Then Equation (1) becomes

$$v_{o1}(10) + v_{o2}(0.1222)(20.1) = -v_{o2}(10)$$

or

$$v_{o1} = -v_{o2}(1.246)$$

Now consider the first op-amp.

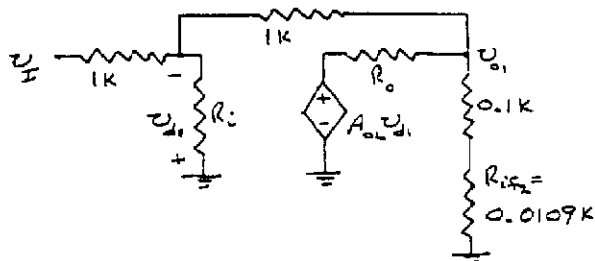

$$\frac{v_I - (-v_{d1})}{1} + \frac{v_{d1}}{R_i} = \frac{-v_{d1} - v_{o1}}{1} \quad (1)$$

$$v_I(1) + v_{d1} \left(\frac{1}{1} + \frac{1}{10} + \frac{1}{1} \right) = -v_{o1}(1)$$

or

$$v_I(1) + v_{d1}(2.1) = -v_{o1}(1)$$

$$\frac{v_{o1}}{0.1109} + \frac{v_{o1} - A_{OL} v_{d1}}{R_o} + \frac{v_{o1} - (-v_{d1})}{1} = 0 \quad (2)$$

$$v_{o1} \left(\frac{1}{0.1109} + \frac{1}{1} + \frac{1}{1} \right) - v_{d1} \left(\frac{100}{1} - \frac{1}{1} \right) = 0$$

$$v_{o1}(11.017) - v_{d1}(99) = 0$$

or

$$v_{d1} = v_{o1}(0.1113)$$

Then Equation (1) becomes

$$v_I(1) + v_{o1}(0.1113)(2.1) = -v_{o1}$$

$$\text{or } v_I = -v_{o1}(1.234)$$

$$\text{We had } v_{o1} = -v_{o2}(1.246)$$

$$\text{So } v_I = v_{o2}(1.246)(1.234)$$

$$\text{or } \frac{v_{o2}}{v_I} = 0.650$$

d. Ideal $\frac{v_{o2}}{v_I} = 1$

So ratio of actual to ideal = 0.650.

14.9

The open loop gain can be written as

$$A_{OL}(f) = \frac{A_0}{\left(1 + j \cdot \frac{f}{f_{PD}}\right) \left(1 + j \cdot \frac{f}{5 \times 10^6}\right)}$$

where $A_0 = 2 \times 10^5$.

The closed-loop response is

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

At low frequency,

$$100 = \frac{2 \times 10^5}{1 + \beta(2 \times 10^5)}$$

So that $\beta = 9.995 \times 10^{-3}$.

Assuming the second pole is the same for both the open-loop and closed-loop, then

$$\phi = -\tan^{-1}\left(\frac{f}{f_{PD}}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^6}\right)$$

For a phase margin of 80° , $\phi = -100^\circ$.

So

$$-100 = -90 - \tan^{-1}\left(\frac{f}{5 \times 10^6}\right)$$

or

$$f = 8.816 \times 10^5 \text{ Hz}$$

Then

$$|A_{OL}| = 1 = \frac{2 \times 10^5}{\sqrt{1 + \left(\frac{8.816 \times 10^5}{f_{PD}}\right)^2} \sqrt{1 + \left(\frac{8.816 \times 10^5}{5 \times 10^6}\right)^2}}$$

or

$$\frac{8.816 \times 10^5}{f_{PD}} \approx 1.9696 \times 10^5$$

or

$$f_{PD} = 4.48 \text{ Hz}$$

14.10

(a) 1st stage

$$(10)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 100 \text{ kHz}$$

2nd stage

$$(50)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 20 \text{ kHz}$$

Bandwidth of overall system $\approx 20 \text{ kHz}$


(b) If each stage has the same gain, so

$$K^2 = 500 \Rightarrow K = 22.36$$

Then bandwidth of each stage

$$(22.36)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 44.7 \text{ kHz}$$

14.11

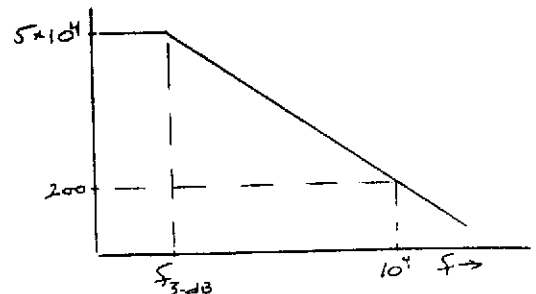

$$A = \frac{A_0}{1 + j \frac{f}{f_{3-dB}}}$$

$$|A| = \frac{A_0}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}}$$

$$200 = \frac{5 \times 10^4}{\sqrt{1 + \left(\frac{10^4}{f_{3-dB}}\right)^2}} \Rightarrow f_{3-dB} = 40 \text{ Hz}$$

Then

$$f_T = (5 \times 10^4)(40) \Rightarrow f_T = 2 \text{ MHz}$$

14.12

$$(5 \times 10^4)f_{PD} = 10^6 \Rightarrow f_{PD} = 20 \text{ Hz}$$

$$(25)f_{3-dB} = 10^6 \Rightarrow f_{3-dB} = 40 \text{ kHz}$$

$$A_v = \frac{A_{v0}}{1 + j \frac{f}{f_{3-dB}}} \Rightarrow |A_v| = \frac{25}{\sqrt{1 + \left(\frac{f}{40 \times 10^3}\right)^2}}$$

At $f = 0.5f_{3-dB} = 20 \text{ kHz}$

$$|A_v| = \frac{25}{\sqrt{1 + (0.5)^2}} = 22.36$$

At $f = 2f_{3-dB} = 80 \text{ kHz}$

$$|A_v| = \frac{25}{\sqrt{1 + (2)^2}} = 11.18$$

14.13

$$(20 \times 10^3) \cdot |A_v|_{\max} = 10^6 \Rightarrow |A_v|_{\max} = 50$$

14.14

From Equation (14.55),

$$FPBW = \frac{SR}{2\pi V_{PO}} = \frac{10 \times 10^6}{2\pi(10)}$$

or

$$FPBW = f_{\max} = 159 \text{ kHz}$$

14.15


a. Using Equation (14.55),

$$V_{P0} = \frac{8 \times 10^6}{2\pi(250 \times 10^3)}$$

or

$$V_{P0} = 5.09 \text{ V}$$

b.

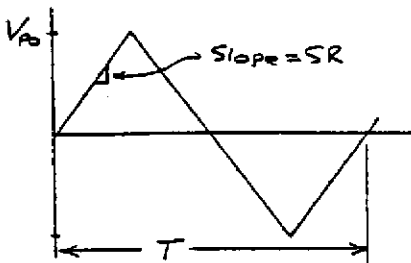

$$\text{Period } T = \frac{1}{f} = \frac{1}{250 \times 10^3} = 4 \times 10^{-6} \text{ s}$$

One-fourth period = $1 \mu\text{s}$

$$\text{Slope} = \frac{V_{P0}}{1 \mu\text{s}} = SR = 8 \text{ V}/\mu\text{s}$$


$$\Rightarrow V_{P0} = 8 \text{ V}$$

14.16


For input (a), maximum output is 5 V.

$$SR = 1 \text{ V}/\mu\text{s}$$


so

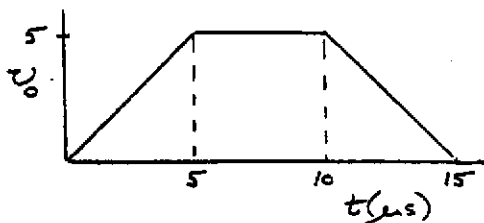

For input (b), maximum output is 2 V.

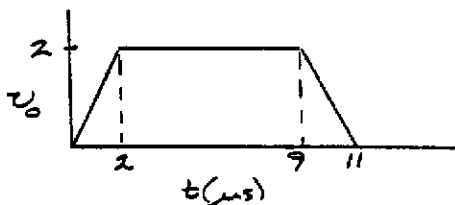


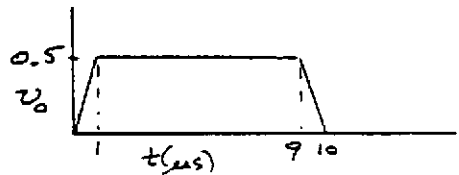For input (c), maximum output is 0.5 V so the output is




14.17


For input (a), $\max |v_{O1}| = 3 \text{ V}$.

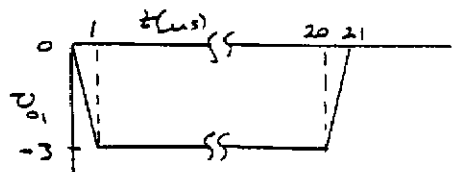


$$\text{Then } |v_{O2}|_{\max} = 3(3) = 9 \text{ V}$$

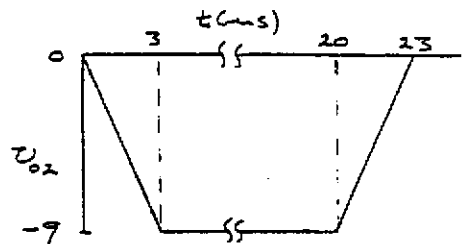

For input (b), $\max |v_{O1}| = 1.5 \text{ V}$.

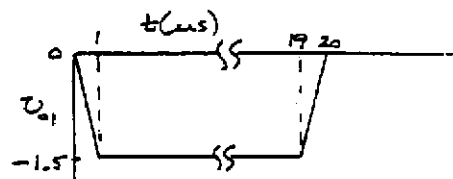

$$\text{Then } |v_{O2}|_{\max} = 3(1.5) = 4.5 \text{ V}$$

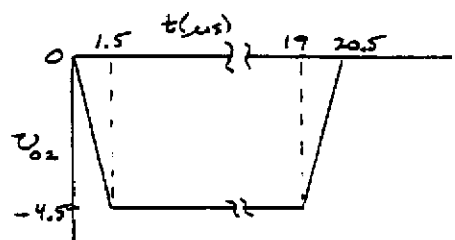

14.18

$$f_{max} = 20 \text{ kHz}, \quad SR = 0.8 \text{ V} / \mu\text{s}$$

$$V_p = \frac{SR}{2\pi f_{max}} = \frac{0.8 \times 10^6}{2\pi(20 \times 10^3)} \Rightarrow$$

$$\underline{V_p = 6.37 \text{ V}}$$

14.19

$$I_1 = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right), \quad I_2 = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$

Want $I_1 = I_2$, so

$$\frac{I_1}{I_2} = 1 = \frac{5 \times 10^{-14}(1+x) \exp\left(\frac{V_{BE1}}{V_T}\right)}{5 \times 10^{-14}(1-x) \exp\left(\frac{V_{BE2}}{V_T}\right)}$$

$$= \frac{(1+x)}{(1-x)} \exp\left(\frac{V_{BE1} - V_{BE2}}{V_T}\right)$$

Or

$$\frac{1+x}{1-x} = \exp\left(\frac{V_{BE2} - V_{BE1}}{V_T}\right) = \exp\left(\frac{V_{OS}}{V_T}\right)$$

$$= \exp\left(\frac{0.0025}{0.026}\right) = 1.10$$

Now

$$1+x = (1-x)(1.10) \Rightarrow$$

$$x = 0.0476 \Rightarrow 4.76\%$$

14.20

From Equation (14.62),

$$\left(\frac{1 + \frac{V_{CE1}}{V_{AN}}}{1 + \frac{V_{EB}}{V_{AP}}}\right) = \frac{I_{S3}}{I_{S4}} \cdot \left(\frac{1 + \frac{V_{CE2}}{V_{AN}}}{1 + \frac{V_{EC4}}{V_{AP}}}\right)$$

For $V_{CE1} = 0.6 \text{ V}$, then $V_{EC4} = 5 \text{ V}$. We have $V_{CE1} = 5 \text{ V}$ so

$$\left(\frac{1 + \frac{5}{80}}{1 + \frac{0.6}{80}}\right) = \frac{I_{S3}}{I_{S4}} \cdot \left(\frac{1 + \frac{0.6}{80}}{1 + \frac{5}{80}}\right)$$

or

$$\frac{I_{S3}}{I_{S4}} = \frac{(1.0625)^2}{(1.0073)^2} = 1.112$$


So

$$I_{S3} = (10^{-14})(1.112)$$

or

$$\underline{I_{S3} = 1.112 \times 10^{-14} \text{ A}}$$

14.21

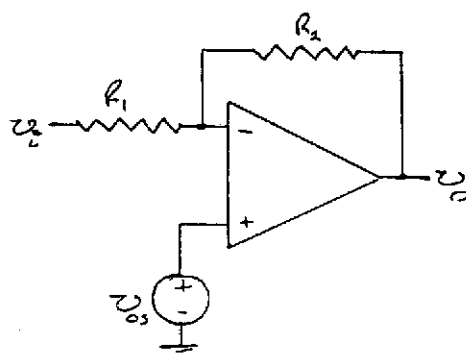

By superposition:

$$v_o(v_i) = -\frac{R_2}{R_1} \cdot v_i = -50v_i$$

$$v_o(v_{os}) = \left(1 + \frac{R_2}{R_1}\right) \cdot v_{os} = 51v_{os}$$

So

$$v_o = v_o(v_i) + v_o(v_{os}) = -50v_i + 51v_{os}$$

For $v_i = 20 \text{ mV}$ and $v_{os} = 2.5 \text{ mV}$

$$v_o = -50(0.02) + 51(0.0025) = -0.8725 \text{ V}$$


For $v_i = 20 \text{ mV}$ and $v_{os} = -2.5 \text{ mV}$

$$v_o = -50(0.02) + 51(-0.0025) = -1.1275 \text{ V}$$

So

$$-1.1275 \leq v_o \leq -0.8725 \text{ V}$$

14.22

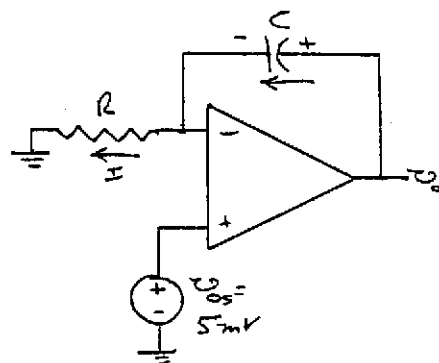

$$I = \frac{0.5 \times 10^{-3}}{10^4} = 5 \times 10^{-8} \text{ A}$$

Also

$$I = C \frac{dV_o}{dt} \Rightarrow V_o = \frac{1}{C} \int I dt = \frac{I}{C} \cdot t$$

Then

$$5 = \frac{5 \times 10^{-8}}{10 \times 10^{-6}} t \Rightarrow \underline{t = 10^3 \text{ s}}$$

14.23

a.

$$|v_{o1}| = 10 \left(1 + \frac{100}{10} \right) \text{ or } |v_{o1}| = 110 \text{ mV}$$

Then

$$|v_{o2}| = |v_{o1}|(5) + 10 \left(1 + \frac{50}{10} \right) = (110)(5) + (10)(6)$$

or

$$|v_{o2}| = 610 \text{ mV}$$

14.24

 v_o due to v_I

$$v_o = (0.5) \left(1 + \frac{1}{1.1} \right) = 0.9545 \text{ V}$$

Wiper arm at $V^+ = 10 \text{ V}$, (using superposition)

$$v_1 = \left(\frac{R_1 \| R_5}{R_1 \| R_5 + R_4} \right) (10) = \left(\frac{0.0909}{0.0909 + 10} \right) (10) \\ = 0.090$$

$$\text{Then } v_{o1} = - \left(\frac{1}{1} \right) (0.090) = -0.090$$

Wiper arm in center, $v_1 = 0$ and $v_{o2} = 0$ Wiper arm at $V^- = -10 \text{ V}$, $v_1 = -0.090$

So

$$v_{o3} = 0.090$$

Finally, total output v_o : (from superposition)Wiper arm at V^+ ,

$$v_o = 0.8645 \text{ V}$$

Wiper arm in center,

$$v_o = 0.9545 \text{ V}$$

Wiper arm at V^- ,

$$v_o = 1.0445 \text{ V}$$

14.25

$$\text{a. } R'_1 = R'_2 = 0.5 \| 25 = 0.490 \text{ k}\Omega$$

or

$$R'_1 = R'_2 = 490 \Omega$$

b. From Equation (14.75),

$$(0.026) \ln \left(\frac{125 \times 10^{-6}}{2 \times 10^{-14}} \right) + (0.125) R'_1 \\ = (0.026) \ln \left(\frac{125 \times 10^{-6}}{2.2 \times 10^{-14}} \right) + (0.125) R'_2$$

$$0.586452 + (0.125) R'_1 = 0.583974 + (0.125) R'_2$$

$$0.002478 = (0.125) (R'_2 - R'_1)$$

$$\text{So } R'_2 - R'_1 = 0.0198 \text{ k}\Omega \Rightarrow 19.8 \Omega$$

Then

$$\frac{R_2(1-x)R_x}{R_2 + (1-x)R_x} - \frac{R_1 x R_x}{R_1 + x R_x} = 0.0198$$

$$\frac{(0.5)(1-x)(50)}{(0.5) + (1-x)(50)} - \frac{(0.5)(50)x}{(0.5) + x(50)} = 0.0198$$

$$\frac{25(1-x)}{50.5 - 50x} - \frac{25x}{0.5 + 50x} = 0.0198$$

$$\frac{(0.5 + 50x)(25 - 25x) - (25x)(50.5 - 50x)}{(50.5 - 50x)(0.5 + 50x)} \\ = 0.0198$$

$$25\{0.5 - 0.5x + 50x - 50x^2 - 50.5x + 50x^2\} \\ = 0.0198\{25.25 + 2525x - 25x - 2500x^2\}$$

$$25\{0.5 - x\} = 0.0198\{25.25 + 2500x - 2500x^2\}$$

$$0.5 - x = 0.01998 + 1.98x - 1.98x^2$$

$$1.98x^2 - 2.98x + 0.48 = 0$$

$$x = \frac{2.98 \pm \sqrt{(2.98)^2 - 4(1.98)(0.48)}}{2(1.98)}$$

So

$$x = 0.183$$

and

$$1 - x = 0.817$$

14.26

$$R'_1 = R_1 \| 15 = 0.5 \| 15 = 0.4839 \text{ k}\Omega$$

$$R'_2 = R_2 \| 35 = 0.5 \| 35 = 0.4930 \text{ k}\Omega$$

From Equation (14.75),

$$(0.026) \ln \left(\frac{i_{C1}}{I_{S3}} \right) + i_{C1} R'_1 = (0.026) \ln \left(\frac{i_{C2}}{I_{S4}} \right) + i_{C2} R'_2$$

$$(0.026) \ln \left(\frac{i_{C1}}{i_{C2}} \right) = i_{C2} R'_2 - i_{C1} R'_1$$

$$(0.026) \ln \left(\frac{i_{C1}}{i_{C2}} \right) = i_{C2} R'_2 \left[1 - \frac{i_{C1}}{i_{C2}} \cdot \frac{R'_1}{R'_2} \right]$$

$$(0.026) \ln \left(\frac{i_{C1}}{i_{C2}} \right) = i_{C2} (0.4930) \left[1 - (0.9815) \left(\frac{i_{C1}}{i_{C2}} \right) \right]$$

By trial and error:


$$i_{C1} = 252 \mu\text{A} \text{ and } i_{C2} = 248 \mu\text{A}$$

or

$$\frac{i_{C1}}{i_{C2}} = 1.0155$$

14.27

a.

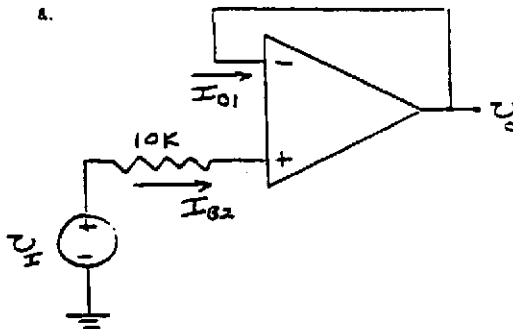


$$\text{For } I_{B2} = 1 \mu\text{A, then } v_O = -(10^{-6})(10^4)$$

or

$$v_O = -0.010 \text{ V}$$

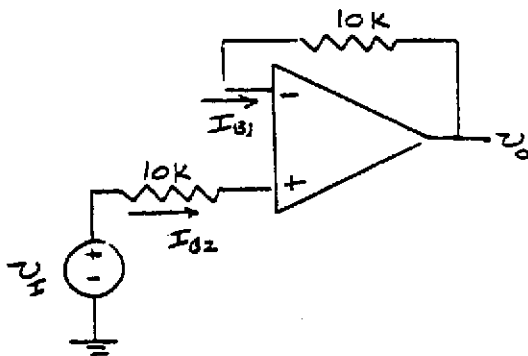b. If a $10 \text{ k}\Omega$ resistor is included in the feedback loop



$$\text{Now } v_O = -I_{B2}(10) + I_{B1}(10) = 0$$

Circuit is compensated if $I_{B1} = I_{B2}$.

14.28

From Equation (14.83), we have

$$v_O = R_2 I_{OS}$$

where $R_2 = 40 \text{ k}\Omega$ and $I_{OS} = 3 \mu\text{A}$.

Then

$$v_O = (40 \times 10^3)(3 \times 10^{-6})$$

or

$$v_O = 0.12 \text{ V}$$

14.29

a. Assume all bias currents are in the same direction and into each op-amp:

$$v_{O1} = I_{B1}(100 \text{ k}\Omega) = (10^{-6})(10^5) \Rightarrow v_{O1} = 0.1 \text{ V}$$

Then

$$\begin{aligned} v_{O2} &= v_{O1}(-5) + I_{B1}(50 \text{ k}\Omega) \\ &= (0.1)(-5) + (10^{-6})(5 \times 10^4) \\ &= -0.5 + 0.05 \end{aligned}$$

or

$$v_{O2} = -0.45 \text{ V}$$

b. Connect $R_3 = 10 \parallel 100 = 9.09 \text{ k}\Omega$ resistor to noninverting terminal of first op-amp, and $R_4 = 10 \parallel 50 = 8.33 \text{ k}\Omega$ resistor to noninverting terminal of second op-amp.

14.30

a. For a constant current through a capacitor,

$$v_O = \frac{1}{C} \int_0^t I \, dt$$

$$\text{or } v_O = \frac{0.1 \times 10^{-6}}{10^{-6}} \cdot t \Rightarrow v_O = (0.1)t$$

b. At $t = 10 \text{ s}$, $v_O = 1 \text{ V}$

c. Then

$$v_O = \frac{100 \times 10^{-12}}{10^{-6}} \cdot t \Rightarrow v_O = (10^{-4})t$$

At $t = 10 \text{ s}$, $v_O = 1 \text{ mV}$

14.31

a. Assume all bias currents are into the op-amp.

$$v_{O1} = I_{B1}(50 \text{ k}\Omega) = (10 \times 10^{-9})(50 \times 10^3)$$

or

$$v_{O1} = v_{O2} = 0.5 \text{ V}$$

$$v_{O3} = (-1)(v_{O1}) + (10 \times 10^{-9})(20 \times 10^3)$$

or

$$v_{O3} = -0.3 \text{ V}$$

b. $R_A = 10 \parallel 50 \Rightarrow R_A = 8.33 \text{ k}\Omega$

$$R_B = 20 \parallel 20 \Rightarrow R_B = 10 \text{ k}\Omega$$

- c. Assume the worst case offset current, that is, $I_{OS} = I_{B1} - I_{B2}$ or $I_{OS} = I_{B2} - I_{B1}$.
From Equation (14.83),

$$v_{O1} = R_2 I_{OS} = (50 \times 10^3)(2 \times 10^{-6})$$

or

$$\underline{v_{O1} = v_{O2} = 0.1 \text{ V}}$$

$$v_{O3} = (-1)v_{O1} - I_{OS}R_2$$

$$= (-1)(0.1) - (2 \times 10^{-6})(20 \times 10^3)$$

or

$$\underline{v_{O3} = -0.14 \text{ V}}$$

14.32

- a. Using Equation (14.79),

Circuit (a),

$$v_O = (0.8 \times 10^{-6})(50 \times 10^3) - (0.8 \times 10^{-6})(25 \times 10^3) \left(1 + \frac{50}{50}\right)$$

or

$$\underline{v_O = 0}$$

Circuit (b),

$$v_O = (0.8 \times 10^{-6})(50 \times 10^3) - (0.8 \times 10^{-6})(10^3) \left(1 + \frac{50}{50}\right)$$

$$= 4 \times 10^{-2} - 1.6$$

or

$$\underline{v_O = -1.56 \text{ V}}$$

- b. Assume $I_{B1} = 0.7 \mu\text{A}$ and $I_{B2} = 0.9 \mu\text{A}$, then using Equation (14.79):

Circuit (a),

$$v_O = (0.7 \times 10^{-6})(50 \times 10^3) - (0.9 \times 10^{-6})(25 \times 10^3) \left(1 + \frac{50}{50}\right)$$

$$= 0.035 - 0.045$$

or

$$\underline{v_O = -0.010 \text{ V}}$$

Circuit (b),

$$v_O = (0.7 \times 10^{-6})(50 \times 10^3) - (0.9 \times 10^{-6})(10^3) \left(1 + \frac{50}{50}\right)$$

$$= 0.035 - 1.8$$


or

$$\underline{v_O = -1.765 \text{ V}}$$

- a. If $R = 0$,

$$\begin{aligned} v_{O,\max} &= \left(1 + \frac{100}{10}\right) V_{OS} + I_B(100 \text{ k}\Omega) \\ &= (11)(10 \times 10^{-3}) + (2 \times 10^{-6})(100 \times 10^3) \\ v_{O,\max} &= 0.110 + 0.20 \\ &\Rightarrow \underline{v_{O,\max} = 0.310 \text{ V}} \end{aligned}$$

b.

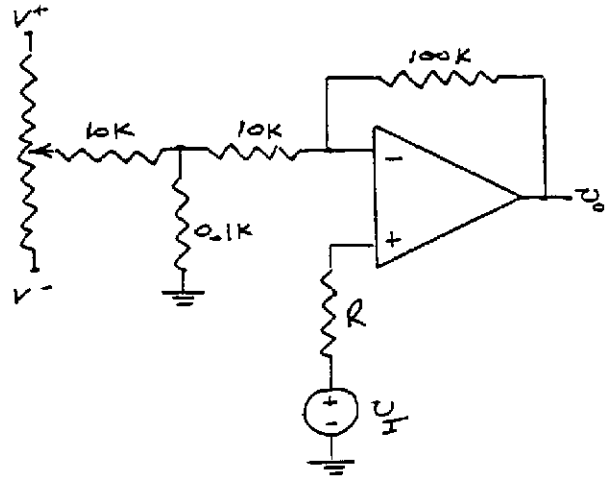

$$R = 10.1 \parallel 100 = \underline{9.17 \text{ k}\Omega = R}$$

14.34

$$a. \left(\frac{R_i}{R_i + R_2}\right)(15) = 0.010 \text{ V}$$

$$\frac{15}{15 + R_2} = 0.0006667$$

$$15(1 - 0.0006667) = 0.0006667 R_2$$

Then

$$\underline{R_2 = 22.48 \text{ M}\Omega}$$

$$b. R_1 = R_i \parallel R_F = 15 \parallel 10 \Rightarrow \underline{R_1 = 6 \text{ k}\Omega}$$

14.35

- a. Assume the offset voltage polarities are such as to produce the worst case values, but the bias currents are in the same direction.

Use superposition:
Offset voltages

$$|\nu_{01}| = \left(1 + \frac{100}{10}\right)(10) = 110 \text{ mV} = |\nu_{01}|$$

$$|\nu_{02}| = (5)(110) + \left(1 + \frac{50}{10}\right)(10) \\ \Rightarrow |\nu_{02}| = 610 \text{ mV}$$

Bias Currents:

$$\nu_{01} = I_B(100 \text{ k}\Omega) = (2 \times 10^{-6})(100 \times 10^3) = 0.2 \text{ V}$$


Then

$$\nu_{02} = (-5)(0.2) + (2 \times 10^{-6})(50 \times 10^3) = -0.9 \text{ V}$$

Worst case: ν_{01} is positive and ν_{02} is negative, then

$$\nu_{01} = 0.31 \text{ V and } \nu_{02} = -1.51 \text{ V}$$

- b. Compensation network:

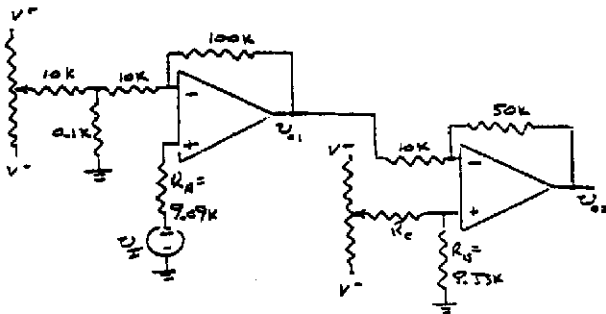

If we want

$$\left(\frac{R_B}{R_B + R_C}\right)V^+ = 20 \text{ mV and } V^+ = 10 \text{ V}$$

$$\left(\frac{8.33}{8.33 + R_C}\right)(10) = 0.020$$

or

$$R_C \approx 4.15 \text{ M}\Omega$$

14.36

Assume bias currents are in same direction, but assume polarity of offset voltages are such as to produce the worst case output.

- a. Let $I_{B1} = 5.5 \mu\text{A}$, $I_{B2} = 4.5 \mu\text{A}$

Bias Current Effects:

$$\nu_{01} = I_{B1}(50 \text{ k}\Omega) = 0.275 \text{ V} \Rightarrow \nu_{02} = 0.275 \text{ V}$$

$$\nu_{03} = I_{B1}(20 \text{ k}\Omega) - \nu_{01} \Rightarrow \nu_{03} = -0.165 \text{ V}$$

Offset Voltage Effects:

$$\nu_{01} = (5)\left(1 + \frac{50}{10}\right) = 30 \text{ mV} \Rightarrow \nu_{02} = 30 \text{ mV}$$

$$\nu_{03} = -\nu_{01} - 5\left(1 + \frac{20}{20}\right) \Rightarrow \nu_{03} = -40 \text{ mV}$$

Total Effect:

$$\nu_{01} = 0.305 \text{ V and } \nu_{02} = 0.305 \text{ V}$$

$$\nu_{03} = -0.205 \text{ V}$$

14.37

For circuit (a), effect of bias current:

$$\nu_0 = (50 \times 10^3)(100 \times 10^{-9}) \Rightarrow 5 \text{ mV}$$

Effect of offset voltage

$$\nu_0 = (2)\left(1 + \frac{50}{50}\right) = 4 \text{ mV}$$

So net output voltage is $\nu_0 = 9 \text{ mV}$

For circuit (b), effect of bias current:

Let $I_{B2} = 550 \text{ nA}$, $I_{B1} = 450 \text{ nA}$, then from Equation (14.79),

$$\nu_0 = (450 \times 10^{-9})(50 \times 10^3) \\ - (550 \times 10^{-9})(10^4)\left(1 + \frac{50}{50}\right) \\ = 2.25 \times 10^{-2} - 1.1$$

or

$$\nu_0 = -1.0775 \text{ V}$$

If the offset voltage is negative, then

$$\nu_0 = (-2)(2) = -4 \text{ mV}$$

So the net output voltage is

$$\nu_0 = -1.0815 \text{ V}$$

14.38

- a. At $T = 25^\circ\text{C}$, $V_{OS} = 2\text{ mV}$ so the output voltage for each circuit is

$$\underline{v_o = 4\text{ mV}}$$

- b. For $T = 50^\circ\text{C}$, the offset voltage for is

$$V_{OS} = 2\text{ mV} + (0.0067)(25) = 2.1675\text{ mV}$$

so the output voltage for each circuit is

$$\underline{v_o = 4.335\text{ mV}}$$

14.39

- a. At $T = 25^\circ\text{C}$, $V_{OS} = 1\text{ mV}$, then

$$v_{o1} = (1)\left(1 + \frac{50}{10}\right) \Rightarrow \underline{v_{o1} = 6\text{ mV}}$$

and

$$\begin{aligned} v_{o2} &= v_{o1}\left(1 + \frac{60}{20}\right) + (1)\left(1 + \frac{60}{20}\right) \\ &= 6(4) + (1)(4) \Rightarrow \underline{v_{o2} = 28\text{ mV}} \end{aligned}$$

- b. At $T = 50^\circ\text{C}$, $V_{OS} = 1 + (0.0033)(25) = 1.0825\text{ mV}$, then

$$v_{o1} = (1.0825)(6) \Rightarrow \underline{v_{o1} = 6.495\text{ mV}}$$

and

$$v_{o2} = (6.495)(4) + (1.0825)(4)$$

or

$$\underline{v_{o2} = 30.31\text{ mV}}$$

14.40

$$25^\circ\text{C}; I_B = 500\text{ nA}, I_{OS} = 200\text{ nA}$$

$$50^\circ\text{C}, I_B = 500\text{ nA} + (8\text{ nA}/^\circ\text{C})(25^\circ\text{C}) = 700\text{ nA}$$

$$I_{OS} = 200\text{ nA} + (2\text{ nA}/^\circ\text{C})(25^\circ\text{C}) = 250\text{ nA}$$

- a. Circuit (a): For I_B , bias current cancellation, $\underline{v_o = 0}$

Circuit (b): For I_B , Equation (14.79),

$$\begin{aligned} v_o &= (500 \times 10^{-9})(50 \times 10^3) \\ &\quad - (500 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.025 - 1.00 \Rightarrow \underline{v_o = -0.975\text{ V}} \end{aligned}$$

- b. Due to offset bias currents.

Circuit (a):

$$v_o = (200 \times 10^{-9})(50 \times 10^3) \Rightarrow \underline{v_o = 0.010\text{ V}}$$

Circuit (b):

$$\text{Let } I_{B2} = 600\text{ nA}$$

$$I_{B1} = 400\text{ nA}$$

Then

$$\begin{aligned} v_o &= (400 \times 10^{-9})(50 \times 10^3) \\ &\quad - (600 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.020 - 1.20 \Rightarrow \underline{v_o = -1.18\text{ V}} \end{aligned}$$

- c. Circuit (a): Due to I_B , $\underline{v_o = 0}$

Circuit (b): Due to I_B ,

$$\begin{aligned} v_o &= (700 \times 10^{-9})(50 \times 10^3) \\ &\quad - (700 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.035 - 1.40 \Rightarrow \underline{v_o = -1.365\text{ V}} \end{aligned}$$

Circuit (a): Due to I_{OS} ,

$$v_o = (250 \times 10^{-9})(50 \times 10^3) \Rightarrow \underline{v_o = 0.0125\text{ V}}$$

Circuit (b): Due to I_{OS} ,

$$\text{Let } I_{B2} = 825\text{ nA}$$

$$I_{B1} = 575\text{ nA}$$

Then

$$\begin{aligned} v_o &= (575 \times 10^{-9})(50 \times 10^3) \\ &\quad - (825 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.02875 - 1.65 \Rightarrow \underline{v_o = -1.62\text{ V}} \end{aligned}$$

14.41

$$25^\circ\text{C}; I_B = 2\text{ }\mu\text{A}, I_{OS} = 0.2\text{ }\mu\text{A}$$

$$50^\circ\text{C}, I_B = 2\text{ }\mu\text{A} + (0.020\text{ }\mu\text{A}/^\circ\text{C})(25^\circ\text{C}) = 2.5\text{ }\mu\text{A}$$

$$\begin{aligned} I_{OS} &= 0.2\text{ }\mu\text{A} + (0.005\text{ }\mu\text{A}/^\circ\text{C})(25^\circ\text{C}) \\ &= 0.325\text{ }\mu\text{A} \end{aligned}$$

- a. Due to I_B : (Assume bias currents into op-amp).

$$\begin{aligned} v_{o1} &= I_B(50\text{ k}\Omega) = (2 \times 10^{-6})(50 \times 10^3) \\ &\Rightarrow \underline{v_{o1} = 0.10\text{ V}} \end{aligned}$$

$$\begin{aligned} v_{o2} &= v_{o1}\left(1 + \frac{60}{20}\right) + I_B(60\text{ k}\Omega) \\ &\quad - I_B(50\text{ k}\Omega)\left(1 + \frac{60}{20}\right) \\ &= (0.1)(4) + (2 \times 10^{-6})(60 \times 10^3) \\ &\quad - (2 \times 10^{-6})(50 \times 10^3)(4) \end{aligned}$$

or

$$\underline{v_{02} = 0.12 \text{ V}}$$

b. Due to I_{OS} :1st op-amp. Let $I_{B1} = 2.1 \mu\text{A}$ 2nd op-amp. Let $I_{B1} = 2.1 \mu\text{A}$

$$I_{B2} = 1.9 \mu\text{A}$$

$$v_{01} = I_{B1}(50 \text{ k}\Omega) = (2.1 \times 10^{-6})(50 \times 10^3)$$

$$\Rightarrow \underline{v_{01} = 0.105 \text{ V}}$$

$$v_{02} = v_{01} \left(1 + \frac{60}{20} \right) + I_{B1}(60 \text{ k}\Omega)$$

$$- I_{B2}(50 \text{ k}\Omega) \left(1 + \frac{60}{20} \right)$$

$$= (0.105)(4) + (2.1 \times 10^{-6})(60 \times 10^3)$$

$$- (1.9 \times 10^{-6})(50 \times 10^3)(4)$$

or

$$\underline{v_{02} = 0.166 \text{ V}}$$

c. Due to I_B :

$$v_{01} = (2.5 \times 10^{-8})(50 \times 10^3) \Rightarrow \underline{v_{01} = 0.125 \text{ V}}$$

$$v_{02} = v_{01} \left(1 + \frac{60}{20} \right) + I_B(60 \text{ k}\Omega)$$

$$- I_B(50 \text{ k}\Omega) \left(1 + \frac{60}{20} \right)$$

$$= (0.125)(4) + (2.5 \times 10^{-8})(60 \times 10^3)$$

$$- (2.5 \times 10^{-8})(50 \times 10^3)(4)$$

or

$$\underline{v_{02} = 0.15 \text{ V}}$$

Due to I_{OS} :

$$\text{Let } I_{B1} = 2.6625 \mu\text{A}$$

$$I_{B2} = 2.3375 \mu\text{A}$$

$$v_{01} = I_{B1}(50 \text{ k}\Omega) = (2.6625 \times 10^{-6})(50 \times 10^3)$$

$$\Rightarrow \underline{v_{01} = 0.133 \text{ V}}$$

$$v_{02} = v_{01} \left(1 + \frac{60}{20} \right) + I_{B1}(60 \text{ k}\Omega)$$

$$- I_{B2}(50 \text{ k}\Omega) \left(1 + \frac{60}{20} \right)$$


$$= (0.133)(4) + (2.6625 \times 10^{-6})(60 \times 10^3)$$

$$- (2.3375 \times 10^{-6})(50 \times 10^3)(4)$$

or

$$\underline{v_{02} = 0.224 \text{ V}}$$

14.42

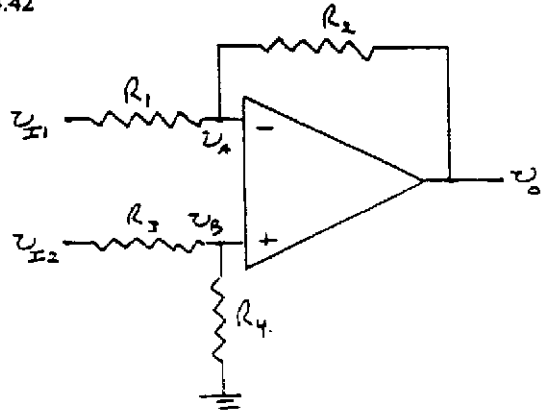

$$v_B = \left(\frac{R_4}{R_3 + R_4} \right) v_{I2} \text{ and } v_O(v_{I2}) = v_B \left(1 + \frac{R_2}{R_1} \right)$$

or

$$v_O(v_{I2}) = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) v_{I2}$$

For v_{I1} ,

$$v_O(v_{I1}) = -\frac{R_2}{R_1} \cdot v_{I1}$$

Then

$$v_O = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) v_{I2} - \frac{R_2}{R_1} \cdot v_{I1}$$

We can write $v_{I2} = V_{cm} + \frac{V_d}{2}$ and $v_{I1} = V_{cm} - \frac{V_d}{2}$. Then

$$v_O = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) \left(V_{cm} + \frac{V_d}{2} \right) - \frac{R_2}{R_1} \cdot \left(V_{cm} - \frac{V_d}{2} \right)$$

Common-mode gain

$$A_{cm} = \frac{v_O}{V_{cm}} = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1}$$

Differential mode gain

$$A_d = \frac{v_O}{V_d} = \frac{1}{2} \left[\left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_1} \right]$$

Then

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \frac{\frac{1}{2} \left[\left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_1} \right]}{\left[\left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \right]}$$

$$CMRR = \frac{\frac{1}{2} \left[\frac{R_4}{R_3} \cdot \frac{1}{\left(1 + \frac{R_4}{R_3}\right)} \cdot \left(1 + \frac{R_2}{R_1}\right) + \frac{R_2}{R_1} \right]}{\left[\frac{R_4}{R_3} \cdot \frac{1}{\left(1 + \frac{R_4}{R_3}\right)} \cdot \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1} \right]}$$

Minimum $CMRR \Rightarrow$ Maximum denominator

\Rightarrow maximum $\frac{R_4}{R_3}$ and minimum $\frac{R_2}{R_1}$. Then

$$\frac{R_4}{R_3} = \frac{(1.02)(50)}{(0.98)(10)} = 5.204$$

$$\frac{R_2}{R_1} = \frac{(0.98)(50)}{(1.02)(10)} = 4.804$$

Then

$$CMRR = \frac{\frac{1}{2} \left[\frac{5.204}{6.204} \cdot (5.804) + (4.804) \right]}{\left[\frac{5.204}{6.204} \cdot (5.804) - (4.804) \right]}$$

$$= \frac{\frac{1}{2} \cdot (9.6725)}{(0.06447)}$$

$$CMRR = 75.0 \Rightarrow CMRR_{dB} = 20 \log_{10} (75.0)$$

$$\Rightarrow \underline{CMRR_{dB} = 37.5 \text{ dB}}$$

14.43

Use the results of Problem 14.42:

$$\text{Let } \frac{R_4}{R_3} = \frac{1+x}{1-x} \cdot \left(\frac{50}{10}\right) \approx (1+2x)(5)$$

$$\text{Let } \frac{R_2}{R_1} = \frac{1-x}{1+x} \cdot \left(\frac{50}{10}\right) \approx (1-2x)(5)$$

Then

$$CMRR = \frac{\frac{1}{2} \left[\frac{(1+2x)5}{6+10x} \cdot (6-10x) + (1-2x)(5) \right]}{\left[\frac{(1+2x)5}{6+10x} \cdot (6-10x) - (1-2x)(5) \right]}$$

$$= \frac{\frac{1}{2} [30 + 10x - 100x^2 + 30 - 10x - 100x^2]}{[30 + 10x - 100x^2 - (30 - 10x - 100x^2)]}$$

$$= \frac{\frac{1}{2} \cdot [60 - 200x^2]}{20x} = \frac{30 - 100x^2}{20x}$$

a. For $CMRR_{dB} = 90 \text{ dB} \Rightarrow CMRR = 31,623$
 x will be small, neglect the x^2 term. Then

$$20x = \frac{30}{31,623} \Rightarrow x = 0.0000474 = \underline{0.00474\%}$$

b. For $CMRR_{dB} = 60 \text{ dB} \Rightarrow CMRR = 1000$. Then

$$20x = \frac{30}{1000} \Rightarrow x = 0.0015 = \underline{0.15\%}$$