

Chapter 17

Exercise Solutions

E17.1

$$a. \quad i_E = \frac{-0.7 - (-5)}{R_E} = 1 \text{ mA} \Rightarrow \underline{R_E = 4.3 \text{ k}\Omega}$$

$$i_{C1} = i_{C2} = 0.5 \text{ mA} = \frac{5 - 3.5}{R_{C1}} \\ \Rightarrow \underline{R_{C1} = R_{C2} = 3 \text{ k}\Omega}$$

$$b. \quad i. \quad v_1 = 1 \text{ V}$$

$$i_E = \frac{(1 - 0.7) - (-5)}{4.3} \Rightarrow \underline{i_E = 1.23 \text{ mA}}$$

$$i_{C1} = i_E = v_{01} = 5 - (1.23)(3) \\ \Rightarrow \underline{v_{01} = 1.31 \text{ V}}$$

$$\underline{v_{02} = 5 \text{ V}}$$

$$ii. \quad v_f = -1 \text{ V}$$

$$i_E = 1 \text{ mA} \Rightarrow v_{02} = 5 - (1)(3)$$

$$\Rightarrow \underline{v_{02} = 2 \text{ V}}$$

$$\underline{v_{01} = 5 \text{ V}}$$

E17.2

a. Q_R on

$$i_E = \frac{1.5 - 0.7 - (-3.5)}{R_E} = 2 \text{ mA}$$

$$\Rightarrow \underline{R_E = 2.15 \text{ k}\Omega}$$

$$i_{CR} \approx i_E = 2 \text{ mA} = \frac{3.5 - 2}{R_{C2}}$$

$$\Rightarrow \underline{R_{C2} = 0.75 \text{ k}\Omega}$$

b. $v_X = v_Y = 2 \text{ V} \Rightarrow Q_1$ and Q_2 on

$$i_E = \frac{2 - 0.7 - (-3.5)}{R_E} = \frac{4.8}{2.15} \Rightarrow \underline{i_E = 2.23 \text{ mA}}$$

$$R_{C1} = \frac{3.5 - 2}{i_{CXY}} = \frac{1.5}{2.23} \Rightarrow \underline{R_{C1} = 0.673 \text{ k}\Omega}$$

E17.3

$$\text{logic 1} = -0.7 \text{ V}$$

$$Q_1 \text{ and } Q_2 \text{ on when } v_X = v_Y = -0.7 \text{ V}$$

$$i_E = \frac{-0.7 - 0.7 - (-5.2)}{R_E} = 2.5$$

$$\Rightarrow \underline{R_E = 1.52 \text{ k}\Omega}$$

$$v_{NOR} = -1.5 \Rightarrow R_{C1} = \frac{0 - (-1.5 + 0.7)}{2.5}$$

$$\Rightarrow \underline{R_{C1} = 320 \Omega}$$

$$V_R = \frac{-1.5 - 0.7}{2} \Rightarrow \underline{V_R = -1.1 \text{ V}}$$

$$Q_R \text{ on} \Rightarrow i_E = \frac{-1.1 - 0.7 - (-5.2)}{1.52} = 2.24 \text{ mA}$$

$$R_{C2} = \frac{0 - (-1.5 + 0.7)}{2.24} \Rightarrow \underline{R_{C2} = 357 \Omega}$$

$$R_3 = R_4 = \frac{-0.7 - (-5.2)}{2.5} \Rightarrow \underline{R_3 = R_4 = 1.8 \text{ k}\Omega}$$

E17.4

$$P(i_{CXY} + i_{CR} + i_3 + i_4)(5.2)$$

a. $v_X = v_Y = \text{logic 1}$

$$\Rightarrow i_{CXY} = 3.22 \text{ mA}$$

$$i_{CR} = 0$$

$$i_3 = \frac{-0.7 + 5.2}{1.5} = 3 \text{ mA}$$

$$i_4 = \frac{-1.4 + 5.2}{1.5} = 2.53 \text{ mA}$$

$$P = (3.22 + 0 + 3 + 2.53)(5.2)$$

$$\Rightarrow \underline{P = 45.5 \text{ mW}}$$

b. $v_X = v_Y = \text{logic 0}$

$$\Rightarrow i_{CXY} = 0$$

$$i_{CR} = 2.92 \text{ mA}$$


$$i_3 = 2.53 \text{ mA}$$

$$i_4 = 3 \text{ mA}$$

$$P = (0 + 2.92 + 2.53 + 3)(5.2)$$

$$\Rightarrow \underline{P = 43.9 \text{ mW}}$$

E17.5

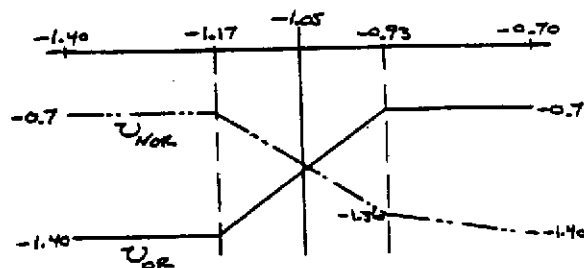

$$NM_H = -0.70 - (-0.93) \Rightarrow \underline{NM_H = 0.23 \text{ V}}$$

$$NM_L = -1.17 - (-1.40) \Rightarrow \underline{NM_L = 0.23 \text{ V}}$$

E17.6

$$P = I_Q \cdot V_{CC} \Rightarrow 0.2 = I_Q(1.7)$$

$$\Rightarrow I_Q = 118 \mu\text{A}$$

$$Q_R \text{ on} \Rightarrow v_o = 1.7 - I_Q R_C = 1.7 - 0.4$$

$$\Rightarrow R_C = \frac{0.4}{0.118} \Rightarrow R_C = 3.39 \text{ k}\Omega$$

$$V_R = \frac{1.7 + 1.3}{2} \Rightarrow V_R = 1.5 \text{ V}$$

E17.7

State	A	B	C	Q ₀₁	Q ₀₂	Q ₀₃	Q ₁	Q ₂	Q _R	v _o
1	0	0	0	off	off	off	off	on	on	0
2	1	0	0	"on"	off	off	off	on	on	0
3	0	1	0	off	on	off	off	on	"off"	1
4	0	0	1	off	off	on	on	off	on	0
5	1	1	0	on	on	off	off	on	off	1
6	1	0	1	on	off	on	on	off	"off"	1
7	0	1	1	off	on	on	on	off	on	0
8	1	1	1	on	on	on	on	off	off	1

$(A \text{ AND } C)$ OR $(B \text{ AND } \overline{C})$
 true for true for
 states 6 and 8 states 3 and 5
 Output goes high for these 4 states

E17.8

A	B	C	v _o
0	0	0	0
1	0	0	1
0	1	0	1
0	0	1	1
1	1	0	0
1	0	1	0
0	1	1	0
1	1	1	1

$$\Rightarrow (A \oplus B) \oplus C$$

E17.9

$$i_C = \frac{5 - 0.1}{1} = 4.9 \text{ mA}$$

$$i_B = \frac{4.9}{30} = 0.163 \text{ mA} = \frac{v_T - 0.7}{R_B} = \frac{4.3}{R_B}$$

$$\Rightarrow R_B = 26.4 \text{ k}\Omega$$

E17.10

$$(a) v_X = v_T = 5 \text{ V}$$

$$v_i = V_{BE}(\text{sat}) + 2V_T = 0.8 + 2(0.7) = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{4} = 0.70 \text{ mA}$$

$$i_{RC} = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C} = \frac{5 - 0.1}{4} = 1.23 \text{ mA}$$

$$P = (i_1 + i_{RC})V_{CC} = (0.70 + 1.23)(5)$$

$$\text{or } P = 9.65 \text{ mW}$$

$$(b) v_X = v_T = 0 \Rightarrow v_i = 0.70 \text{ V}$$

$$i_1 = \frac{V_{CC} - v_i}{R_1} = \frac{5 - 0.70}{4} = 1.08 \text{ mA}$$

$$P = i_1 V_{CC} = (1.08)(5) \Rightarrow P = 5.4 \text{ mW}$$

E17.11

$$a. \text{ Inputs high } v_i = 0.8 + 0.7 + 0.8 = 2.3 \text{ V}$$

$$i_1 = i_{B1} = \frac{5 - 2.3}{4} = 0.675 \text{ mA}$$

$$v_{C1} = 0.8 + 0.7 + 0.7 = 1.6 \text{ V}$$

$$i_2 = \frac{5 - 1.6}{2} = 1.7 \text{ mA}$$

$$i_3 = 1.7 + 0.675 = 2.38 \text{ mA}$$

$$i_4 = \frac{0.8}{10} = 0.08 \text{ mA}$$

$$i_{B0} = 2.38 - 0.08 = 2.3 \text{ mA}$$

$$i_{RC} = \frac{5 - 0.1}{4} = 1.23 \text{ mA}$$

$$i'_L = \frac{5 - 0.8}{4} = 1.05 \text{ mA}$$

$$\beta i_{B0} = N i'_L + i_{RC}$$

$$(30)(2.3) = N(1.05) + 1.23 \Rightarrow N = 64$$

$$b. I_{C, \text{rated}} = 20 \text{ mA}$$

$$20 = N i'_L + i_{RC} = N(1.05) + 1.23$$

$$\Rightarrow N = 17$$

E17.12

a. $v_X = v_Y = 0.1 \Rightarrow v_1 = 0.8$

$$i_1 = \frac{5 - 0.8}{6} \Rightarrow i_1 = 0.7 \text{ mA}$$

$$i_2 = i_R = i_B = i_{RC} = 0$$

$$v_O = 5 \text{ V}$$

b. Same as part (a).

c. $v_X = v_Y = 5 \text{ V} \Rightarrow v_1 = 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$

$$i_1 = i_2 = \frac{5 - 2.2}{6} \Rightarrow i_1 = i_2 = 0.467 \text{ mA}$$

$$i_R = \frac{0.8}{15} \Rightarrow i_R = 0.053 \text{ mA}$$

$$i_B = i_2 - i_R \Rightarrow i_B = 0.414 \text{ mA}$$

$$i_{RC} = \frac{5 - 0.1}{5} \Rightarrow i_{RC} = 0.98 \text{ mA}$$

$$v_O = 0.1 \text{ V}$$

$$i_{BX} = i_{BY} = i_1 \cdot \beta_R = (0.45)(0.1) = 0.045 \text{ mA}$$

$$i_{B2} = |i_{C1}| = i_1 + i_{BX} + i_{BY} = 0.45 + 2(0.045)$$

$$i_{B2} = |i_{C1}| = 0.54 \text{ mA}$$

$$v_{C2} = 0.8 + 0.1 = 0.9$$

$$i_2 = i_{C2} = \frac{5 - 0.9}{1.5} \Rightarrow i_2 = i_{C2} = 2.73 \text{ mA}$$

$$i_{B2} = 2.73 + 0.54 = 3.27 \text{ mA}$$

$$i_4 = \frac{0.8}{1.5} = 0.533 \text{ mA}$$

$$i_{B0} = 3.27 - 0.533 \Rightarrow i_{B0} = 2.74 \text{ mA}$$

$$i_3 = i_{C0} = \frac{5 - 0.1}{2.2} \Rightarrow i_3 = i_{C0} = 2.23 \text{ mA}$$

For Q_2 :

$$\frac{i_{C2}}{i_{B2}} = \frac{2.73}{3.27} = 0.83 < \beta_F \Rightarrow Q_2 \text{ in saturation}$$

For Q_0 :

$$\frac{i_{C0}}{i_{B0}} = \frac{2.23}{2.74} = 0.81 < \beta_F \Rightarrow Q_0 \text{ in saturation}$$

E17.13

a. $v_X = v_Y = 0.1 \text{ V}$

$$i_1 = \frac{5 - 0.8}{8} = 0.525 \text{ mA}$$

$$P = i_1(5 - 0.1) = (0.525)(4.9) \\ \Rightarrow P = 2.57 \text{ mW}$$

b. $v_X = v_Y = 5 \text{ V}, v_1 = 2.3 \text{ V}$

$$i_1 = \frac{5 - 2.3}{8} = 0.338 \text{ mA}$$

$$v_{C1} = 1.6 \text{ V} \Rightarrow i_2 = \frac{5 - 1.6}{3.6} = 0.944 \text{ mA}$$

$$i_{RC} = \frac{5 - 0.1}{6} = 0.817 \text{ mA}$$

$$P = (i_1 + i_2 + i_{RC})(V_{CC}) \\ = (0.338 + 0.944 + 0.817)(5)$$

$$P = 10.3 \text{ mW}$$

E17.14

a. $v_X = v_Y = 0.1 \text{ V}$

$$v_{B1} = 0.1 + 0.8 = 0.9 \text{ V}$$

$$i_{B1} = i_1 = \frac{5 - 0.9}{6} \Rightarrow i_1 = i_{B1} = 0.683 \text{ mA}$$

$$i_{C1} \approx 0$$

$$i_{B2} = i_{C2} = 0$$

$$i_{B0} = i_{C0} = 0$$

b. $v_X = v_Y = 3.6 \text{ V}$

$$v_{B1} = 0.8 + 0.8 + 0.7 = 2.3 \text{ V}$$

$$i_1 = i_{B1} = \frac{5 - 2.3}{6} \Rightarrow i_1 = i_{B1} = 0.45 \text{ mA}$$

E17.15

a. Output low:

$$i'_L = \frac{5 - (0.1 + 0.8)}{6} = 0.683$$

$$i_{C0}(\text{max}) = \beta_F \cdot i_{B0} = N i'_L + i_3$$

$$(20)(2.74) = N(0.683) + 2.23$$

$$\Rightarrow N = 76$$

b. Output high:

Q'_1 inverse active

$$i'_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i'_L = \beta_R \cdot i'_1 = (0.1)(0.45) = 0.045 \text{ mA}$$

$$v_O(\text{min}) = 2.4 \text{ V} \Rightarrow i_L(\text{max}) = \frac{5 - 2.4}{2.2} - N \cdot i'_L$$

$$1.18 = N(0.045)$$

$$\Rightarrow N = 26$$

E17.16

a. $v_X = v_Y = 0.1 \text{ V} \Rightarrow v_O(\text{max}) = 3.6 \text{ V}$

Q'_1 inverse active

$$i'_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i'_L = \beta_R \cdot i'_1 = (0.1)(0.45) = 0.045$$

$$i_{B3} = \frac{0.1}{2} = 0.05 \text{ mA}$$

$$i_L = (1 + \beta_F) i_{B3} = (21)(0.05) = 1.05 \text{ mA}$$

$$i_L = N i'_L \Rightarrow 1.05 = N(0.045) \Rightarrow N = 23$$

b. $v_X = v_Y = 3.6 \text{ V}$, Output low:

$$i_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i_{B1} = (1 + 2\beta_R)i_1$$

$$i_{B1} = 0.54 \text{ mA}$$

$$v_{B3} = 0.8 + 0.1 = 0.9$$

$$i_2 = \frac{5 - 0.9}{2} = 2.05 \text{ mA}$$

$$i_{B0} = 2.05 + 0.54 - \frac{0.8}{1.5} \Rightarrow i_{B0} = 2.06 \text{ mA}$$

$$i'_L = \frac{5 - 0.9}{6} = 0.683 \text{ mA}$$

$$\beta_F \cdot i_{B0} = N \cdot i'_L \Rightarrow (20)(2.06) = N(0.683)$$

$$\Rightarrow N = 60$$

E17.17

a. $v_X = v_Y = 3.6 \text{ V}$

$$i_{B1} = \frac{5 - 2.3}{4} = 0.675 \text{ mA} = i_{B1} = |i_{C1}| = i_{B2}$$

$$v_{B4} = 0.8 + 0.1 = 0.9 \text{ V}$$

$$i_2 = \frac{5 - 0.9}{1.6} = 2.56 \text{ mA}$$

$$i_{B4} = \frac{0.2}{(1 + \beta_F)(4)} = \frac{0.2}{(31)(4)} \Rightarrow i_{B4} = 1.61 \mu\text{A}$$

$$i_{C4} = 48.3 \mu\text{A}$$

$$i_{B3} = i_{C3} = 0$$

$$\Rightarrow i_{C2} \approx i_2 = 2.56 \text{ mA}$$

$$i_{B0} = 2.45 + 0.675 - \frac{0.8}{1} \Rightarrow i_{B0} = 2.44 \text{ mA}$$

One load:

$$i'_L = i_{C0} = \frac{5 - 0.9}{4} \Rightarrow i_{C0}(\text{max}) = 1.03 \text{ mA}$$

b. $v_X = v_Y = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - 0.9}{4} \Rightarrow i_{B1} = 1.03 \text{ mA}$$

$$|i_{C1}| = i_{B2} = i_{C2} = 0$$

$$i_{B0} = i_{C0} = 0$$

Output high, $\beta_R = 0 \Rightarrow i_{B3} = i_{C3} = 0$

$$5 = i_{B4}(1.6) + 0.7 + (31)i_{B4}(4)$$

$$\Rightarrow i_{B4} = 0.0342 \text{ mA}$$

$$i_{C4} = 1.03 \text{ mA}$$

E17.18

Q_1 in saturation

$$i_{B1} = \frac{5 - 0.9}{6} \Rightarrow i_{B1} = 0.683 \text{ mA}$$

$$|i_{C1}| = i_{B2} = i_{C2} = 0$$

$$i_{B0} = i_{C0} = 0$$

$$v_{B4} = 0.1 + 0.7 = 0.8 \text{ V}$$

$$i_{B4} = \frac{0.1}{(21)(4)} \Rightarrow i_{B4} = 1.19 \mu\text{A}$$

$$i_{C4} = 23.8 \mu\text{A}$$

$$i_{B3} = i_{C3} = 0$$

E17.19

$$a. \quad i_{RC} = \frac{5 - 0.4}{2.25} = 2.04 \text{ mA}$$

$$i'_C = \frac{2 + 2.04}{1 + \frac{1}{10}} \Rightarrow i'_C = 3.67 \text{ mA}$$

$$i'_B = \frac{3.67}{10} = 0.367 \text{ mA}$$

$$i_D = 2 - 0.367 \Rightarrow i_D = 1.63 \text{ mA}$$

$$b. \quad i_D = 0 \Rightarrow i'_B = i_B = 2 \text{ mA}$$

$$i'_C = \beta i'_B = (10)(2) = 20 \text{ mA} = i_{RC} + i_L$$

$$i_L = 20 - 2.04 \Rightarrow i_L(\text{max}) \approx 18 \text{ mA}$$

Chapter 17

Problem Solutions

17.1

a. $v_I = -1.5 \text{ V}$; Q_1 off, Q_2 on

$$i_E = \frac{-0.7 - (-3.5)}{5} \Rightarrow i_E = 0.56 \text{ mA}$$

$$i_{C1} = 0 \Rightarrow v_{O1} = 3.5 \text{ V}$$

$$i_{C2} = i_E \Rightarrow v_{O2} = 3.5 - i_E R_{C2} = 3.5 - (0.56)(2)$$

or

$$v_{O2} = 2.38 \text{ V}$$

b. $v_I = 1.0 \text{ V}$; Q_1 on, Q_2 off

$$i_E = \frac{(1 - 0.7) - (-3.5)}{5} \Rightarrow i_E = 0.76 \text{ mA}$$

$$i_{C2} = 0 \Rightarrow v_{O2} = 3.5 \text{ V}$$

c. logic 0 at v_{O2} (low level) = 2.38 V

Then

$$v_{O1} = 2.38 = 3.5 - (0.76)R_{C1}$$

or

$$R_{C1} = 1.47 \text{ k}\Omega$$

17.2

(a) Q_1 on, $v_E = -1.2 - 0.7 = -1.9 \text{ V}$

$$i_E = i_{C2} = \frac{-1.9 - (-5.2)}{2.5} = 1.32 \text{ mA}$$

$$v_2 = -1 \text{ V} = -i_{C2} R_{C2} = -(1.32)(R_{C2})$$

$$R_{C2} = 0.758 \text{ k}\Omega$$

(b) Q_1 on, $v_E = -0.7 - 0.7 = -1.40 \text{ V}$

$$i_E = i_{C1} = \frac{-1.4 - (-5.2)}{2.5} = 1.52 \text{ mA}$$

$$v_1 = -1 \text{ V} = -i_{C1} R_{C1} = -(1.52)(R_{C1})$$

$$R_{C1} = 0.658 \text{ k}\Omega$$

(c) For $v_{in} = -0.7 \text{ V}$, Q_1 on, Q_2 off

$$\Rightarrow v_{O1} = -0.70 \text{ V}$$

$$v_{O2} = -1 - 0.7 \Rightarrow v_{O2} = -1.7 \text{ V}$$

For $v_{in} = -1.7 \text{ V}$, Q_1 off, Q_2 on

$$\Rightarrow v_{O2} = -0.7 \text{ V}$$

$$v_{O1} = -1 - 0.7 \Rightarrow v_{O1} = -1.7 \text{ V}$$

(d) (i) For $v_{in} = -0.7 \text{ V}$, $i_E = 1.52 \text{ mA}$

$$i_{C4} = \frac{-1.7 - (-5.2)}{3} = 1.17 \text{ mA}$$

$$i_{C3} = \frac{-0.7 - (-5.2)}{3} = 1.5 \text{ mA}$$

$$P = (i_E + i_{C4} + i_{C3})(5.2) = (1.52 + 1.17 + 1.5)(5.2)$$

$$\text{or } P = 218 \text{ mW}$$

(ii) For $v_{in} = -1.7 \text{ V}$, $i_E = 1.32 \text{ mA}$

$$i_{C4} = \frac{-0.7 - (-5.2)}{3} = 1.5 \text{ mA}$$

$$i_{C3} = \frac{-1.7 - (-5.2)}{3} = 1.17 \text{ mA}$$

$$P = (1.32 + 1.5 + 1.17)(5.2)$$

$$\text{or } P = 20.7 \text{ mW}$$

17.3

$$a. \quad I_3 = \frac{3.7 - 0.7}{0.67 + 1.33} = 1.5 \text{ mA}$$

$$V_R = I_3 R_4 + V_T = (1.5)(1.33) + 0.7$$

or

$$V_R = 2.70 \text{ V}$$

b. logic 1 level = $3.7 - 0.7 \Rightarrow 3.0 \text{ V}$ For $v_X = v_Y = \text{logic 1}$,

$$i_E = \frac{3 - 0.7}{0.8} = 2.875 \text{ mA} = i_{RC1}$$

$$v_{B3} = 3.7 - (2.875)(0.21) = 3.10 \text{ V}$$

$$\Rightarrow v_{O1}(\text{logic 0}) = 2.4 \text{ V}$$

For $v_X = v_Y = \text{logic 0}$, Q_R on

$$i_E = \frac{2.7 - 0.7}{0.8} = 2.5 \text{ mA} = i_{RC2}$$

$$v_{B4} = 3.7 - (2.5)(0.24) = 3.1 \text{ V}$$

$$\Rightarrow v_{O2}(\text{logic 0}) = 2.4 \text{ V}$$

17.4

$$V_R = \frac{\text{logic 1} + \text{logic 0}}{2} = \frac{1 + 0}{2} = 0.5 \text{ V}$$

For $i_2 = 1 \text{ mA}$

$$R_4 = \frac{0.5 - (-2.3)}{1} \Rightarrow R_4 = 2.8 \text{ k}\Omega$$

For Q_R on,

$$i_E = \frac{V_R - V_{BE} - (-2.3)}{R_E}$$

or

$$R_E = \frac{0.5 - 0.7 + 2.3}{1} \Rightarrow R_E = 2.1 \text{ k}\Omega$$

$$V_{B2} = V_R + V_{BE} = 0.5 + 0.7 = 1.2 \text{ V}$$

$$i_1 = \frac{1.2 - 1.4 - (-2.3)}{R_2}$$

or

$$R_2 = \frac{1.2 - 1.4 + 2.3}{1} \Rightarrow \underline{R_2 = 2.1 \text{ k}\Omega}$$

$$R_1 = \frac{1.7 - 1.2}{1} \Rightarrow \underline{R_1 = 0.5 \text{ k}\Omega}$$

$$i_3 = \frac{1 - (-2.3)}{R_3} = 3 \Rightarrow \underline{R_3 = 1.1 \text{ k}\Omega}$$

$$i_4 = \frac{0 - (-2.3)}{R_4} = 3 \Rightarrow \underline{R_4 = 0.767 \text{ k}\Omega}$$

For Q_R on,

$$v_{OR} = \text{logic } 0 = 0 \text{ V} \Rightarrow v_{B3} = 0.7 \text{ V}$$

$$i_E = i_{CR} = 1 \text{ mA}$$

So

$$R_{C2} = \frac{1.7 - 0.7}{1} \Rightarrow \underline{R_{C2} = 1 \text{ k}\Omega}$$

For $v_I = \text{logic } 1 = 1 \text{ V}$,

$$i_E = \frac{1 - 0.7 - (-2.3)}{2.1} = 1.238 \text{ mA}$$

For $v_{NOR} = \text{logic } 0 = 0 \text{ V}$,

$$v_{B4} = 0.7 \text{ V}$$

Then

$$R_{C1} = \frac{1.7 - 0.7}{1.238} \Rightarrow \underline{R_{C1} = 0.808 \text{ k}\Omega}$$

17.5

Maximum i_E for $v_I = \text{logic } 1 = 3.3 \text{ V}$

$$\text{Then } i_E = 5 \text{ mA} = \frac{3.3 - 0.7}{R_E} \Rightarrow \underline{R_E = 0.52 \text{ k}\Omega}$$

For $v_{O2} = \text{logic } 1 = 3.3 \text{ V}$

$$i_{E3} = \frac{3.3 - 0}{R_3} = 5 \text{ mA}$$

or

$$\underline{R_3 = 0.66 \text{ k}\Omega}$$

By symmetry,

$$\underline{R_2 = 0.66 \text{ k}\Omega}$$

For Q_1 on,

$$i_E = i_{RC1} = 5 \text{ mA} = \frac{4 - (2.7 + 0.7)}{R_{C1}}$$

So

$$\underline{R_{C1} = 0.12 \text{ k}\Omega}$$

For Q_R on,

$$i_E = \frac{3 - 0.7}{0.52} = 4.423 \text{ mA} = i_{RC2}$$

$$\text{and } i_{RC2} = 4.423 = \frac{4 - (2.7 + 0.7)}{R_{C2}}$$

$$\Rightarrow \underline{R_{C2} = 0.136 \text{ k}\Omega}$$

17.6

Neglecting base currents:

$$(a) \underline{I_{E1} = 0, I_{E3} = 0}$$

$$I_{E5} = \frac{5 - 0.7}{2.5} \Rightarrow \underline{I_{E5} = 1.72 \text{ mA}}$$

$$Y = 0.7 \text{ V}$$

$$(b) \underline{I_{E1} = \frac{5 - 0.7}{18} \Rightarrow I_{E1} = 0.239 \text{ mA}}$$

$$\underline{I_{E3} = 0}$$

$$I_{E5} = \frac{5 - 0.7}{2.5} \Rightarrow \underline{I_{E5} = 1.72 \text{ mA}}$$

$$Y = 0.7 \text{ V}$$

$$(c) \underline{I_{E1} = I_{E3} = \frac{5 - 0.7}{18} \Rightarrow I_{E1} = I_{E3} = 0.239 \text{ mA}}$$

$$\underline{I_{E5} = 0, Y = 5 \text{ V}}$$

$$(d) \text{ Same as (c).}$$

17.7

$$(a) \underline{V_R = -(1)(1) - 0.7 \Rightarrow V_R = -1.7 \text{ V}}$$

$$(b) \underline{Q_R \text{ off, then } v_{O1} = \text{Logic } 1 = -0.7 \text{ V}}$$

$$\underline{Q_R \text{ on, then } v_{O1} = -(1)(2) - 0.7 \Rightarrow}$$

$$\underline{v_{O1} = \text{Logic } 0 = -2.7 \text{ V}}$$

$$\underline{Q_A / Q_B \text{ off, then } v_{O2} = \text{Logic } 1 = -0.7 \text{ V}}$$

$$\underline{Q_A / Q_B \text{ on, then } v_{O2} = -(1)(2) - 0.7 \Rightarrow}$$

$$\underline{v_{O2} = \text{Logic } 0 = -2.7 \text{ V}}$$

$$(c) \underline{A = B = \text{Logic } 0 = -2.7 \text{ V}, Q_R \text{ on,}}$$

$$\underline{V_E = -1.7 - 0.7 \Rightarrow V_E = -2.4 \text{ V}}$$

$$\underline{A = B = \text{Logic } 1 = -0.7 \text{ V}, Q_A / Q_B \text{ on,}}$$

$$\underline{V_E = -0.7 - 0.7 \Rightarrow V_E = -1.4 \text{ V}}$$

$$(d) \underline{A = B = \text{Logic } 1 = -0.7 \text{ V}, Q_A / Q_B \text{ on,}}$$

$$\underline{i_{C3} = \frac{-2.7 - (-5.2)}{15} = 1.67 \text{ mA}}$$

$$\underline{i_{C2} = \frac{-0.7 - (-5.2)}{15} = 3 \text{ mA}}$$

$$\underline{P = (1.67 + 1 + 1 + 1 + 3)(5.2) \Rightarrow P = 39.9 \text{ mW}}$$

$$\underline{A = B = \text{Logic } 0 = -2.7 \text{ V}}$$

$$\underline{i_{C3} = 3 \text{ mA}, i_{C2} = 1.67 \text{ mA}}$$

$$\underline{P = 39.9 \text{ mW}}$$

17.8

a. AND logic function

b. logic 0 = 0 V

$$\underline{Q_A \text{ on, } i = \frac{5 - (1.6 + 0.7)}{1.2} = 2.25 \text{ mA}}$$

$$\underline{V_2 = (2.25)(0.8) \Rightarrow \text{logic } 1 = 1.8 \text{ V}}$$

$$c. \quad i_{E1} = \frac{5 - 0.7}{2.6} \Rightarrow i_{E1} = 1.65 \text{ mA}$$

$$i_{E2} = \frac{5 - (0.7 + 0.7)}{1.2} \Rightarrow i_{E2} = 3 \text{ mA}$$

$$i_{C1} = 0, \quad i_{C2} = i_{E2} = 3 \text{ mA}$$

$$V_2 = 0$$

$$d. \quad i_{E1} = \frac{5 - (1.8 + 0.7)}{2.6} \Rightarrow i_{E1} = 0.962 \text{ mA}$$

$$i_{E2} = \frac{5 - (1.6 + 0.7)}{1.2} \Rightarrow i_{E2} = 2.25 \text{ mA}$$

$$i_{C2} = 0, \quad i_{C3} = i_{E2} = 2.25 \text{ mA}$$

$$V_2 = 1.8 \text{ V}$$

17.9

$$a. \quad V_R = \frac{3.5 + 3.1}{2} - 0.7 \Rightarrow V_R = 2.6 \text{ V}$$

$$b. \quad \text{For } Q_1 \text{ on, } v_X = v_Y = \text{logic } 1 = 3.5 \text{ V}$$

$$i_E = \frac{3.5 - (0.7 + 0.7)}{12} = 0.175 \text{ mA}$$

$$\text{Want } i_{RC1} = \frac{0.175}{2} = \frac{0.4}{R_{C1}} \Rightarrow R_{C1} = 4.57 \text{ k}\Omega$$

$$c. \quad \text{For } Q_2 \text{ on, } i_E = \frac{2.6 - 0.7}{12} = 0.158 \text{ mA}$$

$$\text{Want } i_{RC2} = \frac{0.158}{2} = \frac{0.4}{R_{C2}} \Rightarrow R_{C2} = 5.06 \text{ k}\Omega$$

$$d. \quad \text{For } v_Y = \text{logic } 1 = 3.5 \text{ V}$$

$$i_{R1} = \frac{3.5 - 0.7}{8} = 0.35 \text{ mA}, \quad i_E = 0.175 \text{ mA}$$

$$P = (i_{R1} + i_E)(V_{CC}) = (0.35 + 0.175)(3.5) \\ \Rightarrow P = 1.84 \text{ mW}$$

17.10

$$a. \quad \text{logic } 1 = 0.2 \text{ V}$$

$$\text{logic } 0 = -0.2 \text{ V}$$

$$b. \quad i_E = \frac{(0 - 0.7) - (-3.1)}{R_E} = 0.8$$

So

$$R_E = 3 \text{ k}\Omega$$

$$c. \quad \text{Want } i_{R1} = \frac{0.8}{2} = \frac{0.4}{R_1} \Rightarrow R_1 = 1 \text{ k}\Omega$$

$$d. \quad \text{For } v_X = v_Y = \text{logic } 1 = 0.2 \text{ V}$$

$$i_E = \frac{(0.2 - 0.7) - (-3.1)}{3} = 0.867 \text{ mA}$$

$$i_{R2} = \frac{0.4}{1} \Rightarrow i_{R2} = 0.4 \text{ mA}$$

$$i_{D2} = 0.467 \text{ mA}$$

$$e. \quad i_E = 0.867 \text{ mA}$$

$$i_3 = \frac{0.2 - (-3.1)}{3.3} = 1 \text{ mA}$$

$$i_4 = \frac{-0.2 - (-3.1)}{3.3} = 0.879 \text{ mA}$$

$$P = (0.867 + 1 + 0.879)(0.9 - (-3.1))$$

or

$$P = 11.0 \text{ mW}$$

17.11

$$a. \quad i_1 = \frac{(-0.9 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.4 \text{ mA}$$

$$i_3 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.14 \text{ mA}$$

$$i_4 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_4 = 0.14 \text{ mA}$$

$$i_2 + i_D = i_1 + i_3 = 1.4 + 0.14 = 1.54 \text{ mA}$$

$$i_2 = \frac{0.4}{0.5} \Rightarrow i_2 = 0.8 \text{ mA}$$

$$i_D = 0.74 \text{ mA}$$

$$v_0 = -0.4 \text{ V}$$

$$b. \quad i_1 = 1.4 \text{ mA}$$

$$i_3 = \frac{(0 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.153 \text{ mA}$$

$$i_4 = i_3 \Rightarrow i_4 = 0.153 \text{ mA}$$

$$i_2 + i_D = i_4 \Rightarrow i_2 = 0.153 \text{ mA}$$

$$i_D = 0$$

$$v_0 = -(0.153)(0.5) \Rightarrow v_0 = -0.0765 \text{ V}$$

$$c. \quad i_1 = \frac{(0 - 0.7 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.6 \text{ mA}$$

$$i_3 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.14 \text{ mA}$$

$$i_4 = i_3 \Rightarrow i_4 = 0.14 \text{ mA}$$

$$i_2 + i_D = i_3 \Rightarrow i_2 = 0.14 \text{ mA}$$

$$i_D = 0.0$$

$$v_0 = -(0.14)(0.5) \Rightarrow v_0 = -0.07 \text{ V}$$

$$d. \quad i_1 = \frac{(0 - 0.7 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.6 \text{ mA}$$

$$i_3 = \frac{(0 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.153 \text{ mA}$$

$$i_4 = i_3 \Rightarrow i_4 = 0.153 \text{ mA}$$

$$i_2 + i_D = i_1 + i_4 = 1.6 + 0.153 = 1.753 \text{ mA}$$

$$i_2 = \frac{0.4}{0.5} \Rightarrow i_2 = 0.8 \text{ mA}$$

$$i_D = 0.953 \text{ mA}$$

$$v_0 = -0.40 \text{ V}$$

17.12

- a. i. $A = B = C = D = 0 \Rightarrow Q_1 - Q_1$ cutoff

So

$$V_{DD} = 2I_E R_1 + V_{EB} + I_E R_2$$

and

$$I_B = \frac{I_E}{1 + \beta_F} = \frac{I_E}{51}$$

Then

$$2.5 = 2I_E(2) + 0.7 + \frac{I_E}{51} \cdot (15)$$

$$2.5 - 0.7 = I_E \cdot \left(4 + \frac{15}{51}\right)$$

So

$$I_E = 0.419 \text{ mA}$$

and

$$Y = 2.5 - 2(0.419)(2) \Rightarrow Y = 0.824 \text{ V}$$

- ii. $A = C = 0, B = D = 2.5 \text{ V}$

Now

$$V_{B5} = V_{B6} = 2.5 - 0.7 = 1.8 \text{ V}$$

and

$$Y = V_{B5} + 0.7 \Rightarrow Y = 2.5 \text{ V}$$

- b. $Y = (A \text{ OR } B) \text{ AND } (C \text{ OR } D)$

17.13

- a. logic 1 = 0 V

$$\text{logic 0} = -0.4 \text{ V}$$

- b. $v_{01} = \overline{A \text{ OR } B}$

$$v_{02} = \overline{C \text{ OR } D}$$

$$v_{03} = \overline{v_{01} \text{ OR } v_{02}}$$

or

$$v_{03} = (A \text{ OR } B) \text{ AND } (C \text{ OR } D)$$

17.14

- a. For CLOCK = high, I_{DC} flows through the left side of the circuit. If D is high, I_{DC} flows through the left R resistor pulling \overline{Q} low. If D is low, I_{DC} flows through the right R resistor pulling Q low.

For CLOCK = low, I_{DC} flows through the right side of the circuit maintaining Q and \overline{Q} in their previous state.

- b. $P = (I_{DC} + 0.5I_{DC} + 0.1I_{DC} + 0.1I_{DC})(3)$

$$P = 1.7I_{DC}(3) = (1.7)(50)(3) \Rightarrow P = 255 \mu\text{W}$$

17.15

- i. For $v_X = v_Y = 0.1 \text{ V} \Rightarrow v' = 0.8 \text{ V}$

$$i_1 = \frac{5 - 2.2}{8} \Rightarrow i_1 = 0.525 \text{ mA}$$

$$i_2 = i_4 = 0$$

- ii. For $v_X = v_Y = 5 \text{ V}$,

$$v' = 0.8 + 0.7 + 0.7 \Rightarrow v' = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{8} \Rightarrow i_1 = 0.35 \text{ mA}$$

$$i_4 = i_1 - \frac{0.8}{15} \Rightarrow i_4 = 0.297 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{2.4} \Rightarrow i_3 = 2.04 \text{ mA}$$

17.16

- a. For $v_X = v_Y = 5 \text{ V}$, both Q_1 and Q_2 driven into saturation.

$$v_1 = 0.8 + 0.7 + 0.8 \Rightarrow v_1 = 2.3 \text{ V}$$

$$i_1 = \frac{5 - 2.3}{4} \Rightarrow i_1 = i_{B1} = 0.675 \text{ mA}$$

$$i_2 = \frac{5 - (0.8 + 0.7 + 0.1)}{2} \Rightarrow i_2 = 1.7 \text{ mA}$$

$$i_4 = i_{B1} + i_2 \Rightarrow i_4 = 2.375 \text{ mA}$$

$$i_5 = \frac{0.8}{10} \Rightarrow i_5 = 0.08 \text{ mA}$$

$$i_{B2} = i_4 - i_5 \Rightarrow i_{B2} = 2.295 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{4} \Rightarrow i_3 = 1.225 \text{ mA}$$

$$v_2 = 0.1 \text{ V}$$

- b. $i'_L = \frac{5 - (0.1 + 0.7)}{4} = 1.05 \text{ mA}$

$$i_C(\text{max}) = \beta i_{B2} = N i'_L + i_3$$

$$(20)(2.295) = N(1.05) + 1.225$$

So

$$N = 42$$

17.17

D_x and D_r off, Q_1 forward active mode

$$v_1 = 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$$

$$5 = i_1 R_1 + i_2 R_2 + v_1 \text{ and } i_1 = (1 + \beta) i_2$$

$$\text{So } 5 - 2.2 = i_2 [(1 + \beta) R_1 + R_2]$$

Assume $\beta = 25$

$$i_2 = \frac{5 - 2.2}{(26)(1.75) + 2} \Rightarrow i_2 = 0.0589 \text{ mA}$$

$$i_1 = (1 + \beta) i_2 = (26)(0.0589) \Rightarrow i_1 = 1.53 \text{ mA}$$

$$i_3 = \beta i_2 \Rightarrow i_3 = 1.47 \text{ mA}$$

$$i_{B0} = i_2 + i_3 - \frac{0.8}{5} = 0.0589 + 1.47 - 0.16 \Rightarrow$$

$$i_{B0} = 1.37 \text{ mA}$$

Q_2 in saturation

$$i_{C0} = \frac{5 - 0.1}{6} \Rightarrow i_{C0} = 0.817 \text{ mA}$$

17.18

- a. i. $v_X = v_Y = 0.1$ V, so Q_1 in saturation.

$$i_1 = \frac{5 - (0.1 + 0.8)}{6} \Rightarrow i_1 = 0.683 \text{ mA}$$

$$\Rightarrow i_{B2} = i_2 = i_4 = i_{B3} = i_3 = 0$$

- ii. $v_X = v_Y = 5$ V, so Q_1 in inverse active mode.
Assume Q_2 and Q_3 in saturation.

$$i_1 = \frac{5 - (0.8 + 0.8 + 0.7)}{6} \Rightarrow i_1 = i_{B2} = 0.45 \text{ mA}$$

$$i_2 = \frac{5 - (0.8 + 0.1)}{2} \Rightarrow i_2 = 2.05 \text{ mA}$$

$$i_4 = \frac{0.8}{1.5} \Rightarrow i_4 = 0.533 \text{ mA}$$

$$i_{B3} = (i_{B2} + i_2) - i_4 = 0.45 + 2.05 - 0.533$$

or

$$i_{B3} = 1.97 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{2.2} \Rightarrow i_3 = 2.23 \text{ mA}$$

- b. For Q_3 :

$$\frac{i_3}{i_{B3}} = \frac{2.23}{1.97} = 1.13 < \beta$$

For Q_2 :

$$\frac{i_2}{i_{B2}} = \frac{2.05}{0.45} = 4.56 < \beta$$

Since $(I_C/I_B) < \beta$, then each transistor is in saturation.

17.19

- (a) $v_X = v_Y = \text{Logic 1}$

$$v' = 0.8 + 2(0.7) = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{8} = 0.35 \text{ mA}$$

$$i_4 = i_1 - \frac{0.8}{15} = 0.35 - 0.0533 = 0.2967 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{2.4} = 2.04 \text{ mA}$$

$$i'_L = \frac{5 - (0.1 + 0.7)}{8} = 0.525 \text{ mA}$$

Assume $\beta = 25$

$$\text{Then } (25)(0.2967) = 2.04 + N(0.525)$$

$$\text{So } N = 10.2 \Rightarrow \underline{N = 10}$$

(b) Now

$$5 = 2.04 + N(0.525)$$

$$\text{So } N = 5.64 \Rightarrow \underline{N = 5}$$

17.20

- a. For $v_X = v_Y = 5$ V, Q_1 in inverse active mode.

$$i_{B1} = \frac{5 - (0.8 + 0.8 + 0.7)}{6} = 0.45 \text{ mA}$$

$$i_{B2} = i_{B1} + 2\beta_R i_{B1} = 0.45(1 + 2[0.1]) = 0.54 \text{ mA}$$

$$i_{C2} = \frac{5 - (0.8 + 0.1)}{2} = 2.05 \text{ mA}$$

$$i_{B3} = (i_{B2} + i_{C2}) - \frac{0.8}{1.5} = 0.54 + 2.05 - 0.533$$

or

$$i_{B3} = 2.06 \text{ mA}$$

Now

$$i'_L = \frac{5 - (0.1 + 0.8)}{6} = 0.683 \text{ mA}$$

Then

$$i_{C3}(\text{max}) = \beta_F i_{B3} = N i'_L$$

$$\text{or } (20)(2.06) = N(0.683)$$

$$\Rightarrow \underline{N = 60}$$

- b. From above, for v_O high, $I'_L = (0.1)(0.45) = 0.045 \text{ mA}$. Now

$$I'_L(\text{max}) = (1 + \beta_F) \left(\frac{5 - 4.9}{R_2} \right) = \frac{(21)(0.1)}{2} = 1.05 \text{ mA}$$

So

$$I_L(\text{max}) = N I'_L$$

$$\text{or } 1.05 = N(0.045)$$

$$\Rightarrow \underline{N = 23}$$

17.21

- (a) $V_{in} = 0.1$ V: Q_1 , Sat; Q_2 , Q_3 , Cutoff

$$i_1 = \frac{5 - (0.1 + 0.8)}{4} = 1.025 \text{ mA}$$

$$P = i_1(5 - 0.1) = (1.025)(4.9) \Rightarrow$$

$$P = 5.02 \text{ mW}$$

- (b) $V_{in} = 5$ V, Q_1 , Inverse Active; Q_2 , Q_3 , Saturation

$$v_{B1} = 0.7 + 0.8 + 0.7 = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{4} = 0.7 \text{ mA}$$

$$i_{B2} = \beta_R \cdot i_1 = (0.1)(0.7) = 0.07 \text{ mA}$$

$$V_{out} = 0.7 + 0.1 = 0.8 \text{ V}$$

$$i_2 = \frac{5 - 0.8}{1} = 4.2 \text{ mA}$$

$$P = (i_1 + i_{B2} + i_2)(5) = (0.7 + 0.07 + 4.2)(5) \Rightarrow$$

$$P = 24.9 \text{ mW}$$

17.22

a. $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{3.9} \Rightarrow \underline{i_{B1} = 1.05 \text{ mA}}$$

Then

$$\underline{i_{C1} = i_{B1} = i_{C2} = i_{B3} = i_{C3} = 0}$$

b. $v_X = v_Y = v_Z = 5 \text{ V}$

$$i_{B1} = \frac{5 - (0.8 + 0.8 + 0.7)}{3.9} \Rightarrow \underline{i_{B1} = 0.692 \text{ mA}}$$

Then

$$i_{C1} = i_{B2} = i_{B1}(1 + 3\beta_R) = (0.692)(1 + 3[0.5])$$

$$\Rightarrow \underline{i_{C1} = i_{B2} = 1.73 \text{ mA}}$$

$$i_{C2} = \frac{5 - (0.1 + 0.8)}{2} \Rightarrow \underline{i_{C2} = 2.05 \text{ mA}}$$

$$i_{B3} = i_{B1} + i_{C2} - \frac{0.8}{0.8} = 1.73 + 2.05 - 1.0$$

$$\Rightarrow \underline{i_{B3} = 2.78 \text{ mA}}$$

$$i_{R3} = \frac{5 - 0.1}{2.4} = 2.04 \text{ mA}$$

$$i'_L = \frac{5 - (0.1 + 0.8)}{3.9} = 1.05 \text{ mA}$$

$$i_{C3} = i_{R3} + 5i'_L = 2.04 + (5)(1.05)$$

$$\Rightarrow \underline{i_{C3} = 7.29 \text{ mA}}$$

17.23

a. $v_X = v_Y = v_Z = 2.8 \text{ V}$, Q_1 biased in the inverse active mode.

$$i_{B1} = \frac{2.8 - (0.8 + 0.8 + 0.7)}{2} \Rightarrow \underline{i_{B1} = 0.25 \text{ mA}}$$

$$i_{B2} = i_{B1}(1 + 3\beta_R) = 0.25(1 + 3[0.3])$$

$$\Rightarrow \underline{i_{B2} = 0.475 \text{ mA}}$$

$$v_{C2} = 0.8 + 0.1 = 0.9 \text{ V}$$

$$i_{B4} = \frac{0.9 - (0.7 + 0.1)}{(1 + \beta_F)(0.5)} = \frac{0.1}{(101)(0.5)}$$

$$= 0.00198 \text{ mA (Negligible)}$$

$$i_{R2} = \frac{5 - 0.9}{0.9} = 4.56 \text{ mA}$$

$$\Rightarrow \underline{i_{C2} = 4.56 \text{ mA}}$$

$$i_{B3} = i_{B2} + i_{C2} - \frac{0.8}{1} = 0.475 + 4.56 - 0.8$$

$$\Rightarrow \underline{i_{B3} = 4.235 \text{ mA}}$$

b. $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{2} \Rightarrow \underline{i_{B1} = 2.05 \text{ mA}}$$

From part (a),

$$i'_L = \beta_R i_{B1} = (0.3)(2.05) = 0.075 \text{ mA}$$

Then

$$i_{B4} = \frac{5i'_L}{1 + \beta_F} = \frac{5(0.075)}{101} \Rightarrow \underline{i_{B4} = 0.00371 \text{ mA}}$$

17.24

a. $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{R_{B1}} + i_{B3}$$

where

$$i_{B3} = \frac{(2 - 0.7) - (0.9)}{R_{B2}} = \frac{0.4}{1}$$

$$\Rightarrow \underline{i_{B3} = 0.4 \text{ mA}}$$

Then

$$i_{B1} = \frac{1.1}{1} + 0.4 \Rightarrow \underline{i_{B1} = 1.5 \text{ mA}}$$

$$\underline{i_{B2} = 0 = i_{C2}}$$

Q_3 in saturation $i_{C3} = 5i'_L$
For v_o high,

$$v'_{B1} = 0.8 + 0.7 = 1.5 \text{ V} \Rightarrow Q'_3 \text{ off}$$

$$i'_{B1} = \frac{2 - 1.5}{1} = 0.5 \text{ mA}$$

$$i'_L = \beta_R i'_{B1} = (0.2)(0.5) = 0.1 \text{ mA}$$

Then

$$\underline{i_{C3} = 0.5 \text{ mA}}$$

b. $v_X = v_Y = v_Z = 2 \text{ V}$

From part (a),

$$\Rightarrow \underline{i_{B1} = 0.5 \text{ mA}}$$

$$\underline{i_{B3} = 0 = i_{C1}}$$

$$i_{B2} = i_{B1}(1 + 3\beta_R) = (0.5)(1 + 3[0.2])$$

$$\underline{i_{B2} = 0.8 \text{ mA}}$$

$$i_{C2} = 5i'_L, \text{ and from part (a), } i'_L = 1.5 \text{ mA}$$

So

$$\underline{i_{C2} = 7.5 \text{ mA}}$$

17.25

$$(a) I_B + I_D = \frac{5.8 - 0.7}{10} = 0.51 \text{ mA}$$

$$I_C - I_D = \frac{5 - (0.7 - 0.3)}{1} = 4.6 \text{ mA}$$

Now

$$I_D = 0.51 - I_B = 0.51 - \frac{I_C}{\beta} = 0.51 - \frac{I_C}{50}$$

Then

$$I_C - I_D = I_C - \left(0.51 - \frac{I_C}{50}\right) = I_C \left(1 + \frac{1}{50}\right) - 0.51 = 4.6$$

So $I_C = 5.01 \text{ mA}$

$$I_B = \frac{I_C}{\beta} = \frac{5.01}{50} \Rightarrow I_B = 0.1002 \text{ mA}$$

$$I_D = 0.51 - 0.1002 \Rightarrow I_D = 0.4098 \text{ mA}$$

$$V_{CE} = 0.4 \text{ V}$$

$$(b) I_D = 0, V_{CE} = V_{CE(sat)} = 0.1 \text{ V}$$

$$I_B = \frac{5.8 - 0.8}{10} \Rightarrow I_B = 0.5 \text{ mA}$$

$$I_C = \frac{5 - 0.1}{1} \Rightarrow I_C = 4.9 \text{ mA}$$

17.26

$$a. \quad v_X = v_Y = 0.4 \text{ V}$$

$$v_{B1} = 0.4 + 0.7 \Rightarrow v_{B1} = 1.1 \text{ V}$$

$$i_{B1} = \frac{5 - 1.1}{2.8} \Rightarrow i_{B1} = 1.39 \text{ mA}$$

$$v_{B2} = 0.4 + 0.4 \Rightarrow v_{B2} = 0.8 \text{ V}$$

$$i_{B2} = i_{C2} = i_{B3} = i_{C3} = i_{B5} = i_{C5}$$

$$= i_{B3} = i_{C3} = 0 \text{ (No load)}$$

$$5 = i_{B1}R_2 + V_{BE} + (1 + \beta)i_{B1}R_4$$

$$i_{B1} = \frac{5 - 0.7}{0.76 + (31)(3.5)}$$

$$\Rightarrow i_{B1} = 0.0394 \text{ mA}$$

$$i_{C1} = \beta i_{B1}$$

$$\Rightarrow i_{C1} = 1.18 \text{ mA}$$

$$v_{B4} = 5 - (0.0394)(0.76)$$

$$\Rightarrow v_{B4} = 4.97 \text{ V}$$

$$b. \quad v_X = v_Y = 3.6 \text{ V}$$

$$v_{B1} = 0.7 + 0.7 + 0.3 \Rightarrow v_{B1} = 1.7 \text{ V}$$

$$v_{B2} = 1.4 \text{ V}$$

$$v_{B3} = 0.7 \text{ V}$$

$$v_{C2} = 1.1 \text{ V}$$

$$i_{B1} = \frac{5 - 1.7}{2.8}$$

$$\Rightarrow i_{B1} = 1.18 \text{ mA}$$

$$i_{B2} = i_{B1}(1 + 2\beta_N) = 1.18(1 + 2(0.1))$$

$$i_{B2} = 1.42 \text{ mA}$$

$$i_{B4} = \frac{1.1 - 0.7}{(31)(3.5)}$$

$$\Rightarrow i_{B4} = 0.00369 \text{ mA}$$

$$i_{B2} = \frac{5 - 1.1}{0.76} = 5.13 \text{ mA}$$

$$\Rightarrow i_{C2} \approx 5.13 \text{ mA}$$

$$i_{B3} \approx i_{B2} + i_{C2}$$

$$i_{B3} = 6.55 \text{ mA}$$

17.27

a. Assuming the output transistor Q_2 is a Schottky transistor, then

$$v_0 = 0.4 \text{ V}, i'_L = \frac{2.5 - (0.4 + 0.3)}{R_{B1}} = 0.5$$

Then

$$R_{B1} = 3.6 \text{ k}\Omega$$

Then

$$i_{B1} = \frac{2.5 - (0.7 + 0.8)}{R_{B1}} = \frac{10}{3.6} = 0.278 \text{ mA}$$

$$i_{B2} = 0.5 \text{ mA}, i_{E1} = 0.5 + \frac{0.7}{0.7} = 1.50 \text{ mA}$$

$$i_{E1} = i_{B1} + i_{C1} \Rightarrow i_{C1} = 1.50 - 0.278 = 1.222 \text{ mA}$$

$$\text{and } i_{C1} = \frac{2.5 - (0.7 + 0.1)}{R_{C1}} = 1.222 \text{ mA}$$

$$\Rightarrow R_{C1} = 1.39 \text{ k}\Omega$$

$$b. \quad v_X = v_Y = 0.4 \text{ V}, v_{B1} = 0.7 \text{ V}$$

$$v_{C2} = 2.5 - 0.7 \Rightarrow v_{C2} = 1.8 \text{ V}$$

All transistor currents are zero.

$$c. \quad v_{B1} = 1.5 \text{ V}, v_{C1} = 0.8 \text{ V}$$

Currents calculated in part (a).

$$d. \quad i_{B2} = 0.5 \text{ mA}, i'_L = 0.5 \text{ mA}$$

$$i_{C2}(\text{max}) = \beta i_{B2} = N i'_L \text{ or } (50)(0.5) = N(0.5)$$

So

$$N = 50$$

17.28

$$a. \quad \text{For } v_X = v_Y = 3.6 \text{ V}$$

$$v_{B1} = 3(0.7) = 2.1$$

$$\Rightarrow i_{B1} = \frac{5 - 2.1}{10} = 0.29 \text{ mA}$$

$$v_{C1} = 0.7 + 0.7 + 0.4 = 1.8 \text{ V}$$

$$\Rightarrow i_{C1} = \frac{5 - 1.8}{10} = 0.32 \text{ mA}$$

$$i_{B2} = i_{B1} + i_{C1} - \frac{1.4}{15} = 0.29 + 0.32 - 0.0933$$

So

$$i_{B2} = 0.517 \text{ mA}$$

$$v_{C2} = 0.7 + 0.4 = 1.1 \text{ V}$$

$$i_{C2} = \frac{5 - 1.1}{4.1} = 0.951 \text{ mA}$$

$$i_{B3} = i_{B1} + i_{C2} - \frac{0.7}{4} = 0.517 + 0.951 - 0.175$$

$$\text{or } i_{B3} = 1.293 \text{ mA}$$

$$\text{For } v_0 = 0.4 \text{ V, } v'_{B1} = 0.4 + 0.7 = 1.1 \text{ V}$$

Then

$$i'_{B1} = \frac{1.1 - 0.7}{(31)(15)} = 0.00086 \text{ mA}$$

$$i'_L = \frac{5 - 1.1}{10} - 0.00086 \text{ or } i'_L \approx 0.39 \text{ mA}$$

$$\text{So } i_{C3}(\text{max}) = \beta i_{B3} = N i'_L$$

$$(30)(1.293) = N(0.39)$$

$$\Rightarrow N = 99$$

$$\text{b. } P = (0.29 + 0.32 + 0.951)(5) + (99)(0.39)(0.4)$$

$$P = 7.805 + 15.444 \text{ or } P = 23.2 \text{ mW}$$

(Assuming 99 load circuits which is unreasonably large.)

17.29

$$\text{a. Assume no load. For } v_X = \text{logic } 0 = 0.4 \text{ V}$$

$$i_{B1} = \frac{5 - (0.4 + 0.7)}{40} = 0.0975 \text{ mA}$$

Essentially all of this current goes to ground from V_{CC} .

$$P = i_{B1} \cdot V_{CC} = (0.0975)(5)$$

$$\Rightarrow P = 0.4875 \text{ mW}$$

$$\text{b. } i_{R3} = \frac{5 - (3)(0.7)}{40} = 0.0725 \text{ mA}$$

$$i_{R2} = \frac{5 - (0.7 + 0.7 + 0.4)}{50} = 0.064 \text{ mA}$$

$$i_{R3} = \frac{5 - (0.7 + 0.4)}{15} = 0.26 \text{ mA}$$

$$P = (0.0725 + 0.064 + 0.26)(5)$$

$$P = 1.98 \text{ mW}$$

$$\text{c. For } v_0 = 0, v_{C1} = 0.7 + 0.4 = 1.1 \text{ V}$$

$$i_{R1} = \frac{5 - 1.1}{0.050} \Rightarrow i_{R1} = 78 \text{ mA} \approx i_{SC}$$

17.30

$$\text{(a) } v_i = v_o = 2.5 \text{ V; A transient situation}$$

$$v_{DS}(M_N) = 2.5 - 0.7 = 1.8 \text{ V}$$

$$v_{GS}(M_N) = 2.5 - 0.7 = 1.8 \text{ V} \Rightarrow M_N \text{ in saturation}$$

$$v_{SD}(M_P) = 5 - (2.5 + 0.7) = 1.8 \text{ V}$$

$$v_{SG}(M_P) = 5 - 2.5 = 2.5 \text{ V} \Rightarrow M_P \text{ in saturation}$$

$$i_{DN} = K_n (v_{GSN} - V_{TN})^2 = (0.1)(1.8 - 0.8)^2 \Rightarrow$$

$$i_{DN} = 0.1 \text{ mA}$$

$$i_{DP} = K_p (v_{SGP} - V_{TP})^2 = (0.1)(2.5 - 0.8)^2 \Rightarrow$$

$$i_{DP} = 0.289 \text{ mA}$$

$$i_{C1} = \beta i_{DP} = (50)(0.289) \Rightarrow i_{C1} = 14.45 \text{ mA}$$

$$i_{C2} = \beta i_{DN} = (50)(0.1) \Rightarrow i_{C2} = 5 \text{ mA}$$

Difference between i_{E1} and $i_{DN} + i_{C2}$ is a load current.

$$\text{(b) Assume } i_{C1} = 14.45 \text{ mA is a constant}$$

$$V_C = \frac{1}{C} \int i_{C1} dt = \frac{i_{C1} \cdot t}{C} \Rightarrow t = \frac{(V_C)(C)}{i_{C1}}$$

$$t = \frac{(5)(15 \times 10^{-12})}{14.45 \times 10^{-3}} \Rightarrow t = 5.19 \text{ ns}$$

$$\text{(c) } t = \frac{(5)(15 \times 10^{-12})}{0.289 \times 10^{-3}} \Rightarrow t = 260 \text{ ns}$$

17.31

$$\text{Let } R_1 = R_2 = 10 \text{ k}\Omega$$

$$\text{(a) } i_{DN} = 0.1 \text{ mA, } i_{DP} = 0.289 \text{ mA}$$

(Same as Problem 17.30)

$$i_{R1} = \frac{0.7}{10} = 0.07 \text{ mA} \Rightarrow i_{B1} = 0.289 - 0.07 = 0.219 \text{ mA}$$

$$i_{C1} = (50)(0.219) \Rightarrow i_{C1} = 10.95 \text{ mA}$$

$$i_{R2} = \frac{0.7}{10} = 0.07 \text{ mA} \Rightarrow i_{B2} = 0.1 - 0.07 = 0.03 \text{ mA}$$

$$i_{C2} = (50)(0.03) \Rightarrow i_{C2} = 1.5 \text{ mA}$$

$$\text{(b) } t = \frac{(5)(15 \times 10^{-12})}{10.95 \times 10^{-3}} \Rightarrow t = 6.85 \text{ ns}$$

$$\text{(c) } t = 260 \text{ ns (Same as Problem 17.30)}$$