

## Chapter 10

## Exercise Solutions

E10.1

$$I_{REF} = \frac{V^+ - V_{BE(on)}}{R_1} = \frac{10 - 0.7}{15}$$

$$I_{REF} = 0.62 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{0.62}{1 + \frac{2}{75}}$$

$$I_0 = 0.604 \text{ mA}$$

E10.2

$$\text{For } I_0 = 0.75 \text{ mA}$$

$$I_{REF} = I_0 \left( 1 + \frac{2}{\beta} \right) = (0.75) \left( 1 + \frac{2}{100} \right)$$

$$I_{REF} = 0.765 \text{ mA}$$

$$I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1}$$

$$R_1 = \frac{5 - 0.7 - (-5)}{0.765}$$

$$R_1 = 12.2 \text{ k}\Omega$$

E10.3

$$I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1} = \frac{5 - 0.7 - (-5)}{12}$$

$$I_{REF} = 0.775 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{0.775}{1 + \frac{2}{75}} = 0.754 \text{ mA}$$

$$\Delta I_0 = (0.02)(0.754) = 0.0151 \text{ mA}$$

$$\text{and } \Delta I_0 = \frac{1}{r_0} \Delta V_{CE2} \Rightarrow r_0 = \frac{\Delta V_{CE2}}{\Delta I_0}$$

$$r_0 = \frac{4}{0.0151} = 265 \text{ k}\Omega = \frac{V_A}{I_0}$$

$$\Rightarrow V_A = (265)(0.754) \Rightarrow V_A \approx 200 \text{ V}$$

E10.4

$$I_{REF} = \frac{V^+ - 2V_{BE(on)}}{R_1} = \frac{9 - 2(0.7)}{12}$$

$$I_{REF} = 0.6333 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta(1+\beta)}} = \frac{0.6333}{1 + \frac{2}{75(76)}} = 0.6331 \text{ mA}$$

$$I_0 = 0.6331 \text{ mA} = I_{C1}$$

$$I_{B1} = I_{B2} = \frac{I_0}{\beta} \Rightarrow I_{B1} = I_{B2} = 8.44 \text{ }\mu\text{A}$$

$$I_{E3} = I_{B1} + I_{B2} \Rightarrow I_{E3} = 16.88 \text{ }\mu\text{A}$$

$$I_{B3} = \frac{I_{E3}}{1 + \beta} \Rightarrow I_{B3} = 0.222 \text{ }\mu\text{A}$$

E10.5

$$I_{REF} = \frac{10 - (0.7)(2)}{12} = 0.717 \text{ mA}$$

$$I_0 \approx I_{REF} = 0.717$$

$$r_0 = \frac{V_A}{I_0} = \frac{100}{0.717} \Rightarrow r_0 = 139 \text{ k}\Omega$$

$$\Delta I_0 = \frac{1}{r_0} \Delta V_{CE2} = \frac{4}{139}$$

$$\Rightarrow \Delta I_0 = 0.0288 \text{ mA}$$

E10.6

$$I_0 = I_{REF} \cdot \frac{1}{\left( 1 + \frac{2}{\beta(1+\beta)} \right)} = \frac{0.50}{\left( 1 + \frac{2}{50(51)} \right)}$$

$$\Rightarrow I_0 = 0.4996 \text{ mA}$$

$$I_{B3} = \frac{I_0}{\beta} \Rightarrow I_{B3} = 9.99 \text{ }\mu\text{A}$$

$$I_{E3} = \left( 1 + \frac{\beta}{\beta} \right) I_{C3} \Rightarrow I_{E3} = 0.5096 \text{ mA}$$

$$I_{C2} = \frac{I_{E3}}{\left( 1 + \frac{2}{\beta} \right)} = \frac{0.5096}{\left( 1 + \frac{2}{50} \right)}$$

$$\Rightarrow I_{C2} = 0.490 \text{ mA} = I_{C1}$$

$$I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} \Rightarrow I_{B1} = I_{B2} = 9.80 \text{ }\mu\text{A}$$

E10.7

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$R_E = \frac{V_T}{I_0} \ln \left( \frac{I_{REF}}{I_0} \right) = \frac{0.026}{0.025} \ln \left( \frac{0.75}{0.025} \right)$$

$$\Rightarrow R_E = 3.54 \text{ k}\Omega$$

$$R_1 = \frac{5 - 0.7}{0.75} \Rightarrow R_1 = 5.73 \text{ k}\Omega$$

$$V_{BE1} - V_{BE2} = I_0 R_E = (0.025)(3.54)$$

$$\Rightarrow V_{BE1} - V_{BE2} = 88.5 \text{ mV}$$

E10.8

$$I_{REF} = \frac{5 - 0.7 - (-5)}{12} \Rightarrow I_{REF} = 0.775 \text{ mA}$$

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$I_0(6) = (0.026) \ln \left( \frac{0.775}{I_0} \right)$$

$$\Rightarrow I_0 \approx 16.6 \text{ }\mu\text{A}$$

E10.9

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$R_E = \frac{0.026}{0.025} \ln \left( \frac{0.70}{0.025} \right) \Rightarrow R_E = 3.47 \text{ k}\Omega$$

$$g_{m1} = \frac{I_0}{V_T} = \frac{0.025}{0.026} \Rightarrow g_{m2} = 0.962 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_0} = \frac{(150)(0.026)}{0.025} = 156 \text{ k}\Omega$$

$$r_{o2} = \frac{V_A}{I_0} = \frac{100}{0.025} = 4000 \text{ k}\Omega$$

$$R'_E = R_E \parallel r_{\pi 2} = 3.47 \parallel 156 = 3.39 \text{ k}\Omega$$

$$R_0 = r_{o2} (1 + g_{m2} R'_E) = 4000 [1 + (0.962)(3.39)]$$

$$R_0 = 17,045 \text{ k}\Omega$$

$$dI_0 = \frac{1}{R_0} \cdot dV_{C2} = \frac{3}{17,045}$$

$$\Rightarrow dI_0 = 0.176 \text{ }\mu\text{A}$$

E10.10

$$I_{REF} = I_R + I_{B1} + I_{B2} + \dots + I_{BN}$$

$$I_R = I_{O1} = I_{O2} = \dots = I_{ON}$$

$$\text{and } I_{B1} = I_{B2} = \dots = I_{BN} = \frac{I_{O1}}{\beta}$$

$$I_{REF} = I_{O1} + (N+1) \left( \frac{I_{O1}}{\beta} \right) = I_{O1} \left( 1 + \frac{N+1}{\beta} \right)$$

$$\text{So } I_{O1} = I_{O2} = \dots = I_{ON} = \frac{I_{REF}}{1 + \frac{N+1}{\beta}}$$

$$\frac{I_{O1}}{I_{REF}} = 0.90 = \frac{1}{1 + \frac{N+1}{50}}$$

$$1 + \frac{N+1}{50} = \frac{1}{0.9}$$

$$N+1 = \left( \frac{1}{0.9} - 1 \right) (50)$$

$$N = \left( \frac{1}{0.9} - 1 \right) (50) - 1$$

$$N = 4.55 \Rightarrow \underline{N=4}$$

E10.11

a. From Equation (10.52),

$$V_{GS1} = \frac{\sqrt{\frac{3}{12}}}{1 + \sqrt{\frac{3}{12}}} \times 10 + \left( \frac{1 - \sqrt{\frac{3}{12}}}{1 + \sqrt{\frac{3}{12}}} \right) \times (1.8)$$

$$V_{GS1} = \left( \frac{0.5}{1 + 0.5} \right) (10) + \left( \frac{1 - 0.5}{1 + 0.5} \right) \times (1.8)$$

$$V_{GS1} = 3.93 \text{ V also } V_{DS1} = 3.93 \text{ V}$$

$$I_{REF} = (12)(0.020)[3.93 - 1.8]^2 [1 + (0.01)(3.93)]$$

$$\Rightarrow \underline{I_{REF} = 1.13 \text{ mA}}$$

$$\text{b. } I_0 = I_{REF} \times \frac{(W/L)_2}{(W/L)_1} \times \frac{(1 + \lambda V_{DS2})}{(1 + \lambda V_{DS1})}$$

$$I_0 = (1.13) \times \left( \frac{6}{12} \right) \times \frac{[1 + (0.01)(2)]}{[1 + (0.01)(3.93)]}$$

$$\Rightarrow \underline{I_0 = 0.555 \text{ mA}}$$

$$\text{c. For } V_{DS2} = 6 \text{ V}$$

$$\Rightarrow \underline{I_0 = 0.576 \text{ mA}}$$

E10.12

$$K_{n1}(V_{GS1} - V_{TN})^2 = K_{n3}(V_{GS3} - V_{TN})^2$$

$$V_{GS1} - 2 = \left( \sqrt{\frac{0.10}{0.25}} \right) (V_{GS3} - 2)$$

$$V_{GS1} - 2 = (0.632)(V_{GS3} - 2)$$

$$V_{GS3} = 10 - V_{GS1}$$

$$V_{GS1} - 2 = (0.632)(10 - V_{GS1}) - (0.632)(2)$$

$$1.632V_{GS1} = 7.056 \Rightarrow V_{GS1} = 4.32 \text{ V}$$

$$I_{REF} = K_{n1}(V_{GS1} - V_{TN})^2 = (0.25)(4.32 - 2)^2 \Rightarrow$$

$$\underline{I_{REF} = 1.35 \text{ mA}}$$

$$I_O = 3K_{n2}(V_{GS1} - V_{TN})^2 = 3(0.25)(4.32 - 2)^2$$

$$I_O = 3I_{REF} \Rightarrow \underline{I_O = 4.04 \text{ mA}}$$

E10.13

$$V_{DS}(\text{sat}) = 1 \text{ V} = V_{GS2} - V_{TN} = V_{GS2} - 2$$

$$\Rightarrow V_{GS2} = 3 \text{ V}$$

$$I_O = K_{n2}(V_{GS2} - V_{TN})^2 = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2$$

$$0.20 = (0.020) \left( \frac{W}{L} \right)_2 (3 - 2)^2 \Rightarrow \underline{\left( \frac{W}{L} \right)_2 = 10}$$

$$I_{REF} = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2$$

$$V_{GS1} = V_{GS2}$$

$$0.5 = (0.020) \left( \frac{W}{L} \right)_1 (3 - 2)^2 \Rightarrow \underline{\left( \frac{W}{L} \right)_1 = 25}$$

$$V_{GS3} = V^+ - V_{GS1} = 10 - 3 = 7 \text{ V}$$

$$I_{REF} = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$0.5 = (0.020) \left( \frac{W}{L} \right)_3 (7 - 2)^2 \Rightarrow \underline{\left( \frac{W}{L} \right)_3 = 1}$$

E10.14

$$\text{a. } I_{REF} = K_n(V_{GS} - V_{TN})^2$$

$$0.020 = 0.080(V_{GS} - 1)^2$$

$$\underline{V_{GS} = 1.5 \text{ V all transistors}}$$

$$b. \quad V_{G4} = V_{GS3} + V_{GS1} + V^- = 1.5 + 1.5 - 5 = -2 \text{ V}$$

$$V_{S4} = V_{G4} - V_{GS4} = -2 - 1.5 = -3.5 \text{ V}$$

$$V_{D4}(\min) = V_{S4} + V_{DS4}(\text{sat})$$

$$\text{and } V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 1.5 - 1 = 0.5 \text{ V}$$

$$\text{So } V_{D4}(\min) = -3.5 + 0.5$$

$$\Rightarrow \underline{V_{D4}(\min) = -3.0 \text{ V}}$$

$$c. \quad R_0 = r_{o4} + r_{o2}(1 + g_m r_{o4})$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_0} = \frac{1}{(0.02)(0.020)} = 2500 \text{ k}\Omega$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.080)(1.5 - 1) \Rightarrow$$

$$g_m = 0.080 \text{ mA/V}$$

$$R_0 = 2500 + 2500(1 + (0.080)(2500))$$

$$\Rightarrow \underline{R_0 = 505 \text{ M}\Omega}$$

E10.15

$$I_{REF} = 0.20 = K_{n1}(V_{GS1} - V_{TN})^2 = 0.15(V_{GS1} - 1)^2$$

$$\Rightarrow \underline{V_{GS1} = V_{GS2} = 2.15 \text{ V}}$$

$$I_0 = K_{n2}(V_{GS2} - V_{TN})^2 = \frac{0.15}{2}(2.15 - 1)^2 \Rightarrow$$

$$\underline{I_0 = 0.10 \text{ mA}}$$

$$I_0 = K_{n3}(V_{GS3} - V_{TN})^2$$

$$0.10 = 0.15(V_{GS3} - 1)^2 \Rightarrow \underline{V_{GS3} = 1.82 \text{ V}}$$

E10.16

All transistors are identical

$$\Rightarrow \underline{I_0 = I_{REF} = 250 \text{ }\mu\text{A}}$$

$$I_{REF} = K_n(V_{GS} - V_{TN})^2$$

$$0.25 = 0.20(V_{GS} - 1)^2$$

$$\Rightarrow \underline{V_{GS} = 2.12 \text{ V}}$$

E10.17

$$\text{For } Q_2: \nu_{DS}(\min) = |V_P| = 2 \text{ V}$$

$$\Rightarrow V_S(\min) = \nu_{DS}(\min) - 5 = 2 - 5$$

$$\Rightarrow \underline{V_S(\min) = -3 \text{ V}}$$

$$I_0 = I_{DSS2}(1 + \lambda \nu_{DS2}) = 0.5(1 + (0.15)(2))$$

$$\Rightarrow \underline{I_0 = 0.65 \text{ mA}}$$


$$I_0 = I_{DSS1}\left(1 - \frac{\nu_{GS1}}{V_{P1}}\right)^2$$

$$0.65 = 0.80\left(1 - \frac{\nu_{GS1}}{-2}\right)^2$$


$$\frac{\nu_{GS1}}{-2} = 0.0986 \Rightarrow \nu_{GS1} = -0.197 \text{ V}$$

$$\nu_{GS1} = V_I - V_S$$
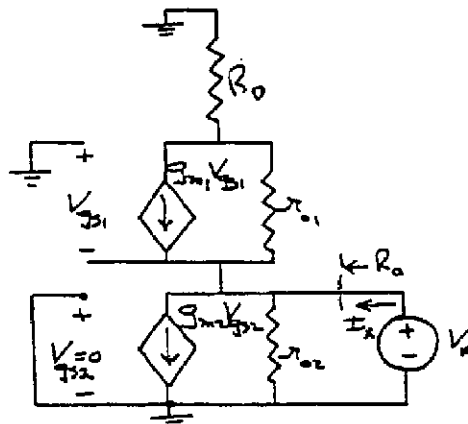
$$-0.197 = V_I - (-3) \Rightarrow \underline{V_I(\min) = -3.2 \text{ V}}$$



$$V_{gs2} = 0, \quad V_{gs1} = -V_X$$

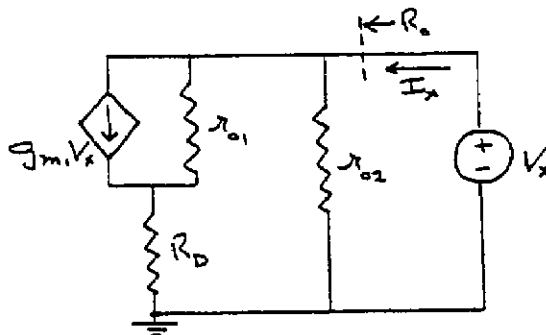

$$I_X = \frac{V_X}{R_D} + \frac{V_X - V_1}{r_{o1}} + g_{m1} V_X \quad (1)$$

$$\frac{V_1}{R_D} + \frac{V_1 - V_X}{r_{o1}} = g_{m1} V_X \quad (2)$$

$$V_1 = \frac{V_X \left( \frac{1}{r_{o1}} + g_{m1} \right)}{\frac{1}{R_D} + \frac{1}{r_{o1}}}$$

$$\begin{aligned} \frac{I_X}{V_X} &= \frac{1}{R_D} = \frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_{m1} - \frac{\frac{1}{r_{o1}} \left( \frac{1}{r_{o1}} + g_{m1} \right)}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \\ &= \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right) \left[ 1 - \frac{\frac{1}{r_{o1}}}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \right] \\ &= \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right) \left( \frac{\frac{1}{R_D}}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \right) \end{aligned}$$

For  $R_D \ll r_{o1}$ 

$$\Rightarrow \frac{1}{R_o} \approx \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right)$$

For  $Q_1$ :

$$g_{m1} = \frac{2I_{DSS1}}{|V_P|} \left( 1 - \frac{V_{GS1}}{V_P} \right) = \frac{2(0.8)}{2} \left( 1 - \frac{-0.197}{-2} \right)$$

$$g_{m1} = 0.721 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_o} = \frac{1}{(0.15)(0.65)} = 10.3 \text{ k}\Omega$$

$$\frac{1}{R_o} = \frac{1}{10.3} + \frac{1}{10.3} + 0.721 = 0.915$$

$$\Rightarrow \underline{R_o = 1.09 \text{ k}\Omega}$$

E10.18

$$\text{For } Q_1: i_D = I_{DSS1}(1 + \lambda v_{DS1})$$

$$\text{For } Q_2: i_D = I_{DSS2} \left( 1 - \frac{v_{GS2}}{V_P} \right)^2 (1 + \lambda v_{DS2})$$

$$v_{GS2} = -v_{DS1}$$

$$\text{and } v_{DS2} = V_{DS} - v_{DS1}$$

So

$$\begin{aligned} I_{DSS1}(1 + \lambda v_{DS1}) \\ = I_{DSS2} \left[ 1 - \frac{-v_{DS1}}{V_P} \right]^2 [1 + \lambda(V_{DS} - v_{DS1})] \end{aligned}$$

$$I_{DSS1} = I_{DSS2}$$

$$[1 + (0.1)v_{DS1}]$$

$$= \left[ 1 - \frac{v_{DS1}}{2} \right]^2 [1 + (0.1)(3) - (0.1)v_{DS1}]$$

$$1 + 0.1v_{DS1} = (1 - v_{DS1} + 0.25v_{DS1}^2)(1.3 - 0.1v_{DS1})$$

This becomes

$$0.025v_{DS1}^3 - 0.425v_{DS1}^2 + 1.5v_{DS1} - 0.3 = 0$$

$$\text{We find } \underline{v_{DS1} = 0.212 \text{ V}}, \quad \underline{v_{DS2} = 2.79 \text{ V}}$$

$$\underline{v_{GS2} = -0.212 \text{ V}}$$

$$i_D = I_{DSS1}(1 + \lambda v_{DS1}) = 2[1 + (0.1)(0.212)]$$

$$\underline{i_D = 2.04 \text{ mA}}$$

$$R_o = r_{o2} + r_{o1}(1 + g_{m2}r_{o2})$$

$$g_m = \frac{2I_{DSS}}{-V_P} \left( 1 - \frac{v_{GS2}}{V_P} \right) = \frac{2(2)}{-2} \left( 1 - \frac{-0.212}{-2} \right)$$

$$g_m = 1.79 \text{ mA/V}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_{DSS}} = \frac{1}{(0.1)(2)} = 5 \text{ k}\Omega$$

$$R_o = 5 + 5[1 + (1.79)(5)]$$

$$\Rightarrow \underline{R_o = 54.8 \text{ k}\Omega}$$

E10.19

$$\text{a. } I_{REF} = I_S \exp \left( \frac{V_{EB2}}{V_T} \right)$$

$$V_{EB2} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{10^{-12}} \right)$$

$$\Rightarrow \underline{V_{EB2} = 0.521 \text{ V}}$$

$$\text{b. } R_1 = \frac{5 - 0.521}{0.5} \Rightarrow \underline{R_1 = 8.96 \text{ k}\Omega}$$

c. From Equation (10.72)

$$I_{S0} \left[ \exp \left( \frac{V_I}{V_T} \right) \right] \left( 1 + \frac{V_{CE0}}{V_{AN}} \right) = I_{REF} \times \frac{\left( 1 + \frac{V_{EC2}}{V_{AP}} \right)}{\left( 1 + \frac{V_{EB2}}{V_{AP}} \right)}$$

$$\begin{aligned} 10^{-12} \left[ \exp \left( \frac{V_I}{V_T} \right) \right] \left( 1 + \frac{2.5}{100} \right) \\ = (0.5 \times 10^{-3}) \frac{\left( 1 + \frac{2.5}{100} \right)}{\left( 1 + \frac{0.521}{100} \right)} \end{aligned}$$

$$1.03 \times 10^{-12} \exp \left( \frac{V_I}{V_T} \right) = 5.125 \times 10^{-4}$$

$$\exp \left( \frac{V_I}{V_T} \right) = 4.976 \times 10^8$$

$$\Rightarrow \underline{V_I = 0.521 \text{ V}}$$

d.

$$A_v = \frac{-\left( \frac{1}{V_T} \right)}{\frac{1}{V_{AN}} + \frac{1}{V_{AP}}} = \frac{-\frac{1}{0.026}}{\frac{1}{100} + \frac{1}{100}} = \frac{-38.46}{0.01 + 0.01}$$

$$\Rightarrow \underline{A_v = -1923}$$

E10.20

$$\text{a. } V_{EB2} = (0.026) \ln \left( \frac{0.1 \times 10^{-3}}{5 \times 10^{-14}} \right)$$

$$\Rightarrow \underline{V_{EB2} = 0.557 \text{ V}}$$

$$\text{b. } R_1 = \frac{5 - 0.557}{0.1} \Rightarrow \underline{R_1 = 44.4 \text{ k}\Omega}$$

$$\begin{aligned} \text{c. } I_{S0} \left[ \exp \left( \frac{V_I}{V_T} \right) \right] \left( 1 + \frac{V_{CE0}}{V_{AN}} \right) \\ = I_{REF} \times \frac{\left( 1 + \frac{V_{EC2}}{V_{AP}} \right)}{\left( 1 + \frac{V_{EB2}}{V_{AP}} \right)} \end{aligned}$$

$$5 \times 10^{-14} \left[ \exp \left( \frac{V_I}{V_T} \right) \right] \left( 1 + \frac{2.5}{100} \right) \\ = (0.1 \times 10^{-3}) \left( \frac{1 + \frac{2.5}{100}}{1 + \frac{0.557}{100}} \right)$$

$$(5.125 \times 10^{-14}) \exp \left( \frac{V_I}{V_T} \right) = 1.019 \times 10^{-4}$$

$$\exp \left( \frac{V_I}{V_T} \right) = 1.988 \times 10^9$$

$$\Rightarrow \underline{V_I = 0.557 \text{ V}}$$

$$d. \quad A_v = \frac{-\frac{1}{0.026}}{\frac{1}{100} + \frac{1}{100}} \Rightarrow \underline{A_v = -1923}$$

## E10.21

$$a. \quad I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$0.25 = 0.20(V_{SG} - 1)^2$$

$$\Rightarrow \underline{V_{SG} = 2.12 \text{ V}}$$

$$b. \quad \text{From Equation (10.89)}$$

$$V_{DSO} = V_o = \frac{[1 + \lambda_p(V^+ - V_{SG})]}{\lambda_n + \lambda_p} - \frac{K_n(V_I - V_{TN})^2}{I_{REF}(\lambda_n + \lambda_p)}$$

$$5 = \frac{1 + (0.015)(10 - 2.12)}{0.030} - \frac{(0.2)(V_I - 1)^2}{0.25(0.030)}$$

$$0.15 = 1.12 - 0.8(V_I - 1)^2$$

$$\Rightarrow \underline{V_I = 2.10 \text{ V}}$$

$$c. \quad A_v = \frac{-2K_n(V_I - V_{TN})}{I_{REF}(\lambda_n + \lambda_p)}$$

$$A_v = -\frac{2(0.2)(2.10 - 1.0)}{0.25(0.030)}$$

$$\Rightarrow \underline{A_v = -58.7}$$

## E10.22

$$(a) \quad I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$80 = 50(V_{SG} - 1)^2 \Rightarrow \underline{V_{SG} = 2.26 \text{ V}}$$

$$(b) \quad V_{DSO} = V_o = \frac{[1 + \lambda_p(V^+ - V_{SG})]}{\lambda_n + \lambda_p} - \frac{K_n(V_I - V_{TN})^2}{I_{REF}(\lambda_n + \lambda_p)}$$

$$5 = \frac{[1 + (0.015)(10 - 2.26)]}{0.030} - \frac{(50)(V_I - 1)^2}{(80)(0.030)}$$

$$20.83(V_I - 1)^2 = 32.2 \Rightarrow \underline{V_I = 2.24 \text{ V}}$$

$$(c) \quad A_v = \frac{-2K_n(V_I - V_{TN})}{I_{REF}(\lambda_n + \lambda_p)} = \frac{-2(50)(2.24 - 1)}{(80)(0.030)} \Rightarrow$$

$$\underline{A_v = -51.7}$$

## E10.23

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.8}{0.026} = 30.8 \text{ mA/V}$$

$$r_o = r_{o2} = \frac{V_A}{I_{CQ}} = \frac{80}{0.8} = 100 \text{ k}\Omega$$

$$a. \quad V_o = -g_m V_{x1}(r_o || r_{o2}), \quad V_{x1} = V_i$$

$$A_v = -g_m(r_o || r_{o2}) = -(30.8)[100 || 100]$$

$$\Rightarrow \underline{A_v = -1540}$$

$$b. \quad A_v = -g_m(r_o || r_{o2} || R_L)$$

$$A_v = -\frac{1540}{2} = -770$$

$$-770 = -(30.8)(50 || R_L) \Rightarrow (50 || R_L) = 25$$

$$\Rightarrow \underline{R_L = 50 \text{ k}\Omega}$$

## E10.24

$$a. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} \Rightarrow \underline{g_m = 19.2 \text{ mA/V}}$$

$$r_o = \frac{V_{AN}}{I_{CQ}} = \frac{120}{0.5} \Rightarrow \underline{r_o = 240 \text{ k}\Omega}$$

$$r_{o2} = \frac{V_{AP}}{I_{CQ}} = \frac{80}{0.5} \Rightarrow \underline{r_{o2} = 160 \text{ k}\Omega}$$

$$b. \quad A_v = -g_m(r_o || r_{o2} || R_L) = -(19.2)[240 || 160 || 50]$$

$$\Rightarrow \underline{A_v = -631}$$

## E10.25

(a) Neglecting effect of  $\lambda$  and  $R_L$ 

$$I_O = I_{REF} = K_n (V_{IQ} - V_{TN})^2$$

$$0.40 = 0.25(V_{IQ} - 1)^2$$

$$\text{Then } \underline{V_{IQ} = 2.26 \text{ V}}$$

$$\text{b. } r_o = r_{o2} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.4)} = 125 \text{ k}\Omega$$

$$g_m = 2K_n(V_{IQ} - V_{TN}) = 2(0.25)(2.26 - 1) \\ = 0.63 \text{ mA/V}$$

$$A_v = -g_m(r_o \parallel r_{o2}) = -(0.63)(125 \parallel 125)$$

$$\Rightarrow \underline{A_v = -39.4}$$

$$\text{c. } A_v = -g_m(r_o \parallel r_{o2} \parallel R_L)$$

$$-\frac{39.4}{2} = -(0.63)(62.5 \parallel R_L)$$

$$\Rightarrow 62.5 \parallel R_L = 31.25 \Rightarrow \underline{R_L = 62.5 \text{ k}\Omega}$$

## E10.26

$$M_1 \text{ and } M_2 \text{ identical} \Rightarrow I_O = I_{REF}$$

$$\text{a. } I_O = K_n(V_I - V_{TN})^2$$

$$0.25 = 0.2(V_I - 1)^2$$

$$V_I = 2.12 \text{ V}$$

$$g_m = 2K_n(V_I - V_{TN}) = 2(0.2)(2.12 - 1)$$

$$\Rightarrow \underline{g_m = 0.448 \text{ mA/V}}$$

$$r_{on} = \frac{1}{\lambda_n I_O} = \frac{1}{(0.01)(0.25)} \Rightarrow \underline{r_{on} = 400 \text{ k}\Omega}$$

$$r_{op} = \frac{1}{\lambda_p I_O} = \frac{1}{(0.02)(0.25)} \Rightarrow \underline{r_{op} = 200 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_m(r_o \parallel r_{o2} \parallel R_L)$$

$$A_v = -(0.448)[400 \parallel 200 \parallel 100]$$

$$\Rightarrow \underline{A_v = -25.6}$$

## Chapter 10

## Problem Solutions

10.1

$$a. \quad I_1 = I_2 = \frac{0 - 2V_T - V^-}{R_1 + R_2}$$

$$2V_T + I_2 R_2 = V_{BE} + I_C R_3$$

$$2V_T + \frac{R_2}{R_1 + R_2}(-2V_T - V^-) = V_{BE} + I_C R_3$$

$$I_C = \frac{1}{R_3} \left\{ 2V_T - (2V_T + V^-) \left( \frac{R_2}{R_1 + R_2} \right) - V_{BE} \right\}$$

$$b. \quad V_T = V_{BE} \text{ and } R_1 = R_2$$

$$I_C = \frac{1}{R_3} \left\{ 2V_T - \frac{1}{2}(2V_T + V^-) - V_{BE} \right\}$$

$$\text{or } I_C = \frac{-V^-}{2R_3}$$

$$c. \quad I_C = 2 \text{ mA} = \frac{-(-10)}{2R_3} \Rightarrow R_3 = 2.5 \text{ k}\Omega$$

$$I_1 = I_2 = 2 \text{ mA} = \frac{-2(0.7) - (-10)}{R_1 + R_2}$$

$$\Rightarrow R_1 + R_2 = 4.3 \text{ k}\Omega$$

$$\Rightarrow R_1 = R_2 = 2.15 \text{ k}\Omega$$

10.2

$$I_{C2} = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{1}{1 + \frac{2}{50}}$$

$$I_{C1} = I_{C2} = 0.962 \text{ mA}$$

$$I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} \Rightarrow I_{B1} = I_{B2} = 0.0192 \text{ mA}$$

10.3

$$(a) \quad I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1}$$

or

$$R_1 = \frac{15 - 0.7 - (-15)}{0.5} \Rightarrow R_1 = 58.6 \text{ k}\Omega$$

$$(b) \quad R_2 = \frac{V^+ - V_{BE(on)} - V^-}{I_{REF}} = \frac{0 - 0.7 - (-15)}{0.5} \Rightarrow$$

$$R_2 = 28.6 \text{ k}\Omega$$

Advantage: Requires smaller resistance.

(c) For part (a):

$$I_O(\text{max}) = \frac{29.3}{(58.6)(0.95)} = 0.526 \text{ mA}$$

$$I_O(\text{min}) = \frac{29.3}{(58.6)(1.05)} = 0.476 \text{ mA}$$

$$\Delta I_O = 0.526 - 0.476 = 0.05 \text{ mA} \Rightarrow \pm 5\%$$

$$\text{For part (b): } I_O(\text{max}) = \frac{14.3}{(28.6)(0.95)} = 0.526 \text{ mA}$$

$$I_O(\text{min}) = \frac{14.3}{(28.6)(1.05)} = 0.476 \text{ mA}$$

$$\Delta I_O = 0.05 \text{ mA} \Rightarrow \pm 5\%$$

10.4

$$a. \quad I_{REF} = I_O \left( 1 + \frac{2}{\beta} \right) = 2 \left( 1 + \frac{2}{100} \right)$$

$$\text{or } I_{REF} = 2.04 \text{ mA}$$

$$R_1 = \frac{15 - 0.7}{2.04} \Rightarrow R_1 = 7.01 \text{ k}\Omega$$

$$b. \quad r_o = \frac{V_A}{I_O} = \frac{80}{2} = 40 \text{ k}\Omega$$

$$\frac{\Delta I_O}{\Delta V_{CE}} = \frac{1}{r_o} \Rightarrow \Delta I_O = \left( \frac{1}{40} \right) (9.3) = 0.2325 \text{ mA}$$

$$\frac{\Delta I_O}{I_O} = \frac{0.2325}{2} \Rightarrow \frac{\Delta I_O}{I_O} = 11.6\%$$

10.5

$$I_{REF} = I_O \left( 1 + \frac{2}{\beta} \right) = (0.5) \left( 1 + \frac{2}{25} \right)$$

$$= 0.54 \text{ mA} = I_{REF}$$

$$R_1 = \frac{5 - 0.7}{0.54} \Rightarrow R_1 = 7.96 \text{ k}\Omega$$

10.6

$$a. \quad I_{REF} = \frac{5 - 0.7}{18} = 0.239 \text{ mA}$$

$$I_O = \frac{0.239}{1 + \frac{2}{50}} \Rightarrow I_O = 0.230 \text{ mA}$$

$$b. \quad r_o = \frac{V_A}{I_O} = \frac{50}{0.230} = 217 \text{ k}\Omega$$

$$\Delta I_O = \frac{1}{r_o} \cdot \Delta V_{EC} = \left( \frac{1}{217} \right) (1.3) = 0.00599 \text{ mA}$$

$$\Rightarrow I_O = 0.236 \text{ mA}$$

$$c. \quad \Delta I_O = \left( \frac{1}{217} \right) (3.3) = 0.0152 \text{ mA}$$

$$\Rightarrow I_O = 0.245 \text{ mA}$$

10.7

$$a. \quad I_{REF} = 1 = \frac{5 - 0.7 - (-5)}{R_1}$$

$$\Rightarrow R_1 = 9.3 \text{ k}\Omega$$

$$b. \quad I_0 = 2I_{REF} \Rightarrow I_0 = 2 \text{ mA}$$

$$c. \quad \text{For } V_{BE2}(\min) = 0.7 \Rightarrow R_{C2} = \frac{5 - 0.7}{2}$$

$$\Rightarrow R_{C2} = 2.15 \text{ k}\Omega$$

10.8

$$I_0 = nI_{C1}$$

$$I_{REF} = I_{C1} + I_{B1} + I_{B2} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_0}{\beta}$$

$$I_{REF} = I_{C1} \left( 1 + \frac{1}{\beta} + \frac{n}{\beta} \right) = I_{C1} \left( 1 + \frac{1+n}{\beta} \right)$$

$$= \frac{I_0}{n} \left( 1 + \frac{1+n}{\beta} \right)$$

$$\text{or } I_0 = \frac{nI_{REF}}{\left( 1 + \frac{1+n}{\beta} \right)}$$

10.9

Using the results of Problem 10-8,

$$2 = \frac{2I_{REF}}{1 + \frac{3}{50}} \Rightarrow I_{REF} = 1.06 \text{ mA}$$

$$R_1 = \frac{5 - 0.7}{1.06} \Rightarrow R_1 = 4.06 \text{ k}\Omega$$

10.10

First approximation - BE area of  $Q_2$  is 3 times that of  $Q_1$ .

$$R_1 \approx \frac{5 - 0.7 - (-5)}{0.5} \Rightarrow R_1 = 18.6 \text{ k}\Omega$$

Second approximation - take into account  $I_C$  vs  $V_{BE}$  variation.For  $Q_1$ :

$$\frac{I_{C1}}{I_{C2}} = \exp\left(\frac{V_{BE1} - V_{BE2}}{V_T}\right)$$

or

$$V_{BE1} - V_{BE2} = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

$$0.7 - V_{BE2} = 0.026 \ln\left(\frac{1}{0.5}\right) = V_{BE} = 0.682 \text{ V for}$$

$$I_C = 0.5 \text{ mA}$$

Then

$$R_1 = \frac{5 - 0.682 - (-5)}{0.5} \Rightarrow R_1 = 18.64 \text{ k}\Omega$$

Now

$$I_{S1} = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{1 \times 10^{-3}}{\exp\left(\frac{0.7}{0.026}\right)} \Rightarrow I_{S1} = 2.03 \times 10^{-15} \text{ A}$$

For  $Q_2$ :

$$I_{S2} = \frac{I_{C2}}{\exp\left(\frac{V_{BE2}}{V_T}\right)} = \frac{1.5 \times 10^{-3}}{\exp\left(\frac{0.682}{0.026}\right)} = 6.09 \times 10^{-15} \text{ A}$$

10.11

$$I_2 = 2I_1 \text{ and } I_3 = 3I_1$$

$$(a) \quad I_2 = 1.0 \text{ mA}, I_3 = 1.5 \text{ mA}$$

$$(b) \quad I_1 = 0.25 \text{ mA}, I_3 = 0.75 \text{ mA}$$

$$(c) \quad I_1 = 0.167 \text{ mA}, I_2 = 0.333 \text{ mA}$$

10.12

$$a. \quad I_0 = I_{C1} \text{ and } I_{REF} = I_{C1} + I_{B3} = I_{C1} + \frac{I_{E3}}{1 + \beta}$$

$$I_{E3} = I_{B1} + I_{B2} + \frac{V_{BE}}{R_2} = \frac{2I_{C1}}{\beta} + \frac{V_{BE}}{R_2}$$

$$I_{REF} = I_{C1} + \frac{2I_{C1}}{\beta(1 + \beta)} + \frac{V_{BE}}{(1 + \beta)R_2}$$

$$I_{REF} - \frac{V_{BE}}{(1 + \beta)R_2} = I_0 \left( 1 + \frac{2}{\beta(1 + \beta)} \right)$$

$$I_0 = \frac{I_{REF} - \frac{V_{BE}}{(1 + \beta)R_2}}{\left( 1 + \frac{2}{\beta(1 + \beta)} \right)}$$

$$b. \quad I_{REF} = (0.70) \left( 1 + \frac{2}{(80)(81)} \right) + \frac{0.7}{(81)(10)}$$

$$I_{REF} = 0.700216 + 0.000864$$

$$I_{REF} = 0.7011 \text{ mA} = \frac{10 - 2(0.7)}{R_1}$$

$$\Rightarrow R_1 = 12.27 \text{ k}\Omega$$

10.13

$$a. \quad I_{0i} = I_{CR} \text{ and } I_{REF} = I_{CR} + I_{BS} = I_{CR} + \frac{I_{ES}}{1 + \beta}$$

$$I_{ES} = I_{BR} + I_{B1} + I_{B2} + \dots + I_{BN} = (1 + N)I_{BR}$$

$$= \frac{(1 + N)I_{CR}}{\beta}$$

$$\text{Then } I_{REF} = I_{CR} + \frac{(1 + N)I_{CR}}{\beta(1 + \beta)}$$

$$\text{or } I_{0i} = \frac{I_{REF}}{\left( 1 + \frac{(1 + N)}{\beta(1 + \beta)} \right)}$$


$$b. \quad I_{REF} = (0.5) \left[ 1 + \frac{6}{(50)(51)} \right] = 0.5012 \text{ mA}$$

$$R_1 = \frac{5 - 2(0.7) - (-5)}{0.5012}$$

$$\Rightarrow R_1 = 17.16 \text{ k}\Omega$$



10.14

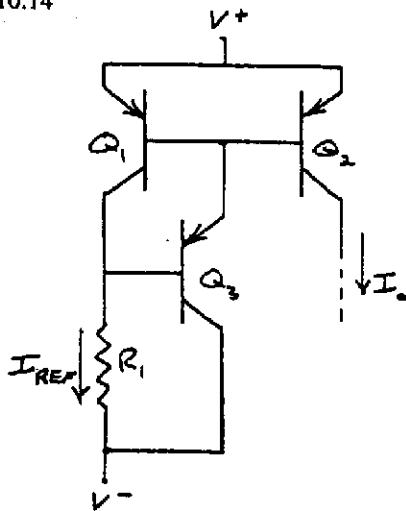


$$I_{REF} = I_0 \left( 1 + \frac{2}{\beta(1+\beta)} \right) = (0.5) \left[ 1 + \frac{2}{(50)(51)} \right]$$

$$\Rightarrow I_{REF} = 0.5004 \text{ mA}$$

$$R_1 = \frac{5 - 2(0.7) - (-5)}{0.5004} \Rightarrow R_1 = 17.19 \text{ k}\Omega$$

10.15

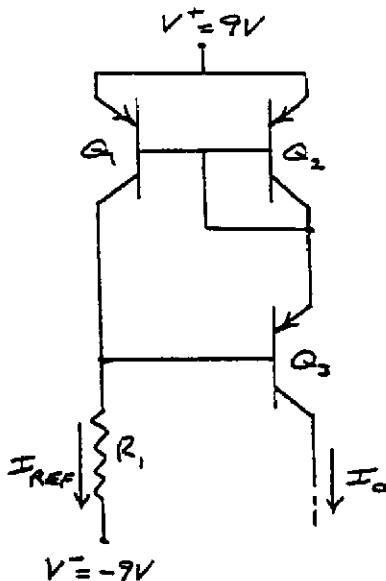

$$I_0 = I_{REF} \cdot \frac{1}{\left( 1 + \frac{2}{\beta(2+\beta)} \right)}$$

For  $I_0 = 0.8 \text{ mA}$

$$I_{REF} = (0.8) \left( 1 + \frac{2}{25(27)} \right)$$

$$\Rightarrow I_{REF} = 0.8024 \text{ mA}$$

$$R_1 = \frac{18 - 2(0.7)}{0.8024} \Rightarrow R_1 = 20.69 \text{ k}\Omega$$

10.16

The analysis is exactly the same as in the text. We have

$$I_0 = I_{REF} \cdot \frac{1}{\left( 1 + \frac{2}{\beta(2+\beta)} \right)}$$

10.17

$$I_0 = 2 \text{ mA}, I_{B2} = \frac{2}{75} = 0.0267 \text{ mA}$$

$$I_{C1} = 1 \text{ mA}, I_{B1} = \frac{1}{75} = 0.0133 \text{ mA}$$

$$I_{E3} = I_{B1} + I_{B2} = 0.0133 + 0.0267 = 0.04 \text{ mA}$$

$$I_{B3} = \frac{I_{E3}}{1+\beta} = \frac{0.04}{76} = 0.000526 \text{ mA}$$

$$I_{REF} = I_{C1} + I_{B3} \Rightarrow I_{REF} = 1.000526 \approx 1 \text{ mA}$$

$$R_1 = \frac{10 - 2(0.7)}{I_{REF}} = \frac{8.6}{1} \Rightarrow R_1 = 8.6 \text{ k}\Omega$$

10.18

a. We have

$$R_0 \approx \frac{\beta r_{o3}}{2}$$

$$r_{o3} = \frac{V_A}{I_0} \approx \frac{V_A}{I_{REF}} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

Then

$$R_0 \approx \frac{(80)(160)}{2} \Rightarrow R_0 \approx 5.4 \text{ M}\Omega$$

$$b. \Delta I_0 = \frac{1}{R_0} \cdot \Delta V_C = \frac{5}{6.4} \Rightarrow \Delta I_0 = 0.781 \mu\text{A}$$

10.19

$$V_{BE} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

$$\text{At } 2 \text{ mA}, V_{BE} = (0.026) \ln \left( \frac{2 \times 10^{-3}}{2.03 \times 10^{-15}} \right)$$

$$= 0.718 \text{ V}$$

$$R_1 = \frac{15 - 0.718}{2} \Rightarrow R_1 = 7.14 \text{ k}\Omega$$

$$R_E = \frac{V_T}{I_0} \ln \left( \frac{I_{REF}}{I_0} \right) = \frac{0.026}{0.050} \cdot \ln \left( \frac{2}{0.050} \right)$$

$$\Rightarrow R_E = 1.92 \text{ k}\Omega$$

10.20

$$a. \quad I_{REF} \approx \frac{10 - 0.7}{20} = 0.465 \text{ mA}$$

$$\text{Let } V^- = 0$$

$$V_{BE} \approx V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

Then

$$V_{BE} \approx (0.026) \ln \left( \frac{0.465 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.680 \text{ V}$$

Then

$$I_{REF} \approx \frac{10 - 0.680}{20} \Rightarrow I_{REF} = 0.466 \text{ mA}$$

$$b. \quad R_E = \frac{V_T}{I_O} \ln \left( \frac{I_{REF}}{I_O} \right) = \frac{0.026}{0.10} \cdot \ln \left( \frac{0.466}{0.10} \right)$$

$$\Rightarrow R_E = 400 \Omega$$

10.21

$$(a) \quad I_{REF} = \frac{V^+ - V_{BE1} - V^-}{R_1} = \frac{5 - 0.7 - (-5)}{100} \Rightarrow$$

$$I_{REF} = 93 \mu\text{A}$$

$$I_O R_E = V_T \ln \left( \frac{I_{REF}}{I_O} \right) \Rightarrow I_O(10) = 0.026 \ln \left( \frac{93 \times 10^{-3} \text{ mA}}{I_O} \right)$$

$$\text{By trial and error, } I_O \approx 6.8 \mu\text{A}$$

$$R_o = r_{o2}(1 + g_{m2} R'_E)$$

Now

$$r_{o2} = \frac{30}{6.8} = 4.41 \text{ M}\Omega$$

$$g_{m2} = \frac{0.0068}{0.026} = 0.262 \text{ mA/V}$$

$$r_{\pi2} = \frac{(100)(0.026)}{0.0068} = 382 \text{ k}\Omega$$

So

$$R'_E = r_{\pi2} \| R_E = 382 \| 10 = 9.74 \text{ k}\Omega$$

Then

$$R_o = 4.41 [1 + (0.262)(9.74)] \Rightarrow R_o = 15.7 \text{ M}\Omega$$

$$(d) \quad V_{BE1} - V_{BE2} = I_O R_E = (0.0068)(10) \Rightarrow$$

$$V_{BE1} - V_{BE2} = 0.068 \text{ V}$$

10.22

$$\Delta I_O = \frac{1}{R_o} \cdot \Delta V_C$$

$$R_o = r_{o2}(1 + g_{m2} R'_E)$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{80}{17.4} = 4.6 \text{ M}\Omega$$

$$g_{m2} = \frac{I_O}{V_T} = \frac{0.0174}{0.026} = 0.669 \text{ mA/V}$$

$$r_{\pi2} = \frac{(80)(0.026)}{0.0174} = 119.5 \text{ k}\Omega$$

$$R'_E = R_E \| r_{\pi2} = 7 \| 119.5$$

$$R'_E = 6.61 \text{ k}\Omega$$

$$R_o = (4.6)[1 + (0.669)(6.61)] \Rightarrow R_o = 24.9 \text{ M}\Omega$$

Now

$$\Delta I_O = \left( \frac{1}{24.9} \right) (5) \Rightarrow \Delta I_O = 0.0201 \mu\text{A}$$

10.23

$$R_o = r_{o2}(1 + g_{m2} R'_E) \text{ where } R'_E = R_E \| r_{\pi2}$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{75}{25} = 3 \text{ M}\Omega$$

$$g_{m2} = \frac{I_O}{V_T} = \frac{0.025}{0.026} = 0.962 \text{ mA/V}$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(80)(0.026)}{0.025} = 83.2 \text{ k}\Omega$$

$$R_E = \frac{V_T}{I_O} \ln \left( \frac{I_{REF}}{I_O} \right) = \frac{0.026}{0.025} \cdot \ln \left( \frac{0.75}{0.025} \right) = 3.54 \text{ k}\Omega$$

$$R'_E = 3.54 \| 83.2 = 3.40 \text{ k}\Omega$$

$$R_o = 3[1 + (0.962)(3.4)] = 12.8 \text{ M}\Omega$$

$$\Delta I_O = \frac{1}{R_o} \cdot \Delta V_{C2} = \frac{3}{12.8} = 0.234 \mu\text{A}$$

So

$$\frac{\Delta I_O}{I_O} = \frac{0.234}{25} \Rightarrow 0.936\%$$

10.24

$$\text{Let } R_1 = 5 \text{ k}\Omega, \text{ Then}$$

$$I_{REF} = \frac{12 - 0.7 - (-12)}{5} \Rightarrow I_{REF} = 4.66 \text{ mA}$$

Now

$$I_O R_E = V_T \ln \left( \frac{I_{REF}}{I_O} \right) \Rightarrow$$

$$R_E = \frac{0.026}{0.10} \ln \left( \frac{4.66}{0.10} \right) \Rightarrow R_E \approx 1 \text{ k}\Omega$$

10.25

$$I_{REF} \approx \frac{10 - 0.7 - (-10)}{40} = 0.4825 \text{ mA}$$

$$V_{BE} \approx V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

Now

$$V_{BE} = (0.026) \ln \left( \frac{0.4825 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.681 \text{ V}$$

$$V_{BE1} = 0.681 \text{ V}$$

So

$$I_{REF} \approx \frac{10 - 0.681 - (-10)}{40}$$

$$\Rightarrow I_{REF} = 0.483 \text{ mA}$$

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$I_0(12) = (0.026) \ln \left( \frac{0.483}{I_0} \right)$$

By trial and error,

$$\Rightarrow I_0 \approx 8.7 \mu\text{A}$$

$$V_{BE2} = V_{BE1} - I_0 R_E = 0.681 - (0.0087)(12)$$

$$\Rightarrow V_{BE2} = 0.5766 \text{ V}$$

10.26

$$V_{BE1} + I_{REF} R_{E1} = V_{BE2} + I_0 R_{E2}$$

$$V_{BE1} - V_{BE2} = I_0 R_{E2} - I_{REF} R_{E1}$$

For matched transistors

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$V_{BE2} = V_T \ln \left( \frac{I_0}{I_S} \right)$$


Then

$$V_T \ln \left( \frac{I_{REF}}{I_0} \right) = I_0 R_{E2} - I_{REF} R_{E1}$$

 Output resistance looking into the collector of  $Q_2$  is increased.

10.27

a.

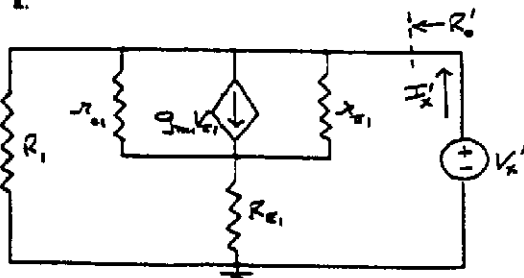

$$I_X = \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{o1}} + \frac{V_X}{R_1} \quad (1)$$

$$V_X = V_{\pi 1} + \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{o1}} \right) R_{E1} \quad (2)$$

$$V_X = V_{\pi 1} \left[ 1 + \left( \frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{o1}} \right) R_{E1} \right]$$

$$I_{REF} \approx \frac{10 - 0.7}{13.6 + 5} = 0.5 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.5} = 2.6 \text{ k}\Omega$$

$$r_{o1} = \frac{75}{0.5} = 150 \text{ k}\Omega$$

$$g_{m1} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$


$$V_X = V_{\pi 1} \left[ 1 + \left( \frac{1}{2.6} + 19.23 + \frac{1}{150} \right) (5) \right]$$

$$\Rightarrow V_{\pi 1} = V_X (0.01009)$$

$$\text{Then } I_X = V_X (0.01009) \left[ \frac{1}{2.6} + 19.23 + \frac{1}{150} \right] + \frac{V_X}{13.6}$$

$$I_X = V_X (0.1980) + V_X (0.0735)$$
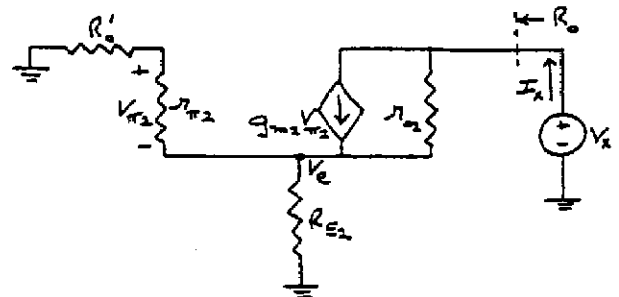
$$\Rightarrow R_o' = \frac{V_X}{I_X} = 3.683 \text{ k}\Omega$$



$$I_X = \frac{V_X - V_e}{r_{o2}} + g_{m2} V_{\pi 2}$$

$$V_e = I_X [R_{E2} \parallel (r_{\pi 2} + R_o')]$$

$$V_{\pi 2} = - \left( \frac{r_{\pi 2}}{r_{\pi 2} + R_o'} \right) V_e$$

Then

$$I_X = \frac{V_X}{r_{o2}} - \frac{I_X}{r_{o2}} [R_{E2} \parallel (r_{\pi 2} + R_o')]$$

$$- g_{m2} \left( \frac{r_{\pi 2}}{r_{\pi 2} + R_o'} \right) (I_X) [R_{E2} \parallel (r_{\pi 2} + R_o')]$$

$$R_{E1} = R_{E2} \Rightarrow I_{REF} = I_0 \Rightarrow r_{\pi 2} = 2.6 \text{ k}\Omega$$

$$r_{o2} = 150 \text{ k}\Omega$$

$$g_{m2} = 19.23 \text{ mA/V}$$

$$I_X = \frac{V_X}{150} - \frac{I_X}{150}[5\|(2.6 + 3.68)]$$

$$- (19.23)\left(\frac{2.6}{2.6 + 3.68}\right)(I_X)[5\|(2.6 + 3.68)]$$

$$I_X = V_X(0.00666) - I_X(0.01853) - I_X(22.13)$$

$$I_X(23.148) = V_X(0.00666)$$

$$\Rightarrow R_0 = \frac{V_X}{I_X} = 3.48 \text{ M}\Omega$$

b. When  $R_{E1} = R_{E2} = 0$

$$R_0 \approx r_{02} = 150 \text{ k}\Omega$$

10.28

Assume all transistors are matched.

a.

$$2V_{BE1} = V_{BE3} + I_0 R_E$$

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$V_{BE3} = V_T \ln \left( \frac{I_0}{I_S} \right)$$

$$2V_T \ln \left( \frac{I_{REF}}{I_S} \right) - V_T \ln \left( \frac{I_0}{I_S} \right) = I_0 R_E$$

$$V_T \left[ \ln \left( \frac{I_{REF}}{I_S} \right)^2 - \ln \left( \frac{I_0}{I_S} \right) \right] = I_0 R_E$$

$$V_T \ln \left( \frac{I_{REF}^2}{I_0 I_S} \right) = I_0 R_E$$

b.  $V_{BE} = 0.7 \text{ V at } 1 \text{ mA} \Rightarrow 10^{-3} = I_S \exp \left( \frac{0.7}{0.026} \right)$

$$\text{or } I_S = 2.03 \times 10^{-15} \text{ A}$$

$$V_{BE} \text{ at } 0.1 \text{ mA}$$

$$\Rightarrow V_{BE} = (0.026) \ln \left( \frac{0.1 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.640 \text{ V}$$

Since  $I_0 = I_{REF}$ , then

$$V_{BE} = I_0 R_E \Rightarrow R_E = \frac{0.640}{0.1}$$

$$\text{or } R_E = 6.4 \text{ k}\Omega$$

10.29

$$I_{REF} = \frac{10 - 0.7}{R_1} = 0.3 \Rightarrow R_1 = 18.6 \text{ k}\Omega$$

$$I_{01} R_{E2} = V_T \ln \left( \frac{I_{REF}}{I_{01}} \right)$$

$$R_{E2} = \frac{0.026}{0.010} \cdot \ln \left( \frac{0.30}{0.01} \right) \Rightarrow R_{E2} = 10.17 \text{ k}\Omega$$

$$R_{E3} = \frac{0.026}{0.030} \cdot \ln \left( \frac{0.50}{0.03} \right) \Rightarrow R_{E3} = 2.438 \text{ k}\Omega$$

$$V_{BE2} = 0.7 - I_{02} R_{E2} = 0.7 - (0.01)(10.17)$$

$$\Rightarrow V_{BE2} = 0.598 \text{ V}$$

$$V_{BE3} = 0.7 - I_{03} R_{E3} = 0.7 - (0.03)(2.438)$$

$$\Rightarrow V_{BE3} = 0.627 \text{ V}$$

10.30

$$(a) V_{BE1} = V_{BE2}$$

$$I_{REF} = \frac{V^+ - 2V_{BE1} - V^-}{R_1 + R_2}$$

Now

$$2V_{BE1} + I_{REF} R_2 = V_{BE3} + I_0 R_E$$

or

$$I_0 R_E = 2V_{BE1} - V_{BE3} + I_{REF} R_2$$

We have

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) \text{ and } V_{BE3} = V_T \ln \left( \frac{I_0}{I_S} \right)$$

$$(b) \text{ Let } R_1 = R_2 \text{ and } I_0 = I_{REF} \Rightarrow V_{BE1} = V_{BE3} \equiv V_{BE}$$

Then

$$V_{BE} = I_0 R_E - I_{REF} R_2 = I_0 (R_E - R_2)$$

so

$$I_{REF} = I_0 = \frac{V^+ - V^- - 2I_0 (R_E - R_2)}{2R_2}$$

$$= \frac{V^+ - V^-}{2R_2} - I_0 \left( \frac{R_E}{R_2} \right) + I_0$$

Then

$$I_0 = \frac{V^+ - V^-}{2R_E}$$

$$(c) \text{ Want } I_0 = 0.5 \text{ mA}$$

$$\text{So } R_E = \frac{5 - (-5)}{2(0.5)} \Rightarrow R_E = 10 \text{ k}\Omega$$

$$2R_2 = \frac{5 - 2(0.7) - (-5)}{0.5} = 17.2 \text{ k}\Omega$$

$$\text{Then } R_1 = R_2 = 8.6 \text{ k}\Omega$$

10.31

$$a. I_{REF} = \frac{20 - 0.7 - 0.7}{12} = 1.55 \text{ mA}$$

$$I_{01} = 2I_{REF} = 3.1 \text{ mA}$$

$$I_{02} = I_{REF} = 1.55 \text{ mA}$$

$$I_{03} = 3I_{REF} = 4.65 \text{ mA}$$

$$b. V_{CE1} = -I_{01} R_{C1} - (-10) = -(3.1)(2) + 10$$

$$\Rightarrow V_{CE1} = 3.8 \text{ V}$$

$$V_{EC2} = 10 - I_{02} R_{C2} = 10 - (1.55)(3)$$

$$\Rightarrow V_{EC2} = 5.35 \text{ V}$$

$$V_{EC3} = 10 - I_{03} R_{C3} = 10 - (4.65)(1)$$

$$\Rightarrow V_{EC3} = 5.35 \text{ V}$$

10.32

a. 1st approximation

$$I_{REF} \approx \frac{20 - 1.4}{8} = 2.325 \text{ mA}$$

$$\text{Now } V_{BE} - 0.7 = (0.026) \ln \left( \frac{2.32}{1} \right)$$

$$\Rightarrow V_{BE} = V_{EB} = 0.722 \text{ V}$$

Then 2nd approximation

$$I_{REF} \approx \frac{20 - 2(0.722)}{8} = 2.32 \text{ mA}$$

$$I_{O1} = 2I_{REF} = 4.64 \text{ mA}$$

$$I_{O2} = I_{REF} = 2.32 \text{ mA}$$

$$I_{O3} = 3I_{REF} = 6.96 \text{ mA}$$

b. At the edge of saturation,  $V_{CE} = V_{BE} = 0.722 \text{ V}$ 

$$R_{C1} = \frac{0 - 0.722 - (-10)}{4.64} \Rightarrow \underline{R_{C1} = 2.0 \text{ k}\Omega}$$

$$R_{C2} = \frac{10 - 0.722}{2.32} \Rightarrow \underline{R_{C2} = 4.0 \text{ k}\Omega}$$

$$R_{C3} = \frac{10 - 0.722}{6.96} \Rightarrow \underline{R_{C3} = 1.33 \text{ k}\Omega}$$

10.33

1st approximation

$$I_{REF} = \frac{10 - 0.7}{6.3 + 3} = 1 \text{ mA}$$

$$\Rightarrow V_B = 0.7 \text{ V as assumed}$$

$$V_{RE1} = I_{REF} \cdot R_{E1} = (1)(3) = 3 \text{ V}$$

$$V_{RE1} = 3 \text{ V} \Rightarrow R_{E1} = \frac{V_{RE1}}{I_{O1}} = \frac{3}{1} \Rightarrow \underline{R_{E1} = 3 \text{ k}\Omega}$$

$$V_{RE2} = 3 \text{ V} \Rightarrow R_{E2} = \frac{V_{RE2}}{I_{O2}} = \frac{3}{2} \Rightarrow \underline{R_{E2} = 1.5 \text{ k}\Omega}$$

$$V_{RE3} = 3 \text{ V} \Rightarrow R_{E3} = \frac{V_{RE3}}{I_{O3}} = \frac{3}{4} \Rightarrow \underline{R_{E3} = 0.75 \text{ k}\Omega}$$

$$I_{O1} = 1 \text{ mA}$$

$$I_{O2} = 2 \text{ mA}$$

$$I_{O3} = 4 \text{ mA}$$

10.34

$$V_{GS} = V_{TN1} + \sqrt{\frac{I_{REF}}{K_{n1}}} = 1 + \sqrt{\frac{200}{250}} = 1.89 \text{ V} = V_{DS1}$$

$$\frac{I_O}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

a.  $V_{DS2} = 2 \text{ V}$ 

$$I_O = (200) \left[ \frac{1 + (0.02)(2)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_O \approx 200 \text{ }\mu\text{A}}$$

b.  $V_{DS2} = 4 \text{ V}$ 

$$I_O = (200) \left[ \frac{1 + (0.02)(4)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_O \approx 208 \text{ }\mu\text{A}}$$

c.  $V_{DS2} = 6 \text{ V}$ 

$$I_O = (200) \left[ \frac{1 + (0.02)(6)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_O \approx 216 \text{ }\mu\text{A}}$$

10.35

$$(a) V_{GS} = V_{TN1} + \sqrt{\frac{I_{REF}}{K_{n1}}} = 1 + \sqrt{\frac{0.5}{0.5}} = 2 \text{ V}$$

$$I_O = K_{n2} \left( \sqrt{\frac{I_{REF}}{K_{n1}}} \right)^2 = K_{n2} \left( \frac{I_{REF}}{K_{n1}} \right)$$

$$I_O(\text{max}) = (0.5)(1.05) \left( \frac{0.5}{0.5} \right) \Rightarrow I_O(\text{max}) = 0.525 \text{ mA}$$

$$I_O(\text{min}) = (0.5)(0.95) \left( \frac{0.5}{0.5} \right) \Rightarrow I_O(\text{min}) = 0.475 \text{ mA}$$

So

$$0.475 \leq I_O \leq 0.525 \text{ mA}$$

$$(b) I_O = K_{n2} \left[ \sqrt{\frac{I_{REF}}{K_{n1}}} + V_{TN1} - V_{TN2} \right]^2$$

$$I_O(\text{min}) = (0.5) \left[ \sqrt{\frac{0.5}{0.5}} + 1 - 1.05 \right]^2$$

$$\Rightarrow I_O(\text{min}) = 0.451 \text{ mA}$$


$$I_O(\text{max}) = (0.5) \left[ \sqrt{\frac{0.5}{0.5}} + 1 - 0.95 \right]^2$$

$$\Rightarrow I_O(\text{max}) = 0.551 \text{ mA}$$

So

$$0.451 \leq I_O \leq 0.551 \text{ mA}$$

10.36

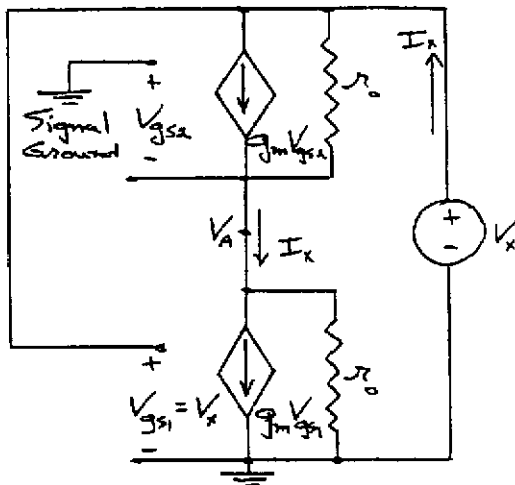

$$(1) I_x = \frac{V_x - V_A}{r_o} + g_m V_{gs2}$$

$$(2) I_x = \frac{V_A}{r_o} + g_m V_{gs1}$$

$$V_{gs1} = V_x, \quad V_{gs2} = -V_A$$

So

$$(1) I_x = \frac{V_x}{r_o} - V_A \left( \frac{1}{r_o} + g_m \right)$$

$$(2) I_x = \frac{V_A}{r_o} + g_m V_x \Rightarrow V_A = r_o [I_x - g_m V_x]$$

Then

$$I_x = \frac{V_x}{r_o} - r_o (I_x - g_m V_x) \left( \frac{1}{r_o} + g_m \right)$$

$$I_x = \frac{V_x}{r_o} - r_o \left[ \frac{I_x}{r_o} + g_m I_x - \frac{g_m}{r_o} V_x - g_m^2 V_x \right]$$

$$I_x = \frac{V_x}{r_o} - I_x - g_m r_o I_x + g_m V_x + g_m^2 r_o V_x$$

$$I_x [2 + g_m r_o] = V_x \left[ \frac{1}{r_o} + g_m + g_m^2 r_o \right]$$

$$\text{Since } g_m \gg \frac{1}{r_o}$$

$$I_x [2 + g_m r_o] \approx V_x (g_m) (1 + g_m r_o)$$

Then

$$\frac{V_x}{I_x} = R_o = \frac{2 + g_m r_o}{g_m (1 + g_m r_o)}$$

Usually,  $g_m r_o \gg 2$ , so that

$$R_o \approx \frac{1}{g_m}$$

10.37

$$(a) V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

$$\text{or } V_{GS} = V_{DS}(\text{sat}) + V_{TN} = 0.2 + 0.8 = 1.0$$

$$I_D = \frac{k'_n}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

$$50 = 48 \left( \frac{W}{L} \right) (0.2)^2 \Rightarrow \left( \frac{W}{L} \right) = 26$$

$$(b) V_{GS5} - V_{TN} = 2(V_{GS} - V_{TN})$$

$$V_{GS5} = 0.8 + 2(0.2) \Rightarrow \underline{V_{GS5} = 1.2 \text{ V}}$$

$$(c) V_{D1}(\text{min}) = 2V_{DS}(\text{sat}) = 2(0.2) \Rightarrow$$

$$\underline{V_{D1}(\text{min}) = 0.4 \text{ V}}$$

10.38

$$V_{DS2}(\text{sat}) = 2 \text{ V} = V_{GS2} - V_{TN2} = V_{GS2} - 1.5 \Rightarrow$$

$$V_{GS2} = 3.5 \text{ V}$$

$$I_O = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN2})^2$$

$$250 = (20) \left( \frac{W}{L} \right)_1 (3.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_2 = 3.125$$

$$I_{REF} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_1 (V_{GS2} - V_{TN1})$$

$$100 = (20) \left( \frac{W}{L} \right)_2 (3.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_1 = 1.25$$

$$\text{Now } V_{GS1} = 10 - V_{GS2} = 10 - 3.5 = 6.5 \text{ V}$$

$$\text{So } 100 = (20) \left( \frac{W}{L} \right)_3 (6.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_3 = 0.2$$

10.39

a. From Equation (10.50).

$$\begin{aligned} V_{GS1} = V_{GS2} &= \left( \frac{\sqrt{\frac{5}{25}}}{1 + \sqrt{\frac{5}{25}}} \right) (5) + \left( \frac{1 - \sqrt{\frac{5}{25}}}{1 + \sqrt{\frac{5}{25}}} \right) (0.5) \\ &= \left( \frac{0.447}{1 + 0.447} \right) (5) + \left( \frac{1 - 0.447}{1 + 0.447} \right) (0.5) \end{aligned}$$

$$\underline{V_{GS1} = V_{GS2} = 1.74 \text{ V}}$$

$$I_{REF} \equiv K_{n1}(V_{GS1} - V_{TN})^2 = (18)(25)(1.74 - 0.5)^2 \Rightarrow I_{REF} = 0.692 \text{ mA}$$

$$\begin{aligned} \text{b. } I_O &= \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2}) \\ I_O &= (18)(15)(1.74 - 0.5)^2 [1 + (0.02)(2)] \\ &= (415)(104) \Rightarrow I_O = 0.432 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{c. } I_O &= (415)[1 + (0.02)(4)] \\ &\Rightarrow I_O = 0.448 \text{ mA} \end{aligned}$$

10.40

$$\begin{aligned} \text{(a) } I_{REF} &= \left( \frac{k'_p}{2} \right) \left( \frac{W}{L} \right)_1 (V_{SG1} + V_{TP})^2 \\ &= \left( \frac{k'_p}{2} \right) \left( \frac{W}{L} \right)_3 (V_{SG3} + V_{TP})^2 \end{aligned}$$

$$\text{But } V_{SG3} = 3 - V_{SG1}$$

So

$$25(V_{SG1} - 0.4)^2 = 5(3 - V_{SG1} - 0.4)^2$$

which yields  $V_{SG1} = 1.08 \text{ V}$  and  $V_{SG3} = 1.92 \text{ V}$

$$I_{REF} = 20(25)(1.08 - 0.4)^2 \Rightarrow I_{REF} = 231 \mu\text{A}$$

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1} = \frac{15}{25} = 0.6$$

$$\text{Then } I_O = (0.6)(231) = 139 \mu\text{A}$$

$$\text{(b) } V_{DS2}(\text{sat}) = 1.08 - 0.4 = 0.68 \text{ V}$$

$$V_R = 3 - 0.68 = 2.32 = I_O R$$

then

$$R = \frac{2.32}{0.139} \Rightarrow R = 16.7 \text{ k}\Omega$$

10.41

$$V_{SD2}(\text{sat}) = 0.25 = V_{SG} + V_{TP} = V_{SG} - 0.4 \Rightarrow V_{SG2} = 0.65 \text{ V}$$

$$I_O = \frac{k'_p}{2} \left( \frac{W}{L} \right)_2 (V_{SG2} + V_{TP})^2$$

$$25 = \frac{40}{2} \left( \frac{W}{L} \right)_2 (0.65 - 0.4)^2 \Rightarrow \left( \frac{W}{L} \right)_2 = 20$$

$$I_{REF} = 75 \mu\text{A} = \frac{(W/L)_1}{(W/L)_2} \cdot I_O \Rightarrow \left( \frac{W}{L} \right)_1 = 60$$

$$I_{REF} = \frac{k'_p}{2} \left( \frac{W}{L} \right)_3 (V_{SG3} + V_{TP})^2$$

$$V_{SG3} = 3 - 0.65 = 2.35 \text{ V}$$

Then

$$75 = \frac{40}{2} \left( \frac{W}{L} \right)_3 (2.35 - 0.4)^2 \Rightarrow \left( \frac{W}{L} \right)_3 = 0.986$$

10.42

$$\text{a. } I_{REF} = K_n(V_{GS} - V_{TN})^2$$

$$100 = 100(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3 \text{ V}$$

$$\text{For } V_{D4} = -3 \text{ V, } I_O \approx 100 \mu\text{A}$$

$$\text{b. } R_O = r_{o4} + r_{o2}(1 + g_m r_{o4})$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$


$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.1)(3 - 2) = 0.2 \text{ mA/V}$$

$$R_O = 500 + 500[1 + (0.2)(500)]$$

$$R_O = 51 \text{ M}\Omega$$

$$\Delta I_O = \frac{1}{R_O} \cdot \Delta V_{D4} = \frac{6}{51} \Rightarrow \Delta I_O = 0.118 \mu\text{A}$$

10.43

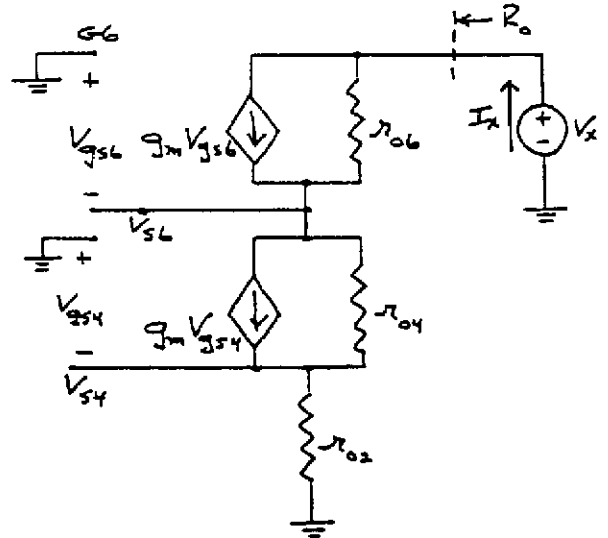

$$V_{gs4} = -I_X r_{o2}$$

$$V_{S6} = (I_X - g_m V_{gs4}) r_{o4} + I_X r_{o2}$$

$$= (I_X + g_m I_X r_{o2}) r_{o4} + I_X r_{o2}$$

$$V_{S6} = I_X [r_{o2} + (1 + g_m r_{o2}) r_{o4}] = -V_{gs6}$$

$$I_X = g_m V_{gs6} + \frac{V_X - V_{S6}}{r_{o6}} = \frac{V_X}{r_{o6}} - V_{S6} \left( g_m + \frac{1}{r_{o6}} \right)$$

$$I_X = \frac{V_X}{r_{o6}} - I_X \left( g_m + \frac{1}{r_{o6}} \right) [r_{o2} + (1 + g_m r_{o2}) r_{o4}]$$

$$I_X \left\{ 1 + \left( g_m + \frac{1}{r_{o6}} \right) [r_{o2} + (1 + g_m r_{o2}) r_{o4}] \right\} = \frac{V_X}{r_{o6}}$$

$$\frac{V_X}{I_X} = R_O = r_{o6} + (1 + g_m r_{o6}) [r_{o2} + (1 + g_m r_{o2}) r_{o4}]$$

$$I_O \approx I_{REF} = 0.2 \text{ mA} = 0.2(V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.2)(2 - 1) = 0.4 \text{ mA/V}$$

$$r_{o3} = r_{o4} = r_{o6} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.2)} = 250 \text{ k}\Omega$$

$$R_0 = 250 + [1 + (0.4)(250)] \\ \times \{250 + [1 + (0.4)(250)](250)\}$$

$$R_0 = 2575750 \text{ k}\Omega$$

$$\Rightarrow R_0 = 2.58 \times 10^9 \Omega$$

10.44

$$\frac{k'_n \left(\frac{W}{L}\right)_1}{2} (V_{GS1} - V_{TN})^2 = \frac{k'_n \left(\frac{W}{L}\right)_3}{2} (V_{GS3} - V_{TN})^2 \\ = \frac{k'_p \left(\frac{W}{L}\right)_4}{2} (V_{SG4} + V_{TP})^2$$

$$(1) 50(20)(V_{GS1} - 0.5)^2 = 50(5)(V_{GS3} - 0.5)^2$$

$$(2) 50(20)(V_{GS1} - 0.5)^2 = 20(10)(V_{SG4} - 0.5)^2$$

$$(3) V_{SG4} + V_{GS3} + V_{GS1} = 6$$

$$\text{From (1)} 4(V_{GS1} - 0.5)^2 = (V_{GS3} - 0.5)^2 \Rightarrow$$

$$V_{GS3} = 2(V_{GS1} - 0.5) + 0.5$$

$$\text{From (2)} 5(V_{GS1} - 0.5)^2 = (V_{SG4} - 0.5)^2 \Rightarrow$$

$$V_{SG4} = \sqrt{5}(V_{GS1} - 0.5) + 0.5$$

Then (3) becomes

$$\sqrt{5}(V_{GS1} - 0.5) + 0.5 + 2(V_{GS1} - 0.5) + 0.5 + V_{GS1} = 6$$

which yields  $V_{GS1} = 1.36 \text{ V}$  and

$$V_{GS3} = 2.22 \text{ V}, \quad V_{SG4} = 2.42 \text{ V}$$

Then

$$I_{REF} = \frac{k'_n \left(\frac{W}{L}\right)_1}{2} (V_{GS1} - V_{TN})^2 = 50(20)(1.36 - 0.5)^2$$

$$\text{or } I_{REF} = I_O = 0.740 \text{ mA}$$

$$V_{GS1} = V_{GS2} = 1.36 \text{ V}$$

$$V_{DS2}(\text{sat}) = V_{GS2} - V_{TN} = 1.36 - 0.5 \Rightarrow$$

$$V_{DS2}(\text{sat}) = 0.86 \text{ V}$$

10.45

$$V_{DS2}(\text{sat}) = 0.5 \text{ V} = V_{GS2} - V_{TN} = V_{GS2} - 0.5 \Rightarrow$$

$$V_{GS2} = 1 \text{ V}$$

$$I_O = 50 \mu\text{A} = \frac{k'_n \left(\frac{W}{L}\right)_2}{2} (V_{GS2} - V_{TN})^2$$

$$= 50 \left(\frac{W}{L}\right)_2 (1 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_2 = 4$$

$$V_{GS1} = V_{GS2} = 1 \text{ V} \Rightarrow$$

$$I_{REF} = 150 = \frac{k'_n \left(\frac{W}{L}\right)_1}{2} (V_{GS1} - V_{TN})^2$$

$$= 50 \left(\frac{W}{L}\right)_1 (1 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_1 = 12$$

$$V_{GS3} + V_{SG4} + V_{GS1} = 6$$

$$2V_{GS3} = 6 - 1 = 5 \text{ V} \Rightarrow V_{GS3} = 2.5 \text{ V}$$

$$I_{REF} = 150 = 50 \left(\frac{W}{L}\right)_3 (2.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_3 = 0.75$$

$$I_{REF} = \frac{k'_p \left(\frac{W}{L}\right)_4}{2} (V_{SG4} + V_{TP})^2$$

$$150 = 20 \left(\frac{W}{L}\right)_4 (2.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_4 = 1.88$$

10.46

a. As a first approximation

$$I_{REF} = 80 = 80(V_{GS1} - 1)^2 \Rightarrow V_{GS1} = 2 \text{ V}$$

$$\text{Then } V_{DS1} \approx 2(2) = 4 \text{ V}$$

The second approximation

$$80 = 80(V_{GS1} - 1)^2 [1 + (0.02)(4)]$$

$$\text{Or } \frac{80}{86.4} = (V_{GS1} - 1)^2 \Rightarrow V_{GS1} = 1.962$$

Then

$$I_O = K_n(V_{GS1} - V_{TN})^2 (1 + \lambda_n V_{GS1})$$

$$= 80(1.962 - 1)^2 [1 + (0.02)(1.962)]$$

$$\text{Or } I_O = 76.94 \mu\text{A}$$

b. From a PSpice analysis,  $I_O = 77.09 \mu\text{A}$  for  $V_{D3} = -1 \text{ V}$  and  $I_O = 77.14 \mu\text{A}$  for  $V_{D3} = 3 \text{ V}$ . The change is  $\Delta I_O \approx 0.05 \mu\text{A}$  or 0.065%.

10.47

a. For a first approximation,

$$I_{REF} = 80 = 80(V_{GS4} - 1)^2 \Rightarrow V_{GS4} = 2 \text{ V}$$

As a second approximation

$$I_{REF} = 80 = 80(V_{GS4} - 1)^2 [1 + (0.02)(2)]$$

$$\text{Or } V_{GS4} = 1.98 \text{ V} = V_{GS1}$$

$$I_O = K_n(V_{GS2} - V_{TN})^2 (1 + \lambda V_{GS2})$$

To a very good approximation

$$I_O = 80 \mu\text{A}$$

b. From a PSpice analysis,  $I_O = 80.00 \mu\text{A}$  for  $V_{D3} = -1 \text{ V}$  and the output resistance is  $R_O = 76.9 \text{ M}\Omega$ . Then

$$\Delta I_O = \frac{1}{R_O} \cdot V_{D3} = \frac{4}{76.9} = 0.052 \mu\text{A}$$

or a change of 0.065%.



10.48

$$(a) K_{n1} = \frac{k'_n}{2} \left( \frac{W}{L} \right)_1 = 50(5) = 250 \mu\text{A}/\text{V}^2$$

$$R = \frac{1}{\sqrt{K_{n1} I_{D1}}} \left( 1 - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \right)$$

$$= \frac{1}{\sqrt{(0.25)(0.05)}} \left( 1 - \sqrt{\frac{5}{50}} \right) = (8.94)(0.684)$$

$$R = 6.11 \text{ k}\Omega$$

$$(b) V^+ - V^- = V_{SD3}(\text{sat}) + V_{GS1}$$

$$V_{SD3}(\text{sat}) = V_{SG3} + V_{TP}$$

$$I_{D1} = 50 = 20(5)(V_{SG3} - 0.5)^2 \Rightarrow V_{SG3} = 1.21 \text{ V}$$

Then

$$V_{SD3}(\text{sat}) = 1.21 - 0.5 = 0.71 \text{ V}$$

Also

$$I_{D1} = 50 = 50(5)(V_{GS1} - 0.5)^2 \Rightarrow V_{GS1} = 0.947 \text{ V}$$

Then

$$(V^+ - V^-)_{\min} = 0.71 + 0.947 = 1.66 \text{ V}$$

$$(c) I_{O1} = 25 = 50 \left( \frac{W}{L} \right)_5 (0.947 - 0.5)^2 \Rightarrow \left( \frac{W}{L} \right)_5 = 2.5$$

$$I_{O2} = 75 = 20 \left( \frac{W}{L} \right)_6 (1.21 - 0.5)^2 \Rightarrow \left( \frac{W}{L} \right)_6 = 7.44$$

10.49

$$V_{GS3} = \frac{1}{3}(5) = 1.667 \text{ V}$$

$$I_{REF} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$100 = (20) \left( \frac{W}{L} \right)_3 (1.667 - 1)^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_3 = \left( \frac{W}{L} \right)_4 = \left( \frac{W}{L} \right)_5 = 11.2$$

$$I_{O1} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_1 (V_{GS3} - V_{TN})^2$$

$$\text{Or } \frac{I_{REF}}{I_{O1}} = \frac{\left( \frac{W}{L} \right)_3}{\left( \frac{W}{L} \right)_1}$$

$$\left( \frac{W}{L} \right)_1 = \left( \frac{I_{O1}}{I_{REF}} \right) \left( \frac{W}{L} \right)_3 = \left( \frac{0.2}{0.1} \right) (11.2)$$

$$\Rightarrow \left( \frac{W}{L} \right)_1 = 22.4$$

$$\text{And } \left( \frac{W}{L} \right)_2 = \left( \frac{I_{O2}}{I_{REF}} \right) \left( \frac{W}{L} \right)_3 = \left( \frac{0.3}{0.1} \right) (11.2)$$

$$\Rightarrow \left( \frac{W}{L} \right)_2 = 33.6$$

10.50

$$I_{REF} = \frac{24 - V_{SGP} - V_{GSN}}{R}$$

Also

$$I_{REF} = 40(1)(V_{GSN} - 1.2)^2$$

$$I_{REF} = 18(1)(V_{SGP} - 1.2)^2$$

Then

$$\sqrt{40}(V_{GSN} - 1.2) = \sqrt{18}(V_{SGP} - 1.2)$$

which yields

$$V_{SGP} = \frac{6.325}{4.243}(V_{GSN} - 1.2) + 1.2$$

Then

$$\left[ 0.040(V_{GSN} - 1.2)^2 \right] \cdot R = 24 - V_{GSN} - 1.49(V_{GSN} - 1.2) - 1.2$$

which yields

$$V_{GSN} = 2.69 \text{ V and } V_{SGP} = 3.42 \text{ V}$$

Now

$$I_{REF} = \frac{24 - 3.42 - 2.69}{200} \Rightarrow I_{REF} = 89.5 \mu\text{A}$$

$$I_1 = \frac{89.5}{5} = 17.9 \mu\text{A}$$

$$I_2 = (1.25)(89.5) = 112 \mu\text{A}$$

$$I_3 = (0.8)(89.5) = 71.6 \mu\text{A}$$

$$I_4 = 4(89.5) = 358 \mu\text{A}$$

10.51

$$\text{We have } V_{GSN} = 2.69 \text{ V and } V_{SGP} = 3.42 \text{ V}$$

So

$$I_{REF} = \frac{10 - 2.69 - 3.42}{R} = \frac{3.89}{200} \Rightarrow I_{REF} = 19.45 \mu\text{A}$$

Then

$$I_1 = (0.2)(19.45) = 3.89 \mu\text{A}$$

$$I_2 = (1.25)(19.45) = 24.3 \mu\text{A}$$

$$I_3 = (0.8)(19.45) = 15.56 \mu\text{A}$$

$$I_4 = 4(19.45) = 77.8 \mu\text{A}$$

10.52

$$\text{For } v_{GS} = 0, i_D = I_{DSS}(1 + \lambda v_{DS})$$

$$a. V_D = -5 \text{ V, } v_{DS} = 5$$

$$i_D = (2)[1 + (0.05)(5)]$$

$$\Rightarrow i_D = 2.5 \text{ mA}$$

$$b. V_D = 0, v_{DS} = 10$$

$$i_D = (2)[1 + (0.05)(10)]$$

$$\Rightarrow i_D = 3 \text{ mA}$$

$$c. V_D = 5 \text{ V, } v_{DS} = 15 \text{ V}$$

$$i_D = (2)[1 + (0.05)(15)]$$

$$\Rightarrow i_D = 3.5 \text{ mA}$$

10.54

$$I_0 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2 = 4 \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{V_{GS}}{V_P} = 1 - \sqrt{\frac{2}{4}} = 0.293$$

$$\text{So } V_{GS} = (0.293)(-4) = -1.17 \text{ V}$$

$$\text{Then } I_0 = \frac{V_S}{R} \text{ and } V_S = -V_{GS}$$

$$R = \frac{-V_{GS}}{I_0} = \frac{-(-1.17)}{2} \Rightarrow R = 0.585 \text{ k}\Omega$$

10.55

$$\text{a. } I_{REF} = I_{S1} \exp\left(\frac{V_{EB1}}{V_T}\right)$$

$$\text{or } V_{EB1} = V_T \ln\left(\frac{I_{REF}}{I_{S1}}\right) = (0.026) \ln\left(\frac{1 \times 10^{-3}}{5 \times 10^{-13}}\right)$$

$$\Rightarrow V_{EB1} = 0.5568$$

$$\text{b. } R_1 = \frac{5 - 0.5568}{1} \Rightarrow R_1 = 4.44 \text{ k}\Omega$$

$$\text{c. From Equation (10.72) and letting } V_{CE0} = V_{EC2} = 2.5 \text{ V}$$

$$10^{-12} \exp\left(\frac{V_I}{V_T}\right) \left[1 + \frac{2.5}{120}\right] = 10^{-3} \left[\frac{1 + \frac{2.5}{80}}{1 + \frac{0.5568}{80}}\right]$$

$$1.0208 \times 10^{-12} \exp\left(\frac{V_I}{V_T}\right) = (10^{-3}) \left(\frac{1.03125}{1.00696}\right)$$

Then

$$V_I = 0.026 \ln(1.003613 \times 10^9)$$

$$\text{So } V_I = 0.5389 \text{ V}$$

$$\text{d. } A_v = \frac{-(1/V_T)}{(1/V_{AN}) + (1/V_{AP})}$$

$$A_v = \frac{-\frac{1}{0.026}}{\frac{1}{120} + \frac{1}{80}} = \frac{-38.46}{0.00833 + 0.0125}$$

$$A_v = -1846$$

10.56

$$\text{a. } V_{BE} = V_T \ln\left(\frac{I_{REF}}{I_{S1}}\right) = (0.026) \ln\left(\frac{0.5 \times 10^{-3}}{10^{-12}}\right)$$

$$\Rightarrow V_{BE} = 0.5208$$

$$\text{b. } R_1 = \frac{5 - 0.5208}{0.5} \Rightarrow R_1 = 8.96 \text{ k}\Omega$$

c. From Equation (10.72) applies with slight modifications

$$I_{S0} \exp\left(\frac{V_{EB0}}{V_T}\right) \left[1 + \frac{V_{EC0}}{V_{AP}}\right] = I_{REF} \cdot \left(\frac{1 + \frac{V_{CE2}}{V_{AN}}}{1 + \frac{V_{BE2}}{V_{AN}}}\right)$$

$$(5 \times 10^{-13}) \left[\exp\left(\frac{V_{EB0}}{V_T}\right)\right] \left(1 + \frac{2.5}{80}\right)$$

$$= (0.5 \times 10^{-3}) \cdot \left(\frac{1 + \frac{2.5}{120}}{1 + \frac{0.5208}{120}}\right)$$

$$5.15625 \times 10^{-13} \exp\left(\frac{V_{EB0}}{V_T}\right) = (0.5 \times 10^{-3}) \cdot \frac{1.02083}{1.00434}$$

$$V_{EB0} = 0.5384 \Rightarrow V_I = 5 - 0.5384$$

$$\Rightarrow V_I = 4.462 \text{ V}$$

$$\text{d. } A_v = \frac{-(1/V_T)}{(1/V_{AN}) + (1/V_{AP})}$$

$$A_v = \frac{-\frac{1}{0.026}}{\frac{1}{120} + \frac{1}{80}} = \frac{-38.46}{0.00833 + 0.0125}$$

$$A_v = -1846$$

10.57

Ignore  $(W/L)_3 = 5$  specificationa.  $M_1$  and  $M_2$  matched, so we must have

$$V_{SD2} = V_{SG} = V_{SG3} = V_{DS0} = 2.5 \text{ V}$$

For  $M_1$  and  $M_3$ :

$$I_{REF} = \left(\frac{1}{2} \mu_n C_{ox}\right) \left(\frac{W}{L}\right)_1 (V_{SG} + V_{TP})^2 (1 + \lambda_p V_{SD})$$

$$100 = 10 \left(\frac{W}{L}\right)_1 (2.5 - 1)^2 [1 + (0.02)(2.5)]$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 4.23 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_2$$

For  $M_0$ :

$$I_O = \left(\frac{1}{2} \mu_n C_{ox}\right) \left(\frac{W}{L}\right)_0 (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$100 = 20 \left(\frac{W}{L}\right)_0 (2 - 1)^2 [1 + (0.02)(2.5)]$$

$$\Rightarrow \left(\frac{W}{L}\right)_0 = 4.76$$

$$b. \quad r_{on} = r_{op} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_O} = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)_n I_O}$$

$$= 2\sqrt{(0.02)(4.76)(0.1)}$$

$$g_m = 0.195 \text{ mA/V}$$

$$A_v = -g_m(r_{on} \| r_{op}) = -(0.195)(500 \| 500)$$

$$\Rightarrow A_v = -48.75$$

10.58

$$a. \quad I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$100 = 100(V_{SG} - 1)^2 \Rightarrow V_{SG} = 2 \text{ V}$$

$$b. \quad V_{DS0} = V_{DS2} = 5 \text{ V}$$

From Equation (10.87)

$$100(V_T - 1)^2 = 100[1 + (0.02)(5)]$$

$$\times [1 - (0.02)(2)][1 - (0.02)(5)]$$

$$(V_T - 1)^2 = (1.1)(0.96)(0.90) = 0.9504$$

$$\Rightarrow V_T = 1.975 \text{ V}$$

$$c. \quad A_v = -g_m(r_{on} \| r_{op})$$

$$r_{on} = r_{op} = \frac{1}{\lambda I_{REF}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{REF}} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$A_v = -(0.2)(500 \| 500)$$

$$\Rightarrow A_v = -50$$

10.59

- a. Using the results of problem 10.27, we find the resistance looking into the collector of  $Q_2$  to be

$$R_0 = r_{02} \left[ 1 + \frac{R_E \| (r_{\pi 2} + R'_0)}{r_{02}} \right]$$

$$+ g_{m2} \left( \frac{r_{\pi 2}}{r_{\pi 2} + R'_0} \right) [R_E \| (r_{\pi 2} + R'_0)]$$

where  $R'_0$  is the resistance from the base of  $Q_2$  toward  $Q_1$ . We found

$$\frac{1}{R'_0} = \frac{1}{R_1} + \frac{\frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{01}}}{1 + \left( \frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{01}} \right) (R_E)}$$

$$b. \quad A_v = -g_{m0}(r_0 \| R_L \| R_0)$$

10.60

Output resistance of Wilson source

$$R_0 \approx \frac{\beta r_{03}}{2}$$

Then

$$A_v = -g_m(r_0 \| R_0)$$

$$r_{03} = \frac{V_{AP}}{I_{REF}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

$$r_0 = \frac{V_{AN}}{I_{REF}} = \frac{120}{0.2} = 600 \text{ k}\Omega$$

$$g_m = \frac{I_{REF}}{V_T} = \frac{0.2}{0.026} = 7.69 \text{ mA/V}$$

$$A_v = -7.69 \left[ 600 \parallel \left( \frac{(80)(400)}{2} \right) \right] = -7.69[600 \| 16,000]$$

$$\Rightarrow A_v = -4447$$

10.61

$$a. \quad g_m(M_0) = 2\sqrt{K_n I_{REF}}$$

$$g_m(M_0) = 2\sqrt{(0.25)(0.2)}$$

$$\Rightarrow g_m(M_0) = 0.447 \text{ mA/V}$$

$$r_{on} = \frac{1}{\lambda_n I_{REF}} = \frac{1}{(0.02)(0.2)} \Rightarrow r_{on} = 250 \text{ k}\Omega$$


$$r_{op} = \frac{1}{\lambda_p I_{REF}} = \frac{1}{(0.03)(0.2)} \Rightarrow r_{op} = 167 \text{ k}\Omega$$


$$b. \quad A_v = -g_m(r_{on} \| r_{op}) = -(0.447)(250 \| 167)$$

$$\Rightarrow A_v = -44.8$$

$$c. \quad R_L = 250 \| 167 = r_{on} \| r_{op} \text{ or } R_L = 100 \text{ k}\Omega$$

10.62

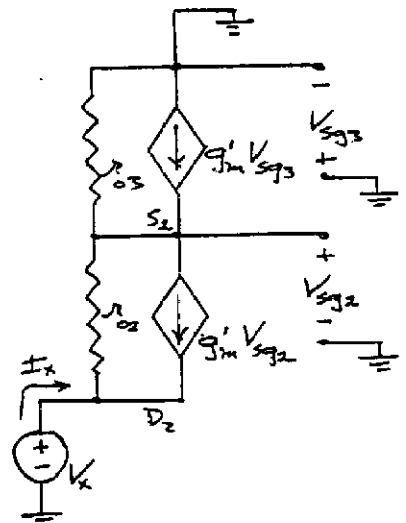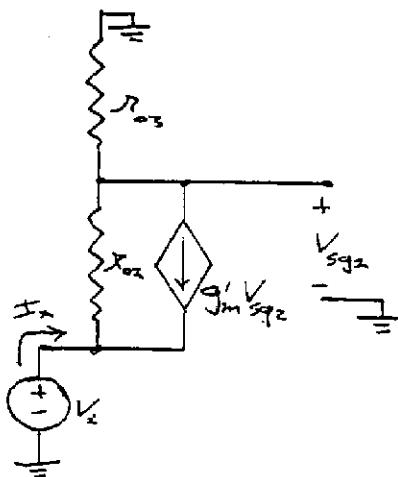
 Since  $V_{sg3} = 0$ , the circuit becomes



$$I_x = -g_m' V_{gs2} + \frac{V_x - V_{gs2}}{r_{o2}} \quad \text{and} \quad V_{gs2} = I_x r_{o3}$$

Then

$$I_x \left( 1 + g_m' r_{o3} + \frac{r_{o3}}{r_{o2}} \right) = \frac{V_x}{r_{o2}}$$

so that

$$\frac{V_x}{I_x} = R_o = r_{o2} \left( 1 + g_m' r_{o3} + \frac{r_{o3}}{r_{o2}} \right)$$

or

$$R_o = r_{o2} + r_{o3} (1 + g_m' r_{o2})$$

$$A_v = \frac{v_o}{v_i} = -g_m (r_{o1} \parallel R_o)$$

Now

$$g_m = 2\sqrt{(0.050)(20)(0.10)} = 0.632 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.02)(0.10)} = 500 \text{ k}\Omega$$

$$g_m' = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.020)(80)(0.1)} = 0.80 \text{ mA/V}$$

$$r_{o2} = r_{o3} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.020)(0.1)} = 500 \text{ k}\Omega$$

Then

$$R_o = 500 + 500[1 + (0.8)(500)] \Rightarrow 201 \text{ M}\Omega$$

$$A_v = -(0.632)(500 \parallel 201000) \Rightarrow \underline{A_v = -315}$$

10.63

$$A_v = -g_{m1} (R_{o2} \parallel R_{o3})$$

From the results of JFETs:

$$R_{o2} = r_{o1} + r_{o2}(1 + g_m' r_{o1})$$

From results of Problem 10.62

$$R_{o3} = r_{o3} + r_{o4}(1 + g_m' r_{o3})$$

We find

$$g_{m1} = 2\sqrt{(0.05)(20)(0.08)} = 0.566 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.02)(0.08)} = 625 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.08)} = 625 \text{ k}\Omega$$

$$g_m' = 2\sqrt{(0.02)(40)(0.08)} = 0.506 \text{ mA/V}$$

Then

$$R_{o2} = 625 + 625[1 + (0.506)(625)] \Rightarrow 199 \text{ M}\Omega$$

$$R_{o3} = 625 + 625[1 + (0.506)(625)] \Rightarrow 199 \text{ M}\Omega$$

Then

$$A_v = -(0.566)[199000 \parallel 199000] \Rightarrow \underline{A_v = -56,317}$$