

Chapter 15

Exercise Solutions

E15.1

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_{3dB}} = \frac{1}{2\pi(10^4)} = 1.59 \times 10^{-5}$$

$$\text{Let } C = 0.01 \mu\text{F} \Rightarrow \underline{R = 1.59 \text{ k}\Omega}$$

Then

$$C_1 = 0.03546 \mu\text{F}$$

$$C_2 = 0.01392 \mu\text{F}$$

$$C_3 = 0.002024 \mu\text{F}$$

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^6}} = \frac{1}{\sqrt{1 + \left(\frac{20}{10}\right)^6}}$$

$$|T| = 0.124 \text{ or } |T| = -18.1 \text{ dB}$$

E15.2

$$f_{3dB} = \frac{1}{2\pi RC} \Rightarrow RC = \frac{1}{2\pi f_{3dB}}$$

$$RC = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

$$\text{Let } C = 0.001 \mu\text{F} = 1 \text{ nF} \Rightarrow \underline{R = 3.18 \text{ k}\Omega}$$

Then

$$R_1 = 2.94 \text{ k}\Omega$$

$$R_2 = 3.44 \text{ k}\Omega$$

$$R_3 = 1.22 \text{ k}\Omega$$

$$R_4 = 8.31 \text{ k}\Omega$$

$$|T| = 0.01 = \frac{1}{\sqrt{1 + \left(\frac{f_{3dB}}{f}\right)^4}}$$

$$1 + \left(\frac{f_{3dB}}{f}\right)^4 = \left(\frac{1}{0.01}\right)^2 = 10^4$$

$$\left(\frac{f_{3dB}}{f}\right)^2 \approx 10 \Rightarrow f = \frac{f_{3dB}}{\sqrt{10}}$$

$$\Rightarrow \underline{f \approx 15.8 \text{ kHz}}$$

E15.3

$$\text{1-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^2}} \Rightarrow -3.87 \text{ dB}$$

$$\text{2-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^4}} \Rightarrow -4.88 \text{ dB}$$

$$\text{3-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^6}} \Rightarrow -6.0 \text{ dB}$$

$$\text{4-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^8}} \Rightarrow -7.24 \text{ dB}$$

E15.4

$$R_{eq} = \frac{1}{f_C C}$$

$$\text{or } f_C C = \frac{1}{R_{eq}} = \frac{1}{5 \times 10^6} = 2 \times 10^{-7}$$

$$\text{If } C = 10 \text{ pF} \Rightarrow \underline{f_C = 20 \text{ kHz}}$$

E15.5

$$\text{Low-frequency gain: } T = -\frac{C_1}{C_2} = -\frac{30}{5} = -6$$

$$f_{3dB} = \frac{f_C C_2}{2\pi C_F} = \frac{(100 \times 10^3)(5 \times 10^{-12})}{2\pi(12 \times 10^{-12})}$$

$$\Rightarrow \underline{f_{3dB} = 6.63 \text{ kHz}}$$

E15.6

$$f_0 = \frac{1}{2\pi\sqrt{3}RC}$$

$$RC = \frac{1}{2\pi f_0 \sqrt{3}} = \frac{1}{2\pi(15 \times 10^3)\sqrt{3}} = 6.13 \times 10^{-6}$$

$$\text{Let } C = 0.001 \mu\text{F} = 1 \text{ nF}$$

$$\text{Then } \underline{R = 6.13 \text{ k}\Omega} \text{ so } \underline{R_2 = 8R = 49 \text{ k}\Omega}$$

E15.7

$$f_0 = \frac{1}{2\pi\sqrt{6}RC} = \frac{1}{2\pi\sqrt{6}(10^4)(100 \times 10^{-12})}$$

$$\Rightarrow \underline{f_0 \approx 65 \text{ kHz}}$$

$$R_2 = 29R = 29(10^4)$$

$$\Rightarrow \underline{R_2 = 290 \text{ k}\Omega}$$

E15.8

$$f_0 = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi f_0 R}$$

$$C = \frac{1}{2\pi(800)(10^4)} \Rightarrow \underline{C \approx 0.02 \mu\text{F}}$$

$$R_2 = 2R_1 = 2(10) \Rightarrow \underline{R_2 = 20 \text{ k}\Omega}$$

E15.9

$$f_0 = \frac{1}{2\pi\sqrt{L \cdot \left(\frac{C_1 C_2}{C_1 + C_2}\right)}} = \frac{1}{2\pi\sqrt{(10^{-6}) \left[\frac{(10^{-9})^2}{2 \times 10^{-9}}\right]}}$$

$$\Rightarrow f_0 = 7.12 \text{ MHz}$$

$$\frac{C_2}{C_1} = g_m R$$

$$g_m = \frac{C_2}{C_1} \cdot \frac{1}{R} = \frac{1}{4 \times 10^3} \Rightarrow g_m = 0.25 \text{ mA/V}$$

We have

$$g_m = 2 \left(\frac{k'}{2} \right) \left(\frac{W}{L} \right) (V_{GS} - V_{TH})$$

$$k' \approx 20 \mu\text{A/V}^2, V_{GS} - V_{TH} \approx 1 \text{ V}$$

$$\text{So } \frac{W}{L} = \frac{0.25 \times 10^{-3}}{(20 \times 10^{-6})(1)} = 12.5$$

and a value of $W/L = 12.5$ is certainly reasonable.

E15.10

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) V_H$$

$$2 = \left(\frac{R_1}{R_1 + 20} \right) (12)$$

$$2(R_1 + 20) = 12R_1$$

$$40 = 10R_1 \Rightarrow R_1 = 4 \text{ k}\Omega$$

E15.11

$$V_{TH} = - \left(\frac{R_1}{R_2} \right) V_L$$

$$0.10 = - \left(\frac{R_1}{R_2} \right) (-10) \Rightarrow \frac{R_1}{R_2} = 0.010$$

$$\text{Let } R_1 = 0.10 \text{ k}\Omega \text{ then } R_2 = 10 \text{ k}\Omega$$

E15.12

$$a. \quad V_S = \left(\frac{R_2}{R_1 + R_2} \right) V_{REF} = \left(\frac{10}{1 + 10} \right) (2)$$

$$V_S = 1.82 \text{ V}$$


$$V_{TH} = V_S + \left(\frac{R_1}{R_1 + R_2} \right) V_H = 1.82 + \left(\frac{1}{1 + 10} \right) (10)$$

$$V_{TH} = 2.73 \text{ V}$$

$$V_{TL} = V_S + \left(\frac{R_1}{R_1 + R_2} \right) V_L = 1.82 + \left(\frac{1}{1 + 10} \right) (-10)$$

$$V_{TL} = 0.91 \text{ V}$$

b.

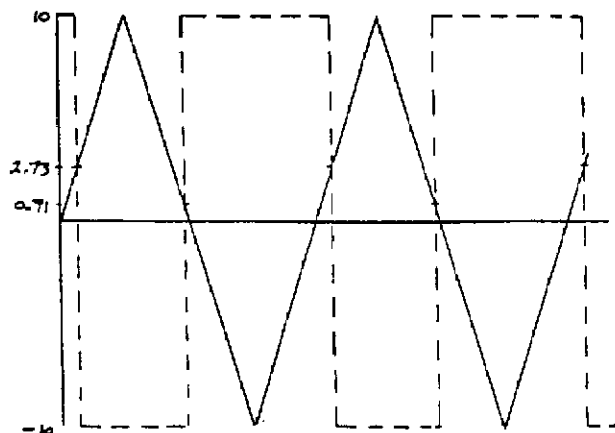

E15.13

$$V_S = \left(1 + \frac{R_1}{R_2} \right) V_{REF}$$

$$V_{TH} = V_S - \left(\frac{R_1}{R_2} \right) V_L \text{ and } V_{TL} = V_S - \left(\frac{R_1}{R_2} \right) V_H$$

$$\text{Hysteresis Width} = V_{TH} - V_{TL} = \left(\frac{R_1}{R_2} \right) (V_H - V_L)$$

$$2.5 = \left(\frac{R_1}{R_2} \right) (5 - [-5]) = 10 \left(\frac{R_1}{R_2} \right)$$

$$\text{So } \frac{R_1}{R_2} = 0.25$$

Then

$$V_S = -1 = \left(1 + \frac{R_1}{R_2} \right) V_{REF} = (1 + 0.25) V_{REF}$$

$$\Rightarrow V_{REF} = -0.8 \text{ V}$$

Then

$$V_{TH} = -1 - (0.25)(-5) \Rightarrow V_{TH} = 0.25 \text{ V}$$

$$V_{TL} = -1 - (0.25)(5) \Rightarrow V_{TL} = -2.25 \text{ V}$$

E15.14

$$V_{TH} - V_{TL} = \left(\frac{R_1}{R_1 + R_2} \right) (V_H - V_L)$$

$$0.10 = \left(\frac{R_1}{R_1 + R_2} \right) (10 - [-10])$$

$$1 + \frac{R_2}{R_1} = \frac{20}{0.10} = 200 \Rightarrow \frac{R_2}{R_1} = 199$$

$$V_S = \left(\frac{R_2}{R_1 + R_2} \right) V_{REF}$$

$$V_{REF} = \left(1 + \frac{R_1}{R_2} \right) V_S = \left(1 + \frac{1}{199} \right) (1)$$

$$\Rightarrow V_{REF} = 1.005 \text{ V}$$

$$I = \frac{V_H - V_{BE(on)} - V_f}{R + 0.1}$$

$$R + 0.1 = \frac{10 - 0.7 - 0.7}{0.2} = 43 \text{ k}\Omega$$

$$\underline{R = 42.9 \text{ k}\Omega}$$

E15.15

At $t = 0^-$, let $v_o = -5$ so $v_X = -2.5$. For $t > 0$

$$v_X = 10 + (-2.5 - 10) \exp\left(-\frac{t}{\tau_X}\right)$$

When $v_X = 5.0$, output switches

$$5.0 = 10 - 12.5 \exp\left(-\frac{t_1}{\tau_X}\right)$$

$$\exp\left(-\frac{t_1}{\tau_X}\right) = \frac{10 - 5}{12.5} = \frac{5.0}{12.5}$$

$$\exp\left(+\frac{t_1}{\tau_X}\right) = \frac{12.5}{5.0} \Rightarrow t_1 = \tau_X \cdot \ln\left(\frac{12.5}{5.0}\right)$$

$$\Rightarrow t_1 = \tau_X(0.916)$$

During the next part of the cycle

$$v_X = -5 + (5 - [-5]) \exp\left(-\frac{t}{\tau_X}\right)$$

When $v_X = -2.5$, output switches

$$-2.5 = -5 + 10 \exp\left(-\frac{t_2}{\tau_X}\right)$$

$$\exp\left(-\frac{t_2}{\tau_X}\right) = \frac{5 - 2.5}{10} = \frac{2.5}{10}$$

$$\exp\left(+\frac{t_2}{\tau_X}\right) = \frac{10}{2.5} \Rightarrow t_2 = \tau_X \cdot \ln\left(\frac{10}{2.5}\right)$$

$$\Rightarrow t_2 = \tau_X(1.39)$$

$$\text{Period} = t_1 + t_2 = T = [(0.916) + (1.39)]\tau_X$$

$$= 2.31\tau_X$$

$$\Rightarrow \text{Frequency} = \frac{1}{2.31\tau_X}$$


$$\tau_X = (50 \times 10^3)(0.01 \times 10^{-6}) = 5 \times 10^{-4} \text{ s}$$

$$\Rightarrow \underline{f = 866 \text{ Hz}}$$

$$\text{Duty cycle} = \frac{t_1}{t_1 + t_2} \times 100\%$$

$$= \frac{(0.916)}{(0.916) + (1.39)} \times 100\%$$
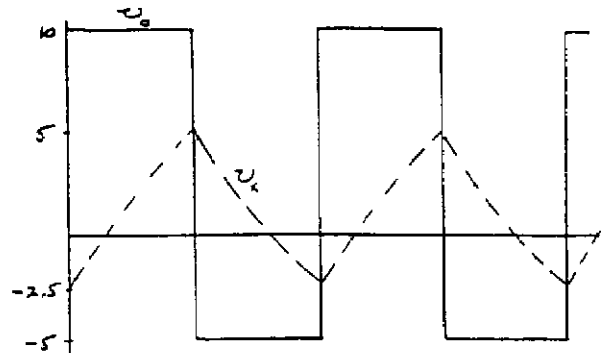
$$\Rightarrow \underline{\text{Duty cycle} = 39.7\%}$$



E15.16

$$v_X = \left(\frac{R_1}{R_1 + R_2}\right)v_o = \left(\frac{10}{10 + 20}\right)v_o = \frac{1}{3}v_o$$

$$t = 0, v_X = -\frac{10}{3}$$

$$v_X = 10 + \left(-\frac{10}{3} - 10\right) \exp\left(-\frac{t}{\tau_X}\right)$$

Output switches when $v_X = \frac{10}{3}$

$$\frac{10}{3} = 10 - 13.33 \exp\left(-\frac{t_1}{\tau_X}\right)$$

$$\exp\left(-\frac{t_1}{\tau_X}\right) = \frac{10 - 3.33}{13.33} = \frac{6.67}{13.33}$$

$$\exp\left(+\frac{t_1}{\tau_X}\right) = \frac{13.33}{6.67} \approx 2$$

$$t_1 = \tau_X \ln(2) = (0.693)\tau_X$$


$$T = 2(0.693)\tau_X$$

$$f = \frac{1}{2(0.693)\tau_X}$$

$$\tau_X = R_X C_X = (10^4)(0.1 \times 10^{-6}) = 1 \times 10^{-3}$$

$$\Rightarrow \underline{f = 722 \text{ Hz}}$$
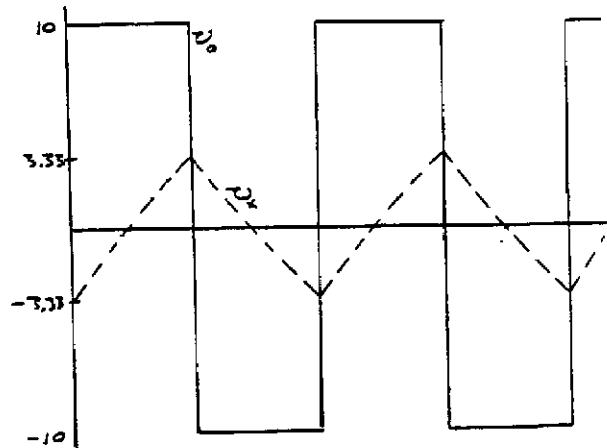
$$\Rightarrow \underline{\text{Duty cycle} = 50\%}$$



E15.17

a. $\tau_X = R_X C_X$

$$v_X = \left(\frac{R_1}{R_1 + R_2} \right) v_0 = \left(\frac{10}{10 + 90} \right) (12) = 1.2 \text{ V}$$

$$\beta = \frac{R_1}{R_1 + R_2} = 0.10$$

$$T = \tau_X \ln \left[\frac{1 + V_T/V_P}{1 - \beta} \right] = \tau_X \ln \left[\frac{1 + \frac{0.7}{12}}{1 - (0.10)} \right]$$

$$T = 50 \times 10^{-6} = \tau_X \ln [1.18] = (0.162) \tau_X$$

$$R_X = \frac{50 \times 10^{-6}}{(0.1 \times 10^{-6})(0.162)} \Rightarrow R_X = 3.09 \text{ k}\Omega$$

b. Recovery time

$$v_X = V_P + (-1.2 - V_P) \exp \left(-\frac{t}{\tau_X} \right)$$

When $v_X = V_T$, $t = t_2$

$$0.7 = 12 + (-1.2 - 12) \exp \left(-\frac{t_2}{\tau_X} \right)$$

$$\exp \left(-\frac{t_2}{\tau_X} \right) = \frac{12 - 0.7}{13.2} = 0.856$$

$$t_2 = \tau_X \ln \left(\frac{1}{0.856} \right) = (0.155) \tau_X$$

$$\tau_X = (3.09 \times 10^3)(0.1 \times 10^{-6}) = 3.09 \times 10^{-4}$$

$$\Rightarrow t_2 = 47.9 \text{ }\mu\text{s}$$

E15.18

$$\beta = \left(\frac{R_1}{R_1 + R_2} \right) = \frac{20}{20 + 40} = 0.333$$

$$\tau_X = R_X C_X = (10^4)(0.01 \times 10^{-6}) = 1 \times 10^{-4}$$

$$T = \tau_X \ln \left(\frac{1 + V_T/V_P}{1 - \beta} \right) = (1 \times 10^{-4}) \ln \left[\frac{1 + \frac{0.7}{8}}{1 - 0.333} \right]$$

$$\Rightarrow T = 48.9 \text{ }\mu\text{s}$$

Recovery time

$$0.7 = 8 + (-2.66 - 8) \exp \left(-\frac{t_2}{\tau_X} \right)$$

$$\exp \left(-\frac{t_2}{\tau_X} \right) = \frac{8 - 0.7}{10.66} = 0.685$$

$$t_2 = \tau_X \ln \left(\frac{1}{0.685} \right)$$

$$\Rightarrow t_2 = 37.8 \text{ }\mu\text{s}$$

E15.19

$$f = \frac{1}{0.693(R_A + 2R_B)C}$$

$$= \frac{1}{(0.693)[20 + 2(80)] \times 10^3 \times (0.01 \times 10^{-6})}$$

$$\Rightarrow f = 802 \text{ Hz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$= \frac{20 + 80}{20 + 2(80)} \times 100\%$$

$$\Rightarrow \text{Duty cycle} = 55.6\%$$

E15.20

$$f = \frac{1}{(0.693)(R_A + R_B)C}$$

$$R_A + R_B = \frac{1}{(0.693)fC}$$

Let $C = 0.01 \text{ }\mu\text{F}$, $f = 1 \text{ kHz}$

$$R_A + R_B = \frac{1}{(0.693)(10^3)(0.01 \times 10^{-6})} = 1.44 \times 10^5$$

$$\text{Duty cycle} = 55 = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$55 = \frac{(1.44 \times 10^5)(100)}{(1.44 \times 10^5) + R_B}$$

$$R_B = \frac{(1.44 \times 10^5)(100 - 55)}{55}$$

$$\Rightarrow R_B = 118 \text{ k}\Omega \text{ so } R_A = 26 \text{ k}\Omega$$

E15.21

a. $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

$$V_P = \sqrt{2R_L \bar{P}} = \sqrt{2(8)(1)} \Rightarrow V_P = 4 \text{ V}$$

$$I_P = \frac{V_P}{R_L} = \frac{4}{8} \Rightarrow I_P = 0.5 \text{ A}$$

b. $V_{CE} = 12 - 4 = 8 \text{ V}$

$$I_C \approx 0.5 \text{ A}$$

$$\text{So } P = I_C \cdot V_{CE} = (0.5)(8) \Rightarrow P = 4 \text{ W}$$

E15.22

a. $\frac{v_{o1}}{v_i} = \left(1 + \frac{R_2}{R_1} \right) = \left(1 + \frac{30}{20} \right) = 2.5$

$$\frac{v_{o2}}{v_i} = -\frac{R_4}{R_3} = -\frac{50}{20} = -2.5$$

(b) $\bar{P} = \frac{1}{2} \frac{V_L^2}{R_L} = \frac{1}{2} \frac{[12 - (-12)]^2}{12} = 240 \text{ mW}$

Or

$$\bar{P} = 0.24 \text{ W}$$

c. $\frac{12}{2.5} = V_{P1} = 4.8 \text{ V}$

E15.23

$$\text{Line regulation} = \frac{dV_o}{dV^+} = \frac{dV_o}{dV_Z} \cdot \frac{dV_Z}{dV^+}$$

Now

$$\frac{dV_o}{dV_Z} = \left(1 + \frac{10}{10}\right) = 2$$

$$\frac{dV_Z}{dV^+} = \left(\frac{r_z}{r_z + R_1}\right) = \frac{10}{10 + 4400} = 0.00227$$

$$\text{So Line regulation} = (2)(0.00227) = 0.00454$$

$$\underline{0.454\%}$$

$$V_o[0.10 + 2.0 - 0.05 + 1000] + I_o = 12,600$$


$$V_o(1002.05) + I_o = 12,600$$

$$\text{For } I_o = 1 \text{ mA} \Rightarrow V_o = 12.5732$$

$$\text{For } I_o = 100 \text{ mA} \Rightarrow V_o = 12.4744$$

$$\begin{aligned} \text{Load reg} &= \frac{V_o(\text{NL}) - V_o(\text{FL})}{V_o(\text{NL})} \times 100\% \\ &= \frac{12.5732 - 12.4744}{12.5732} \times 100\% \\ \text{Load reg} &= \underline{0.786\%} \end{aligned}$$

E15.24

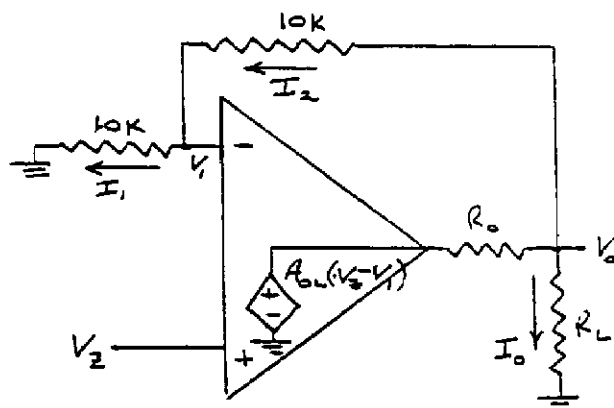

$$\frac{V_1}{10} = \frac{V_o - V_1}{10} \Rightarrow V_1 \left(\frac{1}{10} + \frac{1}{10}\right) = \frac{V_o}{10}$$

$$V_1 \left(\frac{2}{10}\right) = \frac{V_o}{10} \Rightarrow V_o = 2V_1 \Rightarrow V_1 = \frac{V_o}{2}$$

$$\frac{V_o - V_1}{10} + \frac{V_o}{R_L} + \frac{V_o - A_{0L}(V_2 - V_1)}{R_o} = 0$$

$$\begin{aligned} \frac{V_o}{10} + \frac{V_o}{R_L} + \frac{V_o}{R_o} - \frac{A_{0L}V_2}{R_o} &= \frac{V_1}{10} - \frac{A_{0L}V_1}{R_o} \\ &= \frac{V_o}{2(10)} - \frac{A_{0L}V_o}{2R_o} \end{aligned}$$

$$\frac{V_o}{10} + I_o + \frac{V_o}{0.5} - \frac{1000(6.3)}{0.5} = \frac{V_o}{20} - \frac{(1000)V_o}{2(0.5)}$$

E15.25

$$\text{a. } I_{C3} = \frac{V_Z - 3V_{BE}(\text{on})}{R_1 + R_2 + R_3}$$

$$\begin{aligned} I_{C3} &= \frac{5.6 - 3(0.6)}{3.9 + 3.4 + 0.576} = \frac{3.8}{7.88} \\ &\Rightarrow \underline{I_{C3} = 0.482 \text{ mA}} \end{aligned}$$

$$I_{C4}R_4 = V_T \ln \left(\frac{I_{C3}}{I_{C4}}\right)$$

$$I_{C4}(0.1) = (0.026) \ln \left(\frac{0.482}{I_{C4}}\right)$$

By trial and error

$$\underline{I_{C4} = 0.213 \text{ mA}}$$

$$V_{BT} = 2(0.6) + (0.482)(3.9)$$

$$\Rightarrow \underline{V_{BT} = 3.08 \text{ V}}$$

$$\text{b. } \left(\frac{R_{13}}{R_{13} + R_{12}}\right)V_o = V_{B8} = V_{BT}$$

$$\left(\frac{2.23}{2.23 + R_{12}}\right)(5) = 3.08$$

$$(2.23)(5) = (3.08)(2.23) + (3.08)R_{12}$$

$$11.15 = 6.868 = 3.08R_{12}$$


$$\Rightarrow \underline{R_{12} = 1.39 \text{ k}\Omega}$$

Chapter 15

Problem Solutions

15.1

(a) For example:

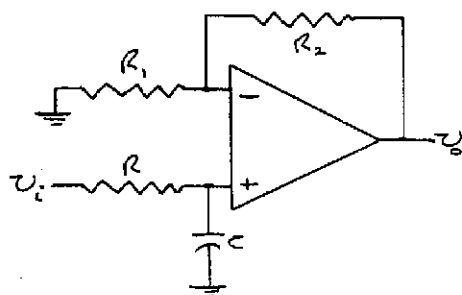


Low-Frequency: $\frac{v_o}{v_i} = \left(1 + \frac{R_2}{R_1}\right) = 10 \Rightarrow \frac{R_2}{R_1} = 9$

Corner Frequency:

$$f = \frac{1}{2\pi RC} = 5 \times 10^3 \Rightarrow RC = 3.18 \times 10^{-5}$$

(b) For Example:

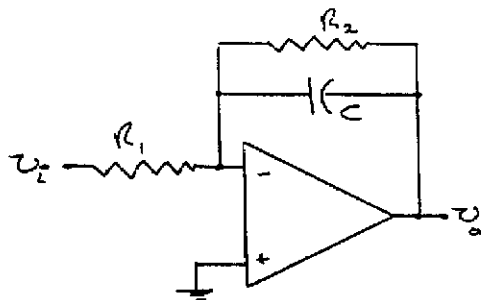

$$\frac{v_o}{v_i} = \frac{-R_2 \parallel \frac{1}{j\omega C}}{R_1} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C}$$

So, set

$$\frac{R_2}{R_1} = 15 \Rightarrow \text{For example, } R_1 = 10 \text{ k}\Omega, R_2 = 150 \text{ k}\Omega$$

$$R_2 C = \frac{1}{2\pi f_{3-dB}} = \frac{1}{2\pi(15 \times 10^3)} = 1.06 \times 10^{-5}$$

Then $C = 70.7 \text{ pF}$

15.2

$$(a) |A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^2}} = 0.447 \Rightarrow$$

$$|A_v| = -7 \text{ dB}$$

$$(b) |A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^4}} = 0.2425 \Rightarrow$$

$$|A_v| = -12.3 \text{ dB}$$

$$(c) |A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^6}} = 0.1240 \Rightarrow$$

$$|A_v| = -18.1 \text{ dB}$$

15.3

Using Figure 15.9(a)

$$f_{3-dB} = \frac{1}{2\pi RC}$$

So

$$RC = \frac{1}{2\pi f_{3-dB}} = \frac{1}{2\pi(10 \times 10^3)} = 1.59 \times 10^{-5}$$

For example, $C = 0.001 \mu\text{F}$, $R = 15.9 \text{ k}\Omega$ so that $R_3 = 11.2 \text{ k}\Omega$ and $R_4 = 22.4 \text{ k}\Omega$

15.4

Use Figure 15.10(b)

$$f_{3-dB} = \frac{1}{2\pi RC}$$

or

$$RC = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

For example, let $C = 100 \text{ pF}$ Then $R = 31.8 \text{ k}\Omega$ And $R_1 = 8.97 \text{ k}\Omega$ $R_2 = 22.8 \text{ k}\Omega$ $R_3 = 157 \text{ k}\Omega$

From Equation (15.26)

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f_{3-dB}}{f}\right)^4}}$$

We find

f kHz	$ T $
30	0.211
35	0.324
40	0.456
45	0.589

15.5

From Equation (15.7),

$$T(s) = \frac{Y_1 Y_2}{Y_1 Y_2 + Y_4 (Y_1 + Y_2 + Y_3)}$$

For a high-pass filter, let $Y_1 = Y_2 = sC$,

$$Y_3 = \frac{1}{R_3}, \text{ and } Y_4 = \frac{1}{R_4}$$

Then

$$\begin{aligned} T(s) &= \frac{s^2 C^2}{s^2 C^2 + \frac{1}{R_4} \left(sC + sC + \frac{1}{R_3} \right)} \\ &= \frac{1}{1 + \frac{1}{sR_4 C} \left(2 + \frac{1}{sR_3 C} \right)} \end{aligned}$$

Define $\tau_3 = R_3 C$ and $\tau_4 = R_4 C$

$$T(s) = \frac{1}{1 + \frac{1}{s\tau_4} \left(2 + \frac{1}{s\tau_3} \right)}$$

Set $s = j\omega$

$$\begin{aligned} T(j\omega) &= \frac{1}{1 + \frac{1}{j\omega\tau_4} \left(2 + \frac{1}{j\omega\tau_3} \right)} \\ &= \frac{1}{1 - \frac{j}{\omega\tau_4} \left(2 - \frac{j}{\omega\tau_3} \right)} \\ &= \frac{1}{\left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2j}{\omega\tau_4}} \end{aligned}$$

$$|T(j\omega)| = \left\{ \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right)^2 + \frac{4}{\omega^2\tau_4^2} \right\}^{-1/2}$$

For a maximally flat filter, we want

$$\left. \frac{d|T|}{d\omega} \right|_{\omega=\infty} = 0$$

Taking the derivative, we find

$$\begin{aligned} \frac{d|T(j\omega)|}{d\omega} &= -\frac{1}{2} \left\{ \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right)^2 + \frac{4}{\omega^2\tau_4^2} \right\}^{-3/2} \\ &\quad \times \left[2 \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right) \left(\frac{2}{\omega^3\tau_3\tau_4} \right) + \frac{4(-2)}{\omega^3\tau_4^2} \right] \end{aligned}$$

or

$$\begin{aligned} \left. \frac{d|T(j\omega)|}{d\omega} \right|_{\omega=\infty} &= 0 \\ &= \left[\left(\frac{4}{\omega^3\tau_3\tau_4} \right) \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{8}{\omega^3\tau_4^2} \right] \\ &= \frac{4}{\omega^3} \left[\frac{1}{\tau_3\tau_4} \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2}{\tau_4^2} \right] \end{aligned}$$

Then

$$\left[\frac{1}{\tau_3\tau_4} \left(1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2}{\tau_4^2} \right] \bigg|_{\omega=\infty} = 0$$

$$\text{So that } \frac{1}{\tau_3} = \frac{2}{\tau_4} \Rightarrow 2\tau_3 = \tau_4$$

Then the transfer function can be written as:

$$\begin{aligned} |T(j\omega)| &= \left\{ \left[1 - \frac{1}{\omega^2(2\tau_3^2)} \right]^2 + \frac{4}{\omega^2(4\tau_3^2)} \right\}^{-1/2} \\ &= \left\{ 1 - \frac{1}{\omega^2\tau_3^2} + \frac{1}{4(\omega^2\tau_3^2)^2} + \frac{1}{\omega^2\tau_3^2} \right\}^{-1/2} \\ &= \left\{ 1 + \frac{1}{4(\omega^2\tau_3^2)^2} \right\}^{-1/2} \end{aligned}$$

3 - dB frequency

$$2\omega^2\tau_3^2 = 1 \text{ or } \omega = \frac{1}{\sqrt{2}\tau_3} = \frac{1}{\sqrt{2}R_3C}$$

Define

$$\omega = \frac{1}{RC}$$

So that

$$R_3 = \frac{R}{\sqrt{2}}$$

We had $2\tau_3 = \tau_4$ or $2(R_3C) = R_4C \Rightarrow R_4 = 2R_3$

So that $R_4 = \sqrt{2} \cdot R$

15.6

From Equation (15.25)

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}} \right)^{2N}}}$$

$$-25 \text{ dB} \Rightarrow |T| = 0.0562$$

$$\frac{f}{f_{3-dB}} = \frac{20}{10} = 2$$

So

$$0.0562 = \frac{1}{\sqrt{1 + (2)^{2N}}}$$


$$1 + (2)^{2N} = 316.6 \Rightarrow (2)^{2N} = 315.6$$

$$2N \cdot \ln(2) = \ln(315.6)$$

$$\Rightarrow N = 4.15 \Rightarrow \underline{N = 5} \text{ A 5-pole filter}$$

15.7

Consider

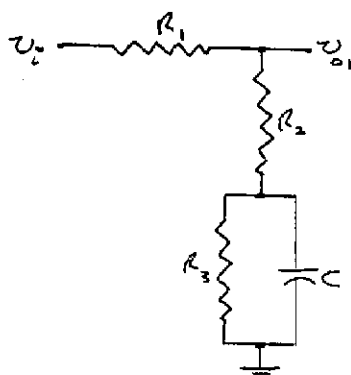


For low-frequency: $\frac{v_o}{v_i} = \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

For high-frequency: $\frac{v_o}{v_i} = \frac{R_2}{R_1 + R_2}$

So we need
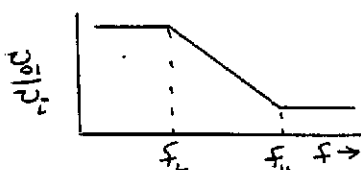
$$\frac{R_2 + R_3}{R_1 + R_2 + R_3} = 25 \left(\frac{R_2}{R_1 + R_2} \right)$$




Let $R_1 + R_2 = 50 \text{ k}\Omega$ and $R_2 = 15 \text{ k}\Omega \Rightarrow$

$$\underline{R_1 = 48.5 \text{ k}\Omega}$$

Then

$$\frac{15 + R_3}{50 + R_3} = 25 \left(\frac{15}{50} \right) \Rightarrow \underline{R_3 = 144 \text{ k}\Omega}$$

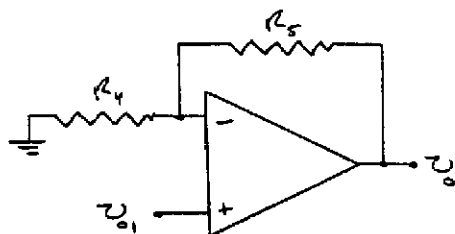Connect the output of this circuit to a non-inverting op-amp circuit.



At low-frequency:

$$v_{o1} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \cdot v_i = \frac{15 + 144}{48.5 + 15 + 144} \cdot v_i = 0.75 v_i$$

Need to have $v_o = 25$.

$$v_o = 25 = \left(1 + \frac{R_5}{R_4} \right) \cdot v_{o1} = \left(1 + \frac{R_5}{R_4} \right) (0.75) v_i \Rightarrow$$

$$\frac{R_5}{R_4} = 32.3$$

To check at high-frequency.

$$v_{o1} = \frac{R_2}{R_1 + R_2} v_i = \frac{15}{15 + 48.5} v_i = 0.03 v_i$$

$$v_o = (1 + 32.3) v_{o1} = (33.3)(0.03) v_i = (1.0) v_i$$

which meets the design specification

Consider the frequency response.

$$\frac{v_{o1}}{v_i} = \frac{R_2 + R_3 \parallel \frac{1}{sC}}{R_1 + R_2 + R_3 \parallel \frac{1}{sC}}$$

Now

$$R_3 \parallel \frac{1}{sC} = \frac{R_3}{1 + sR_3C}$$

Then, we find

$$\frac{v_{o1}}{v_i} = \frac{R_2 + R_3(1 + sR_3C)}{R_3 + (R_1 + R_2)(1 + sR_3C)}$$

which can be rearranged as

$$\frac{v_{o1}}{v_i} = \frac{(R_2 + R_3)(1 + s(R_3 \parallel R_3)C)}{(R_1 + R_2 + R_3)(1 + s(R_3 \parallel (R_1 + R_2))C)}$$

So

$$f_L \approx \frac{1}{2\pi(R_3 \parallel R_3)C} = \frac{1}{2\pi(15 \parallel 144) \times 10^3 C} = \frac{1}{(9.33 \times 10^3)C}$$

$$f_H \approx \frac{1}{2\pi(R_3 \parallel (R_1 + R_2))C} = \frac{1}{2\pi(144 \parallel 50) \times 10^3 C}$$

$$= \frac{1}{(2.33 \times 10^5)C}$$


Set

$$25 \text{ kHz} = \frac{f_L + f_H}{2} = \frac{1}{2} \left[\frac{1}{(9.33 \times 10^3)C} + \frac{1}{(2.33 \times 10^5)C} \right]$$

Which yields

$$\underline{C = 2.23 \text{ nF}}$$

15.8

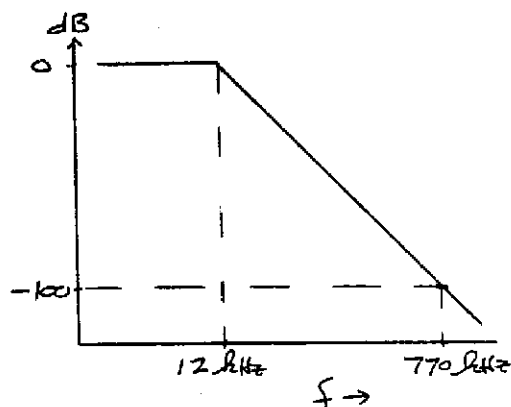

$$|A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c - 0}\right)^{2N}}}$$

$$-100 \text{ dB} \Rightarrow 10^{-5}$$

So

$$10^{-5} = \frac{1}{\sqrt{1 + \left(\frac{770}{12}\right)^{2N}}}$$

or

$$1 + (64.2)^{2N} = \left(\frac{1}{10^{-5}}\right)^2 = 10^{10}$$

or


$$(64.2)^{2N} \approx 10^{10}$$

Now

N	Left Side
1	4.112×10^3
2	1.7×10^7
3	7×10^{10}

So, we need a 3rd order filter.

15.9

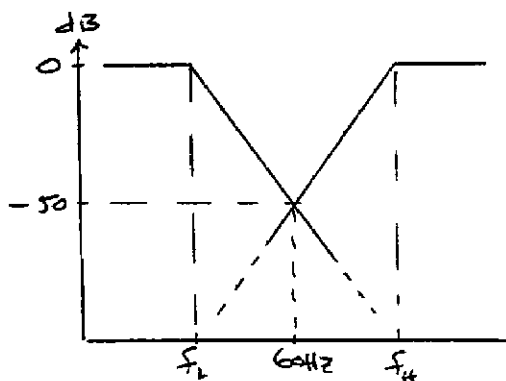Low-pass: $-50 \text{ dB} \Rightarrow 3.16 \times 10^{-3}$

Then

$$3.16 \times 10^{-3} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_L}\right)^4}} = \frac{1}{\sqrt{1 + \left(\frac{60}{f_L}\right)^4}}$$

We find $f_L = 3.37 \text{ Hz}$

High Pass:

$$3.16 \times 10^{-3} = \frac{1}{\sqrt{1 + \left(\frac{f_H}{f}\right)^4}} = \frac{1}{\sqrt{1 + \left(\frac{f_H}{60}\right)^4}}$$

We find $f_H = 1067 \text{ Hz}$ Bandwidth: $BW = f_H - f_L = 1067 - 3.37 \Rightarrow$

$$BW \approx 1064 \text{ Hz}$$

15.10

a.

$$\frac{v_I}{R_4} = -\frac{v_{O2}}{R_3} - \frac{v_O}{R_1 \parallel \left(\frac{1}{sC}\right)} \quad (1)$$

$$\frac{v_O}{R_2} = -\frac{v_{O1}}{\left(\frac{1}{sC}\right)} \quad (2)$$

$$\frac{v_{O1}}{R_5} = -\frac{v_{O2}}{R_5} \Rightarrow v_{O1} = -v_{O2} \quad (3)$$

Then

$$\frac{v_O}{R_2} = +\frac{v_{O2}}{\left(\frac{1}{sC}\right)} \text{ or } v_{O2} = v_O \left(\frac{1}{sR_2C}\right) \quad (2)$$

And

$$\begin{aligned} \frac{v_I}{R_4} &= -\frac{v_O}{R_3} \cdot \left(\frac{1}{sR_2C}\right) - \frac{v_O}{R_1 \parallel \left(\frac{1}{sC}\right)} \\ &= -v_O \left[\frac{1}{R_3(sR_2C)} + \frac{1}{\frac{R_1 \cdot (1/sC)}{R_1 + (1/sC)}} \right] \\ &= -v_O \left[\frac{1}{R_3(sR_2C)} + \frac{1 + sR_1C}{R_1} \right] \\ &= -v_O \left[\frac{R_1 + (1 + sR_1C)(sR_2R_3C)}{(sC)R_1R_2R_3} \right] \end{aligned} \quad (1)$$

Then

$$\frac{v_O}{v_I} = -\frac{1}{R_4} \left[\frac{(sC)(R_1R_2R_3)}{R_1 + sR_2R_3C + s^2R_1R_2R_3C^2} \right]$$

or

$$A_v(s) = \frac{v_O}{v_I} = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + sC + \frac{1}{sCR_2R_3}}$$

$$b. \quad A_v(j\omega) = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + j\omega C + \frac{1}{j\omega C R_2 R_3}}$$

or

$$A_v(j\omega) = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + j\left[\omega C - \frac{1}{\omega C R_2 R_3}\right]}$$

$$= -\frac{R_1}{R_4} \cdot \frac{1}{\left\{1 + j\left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right]\right\}}$$

$$|A_v(j\omega)| = \frac{R_1}{R_4} \cdot \frac{1}{\left\{1 + \left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right]^2\right\}^{1/2}}$$

$$|A_v|_{\max} \text{ when } \left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right] = 0$$

Then

$$|A_v|_{\max} = \frac{R_1}{R_4} = \frac{85}{3} \Rightarrow |A_v|_{\max} = 28.3$$

Now

$$\omega R_1 C \left[1 - \frac{1}{\omega^2 C^2 R_2 R_3}\right] = 0 \text{ or } \omega = \frac{1}{C\sqrt{R_2 R_3}}$$

Then

$$f = \frac{1}{2\pi C\sqrt{R_2 R_3}} = \frac{1}{2\pi(0.1 \times 10^{-6})\sqrt{(300)^2}}$$

So

$$f = 5.305 \text{ kHz}$$

To find the two 3-dB frequencies,

$$\left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right] = \pm 1$$

$$\omega^2 R_1 R_2 R_3 C^2 - R_1 = \pm \omega R_2 R_3 C$$

$$\omega^2 (85 \times 10^3) (300)^2 (0.1 \times 10^{-6})^2 - 85 \times 10^3$$

$$= \pm \omega (300)^2 (0.1 \times 10^{-6})$$

$$\omega^2 (7.65 \times 10^{-5}) - 85 \times 10^3 = \pm \omega (9 \times 10^{-3})$$

$$\omega^2 (7.65 \times 10^{-5}) \pm \omega (9 \times 10^{-3}) - 85 \times 10^3 = 0$$

$$\omega = \frac{\pm(9 \times 10^{-3})}{2(7.65 \times 10^{-5})}$$

$$\pm \frac{\sqrt{(9 \times 10^{-3})^2 + 4(7.65 \times 10^{-5})(85 \times 10^3)}}{2(7.65 \times 10^{-5})}$$

We find $f = 5.315 \text{ kHz}$ and $f = 5.296 \text{ kHz}$

15.11

a.

$$\frac{v_I - v_A}{R} = \left(\frac{1}{sC}\right) v_A \quad (1)$$

$$\frac{v_I - v_B}{R} = \frac{v_B - v_O}{R} \quad (2)$$

and $v_A = v_B$

So

$$\frac{v_I}{R} = v_A \left(\frac{1}{R} + sC\right) = v_A \left(\frac{1 + sRC}{R}\right) \quad (1)$$

or

$$v_A = \frac{v_I}{1 + sRC}$$

Then

$$v_I + v_O = 2v_B = 2v_A = \frac{2v_I}{1 + sRC} \quad (2)$$

$$v_O = v_I \left[\frac{2}{1 + sRC} - 1 \right] = v_I \left[\frac{1 - sRC}{1 + sRC} \right]$$

Now

$$\frac{v_O}{v_I} = A(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}$$

$$|A| = \frac{\sqrt{1 + \omega^2 R^2 C^2}}{\sqrt{1 + \omega^2 R^2 C^2}} \Rightarrow |A| = 1$$

Phase:

$$\phi = -2 \tan^{-1}(\omega RC)$$

$$b. \quad RC = (10^4)(15.9 \times 10^{-9}) = 1.59 \times 10^{-4}$$

f	ϕ
0	0
10^2	-11.4
5×10^3	-53.1
$1/2\pi RC = 10^3 \text{ Hz}$	-90°
5×10^3	-157
10^4	-169

15.12

$$a. \quad \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2 \parallel (1/sC)} = 0$$

$$\frac{V_i}{R_1} + \frac{V_i - V_o}{\left[\frac{R_2}{1 + sR_2C} \right]} = 0$$

$$\frac{R_2}{R_1} \cdot \frac{1}{1 + sR_2C} (V_i) + V_i = V_o$$

$$\frac{V_o}{V_i} = \frac{R_2 + R_1(1 + sR_2C)}{R_1(1 + sR_2C)}$$

$$= \frac{(R_2 + R_1)[1 + s(R_1 \parallel R_2)C]}{R_1(1 + sR_2C)}$$

$$\Rightarrow \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1} \right) \left[\frac{1 + s(R_1 \parallel R_2)C}{(1 + sR_2C)} \right]$$

$$\Rightarrow f_{3dB1} = \frac{1}{2\pi R_2 C}$$

$$\Rightarrow f_{3dB2} = \frac{1}{2\pi(R_1 \parallel R_2)C}$$

$$b. \quad \frac{V_i}{R_1 \parallel (1/sC)} + \frac{V_i - V_o}{R_2} = 0$$

$$\frac{V_i}{\left(\frac{R_1}{1 + sR_1C} \right)} + \frac{V_i}{R_2} = \frac{V_o}{R_2}$$

$$V_i \left[\frac{R_2}{R_1} \cdot (1 + sR_1C) + 1 \right] = V_o$$

$$\frac{V_i}{R_1} \cdot [R_2 + R_1 + sR_1R_2C] = V_o$$

$$\frac{V_o}{V_i} = \frac{R_2 + R_1}{R_1} \cdot [1 + s(R_1 \parallel R_2)C]$$

$$\Rightarrow \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1} \right) [1 + s(R_1 \parallel R_2)C]$$

$$\Rightarrow f_{3dB} = \frac{1}{2\pi(R_1 \parallel R_2)C}$$

15.13

$$a. \quad \frac{V_i}{R_1 + (1/sC_1)} = \frac{-V_o}{R_2 \parallel (1/sC_2)}$$

$$V_i \left(\frac{sC_1}{1 + sR_1C_1} \right) = -V_o \left(\frac{1 + sR_2C_2}{sC_2} \right)$$

$$\frac{V_o}{V_i} = \frac{-sR_2C_1}{(1 + sR_1C_1)(1 + sR_2C_2)}$$

$$= \frac{-sR_2C_1}{1 + sR_1C_1 + sR_2C_2 + s^2R_1R_2C_1C_2}$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \times$$

$$\times \left[\frac{sC_1}{\frac{1}{R_1} + sC_1 \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1} \right) + s^2R_2C_1C_2} \right]$$

or

$$T(s) = \frac{V_o}{V_i}$$

$$= -\frac{R_2}{R_1} \cdot \left[\frac{1}{\frac{1}{sR_1C_1} + \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1} \right) + sR_2C_2} \right]$$

b.

$$|T(j\omega)| = -\frac{R_2}{R_1} \times$$

$$\times \frac{1}{\left\{ \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1} \right)^2 + \left(\omega R_2C_2 - \frac{1}{\omega R_1C_1} \right)^2 \right\}^{1/2}}$$

when $\left(\omega R_2C_2 - \frac{1}{\omega R_1C_1} \right) = 0$, we want

$$|T(j\omega)| = 50 = \frac{R_2}{R_1} \cdot \frac{1}{\left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1} \right)}$$

At the 3 - dB frequencies, we want

$$\left(\omega R_2C_2 - \frac{1}{\omega R_1C_1} \right) = \pm \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1} \right)$$

For $f = 5$ kHz, use + sign and for $f = 200$ Hz, use - sign.

$$\omega_1 = 2\pi(200) = 1257$$

$$\omega_2 = 2\pi(5 \times 10^3) = 3.142 \times 10^4$$

Define $\tau_2 = R_2C_2$ and $\tau_1 = R_1C_1$

Then

$$50 = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{\tau_2}{\tau_1}} \quad (1)$$

$$\left(\omega_2\tau_2 - \frac{1}{\omega_2\tau_1} \right) = + \left(1 + \frac{\tau_2}{\tau_1} \right) \quad (2)$$

$$\left(\omega_1\tau_2 - \frac{1}{\omega_1\tau_1} \right) = - \left(1 + \frac{\tau_2}{\tau_1} \right) \quad (3)$$

From (2)

$$\frac{\omega_2^2\tau_1\tau_2 - 1}{\omega_2\tau_1} = \frac{\tau_1 + \tau_2}{\tau_1}$$

or

$$\omega_2\tau_1\tau_2 - \frac{1}{\omega_2} = \tau_1 + \tau_2$$

$$\tau_1(\omega_2\tau_2 - 1) = \frac{1}{\omega_2} + \tau_2$$

So

$$r_1 = \frac{\frac{1}{\omega_2} + r_2}{\omega_2 r_2 - 1}$$

Substituting into (3), we find

$$\omega_1 r_2 - \frac{1}{\omega_1 \left[\frac{\frac{1}{\omega_2} + r_2}{\omega_2 r_2 - 1} \right]} = - \left[1 + \frac{r_2 (\omega_2 r_2 - 1)}{\frac{1}{\omega_2} + r_2} \right]$$

$$\begin{aligned} \omega_1 r_2 \left[\frac{1}{\omega_2} + r_2 \right] - \frac{1}{\omega_1} (\omega_2 r_2 - 1) \\ = - \left[\left(\frac{1}{\omega_2} + r_2 \right) + r_2 (\omega_2 r_2 - 1) \right] \end{aligned}$$

$$\begin{aligned} \frac{\omega_1}{\omega_2} \cdot r_2 + \omega_1 r_2^2 - \frac{\omega_2}{\omega_1} \cdot r_2 + \frac{1}{\omega_1} \\ = - \frac{1}{\omega_2} - r_2 - \omega_2 r_2^2 + r_2 \end{aligned}$$

$$\begin{aligned} (\omega_1 + \omega_2) r_2^2 + \left(\frac{\omega_1}{\omega_2} - \frac{\omega_2}{\omega_1} \right) r_2 + \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) = 0 \\ (3.2677 \times 10^4) r_2^2 - 24.96 r_2 + 8.273 \times 10^{-4} = 0 \end{aligned}$$

$$\begin{aligned} r_2 = \frac{24.96}{2(3.2677 \times 10^4)} \\ \pm \frac{\sqrt{(24.96)^2 - 4(3.2677 \times 10^4)(8.273 \times 10^{-4})}}{2(3.2677 \times 10^4)} \end{aligned}$$

Since ω_2 is large, r_2 should be small so use minus sign:

$$r_2 = 3.47 \times 10^{-5}$$

Then

$$r_1 = \frac{3.18 \times 10^{-5} + 3.47 \times 10^{-5}}{9.09 \times 10^{-2}} \Rightarrow r_1 = 7.32 \times 10^{-4}$$

Now

$$50 = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{3.47 \times 10^{-5}}{7.32 \times 10^{-4}}}$$

Then

$$\frac{R_2}{R_1} = 52.37 \text{ or } \underline{R_2 = 524 \text{ k}\Omega}$$

Also


$$r_1 = R_1 C_1 \text{ so that } C_1 = 0.0732 \mu\text{F}$$

$$r_2 = R_2 C_2 \text{ so that } C_2 = 66.3 \text{ pF}$$

15.14

$$\text{Gain} = 10 \text{ dB} \Rightarrow \text{Gain} = 3.162$$

For example, we may have

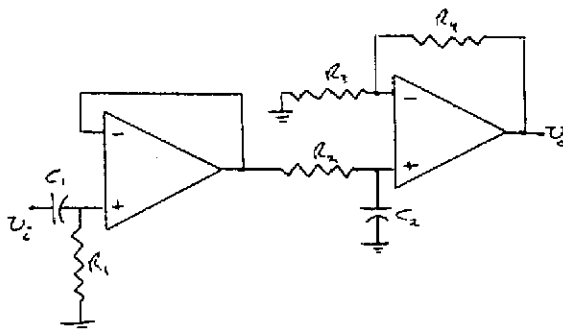

$$\text{Want } \frac{R_4}{R_3} = 2.162$$

For example, let $R_3 = 50 \text{ k}\Omega$,

$$R_4 = 108 \text{ k}\Omega$$

$$f_1 = \frac{1}{2\pi R_1 C_1} = 200$$

So

$$R_1 C_1 = \frac{1}{2\pi(200)} = 0.796 \times 10^{-3}$$

For example, let $R_1 = 200 \text{ k}\Omega \Rightarrow$ A large input resistance

$$C_1 = 0.00398 \mu\text{F}$$

$$f_2 = \frac{1}{2\pi R_2 C_2} = 50 \times 10^3$$

$$\Rightarrow R_2 C_2 = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

For example, let

$$R_2 = 10 \text{ k}\Omega \text{ and } C_2 = 318 \text{ pF}$$

15.15

$$f_c = 100 \text{ kHz}$$

$$R_{eq} = \frac{1}{f_c C}$$

$$\text{a. For } C = 1 \text{ pF, } R_{eq} = 10 \text{ M}\Omega$$

$$\text{b. For } C = 10 \text{ pF, } R_{eq} = 1 \text{ M}\Omega$$

$$\text{c. For } C = 30 \text{ pF, } R_{eq} = 333 \text{ k}\Omega$$

15.16

- a. From Equation (15.28),

$$Q = \frac{V_1 - V_2}{R_{eq}} \cdot T_C$$

and $f_C = 100 \text{ kHz}$ so that $T_C = \frac{1}{100 \times 10^3} \Rightarrow 10 \mu\text{s}$

Now

$$R_{eq} = \frac{1}{f_C C} = \frac{1}{(100 \times 10^3)(10 \times 10^{-12})} \Rightarrow 1 \text{ M}\Omega$$

So

$$Q = \frac{(2 - 1)(10 \times 10^{-6})}{10^6} = 10 \times 10^{-12} \text{ C}$$

or

$$\underline{Q = 10 \text{ pC}}$$

$$\text{b. } I_{eq} = \frac{Q}{T_C} = \frac{10 \times 10^{-12}}{10 \times 10^{-6}} \text{ or } \underline{I_{eq} = 1 \mu\text{A}}$$

c.

$Q = CV$ so find the time that V_0 reaches 99% of its full value.

$$V_0 = V_1(1 - e^{-t/\tau}) \text{ where } \tau = RC$$

$$\text{Then } 0.99 = 1 - e^{-t/\tau} \text{ or } e^{-t/\tau} = 0.01$$

$$\text{or } t = \tau \ln(100)$$

$$\tau = RC = (10^3)(10 \times 10^{-12}) = 10^{-8} \text{ s}$$

Then

$$\underline{t = 4.61 \times 10^{-8} \text{ s}}$$

15.17

$$\text{Low frequency gain} = -10 \Rightarrow \frac{C_1}{C_2} = 10$$

$$f_{3dB} = 10 \times 10^3 \text{ Hz} = \frac{f_C C_2}{2\pi C_F}$$

Set

$$f_C = 10 f_{3dB} = 100 \text{ kHz}$$

Then

$$\frac{C_2}{C_F} = \frac{2\pi(10 \times 10^3)}{100 \times 10^3} = 0.628$$

The largest capacitor is C_1 , so let

$$\underline{C_1 = 30 \text{ pF}}$$

Then

$$\underline{C_2 = 3 \text{ pF}}$$

and

$$\underline{C_F = 4.78 \text{ pF}}$$

15.18

- a. Time constant
- $= R_{eq} \cdot C_F = \tau$
- where

$$R_{eq} = \frac{1}{f_C C_1} = \frac{1}{(100 \times 10^3)(5 \times 10^{-12})} = 2 \times 10^4 \Omega$$

Then

$$\tau = (2 \times 10^4)(30 \times 10^{-12})$$

or

$$\underline{\tau = 60 \mu\text{s}}$$

$$\text{b. } v_0 = -\frac{1}{\tau} \int v_1 \cdot dt$$

or

$$\Delta v_0 = \frac{(1)T_C}{\tau}, \quad T_C = \frac{1}{f_C}$$

So

$$\Delta v_0 = \frac{1}{(60 \times 10^{-6})(100 \times 10^3)}$$

or

$$\underline{\Delta v_0 = 0.167 \text{ V}}$$

- c. Now
- $\Delta v_0 = 13 = N(0.167)$

or

$$\underline{N = 78 \text{ clock pulses}}$$

15.19

Using Equation (15.41)

$$f_0 = \frac{1}{2\pi\sqrt{3}RC} = \frac{1}{2\pi\sqrt{3}(4 \times 10^3)(10 \times 10^{-9})}$$

or

$$\underline{f_0 = 2.3 \text{ kHz}}$$

$$\frac{R_2}{R} = 8 \text{ so that } R_2 = 8(4 \times 10^3)$$

$$\Rightarrow \underline{R_2 = 32 \text{ k}\Omega}$$

15.20

$$\text{a. } v_1 = \frac{R}{R + (1/sC_V)} \cdot v_0 = \left(\frac{sRC_V}{1 + sRC_V} \right) \cdot v_0$$

$$v_2 = \frac{R}{R + \frac{1}{sC}} \cdot v_1 = \left(\frac{sRC}{1 + sRC} \right) \cdot v_1$$

$$v_3 = \frac{R}{R + \frac{1}{sC}} \cdot v_2 = \left(\frac{sRC}{1 + sRC} \right) \cdot v_2$$

$$v_0 = -\frac{R_2}{R} \cdot v_3$$

Then

$$v_0 = -\frac{R_2}{R} \left(\frac{sRC}{1+sRC} \right)^2 \left(\frac{sRCV}{1+sRCV} \right) v_0$$

Set $s = j\omega$

$$1 = -\frac{R_2}{R} \left(\frac{-\omega^2 R^2 C^2}{1+2j\omega RC - \omega^2 R^2 C^2} \right) \left(\frac{j\omega RCV}{1+j\omega RCV} \right)$$

The real part of the denominator must be zero.

$$1 - \omega^2 R^2 C^2 - 2\omega^2 R^2 C C_V = 0$$

so

$$\omega_0 = \frac{1}{R\sqrt{C(C+2C_V)}}$$

$$b. f_{0,\max} = \frac{1}{2\pi(10^4)\sqrt{(10^{-11})(10^{-11} + 2[10^{-11}])}}$$

$$f_{0,\max} = 919 \text{ kHz}$$

$$f_{0,\min} = \frac{1}{2\pi(10^4)\sqrt{(10^{-11})(10^{-11} + 2[50 \times 10^{-12}])}}$$

$$f_{0,\min} = 480 \text{ kHz}$$

15.21

From Equation (15.46)

$$f_0 = \frac{1}{2\pi\sqrt{6}RC}$$

$$\text{so } R = \frac{1}{2\pi\sqrt{6}(80 \times 10^3)(100 \times 10^{-12})} \text{ or } R = 8.12 \text{ k}\Omega$$

We need

$$\frac{R_2}{R} = 29$$

so that

$$R_2 = 236 \text{ k}\Omega$$

15.22

$$\frac{v_0 - v_1}{\frac{1}{sC}} = \frac{v_1}{R} + \frac{v_1 - v_2}{\frac{1}{sC}} \quad (1)$$

$$\text{or } (v_0 - v_1)sC = \frac{v_1}{R} + (v_1 - v_2)sC$$

$$\frac{v_1 - v_2}{\frac{1}{sC}} = \frac{v_1}{R} + \frac{v_2}{\frac{1}{sC} + R} \quad (2)$$

$$\text{or } (v_1 - v_2)sC = \frac{v_1}{R} + \frac{v_2(sC)}{1+sRC}$$

$$\frac{\frac{v_2}{sC}}{\frac{1}{sC} + R} = -\frac{v_0}{R_2} \quad (3)$$

$$\text{or } \frac{v_2 sC}{1+sRC} = -\frac{v_0}{R_2}$$

so

$$v_2 = \frac{-v_0}{sR_2C} (1+sRC)$$

From (2)

$$v_1(sC) = v_2 \left[sC + \frac{1}{R} + \frac{sC}{1+sRC} \right]$$

or

$$v_1 = -\frac{v_0(1+sRC)}{sR_2C} \cdot \left[1 + \frac{1}{sRC} + \frac{1}{1+sRC} \right]$$

From (1)

$$v_0(sC) = v_1 \left[sC + \frac{1}{R} + sC \right] - v_2(sC)$$

Then

$$\begin{aligned} v_0 &= \left[2 + \frac{1}{sRC} \right] \left[\frac{-v_0(1+sRC)}{sR_2C} \right] \times \\ &\quad \times \left[\frac{1+sRC}{sRC} + \frac{1}{1+sRC} \right] + \frac{v_0}{sR_2C} \cdot (1+sRC) \\ -1 &= \left[\frac{1+2sRC}{sRC} \right] \left[\frac{1+sRC}{sR_2C} \right] \left[\frac{(1+sRC)^2 + sRC}{(sRC)(1+sRC)} \right] \\ &\quad - \frac{1+sRC}{sR_2C} \\ -1 &= \frac{(1+2sRC)(1+2sRC+s^2R^2C^2+sRC)}{(sRC)^2(sR_2C)} \\ &\quad - \frac{(1+sRC)(sRC)^2}{(sRC)^2(sR_2C)} \end{aligned}$$

Set $s = j\omega$

$$\begin{aligned} -1 &= \frac{(1+2j\omega RC)(1+3j\omega RC + \omega^2 R^2 C^2)}{(-\omega^2 R^2 C^2)(j\omega R_2 C)} \\ &\quad - \frac{(1+j\omega RC)(-\omega^2 R^2 C^2)}{(-\omega^2 R^2 C^2)(j\omega R_2 C)} \end{aligned}$$

The real part of the numerator must be zero.

$$1 - \omega^2 R^2 C^2 - 6\omega^2 R^2 C^2 + \omega^2 R^2 C^2 = 0$$

$$6\omega^2 R^2 C^2 = 1$$

so that

$$\omega_0 = \frac{1}{\sqrt{6}RC}$$

Condition for oscillation:

$$-1 = \frac{2j\omega RC + 3j\omega RC - 2j\omega^3 R^3 C^3 + j\omega^3 R^3 C^3}{(-\omega^2 R^2 C^2)(j\omega R_2 C)}$$

$$1 = \frac{5 - \omega^2 R^2 C^2}{(\omega RC)(\omega R_2 C)}$$

But

$$\omega = \omega_0 = \frac{1}{\sqrt{6}RC}$$

Then

$$1 = \frac{5 - \frac{1}{6}}{\frac{(RC)(R_2C)}{6R^2C^2}} = \frac{\left(5 - \frac{1}{6}\right)(6R^2C^2)}{RR_2C^2}$$

$$1 = \frac{\left(\frac{29}{6}\right)(6R)}{R_2} \text{ or } \frac{R_2}{R} = 29$$

15.23

a.

$$v_{01} = \left(1 + \frac{R_{F1}}{R_{A1}}\right) \left(\frac{\frac{1}{sC_1}}{\frac{1}{sC_1} + R_1}\right) \cdot v_0 \quad (1)$$

$$v_{02} = \left(1 + \frac{R_{F2}}{R_{A2}}\right) \left(\frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + R_2}\right) \cdot v_{01} \quad (2)$$

$$v_{03} = \left(\frac{R_{A3} \parallel \frac{1}{sC_3}}{R_{A3} \parallel \frac{1}{sC_3} + R_3}\right) \cdot v_{02} \quad (3)$$

$$v_0 = -\frac{R_{F3}}{R_{A3}} \cdot v_{03} \quad (4)$$

With all resistors equal and all capacitors equal, we find:

$$v_{01} = (2) \left(\frac{1}{1 + sRC}\right) v_0 \quad (1)$$

$$v_{02} = (2) \left(\frac{1}{1 + sRC}\right) v_{01} \quad (2)$$

$$\begin{aligned} v_{03} &= (2) \left(\frac{\frac{R}{1 + sRC}}{\frac{R}{1 + sRC} + R}\right) v_{02} \\ &= \left[\frac{R}{R + R(1 + sRC)}\right] v_{02} \\ v_{03} &= \left(\frac{1}{2 + sRC}\right) v_{02} \end{aligned} \quad (3)$$

and

$$v_0 = -v_{03} \quad (4)$$

Then

$$v_0 = -\left(\frac{1}{2 + sRC}\right) (2) \left(\frac{1}{1 + sRC}\right) (2) \left(\frac{1}{1 + sRC}\right) v_0$$

Let $s = j\omega$

$$(2 + j\omega RC)(1 + j\omega RC)(1 + j\omega RC) = -4$$

$$(2 + j\omega RC)(1 + 2j\omega RC - \omega^2 R^2 C^2) = -4 \quad (A)$$

The imaginary term on the left must be zero.

$$4j\omega RC + j\omega RC - j\omega^3 R^3 C^3 = 0$$

$$\omega RC(5 - \omega^2 R^2 C^2) = 0$$

or

$$\omega = \frac{\sqrt{5}}{RC} \quad (\text{Not the same as in book})$$

15.24

a.

$$\frac{v_0 - v_{01}}{R} = \frac{v_{01}}{\left(\frac{1}{sC}\right)} + \frac{v_{01} - v_{02}}{R} \quad (1)$$

$$\frac{v_{01} - v_{02}}{R} = \frac{v_{02}}{\left(\frac{1}{sC}\right)} + \frac{v_{02} - v_{03}}{R} \quad (2)$$

$$\frac{v_{02} - v_{03}}{R} = \frac{v_{03}}{\left(\frac{1}{sC}\right)} + \frac{v_{03}}{R} \quad (3)$$

$$v_0 = -\frac{R_F}{R} \cdot v_{03} \quad (4)$$

We can write the equations as

$$v_0 - v_{01} = v_{01}(sRC) + v_{01} - v_{02} \quad (1)$$

$$v_{01} - v_{02} = v_{02}(sRC) + v_{02} - v_{03} \quad (2)$$

$$v_{02} - v_{03} = v_{03}(sRC) + v_{03} \quad (3)$$

and

$$v_0 = -\frac{R_F}{R} \cdot v_{03} \quad (4)$$

Combining terms, we find

$$v_0 = v_{01}(2 + sRC) - v_{02} \quad (1)$$

$$v_{01} = v_{02}(2 + sRC) - v_{03} \quad (2)$$

$$v_{02} = v_{03}(2 + sRC) \quad (3)$$

and

$$v_0 = -\frac{R_F}{R} \cdot v_{03} \quad (4)$$

Combining Equations (3) and (2)

$$v_{01} = v_{03}(2 + sRC)^2 - v_{03} = v_{03}[(2 + sRC)^2 - 1] \quad (2)$$

Then Equation (1) is

$$\begin{aligned} v_0 &= v_{03}[(2 + sRC)^2 - 1](2 + sRC) \\ &\quad - v_{03}(2 + sRC) \end{aligned}$$

Using Equation (4), we find

$$-\frac{R_F}{R} \cdot v_{03} = v_{03} \{ [(2 + sRC)^2 - 1](2 + sRC) - (2 + sRC) \}$$

To find the frequency of oscillation, set $s = j\omega$ and set the imaginary part of the right side of the equation to zero.

We will have

$$-\frac{R_F}{R} = (2 + j\omega RC)[4 + 4j\omega RC - \omega^2 R^2 C^2 - 1 - 1]$$

Then

$$j\omega RC(2 - \omega^2 R^2 C^2) + 8j\omega RC = 0$$

or

$$j\omega RC[2 - \omega^2 R^2 C^2 + 8] = 0$$

Then the frequency of oscillation is

$$f_0 = \frac{1}{2\pi} \cdot \frac{\sqrt{10}}{RC}$$

The condition to sustain oscillations is determined from

$$-\frac{R_F}{R} = 2[2 - \omega^2 R^2 C^2] - 4\omega^2 R^2 C^2$$

or

$$-\frac{R_F}{R} = 4 - 6\omega^2 R^2 C^2$$

Setting $\omega^2 = \frac{10}{R^2 C^2}$, we have

$$-\frac{R_F}{R} = 4 - 6(10)$$

or

$$\frac{R_F}{R} = 56$$

b. For $R = 5 \text{ k}\Omega$ and $f_0 = 5 \text{ kHz}$, we find

$$C = \frac{\sqrt{10}}{2\pi(5 \times 10^3)(5 \times 10^3)} \Rightarrow C = 0.02 \text{ }\mu\text{F}$$

$$\text{and } R_F = 56(5) \Rightarrow R_F = 280 \text{ k}\Omega$$

15.25

a. We can write

$$v_A = \left(\frac{R_1}{R_1 + R_2} \right) v_0 \text{ and } v_B = \left(\frac{Z_p}{Z_p + Z_s} \right) v_0$$

$$\text{where } Z_p = R_B \parallel \frac{1}{sC_B} = \frac{R_B}{1 + sR_B C_B}$$

$$\text{and } Z_s = R_A + \frac{1}{sC_A} = \frac{1 + sR_A C_A}{sC_A}$$

Setting $v_A = v_B$, we have

$$\frac{R_1}{R_1 + R_2} = \frac{\frac{R_B}{1 + sR_B C_B}}{\frac{R_B}{1 + sR_B C_B} + \frac{1 + sR_A C_A}{sC_A}}$$

$$\frac{R_1}{R_1 + R_2} = \frac{sR_B C_A}{sR_B C_A + (1 + sR_A C_A)(1 + sR_B C_B)} \quad (1)$$

To find the frequency of oscillation, set $s = j\omega$ and set the real part of the denominator on the right side of Equation (1) equal to zero.

The denominator term is

$$j\omega R_B C_A + (1 + j\omega R_A C_A)(1 + j\omega R_B C_B)$$

or

$$j\omega R_B C_A + 1 + j\omega R_A C_A + j\omega R_B C_B - \omega^2 R_A R_B C_A C_B \quad (2)$$

Then from (2), we must have

$$1 - \omega^2 R_A R_B C_A C_B = 0$$

or

$$f_0 = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

b. To find the condition for sustained oscillation, combine Equations (1) and (2). Then

$$\frac{R_1}{R_1 + R_2} = \frac{j\omega R_B C_A}{j\omega R_B C_A + j\omega R_A C_A + j\omega R_B C_B}$$

or

$$1 + \frac{R_2}{R_1} = 1 + \frac{R_A}{R_B} + \frac{C_B}{C_A}$$

Then

$$\frac{R_2}{R_1} = \frac{R_A}{R_B} + \frac{C_B}{C_A}$$

15.26

a. We can write

$$v_A = \left(\frac{R_1}{R_1 + R_2} \right) v_0$$

and

$$v_B = \left(\frac{R \parallel sL}{R \parallel sL + R + sL} \right) v_0$$

Setting $v_A = v_B$, we have

$$\frac{R_1}{R_1 + R_2} = \left[\frac{\frac{sRL}{R + sL}}{\frac{sRL}{R + sL} + R + sL} \right] v_0$$

$$\frac{R_1}{R_1 + R_2} = \frac{sRL}{sRL + (R + sL)^2} \quad (1)$$

To find the frequency of oscillation, set $s = j\omega$ and set the real part of the denominator on the right side of Equation (1) equal to zero.

The denominator term is:

$$j\omega RL + (R + j\omega L)^2$$

or

$$j\omega RL + R^2 + 2j\omega RL - \omega^2 L^2 \quad (2)$$

Then

$$R^2 - \omega_0^2 L^2 = 0$$

or

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{R}{L}}$$

b. To find the condition for sustained oscillations, combine Equations (1) and (2).

$$\frac{R_1}{R_1 + R_2} = \frac{j\omega RL}{j\omega RL + 2j\omega RL} = \frac{1}{3}$$

Then

$$1 + \frac{R_2}{R_1} = 3$$

so that

$$\frac{R_2}{R_1} = 2$$

15.27

From Equation (15.52(b))

$$f_0 = \frac{1}{2\pi RC}$$

or

$$RC = \frac{1}{2\pi f} = \frac{1}{2\pi(80 \times 10^3)}$$

$$RC \approx 2 \times 10^{-6}$$

Set $R = 20 \text{ k}\Omega$ and $C = 100 \text{ pF}$

We must have

$$\frac{R_2}{R_1} = 2$$

Set $R_2 = 40 \text{ k}\Omega$ and $R_1 = 20 \text{ k}\Omega$, for example.

15.28

From Equation (15.59)

$$f_0 = \frac{1}{2\pi \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}}$$

and from Equation (15.61)

$$\frac{C_2}{C_1} = g_m R$$

Now,

$$g_m = 2\sqrt{k_n I_{DQ}} = 2\sqrt{(0.5)(1)} = 1.414 \text{ mA/V}$$

We have $C_1 = 0.01 \text{ }\mu\text{F}$, $R = 4 \text{ k}\Omega$, $f_0 = 400 \text{ kHz}$

So

$$C_2 = g_m R C_1 = (1.414)(4)(0.01)$$

or

$$C_2 = 0.0566 \text{ }\mu\text{F}$$

and

$$400 \times 10^3 = \frac{1}{2\pi \sqrt{L \left[\frac{(0.01)(0.0566)}{0.01 + 0.0566} \right]}} \times 10^{-6}$$

$$L(8.5 \times 10^{-9}) = \left[\frac{1}{2\pi(400 \times 10^3)} \right]^2 = 1.58 \times 10^{-13}$$

Then

$$L = 18.6 \text{ }\mu\text{H}$$

15.29

$$V_{\pi} = -V_0$$

$$\frac{V_0}{\left(\frac{1}{sC_2}\right)} + \frac{V_0}{R_L} + \frac{V_0 - V_1}{\left(\frac{1}{sC_1}\right)} = g_m V_{\pi} = -g_m V_0$$

$$V_0 \left[sC_2 + sC_1 + \frac{1}{R_L} + g_m \right] = V_1 (sC_1) \quad (1)$$

$$\frac{V_1}{sL} + \frac{V_0 - V_1}{\left(\frac{1}{sC_1}\right)} + g_m V_{\pi} = 0 \quad (2)$$

$$V_1 \left(\frac{1}{sL} + sC_1 \right) = V_0 (sC_1 + g_m)$$

$$V_1 = \frac{V_0 (sC_1 + g_m)}{\left(\frac{1}{sL} + sC_1 \right)}$$

Then

$$V_0 \left[s(C_1 + C_2) + \frac{1}{R_L} + g_m \right] = \frac{V_0 (sC_1) (sC_1 + g_m)}{\left(\frac{1}{sL} + sC_1 \right)}$$

$$\left[s(C_1 + C_2) + \frac{1}{R_L} + g_m \right] \left(\frac{1}{sL} + sC_1 \right) = sC_1 (sC_1 + g_m)$$

$$\frac{C_1 + C_2}{L} + s^2 C_1 (C_1 + C_2) + \frac{1}{sR_L L} + \frac{sC_1}{R_L} + sg_m C_1 + \frac{g_m}{sL} = s^2 C_1^2 + sg_m C_1$$

$$\frac{C_1 + C_2}{L} + s^2 C_1 C_2 + \frac{1}{sR_L L} + \frac{sC_1}{R_L} + \frac{g_m}{sL} = 0$$

Set $s = j\omega$

$$\frac{C_1 + C_2}{L} - \omega^2 C_1 C_2 + \frac{1}{j\omega R_L L} + \frac{j\omega C_1}{R_L} + \frac{g_m}{j\omega L} = 0$$

Then

$$\omega^2 = \frac{C_1 + C_2}{C_1 C_2 L} \Rightarrow \omega_0 = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

and

$$\frac{g_m}{\omega L} + \frac{1}{\omega R_L L} = \frac{\omega C_1}{R_L}$$

Then

$$\frac{g_m}{L} + \frac{1}{R_L L} = \frac{(C_1 + C_2) C_1}{C_1 C_2 L R_L}$$

$$g_m + \frac{1}{R_L} = \frac{C_1 + C_2}{C_2 R_L}$$

$$g_m R_L + 1 = \frac{C_1}{C_2} + 1 \text{ or } \underline{\underline{\frac{C_1}{C_2} = g_m R_L}}$$

15.30

a.

$$\frac{V_0}{sL_1} + \frac{V_0}{R} + g_m V_{\pi} + \frac{V_0}{\frac{1}{sC} + sL_2} = 0 \quad (1)$$

$$V_{\pi} = \left(\frac{sL_2}{\frac{1}{sC} + sL_2} \right) V_0 \quad (2)$$

Then

$$V_0 \left\{ \frac{1}{sL_1} + \frac{1}{R} + \frac{sC}{1 + s^2 L_2 C} + \frac{g_m (s^2 L_2 C)}{1 + s^2 L_2 C} \right\} = 0$$

$$\left\{ \frac{R(1 + s^2 L_2 C) + (sL_1)(1 + s^2 L_2 C)}{(sRL_1)(1 + s^2 L_2 C)} + \frac{s^2 RL_1 C + g_m (sRL_1)(s^2 L_2 C)}{(sRL_1)(1 + s^2 L_2 C)} \right\} = 0$$

Set $s = j\omega$. Both real and imaginary parts of the numerator must be zero.

$$R(1 - \omega^2 L_2 C) + j\omega L_1(1 - \omega^2 L_2 C) - \omega^2 RL_1 C + (j\omega g_m RL_1)(-\omega^2 L_2 C) = 0$$

Real part:

$$R(1 - \omega^2 L_2 C) - \omega^2 RL_1 C = 0$$

$$R = \omega^2 RC(L_1 + L_2)$$

or

$$\omega_0 = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

b. Imaginary part:

$$j\omega L_1(1 - \omega^2 L_2 C) - j\omega g_m RL_1(\omega^2 L_2 C) = 0$$

$$L_1 = \omega^2 L_1 L_2 C + g_m RL_1(\omega^2 L_2 C)$$

$$\text{Now } \omega^2 = \frac{1}{(L_1 + L_2)}$$

$$1 = \frac{1}{C(L_1 + L_2)} [L_2 C + g_m RL_2 C]$$

$$1 = \frac{L_2}{L_1 + L_2} (1 + g_m R) \Rightarrow \frac{L_1}{L_2} = (1 + g_m R) - 1$$

or

$$\underline{\underline{\frac{L_1}{L_2} = g_m R}}$$

15.31

$$\omega_0 = 2\pi(800 \times 10^3) = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

or

$$C(L_1 + L_2) = 3.96 \times 10^{-14}$$

Also $\frac{L_1}{L_2} = g_m R$

For example, if $R = 1 \text{ k}\Omega$, then $\frac{L_1}{L_2} = (20)(1) = 20$

So

$$L_1 = 20 L_2$$

Then

$$C(21L_2) = 3.96 \times 10^{-14} \text{ or } CL_2 = 1.89 \times 10^{-15}$$

If $C = 0.01 \text{ }\mu\text{F}$

then $L_2 = 0.189 \text{ }\mu\text{H}$

and $L_1 = 3.78 \text{ }\mu\text{H}$

15.32

$$\frac{v_0 - v_1}{\left(\frac{1}{sC}\right)} = \frac{v_1}{R} + \frac{v_1 - v_B}{R} \quad (1)$$

and

$$\frac{v_B}{\left(\frac{1}{sC}\right)} + \frac{v_B - v_1}{R} = 0 \quad (2)$$

or

$$v_B \left(sC + \frac{1}{R} \right) = \frac{v_1}{R} \Rightarrow v_1 = v_B (1 + sRC)$$

From (1)

$$v_0(sC) = v_1 \left(sC + \frac{2}{R} \right) - \frac{v_B}{R}$$

or

$$\begin{aligned} v_0(sRC) &= v_B(1 + sRC)(2 + sRC) - v_B \\ &= v_B[(1 + sRC)(2 + sRC) - 1] \end{aligned}$$

Now

$$\begin{aligned} T(s) &= \left(1 + \frac{R_2}{R_1} \right) \left[\frac{sRC}{(1 + sRC)(2 + sRC) - 1} \right] \\ &= \left(1 + \frac{R_2}{R_1} \right) \left[\frac{sRC}{2 + 3sRC + s^2 R^2 C^2 - 1} \right] \end{aligned}$$

or

$$T(s) = \left(1 + \frac{R_2}{R_1} \right) \left[\frac{sRC}{s^2 R^2 C^2 + 3sRC + 1} \right]$$

$$T(j\omega) = \left(1 + \frac{R_2}{R_1} \right) \left[\frac{j\omega RC}{1 - \omega^2 R^2 C^2 + 3j\omega RC} \right]$$

Frequency of oscillation:

$$f_0 = \frac{1}{2\pi RC}$$

Condition for oscillation:

$$1 = \left(1 + \frac{R_2}{R_1} \right) \left[\frac{j\omega RC}{3j\omega RC} \right]$$

or

$$\frac{R_2}{R_1} = 2$$

15.33

$$\frac{v_0 - v_1}{sL} = \frac{v_1}{R} + \frac{v_1 - v_B}{R} \quad (1)$$

$$v_B = \left(\frac{sL}{R + sL} \right) v_1 \quad (2)$$

or

$$v_1 = \left(\frac{R + sL}{sL} \right) v_B$$

Then

$$\frac{v_0}{sL} = v_1 \left(\frac{1}{sL} + \frac{2}{R} \right) - \frac{v_B}{R}$$

or

$$\begin{aligned} \frac{v_0}{sL} &= \left(\frac{R + sL}{sL} \right) \left(\frac{1}{sL} + \frac{2}{R} \right) v_B - \frac{v_B}{R} \\ &= v_B \left\{ \left(\frac{R + sL}{sL} \right) \left(\frac{R + 2sL}{sRL} \right) - \frac{1}{R} \right\} \end{aligned} \quad (1)$$

Then

$$v_B = \frac{v_0}{sL} \cdot \frac{1}{\left\{ \frac{(R + sL)(R + 2sL) - (sL)^2}{(sL)(sRL)} \right\}}$$

Now

$$T(s) = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{sRL}{R^2 + 3sRL + 2s^2 L^2 - s^2 L^2} \right)$$

or

$$T(s) = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{sRL}{s^2 L^2 + 3sRL + R^2} \right)$$

And

$$T(j\omega) = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{j\omega RL}{R^2 - \omega^2 L^2 + 3j\omega RL} \right)$$

Frequency of oscillation: $f_0 = \frac{R}{2\pi L}$

Condition for oscillation:

$$1 = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{1}{3} \right)$$

or

$$\frac{R_2}{R_1} = 2$$

15.34

From Equation (15.65(b)), the crossover voltage is

$$v_I = -\frac{R_2}{R_1} \cdot V_{REF}$$

Let $R_2 = R_{VAR} + R_F$ where R_{VAR} is the potentiometer and R_F is the fixed resistor.

Let $V_{REF} = -5$ V, $R_F = 10$ k Ω , and $R_{VAR} = 40$ k Ω

Then we have

$$v_I = -\frac{R_F}{R_1} \cdot V_{REF} = -\left(\frac{10}{50}\right)(-5) = 1$$
 V

and

$$v_I = -\left(\frac{50}{50}\right)(-5) = 5$$
 V

15.35

$$i_{max} = \frac{10}{R_1 + R_2} = 0.1 \Rightarrow R_1 + R_2 = 100$$
 k Ω

Hysteresis width

$$\Delta V = V_{TH} - V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right)(V_H - V_L)$$

$$\text{or } 0.1 = \left(\frac{R_1}{100}\right)(20)$$

so that

$$\underline{R_1 = 0.5 \text{ k}\Omega}$$

$$\underline{R_2 = 99.5 \text{ k}\Omega}$$

15.36

$$\text{a. } V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)V_H = \left(\frac{10}{10 + 40}\right)(10)$$

$$\text{so } \underline{V_{TH} = 2 \text{ V}}$$

$$V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right)V_L = \left(\frac{10}{10 + 40}\right)(-10)$$

$$\text{so } \underline{V_{TL} = -2 \text{ V}}$$

$$\text{b. } v_I = 5 \sin \omega t$$

15.37

a. Upper crossover voltage when $v_0 = +V_P$.

Now

$$v_B = \left(\frac{R_1}{R_1 + R_2}\right)(+V_P)$$

and

$$v_A = \left(\frac{R_A}{R_A + R_B}\right)V_{REF} + \left(\frac{R_B}{R_A + R_B}\right)V_{TH}$$

$$v_A = v_B \text{ so that}$$

$$\begin{aligned} &\left(\frac{R_1}{R_1 + R_2}\right)V_P \\ &= \left(\frac{R_A}{R_A + R_B}\right)V_{REF} + \left(\frac{R_B}{R_A + R_B}\right)V_{TH} \end{aligned}$$

or

$$V_{TH} = \left(\frac{R_A + R_B}{R_1 + R_2}\right)\left(\frac{R_1}{R_B}\right)V_P - \left(\frac{R_A}{R_B}\right)V_{REF}$$

Lower crossover voltage when $v_0 = -V_P$

So

$$V_{TL} = -\left(\frac{R_A + R_B}{R_1 + R_2}\right)\left(\frac{R_1}{R_B}\right)V_P - \left(\frac{R_A}{R_B}\right)V_{REF}$$

$$\text{b. } V_{TH} = \left(\frac{10 + 20}{5 + 20}\right)\left(\frac{5}{20}\right)(10) - \left(\frac{10}{20}\right)(2)$$

$$\text{or } \underline{V_{TH} = 2 \text{ V}}$$

and

$$V_{TL} = -\left(\frac{10 + 20}{5 + 20}\right)\left(\frac{5}{20}\right)(10) - 1 \Rightarrow \underline{V_{TL} = -4 \text{ V}}$$

15.38

$$\text{a. } \frac{v_B}{R_1} = \frac{V_{REF} - v_B}{R_3} + \frac{v_0 - v_B}{R_2}$$

$$v_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_{REF}}{R_3} + \frac{v_0}{R_2}$$

$$V_{TH} = v_B \text{ when } v_0 = +V_P \text{ and } V_{TL} = v_B \text{ when } v_0 = -V_P$$

So

$$V_{TH} = \frac{\frac{V_{REF}}{R_3} + \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

and

$$V_{TL} = \frac{\frac{V_{REF}}{R_3} - \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

b.

$$\begin{aligned} V_S &= \frac{V_{REF}}{R_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \\ -5 &= \frac{-10}{10 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{10} \right)} \end{aligned}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{5} - \frac{1}{10} = 0.10$$

$$\Delta V_T = V_{TH} - V_{TL} = \frac{\frac{2V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

$$0.2 = \frac{2(12)}{R_2(0.10 + 0.10)}$$

$$\text{So } R_2 = 600 \text{ k}\Omega$$

Then

$$\frac{1}{R_1} + \frac{1}{R_2} = 0.10$$

$$\frac{1}{R_1} + \frac{1}{600} = 0.10 \Rightarrow R_1 = 10.17 \text{ k}\Omega$$

$$\text{c. } V_{TH} = -5 + 0.1 = -4.9$$

$$V_{TL} = -5 - 0.1 = -5.1$$

15.39

- a. If the saturated output voltage is $|V_P| < 6.2 \text{ V}$, then the circuit behaves as a comparator

where $|v_0| < 6.2 \text{ V}$.

If the saturated output voltage is $|V_P| > 6.2 \text{ V}$, the output will flip to either $+V_P$ or $-V_P$ and the input has no control.

- b. Same as part (a) except the curve at $v_I \approx 0$ will have a finite slope.

c.

Circuit works as a comparator as long as $v_{01} < 8.7 \text{ V}$ and $v_{02} > -3.7 \text{ V}$. Otherwise the input has no control.

15.40

- a. Switching point is when $v_0 = 0$. Then

$$v_+ = v_I \equiv V_S = \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

V_{TH} occurs when $v_0 = V_H$, then by superposition

$$v_+ = V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right) V_H + \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

or

$$V_{TH} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_H$$

V_{TL} occurs when $v_0 = V_L$, then by superposition

$$v_+ = V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right) V_L + \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

or

$$V_{TL} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_L$$

- b. For $V_{TH} = 2 \text{ V}$ and $V_{TL} = 1 \text{ V}$, then $V_S = 1.5 \text{ V}$

Now

$$2 = 1.5 + \left(\frac{10}{10 + R_2}\right)(10)$$

$$\frac{0.5}{10} = \frac{10}{10 + R_2} \Rightarrow R_2 = 190 \text{ k}\Omega$$

$$\text{Now } V_S = 1.5 = \left(\frac{190}{10 + 190}\right) V_{REF}$$

so

$$V_{REF} = 1.579 \text{ V}$$

15.41

- a. Switching point when $v_0 = 0$.

Now

$$v_+ = V_{REF} = \left(\frac{R_2}{R_1 + R_2}\right) v_I \text{ where } v_I = V_S.$$

Then

$$V_S = \left(\frac{R_1 + R_2}{R_2}\right) V_{REF} = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

Now upper crossover voltage for v_I occurs when $v_0 = V_L$ and $v_+ = V_{REF}$. Then

$$\frac{V_{TH} - V_{REF}}{R_1} = \frac{V_{REF} - V_L}{R_2}$$

$$\text{or } V_{TH} = -\frac{R_1}{R_2} \cdot V_L + V_{REF} \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{or } V_{TH} = V_S - \frac{R_1}{R_2} \cdot V_L$$

Lower crossover voltage for v_I occurs when $v_0 = V_H$ and $v_I = V_{REF}$. Then

$$\frac{V_H - V_{REF}}{R_2} = \frac{V_{REF} - V_{TL}}{R_1}$$

$$\text{or } V_{TL} = -\frac{R_1}{R_2} \cdot V_H + V_{REF} \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{or } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H$$

b. For $V_{TH} = -1$ and $V_{TL} = -2$, $V_S = -1.5$ V.

$$\text{Then } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H \Rightarrow -2 = -1.5 - \frac{R_1}{20}(12)$$

so that $R_1 = 0.833 \text{ k}\Omega$

Now

$$V_S = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

$$-1.5 = \left(1 + \frac{0.833}{20}\right) V_{REF}$$

which gives

$$\underline{V_{REF} = -1.44 \text{ V}}$$

15.42

a. $V_H = 5.6 + 0.7 = 6.3$ V and $V_L = -6.3$ V

From Equation (15.72(b)),

$$V_{TH} = -\left(\frac{R_1}{R_2}\right) V_L$$

and from Equation (15.75(b)),

$$V_{TL} = -\left(\frac{R_1}{R_2}\right) V_H$$

$$\begin{aligned} V_{TH} - V_{TL} &= 1 = -\left(\frac{R_1}{R_2}\right)(V_L - V_H) \\ &= +\left(\frac{R_1}{R_2}\right)(2)(6.3) \end{aligned}$$

$$\text{so } \frac{R_1}{R_2} = 0.07937$$

$$\text{Then } R_2 = \frac{1}{0.07937} \Rightarrow \underline{R_2 = 12.6 \text{ k}\Omega}$$

$$\text{Now } V_{TH} = -(0.07937)(-6.3) = 0.5,$$

$$V_{TL} = -0.5$$

b. For v_0 high, we have

$$I = I_D + I_R, \text{ } I \text{ is fixed for a given } R.$$

Assume v_1 varies between ± 12 V

$$I_{R(\max)} = \frac{6.3 - (-12)}{13.6} = 1.35 \text{ mA}$$

$$I_{R(\min)} = \frac{6.3 - 0.5}{13.6} = 0.426 \text{ mA}$$

$$I_{R(\text{avg})} = \frac{1.35 + 0.426}{2} = 0.888 \text{ mA}$$

Then we want

$$I = I_D(\text{avg}) + I_{R(\text{avg})} = 1 + 0.888 = 1.888 \text{ mA}$$

Then

$$R = \frac{12 - 6.3}{1.888} \Rightarrow \underline{R = 3.02 \text{ k}\Omega}$$

15.43

$$\text{a. } v_0 = V_{REF} + 2V_T$$

$$5 = V_{REF} + 2(0.7)$$

or

$$\underline{V_{REF} = 3.6 \text{ V}}$$

$$\text{b. } V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_T)$$

$$0.5 = \left(\frac{R_1}{R_1 + R_2}\right)(5)$$

$$\text{or } 1 + \frac{R_2}{R_1} = 10 \Rightarrow \frac{R_2}{R_1} = 9$$

For example, let $R_2 = 90 \text{ k}\Omega$ and $R_1 = 10 \text{ k}\Omega$

c. For $v_1 = 10$ V, and v_0 is in its low state. D_1 is on and D_2 is off.

$$\frac{v_1 - (v_1 + 0.7)}{100} + \frac{V_{REF} - v_1}{1} = \frac{v_1 - v_0}{1}$$

For $v_1 = -0.7$, then

$$\frac{10 - 0}{100} + \frac{3.6 - (-0.7)}{1} = \frac{-0.7 - v_0}{1}$$

or

$$\underline{v_0 = -5.1 \text{ V}}$$

15.44

For $v_0 = \text{High} = (V_{REF} + 2V_T)$. Then switching point is when

$$v_1 = v_B = \left(\frac{R_1}{R_1 + R_2}\right) v_0$$

$$\text{or } V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_T)$$

Lower switching point is when

$$v_1 = v_B = \left(\frac{R_1}{R_1 + R_2}\right) v_0 \text{ and } v_0 = -(V_{REF} + 2V_T)$$

so

$$V_{TL} = -\left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_T)$$

15.45

By symmetry, inverting terminal switches about zero.

Now, for v_0 low, upper diode is on.

$$V_{REF} - v_1 = v_1 - v_0$$

$$v_0 = 2v_1 - V_{REF} \text{ where } v_1 = -V_T$$

so

$$\underline{v_0 = -(V_{REF} + 2V_T)}$$

Similarly, in the high state

$$\underline{v_0 = (V_{REF} + 2V_T)}$$

Switching occurs when non-inverting terminal is zero.

So for v_o low,

$$\frac{V_{TH} - 0}{R_1} = \frac{0 - (V_{REF} + 2V_T)}{R_2}$$

$$\text{or } V_{TH} = \frac{R_1}{R_2} \cdot (V_{REF} + 2V_T)$$

By symmetry

$$V_{TL} = -\frac{R_1}{R_2} \cdot (V_{REF} + 2V_T)$$

15.46

$f_0 = 5 \text{ kHz}$ and 50% duty cycle.

From Equation (15.88)

$$f = \frac{1}{2.2R_X C_X}$$

so

$$R_X C_X = \frac{1}{2.2(5 \times 10^3)} = 9.09 \times 10^{-4}$$

Let $C_X = 0.01 \mu\text{F}$. Then $R_X = 9.09 \text{ k}\Omega$.

Also let $R_1 = R_2 = 10 \text{ k}\Omega$

15.47

Switching point occurs when

$$v_X = \left(\frac{R_1}{R_1 + R_2} \right) V_P = \left(\frac{30}{30 + 10} \right) (10) \\ \Rightarrow v_X = \pm 7.5 \text{ V}$$

b. Duty cycle = 50%

From Equation (15.83(a)), we can write

$$v_X = V_P + \left(-\frac{3}{4}V_P - V_P \right) e^{-t/\tau_X}$$

$$\text{At time } t = t_1 \text{ (one-half period)} \quad v_X = \frac{3}{4} \cdot V_P$$

So

$$\frac{3}{4} \cdot V_P = V_P - \frac{7}{4} \cdot V_P e^{-t_1/\tau_X}$$

$$1 = 7e^{-t_1/\tau_X}$$

$$\text{or } t_1 = \tau_X \ln(7)$$

One period is $T = 2\tau_X \ln(7) = 3.89\tau_X$ or the frequency is

$$f = \frac{1}{3.89R_X C_X}$$

Then

$$f = \frac{1}{(3.89)(10^4)(0.1 \times 10^{-6})} \Rightarrow f = 257 \text{ Hz}$$

15.48

Only change from Problem (15.47) is that maximum output is $\pm 15 \text{ V}$ and the v_X switching voltages are $\pm 11.25 \text{ V}$.

15.49

$$t_1 = 1.1R_X C_X = (1.1)(10^4)(0.1 \times 10^{-6})$$

$$\Rightarrow t_1 = 1.1 \text{ ms}$$

$$0 < t < t_1, \quad v_Y = 10(1 - e^{-t/\tau_Y})$$

$$\tau_Y = R_Y C_Y = (2 \times 10^3)(0.02 \times 10^{-6}) \\ = 4 \times 10^{-5} \text{ s}$$

$$\text{Now } \frac{t_1}{\tau_Y} = 2.75$$

$\Rightarrow C_Y$ completely charges during each cycle.

15.50

a. Switching voltage

$$v_X = \left(\frac{R_1 + R_3}{R_1 + R_3 + R_2} \right) \cdot V_P = \left(\frac{10 + 10}{10 + 10 + 10} \right) (\pm 10)$$

$$\text{So } v_X = \pm 6.667 \text{ V}$$

Using Equation (15.83(b))

$$v_X = V_P + \left(-\frac{2}{3}V_P - V_P \right) e^{-t_1/\tau_X} = \frac{2}{3}V_P$$

$$\text{Then } 1 - \frac{5}{3} \cdot e^{-t_1/\tau_X} = \frac{2}{3}$$

$$\frac{1}{3} = \frac{5}{3} \cdot e^{-t_1/\tau_X} \text{ or } t_1 = \tau_X \ln(5)$$

$$t_1 = \frac{T}{2} = \frac{1}{2f} = \frac{1}{2(500)} \Rightarrow t_1 = 0.001 \text{ s}$$

$$10^{-3} = \tau_X \ln(5) \Rightarrow \tau_X = 6.21 \times 10^{-4}$$

$$= R_X(0.01 \times 10^{-6})$$

$$\text{So } R_X = 62.1 \text{ k}\Omega$$

b. Switching voltage

$$v_X = \left(\frac{R_1}{R_1 + R_3 + R_2} \right) (\pm V_P)$$

$$= \left(\frac{10}{10 + 10 + 10} \right) (\pm V_P) = \frac{1}{3} \cdot (\pm V_P)$$

Using Equation (15.83(b))

$$v_X = V_P + \left(-\frac{1}{3}V_P - V_P \right) e^{-t_1/\tau_X} = \frac{1}{3}V_P$$

$$\text{Then } 1 - \frac{4}{3} \cdot e^{-t_1/\tau_X} = \frac{1}{3}$$

$$\frac{2}{3} = \frac{4}{3} \cdot e^{-t_1/\tau_X}$$

$$t_1 = \tau_X \ln(2) = (6.21 \times 10^{-4}) \ln(2) = 4.30 \times 10^{-4} \text{ s}$$

$$T = 2t_1 = 8.6 \times 10^{-4} \text{ s}$$

$$f = \frac{1}{T} \Rightarrow f = 1.16 \text{ kHz}$$

15.51

From Equation (15.92)

$$T = \tau_X \ln \left(\frac{1 + \left(\frac{V_Y}{V_P} \right)}{1 - \beta} \right)$$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 25} = 0.2857$$

so

$$100 = \tau_X \ln \left[\frac{1 + \frac{0.7}{5}}{1 - 0.2857} \right]$$

$$\text{so } \tau_X = 213.9 \mu\text{s} = R_X C_X$$

$$\text{For example, } R_X = 10 \text{ k}\Omega, C_X = 0.0214 \mu\text{F}$$

$$v_Y = \left(\frac{R_1}{R_1 + R_2} \right) V_P = \left(\frac{10}{10 + 25} \right) (5) = 1.43 \text{ V}$$

$$\text{and } v_X = 0.7 \text{ V}$$

To trigger the circuit, v_Y must be brought to a voltage less than v_X .

Therefore minimum triggering pulse is -0.73 V .

Using Equation (15.82) for $T < t < T'$

$$v_X = V_P + (-0.2857V_P - V_P)e^{-t'/\tau_X}$$

Recovery period is when $v_X = V_Y = 0.7 \text{ V}$.

$$0.7 = 5 + (-6.43)e^{-t'/\tau_X}$$

$$6.43e^{-t'/\tau_X} = 4.3$$

$$\text{or } t' = \tau_X \ln(1.495)$$

$$\tau_X = 213.9 \mu\text{s}$$

so

$$\underline{t' = T' - T = 86.1 \mu\text{s}}$$

15.52

From Equation (15.92), the pulse width

$$T = \tau_X \ln \left(\frac{1 + \left(\frac{V_Y}{V_P} \right)}{1 - \beta} \right)$$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2} = \frac{20}{20 + 20} = 0.5$$

$$\tau_X = R_X C_X = (50 \times 10^3)(0.1 \times 10^{-6}) = 5 \text{ ms}$$

$$\text{So } T = 5 \ln \left[\frac{1 + \frac{0.7}{10}}{1 - 0.5} \right] \Rightarrow \underline{T = 3.80 \text{ ms}}$$

$$\text{Recovery time} \approx 0.4\tau_X = \underline{2 \text{ ms}}$$

15.53

a. From Equation (15.95)

$$T = 1.1RC$$

$$\text{For } T = 60 \text{ s} = 1.1RC$$

$$\text{then } RC = 54.55 \text{ s}$$

For example, let

$$\underline{C = 50 \mu\text{F} \text{ and } R = 1.09 \text{ M}\Omega}$$

b. Recovery time: capacitor is discharged by current through the discharge transistor.

$$\text{If } V^+ = 5 \text{ V, then } I_B \approx \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

$$\text{If } \beta = 100, I_C = 4.3 \text{ mA}$$

$$V_C = \frac{1}{C} \int I_C dt = \frac{I_C}{C} \cdot t$$

$$\text{Capacitor has charged to } \frac{2}{3} \cdot V^+ = 3.33 \text{ V}$$

$$\text{So that } t = \frac{V_C \cdot C}{I_C} = \frac{(3.33)(50 \times 10^{-6})}{4.3 \times 10^{-3}}$$

$$\text{So recovery time } \underline{t \approx 38.7 \text{ ms}}$$

15.54

$$T = 1.1RC$$

$$5 \times 10^{-6} = 1.1RC$$

$$\text{so } RC = 4.545 \times 10^{-6} \text{ s}$$

For example, let

$$\underline{C = 100 \text{ pF} \text{ and } R = 45.5 \text{ k}\Omega}$$

From Problem (15.53), recovery time

$$t \approx \frac{V_C \cdot C}{I_C} = \frac{(3.33)(100 \times 10^{-12})}{4.3 \times 10^{-3}}$$

or

$$\underline{t = 77.4 \text{ ns}}$$

15.55

From Equation (15.102),

$$f = \frac{1}{(0.693)(20 + 2(20)) \times 10^3 \times (0.1 \times 10^{-6})}$$

$$\text{or } \underline{f = 240.5 \text{ Hz}}$$

$$\text{Duty cycle} = \frac{20 + 20}{20 + 2(20)} \times 100\% = \underline{66.7\%}$$

15.56

$$f = \frac{1}{(0.693)(R_A + 2R_B)C}$$

$$R_A = R_1 = 10 \text{ k}\Omega, R_B = R_2 + xR_3$$

$$\text{So } 10 \text{ k}\Omega \leq R_B \leq 110 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(10 + 2(110)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 627 \text{ Hz}$$

$$f_{\max} = \frac{1}{(0.693)(10 + 2(10)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 4.81 \text{ kHz}$$

$$\text{So } 627 \text{ Hz} \leq f \leq 4.81 \text{ kHz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

Now

$$\frac{10 + 10}{10 + 2(10)} \times 100\% = \underline{66.7\%}$$

and

$$\frac{10 + 110}{10 + 2(110)} \times 100\% = \underline{52.2\%}$$

$$\text{So } 52.2 \leq \text{Duty cycle} \leq 66.7\%$$

15.57

$$1 \text{ k}\Omega \leq R_A \leq 51 \text{ k}\Omega$$

$$1 \text{ k}\Omega \leq R_B \leq 51 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(1 + 2(51)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 1.40 \text{ kHz}$$

$$f_{\max} = \frac{1}{(0.693)(51 + 2(1)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 2.72 \text{ kHz}$$

$$\text{or } 1.40 \text{ kHz} \leq f \leq 2.72 \text{ kHz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$\frac{1 + 51}{1 + 2(51)} \times 100\% = \underline{50.5\%}$$

or

$$\frac{51 + 1}{51 + 2(1)} \times 100\% = \underline{98.1\%}$$

$$\text{or } \underline{50.5\% \leq \text{Duty cycle} \leq 98.1\%}$$

15.58

$$\text{a. } I_{E3} = I_{E4} = \frac{V^+ - 3V_{EB}}{R_{1A} + R_{1B}}$$

$$\text{Assume } V_{EB} = 0.7$$

$$I_{E3} = I_{E4} = \frac{22 - 3(0.7)}{25 + 25} = 0.398 \text{ mA}$$

Now

$$I_{C3} = I_{C4} = I_{C5} = I_{C6} = \left(\frac{20}{21}\right)(0.398)$$

$$\underline{I_{C3} = I_{C4} = I_{C5} = I_{C6} = 0.379 \text{ mA}}$$

$$I_{C1} = I_{C2} = \frac{0.398}{21} \left(\frac{20}{21}\right) \Rightarrow \underline{I_{C1} = I_{C2} = 0.018 \text{ mA}}$$

$$\text{b. } \underline{I_D = 0.398 \text{ mA}}, \text{ current in } D_1 \text{ and } D_2$$

$$V_{BB} = 2V_D = 2V_T \ln \left(\frac{I_D}{I_S} \right)$$

$$= 2(0.026) \ln \left(\frac{0.398 \times 10^{-3}}{10^{-13}} \right)$$

$$\text{or } V_{BB} = 1.149 \text{ V} = V_{BE7} + V_{BE8}$$

Now

$$I_{C7} \approx I_{C4} + I_{C5} + I_{E8}$$

$$I_{C4} = 0.379 \text{ mA}$$

$$I_{B9} = I_{C8} = \left(\frac{20}{21}\right) I_{E8}$$

So

$$I_{E8} = 1.05 I_{B9} = 1.05 \left(\frac{I_{C8}}{100} \right)$$

$$I_{C7} = I_{C4} + \left(\frac{100}{1.05} \right) I_{E8} + I_{E8}$$

$$= I_{C4} + (96.24) \left(\frac{21}{20} \right) I_{C8}$$

$$\text{So } I_{C7} = 0.379 \text{ mA} + 101 I_{C8}$$

and

$$V_{BE7} = V_T \ln \left(\frac{I_{C7}}{I_S} \right); V_{BE8} = V_T \ln \left(\frac{I_{C8}}{I_S} \right)$$

Then

$$1.149 = 0.026 \left[\ln \left(\frac{I_{C7}}{I_S} \right) + \ln \left(\frac{I_{C8}}{I_S} \right) \right]$$

$$44.19 = \ln \left[\frac{I_{C8}(0.379 \times 10^{-3}) + 101 I_{C8}}{(10^{-13})^2} \right]$$

$$(10^{-13})^2 \exp(44.19) = 101 I_{C8}^2 + 3.79 \times 10^{-4} I_{C8}$$

$$1.554 \times 10^{-7} = 101 I_{C8}^2 + 3.79 \times 10^{-4} I_{C8}$$

$$I_{C8} = \frac{-3.79 \times 10^{-4}}{2(101)} \pm \frac{\sqrt{(3.79 \times 10^{-4})^2 + 4(101)(1.554 \times 10^{-7})}}{2(101)}$$

$$\underline{I_{C8} = 37.4 \mu\text{A}}$$

$$I_{C7} = 0.379 + 101(0.0374) \Rightarrow \underline{I_{C7} = 4.16 \text{ mA}}$$

$$I_{C9} = 4.16 - 0.379 - 0.0374 \left(\frac{21}{20} \right)$$

$$\underline{I_{C9} = 3.74 \text{ mA}}$$

$$\text{c. } P = (0.398 + 0.398 + 4.16)(22) \Rightarrow \underline{P = 109 \text{ mW}}$$

15.59

a. From Figure 15.47, 3.7 W to the loadb. $V^+ \approx 19$ V

c. $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L \bar{P}} = \sqrt{2(10)(3.7)} \Rightarrow \underline{V_P = 8.6 \text{ V}}$$

15.60

$$\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$$

$$\text{so } V_P = \sqrt{2R\bar{P}} = \sqrt{2(10)(20)} = 20 \text{ V}$$

peak-to-peak output voltage

Maximum output voltage of each op-amp = ± 10 V. Current is $(20/10) = 2$ A. Bias op-amps at ± 12 V.

For A_1 , $\frac{v_{01}}{v_I} = \left(1 + \frac{R_2}{R_1}\right) = 15 \Rightarrow \frac{R_2}{R_1} = 14$

For A_2 , $\left|\frac{v_{02}}{v_I}\right| = \frac{R_4}{R_3} = 15$

For example, let $R_1 = R_3 = 10 \text{ k}\Omega$, and $R_2 = 140 \text{ k}\Omega$ and $R_4 = 150 \text{ k}\Omega$.

15.61

a. $v_{01} = iR_2 + v_I$ where $i = \frac{v_I}{R_1}$

Then

$$v_{01} = v_I \left(1 + \frac{R_2}{R_1}\right)$$

Now

$$v_{02} = -iR_3 = -v_I \left(\frac{R_3}{R_1}\right)$$

So

$$v_L = v_{01} - v_{02} = v_I \left(1 + \frac{R_2}{R_1}\right) - \left[-v_I \left(\frac{R_3}{R_1}\right)\right]$$

$$A_v = \frac{v_L}{v_I} = 1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}$$

b. Want $A_v = 10 \Rightarrow \frac{R_2}{R_1} + \frac{R_3}{R_1} = 9$

Also want $\left(1 + \frac{R_2}{R_1}\right) = \frac{R_3}{R_1}$

Then $\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) = 9$ so $\frac{R_2}{R_1} = 4$

For $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$

and

$$\frac{R_3}{R_1} = 5 \text{ so } \underline{R_3 = 250 \text{ k}\Omega}$$

c. $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L \bar{P}} = \sqrt{2(20)(10)} = 20 \text{ V}$$

So peak values of output voltages are

$$|v_{01}| = |v_{02}| = 10 \text{ V}$$

$$\text{Peak load current} = \frac{20}{20} = 1 \text{ A}$$

15.62

a. $v_{01} = \left(1 + \frac{R_2}{R_1}\right)v_I$

$$v_{02} = -\frac{R_4}{R_3} \cdot v_{01} = -\frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right)v_I$$

$$v_L = v_{01} - v_{02} = \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right)v_I$$

so

$$A_v = \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right)$$

b. Want $\left(1 + \frac{R_2}{R_1}\right)v_I = |v_{01}| = |v_{02}| \Rightarrow \underline{R_4 = R_3}$

Then

$$\left(1 + \frac{R_2}{R_1}\right)(2) = 15 \Rightarrow \underline{\frac{R_2}{R_1} = 6.5}$$

c. $\bar{P} = \frac{1}{2} \cdot \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L \bar{P}} = \sqrt{2(8)(50)} = 28.3 \text{ V}$$

= peak-to-peak load voltage

Then

$$\underline{|v_{01}| = |v_{02}| = 14.15 \text{ V}}$$

$$\text{Load current} = \frac{28.3}{8} = \underline{3.54 \text{ A}}$$

15.63

$$\text{Line regulation} = \frac{\Delta V_0}{\Delta V^+}$$

Now

$$\Delta I = \frac{\Delta V^+}{R_1} \text{ and } \Delta V_Z = r_Z \cdot \Delta I \text{ and } \Delta V_0 = 10 \Delta V_Z$$

So

$$\Delta V_0 = 10 \cdot r_Z \cdot \frac{\Delta V^+}{R_1}$$

So

$$\text{Line regulation} = \frac{\Delta V_0}{\Delta V^+} = \frac{10(15)}{9300} \Rightarrow 1.61\%$$

15.64

$$R_{of} = -\frac{\Delta V_o}{\Delta I_o}$$

$$\text{So } R_{of} = \frac{-(-10 \times 10^{-3})}{1}$$

or

$$R_{of} = 10 \text{ m}\Omega$$

15.65

For $V_o = 8 \text{ V}$

$$V^+(\text{min}) = V_o + I_o(\text{max})R_{11} + V_{BE11} \\ + V_{BE10} + V_{EB5}$$

This assumes $V_{BC5} = 0$.

Then

$$V^+(\text{min}) = 8 + (0.1)(1.9) + 0.6 + 0.6 + 0.6$$

$$\underline{V^+(\text{min}) = 9.99 \text{ V}}$$

15.66

$$\text{a. } I_{C3} = I_{C5} = \frac{V_Z - 3V_{BE}(\text{npn})}{R_1 + R_2 + R_3}$$

$$I_{C3} = I_{C5} = \frac{6.3 - 3(0.6)}{0.576 + 3.4 + 3.9} = 0.571 \text{ mA}$$

$$I_{C8} = \frac{1}{2} \left(\frac{0.6}{2.84} \right) = 0.106 \text{ mA}$$

Neglecting current in Q_9 , total collector current and emitter current in Q_5 is

$$0.571 + 0.106 = 0.677$$

Now

$$I_{Z2}R_4 + V_{EB4} = V_{EB5}$$

$$V_{EB4} = V_T \ln \left(\frac{I_{Z2}}{I_S} \right)$$

$$V_{EB5} = V_T \ln \left(\frac{I_{C5}}{2I_S} \right)$$

$$\text{Then } I_{Z2}R_4 = V_T \ln \left(\frac{I_{C5}}{2I_{Z2}} \right)$$

$$R_4 = \frac{0.026}{0.25} \cdot \ln \left(\frac{0.677}{2(0.25)} \right)$$

or

$$\underline{R_4 = 31.5 \Omega}$$

b. From Example 15.16, $V_{B7} = 3.43 \text{ V}$. Then

$$\left(\frac{R_{13}}{R_{12} + R_{13}} \right) V_o = V_{B8} = V_{B7}$$

or

$$\left(\frac{2.23}{2.23 + R_{12}} \right) (12) = 3.43$$

$$3.43(2.23 + R_{12}) = (2.23)(12)$$

which yields

$$\underline{R_{12} = 5.57 \text{ k}\Omega}$$

15.67

$$\text{Line regulation} = \frac{\Delta V_o}{\Delta V^+}$$

Now

$$\Delta V_{B7} = \Delta I_{C3} \cdot R_1$$

$$\text{and } \left(\frac{R_{13}}{R_{12} + R_{13}} \right) (\Delta V_o) = \Delta V_{B7} = \Delta I_{C3} R_1$$

$$\text{and } \Delta I_{C3} = \frac{\Delta V_Z}{R_1 + R_2 + R_3} = \frac{\Delta I_Z \cdot r_Z}{R_1 + R_2 + R_3}$$

$$\text{and } \Delta I_Z = \frac{\Delta V^+}{r_o} \text{ where } r_o = \frac{V_A}{I_Z}$$

Then

$$(0.4288)(\Delta V_o) = \Delta I_{C3}(3.9)$$

$$= (3.9)\Delta I_Z \left(\frac{0.015}{7.876} \right)$$

$$r_o = \frac{50}{0.571} = 87.6 \text{ k}\Omega$$

Then

$$(0.4288)(\Delta V_o) = (0.00743) \left(\frac{\Delta V^+}{87.6} \right)$$

So

$$\underline{\frac{\Delta V_o}{\Delta V^+} = 0.0198\%}$$

15.68

$$\text{a. } I_Z = \frac{25 - 5}{R_1 + r_Z} = 10$$

$$\text{So } R_1 + r_Z = \frac{20}{10} = 2 \text{ k}\Omega = R_1 + 0.01 \\ \Rightarrow \underline{R_1 = 1.99 \text{ k}\Omega}$$

b. In the ideal case;

$$\left(\frac{R_3 + R_4}{R_2 + R_3 + R_4} \right) V_o = V_Z$$

$$\left(\frac{2 + 1}{2 + 1 + 1} \right) V_o = 5 \Rightarrow V_o = 6.67 \text{ V}$$

and


$$\left(\frac{R_4}{R_2 + R_3 + R_4} \right) V_o = V_Z$$

$$\left(\frac{1}{2 + 1 + 1} \right) V_o = 5 \Rightarrow V_o = 20 \text{ V}$$

So

$$\underline{6.67 < V_o < 20 \text{ V}}$$

c.

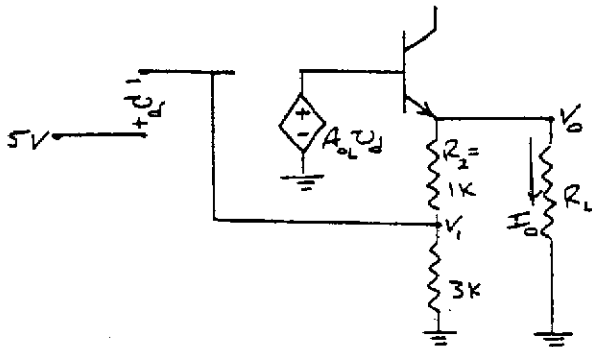

$$V_1 = \frac{3}{4} \cdot V_o \text{ so } v_d = 5 - \frac{3}{4} \cdot V_o$$

$$\text{and } V_o = A_{0L} v_d - V_{BE}$$

$$\text{and } V_{BE} = V_T \ln \left(\frac{I_o}{I_S} \right)$$

Now

$$V_o = A_{0L} \left(5 - \frac{3}{4} \cdot V_o \right) - V_{BE}$$

$$V_o \left(1 + \frac{3}{4} \cdot A_{0L} \right) = 5A_{0L} - V_{BE}$$

$$V_o = \frac{5A_{0L} - V_{BE}}{1 + \frac{3}{4} \cdot A_{0L}}$$

$$\text{Load regulation} = \frac{V_o(\text{NL}) - V_o(\text{FL})}{V_o(\text{NL})}$$

$$= \frac{\frac{5A_{0L} - V_{BE}(\text{NL})}{1 + \frac{3}{4}A_{0L}} - \frac{5A_{0L} - V_{BE}(\text{FL})}{1 + \frac{3}{4}A_{0L}}}{\frac{5A_{0L} - V_{BE}(\text{NL})}{1 + \frac{3}{4}A_{0L}}}$$

$$= \frac{V_{BE}(\text{FL}) - V_{BE}(\text{NL})}{5A_{0L} - V_{BE}(\text{NL})} = \frac{V_T \ln \left(\frac{I_o(\text{FL})}{I_o(\text{NL})} \right)}{5A_{0L} - V_{BE}(\text{NL})}$$

$$I_o(\text{FL}) = 1 \text{ A}, \quad I_o(\text{NL}) = \frac{V_o}{4 \text{ k}\Omega} = \frac{6.67}{4 \text{ k}\Omega} = 1.67 \text{ mA}$$

$$\text{Load regulation} = \frac{(0.026) \ln \left(\frac{1}{1.67 \times 10^{-3}} \right)}{5(10^4) - 0.7}$$

$$\Rightarrow 3.33 \times 10^{-4} \%$$

15.69

$$I_E = \frac{V_Z}{R_2} = \frac{5.6}{5} = 1.12 \text{ mA}$$

$$I_o = \frac{\beta}{1 + \beta} \cdot I_E = \left(\frac{100}{101} \right) (1.12)$$

$$\Rightarrow I_o = 1.109 \text{ mA Load current}$$

For

$$V_{BC} = 0 \Rightarrow V_o = 20 - V_Z - 0.6$$

$$= 20 - 5.6 - 0.6$$

or

$$V_o = 13.8 \text{ V}$$

Then

$$R_L = \frac{V_o}{I_o} = \frac{13.8}{1.109} \Rightarrow R_L = 12.4 \text{ k}\Omega$$

So

$$0 \leq R_L \leq 12.4 \text{ k}\Omega$$