

Chapter 12

Exercise Solutions

E12.1

$$a. \quad A_f = \frac{A}{1 + A\beta}$$

$$1 + A\beta = \frac{A}{A_f} \Rightarrow A\beta = \frac{A}{A_f} - 1$$

$$\beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{20} - \frac{1}{10^4} = 0.05 - 0.0001$$

$$\Rightarrow \underline{\beta = 0.0499}$$

$$b. \quad \frac{A_f}{(1/\beta)} = \frac{20}{(1/0.0499)} = \frac{20}{20.040} = \underline{0.998}$$

E12.2

$$A_f = \frac{A}{1 + A\beta}$$

$$A_f + A_f A\beta = A$$

$$A_f = A(1 - A_f\beta)$$

$$A = \frac{A_f}{1 - A_f\beta} = \frac{80}{1 - (80)(0.0120)}$$

$$\underline{A = 2000}$$

E12.3

$$A_f = \frac{A}{1 + A\beta}$$

$$\beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{100} - \frac{1}{10^5} = 0.01 - 10^{-6}$$

$$\beta = 0.009999$$

$$\frac{dA_f}{A_f} = \frac{1}{(1 + \beta A)} \cdot \frac{dA}{A} = \left(\frac{A_f}{A} \right) \cdot \frac{dA}{A}$$

$$\frac{dA_f}{A_f} = \left(\frac{100}{10^5} \right) (20)\%$$

$$\Rightarrow \underline{\frac{dA_f}{A_f} = 0.002\%}$$

E12.4

$$\frac{dA_f}{A_f} = \frac{1}{(1 + \beta A)} \cdot \frac{dA}{A} = \left(\frac{A_f}{A} \right) \cdot \frac{dA}{A}$$

$$\frac{dA}{A} = \frac{dA_f}{A_f} \cdot \left(\frac{A}{A_f} \right) = (0.001) \left(\frac{5 \times 10^5}{100} \right)$$

$$\Rightarrow \underline{\frac{dA}{A} = \pm 5\%}$$

E12.5

$$\text{Bandwidth} = \omega_H(1 + \beta A_0)$$

$$= \omega_H \left(\frac{A_0}{A_f} \right) = (2\pi)(10) \left(\frac{10^5}{100} \right)$$

$$\omega = (2\pi)(10^4) \text{ rad/sec} \Rightarrow \underline{f = 10 \text{ kHz}}$$

E12.6

$$A_f \cdot f_H = A_0 \cdot f_1$$

$$A_f = \frac{A_0 \cdot f_1}{f_H} = \frac{(10^3)(8)}{250 \times 10^3}$$

$$\Rightarrow \underline{A_f(0) = 32}$$

E12.7

$$a. \quad V_e = V_S - V_{f_b} = 100 - 99 = 1 \text{ mV}$$

$$V_0 = A_v V_e \Rightarrow A_v = \frac{5}{0.001} \Rightarrow \underline{A_v = 5000 \text{ V/V}}$$

$$V_{f_b} = \beta V_0 \Rightarrow \beta = \frac{V_{f_b}}{V_0} = \frac{0.099}{5} \Rightarrow \underline{\beta = 0.0198 \text{ V/V}}$$

$$A_{v_f} = \frac{A_v}{1 + \beta A_v} = \frac{5000}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{A_{v_f} = 50 \text{ V/V}}$$

$$b. \quad R_{i_f} = R_i(1 + \beta A_v) = (5)[1 + (0.0198)(5000)]$$

$$\Rightarrow \underline{R_{i_f} = 500 \text{ k}\Omega}$$

$$R_{o_f} = \frac{R_o}{1 + \beta A_v} = \frac{4}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{R_{o_f} = 40 \Omega}$$

E12.8

$$a. \quad I_e = I_S - I_{f_b} = 100 - 99 = 1 \mu\text{A}$$

$$A_i = \frac{I_0}{I_e} = \frac{5}{0.001} \Rightarrow \underline{A_i = 5000 \text{ A/A}}$$

$$\beta = \frac{I_{f_b}}{I_0} = \frac{0.099}{5} \Rightarrow \underline{\beta = 0.0198 \text{ A/A}}$$

$$A_{i_f} = \frac{A_i}{1 + A_i\beta} = \frac{5000}{1 + (5000)(0.0198)}$$

$$\Rightarrow \underline{A_{i_f} = 50 \text{ A/A}}$$

$$b. \quad R_{i_f} = \frac{R_i}{1 + \beta A_i} = \frac{5}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{R_{i_f} = 50 \Omega}$$

$$R_{o_f} = (1 + \beta A_i)R_o = [1 + (0.0198)(5000)](4)$$

$$\Rightarrow \underline{R_{o_f} = 400 \text{ k}\Omega}$$

E12.9

$$V_e = V_S - V_{f_b} = 100 - 99 = 1 \text{ mV}$$

$$A_g = \frac{I_0}{V_e} = \frac{5 \text{ mA}}{1 \text{ mV}} \Rightarrow \underline{A_g = 5 \text{ A/V}}$$

$$\beta = \frac{V_{f_b}}{I_0} = \frac{99 \text{ mV}}{5 \text{ mA}} \Rightarrow \underline{\beta = 19.8 \text{ V/A}}$$

$$A_{g_f} = \frac{A_g}{1 + \beta A_g} = \frac{5}{1 + (19.8)(5)}$$

$$\Rightarrow \underline{A_{g_f} = 0.05 \text{ A/V} = 50 \text{ mA/V}}$$

E12.10

$$I_c = I_S - I_{f_b} = 100 - 99 = 1 \mu\text{A}$$

$$A_s = \frac{V_0}{I_c} = \frac{5 \text{ V}}{1 \mu\text{A}} \Rightarrow A_s = 5 \times 10^6 \text{ V/A}$$

$$\beta = \frac{I_{f_b}}{V_0} = \frac{99 \mu\text{A}}{5 \text{ V}} \Rightarrow \beta = 1.98 \times 10^{-5} \text{ A/V}$$

$$A_{s_f} = \frac{A_s}{1 + \beta A_s} = \frac{5 \times 10^6}{1 + (1.98 \times 10^{-5})(5 \times 10^6)} \\ \Rightarrow A_{s_f} = 5 \times 10^4 \text{ V/A} = 50 \text{ V/mA}$$

E12.11

$$A_{v_f} = \frac{A_v}{1 + \frac{A_v}{1 + (R_2/R_1)}} = \frac{10^4}{1 + \frac{10^4}{1 + (30/10)}} \\ \Rightarrow A_{v_f} = 3.9984$$

$$A_{v_f} = \frac{10^5}{1 + \frac{10^5}{1 + (30/10)}} = 3.99984 \\ \frac{3.99984 - 3.9984}{3.9984} \times 100\% \Rightarrow 0.0360\%$$

E12.12

$$\text{a. } r_\pi = \frac{h_{FE} V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$A_{v_f} = \frac{\left(\frac{1}{r_\pi} + g_m\right) R_E}{1 + \left(\frac{1}{r_\pi} + g_m\right) R_E} = \frac{\left(\frac{1}{5.2} + 19.23\right)(2)}{1 + \left(\frac{1}{5.2} + 19.23\right)(2)} \\ = \frac{(19.42)(2)}{1 + (19.42)(2)} \Rightarrow A_{v_f} = 0.97490$$

$$R_{i_f} = r_\pi + (1 + h_{FE}) R_E = 5.2 + (101)(2) \\ \Rightarrow R_{i_f} = 207.2 \text{ k}\Omega$$

$$R_{o_f} = R_E \parallel \frac{r_\pi}{1 + h_{FE}} = 2 \parallel \frac{5.2}{101} \\ \Rightarrow R_{o_f} = 0.0502 \text{ k}\Omega \Rightarrow 50.2 \Omega$$

$$\text{b. } h_{FE} = 150 \Rightarrow r_\pi = 7.8 \text{ k}\Omega, g_m = 19.23 \text{ mA/V}$$

$$A_{v_f} = \frac{\left(\frac{1}{7.8} + 19.23\right)(2)}{1 + \left(\frac{1}{7.8} + 19.23\right)(2)} = \frac{(19.36)(2)}{1 + (19.36)(2)} \\ A_{v_f} = 0.97482 \Rightarrow 0.0082\% \text{ change in } A_{v_f}$$


$$A_{v_f} = 0.97482 \Rightarrow 0.0082\% \text{ change in } A_{v_f}$$

$$R_{i_f} = 7.8 + (101)(2) = 209.8 \text{ k}\Omega \\ \Rightarrow 1.25\% \text{ change in } R_{i_f}$$

$$R_{o_f} = R_E \parallel \frac{r_\pi}{1 + h_{FE}} = 2 \parallel \frac{7.8}{151} = 2 \parallel 0.0517$$

$$R_{o_f} = 50.4 \Omega \Rightarrow 0.397\% \text{ change in } R_{o_f}$$

E12.13

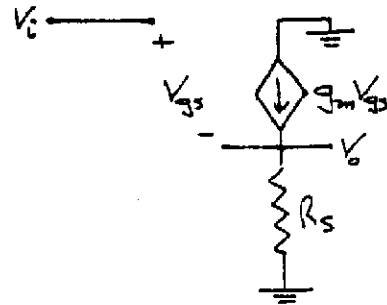

$$V_0 = (g_m V_{gs}) R_S$$

$$V_i = V_{gs} + g_m R_S V_{gs}$$


$$V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(0.25)} = 0.447 \text{ mA/V}$$

$$A_{v_f} = \frac{V_0}{V_i} = \frac{g_m R_S}{1 + g_m R_S}$$

$$A_{v_f} = \frac{(0.447)(5)}{1 + (0.447)(5)} \Rightarrow A_{v_f} = 0.691$$

$$R_{i_f} = \infty$$

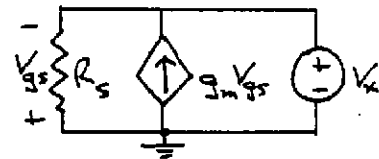

$$I_X = g_m V_{gs} = \frac{V_X}{R_S}$$

$$V_{gs} = -V_X$$

$$I_X = V_X \left(g_m + \frac{1}{R_S} \right)$$

$$R_{o_f} = \frac{1}{g_m} \parallel R_S = \frac{1}{0.447} \parallel 5$$

$$R_{o_f} = 1.55 \text{ k}\Omega$$

E12.15

$$i_o = \left(\frac{h_{FE}}{1 + h_{FE}} \right) \left(\frac{R_E}{R_E + \frac{r_\pi}{1 + h_{FE}}} \right) i_i$$

$$r_\pi = \frac{(80)(0.026)}{0.5} = 4.16 \text{ k}\Omega$$

Then

$$\frac{r_\pi}{1 + h_{FE}} = \frac{4.16}{81} = 0.0514 \text{ k}\Omega$$

Then we want

$$\frac{i_o}{i_i} = 0.95 = \left(\frac{80}{81}\right) \left(\frac{R_E}{R_E + 0.0514}\right)$$

or

$$\left(\frac{R_E}{R_E + 0.0514}\right) = 0.9619$$

which yields

$$R_E(\text{min}) = 1.30 \text{ k}\Omega$$

and

$$V^* = I_E R_E + 0.7 = \left(\frac{81}{80}\right)(0.5)(1.3) + 0.7 \Rightarrow$$

$$V^*(\text{min}) = 1.36 \text{ V}$$

E12.19

$$\text{a. } A_{gf} = \frac{h_{FE} \cdot A_g}{1 + (h_{FE} A_g) R_E} = \frac{(200)(10^3)}{1 + (200)(10^3)(10^3)} \\ \Rightarrow A_{gf} = 10^{-3} \text{ A/V} = 1 \text{ mA/V}$$

$$\text{b. } A_{gf} = \frac{(200)(10^4)}{1 + (200)(10^4)(10^3)} \Rightarrow A_{gf} \approx 1 \text{ mA/V} \\ \text{Percent change is negligible. } (4.5 \times 10^{-7} \%)$$

$$\frac{(200)(10^4)}{1 + (200)(10^4)(10^3)} - \frac{(200)(10^3)}{1 + (200)(10^3)(10^3)} \\ = \frac{(200)(10^4) [1 + (200)(10^3)(10^3)]}{(10^{-3})(2 \times 10^9)(2 \times 10^6)} \\ - \frac{(200)(10^3) [1 + (200)(10^4)(10^3)]}{(10^{-3})(2 \times 10^9)(2 \times 10^6)} \\ = \frac{200 \times 10^4 - 200 \times 10^3}{(10^{-3})(2 \times 10^9)(2 \times 10^6)} = 4.5 \times 10^{-9}$$

E12.20

$$\text{a. } V_G = \left(\frac{R_2}{R_1 + R_2}\right)(10) - 5 = \left(\frac{20}{20 + 30}\right)(10) - 5$$

$$V_G = -1 \text{ V}$$

$$V_S = -1 - V_{GS}$$

$$I_D = \frac{V_S - (-5)}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$1 - V_{GS} + 5 = (1.5)(0.4)(V_{GS} - 2)^2$$

$$4 - V_{GS} = 0.6(V_{GS}^2 - 4V_{GS} + 4)$$


$$0.6V_{GS}^2 - 1.4V_{GS} - 1.6 = 0$$

$$V_{GS} = \frac{1.4 \pm \sqrt{(1.4)^2 + 4(0.6)(1.6)}}{2(0.6)}$$

$$V_{GS} = 3.17 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1.5)(3.17 - 2)$$

$$g_m = 3.51 \text{ mA/V}$$

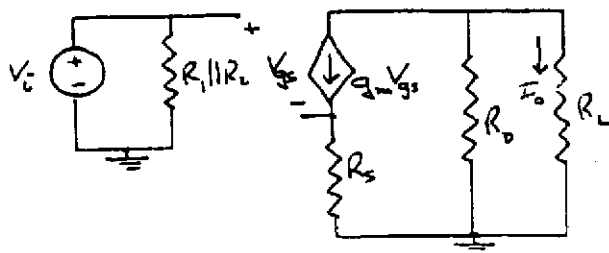

$$I_0 = -\left(\frac{R_D}{R_D + R_L}\right)(g_m V_{gs}) = -\left(\frac{2}{2 + 2}\right)(3.51)V_{gs} \\ I_0 = -1.76V_{gs}$$

$$V_i = V_{gs} + g_m V_{gs} R_S \Rightarrow V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$V_{gs} = \frac{V_i}{1 + (3.51)(0.4)} = (0.416)V_i$$

$$I_0 = -(1.76)(0.416)V_i \\ \Rightarrow A_{gf} = \frac{I_0}{V_i} = -0.732 \text{ mA/V}$$

$$\text{b. For } K_n = 1 \text{ mA/V}^2$$

From dc analysis:

$$4 - V_{GS} = (1)(0.4)(V_{GS} - 2)^2$$

$$4 - V_{GS} = 0.4(V_{GS}^2 - 4V_{GS} + 4)$$

$$0.4V_{GS}^2 - 0.6V_{GS} - 2.4 = 0$$

$$V_{GS} = \frac{0.6 \pm \sqrt{(0.6)^2 + 4(0.4)(2.4)}}{2(0.4)}$$

$$V_{GS} = 3.31 \text{ V}$$

$$g_m = 2(1)(3.31 - 2) = 2.62 \text{ mA/V}$$

$$I_0 = -\left(\frac{2}{2 + 2}\right)(2.62)V_{gs} = -1.31V_{gs}$$

$$V_{gs} = \frac{V_i}{1 + (2.62)(0.4)} = V_i(0.488)$$

$$I_0 = -(1.31)(0.488)V_i$$

$$A_{gf} = \frac{I_0}{V_i} = -0.639 \text{ mA/V}$$

$$\% \text{ change} = \frac{0.732 - 0.639}{0.732} \Rightarrow 12.7\%$$

E12.22

dc analysis:

$$\frac{10 - V_0}{4.7} = I_D + \frac{V_0}{47 + 20} \quad (1)$$

$$I_D = K_n (V_{GS} - V_{TN})^2 \quad (2)$$

$$V_{GS} = \left(\frac{20}{20 + 47} \right) V_0 = 0.2985 V_0 \quad (3)$$

$$2.13 - V_0(0.213) = I_D + (0.0149)V_0 \quad (1)$$

$$I_D = 2.13 - V_0(0.2279)$$

From (2):

$$2.13 - V_0(0.2279) = 1[(0.2985V_0) - 1.5]^2$$

$$2.13 - V_0(0.2279) = 0.0891V_0^2 - 0.8955V_0 + 2.25$$

$$0.0891V_0^2 - 0.6676V_0 + 0.12 = 0$$

$$V_0 = \frac{0.6676 \pm \sqrt{(0.6676)^2 - 4(0.0891)(0.12)}}{2(0.0891)}$$

$$V_0 = 7.31 \text{ V}$$


$$I_D = \frac{10 - 7.31}{4.7} - \frac{7.31}{67} = 0.572 - 0.109$$

$$I_D = 0.463 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{0.463}{1}} + 1.5 = 2.18$$

$$a. \quad g_m = 2K_n(V_{GS} - V_{TN}) = 2(1)(2.18 - 1.5)$$

$$\Rightarrow g_m = 1.36 \text{ mA/V}$$

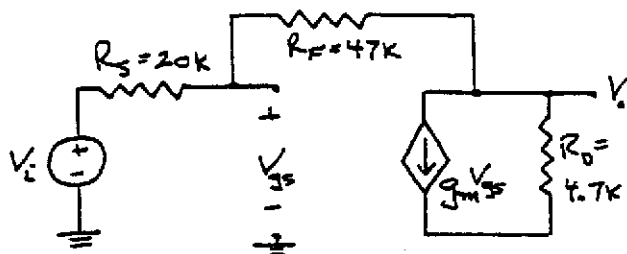

$$\frac{V_0}{R_D} + g_m V_{gs} + \frac{V_0 - V_{gs}}{R_F} = 0 \quad (1)$$

$$\frac{V_{gs} - V_i}{R_S} + \frac{V_{gs} - V_0}{R_F} = 0 \quad (2)$$

$$V_{gs} \left(\frac{1}{R_S} + \frac{1}{R_F} \right) = \frac{V_0}{R_F} + \frac{V_i}{R_S}$$

$$V_{gs} \left(\frac{1}{20} + \frac{1}{47} \right) = \frac{V_0}{47} + \frac{V_i}{20}$$

$$V_{gs}(0.0713) = V_0(0.0213) + V_i(0.050)$$

$$V_{gs} = V_0(0.299) + V_i(0.701)$$

From (1):

$$\frac{V_0}{4.7} + (1.36)V_{gs} + \frac{V_0}{47} - \frac{V_{gs}}{47} = 0$$

$$V_0(0.213) + (1.36)V_{gs}$$

$$+ V_0(0.0213) - V_{gs}(0.0213) = 0$$

$$V_0(0.234) + V_{gs}(1.34) = 0$$

$$V_0(0.234) + (1.34)[V_0(0.299) + V_i(0.701)] = 0$$

$$V_0(0.635) + V_i(0.939) = 0$$

$$\Rightarrow A_{v_f} = \frac{V_0}{V_i} = -1.48$$

b. For $K_n = 1.5 \text{ mA/V}^2$

From dc analysis:

$$2.13 - V_0(0.2279) = 1.5[(0.2985V_0) - 1.5]^2$$

$$= 1.5[0.0891V_0^2 - 0.8955V_0 + 2.25]$$

$$= 0.1337V_0^2 - 1.343V_0 + 3.375$$

$$0.1337V_0^2 - 1.115V_0 + 1.245 = 0$$

$$V_0 = \frac{1.115 \pm \sqrt{(1.115)^2 - 4(0.1337)(1.245)}}{2(0.1337)}$$

$$V_0 = \frac{1.115 \pm 0.7597}{2(0.1337)} \Rightarrow V_0 = 7.01 \text{ V}$$

$$I_D = \frac{10 - 7.01}{4.7} - \frac{7.01}{67} = 0.636 - 0.105$$

$$I_D = 0.531 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{0.531}{1.5}} + 1.5 = 2.09$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1.5)(2.09 - 1.5)$$

$$= 1.77 \text{ mA/V}$$

From ac analysis:

$$\frac{V_0}{4.7} + (1.77)V_{gs} + \frac{V_0}{47} - \frac{V_{gs}}{47} = 0$$

$$V_0(0.213) + (1.77)V_{gs}$$

$$+ V_0(0.0213) - V_{gs}(0.0213) = 0$$

$$V_0(0.234) + V_{gs}(1.75) = 0$$

$$V_0(0.234) + (1.75)[V_0(0.299) + V_i(0.701)] = 0$$


$$V_0(0.757) + V_i(1.23) = 0$$

$$\Rightarrow A_{v_f} = \frac{V_0}{V_i} = -1.62$$

$$\% \text{ change} = \frac{1.62 - 1.48}{1.48} \Rightarrow 9.46\%$$

E12.23

a. Input resistance.

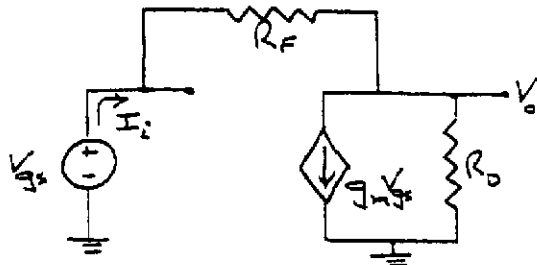

$$\frac{V_o}{R_D} + g_m V_{gs} + \frac{V_o - V_{gs}}{R_F} = 0 \quad (1)$$

$$I_i = \frac{V_{gs} - V_o}{R_F} \quad (2)$$

$$\text{So } V_o = V_{gs} - I_i R_F$$

$$V_o \left(\frac{1}{R_D} + \frac{1}{R_F} \right) + V_{gs} \left(g_m - \frac{1}{R_F} \right) = 0 \quad (1)$$


$$[V_{gs} - I_i(47)] \left(\frac{1}{4.7} + \frac{1}{47} \right) + V_{gs} \left(1.36 - \frac{1}{47} \right) = 0$$

$$[V_{gs} - I_i(47)](0.234) + V_{gs}(1.34) = 0$$

$$V_{gs}(1.57) = I_i(11.0)$$

$$\Rightarrow R_{if} = \frac{V_{gs}}{I_i} = 7.0 \text{ k}\Omega$$

Output Resistance.

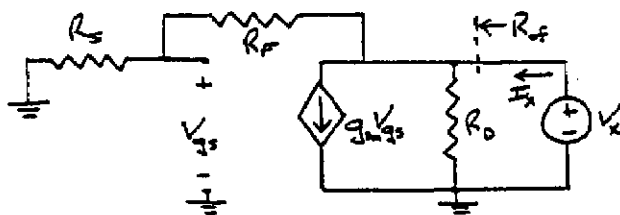

$$I_x = \frac{V_x}{R_D} + g_m V_{gs} + \frac{V_x}{R_S + R_F}$$

$$V_{gs} = \left(\frac{R_S}{R_S + R_F} \right) V_x = \left(\frac{20}{20 + 47} \right) V_x = 0.2985 V_x$$

$$I_x = \frac{V_x}{4.7} + (1.36)(0.2985)V_x + \frac{V_x}{20 + 47}$$

$$I_x = V_x [0.213 + 0.406 + 0.0149]$$

$$R_{of} = \frac{V_x}{I_x} = 1.58 \text{ k}\Omega$$

b. From part (a)

$$[V_{gs} - I_i(47)](0.234) + V_{gs} \left(1.77 - \frac{1}{47} \right) = 0$$

$$V_{gs}(1.98) = I_i(11)$$

$$\Rightarrow R_{if} = \frac{V_{gs}}{I_i} = 5.56 \text{ k}\Omega$$

$$I_x = \frac{V_x}{4.7} + (1.77)(0.2985)V_x + \frac{V_x}{20 + 47}$$

$$I_x = V_x [0.213 + 0.528 + 0.0149]$$

$$\Rightarrow R_{of} = \frac{V_x}{I_x} = 1.32 \text{ k}\Omega$$

E12.25

$$V_{TH} = \left(\frac{5.5}{5.5 + 51} \right) (10) = 0.973 \text{ V}$$

$$R_{TH} = 5.5 \parallel 51 = 4.96 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.973 - 0.7}{4.96 + (121)(1)} = 0.00217 \text{ mA}$$

$$I_{CQ} = 0.260 \text{ mA}$$

$$r_\pi = 12 \text{ k}\Omega, g_m = 10 \text{ mA/V}$$

$$R_{eq} = R_S \parallel R_1 \parallel R_2 \parallel r_\pi = 10,000 \parallel 51 \parallel 5.5 \parallel 12$$

$$= 3.51 \text{ k}\Omega$$


From Equation (12.99(b)):

$$T = (g_m R_C) \left(\frac{R_{eq}}{R_C + R_F + R_{eq}} \right)$$

$$= (10)(10) \left(\frac{3.51}{10 + 82 + 3.51} \right)$$

$$\Rightarrow T = 3.68$$

E12.26

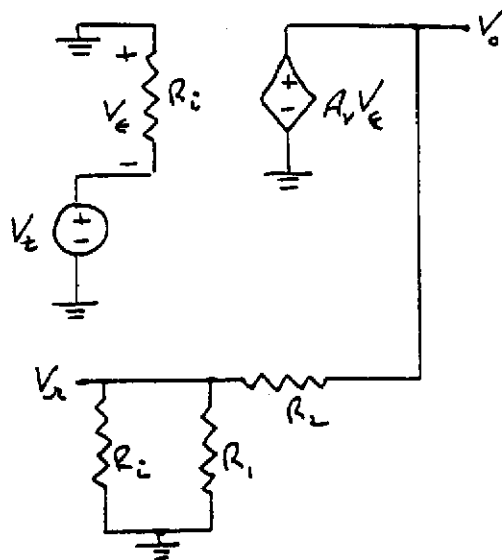

$$V_e = -V_i, V_o = A_v V_e = -A_v V_i$$

$$V_e = \left(\frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) V_o = - \left(\frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) (A_v V_i)$$

$$T = \frac{V_o}{V_i} = A_v \left(\frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right)$$

or

$$T = \frac{A_v}{1 + \frac{R_2}{R_1 \parallel R_i}}$$

E12.27

$$T = A_v \beta = \frac{A_{io} \beta}{\left(1 + j \cdot \frac{f}{f_1} \right)} = \frac{(10^3)(0.01)}{1 + j \cdot \left(\frac{f}{10} \right)}$$

$$|T(f_1)| = 1 = \frac{10^3}{\sqrt{1 + \left(\frac{f'_E}{10} \right)^2}}$$

$$1 + \left(\frac{f'_E}{10} \right)^2 = 10^4$$

$$f'_E = 10\sqrt{10^4 - 1} \Rightarrow \underline{f'_E \approx 10^4 \text{ Hz}}$$

$$\text{Phase} = \phi = -\tan^{-1} \left(\frac{f'_E}{10} \right) = -\tan^{-1} \left(\frac{10^4}{10} \right) \\ = -\tan^{-1} (10^3)$$

$$\phi \approx 90^\circ$$

$$\text{Phase Margin} = 180 - 90 \Rightarrow \underline{\text{Phase Margin} = 90^\circ}$$

E12.28

$$T = A_v \beta = \frac{A_{io} \beta}{\left(1 + j \cdot \frac{f}{f_1} \right) \left(1 + j \cdot \frac{f}{f_2} \right)}$$

$$\text{Phase} = - \left[\tan^{-1} \left(\frac{f}{f_1} \right) + \tan^{-1} \left(\frac{f}{f_2} \right) \right]$$

$$\text{Phase Margin} = 60^\circ \Rightarrow \text{Phase} = -120^\circ$$

$$-120^\circ = - \left[\tan^{-1} \left(\frac{f}{10^4} \right) + \tan^{-1} \left(\frac{f}{10^5} \right) \right]$$

$$\text{At } f' = 7.66 \times 10^4 \text{ Hz,}$$

$$\text{Phase} = - \left[\tan^{-1} (7.66) + \tan^{-1} (0.766) \right]$$

$$= -[82.56 + 37.45]$$

$$= -120^\circ$$

$$|T(f')| = 1 = \frac{(10^3) \beta}{\sqrt{1 + (7.66)^2} \times \sqrt{1 + (0.766)^2}} \\ 1 = \frac{(10^3) \beta}{(7.725)(1.26)} \Rightarrow \underline{\beta = 9.73 \times 10^{-5}}$$

E12.29

$$\text{Phase} = -180^\circ = -3 \tan^{-1} \left(\frac{f'}{10^5} \right)$$

$$\text{or } \tan^{-1} \left(\frac{f'}{10^5} \right) = 60^\circ \Rightarrow f' = 1.732 \times 10^5 \text{ Hz}$$

$$|T(f')| = 1 = \frac{\beta(100)}{\left[\sqrt{1 + \left(\frac{f'}{10^5} \right)^2} \right]^3} \\ = \frac{\beta(100)}{\left[\sqrt{1 + (1.732)^2} \right]^3} \\ \Rightarrow \underline{\beta = 0.08}$$

E12.30

$$\text{Phase Margin} = 60^\circ \Rightarrow \text{Phase} = -120^\circ$$

$$\text{Phase} = -120^\circ = -3 \tan^{-1} \left(\frac{f'}{10^5} \right)$$

$$\tan^{-1} \left(\frac{f'}{10^5} \right) = 40^\circ \Rightarrow f' = 0.839 \times 10^5 \text{ Hz}$$

$$|T(f')| = 1 = \frac{\beta(100)}{\left[\sqrt{1 + \left(\frac{f'}{10^5} \right)^2} \right]^3} \\ = \frac{\beta(100)}{\left[\sqrt{1 + (0.839)^2} \right]^3} \\ \Rightarrow \underline{\beta = 0.0222}$$

E12.31

The new loop gain function is

$$T'(f) = \frac{10^5}{\left(1 + j \cdot \frac{f}{f_{PD}}\right) \left(1 + j \cdot \frac{f}{5 \times 10^5}\right)} \times \frac{1}{\left(1 + j \cdot \frac{f}{10^7}\right) \left(1 + j \cdot \frac{f}{5 \times 10^8}\right)}$$

$$\text{Phase} = -\left\{ \tan^{-1} \left(\frac{f}{f_{PD}} \right) + \tan^{-1} \left(\frac{f}{5 \times 10^5} \right) + \tan^{-1} \left(\frac{f}{10^7} \right) + \tan^{-1} \left(\frac{f}{5 \times 10^8} \right) \right\}$$

For a phase margin $45^\circ \Rightarrow \text{Phase} = -135^\circ$, the poles are far apart so this will occur at approximately $f' = 5 \times 10^5$ Hz. Then

$$|T'(f)| = 1 = \frac{10^5}{\sqrt{1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2} \times \sqrt{1+1} \times \sqrt{1} \times \sqrt{1}}$$

$$1 = \frac{10^5}{(1.414) \sqrt{1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2}}$$

$$1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2 = 5 \times 10^9$$

$$f_{PD} \approx \frac{5 \times 10^5}{\sqrt{5 \times 10^9}} \Rightarrow \underline{f_{PD} = 7.07 \text{ Hz}}$$

E12.32

Phase Margin = $45^\circ \Rightarrow \text{Phase} = -135^\circ$

This will occur at approximately $f' = 10^7$ Hz

$$|T'(f)| = 1 = \frac{10^5}{\sqrt{1 + \left(\frac{10^7}{f_{PD}}\right)^2} \times \sqrt{2} \times \sqrt{1}}$$

$$1 + \left(\frac{10^7}{f_{PD}}\right)^2 = 5 \times 10^9$$

$$f_{PD} \approx \frac{10^7}{\sqrt{5 \times 10^9}} \Rightarrow \underline{f_{PD} = 141 \text{ Hz}}$$

E12.33

$$A_f(0) = \frac{A_o}{1 + \beta A_o} = \frac{2 \times 10^5}{1 + (0.05)(2 \times 10^5)}$$

$$\Rightarrow \underline{A_f(0) \approx 20}$$

$$f_C = f_{PD}(1 + \beta A_o) = 100[1 + (0.05)(2 \times 10^5)]$$

$$\Rightarrow \underline{f_C \approx 1 \text{ MHz}}$$

Chapter 12

Problem Solutions

12.1

$$a. \quad A_f = \frac{A}{1 + A\beta}$$

$$80 = \frac{10^5}{1 + (10^5)\beta} \Rightarrow 1 + (10^5)\beta = \frac{10^5}{80}$$

$$\Rightarrow \beta = \frac{\frac{10^5}{80} - 1}{10^5} \Rightarrow \beta = 0.01249$$

$$b. \quad \frac{dA_f}{A_f} = \left(\frac{A_f}{A} \right) \cdot \frac{dA}{A} = \frac{80}{10^5}(-20)$$

or

$$\frac{dA_f}{A_f} = -0.016\%$$

$$A_f = 80 - (0.00016)80 \Rightarrow A_f \approx 79.99$$

$$c. \quad 80 = \frac{10^3}{1 + (10^3)\beta}$$

$$\beta = \frac{\frac{10^3}{80} - 1}{10^3} \Rightarrow \beta = 0.0115$$

$$\frac{dA_f}{A_f} = \left(\frac{80}{10^3} \right)(-20) \Rightarrow \frac{dA_f}{A_f} = -1.6\%$$

$$A_f = 80 - (0.016)(80) \Rightarrow A_f = 78.72$$

12.2

$$a. \quad A_f = \frac{(A)^3}{1 + (A)^3\beta}$$

$$100 = \frac{1000}{1 + (1000)\beta} \Rightarrow \beta = \frac{\frac{1000}{100} - 1}{1000} \Rightarrow \beta = 0.009$$

b. A goes from 10 to 11 so

$$A_f = \frac{(11)^3}{1 + (11)^3(0.009)} = \frac{1331}{1 + (1331)(0.009)}$$

or

$$A_f = 102.55$$

so

$$\frac{\Delta A_f}{A_f} = \frac{2.55}{100} \Rightarrow 2.55\% \text{ change}$$

12.3

$$(a) \quad V_o = (-10)(-15)(-20)V_s = -3000V_s$$

$$V_s = \beta V_o + V_s$$

$$\text{So } V_o = -3000(\beta V_o + V_s)$$

We find

$$A_v = \frac{V_o}{V_s} = \frac{-3000}{1 + 3000\beta}$$

$$\text{For } A_v = -120 = \frac{-3000}{1 + 3000\beta} \Rightarrow \beta = 0.008$$


$$(b) \text{ Now } V_o = (-9)(-13.5)(-18)V_s = -2187V_s$$

Then

$$A_v = \frac{-2187}{1 + 2187\beta} = \frac{-2187}{1 + 2187(0.008)} = -118.24$$

$$\% \text{ change} = \frac{120 - 118.24}{120} \times 100 \Rightarrow 1.47\% \text{ change}$$

12.4

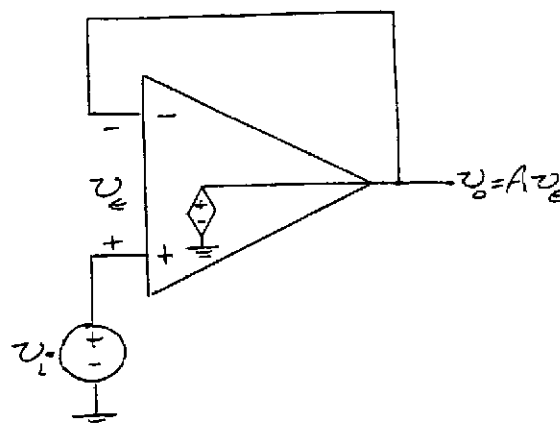

$$v_o = v_i - v_s \Rightarrow v_s = v_i - v_o$$

$$\text{Then } v_o = A(v_i - v_o) = Av_i - Av_o$$

And

$$v_o(1 + A) = Av_i$$

so

$$\frac{v_o}{v_i} = \frac{A}{1 + A} = 0.9998 \Rightarrow A = 4999$$

12.5

$$(10^5)(4) = (50)f_s \Rightarrow f_s = 8 \text{ kHz}$$

12.6

$$(a) \quad (50)f_{3-dB} = (10^5)(4) \Rightarrow f_{3-dB} = 8 \text{ kHz}$$

$$(b) \quad (10)f_{3-dB} = (10^5)(4) \Rightarrow f_{3-dB} = 40 \text{ kHz}$$

12.7

$$(50)(20 \times 10^3) = 5A_0 \text{ so } A_0 = 2 \times 10^5$$




12.8

$$v_o = A_1 A_2 v_i + A_1 v_n$$

$$v_o = (100)v_i + (1)v_n = (100)(10) + (1)(1)$$

$$\Rightarrow \frac{S_o}{N_o} = \frac{1000}{1} = 1000$$

12.9

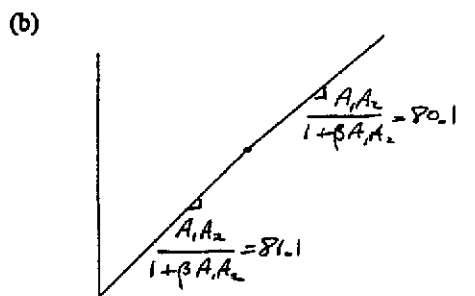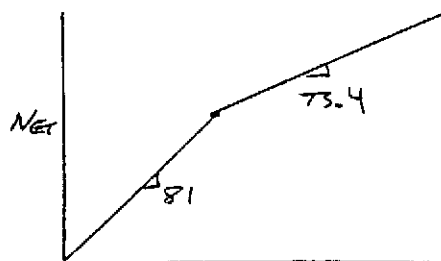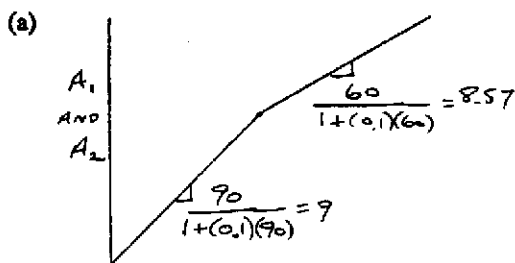

Circuit (b) – less distortion

12.10

- (a) Low input $R \Rightarrow$ Shunt input
Low output $R \Rightarrow$ Shunt output
Or a Shunt-Shunt circuit
- (b) High input $R \Rightarrow$ Series input
High output $R \Rightarrow$ Series output
Or a Series-Series circuit
- (c) Shunt-Series circuit
- (d) Series-Shunt circuit

12.11

(a) $R_i(\max) = R_i(1 + T) = 10(1 + 10^4) \Rightarrow$
 $R_i(\max) \cong 10^5 \text{ k}\Omega$

$R_i(\min) = \frac{R_i}{1 + T} = \frac{10}{1 + 10^4} \cong 10^{-3} \text{ k}\Omega$
 Or $R_i(\min) = 1 \Omega$


(b) $R_o(\max) = R_o(1 + T) = 1(1 + 10^4) \Rightarrow$
 $R_o(\max) \cong 10^4 \text{ k}\Omega$

$R_o(\min) = \frac{R_o}{1 + T} = \frac{1}{1 + 10^4} \cong 10^{-4} \text{ k}\Omega$
 Or $R_o(\min) = 0.1 \Omega$

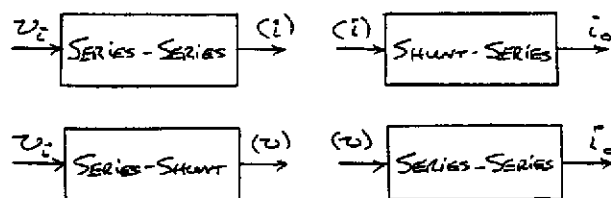12.12


Overall Transconductance Amplifier, $A_x = \frac{i_o}{v_i}$

Series output = current signal and Shunt input = current signal. Also, Shunt output = voltage signal and Series input = voltage signal. Two possible solutions are shown.



12.13

a.

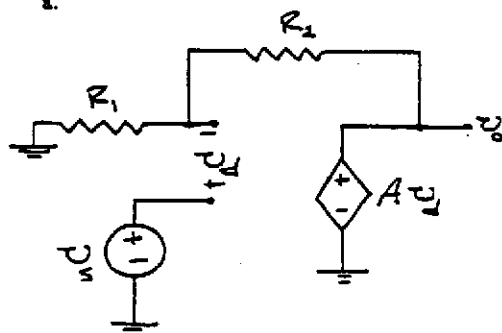

$$\frac{v_s - v_d}{R_1} = \frac{v_o - (v_s - v_d)}{R_2} \text{ and } v_d = \frac{v_o}{A}$$

$$\frac{v_s}{R_1} + \frac{v_s}{R_2} = \frac{v_o}{R_2} + v_d \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{v_o}{R_2} + \frac{v_o}{A} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\nu_S \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{\nu_0}{R_2} \left[1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1} \right) \right]$$

$$\frac{\nu_0}{\nu_S} = \frac{\left(1 + \frac{R_2}{R_1} \right)}{1 + \frac{1}{A} \left(1 + \frac{R_2}{R_1} \right)}$$

which can be written as

$$A_{vf} = \frac{\nu_0}{\nu_S} = \frac{A}{1 + \left[A \left(1 + \frac{R_2}{R_1} \right) \right]}$$

b. $\beta = \frac{1}{1 + \frac{R_2}{R_1}}$

c. $20 = \frac{10^5}{1 + (10^5)\beta}$

So $\beta = \frac{10^5 - 1}{10^5} \Rightarrow \beta = 0.04999$


Then $\frac{R_2}{R_1} = \frac{1}{\beta} - 1 = \frac{1}{0.04999} - 1$
 $\Rightarrow \frac{R_2}{R_1} = 19.004$

d. $A \rightarrow 8 \times 10^4$

$$A_f = \frac{8 \times 10^4}{1 + (8 \times 10^4)(0.04999)} = 19.999$$

$$\frac{\Delta A_f}{A_f} = -\frac{0.001}{20} \Rightarrow \frac{\Delta A_f}{A_f} = -0.005\%$$

12.14

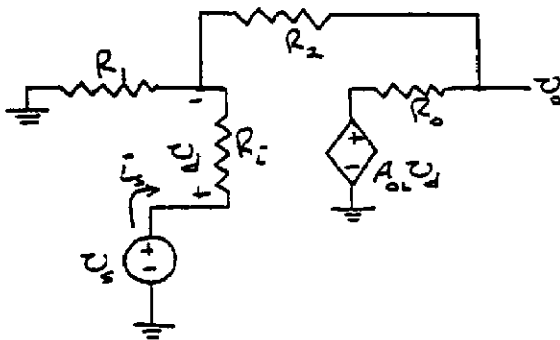

$$A_{vf} \approx \left(1 + \frac{R_2}{R_1} \right) = 20 \Rightarrow \frac{R_2}{R_1} = 19$$

$$\nu_d = i_S R_i$$

$$i_S = \frac{\nu_S - \nu_d}{R_1} + \frac{(\nu_S - \nu_d) - \nu_0}{R_2} \quad (1)$$

$$\frac{\nu_0 - A_{0L}\nu_d}{R_0} + \frac{\nu_0 - (\nu_S - \nu_d)}{R_2} = 0 \quad (2)$$

$$\nu_0 \left(\frac{1}{R_0} + \frac{1}{R_2} \right) = \frac{A_{0L}\nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2}$$

$$\nu_0 = \frac{\frac{A_{0L}\nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2}}{\left(\frac{1}{R_0} + \frac{1}{R_2} \right)}$$

From (1):

$$i_S = \frac{\nu_S - \nu_d}{R_1} + \frac{\nu_S - \nu_d}{R_2} - \frac{\frac{1}{R_2} \left[\frac{A_{0L}\nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2} \right]}{\left(\frac{1}{R_0} + \frac{1}{R_2} \right)}$$

$$i_S = \nu_S \left(\frac{1}{R_1} + \frac{1}{R_2} - \frac{\frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right)$$

$$- \nu_d \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{\frac{A_{0L}}{R_0} - \frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right)$$

$$\nu_d = i_S R_i$$

$$i_S \left\{ 1 + \frac{R_i \left[\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(1 + \frac{R_2}{R_0} \right) + \frac{A_{0L}}{R_0} - \frac{1}{R_2} \right]}{1 + \frac{R_2}{R_0}} \right\}$$

$$= \nu_S \left[\frac{\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(1 + \frac{R_2}{R_0} \right) - \frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right]$$

$$i_S \left\{ 1 + \frac{R_2}{R_0} + R_i \left[\frac{1}{R_1} + \frac{R_2}{R_1} \cdot \frac{1}{R_0} + \frac{1}{R_0} + \frac{A_{0L}}{R_0} \right] \right\}$$

$$= \nu_S \left[\frac{1}{R_1} + \frac{R_2}{R_1} \cdot \frac{1}{R_0} + \frac{1}{R_0} \right]$$

$$i_S \left\{ R_0 + R_2 + R_i \left[\frac{R_0}{R_1} + \left(1 + \frac{R_2}{R_1} \right) + A_{0L} \right] \right\} \quad (1)$$

$$= \nu_S \left[\frac{R_0}{R_1} + \left(1 + \frac{R_2}{R_1} \right) \right]$$

Let $R_2 = 190 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$


$$i_S \left\{ 0.1 + 190 + 100 \cdot \left[\frac{0.1}{10} + 20 + 10^5 \right] \right\}$$

$$= \nu_S \left[\frac{0.1}{10} + 20 \right]$$

$$i_S (1.000219 \times 10^7) = \nu_S (20.01)$$

$$R_{if} = \frac{\nu_S}{i_S} \approx 5 \times 10^5 \text{ k}\Omega \Rightarrow R_{if} \approx 500 \text{ M}\Omega$$

Output Resistance

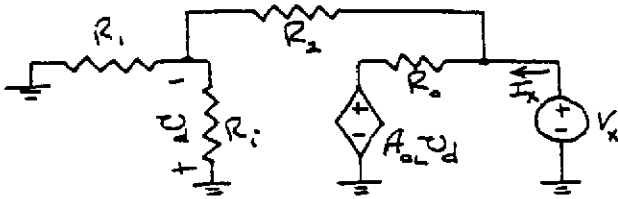

$$I_X = \frac{V_X - A_{OL} v_d}{R_0} + \frac{V_X}{R_2 + R_1 \parallel R_3}$$

$$v_d = \frac{-R_1 \parallel R_3}{R_1 \parallel R_3 + R_2} V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = \frac{1}{R_0} + \frac{A_{OL} \cdot R_1 \parallel R_3}{R_0(R_1 \parallel R_3 + R_2)} + \frac{1}{R_2 + R_1 \parallel R_3}$$

$$R_1 \parallel R_3 = 10 \parallel 100 = 9.09$$


$$\frac{1}{R_{of}} = \frac{1}{0.1} + \frac{10^5}{0.1} \cdot \left(\frac{9.09}{9.09 + 190} \right) + \frac{1}{190 + 9.09}$$

$$= 10 + 4.566 \times 10^4 + 0.00502$$

$$R_{of} = 2.19 \times 10^{-5} \text{ k}\Omega \Rightarrow R_{of} = 0.0219 \Omega$$

12.15

a.

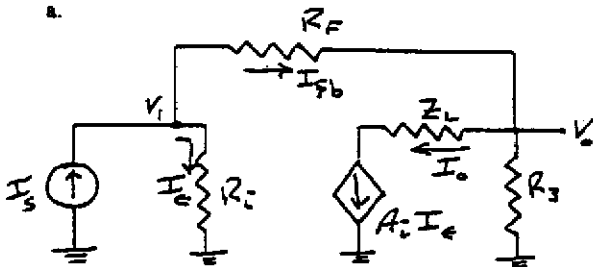Assume that V_1 is at virtual ground.

$$V_0 = -I_{fb} R_F$$

Now

$$I_{fb} = I_0 + \frac{V_0}{R_3} = I_0 - \frac{I_{fb} R_F}{R_3}$$

$$I_{fb} = I_S - I_e$$

and

$$I_0 = A_i I_e \Rightarrow I_e = \frac{I_0}{A_i}$$

so

$$I_{fb} = I_S - \frac{I_0}{A_i}$$

From above

$$I_{fb} \left(1 + \frac{R_F}{R_3} \right) = I_0$$

$$\left(I_S - \frac{I_0}{A_i} \right) \left(1 + \frac{R_F}{R_3} \right) = I_0$$

$$I_S \left(1 + \frac{R_F}{R_3} \right) = I_0 \left[1 + \frac{1}{A_i} \left(1 + \frac{R_F}{R_3} \right) \right]$$

or

$$A_{if} = \frac{I_0}{I_S} = \frac{\left(1 + \frac{R_F}{R_3} \right)}{\left[1 + \frac{1}{A_i} \left(1 + \frac{R_F}{R_3} \right) \right]}$$

$$= \frac{A_i}{1 + \frac{A_i}{\left(1 + \frac{R_F}{R_3} \right)}} = A_{if}$$

$$b. \quad \beta_i = \frac{1}{\left(1 + \frac{R_F}{R_3} \right)}$$

$$c. \quad 25 = \frac{10^5}{1 + (10^5) \beta_i}$$

$$\text{so } \beta_i = \frac{\frac{10^5}{25} - 1}{10^5} \Rightarrow \beta_i = 0.03999$$

$$\text{so } \frac{R_F}{R_3} = \frac{1}{\beta_i} - 1 = \frac{1}{0.03999} - 1 \Rightarrow \frac{R_F}{R_3} = 24.0$$


$$d. \quad A_i = 10^5 - (0.15)(10^5) = 8.5 \times 10^4$$

$$\text{so } A_{if} = \frac{8.5 \times 10^4}{1 + (8.5 \times 10^4)(0.03999)} = 24.9989$$

$$\text{so } \frac{\Delta A_{if}}{A_{if}} = \frac{-1.10 \times 10^{-3}}{25} = -4.41 \times 10^{-5}$$

$$\Rightarrow -4.41 \times 10^{-3} \%$$

12.16

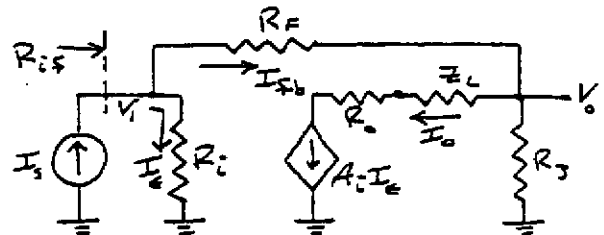

$$I_S = I_e + I_{fb}, \quad V_1 = I_e R_1$$

$$I_{fb} = I_0 + \frac{V_0}{R_3} \text{ and } V_0 = V_1 - I_{fb} R_F$$

$$I_0 = A_i I_e \Rightarrow I_e = \frac{I_0}{A_i}$$

Now

$$I_{fb} = A_i I_e + \frac{1}{R_3}(V_1 - I_{fb} R_F)$$

$$I_{fb} \left[1 + \frac{R_F}{R_3} \right] = A_i I_e + \frac{V_1}{R_3}$$

$$I_{fb} = I_S - I_e$$

$$(I_S - I_e) \left[1 + \frac{R_F}{R_3} \right] = A_i I_e + \frac{V_1}{R_3}$$

$$I_S \left[1 + \frac{R_F}{R_3} \right] = I_e \left[\left(1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{V_1}{R_3}$$

$$I_e = \frac{V_1}{R_i}$$

$$I_S \left[1 + \frac{R_F}{R_3} \right] = V_1 \left\{ \frac{1}{R_i} \cdot \left[\left(1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{1}{R_3} \right\}$$


$$R_{if} = \frac{V_1}{I_S} = \frac{\left(1 + \frac{R_F}{R_3} \right)}{\left\{ \frac{1}{R_i} \cdot \left[\left(1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{1}{R_3} \right\}}$$

The $1/R_3$ term in the denominator will be negligible.
Using the results of Problem 12.15:

$$R_{if} = \frac{25}{\left\{ \frac{1}{2} [(25) + 10^5] \right\}}$$

$$R_{if} \approx 5 \times 10^{-4} \text{ k}\Omega \Rightarrow R_{if} = 0.5 \Omega$$

Output Resistance (Let $Z_L = 0$)

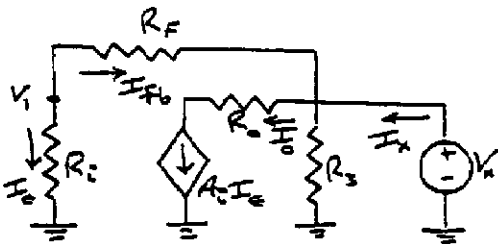

$$I_X = \frac{V_X}{R_3} + A_i I_e + \frac{V_X}{R_F + R_i}$$

$$I_e = \frac{V_X}{R_F + R_i}$$

so

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = \frac{1}{R_3} + \frac{A_i + 1}{R_F + R_i} \cdot \frac{R_F}{R_3} = 24$$

Let $R_F = 240 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$


$$\frac{1}{R_{of}} = \frac{1}{10} + \frac{10^5 + 1}{240 + 2}$$

$$\text{so } R_{of} \approx \frac{R_F + R_i}{A_i + 1} = \frac{240 + 2}{10^5 + 1}$$

$$\Rightarrow R_{of} \approx 2.42 \times 10^{-3} \text{ k}\Omega \text{ or } R_{of} \approx 2.42 \Omega$$

12.17

a.

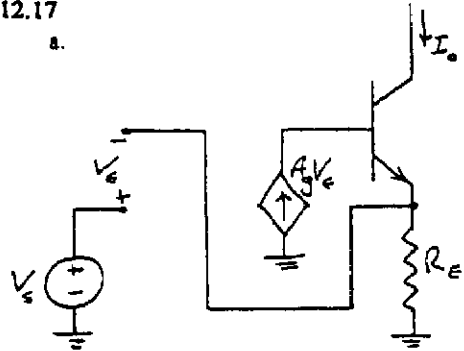

$$I_E = \frac{(1 + h_{FE})}{h_{FE}} \cdot I_o = \frac{V_S - V_e}{R_E}$$

$$\text{Also } I_o = h_{FE}(A_g V_e) \text{ so } V_e = \frac{I_o}{h_{FE} A_g}$$

Then

$$\frac{1 + h_{FE}}{h_{FE}} \cdot I_o = \frac{V_S}{R_E} - \frac{I_o}{h_{FE} A_g R_E}$$

$$\left[\frac{1 + h_{FE}}{h_{FE}} + \frac{1}{h_{FE} A_g R_E} \right] I_o = \frac{V_S}{R_E}$$

$$\left[\frac{A_g(1 + h_{FE})R_E + 1}{h_{FE} A_g R_E} \right] I_o = \frac{V_S}{R_E}$$

$$\frac{I_o}{V_S} = \frac{1}{R_E} \cdot \left[\frac{h_{FE} A_g R_E}{1 + A_g(1 + h_{FE})R_E} \right]$$

$$\Rightarrow \frac{I_o}{V_S} \approx \frac{h_{FE} A_g}{1 + (h_{FE} A_g)R_E}$$

b. $\beta_z = R_E$

c. $10 = \frac{5 \times 10^5}{1 + (5 \times 10^5)\beta_z}$


$$\beta_z = \frac{5 \times 10^5}{5 \times 10^5 - 1} \Rightarrow \beta_z = R_E = 0.999998 \text{ k}\Omega$$

d. If $A_g \rightarrow 5.5 \times 10^5$ then

$$A_{gf} = \frac{5.5 \times 10^5}{1 + (5.5 \times 10^5)(0.999998)} = 10.0000182$$

$$\frac{\Delta A_{gf}}{A_{gf}} = \frac{1.82 \times 10^{-5}}{10} \Rightarrow 1.82 \times 10^{-4} \%$$

12.18

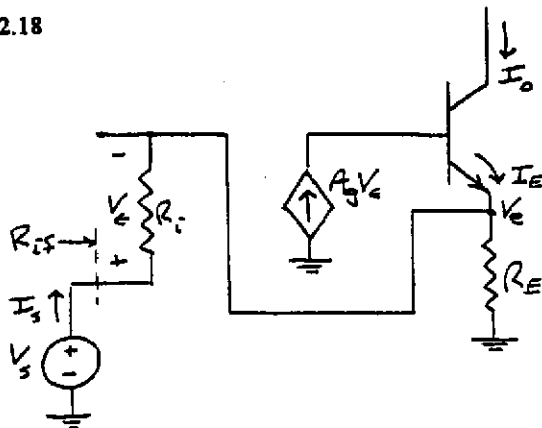

$$I_E = (1 + h_{FE}) A_g V_e, \quad I_E = \frac{V_e}{R_E} - I_S \text{ and } V_e = I_S R_i$$

$$V_e = V_S - V_i = V_S - I_S R_i$$

$$\text{Now } (1 + h_{FE}) A_g I_S R_i = \frac{1}{R_E} \cdot (V_S - I_S R_i) - I_S$$

$$\left[(1 + h_{FE}) A_g R_i + \frac{R_i}{R_E} + 1 \right] I_S = \frac{V_S}{R_E}$$

$$R_{if} = \frac{V_S}{I_S} = R_E \left[(1 + h_{FE}) A_g R_i + \frac{R_i}{R_E} + 1 \right]$$


From Problem 12.16:

$$(1 + h_{FE}) A_g \approx h_{FE} A_g = 5 \times 10^5 \text{ mS}$$

$$R_E \approx 0.1 \text{ k}\Omega$$

$$\text{so } R_{if} = (0.1) \left[(5 \times 10^5)(20) + \frac{20}{0.1} + 1 \right]$$
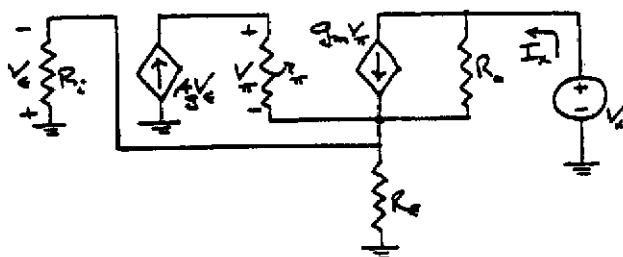
$$\text{or } R_{if} = 10^6 \text{ k}\Omega$$



$$\frac{V_x}{r_\pi} = A_g V_e$$

$$I_X = g_m V_e + \frac{V_X - (-V_e)}{R_o} \quad (1)$$

$$V_e = -(I_X + A_g V_e)(R_E \parallel R_i) \quad (2)$$

$$\text{or } V_e = [1 + A_g(R_E \parallel R_i)] = -I_X(R_E \parallel R_i)$$

Now

$$I_X = g_m A_g r_\pi V_e + \frac{V_X}{R_o} + \frac{V_e}{R_o} \quad (1)$$

$$I_X = \left(g_m A_g r_\pi + \frac{1}{R_o} \right) \left[\frac{-I_X(R_E \parallel R_i)}{1 + A_g(R_E \parallel R_i)} \right] + \frac{V_X}{R_o}$$

$$R_{of} = \frac{V_X}{I_X}$$

$$= R_o \left\{ 1 + \left(g_m A_g r_\pi + \frac{1}{R_o} \right) \left[\frac{(R_E \parallel R_i)}{1 + A_g(R_E \parallel R_i)} \right] \right\}$$

$$g_m r_\pi A_g = h_{FE} A_g = 5 \times 10^5 \text{ mS}$$

$$\text{Let } h_{FE} = 100 \text{ so } A_g = 5 \times 10^3 \text{ mS}$$

$$R_E \parallel R_i = 0.1 \parallel 20 \approx 0.1 \text{ k}\Omega$$


Then

$$R_{of} = 50 \left\{ 1 + \left(5 \times 10^5 + \frac{1}{50} \right) \left[\frac{0.1}{1 + (5 \times 10^3)(0.1)} \right] \right\}$$

$$\text{or } R_{of} = 5.04 \text{ M}\Omega$$

12.19

a.

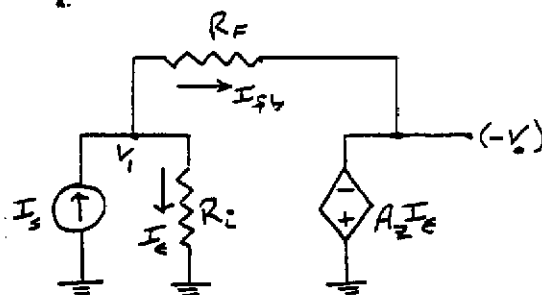Assuming V_i is at virtual ground

$$(-V_o) = -I_{fb} R_F \text{ and } (-V_o) = -A_x I_e \Rightarrow I_e = \frac{V_o}{A_x}$$

$$I_{fb} = I_S - I_e$$

$$\text{So } V_o = (I_S - I_e) R_F = I_S R_F - \left(\frac{V_o}{A_x} \right) R_F$$

$$V_o \left[1 + \frac{R_F}{A_x} \right] = I_S R_F$$

$$\text{so } A_{xf} = \frac{V_o}{I_S} = \frac{R_F}{\left[1 + \frac{R_F}{A_x} \right]} = \frac{A_x R_F}{A_x + R_F}$$

$$\text{or } A_{xf} = \frac{A_x}{1 + A_x \left(\frac{1}{R_F} \right)} = \frac{A_x}{1 + A_x \beta_g}$$

$$\text{b. } \beta_g = \frac{1}{R_F}$$

$$c. \quad 5 \times 10^4 = \frac{5 \times 10^6}{1 + (5 \times 10^4)\beta_g}$$

$$\beta_g = \frac{\frac{5 \times 10^6}{5 \times 10^4} - 1}{5 \times 10^4} \Rightarrow \beta_g = 1.98 \times 10^{-3}$$


$$R_F = \frac{1}{\beta_g} \Rightarrow R_F = 50.5 \text{ k}\Omega$$

$$d. \quad A_z = (0.9)(5 \times 10^6) = 4.5 \times 10^6$$

$$A_{zf} = \frac{4.5 \times 10^6}{1 + (4.5 \times 10^6)(1.98 \times 10^{-3})} = 4.994 \times 10^4$$

$$\frac{\Delta A_{zf}}{A_{zf}} = -\frac{55.4939}{5 \times 10^4} = -1.11 \times 10^{-3} \Rightarrow -0.111\%$$

12.20

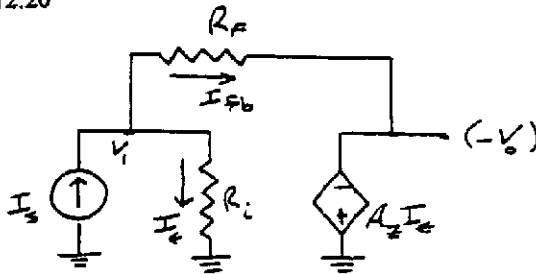

$$V_i = I_e R_i, \quad -V_o = -A_z I_e \Rightarrow V_o = A_z I_e$$

$$I_{Fb} = I_S - I_e \text{ and } -V_o = V_i - I_{Fb} R_F$$

$$-A_z I_e = V_i - (I_S - I_e) R_F$$

$$-A_z \left(\frac{V_i}{R_i} \right) = V_i - I_S R_F + \left(\frac{V_i}{R_i} \right) R_F$$

$$I_S R_F = V_i \left[1 + \frac{A_z}{R_i} + \frac{R_F}{R_i} \right]$$

$$R_{if} = \frac{V_i}{I_S} = \frac{R_F}{1 + \frac{A_z}{R_i} + \frac{R_F}{R_i}}$$

Or, using the results from Problem 12.18.

$$R_{if} = \frac{50.5 \times 10^3}{1 + \frac{5 \times 10^6}{10 \times 10^3} + \frac{50.5 \times 10^3}{10 \times 10^3}}$$


$$= \frac{50.5 \times 10^3}{1 + 500 + 5.05}$$

$$\Rightarrow R_{if} = 99.79 \text{ }\Omega$$

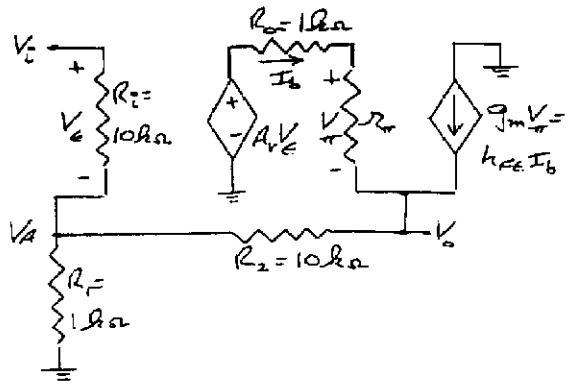12.21

Assume $I_{CQ} = 0.2 \text{ mA}$

$$\text{Then } r_e = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$



$$(1) \quad \frac{V_i - V_A}{R_i} = \frac{V_A}{R_i} + \frac{V_A - V_o}{R_2} \Rightarrow$$

$$\frac{V_i}{R_i} + \frac{V_o}{R_2} = V_A \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_2} \right)$$

Now

$$\frac{V_i}{10} + \frac{V_o}{10} = V_A \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10} \right) \Rightarrow V_i + V_o = V_A (12)$$

$$\text{or } V_A = \frac{1}{12} (V_i + V_o)$$

$$(2) \quad \left(\frac{A_v V_e - V_o}{R_o + r_e} \right) (1 + h_{FE}) = \frac{V_o - V_A}{R_2}$$

where $V_e = V_i - V_A$

Then

$$\left(\frac{A_v (V_i - V_A) - V_o}{R_o + r_e} \right) (1 + h_{FE}) = \frac{V_o - V_A}{R_2}$$

we find

$$\frac{A_v V_i (1 + h_{FE})}{R_o + r_e} - \frac{V_o (1 + h_{FE})}{R_o + r_e} - \frac{V_o}{R_2} = \frac{A_v V_A (1 + h_{FE})}{R_o + r_e} - \frac{V_A}{R_2}$$

Then

$$\frac{(5 \times 10^3)(101)V_i}{14} - \frac{V_o(101)}{14} - \frac{V_o}{10} = \frac{(5 \times 10^3)(101)V_A}{14} - \frac{V_A}{10}$$

$$= \left(\frac{(5 \times 10^3)(101)}{14} - \frac{1}{10} \right) V_A$$

Rearranging terms, we find

$$A_v = \frac{V_o}{V_i} = \frac{10.97}{1}$$


$$R_v = \frac{V_i}{I_i} = \frac{V_i}{\left(\frac{V_i - V_A}{R_i} \right)} = \left(\frac{V_i}{V_i - V_A} \right) R_i$$

$$V_A = \frac{1}{12} (V_i + V_o) = \frac{1}{12} (V_i + 10.97 V_i) = 0.9975 V_i$$

Then

$$R_v = \left(\frac{1}{1 - 0.9975} \right) (10 \text{ k}\Omega) \Rightarrow R_v = 4 \text{ M}\Omega$$

To find the output resistance:

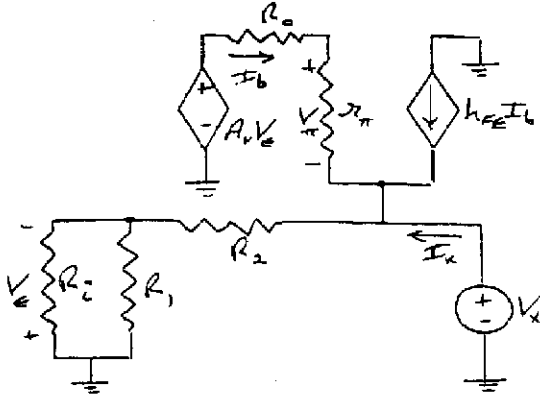

$$I_x + \frac{(A V_x - V_x)(1 + h_{FE})}{R_o + r_{\pi}} = \frac{V_x}{R_2 + R_1 \parallel R_L}$$

$$V_x = -\left(\frac{R_1 \parallel R_L}{R_1 \parallel R_L + R_2}\right) V_x$$

Now

$$R_1 \parallel R_L = 1 \parallel 10 = 0.909$$

Then

$$V_x = -0.0833 V_x$$

Now

$$I_x = V_x \left\{ \left[\frac{(5 \times 10^3)(0.0833) + 1}{1 + 13} \right] (101) + \frac{1}{10 + 0.909} \right\}$$

$$= V_x \{ 3.012 \times 10^3 + 0.0917 \}$$

Or

$$\frac{V_x}{I_x} = R_o = 332 \times 10^{-4} \text{ k}\Omega \Rightarrow R_o = 0.332 \Omega$$

12.22

a. Neglecting base currents

$$I_{C2} = 0.5 \text{ mA}, V_{C2} = 12 - (0.5)(22.6) = 0.7 \text{ V}$$

$$I_{C1} = 0.5 \text{ mA}$$

$$\Rightarrow v_o = 0$$


$$\text{Then } I_{C3} = 2 \text{ mA}$$

$$b. r_{\pi 1} = r_{\pi 2} = \frac{h_{FE} \cdot V_T}{I_{C1}} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(100)(0.026)}{2} = 1.3 \text{ k}\Omega$$
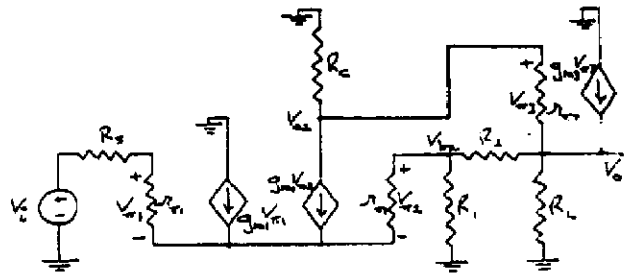
$$g_{m3} = \frac{2}{0.026} = 76.92 \text{ mA/V}$$



$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + g_{m1} V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 1}} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left(\frac{1}{r_{\pi 1}} + g_{m1} \right) = 0$$

$$\Rightarrow V_{\pi 1} = -V_{\pi 2} \quad (1)$$

$$V_i = \frac{V_{\pi 1}}{r_{\pi 1}} (R_S + r_{\pi 1}) - V_{\pi 2} + V_{b2}$$

or

$$V_i = V_{\pi 1} \left(1 + \frac{R_S}{r_{\pi 1}} \right) - V_{\pi 2} + V_{b2}$$

$$\text{But } V_{\pi 2} = -V_{\pi 1}$$

so

$$V_i = V_{\pi 1} \left(2 + \frac{R_S}{r_{\pi 1}} \right) + V_{b2} \quad (2)$$

$$\frac{V_{o2}}{R_C} + g_{m1} V_{\pi 2} + \frac{V_{o2} - V_o}{r_{\pi 3}} = 0 \quad (3)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_o}{R_L} + \frac{V_o - V_{b2}}{R_2}$$

$$V_{\pi 1} = V_{o2} - V_o$$

so

$$(V_{o2} - V_o) \left(\frac{1 + h_{FE}}{r_{\pi 3}} \right) = V_o \left(\frac{1}{R_L} + \frac{1}{R_2} \right) - \frac{V_{b2}}{R_2} \quad (4)$$

$$\frac{V_{b2} - V_o}{R_2} + \frac{V_{b2}}{R_1} + \frac{V_{\pi 2}}{r_{\pi 1}} = 0 \quad (5)$$

Substitute numbers into (2), (3), (4) and (5):

$$V_i = -V_{\pi 2} \left(2 + \frac{1}{5.2} \right) + V_{b2}$$

$$V_i = -V_{\pi 2} (2.192) + V_{b2} \quad (2)$$

$$V_{o2} \left(\frac{1}{22.6} + \frac{1}{1.3} \right) + (19.23) V_{\pi 2} - V_o \left(\frac{1}{1.3} \right) = 0$$

$$V_{o2} (0.8135) + (19.23) V_{\pi 2} - (0.7692) V_o = 0 \quad (3)$$

$$V_{o2} \left(\frac{101}{1.3} \right) = V_o \left(\frac{101}{1.3} + \frac{1}{4} + \frac{1}{50} \right) - V_{o2} \left(\frac{1}{50} \right)$$

$$V_{o2}(77.69) = V_o(77.96) - V_{o2}(0.02) \quad (4)$$

$$V_{o2} \left(\frac{1}{50} + \frac{1}{10} \right) - V_o \left(\frac{1}{50} \right) + V_{\pi 2} \left(\frac{1}{5.2} \right) = 0$$

$$V_{o2}(0.120) - V_o(0.020) + V_{\pi 2}(0.1923) = 0 \quad (5)$$

From (2): $V_{o2} = V_i + V_{\pi 2}(2.192)$. Substitute in (4) and (5) to obtain:

$$V_{o2}(77.69) = V_o(77.96) - [V_i + V_{\pi 2}(2.192)](0.02) \quad (4')$$

$$[V_i + V_{\pi 2}(2.192)](0.120) - V_o(0.020) + V_{\pi 2}(0.1923) = 0 \quad (5')$$

So we now have the following three equations:

$$V_{o2}(0.8135) + (19.23)V_{\pi 2} - (0.7692)V_o = 0 \quad (3)$$

$$V_{o2}(77.69) = V_o(77.96) - V_i(0.02) - V_{\pi 2}(0.04384) \quad (4')$$

$$(0.120)V_i + V_{\pi 2}(0.4553) - V_o(0.020) = 0 \quad (5')$$

From (3): $V_{o2} = V_o(0.9455) - V_{\pi 2}(23.64)$. Substitute for V_{o2} in (4') to obtain:

$$(77.69)[V_o(0.9455) - V_{\pi 2}(23.64)] = V_o(77.96) - V_i(0.02) - V_{\pi 2}(0.04384)$$

or

$$0 = V_o(4.504) - V_i(0.02) + V_{\pi 2}(1836.5)$$

Next, solve (5') for $V_{\pi 2}$:

$$(0.120)V_i + V_{\pi 2}(0.4553) - V_o(0.020) = 0$$

$$V_{\pi 2} = V_o(0.04393) - V_i(0.2636)$$

Finally,

$$0 = V_o(4.504) - V_i(0.02) + (1836.5)[V_o(0.04393) - V_i(0.2636)]$$

$$0 = V_o(85.18) - V_i(484.12)$$

So

$$A_{v_f} = \frac{V_o}{V_i} = \frac{484.12}{85.18} \Rightarrow A_{v_f} = 5.68$$

12.23

a. $R_{TH} = R_1 \parallel R_2 = 400 \parallel 75 = 63.2 \text{ k}\Omega$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{75}{75 + 400} \right) (10) = 1.579 \text{ V}$$

$$I_{BQ1} = \frac{1.579 - 0.7}{63.2 + (121)(0.5)} = 0.007106 \text{ mA}$$

$$I_{CQ1} = 0.853 \text{ mA}$$

$$V_{C1} = 10 - (0.853)(8.8) = 2.49 \text{ V}$$

$$I_{C2} \approx \frac{2.49 - 0.7}{3.6} = 0.497 \text{ mA}$$

$$V_{C2} = 10 - (0.497)(13) = 3.54 \text{ V}$$

$$I_{C3} \approx \frac{3.54 - 0.7}{1.4} = 2.03 \text{ mA}$$

Then

$$r_{\pi 1} = \frac{(120)(0.026)}{0.853} = 3.66 \text{ k}\Omega$$

$$g_{m1} = \frac{0.853}{0.026} = 32.81 \text{ mA/V}$$


$$r_{\pi 2} = \frac{(120)(0.026)}{0.497} = 6.28 \text{ k}\Omega$$

$$g_{m2} = \frac{0.497}{0.026} = 19.12 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(120)(0.026)}{2.03} = 1.54 \text{ k}\Omega$$

$$g_{m3} = \frac{2.03}{0.026} = 78.08 \text{ mA/V}$$

b.

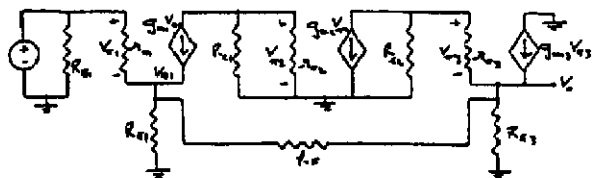

$$V_i = V_{\pi 1} + V_{e1} \Rightarrow V_{e1} = V_i - V_{\pi 1} \quad (1)$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_o}{R_F} \quad (2)$$

$$V_{\pi 2} = -(g_{m1} V_{\pi 1})(R_{C1} \parallel r_{\pi 2}) \quad (3)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3} + V_o}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (4)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_o}{R_{E3}} + \frac{V_o - V_{e1}}{R_F} \quad (5)$$

Substitute numbers in (2), (3), (4) and (5):

$$V_{\pi 1} \left(\frac{1}{3.66} + 32.81 \right) = (V_i - V_{\pi 1}) \left(\frac{1}{0.5} + \frac{1}{10} \right) - \frac{V_0}{10}$$

or $V_{\pi 1}(35.18) = V_i(2.10) - V_0(0.10)$ (2)

$$V_{\pi 2} = -(32.81)V_{\pi 1}(88 \parallel 6.28)$$

or $V_{\pi 2} = -V_{\pi 1}(120.2)$ (3)

$$(19.12)V_{\pi 2} + \frac{V_{\pi 3}}{13} + \frac{V_0}{13} + \frac{V_{\pi 3}}{1.54} = 0$$

or

$$V_{\pi 2}(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$
 (4)

$$V_{\pi 3} \left(\frac{1}{1.54} + 78.08 \right) = V_0 \left(\frac{1}{1.4} + \frac{1}{10} \right) - \frac{V_i - V_{\pi 1}}{10}$$

or

$$V_{\pi 3}(78.73) = V_0(0.8143) - V_i(0.10) + V_{\pi 1}(0.10)$$
 (5)

Now substituting $V_{\pi 2} = -V_{\pi 1}(120.2)$ in (4):

$$(19.12)[-V_{\pi 1}(120.2)] + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

or

$$-V_{\pi 1}(2298.2) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

Then

$$V_{\pi 3} = V_{\pi 1}(3164.3) - V_0(0.1059)$$

Substituting $V_{\pi 3} = V_{\pi 1}(3164.3) - V_0(0.1059)$ in (5):

$$(78.73)[V_{\pi 1}(3164.3) - V_0(0.1059)] = V_0(0.8143) - V_i(0.10) + V_{\pi 1}(0.10)$$

or

$$V_{\pi 1}(2.49 \times 10^5) - V_0(9.152) = -V_i(0.10)$$

Then

$$V_{\pi 1} = V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$$

Now substituting $V_{\pi 1} = V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$ in (2):

$$(35.18)[V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})] = V_i(2.10) - V_0(0.10)$$

or $V_0(0.1013) = V_i(2.10)$

So $\frac{V_0}{V_i} = 20.7$

c. $R_{if} = \frac{V_i}{I_i}$ and $I_i = I_{RB1} + I_{b1}$

$$I_{RB1} = \frac{V_i}{R_{B1}}$$

$$I_{b1} = \frac{V_{\pi 1}}{r_{\pi 1}}$$

Now

$$V_{\pi 1} = (20.7V_i)(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$$

$$V_{\pi 1} = V_i(7.60 \times 10^{-4})$$

Then

$$R_{if} = \frac{V_i}{\frac{V_i}{63.2} + \frac{V_i(7.60 \times 10^{-4})}{3.66}}$$

$$= \frac{1}{0.01582 + 2.077 \times 10^{-4}}$$

or $R_{if} = 62.4 \text{ k}\Omega$

d. To determine R_{of} :

Equation (1) is modified to $V_{\pi 1} + V_{e1} = 0$ ($V_i = 0$)

Equation (5) is modified to:

$$V_{\pi 3}(78.73) + I_X = V_0(0.8143) + V_{\pi 1}(0.10)$$
 (5)

Now

$$V_{\pi 1}(35.18) = -V_0(0.10)$$
 (2)

$$V_{\pi 2} = -V_{\pi 1}(120.2)$$
 (3)

$$V_{\pi 2}(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$
 (4)

Now

$$V_{\pi 1} = -V_0(0.002843)$$

so

$$V_{\pi 2} = -(-V_0)(0.002843)(120.2)$$

$$V_{\pi 2} = V_0(0.3417)$$

Then

$$V_0(0.3417)(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

or

$$V_{\pi 3} = -V_0(9.101)$$
 (4)

So then

$$-V_0(9.101)(78.73) + I_X = V_0(0.8143) + (0.10)(-V_0)(0.002843)$$

or


$$I_X = V_0(717.3)$$
 (5)

or

$$R_{of} = \frac{V_0}{I_X} = 0.00139 \text{ k}\Omega \Rightarrow \underline{R_{of} = 1.39 \text{ }\Omega}$$

12.24

b.

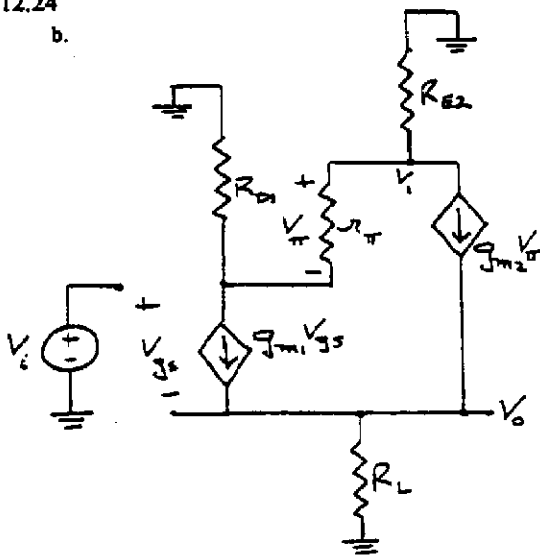

$$V_o = (g_{m1} V_{gs} + g_{m2} V_{\pi}) R_L \quad (1)$$

$$V_i = V_{gs} + V_o \quad (2)$$

$$\begin{aligned} \frac{V_{\pi}}{r_{\pi}} + g_{m2} V_{\pi} + \frac{V_i}{R_{E2}} &= 0 \\ \Rightarrow V_{\pi} \left(\frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{V_i}{R_{E2}} &= 0 \end{aligned} \quad (3)$$

$$\begin{aligned} \frac{V_{\pi}}{r_{\pi}} &= g_{m1} V_{gs} + \frac{V_i - V_{\pi}}{R_{D1}} = 0 \\ \text{or} \quad V_i &= R_{D1} \left[\frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_{D1}} - g_{m1} V_{gs} \right] \end{aligned} \quad (4)$$

Then

$$V_{\pi} \left(\frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{R_{D1}}{R_{E2}} \left[\frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_{D1}} - g_{m1} V_{gs} \right] = 0 \quad (3)$$

$$V_{\pi} \left\{ \left(\frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{R_{D1}}{R_{E2} r_{\pi}} + \frac{1}{R_{E2}} \right\} = g_{m1} \left(\frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

Let

$$V_{\pi} \cdot \frac{1}{R_{eq}} = g_{m1} \left(\frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

$$\text{so } V_{\pi} = g_{m1} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

Then

$$V_o = \left[g_{m1} V_{gs} + g_{m1} g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) V_{gs} \right] R_L \quad (1)$$

so

$$V_o = g_{m1} R_L \left[1 + g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) \right] (V_i - V_o)$$

so

$$A_v = \frac{V_o}{V_i} = \frac{g_{m1} R_L \left[1 + g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) \right]}{1 + g_{m1} R_L \left[1 + g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) \right]}$$

c. Set $V_i = 0$

$$I_X + g_{m1} V_{gs} + g_{m2} V_{\pi} = \frac{V_X}{R_L}$$

$$V_{gs} = -V_X$$

From part (b), we have

$$V_{\pi} = g_{m1} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) V_{gs} = -g_{m1} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right) V_X$$

Then


$$\frac{I_X}{V_X} = \frac{1}{R_o} = \frac{1}{R_L} + g_{m1} g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right)$$

or

$$R_o = R_L \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{m1} g_{m2} R_{eq} \left(\frac{R_{D1}}{R_{E2}} \right)}$$

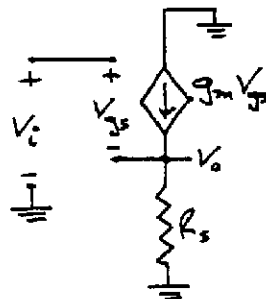12.25

$$\text{a. } g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$$



$$V_o = (g_m V_{gs}) R_S$$

$$V_i = V_{gs} + V_o \text{ so } V_{gs} = V_i - V_o$$

Then

$$V_o = g_m R_S (V_i - V_o)$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} = \frac{1(2)}{1 + (1)(2)} \Rightarrow A_v = 0.667$$

To determine R_{of}

$$I_X + g_m V_{gs} = \frac{V_X}{R_S} \text{ and } V_{gs} = -V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = g_m + \frac{1}{R_S}$$

$$\text{so } R_{of} = \frac{1}{g_m} \parallel R_S = \frac{1}{1} \parallel 2 \Rightarrow R_{of} = 0.667 \text{ k}\Omega$$

b. For $K_n = 0.8 \text{ mA/V}^2$

$$g_m = 2\sqrt{(0.8)(0.5)} = 1.265 \text{ mA/V}$$

$$A_v = \frac{(1.265)(2)}{1 + (1.265)(2)} = 0.7167$$

$$\frac{\Delta A_f}{A_f} = \frac{0.7167 - 0.667}{0.667} \Rightarrow 7.45\% \text{ increase}$$

$$R_{of} = \frac{1}{1.265} \parallel 2 = 0.7905 \parallel 2$$

$$R_{of} = 0.5666$$

$$\frac{\Delta R_{of}}{R_{of}} = \frac{0.5666 - 0.667}{0.667} \Rightarrow 15.05\% \text{ decrease}$$

12.26

dc analysis:

$$R_{TH1} = 150 \parallel 47 = 35.8 \text{ k}\Omega,$$

$$V_{TH1} = \left(\frac{47}{47 + 150} \right) (25) = 5.96 \text{ V}$$

$$R_{TH2} = 33 \parallel 47 = 19.4 \text{ k}\Omega,$$

$$V_{TH2} = \left(\frac{33}{33 + 47} \right) (25) = 10.3 \text{ V}$$

$$I_{B1} = \frac{5.96 - 0.7}{35.8 + (51)(4.8)} = 0.0187 \text{ mA}$$

$$I_{C1} = (50)(0.0187) = 0.935 \text{ mA}$$

$$I_{B2} = \frac{10.3 - 0.7}{19.4 + (51)(4.7)} = 0.03705 \text{ mA}$$


$$I_{C2} = (50)(0.03705) = 1.85 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.935} = 1.39 \text{ k}\Omega;$$

$$r_{\pi 2} = \frac{(50)(0.026)}{1.85} = 0.703 \text{ k}\Omega$$

$$g_{m1} = \frac{0.935}{0.026} = 35.96 \text{ mA/V}$$
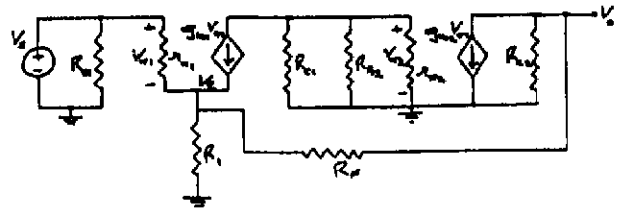
$$g_{m2} = \frac{1.85}{0.026} = 71.15 \text{ mA/V}$$



$$V_S = V_{\pi 1} + V_e \quad (1)$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_e}{R_1} + \frac{V_e - V_o}{R_F} \quad (2)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1}} + \frac{V_{\pi 2}}{R_{B2}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (3)$$

$$g_{m2} V_{\pi 2} + \frac{V_o}{R_{C2}} + \frac{V_o - V_e}{R_F} = 0 \quad (4)$$

Substitute numerical values in (2), (3) and (4):

$$V_e = V_S - V_{\pi 1} \quad (1)$$

$$\begin{aligned} \frac{V_{\pi 1}}{1.39} + (35.96)V_{\pi 1} \\ = (V_S - V_{\pi 1}) \left(\frac{1}{0.1} + \frac{1}{4.7} \right) - V_o \left(\frac{1}{4.7} \right) \end{aligned}$$

or

$$V_{\pi 1}(46.89) = V_S(10.213) - V_o(0.2128) \quad (2)$$

$$(35.96)V_{\pi 1} + V_{\pi 2} \left(\frac{1}{10} + \frac{1}{19.4} + \frac{1}{0.703} \right) = 0$$

or

$$(35.96)V_{\pi 1} + V_{\pi 2}(1.374) = 0 \quad (3)$$

$$\begin{aligned} (71.15)V_{\pi 2} + V_o \left(\frac{1}{4.7} + \frac{1}{4.7} \right) \\ - (V_S - V_{\pi 1}) \left(\frac{1}{4.7} \right) = 0 \end{aligned}$$

or

$$\begin{aligned} (71.15)V_{\pi 2} + V_o(0.4255) - V_S(0.2128) \\ + V_{\pi 1}(0.2128) = 0 \end{aligned} \quad (4)$$

$$\text{From (3): } V_{\pi 2} = -V_{\pi 1}(22.85)$$

Then substitute in (4):

$$\begin{aligned} -(71.15)V_{\pi 1}(22.85) + V_o(0.4255) \\ - V_S(0.2128) + V_{\pi 1}(0.2128) = 0 \end{aligned}$$

or

$$-V_{\pi 1}(1625.6) + V_o(0.4255) - V_S(0.2128) = 0$$

$$\text{From (2): } V_{\pi 1} = V_S(0.2178) - V_o(0.004538)$$

Then

$$\begin{aligned} -(1625.6)[V_S(0.2178) - V_o(0.004538)] \\ + V_o(0.4255) - V_S(0.2128) = 0 \end{aligned}$$

$$\text{or } -V_S(354.3) + V_O(7.802) = 0$$


Finally

$$\Rightarrow \frac{V_O}{V_S} = 45.4$$

12.27

For example, use the circuit shown in Figure 12.23

12.28

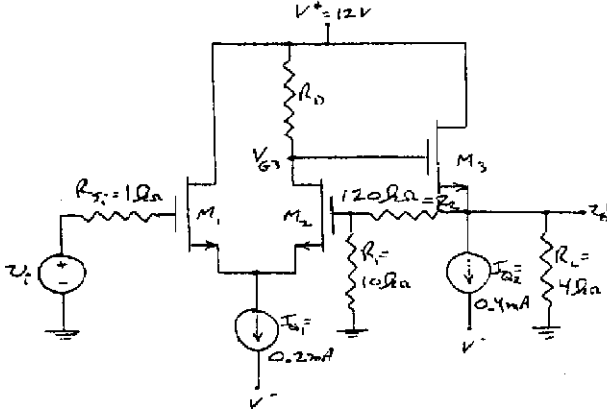

$$\text{For } M_3: K_{n3} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_3 \quad \text{Let } \left(\frac{W}{L} \right)_3 = 25$$

$$\text{Then } K_{n3} = \left(\frac{0.080}{2} \right) (25) = 1 \text{ mA/V}^2$$


Want $v_o = 0$ for $v_i = 0$, so that

$$I_{D3} = I_{D2} = 0.4 = 1 \cdot (V_{GS3} - V_{TN})^2$$

$$\text{Then } V_{GS3} = \sqrt{\frac{0.4}{1}} + 2 = 2.63 \text{ V}$$

$$\text{For } V_{GS3} = 2.63 \text{ V} \Rightarrow V_{DS3} = 12 - I_{D3} R_{D3}$$
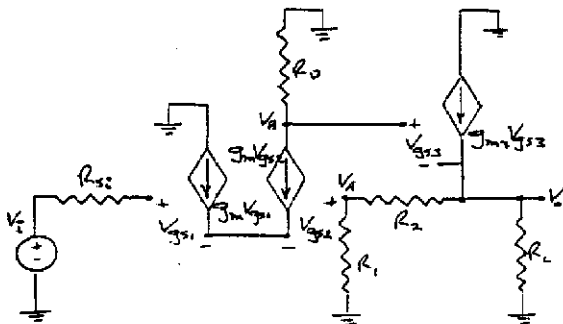
$$\text{Or } 2.63 = 12 - (0.1) R_{D3} \Rightarrow R_{D3} = 93.7 \text{ k}\Omega$$



$$g_{m3} = 2\sqrt{K_{n3} I_{D3}} = 2\sqrt{(1)(0.4)} = 1.26 \text{ mA/V}$$

$$V_A = \left(\frac{R_1}{R_1 + R_2} \right) (V_o) = \left(\frac{10}{120 + 10} \right) (V_o) = 0.0769 V_o$$

(Small amount of feedback)

$$(1) V_i = V_{gs1} - V_{gs2} + V_A$$

$$(2) g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$$

Then

$$V_i = -2V_{gs2} + V_A \Rightarrow V_{gs2} = \frac{1}{2}(V_A - V_i)$$

$$V_{gs2} = 0.03846 V_o - 0.5 V_i$$

$$(3) V_B = -g_m V_{gs2} R_D = -g_m R_D [0.03846 V_o - 0.5 V_i]$$

$$(4) V_{gs3} = V_B - V_o \quad \text{and} \quad V_o = g_{m3} V_{gs3} [R_L \parallel (R_1 + R_2)]$$

So

$$V_o = g_{m3} [R_L \parallel (R_1 + R_2)] (V_B - V_o)$$

Then

$$V_o = g_{m3} [R_L \parallel (R_1 + R_2)] [-g_m R_D (0.03846 V_o - 0.5 V_i) - V_o]$$

Or

$$V_o [1 + g_{m3} [R_L \parallel (R_1 + R_2)] g_m R_D (0.03846 + 1)] = g_{m3} [R_L \parallel (R_1 + R_2)] [0.5 g_m R_D] V_i$$

Now

$$R_L \parallel (R_1 + R_2) = 4 \parallel 130 = 3.88$$

So

$$V_o [1 + (1.26)(3.88) g_{m3} (93.7)(0.03846 + 1)] = (1.26)(3.88)(0.5) g_{m3} (93.7) V_i$$

Rearranging terms, we find

$$\frac{V_o}{V_i} = \frac{229 g_{m3}}{5.89 + 17.6 g_{m3}} = 10 \Rightarrow g_{m3} = 1.11 \text{ mA/V}$$

We have

$$g_{m3} = 2\sqrt{\left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right) I_{D3}} \Rightarrow$$

$$1.11 = 2\sqrt{\left(\frac{0.080}{2} \right) \left(\frac{W}{L} \right) (0.1)} \Rightarrow$$

$$\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_1 = 77$$

12.29

Assuming an ideal op-amp, then from Equation (12.58)

$$\frac{I_o}{I_S} = 1 + \frac{R_1}{R_2} = \frac{20}{0.2} = 100$$

$$\text{Then } \frac{R_1}{R_2} = 99$$

For example, set $R_2 = 5 \text{ k}\Omega$ and $R_1 = 495 \text{ k}\Omega$

12.30

$$(a) I_{C1} = \left(\frac{h_{FE}}{1 + h_{FE}} \right) I_{E1} = \left(\frac{100}{101} \right) (0.2) = 0.198 \text{ mA}$$

$$V_{C1} = 10 - (0.198)(40) = 2.08 \text{ V}$$

$$I_{E2} = \frac{2.08 - 0.7}{1} = 1.38 \text{ mA}$$

$$I_{C2} = \left(\frac{100}{101} \right) (1.38) = 1.37 \text{ mA}$$

For Q_1 :

$$r_{\pi 1} = \frac{(100)(0.026)}{0.198} = 13.1 \text{ k}\Omega$$


$$g_{m1} = \frac{0.198}{0.026} = 7.62 \text{ mA/V}$$

For Q_2 :

$$r_{\pi 2} = \frac{(100)(0.026)}{1.37} = 1.90 \text{ k}\Omega$$

$$g_{m2} = \frac{1.37}{0.026} = 52.7 \text{ mA/V}$$

(b)

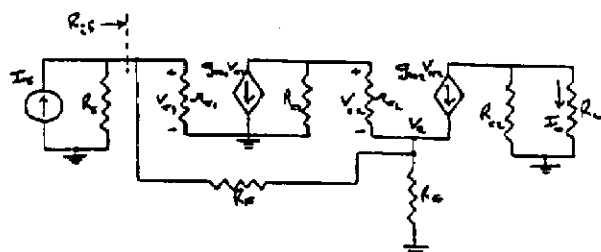

$$I_S = \frac{V_{\pi 1}}{R_S} + \frac{V_{\pi 1}}{r_{\pi 1}} + \frac{V_{\pi 1} - V_c}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2} + V_c}{R_{C1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_c}{R_E} + \frac{V_c - V_{\pi 1}}{R_F} \quad (3)$$

Substitute numerical values in (1), (2), and (3):

$$I_S = V_{\pi 1} \left(\frac{1}{10} + \frac{1}{13.1} + \frac{1}{10} \right) - V_c \left(\frac{1}{10} \right)$$

$$I_S = V_{\pi 1}(0.2763) - V_c(0.10) \quad (1)$$

$$(7.62)V_{\pi 1} + V_{\pi 2} \left(\frac{1}{40} + \frac{1}{1.90} \right) + V_c \left(\frac{1}{40} \right) = 0$$

$$(7.62)V_{\pi 1} + V_{\pi 2}(0.5513) + V_c(0.025) = 0 \quad (2)$$

$$V_{\pi 2} \left(\frac{1}{1.90} + 52.7 \right) = V_c \left(\frac{1}{1} + \frac{1}{10} \right) - V_{\pi 1} \left(\frac{1}{10} \right)$$

$$V_{\pi 2}(53.23) = V_c(1.10) - V_{\pi 1}(0.10) \quad (3)$$

From (3),

$$V_c = V_{\pi 2}(48.39) + V_{\pi 1}(0.0909)$$

Substituting into (1),

$$I_S = V_{\pi 1}(0.2763) - (0.10)[V_{\pi 2}(48.39) + V_{\pi 1}(0.0909)]$$

or

$$I_S = V_{\pi 1}(0.2672) - V_{\pi 2}(4.839) \quad (1')$$

and substituting into (2),

$$(7.62)V_{\pi 1} + V_{\pi 2}(0.5513) + (0.025)[V_{\pi 2}(48.39) + V_{\pi 1}(0.0909)] = 0$$

or

$$(7.622)V_{\pi 1} + V_{\pi 2}(1.761) = 0$$

$$\Rightarrow V_{\pi 1} = -V_{\pi 2}(0.2310) \quad (2')$$

Then substituting (2') into (1'), we obtain

$$I_S = (0.2672)(-V_{\pi 2})(0.2310) - V_{\pi 2}(4.839)$$

or

$$I_S = -V_{\pi 2}(4.901)$$

Now

$$I_O = -g_{m2} V_{\pi 2} \left(\frac{R_{C2}}{R_{C2} + R_L} \right)$$

$$= -(52.7) \left(\frac{2}{2 + 0.5} \right) V_{\pi 2} = -(42.16)V_{\pi 2}$$

Then

$$I_O = -(42.16) \left(\frac{-I_S}{4.901} \right)$$

or

$$A_v = \frac{I_O}{I_S} = 8.60$$

$$(c) R_i = \frac{V_{\pi 1}}{I_S} \text{ and } R_i = R_S \parallel R_{if}$$

We had

$$V_{\pi 1} = -V_{\pi 2}(0.2310) \text{ and } I_S = -V_{\pi 2}(4.901)$$

so

$$I_S = - \left(\frac{-V_{\pi 1}}{0.2310} \right) (4.901) = V_{\pi 1}(21.22)$$

Then

$$R_i = \frac{V_{\pi 1}}{I_S} = \frac{1}{21.22} = 0.04713$$

Finally

$$0.04713 = \frac{10R_{if}}{10 + R_{if}} \Rightarrow$$

$$R_{if} = 47.4 \Omega$$

12.31

(a) Using Figure 12.25

$$I_i = \frac{V_{\pi 1}}{R_S \parallel R_{B1} \parallel r_{\pi 1}} + \frac{V_{\pi 1} - V_{\pi 2}}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1} \parallel R_{B2}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0$$

$$= g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1} \parallel R_{B2} \parallel r_{\pi 2}} \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_{e2}}{R_{E2}} + \frac{V_{e2} - V_{\pi 1}}{R_F} \quad (3)$$

$$I_0 = -\left(\frac{R_{C2}}{R_{C2} + R_L}\right)(g_{m2} V_{\pi 2}) \quad (4)$$

$$I_i = \frac{V_{\pi 1}}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F} - \frac{V_{e2}}{R_F} \quad (1')$$

so that

$$V_{e2} = \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) V_{\pi 1} - R_F I_i$$

Then

$$V_{\pi 2} \left(\frac{1 + \beta_2}{r_{\pi 2}}\right) = \left(\frac{1}{R_{E2}} + \frac{1}{R_F}\right) \times \left\{ \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) V_{\pi 1} - R_F I_i \right\} - \frac{V_{\pi 1}}{R_F} \quad (3')$$

From (2):

$$V_{\pi 1} = -\frac{V_{\pi 2}}{g_{m1}} \cdot \frac{1}{(R_{C1} \parallel R_{B2} \parallel r_{\pi 2})}$$

Then

$$V_{\pi 2} \left(\frac{1 + \beta_2}{r_{\pi 2}}\right) = \frac{V_{\pi 2}}{g_{m1} R_F} \cdot \frac{1}{R_{C1} \parallel R_{B2} \parallel r_{\pi 2}} \times \left\{ 1 - \left(1 + \frac{R_F}{R_{E2}}\right) \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) \right\} - \left(1 + \frac{R_F}{R_{E2}}\right) I_i$$

Solve for $V_{\pi 2}$ and substitute into Equation 4.

$$(b) R_{TH1} = 20 \parallel 80 = 16 \text{ k}\Omega = R_{B1}$$

$$V_{TH1} = \left(\frac{20}{100}\right)(10) = 2 \text{ V}$$

$$I_{BQ1} = \frac{2 - 0.7}{16 + (101)(1)} = 0.0111 \text{ mA} \Rightarrow$$

$$I_{CQ1} = 1.11 \text{ mA}$$

$$R_{TH2} = 15 \parallel 85 = 12.75 \text{ k}\Omega$$

$$V_{TH2} = \left(\frac{15}{15 + 85}\right)(10) = 1.5 \text{ V}$$

$$I_{BQ2} = \frac{1.5 - 0.7}{12.75 + (101)(0.5)} = 0.0126 \text{ mA} \Rightarrow$$

$$I_{CQ2} = 1.26 \text{ mA}$$

$$g_{m1} = \frac{1.11}{0.026} = 42.69 \text{ mA/V}$$

$$g_{m2} = \frac{1.26}{0.026} = 48.46 \text{ mA/V}$$

$$r_{\pi 1} = \frac{(100)(0.026)}{1.11} = 2.34 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{(100)(0.026)}{1.26} = 2.06 \text{ k}\Omega$$

From part (a)

$$V_{\pi 2} \left(\frac{101}{2.06}\right) = \frac{V_{\pi 2}}{(42.69)(10)} \cdot \frac{1}{2 \parallel 12.75 \parallel 2.06} \times \left\{ 1 - \left(1 + \frac{10}{0.5}\right) \left(\frac{10}{10000 \parallel 16 \parallel 2.34 \parallel 10}\right) \right\} - \left(1 + \frac{10}{0.5}\right) I_i$$

So

$$V_{\pi 2}(49.34) = -(21)I_i$$

or

$$V_{\pi 2} = -0.4256 I_i$$

Now

$$I_o = -\left(\frac{4}{4 + 4}\right)(48.46)(-0.4256)I_i$$

or

$$A_i = \frac{I_o}{I_i} = 10.3$$

From Example 12.9, computer analysis showed $A_i = 9.58$. The difference in results is usually in the calculation of quiescent currents which leads to slight differences in the small-signal parameter values.

12.32

$$a. \quad R_{TH} = 13.5 \parallel 38.3 = 9.98 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{13.5}{13.5 + 38.3}\right)(10) = 2.606 \text{ V}$$

$$I_{C1} = \frac{(120)(2.606 - 0.7)}{9.98 + (121)(1)} = 1.75 \text{ mA}$$

$$V_{C1} = 10 - (1.75)(3) = 4.75 \text{ V}$$

$$I_{C2} \approx \frac{4.75 - 0.7}{8.1} = 0.50 \text{ mA}$$


$$r_{\pi 1} = \frac{(120)(0.026)}{1.75} = 1.78 \text{ k}\Omega$$

$$g_{m1} = \frac{1.75}{0.026} = 67.31 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(120)(0.026)}{0.50} = 6.24 \text{ k}\Omega$$

$$g_{m2} = \frac{0.50}{0.026} = 19.23 \text{ mA/V}$$

b.

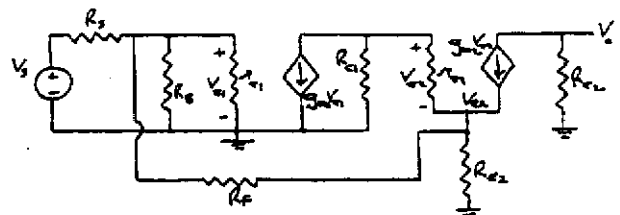

$$\frac{V_S - V_{\pi 1}}{R_S} = \frac{V_{\pi 1}}{R_B \| r_{\pi 1}} + \frac{V_{\pi 1} - V_{e2}}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2} + V_{e2}}{R_{C1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_{e2}}{R_{E2}} + \frac{V_{e2} - V_{\pi 1}}{R_F} \quad (3)$$

and

$$V_0 = -(g_{m2} V_{\pi 2}) R_{C2} \quad (4)$$

Substitute numerical values in (1), (2), and (3):

$$\begin{aligned} \frac{V_S}{0.6} &= V_{\pi 1} \left[\frac{1}{0.6} + \frac{V_{\pi 1}}{9.98 \| 1.78} + \frac{1}{1.2} \right] - \frac{V_{e2}}{1.2} \\ \text{or} \\ V_S(1.667) &= V_{\pi 1}(4.011) - V_{e2}(0.8333) \end{aligned} \quad (1)$$

$$\begin{aligned} (67.31)V_{\pi 1} + V_{\pi 2} \left(\frac{1}{3} + \frac{1}{6.24} \right) + \frac{V_{e2}}{3} &= 0 \\ \text{or} \\ V_{\pi 1}(67.31) + V_{\pi 2}(0.4936) + V_{e2}(0.3333) &= 0 \end{aligned} \quad (2)$$

$$\begin{aligned} V_{\pi 2} \left(\frac{1}{6.24} + 19.23 \right) &= \frac{V_{e2}}{8.1} + \frac{V_{e2}}{1.2} - \frac{V_{\pi 1}}{1.2} \\ \text{or} \\ V_{\pi 2}(19.39) &= V_{e2}(0.9568) - V_{\pi 1}(0.8333) \end{aligned} \quad (3)$$

From (1)

$$V_{e2} = V_{\pi 1}(4.813) - V_S(2.00)$$

Then

$$\begin{aligned} V_{\pi 1}(67.31) + V_{\pi 2}(0.4936) \\ + (0.3333)[V_{\pi 1}(4.813) - V_S(2.00)] &= 0 \\ \text{or} \\ V_{\pi 1}(68.91) + V_{\pi 2}(0.4936) - V_S(0.6666) &= 0 \end{aligned} \quad (2')$$

and

$$\begin{aligned} V_{\pi 2}(19.39) \\ = (0.9568)[V_{\pi 1}(4.813) - V_S(2.00)] - V_{\pi 1}(0.8333) \\ \text{or} \\ V_{\pi 2}(19.39) = V_{\pi 1}(3.772) - V_S(1.914) \end{aligned} \quad (3')$$

We find

$$V_{\pi 1} = V_S(0.009673) - V_{\pi 2}(0.007163)$$

Then

$$\begin{aligned} V_{\pi 2}(19.39) \\ = (3.772)[V_S(0.009673) - V_{\pi 2}(0.007163)] \\ - V_S(1.914) \end{aligned}$$

$$V_{\pi 2}(19.42) = V_S(-1.878) \text{ or } V_{\pi 2} = -V_S(0.09670)$$

so that

$$V_0 = -(19.23)(4)(-V_S)(0.09670)$$

Then

$$\frac{V_0}{V_S} = 1.86$$

12.33

Using the circuit from Problem 12.32, we have $R_T = \frac{V_{e1}}{I_S}$

$$\text{where } I_S = \frac{V_S - V_{\pi 1}}{R_S}$$

From Problem 12.32

$$\begin{aligned} V_{\pi 1} &= V_S(0.009673) - V_{\pi 2}(0.007163) \\ &= V_S(0.009673) - (0.007163)(-V_S)(0.09670) \\ &= V_S(0.01037) \end{aligned}$$

So

$$R_{i1} = \frac{V_S(0.01037) \cdot (0.6)}{V_S - V_S(0.01037)} = 0.00629 \text{ k}\Omega$$

or

$$\underline{R_{i1} = 6.29 \Omega}$$

12.34

$$R_{TH} = 1.4 \| 17.9 = 1.298 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{1.4}{1.4 + 17.9} \right) (10) = 0.7254 \text{ V}$$

$$I_{B1} = \frac{0.7254 - 0.7}{1.298} = 0.0196 \text{ mA}$$

$$I_{C1} = (50)(0.0196) = 0.98 \text{ mA}$$

Neglecting dc base currents,

$$V_{B2} = 10 - (0.98)(7) = 3.14 \text{ V}$$

$$I_{E2} = \frac{3.14 - 0.7}{0.25 + 0.5} = 3.25 \text{ mA}$$


$$I_{C2} = \left(\frac{50}{51} \right) (3.25) = 3.19 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.98} = 1.33 \text{ k}\Omega$$

$$g_{m1} = \frac{0.98}{0.026} = 37.7 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(50)(0.026)}{3.19} = 0.408 \text{ k}\Omega$$
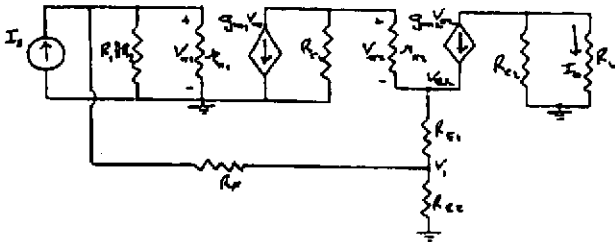
$$g_{m2} = \frac{3.19}{0.026} = 123 \text{ mA/V}$$



$$I_S = \frac{V_{\pi 1}}{R_1 \parallel R_2 \parallel r_{\pi 1}} + \frac{V_{\pi 1} - V_1}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{r_{\pi 2}} + \frac{V_{\pi 2} + V_{e2}}{R_{C1}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_{e2} - V_1}{R_{E1}} \quad (3)$$

$$\frac{V_{e2} - V_{\pi 1}}{R_{E1}} = \frac{V_1}{R_{E2}} + \frac{V_1 - V_{\pi 1}}{R_F} \quad (4)$$

Enter numerical values in (1), (2), (3) and (4):

$$I_S = \frac{V_{\pi 1}}{17.9 \parallel 1.4 \parallel 1.33} + \frac{V_{\pi 1} - V_1}{5}$$

or

$$I_S = V_{\pi 1}(1.722) - V_1(0.20) \quad (1)$$

$$(37.7)V_{\pi 1} + \frac{V_{\pi 2}}{0.408} + \frac{V_{\pi 2} + V_{e2}}{7} = 0$$

or

$$V_{\pi 1}(37.7) + V_{\pi 2}(2.594) + V_{e2}(0.1429) = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{0.408} + (123)V_{\pi 2} = \frac{V_{e2} - V_1}{0.25}$$

or

$$V_{\pi 2}(125.5) = V_{e2}(4) - V_1(4) \quad (3)$$

$$\frac{V_{e2} - V_1}{0.25} = \frac{V_1}{0.50} + \frac{V_1 - V_{\pi 1}}{5}$$

or

$$V_{e2}(4) = V_1(6.20) - V_{\pi 1}(0.20) \quad (4)$$

From (4):

$$V_{e2} = V_1(1.55) - V_{\pi 1}(0.05)$$

Then substituting in (3):

$$V_{\pi 2}(125.5) = (4)[V_1(1.55) - V_{\pi 1}(0.05)] - V_1(4)$$

or

$$V_{\pi 2}(125.5) = V_1(2.20) - V_{\pi 1}(0.20) \quad (3')$$

and substituting in (2):

$$V_{\pi 1}(37.7) + V_{\pi 2}(2.594) + (0.1429)[V_1(1.55) - V_{\pi 1}(0.05)] = 0$$

or

$$V_{\pi 1}(37.69) + V_{\pi 2}(2.594) + V_1(0.2215) = 0$$

Now

$$V_1 = -V_{\pi 1}(170.16) - V_{\pi 2}(11.71)$$

Then substituting in (1):

$$I_S = V_{\pi 1}(1.722) - (0.20)[-V_{\pi 1}(170.16) - V_{\pi 2}(11.71)]$$

or

$$I_S = V_{\pi 1}(35.75) + V_{\pi 2}(2.342)$$

and substituting in (3'):

$$V_{\pi 2}(125.5) = (2.20)[-V_{\pi 1}(170.16) - V_{\pi 2}(11.71)] - V_{\pi 1}(0.20)$$

or $V_{\pi 2}(151.3) = -V_{\pi 1}(374.55)$ so that

$$V_{\pi 1} = -V_{\pi 2}(0.4040)$$

Then

$$I_S = (35.75)[-V_{\pi 2}(0.4040)] + V_{\pi 2}(2.342)$$

$$I_S = -V_{\pi 2}(12.10)$$

$$I_0 = -(g_{m2} V_{\pi 2}) \left(\frac{R_{C2}}{R_{C2} + R_L} \right)$$

$$= -(123) \left(\frac{2.2}{2.2 + 2} \right) V_{\pi 2} = -(64.43) V_{\pi 2}$$

$$\text{or } V_{\pi 2} = -(0.01552) I_0$$

Then

$$\frac{I_0}{I_S} = \frac{1}{(0.01552)(12.10)} \Rightarrow \frac{I_0}{I_S} = 5.33$$

12.35


For example, use the circuit shown in Figure P12.30

12.36

$$r_{\pi 1} = 6.24 \text{ k}\Omega, r_{\pi 2} = 3.12 \text{ k}\Omega, r_{\pi 3} = 1.56 \text{ k}\Omega$$

$$g_{m1} = 19.23 \text{ mA/V}, g_{m2} = 38.46 \text{ mA/V},$$

$$g_{m3} = 76.92 \text{ mA/V}$$

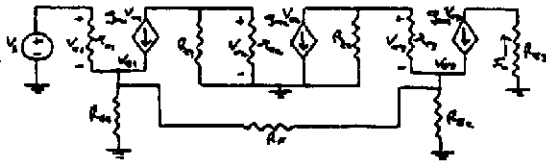

$$V_S = V_{\pi 1} + V_{e1} \quad (1)$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_{e3}}{R_F} \quad (2)$$

$$V_{\pi 2} = -g_{m1} V_{\pi 1} (R_{C1} \parallel r_{\pi 2}) \quad (3)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3} + V_{e3}}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (4)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_{e3}}{R_{E2}} + \frac{V_{e3} - V_{e1}}{R_F} \quad (5)$$

Enter numerical values in (2)-(5):

$$\frac{V_{\pi 1}}{6.24} + (19.23)V_{\pi 1} = V_{e1} \left(\frac{1}{0.1} + \frac{1}{0.8} \right) - V_{e3} \left(\frac{1}{0.8} \right)$$

or

$$V_{\pi 1}(19.39) = V_{e1}(11.25) - V_{e3}(1.25) \quad (2)$$

$$V_{\pi 2} = -(19.23)V_{\pi 1}(5 \parallel 3.12) = -(36.94)V_{\pi 1} \quad (3)$$

$$(38.46)V_{\pi 2} + V_{\pi 3} \left(\frac{1}{2} + \frac{1}{1.56} \right) + V_{e3} \left(\frac{1}{2} \right) = 0$$

or

$$V_{\pi 2}(38.46) + V_{\pi 3}(1.141) + V_{e3}(0.5) = 0 \quad (4)$$

$$V_{\pi 3} \left(\frac{1}{1.56} + 76.92 \right) = V_{e3} \left(\frac{1}{0.1} + \frac{1}{0.8} \right) - V_{e1} \left(\frac{1}{0.8} \right)$$

or

$$V_{\pi 3}(77.56) = V_{e3}(11.25) - V_{e1}(1.25) \quad (5)$$

$$\text{From (1)} \quad V_{\pi 1} = V_S - V_{e1}$$

Then

$$(V_S - V_{e1})(19.39) = V_{e1}(11.25) - V_{e3}(1.25)$$

or

$$V_S(19.39) = V_{e1}(30.64) - V_{e3}(1.25) \quad (2')$$

$$V_{\pi 2} = -V_S(36.94) + V_{e1}(36.94) \quad (3')$$

$$(38.46)[-V_S(36.94) + V_{e1}(36.94)] + V_{\pi 3}(1.141) + V_{e3}(0.5) = 0 \quad (4')$$

$$\text{From (5): } V_{e3} = V_{\pi 3}(6.894) + V_{e1}(0.1111)$$

Then

$$V_S(19.39) = V_{e1}(30.64) - (1.25)[V_{\pi 3}(6.894) + V_{e1}(0.1111)]$$

or

$$V_S(19.39) = V_{e1}(30.50) - V_{\pi 3}(8.6175) \quad (2'')$$

and

$$-V_S(1420.7) + V_{e1}(1420.7) + V_{\pi 3}(1.141) + (0.5)[V_{\pi 3}(6.894) + V_{e1}(0.1111)] = 0$$

or

$$-V_S(1420.7) + V_{e1}(1420.76) + V_{\pi 3}(4.588) = 0 \quad (4'')$$

From (2''):

$$V_{e1} = V_S(0.6357) + V_{\pi 3}(0.2825)$$

Then substituting in (4''):

$$-V_S(1420.7) + (1420.76)[V_S(0.6357) + V_{\pi 3}(0.2825)] + V_{\pi 3}(4.588) = 0$$

$$-V_S(517.5) + V_{\pi 3}(405.95) = 0$$

Now

$$I_0 = g_{m3} V_{\pi 3} = 76.92 V_{\pi 3} \text{ or } V_{\pi 3} = I_0(0.0130)$$

$$\text{Then } -V_S(517.5) + I_0(0.0130)(405.95) = 0$$

or

$$\frac{I_0}{V_S} = 98.06 \text{ mA/V}$$


12.38

$$r_{\pi 1} = r_{\pi 2} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(100)(0.026)}{2} = 1.3 \text{ k}\Omega$$
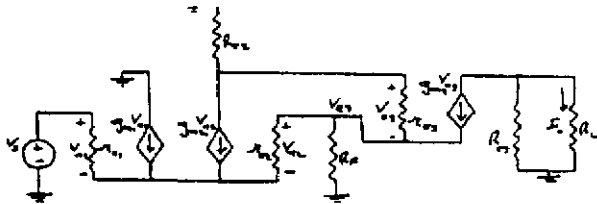
$$g_{m3} = \frac{2}{0.026} = 76.92 \text{ mA/V}$$



$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (1)$$

Since $r_{\pi 1} = r_{\pi 2}$ and $g_{m1} = g_{m2}$, then $V_{\pi 1} = -V_{\pi 2}$

$$V_S = V_{\pi 1} - V_{\pi 2} + V_{e3} = -2V_{\pi 2} + V_{e3} \quad (2)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3}}{r_{\pi 3}} + \frac{V_{\pi 3} + V_{e3}}{R_{C2}} = 0 \quad (3)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_{e3}}{R_F} + \frac{V_{\pi 2}}{r_{\pi 2}} \quad (4)$$

$$I_o = -\left(\frac{R_{C3}}{R_{C3} + R_L}\right)(g_{m3} V_{\pi 3}) \quad (5)$$

From (2): $V_{e3} = V_S + 2V_{\pi 2}$

$$(19.23)V_{\pi 2} + \frac{V_{\pi 3}}{1.3} + \frac{V_{\pi 3}}{18.6} + \frac{1}{18.6}(V_S + 2V_{\pi 2}) = 0$$

or

$$(19.23)V_{\pi 2} + (0.8230)V_{\pi 3} + (0.05376)V_S = 0 \quad (3')$$

$$V_{\pi 3} \left(\frac{1}{1.3} + 76.92 \right) = \left(\frac{1}{10} \right) (V_S + 2V_{\pi 2}) + \frac{V_{\pi 2}}{5.2}$$

or

$$(77.69)V_{\pi 3} = (0.3923)V_{\pi 2} + (0.1)V_S \quad (4')$$

$$I_o = -\left(\frac{2}{2+1}\right)(76.92)V_{\pi 3} = -(51.28)V_{\pi 3} \quad (5')$$

From (3'):

$$V_{\pi 2} = -(0.04255)V_{\pi 3} - (0.002780)V_S$$

Then

$$\begin{aligned} (77.69)V_{\pi 3} &= (0.3923)[-(0.04255)V_{\pi 3} - (0.002780)V_S] \\ &\quad + (0.1)V_S \end{aligned}$$

$$(77.71)V_{\pi 3} = (0.0989)V_S$$

or

$$V_{\pi 3} = (0.001273)V_S$$

so that


$$I_o = -(51.28)(0.001273)V_S$$

or

$$\frac{I_o}{V_S} = -(0.0653) \text{ mA/V}$$

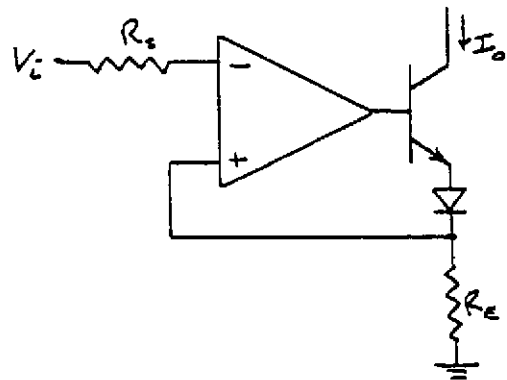12.39

Use the basic circuit shown in Figure 12.27.



For the ideal case

$$\frac{I_o}{V_i} = \frac{1}{R_E}$$

we want

$$\frac{I_o}{V_i} = 10^{-3} \text{ A/V} = 1 \text{ mA/V}$$

Set $R_E = 1 \text{ k}\Omega$

Since the op-amp has a finite gain, finite input resistance, and finite output resistance, the closed-loop gain is slightly less than the ideal. R_E will need to be slightly decreased to increase the gain.

12.40

dc analysis

$$I_B R_E + V_{BE(\text{on})} + I_B R_B + V_{CC} = 0$$


$$I_B = \frac{5 - 0.7}{100 + (51)(0.5)} = 0.0343$$

$$I_C = (50)(0.0343) = 1.71 \text{ mA}$$

$$\text{Then } r_{\pi} = \frac{(50)(0.026)}{1.71} = 0.760 \text{ k}\Omega$$

$$g_m = \frac{1.71}{0.026} = 65.77 \text{ mA/V}$$

a.

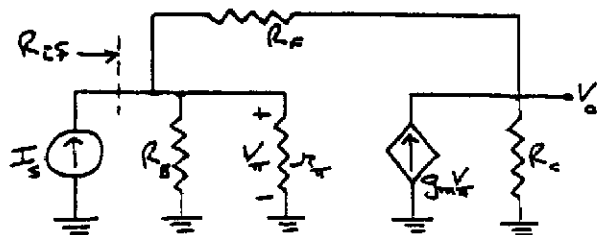To determine R_{if} :

$$I_s + \frac{V_\pi}{R_B \parallel r_\pi} + \frac{V_0 - (-V_\pi)}{R_F} = 0 \quad (1)$$

$$g_m V_\pi = \frac{V_0}{R_C} + \frac{V_0 - (-V_\pi)}{R_F} \quad (2)$$

Now from (2):

$$(65.77)V_\pi - \frac{V_\pi}{10} = V_0 \left(\frac{1}{1} + \frac{1}{10} \right)$$

$$(65.67)V_\pi = V_0(1.10)$$

or

$$V_0 = (59.7)V_\pi$$

and from (1):


$$I_s + \frac{V_\pi}{100 \parallel 0.760} + \frac{V_\pi}{10} + \frac{V_0}{10} = 0$$

$$I_s + V_\pi(0.8543) + (0.1)(59.7)V_\pi = 0$$

$$I_s = -V_\pi(6.824)$$

Now

$$R_{if} = \frac{(-V_\pi)}{I_s} \Rightarrow R_{if} = 147 \, \Omega$$

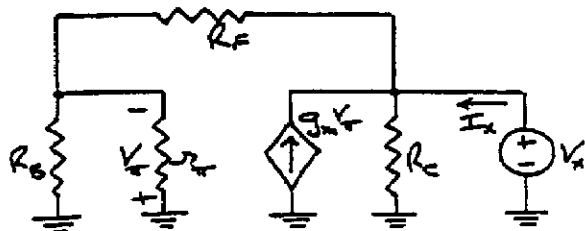To determine R_{of} :

$$I_X = \frac{V_X}{R_C} + \frac{V_X}{R_F + R_B \parallel r_\pi} - g_m V_\pi \quad (3)$$

$$V_\pi = \left(\frac{-(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_F} \right) (V_X) \quad (4)$$

Now

$$V_\pi = \left(\frac{-(100 \parallel 0.760)}{(100 \parallel 0.760) + 10} \right) (V_X) = -(0.07014)V_X$$

so

$$I_X = V_X \left(\frac{1}{1} + \frac{1}{10.754} + (65.77)(0.07014) \right)$$

$$R_{of} = \frac{V_X}{I_X} \Rightarrow R_{of} = 175 \, \Omega$$

b. From part (a), we find

$$V_\pi = -\frac{I_s}{6.824}$$

then

$$V_0 = (59.7) \left(\frac{-I_s}{6.824} \right)$$

or

$$\frac{V_0}{V_s} = -8.75 \, \text{k}\Omega$$

c. If capacitance is finite, a phase shift will be introduced.

12.41

dc analysis: $V_{GS} = V_{DS}$

$$I_D = \frac{V_{DD} - V_{GS}}{R_D} = K_n (V_{GS} - V_{TN})^2$$

$$10 - V_{GS} = (0.20)(8)(V_{GS} - 2)^2$$


$$10 - V_{GS} = 1.6(V_{GS}^2 - 4V_{GS} + 4)$$

$$1.6V_{GS}^2 - 5.4V_{GS} - 3.6 = 0$$

$$V_{GS} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(1.6)(3.6)}}{2(1.6)} = 3.95 \, \text{V}$$

$$I_D = \frac{10 - 3.95}{8} = 0.756 \, \text{mA}$$
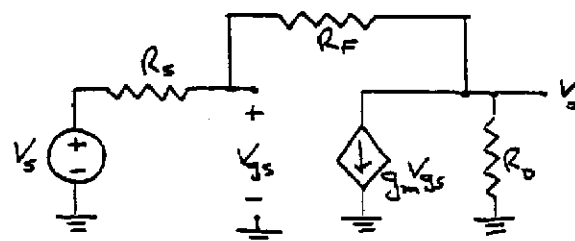
$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.2)(0.756)} \\ \Rightarrow g_m = 0.778 \, \text{mA/V}$$



a.

$$\frac{V_{gs} - V_s}{R_S} + \frac{V_{gs} - V_0}{R_F} = 0$$

$$V_{gs} \left(\frac{1}{R_S} + \frac{1}{R_F} \right) = \frac{V_s}{R_S} + \frac{V_0}{R_F} \quad (1)$$

$$\frac{V_0}{R_D} + g_m V_{gs} + \frac{V_0 - V_{gs}}{R_F} = 0$$

$$V_0 \left(\frac{1}{R_D} + \frac{1}{R_F} \right) = V_{gs} \left(\frac{1}{R_F} - g_m \right) \quad (2)$$

So from (1):

$$V_{gs} \left(\frac{1}{10} + \frac{1}{100} \right) = \frac{V_S}{10} + \frac{V_0}{100}$$

or

$$V_{gs}(0.11) = V_S(0.10) + V_0(0.010)$$

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

Then from (2):

$$V_0 \left(\frac{1}{8} + \frac{1}{100} \right) = V_{gs} \left(\frac{1}{100} - 0.778 \right)$$

$$V_0(0.135) = V_{gs}(-0.768)$$

$$= (-0.768)[V_S(0.909) + V_0(0.0909)]$$

$$V_0(0.2048) = -V_S(0.6981)$$

so

$$A_v = \frac{V_0}{V_S} = -3.41$$

b. We have

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

$$= V_S(0.909) + (0.0909)(-3.41V_S)$$

$$= 0.599V_S$$

Now

$$A_{sf} = \frac{V_0}{I_S} = \frac{V_0}{\frac{V_S - V_{gs}}{R_S}} = \frac{(-3.41V_S)R_S}{V_S - 0.599V_S}$$


or

$$A_{sf} = \frac{(-3.41)(10)}{0.401} \Rightarrow A_{sf} = -85.0 \text{ V/ma}$$

$$c. R_{if} = \frac{V_{gs}}{I_S} = \frac{V_{gs}}{\frac{0.401V_S}{R_S}} = \frac{0.599V_S}{0.401V_S} \cdot (10)$$

$$\Rightarrow R_{if} = 14.9 \text{ k}\Omega$$

d.

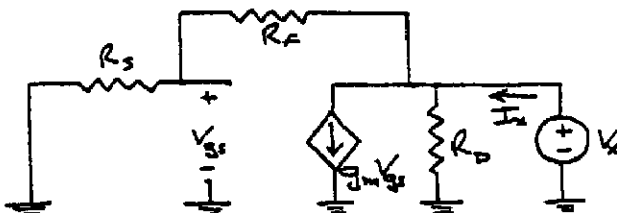

$$I_X = \frac{V_X}{R_D} + g_m V_{gs} + \frac{V_X}{R_S + R_F}$$

$$V_{gs} = \left(\frac{R_S}{R_S + R_F} \right) V_X = \left(\frac{10}{10 + 100} \right) V_X$$

$$= (0.0909)V_X$$

$$I_X = V_X \left[\frac{1}{8} + (0.778)(0.0909) + \frac{1}{10 + 100} \right]$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = 0.2048 \Rightarrow R_{of} = 4.88 \text{ k}\Omega$$

12.42

$$\text{As } g_m \rightarrow \infty, \frac{V_0}{V_S} = \frac{-R_F}{R_S} = \frac{-100}{10} = -10$$

To be within 10% of ideal,

$$\frac{V_0}{V_S} = -10(0.9) = -9$$

From Problem 12.41, we had

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

$$= V_S(0.909) + (-9V_S)(0.0909)$$

$$= 0.0909V_S$$

Also from Problem 12.41, we had

$$V_0(0.135) = V_{gs}(0.010 - g_m)$$

or

$$(-9V_S)(0.135) = (0.0909)V_S(0.010 - g_m)$$

$$-1.215 = 0.000909 - 0.0909g_m$$

or

$$g_m = 13.36 \text{ mA/V}$$

12.43

dc analysis

$$R_{TH} = 24 \parallel 150 = 20.7 \text{ k}\Omega$$


$$V_{TH} = \left(\frac{24}{24 + 150} \right) (12) = 1.655 \text{ V}$$

$$I_{BQ} = \frac{1.655 - 0.7}{20.7 + (151)(1)} = 0.00556 \text{ mA}$$

$$\text{so } I_{CQ} = 0.834 \text{ mA}$$

$$r_x = \frac{(150)(0.026)}{0.834} = 4.68 \text{ k}\Omega$$
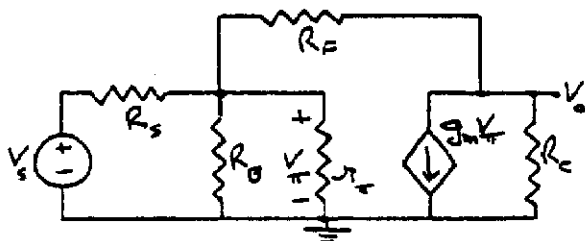
$$g_m = \frac{0.834}{0.026} = 32.08 \text{ mA/V}$$



$$\frac{V_S - V_\pi}{R_S} = \frac{V_\pi}{R_B \parallel r_\pi} + \frac{V_\pi - V_O}{R_F} \quad (1)$$

$$g_m V_\pi + \frac{V_O}{R_C} + \frac{V_O - V_\pi}{R_F} = 0 \quad (2)$$

From (1):

$$\frac{V_S}{5} = V_\pi \left[\frac{1}{5} + \frac{1}{20.7 \parallel 4.68} + \frac{1}{R_F} \right] - \frac{V_O}{R_F}$$

or

$$V_S(0.20) = V_\pi \left(0.4620 + \frac{1}{R_F} \right) - \frac{V_O}{R_F}$$

From (2):

$$\left(32.08 - \frac{1}{R_F} \right) V_\pi + V_O \left(\frac{1}{6} + \frac{1}{R_F} \right) = 0$$

so

$$V_\pi = \frac{-V_O \left(0.1667 + \frac{1}{R_F} \right)}{\left(32.08 - \frac{1}{R_F} \right)} \quad (2)$$

Then

$$\begin{aligned} V_S(0.20) &= \left(0.4620 + \frac{1}{R_F} \right) \left[\frac{-V_O \left(0.1667 + \frac{1}{R_F} \right)}{\left(32.08 - \frac{1}{R_F} \right)} \right] - \frac{V_O}{R_F} \\ &= \left(0.4620 + \frac{1}{R_F} \right) \left[\frac{-V_O \left(0.1667 + \frac{1}{R_F} \right)}{\left(32.08 - \frac{1}{R_F} \right)} \right] - \frac{V_O}{R_F} \end{aligned}$$

Neglect the R_F in the denominator term. Now

$$\frac{V_O}{V_S} = -5 \Rightarrow V_S = -\frac{V_O}{5} = -V_O(0.20)$$

$$\begin{aligned} &-V_O(0.20)(0.20)R_F \\ &= (0.4620R_F + 1) \left[\frac{-V_O(0.1667R_F + 1)}{32.08R_F} \right] - V_O \end{aligned}$$

$$\begin{aligned} -1.283R_F^2 &= -(0.4620R_F + 1)(0.1667R_F + 1) \\ &\quad - 32.08R_F \end{aligned}$$

$$1.206R_F^2 - 32.71R_F - 1 = 0$$

$$R_F = \frac{32.71 \pm \sqrt{(32.71)^2 + 4(1.206)(1)}}{2(1.206)}$$

so that

$$\underline{R_F = 27.2 \text{ k}\Omega}$$

12.44

dc analysis

$$R_{TH} = 4 \parallel 15 = 3.16 \text{ k}\Omega = R_B$$


$$V_{TH} = \left(\frac{4}{4 + 15} \right) 12 = 2.526 \text{ V}$$

$$I_{BQ} = \frac{2.526 - 0.7}{3.16 + (181)(4)} = 0.00251$$

$$I_{CQ} = 0.452 \text{ mA}$$

$$r_\pi = \frac{(180)(0.026)}{0.452} = 10.4 \text{ k}\Omega$$
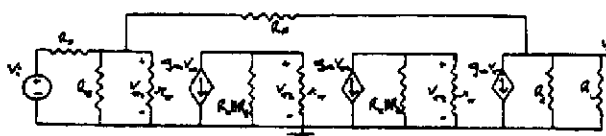
$$g_m = \frac{0.452}{0.026} = 17.4 \text{ mA/V}$$



$$\frac{V_S - V_{\pi 1}}{R_S} = \frac{V_{\pi 1}}{R_B \parallel r_\pi} + \frac{V_{\pi 1} - V_O}{R_F} \quad (1)$$

$$g_m V_{\pi 1} + \frac{V_{\pi 2}}{R_C \parallel R_B \parallel r_\pi} = 0 \quad (2)$$

$$g_m V_{\pi 2} + \frac{V_{\pi 3}}{R_C \parallel R_B \parallel r_\pi} = 0 \quad (3)$$

$$g_m V_{\pi 3} + \frac{V_O}{R_C} + \frac{V_O}{R_L} + \frac{V_O - V_{\pi 1}}{R_F} = 0 \quad (4)$$

Now

$$R_C \parallel R_B \parallel r_\pi = 8 \parallel 3.16 \parallel 10.4 = 1.86 \text{ k}\Omega$$

$$R_B \parallel r_\pi = 3.16 \parallel 10.4 = 2.42 \text{ k}\Omega$$

Now substituting in (2):

$$(17.4)V_{\pi 1} + \frac{V_{\pi 2}}{1.86} = 0 \text{ or } V_{\pi 2} = -(32.36)V_{\pi 1}$$

and substituting in (3):

$$(17.4)V_{\pi 2} + \frac{V_{\pi 3}}{1.86} = 0$$

$$(17.4)[-(32.36)V_{\pi 1}] + \frac{V_{\pi 3}}{1.86} = 0$$

$$\text{or } V_{\pi 3} = (1047.3)V_{\pi 1}$$

Substitute numerical values in (1):

$$\frac{V_i}{10} = V_{\pi 1} \left(\frac{1}{10} + \frac{1}{2.42} + \frac{1}{R_F} \right) - \frac{V_0}{R_F}$$

or

$$V_i(0.10) = V_{\pi 1} \left(0.513 + \frac{1}{R_F} \right) - \frac{V_0}{R_F}$$

Substitute numerical values in (4):

$$(17.4)(1047.3)V_{\pi 1} + V_0 \left(\frac{1}{8} + \frac{1}{4} + \frac{1}{R_F} \right) - \frac{V_{\pi 1}}{R_F} = 0$$

$$V_{\pi 1} \left(1.822 \times 10^4 - \frac{1}{R_F} \right) + V_0 \left(0.375 + \frac{1}{R_F} \right) = 0$$

$$V_{\pi 1} = \frac{-V_0 \left(0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}}$$

so that

$$V_i(0.10)$$

$$= \left(0.513 + \frac{1}{R_F} \right) \left[\frac{-V_0 \left(0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}} \right] - \frac{V_0}{R_F}$$

$$\text{We have } \frac{V_0}{V_i} = -80 \text{ or } V_i = -\frac{V_0}{80}$$

$$= -\frac{(0.10)}{80}$$

$$= \left(0.513 + \frac{1}{R_F} \right) \left[\frac{-\left(0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}} \right] - \frac{1}{R_F}$$

Neglect the $1/R_F$ term in the denominator.

$$\begin{aligned} - (0.00125 R_F) &= - \frac{(0.513 R_F + 1)(0.375 R_F + 1)}{1.822 \times 10^4 R_F} - 1 \\ 22.775 R_F^2 &= (0.513 R_F + 1)(0.375 R_F + 1) + 1.822 \times 10^4 R_F \end{aligned}$$


We find

$$\begin{aligned} 22.58 R_F^2 - 1.822 \times 10^4 R_F - 1 &= 0 \\ R_F &= \frac{1.822 \times 10^4 \pm \sqrt{(1.822 \times 10^4)^2 + 4(22.58)(1)}}{2(22.58)} \end{aligned}$$

or

$$\underline{R_F = 0.807 \text{ M}\Omega}$$

12.45

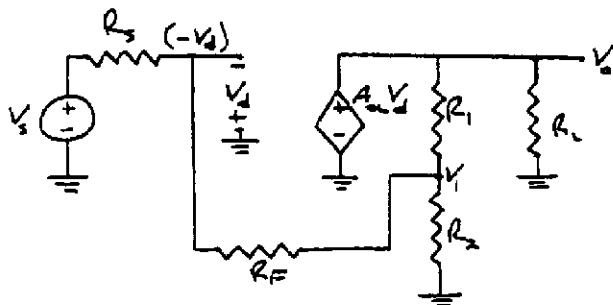

a.

$$\frac{V_S - (-V_d)}{R_S} = \frac{-V_d - V_1}{R_F}$$

or

$$V_d \left(\frac{1}{R_S} + \frac{1}{R_F} \right) + \frac{V_S}{R_S} + \frac{V_1}{R_F} = 0 \quad (1)$$

$$\frac{V_0 - V_1}{R_1} = \frac{V_1}{R_2} + \frac{V_1 - (-V_d)}{R_F}$$

or

$$\frac{V_0}{R_1} = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) + \frac{V_d}{R_F} \quad (2)$$

$$\text{and } V_0 = A_{oL} V_d \text{ or } V_d = \frac{V_0}{A_{oL}}$$

Substitute numerical values in (1) and (2):

$$\frac{V_0}{10^4} \cdot \left(\frac{1}{5} + \frac{1}{10} \right) + \frac{V_S}{5} + \frac{V_1}{10} = 0$$

or

$$V_0(0.3 \times 10^{-4}) + V_S(0.20) + V_1(0.10) = 0 \quad (1)$$

$$\frac{V_0}{50} = V_1 \left(\frac{1}{50} + \frac{1}{10} + \frac{1}{10} \right) + \frac{V_0}{10^4} \cdot \left(\frac{1}{10} \right)$$

or

$$V_0(0.02 - 10^{-5}) = V_1(0.22) \quad (2)$$

$$\text{Then } V_1 = V_0 \left(\frac{0.02 - 10^{-5}}{0.22} \right)$$

and

$$\begin{aligned} V_0(0.3 \times 10^{-4}) + V_S(0.20) \\ + (0.10) \left[V_0 \left(\frac{0.02 - 10^{-5}}{0.22} \right) \right] &= 0 \end{aligned}$$

$$V_0 [0.3 \times 10^{-4} - 0.4545 \times 10^{-4} + 0.00909] + V_S(0.20) = 0$$

$$\text{Then } \frac{V_0}{V_S} = \frac{-0.20}{9.115 \times 10^{-3}} \Rightarrow \frac{V_0}{V_S} = -21.94$$

$$\text{b. } R_{if} = \frac{-V_d}{V_S - (-V_d)} = \frac{-V_d \cdot R_S}{V_S + V_d}$$

$$\text{Now } V_d = \frac{V_0}{A_{OL}} = -\frac{21.94 V_S}{10^4}$$

$$\text{Then } R_{if} = \frac{(21.94 \times 10^{-4})(5)}{1 - 21.94 \times 10^{-4}}$$

$$\text{or } R_{if} = 1.099 \times 10^{-2} \text{ k}\Omega$$

$$\Rightarrow R_{if} = 10.99 \Omega$$

c. Because of the $A_{OL}V_d$ source,


$$R_{of} = 0$$

12.46

For example, use the circuit shown in Figure 12.41

12.47

Break the loop

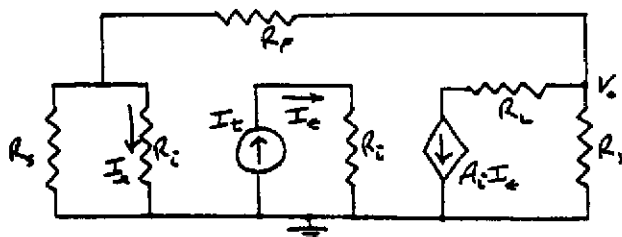

$$I_t = I_e$$

$$\text{Now } A_i I_t + \frac{V_0}{R_i} + \frac{V_0}{R_F + R_S \parallel R_i} = 0$$

$$I_r = \left(\frac{R_S}{R_S + R_i} \right) \cdot \frac{V_0}{R_F + R_S \parallel R_i}$$

$$\text{or } V_0 = I_r \left(\frac{R_S + R_i}{R_S} \right) \cdot (R_F + R_S \parallel R_i)$$


Then

$$A_i I_r + \left(\frac{1}{R_i} + \frac{1}{R_F + R_S \parallel R_i} \right) \times \left[I_r \left(\frac{R_S + R_i}{R_S} \right) (R_F + R_S \parallel R_i) \right] = 0$$

$$T = -\frac{I_r}{I_t} \Rightarrow$$

$$T = \frac{A_i}{\left[\frac{1}{R_i} + \frac{1}{R_F + R_S \parallel R_i} \right] \left(\frac{R_S + R_i}{R_S} \right) (R_F + R_S \parallel R_i)}$$

12.48

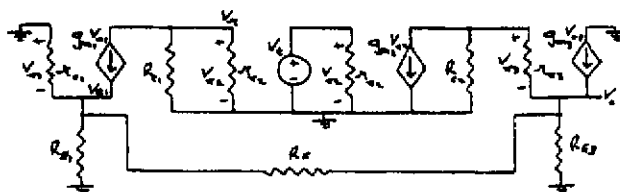

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_0}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_r}{R_{C1} \parallel r_{\pi 2}} = 0$$

$$\Rightarrow V_r = -(g_{m1} V_{\pi 1})(R_{C1} \parallel r_{\pi 2}) \quad (2)$$

$$V_{\pi 2} = V_i \text{ so that}$$

$$g_{m2} V_i + \frac{V_{\pi 3} + V_0}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (3)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_0}{R_{E3}} + \frac{V_0 - V_{e1}}{R_F} \quad (4)$$

From (4):

$$V_0 \left(\frac{1}{R_{E3}} + \frac{1}{R_F} \right) = V_{\pi 3} \left(\frac{1}{r_{\pi 3}} + g_{m3} \right) + \frac{V_{e1}}{R_F}$$

$$\text{But } V_{e1} = -V_{\pi 1}$$

$$\text{so } V_0 = \frac{V_{\pi 3} \left(\frac{1}{r_{\pi 3}} + g_{m3} \right) - \frac{V_{\pi 1}}{R_F}}{\left(\frac{1}{R_{E3}} + \frac{1}{R_F} \right)}$$

Then


$$V_{\pi 1} \left[\left(\frac{1}{r_{\pi 1}} + g_{m1} \right) - \left(\frac{1}{R_{E1}} + \frac{1}{R_F} \right) \right] = \frac{-V_{\pi 3} \left(\frac{1}{r_{\pi 3}} + g_{m3} \right) + \frac{V_{\pi 1}}{R_F}}{R_F \cdot \left(\frac{1}{R_{E3}} + \frac{1}{R_F} \right)} \quad (1')$$

and

$$g_{m2} V_i + V_{\pi 3} \left(\frac{1}{R_{C2}} + \frac{1}{r_{\pi 3}} \right) + \frac{V_{\pi 3} \left(\frac{1}{r_{\pi 3}} + g_{m3} \right) - \frac{V_{\pi 1}}{R_F}}{R_{C2} \cdot \left(\frac{1}{R_{E3}} + \frac{1}{R_F} \right)} = 0 \quad (3')$$

From (3'), solve for $V_{\pi 3}$ and substitute into (1'). Then from (1'), solve for $V_{\pi 1}$ and substitute into (2). Then $T = -\frac{V_r}{V_i}$.

12.49

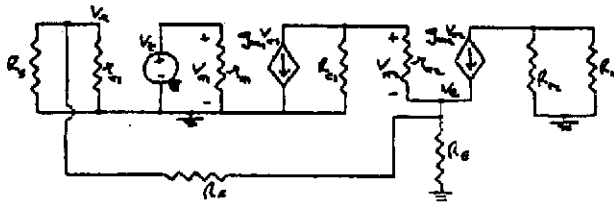

$$\frac{V_r}{R_5} + \frac{V_r}{r_{\pi 1}} + \frac{V_r - V_c}{R_F} = 0 \quad (1)$$

$$g_{m1} V_i + \frac{V_{\pi 2} + V_e}{R_{C1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_e}{R_E} + \frac{V_e - V_r}{R_F} \quad (3)$$

Using the parameters from Problem 12.29, we obtain

$$V_r \left(\frac{1}{10} + \frac{1}{15.8} + \frac{1}{10} \right) - \frac{V_c}{10} = 0$$

or

$$V_r(0.2633) = V_c(0.10) \quad (1)$$

$$(7.62)V_i + V_{\pi 2} \left(\frac{1}{40} + \frac{1}{2.28} \right) + \frac{V_e}{40} = 0$$

or

$$V_i(7.62) + V_{\pi 2}(0.4636) + V_e(0.025) = 0 \quad (2)$$

$$V_{\pi 2} \left(\frac{1}{2.28} + 52.7 \right) = V_e \left(\frac{1}{1} + \frac{1}{10} \right) - \frac{V_r}{10}$$

or

$$V_{\pi 2}(53.14) = V_e(1.10) - V_r(0.10)$$

Then

$$V_{\pi 2} = V_e(0.0207) - V_r(0.001882) \quad (3)$$

Substituting in (2):

$$V_i(7.62) + (0.4636)[V_e(0.0207) - V_r(0.001882)] + V_e(0.025) = 0$$

or

$$V_i(7.62) + V_e(0.03460) - V_r(0.0008725) = 0$$

$$\text{From (1) } V_e = V_r(2.633)$$

Then

$$V_i(7.62) + V_r(2.633)(0.03460) - V_r(0.0008725) = 0$$


$$V_i(7.62) + V_r(0.09023) = 0$$

$$\text{or } \frac{V_r}{V_i} = -84.45$$

Now

$$T = -\frac{V_r}{V_i} \Rightarrow T = 84.45$$

12.50

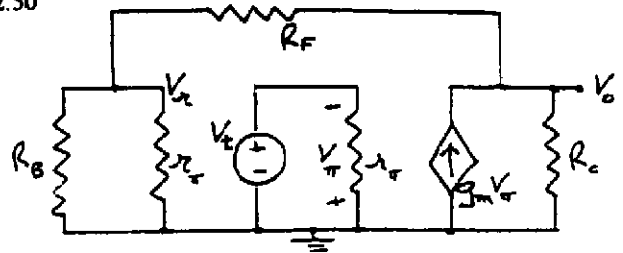

$$V_{\pi} = -V_i$$

$$g_m V_{\pi} = \frac{V_o}{R_C} + \frac{V_o}{R_F + R_B \parallel r_{\pi}} \quad (1)$$

and

$$V_r = \left(\frac{R_B \parallel r_{\pi}}{R_B \parallel r_{\pi} + R_F} \right) V_o \quad (2)$$

Now

$$(65.77)V_{\pi} = V_o \left(\frac{1}{1} + \frac{1}{10 + 100 \parallel 0.760} \right)$$

$$\text{or } (65.77)V_{\pi} = V_o(1.0930)$$

and

$$V_r = \left(\frac{0.754}{10 + 0.754} \right) V_o = (0.07011)V_o$$

$$\text{so } V_o = (14.26)V_r$$

$$\text{Then } (65.77)(-V_i) = (14.26)V_r(1.0930)$$

$$\frac{V_r}{V_i} = -4.22 \text{ so that } T = 4.22$$

12.51

$$\text{a. } \phi = -\tan^{-1} \left(\frac{f}{5 \times 10^2} \right) - 2 \tan^{-1} \left(\frac{f}{10^4} \right)$$

or

$$-180 = -\tan^{-1} \left(\frac{f_{180}}{5 \times 10^2} \right) - 2 \tan^{-1} \left(\frac{f_{180}}{10^4} \right)$$

$$\Rightarrow f_{180} \approx 1.05 \times 10^4 \text{ Hz}$$

b.

$$|T(f_{180})| = 1$$

$$= \frac{\beta(10^5)}{\sqrt{1 + \left(\frac{1.05 \times 10^4}{5 \times 10^2} \right)^2} \left[1 + \left(\frac{1.05 \times 10^4}{10^4} \right)^2 \right]}$$

$$1 = \frac{\beta(10^5)}{(21.02)(2.105)} \quad \text{or}$$

$$\beta = 4.42 \times 10^{-4}$$

12.52

$$A = \frac{5 \times 10^3}{\left(1 + j \frac{f}{10^4}\right) \left(1 + j \frac{f}{10^5}\right)^2}$$

$$\text{Phase} = \phi = -\tan^{-1}\left(\frac{f}{10^4}\right) - 2 \tan^{-1}\left(\frac{f}{10^5}\right)$$

By trial and error, when $f = 1.095 \times 10^5 \text{ Hz}$,
 $\phi \cong 180^\circ$

For $|T| = 1$ at $f = 1.095 \times 10^5 \text{ Hz}$,

$$1 = \frac{\beta(5 \times 10^3)}{\sqrt{1 + \left(\frac{f}{10^4}\right)^2} \cdot \left[1 + \left(\frac{f}{10^5}\right)^2\right]}$$

$$1 = \frac{\beta(5 \times 10^3)}{(10.996)(2.199)} \Rightarrow \beta = 4.84 \times 10^{-3}$$

12.53

$$\phi = -\tan^{-1}\left(\frac{f}{10^4}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right)$$

At $f = 8.1 \times 10^4 \text{ Hz}$, $\phi = -180.28^\circ$

Determine $|T(f)|$ at this frequency.

$$\begin{aligned} |T| &= \beta(10^3) \times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{10^4}\right)^2}} \\ &\times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{5 \times 10^4}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{10^5}\right)^2}} \\ &= \frac{\beta(10^3)}{(8.161)(1.904)(1.287)} \end{aligned}$$

a. For $\beta = 0.005$

$$|T(f)| = 0.250 < 1 \Rightarrow \text{Stable}$$

b. For $\beta = 0.05$

$$|T(f)| = 2.50 > 1 \Rightarrow \text{Unstable}$$

12.54

(b) Phase margin = $80^\circ \Rightarrow \phi = -100^\circ$


$$\phi = -100 = -\tan^{-1}\left(\frac{f}{10^3}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^4}\right)$$

By trial and error, $f = 1.16 \times 10^3 \text{ Hz}$

Then

$$\begin{aligned} |T| = 1 &= \frac{\beta(5 \times 10^3)}{\left(\sqrt{1 + \left(\frac{1.16 \times 10^3}{10^3}\right)^2}\right) \cdot \sqrt{1 + \left(\frac{1.16 \times 10^3}{5 \times 10^4}\right)^2}} \\ &= \frac{\beta(5 \times 10^3)}{(2.35)(1.00)} \Rightarrow \beta = 4.7 \times 10^{-4} \end{aligned}$$

12.55

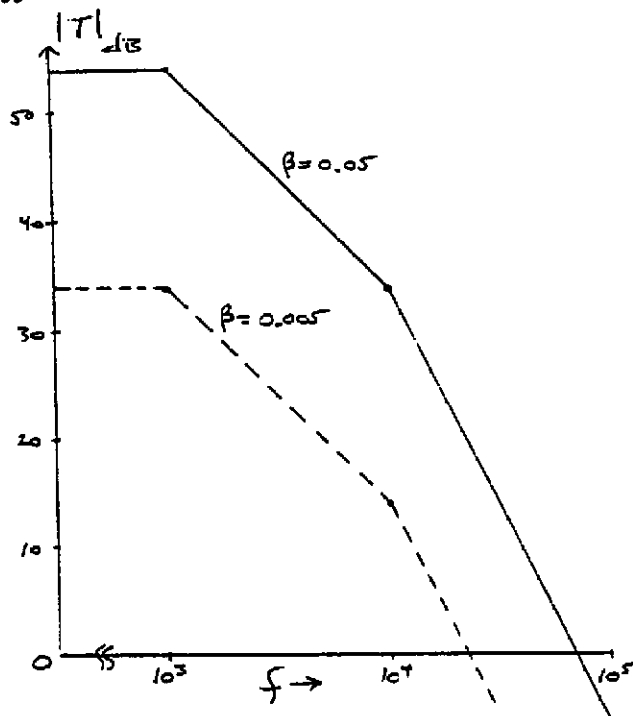

c. For $\beta = 0.005$,

$$|T(f)| = 1 \text{ (0 dB) at } f \approx 2.24 \times 10^4 \text{ Hz}$$

Then

$$\begin{aligned} \phi &= -\tan^{-1}\left(\frac{2.24 \times 10^4}{10^3}\right) - \tan^{-1}\left(\frac{2.24 \times 10^4}{10^4}\right) \\ &\quad - \tan^{-1}\left(\frac{2.24 \times 10^4}{10^5}\right) \\ &= -87.44 - 65.94 - 12.63 \end{aligned}$$

or

$$\phi = -166^\circ \text{ System is stable.}$$

$$\text{Phase margin} = 14^\circ$$

For $\beta = 0.05$,

$$|T(f)| = 1 \text{ (0 dB) at } f \approx 7.08 \times 10^4 \text{ Hz}$$

Then

$$\begin{aligned}\phi &= -\tan^{-1}\left(\frac{7.08 \times 10^4}{10^3}\right) - \tan^{-1}\left(\frac{7.08 \times 10^4}{10^4}\right) \\ &\quad - \tan^{-1}\left(\frac{7.08 \times 10^4}{10^5}\right) \\ &= -89.19 - 81.96 - 35.30\end{aligned}$$

or

$$\phi = -206.45^\circ \Rightarrow \text{System is unstable.}$$

12.56

$$T = A\beta = \frac{\beta(10^5)}{\left(1 + j\frac{f}{5 \times 10^4}\right)\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{5 \times 10^5}\right)}$$

$$\text{Phase Margin} = 60^\circ \Rightarrow \phi = -120^\circ$$

So

$$-120 = -\tan^{-1}\left(\frac{f}{5 \times 10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^5}\right)$$

$$\text{By trial and error, at } f = 10^5 \text{ Hz, } \phi \approx -120^\circ$$

Then

$$\begin{aligned}|T| = 1 &= \frac{\beta(10^5)}{\sqrt{1 + \left(\frac{10^5}{5 \times 10^4}\right)^2} \cdot \sqrt{1 + \left(\frac{10^5}{10^5}\right)^2} \cdot \sqrt{1 + \left(\frac{10^5}{5 \times 10^5}\right)^2}} \\ 1 &= \frac{\beta(10^5)}{(2.236)(1.414)(1.02)} \Rightarrow \underline{\beta = 3.22 \times 10^{-5}}\end{aligned}$$

12.57

$$\text{a. Phase Margin} = 60^\circ \Rightarrow \phi = -120^\circ$$

Then

$$\phi = -120^\circ = -2 \tan^{-1}\left(\frac{f}{10^3}\right)$$

$$\text{or } f = 1.732 \times 10^3 \text{ Hz}$$

Then

$$|T(f)| = 1 = \frac{\beta(10^3)}{\left[1 + \left(\frac{1.732 \times 10^3}{10^3}\right)^2\right]}$$

which yields

$$\underline{\beta = 4 \times 10^{-3}}$$

12.58

$$T(0) = A(0)\beta = (500)(0.6) = 300$$

$$T(f) = \frac{300}{\left(1 + j\frac{f}{10^4}\right)\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{10^6}\right)}$$

Find f at which $|T| = 1$

$$1 = \frac{300}{\sqrt{1 + \left(\frac{f}{10^4}\right)^2} \cdot \sqrt{1 + \left(\frac{f}{10^5}\right)^2} \cdot \sqrt{1 + \left(\frac{f}{10^6}\right)^2}}$$


By trial and error, $f_1 = 5.12 \times 10^5 \text{ Hz}$

Then

$$\begin{aligned}\phi &= -\tan^{-1}\left(\frac{f_1}{10^4}\right) - \tan^{-1}\left(\frac{f_1}{10^5}\right) - \tan^{-1}\left(\frac{f_1}{10^6}\right) \\ &= -88.88 - 78.95 - 27.1 = -194.9^\circ\end{aligned}$$

System is unstable, Phase margin is not defined.

12.59

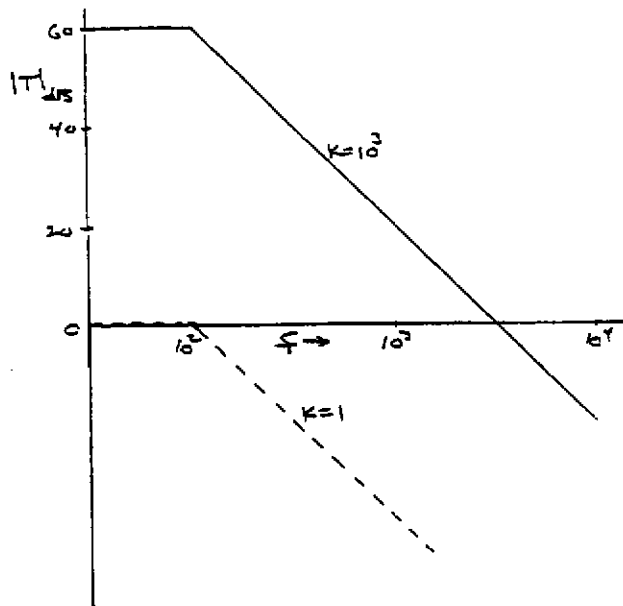

12.60

$$\text{Phase Margin} = 45^\circ \Rightarrow \phi = -135^\circ$$

$$\phi = -135^\circ$$

$$\begin{aligned}\phi &= -\tan^{-1}\left(\frac{f}{10^3}\right) - \tan^{-1}\left(\frac{f}{10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right) \\ &\quad - \tan^{-1}\left(\frac{f}{10^6}\right)\end{aligned}$$

$$\text{At } f = 10^4 \text{ Hz, } \phi = -135.6^\circ$$

$$\begin{aligned}
 |T| = 1 &= \beta(10^3) \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^3}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^4}\right)^2}} \times \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^5}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^6}\right)^2}} \\
 1 &= \frac{\beta(10^3)}{(10.05)(1.414)(1.005)(1.00)}
 \end{aligned}$$

or

$$\beta = 0.01428$$

12.61

$$\begin{aligned}
 T &= 5000 \times \frac{1}{\left(1 + j\frac{f}{f_{PD}}\right)} \times \frac{1}{\left(1 + j\frac{f}{300 \times 10^3}\right)} \\
 &\quad \times \frac{1}{\left(1 + j\frac{f}{2 \times 10^6}\right)} \times \frac{1}{\left(1 + j\frac{f}{25 \times 10^6}\right)}
 \end{aligned}$$

Phase Margin = $45^\circ \Rightarrow \phi = -135^\circ$ at $f = 300$ kHz

$$\begin{aligned}
 -135^\circ &= -\tan^{-1}\left(\frac{300 \times 10^3}{f_{PD}}\right) \\
 &\quad - \tan^{-1}\left(\frac{300 \times 10^3}{300 \times 10^3}\right) - 0 - 0 \\
 &= -90^\circ - 45^\circ
 \end{aligned}$$

Now

$$|T| = 1 @ f = 300 \text{ kHz}$$

$$|T| = 1 \approx \frac{5000}{\sqrt{1 + \left(\frac{300 \times 10^3}{f_{PD}}\right)^2} \cdot \sqrt{2} \cdot 1 \cdot 1}$$

$$1 + \left(\frac{300 \times 10^3}{f_{PD}}\right)^2 = \left(\frac{5000}{\sqrt{2}}\right)^2$$

$$\begin{aligned}
 f_{PD} &\approx \frac{300 \times 10^3 \sqrt{2}}{5000} \\
 &\Rightarrow \underline{f_{PD} = 84.8 \text{ Hz}}
 \end{aligned}$$

12.62

$$a. \quad T(0) = 100 \text{ dB} \Rightarrow T(0) = 10^5$$

 $T(f)$

$$\begin{aligned}
 &= \frac{10^5}{\left(1 + j\frac{f}{10}\right) \left(1 + j\frac{f}{5 \times 10^6}\right) \left(1 + j\frac{f}{10 \times 10^6}\right)}
 \end{aligned}$$

$$\begin{aligned}
 |T| = 1 &= 10^5 \times \frac{1}{\sqrt{1 + \left(\frac{f}{10}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{f}{5 \times 10^6}\right)^2}} \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{f}{10 \times 10^6}\right)^2}}
 \end{aligned}$$

By trial and error

$$\underline{f = 0.976 \text{ MHz}}$$

$$\begin{aligned}
 \phi &= -\tan^{-1}\left(\frac{0.976 \times 10^6}{10}\right) - \tan^{-1}\left(\frac{0.976}{5}\right) \\
 &\quad - \tan^{-1}\left(\frac{0.976}{10}\right) \\
 &= -90^\circ - 11.05^\circ - 5.574^\circ = -106.6^\circ
 \end{aligned}$$

$$\text{Phase Margin} = 180^\circ - 106.6^\circ = \underline{73.4^\circ}$$

$$b. \quad f'_{P1} \propto \frac{1}{C_F} \text{ so } \frac{10}{f'_{P1}} = \frac{75}{20}$$

or

$$\underline{f'_{P1} = 2.67 \text{ Hz}}$$

Now

$$\begin{aligned}
 |T| = 1 &= 10^5 \times \frac{1}{\sqrt{1 + \left(\frac{f}{2.67}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{f}{5 \times 10^6}\right)^2}} \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{f}{10 \times 10^6}\right)^2}}
 \end{aligned}$$

By trial and error

$$\underline{f \approx 2.66 \times 10^5 \text{ Hz}}$$

then

$$\begin{aligned}
 \phi &= -\tan^{-1}\left(\frac{2.66 \times 10^5}{2.67}\right) - \tan^{-1}\left(\frac{0.266}{5}\right) \\
 &\quad - \tan^{-1}\left(\frac{0.266}{10}\right) \\
 &= -90^\circ - 3.045^\circ - 1.524^\circ = -94.57^\circ
 \end{aligned}$$

$$\text{Phase Margin} = 180^\circ - 94.57^\circ = \underline{85.4^\circ}$$

12.63

$$(a) f_{1-dB} = \frac{1}{2\pi\tau} \text{ where } \tau = (R_{o1} \| R_{i2})C_i \\ = (500 \| 1000) \times 10^3 \times 2 \times 10^{-12} \Rightarrow \tau = 6.67 \times 10^{-7} \text{ s}$$

Then

$$f_{1-dB} = \frac{1}{2\pi(6.67 \times 10^{-7})} \Rightarrow f_{1-dB} = 239 \text{ kHz}$$

(b) For

$$f_{PD} = 10 \text{ Hz}, \quad \tau = \frac{1}{2\pi f_{PD}} = \frac{1}{2\pi(10)} = 0.0159 \text{ s}$$

$$\text{Then } \tau = (R_{o1} \| R_{i2})(C_i + C_M)$$

$$0.0159 = (500 \| 1000) \times 10^3 \times (C_i + C_M)$$

or

$$(C_i + C_M) = 4.77 \times 10^{-8} = 2 \times 10^{-12} + C_M \Rightarrow$$

$$C_M = 477 \text{ } \mu\text{F}$$

If we want a phase margin of 45° , then

$$-135^\circ \approx -90^\circ - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{10^7}\right)$$

By trial and error, $f \approx 0.845 \text{ MHz}$

Then

$$|T| = 1 = \frac{0.2 \times 10^4}{\sqrt{1 + \left(\frac{0.845 \times 10^6}{f_{PD}}\right)^2} \sqrt{1 + \left(\frac{0.845}{1}\right)^2}} \\ \times \frac{1}{\sqrt{1 + \left(\frac{0.845}{10}\right)^2}}$$

$$\frac{0.845 \times 10^6}{f_{PD}} \approx \frac{0.2 \times 10^4}{(1.309)(1.0036)}$$

$$\text{so } f_{PD} = 555 \text{ Hz}$$

12.64

Want $f_1 = 12 \text{ MHz}$ for a phase margin of 45°

$$T_{dB}(0) = 80 \text{ dB} \Rightarrow T(0) = 10^4$$

Then

$$T(f) = \frac{T(0)}{\left(1 + j\frac{f}{f_{PD}}\right)\left(1 + j\frac{f}{12 \times 10^6}\right)}$$

$$\text{Set } f = f_1 \text{ and } |T| = 1$$

So

$$|T| = 1 = \frac{10^4}{\sqrt{1 + \left(\frac{12 \times 10^6}{f_{PD}}\right)^2} \cdot \sqrt{2}}$$

which yields

$$\frac{12 \times 10^6}{f_{PD}} = \frac{10^4}{\sqrt{2}} \Rightarrow f_{PD} = 1.70 \text{ kHz}$$

12.65

$$A_0 = 80 \text{ dB} \Rightarrow A_0 = 10^4$$

$$A_f(0) = \frac{A_0}{1 + \beta A_0}$$

$$\text{or } 5 = \frac{10^4}{1 + \beta(10^4)} \Rightarrow \beta \approx 0.2$$

$$\text{Then } T(0) = \beta A_0 = 0.2 \times 10^4$$

Inserting a dominate pole

$$\phi = -\tan^{-1}\left(\frac{f}{f_{PD}}\right) - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{10^7}\right)$$

12.66

Assuming a phase margin of 45° .

$$-135^\circ \approx -90^\circ - \tan^{-1}\left(\frac{f}{2 \times 10^6}\right) \\ - \tan^{-1}\left(\frac{f}{25 \times 10^6}\right)$$

By trial and error, $f \approx 1.74 \text{ MHz}$

Then

$$|T| = 1 \\ = 5000 \times \frac{1}{\sqrt{1 + \left(\frac{1.74 \times 10^6}{f_{PD}}\right)^2}} \\ \times \frac{1}{\sqrt{1 + \left(\frac{1.74}{25}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{1.74}{25}\right)^2}}$$

or

$$\frac{1.74 \times 10^6}{f_{PD}} \approx \frac{5000}{(1.325)(1.0024)}$$

$$\text{so } f_{PD} = 462 \text{ Hz}$$