

Chapter 8

Exercise Solutions

E8.1

$$\text{For } V_{DS} = 0, I_D(\max) = \frac{24}{20} = 1.2 \text{ A} = I_{D(\max)}$$

$$\text{For } I_D = 0 \Rightarrow V_{DS}(\max) = 24 \text{ V}$$


Maximum power when

$$V_{DS} = \frac{V_{DS}(\max)}{2} = 12 \text{ V and}$$

$$I_D = \frac{I_D(\max)}{2} = 0.6 \text{ A}$$

$$\Rightarrow P_{D(\max)} = (12)(0.6) = 7.2 \text{ Watts}$$

E8.2

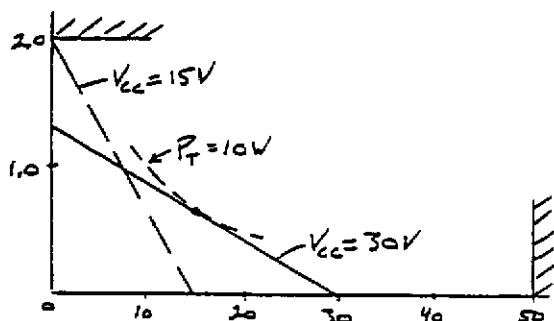

$$\text{a. } V_{CC} = 30 \text{ V, } V_{CE} = 30 - I_C R_C, I_C V_{CE} = 10$$

$$\text{Maximum power at } V_{CE} = \frac{1}{2} V_{CC} = 15$$

$$I_C = \frac{10}{V_{CE}} = \frac{10}{15} = \frac{2}{3}$$

$$\text{So } 15 = 30 - \frac{2}{3} R_L \Rightarrow R_L = 22.5 \Omega$$

$$\Rightarrow \text{Maximum Power} = 10 \text{ W}$$


$$\text{b. } V_{CC} = 15 \text{ V, } I_{C,\max} = 2 \text{ A}$$

$$V_{CE} = 15 - I_C R_L$$

$$0 = 15 - 2 R_L \Rightarrow R_L = 7.5 \Omega$$

$$\Rightarrow \text{Maximum Power} = (1)(7.5) = 7.5 \text{ W}$$

E8.3

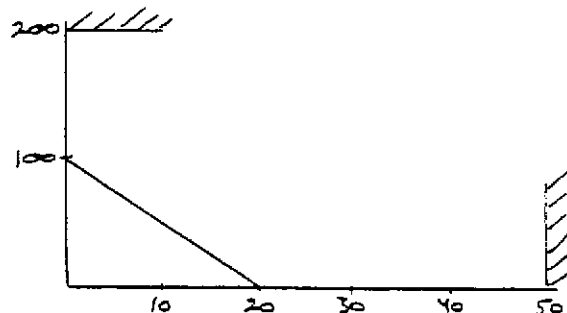

Maximum power at center of load line

$$P_{\max} = (0.05)(10) \Rightarrow P_{\max} = 0.5 \text{ W}$$

E8.4

$$\text{Power} = i_D \cdot v_{DS} = (1)(12) = 12 \text{ watts}$$

$$\text{c. } T_{\text{sink}} = T_{\text{amb}} + P \cdot \theta_{\text{sink-amb}}$$

$$T_{\text{sink}} = 25 + (12)(4) \Rightarrow T_{\text{sink}} = 73^\circ \text{C}$$

$$\text{b. } T_{\text{case}} = T_{\text{sink}} + P \cdot \theta_{\text{case-sink}}$$

$$T_{\text{case}} = 73 + (12)(1) \Rightarrow T_{\text{case}} = 85^\circ \text{C}$$

$$\text{a. } T_{\text{dev}} = T_{\text{case}} + P \cdot \theta_{\text{dev-case}}$$

$$T_{\text{dev}} = 85 + (12)(3) \Rightarrow T_{\text{dev}} = 121^\circ \text{C}$$

E8.5

$$\theta_{\text{dev-case}} = \frac{T_{J,\max} - T_{\text{amb}}}{P_{D,\text{rated}}} = \frac{200 - 25}{50} = 3.5^\circ \text{C/W}$$

$$\begin{aligned} P_{D,\max} &= \frac{T_{J,\max} - T_{\text{amb}}}{\theta_{\text{dev-case}} + \theta_{\text{case-sink}} + \theta_{\text{sink-amb}}} \\ &= \frac{200 - 25}{3.5 + 0.5 + 2} \\ &\Rightarrow P_{D,\max} = 29.2 \text{ W} \end{aligned}$$

$$\begin{aligned} T_{\text{case}} &= T_{\text{amb}} + P_{D,\max}(\theta_{\text{case-sink}} + \theta_{\text{sink-amb}}) \\ &= 25 + (29.2)(0.5 + 2) \\ &\Rightarrow T_{\text{case}} = 98^\circ \text{C} \end{aligned}$$

E8.6

$$a. \quad P_Q = V_{CEQ} \cdot I_{CQ} = (7.5)(7.5)$$

$$\underline{P_Q = 56.3 \text{ mW}}$$

$$b. \quad \overline{P_L} = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{1}{2} \cdot \frac{(6.5)^2}{1} \Rightarrow \underline{\overline{P_L} = 21.1 \text{ mW}}$$

$$\overline{P_S} = (15)(7.5) \Rightarrow \overline{P_S} = 113 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{21.1}{113} \Rightarrow \underline{\eta = 18.7\%}$$

$$\underline{\overline{P_Q} = 56.3 - 21.1 = 35.2 \text{ mW}}$$

$$\overline{P_Q} = \frac{(25)(20)}{\pi(8)} - \frac{(20)^2}{4(8)} = 19.9 - 12.5$$


$$\Rightarrow \underline{\overline{P_Q} = 7.4 \text{ W}}$$

$$d. \quad \eta = \frac{\pi V_P}{4 V_{CC}} = \frac{\pi}{4} \cdot \frac{20}{25} \Rightarrow \underline{\eta = 62.8\%}$$

E8.7

$$a. \quad I_{DQ} = \frac{10 - 4}{0.1} \Rightarrow \underline{I_{DQ} = 60 \text{ mA}}$$

b.

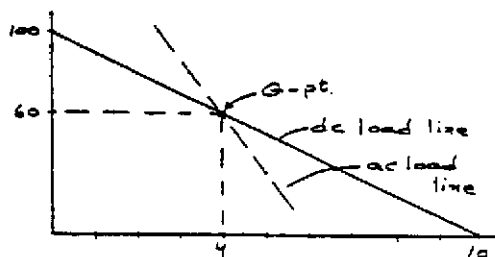

$$v_{ds} = -\left(\frac{9}{10}\right)(60)(0.050) = -2.7 \text{ V}$$

$$\Rightarrow v_{DS}(\min) = 4 - 2.7 = 1.3 \text{ V}$$

So maximum swing is determined by drain-to-source voltage.

$$V_{PP} = 2 \times (2.5) = 5.0 \text{ V}$$

$$c. \quad \overline{P_L} = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{1}{2} \cdot \frac{(2.5)^2}{0.1} \Rightarrow \underline{\overline{P_L} = 31.25 \text{ mW}}$$

$$\overline{P_S} = V_{DD} \cdot I_{DQ} = (10)(60) = 600 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{31.25}{600} \Rightarrow \underline{\eta = 5.2\%}$$

E8.9

$$a. \quad \overline{P_L} = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{(4)^2}{2(0.1)} \Rightarrow \underline{\overline{P_L} = 80 \text{ mW}}$$

$$b. \quad I_P = \frac{V_P}{R_L} = \frac{4}{0.1} \Rightarrow \underline{I_P = 40 \text{ mA}}$$

$$c. \quad \overline{P_Q} = \frac{V_{CC} V_P}{\pi R_L} - \frac{V_P^2}{4 R_L}$$

$$\overline{P_Q} = \frac{(5)(4)}{\pi(0.1)} - \frac{(4)^2}{4(0.1)} = 63.7 - 40$$

$$\Rightarrow \underline{\overline{P_Q} = 23.7 \text{ mW}}$$

$$d. \quad \eta = \frac{\pi V_P}{4 V_{CC}} = \frac{\pi}{4} \cdot \frac{4}{5} \Rightarrow \underline{\eta = 62.8\%}$$

E8.10

$$a. \quad v_I = v_O + v_{GSn} - \frac{V_{BB}}{2}$$

$$\frac{dv_I}{dv_O} = 1 + \frac{dv_{GSn}}{dv_O}$$

$$i_{Dn} = K_n (v_{GSn} - V_{TN})^2$$

$$v_{GSn} = \sqrt{\frac{i_{Dn}}{K_n}} + V_{TN}$$

$$\frac{dv_{GSn}}{dv_O} = \frac{dv_{GSn}}{di_{Dn}} \cdot \frac{di_{Dn}}{dv_O}$$

$$\text{So } \frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{K_n}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{i_{Dn}}}$$

$$\text{At } v_O = 0, i_{Dn} = 0.050 \text{ A}$$

$$\text{So } \frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{0.2}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{0.050}} = 5$$

$$i_{Dn} = i_L + i_{Dp}$$

$$\text{For a small change in } v_O - \Delta i_L = \Delta i_{Dn} - (-\Delta i_{Dp})$$

$$\text{So } \Delta i_{Dn} = \frac{1}{2} \Delta i_L$$

or

$$\frac{di_{Dn}}{dv_O} = \frac{1}{2} \cdot \frac{di_L}{dv_O} = \frac{1}{2} \cdot \frac{1}{R_L} = \frac{1}{2} \cdot \frac{1}{20} = 0.025$$

$$\text{Then } \frac{dv_{GSn}}{dv_O} = (5)(0.025) = 0.125$$

$$\text{Then } \frac{dv_I}{dv_O} = 1 + 0.125 = 1.125$$

$$\text{and } A_v = \frac{dv_O}{dv_I} = \frac{1}{1.125} \Rightarrow \underline{A_v = 0.889}$$

$$b. \quad \text{For } v_O = 5 \text{ V, } i_L = 0.25 \text{ A} = i_{Dn}, \text{ and } i_{Dp} = 0$$

E8.8

$$a. \quad \overline{P_L} = \frac{1}{2} \cdot \frac{V_P^2}{R_L}$$

$$\Rightarrow V_P = \sqrt{2 R_L \overline{P_L}} = \sqrt{2(8)(25)} \Rightarrow V_P = 20 \text{ V}$$

$$\Rightarrow V_{CC} = \frac{20}{0.8} \Rightarrow \underline{V_{CC} = 25 \text{ V}}$$

$$b. \quad I_P = \frac{V_P}{R_L} = \frac{20}{8} \Rightarrow \underline{I_P = 2.5 \text{ A}}$$

$$c. \quad \overline{P_Q} = \frac{V_{CC} V_P}{\pi R_L} - \frac{V_P^2}{4 R_L}$$

$$\frac{dv_{GSn}}{dv_0} = \frac{dv_{GSn}}{di_{Dn}} \cdot \frac{di_{Dn}}{dv_0}$$

$$\frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{K_n}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{i_{Dn}}} = \frac{1}{\sqrt{0.2}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{0.25}} = 2.24$$

$$\frac{di_{Dn}}{dv_0} = \frac{di_L}{dv_0} = \frac{1}{20} = 0.05$$

$$\frac{dv_{GSn}}{dv_0} = (2.24)(0.05) = 0.112$$

$$\frac{dv_I}{dv_0} = 1 + 0.112 = 1.112$$

$$A_v = \frac{dv_0}{dv_I} = \frac{1}{1.112} \Rightarrow A_v = 0.899$$

E8.11

$$a. \quad I_{CQ} \cong \frac{1}{2} \cdot \left(\frac{2V_{CC}}{R_L} \right) = \frac{V_{CC}}{R_L} = \frac{12}{1.5} = 8 \text{ mA}$$

$$R_{TH} = R_1 \parallel R_2$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{8}{75} = 0.107 \text{ mA} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$

$$\text{Let } R_{TH} = (1 + \beta)R_E = (76)(0.1) = 7.6 \text{ k}\Omega$$

$$0.107 = \frac{\frac{1}{R_1} \cdot (7.6)(12) - 0.7}{7.6 + 7.6}$$

$$\frac{1}{R_1} \cdot (91.2) = 2.33 \Rightarrow R_1 = 39.1 \text{ k}\Omega$$

$$\frac{39.1R_2}{39.1 + R_2} = 7.6 \Rightarrow (39.1 - 7.6)R_2 = (7.6)(39.1)$$

$$\Rightarrow R_2 = 9.43 \text{ k}\Omega$$

$$b. \quad \overline{P_L} = \frac{1}{2} \cdot (0.9I_{CQ})^2 R_L = \frac{1}{2} [(0.9)(8)]^2 (1.5)$$

$$\Rightarrow \overline{P_L} = 38.9 \text{ mW}$$

$$\overline{P_S} = V_{CC}I_{CQ} = (12)(8) = 96 \text{ mW}$$

$$\overline{P_Q} = \overline{P_S} - \overline{P_L} = 96 - 38.9 \Rightarrow \overline{P_Q} = 57.1 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{38.9}{96} \Rightarrow \eta = 40.5\%$$

E8.12

$$a. \quad R_b = r_\pi + (1 + \beta)R'_E$$

$$\text{and } R'_E = a^2 R_L = (10)^2 (8) = 800 \Omega$$

$$R_i = 1.5 \text{ k}\Omega = R_{TH} \parallel R_b$$

$$I_Q = \frac{V_{CC}}{a^2 R_L} = \frac{18}{(10)^2 (8)} = 22.5 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{22.5} = 0.116 \text{ k}\Omega$$

$$R_b = 0.116 + (101)(0.8) = 80.9 \text{ k}\Omega$$

$$1.5 = R_{TH} \parallel 80.9 = \frac{R_{TH}(80.9)}{R_{TH} + (80.9)}$$

$$\Rightarrow (80.9 - 1.5)R_{TH} = (1.5)(80.9)$$

$$\Rightarrow R_{TH} = 1.53 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$I_{BQ} = \frac{I_Q}{\beta} = \frac{22.5}{100} = 0.225 \text{ mA}$$

$$I_{BQ} = \frac{V_{TH} - 0.7}{R_{TH}}$$

$$\Rightarrow \frac{1}{R_1} (1.53)(18) = (0.225)(1.53) + 0.7$$

$$\Rightarrow R_1 = 26.4 \text{ k}\Omega$$

$$\frac{26.4R_2}{26.4 + R_2} = 1.53$$

$$(26.4 - 1.53)R_2 = (1.53)(26.4)$$

$$\Rightarrow R_2 = 1.62 \text{ k}\Omega$$

$$b. \quad v_E = 0.9V_{CC} = (0.9)(18) = 16.2 \text{ V}$$

$$i_E = 0.9I_{CQ} = (0.9)(22.5) = 20.25 \text{ mA}$$

$$v_0 = \frac{v_E}{a} = \frac{16.2}{10} \Rightarrow v_P = 1.62 \text{ V}$$

$$i_0 = ai_E = (10)(20.25) \Rightarrow i_P = 203 \text{ mA}$$

$$\overline{P_L} = \frac{1}{2} (1.62)(0.203) \Rightarrow \overline{P_L} = 0.164 \text{ W}$$

E8.13

$$a. \quad I_C = I_{SQ} \exp \left(\frac{V_{BE}}{V_T} \right) \Rightarrow V_{BE} = V_T \ln \left(\frac{I_C}{I_{SQ}} \right)$$

$$V_{BE} = (0.026) \ln \left(\frac{5 \times 10^{-3}}{2 \times 10^{-13}} \right) = 0.6225 \text{ V}$$

$$\Rightarrow V_{D1} = V_{D2} = 0.6225$$

$$I_{Bias} = I_D = I_{SD} \exp \left(\frac{0.6225}{0.026} \right)$$

$$= 5 \times 10^{-13} \exp \left(\frac{0.6225}{0.026} \right)$$

$$\underline{I_{Bias} = 12.5 \text{ mA}}$$

$$b. \quad V_0 = 2 \text{ V}, \quad i_L = \frac{2}{0.075} = 26.7 \text{ mA}$$

1st approximation:

$$i_{Cn} \approx 26.7 \text{ mA}, \quad i_{Bn} = 0.444 \text{ mA}$$

$$V_{BE} = (0.026) \ln \left(\frac{26.7 \times 10^{-3}}{2 \times 10^{-13}} \right) = 0.6661$$

$$I_D = 12.5 - 0.444 = 12.056 \text{ mA}$$

$$V_D = (0.026) \ln \left(\frac{12.056 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6216$$

$$2V_D = 1.243 \text{ V}$$

$$V_{EB} = 2V_D - V_{BE} = 0.5769$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left(\frac{0.5769}{0.026} \right) = 0.866 \text{ mA}$$

2nd approximation:

$$i_{En} = i_L + i_{Cp} = 26.7 + 0.866 \approx 27.6 \text{ mA} = i_{En}$$

$$i_{Cn} = \left(\frac{60}{61} \right) (27.6) \Rightarrow i_{Cn} = 27.1 \text{ mA}$$

$$i_{Bn} = 0.452 \text{ mA}$$

$$I_D = 12.5 - 0.452 \Rightarrow I_D = 12.05 \text{ mA}$$

$$V_{BE_n} = (0.026) \ln \left(\frac{27.1 \times 10^{-3}}{2 \times 10^{-13}} \right)$$

$$\Rightarrow V_{BE_n} = 0.6664 \text{ V}$$

$$V_D = (0.026) \ln \left(\frac{12.05 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6215 \text{ V}$$

$$2V_{DD} = 1.243 \text{ V}$$

$$V_{EB} = 1.243 - 0.6664 \Rightarrow V_{EB_p} = 0.5766 \text{ V}$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left(\frac{0.5766}{0.026} \right) \Rightarrow i_{Cp} = 0.856 \text{ mA}$$

$$c. \quad V_0 = 10 \text{ V}, \quad i_L = \frac{10}{0.075} = 133 \text{ mA}$$

$$i_{En} \approx i_L = 133 \text{ mA} \Rightarrow i_{Cn} = 131 \text{ mA}$$

$$i_{Bn} = 2.18 \text{ mA} \Rightarrow I_D = 12.5 - 2.18$$

$$\Rightarrow I_D = 10.3 \text{ mA}$$

$$V_D = (0.026) \ln \left(\frac{10.3 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6175$$

$$2V_{DD} = 1.235 \text{ V}$$

$$V_{BE_n} = (0.026) \ln \left(\frac{131 \times 10^{-3}}{2 \times 10^{-13}} \right)$$

$$\Rightarrow V_{BE_n} = 0.7074 \text{ V}$$

$$V_{EB_p} = 1.235 - 0.7074 \Rightarrow V_{EB_p} = 0.5276 \text{ V}$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left(\frac{0.5276}{0.026} \right)$$

$$\Rightarrow i_{Cp} = 0.130 \text{ mA}$$

E8.14

$$a. \quad v_I = 0 = v_0, \quad v_{B3} = 0.7 \text{ V}$$

$$I_{R1} = \frac{12 - 0.7}{R_1} = \frac{11.3}{0.25} \Rightarrow I_{R1} = 45.2 \text{ mA}$$

If transistors are matched, then

$$i_{E1} = i_{E3}$$

$$i_{R1} = i_{E1} + i_{B3} = i_{E1} + \frac{i_{E3}}{1 + \beta}$$

$$i_{R1} = i_{E1} \left(1 + \frac{1}{1 + \beta} \right) = i_{E1} \left(1 + \frac{1}{41} \right)$$

$$i_{E1} = \frac{45.2}{1.024} \Rightarrow i_{E1} = i_{E2} = 44.1 \text{ mA}$$

$$i_{B1} = i_{B2} = \frac{i_{E1}}{1 + \beta} = \frac{44.1}{41}$$

$$\Rightarrow i_{B1} = i_{B2} = 1.08 \text{ mA}$$

$$b. \quad \text{For } v_I = 5 \text{ V} \Rightarrow v_0 = 5 \text{ V}$$

$$i_0 = \frac{5}{8} \Rightarrow i_0 = 0.625 \text{ A}$$

$$i_{E3} \approx 0.625 \text{ A}, \quad i_{B3} = \frac{0.625}{41} \Rightarrow i_{B3} = 15.2 \text{ mA}$$

$$v_{B3} = 5.7 \text{ V} \Rightarrow i_{R1} = \frac{12 - 5.7}{0.25} = 25.2 \text{ mA}$$

$$i_{E1} = 25.2 - 15.2 \Rightarrow i_{E1} = 10.0 \text{ mA}$$

$$\Rightarrow i_{B1} = \frac{10}{41} = 0.244 \text{ mA}$$

$$v_{B4} = 5 - 0.7 = 4.3 \text{ V}$$

$$I_{R2} = \frac{4.3 - (-12)}{0.25} = 65.2 \text{ mA} \approx i_{E2}$$

$$i_{B2} = \frac{65.2}{41} = 1.59 \text{ mA}$$


$$i_I = i_{B2} - i_{B1} = 1.59 - 0.244 \Rightarrow i_I = 1.35 \text{ mA}$$

$$c. \quad A_I = \frac{i_0}{i_I} = \frac{625}{1.35} \Rightarrow A_I = 463$$

From Equation (8.54)

$$A_I = \frac{(1 + \beta)R}{2R_L} = \frac{(41)(250)}{2(8)} = 641$$

E8.15

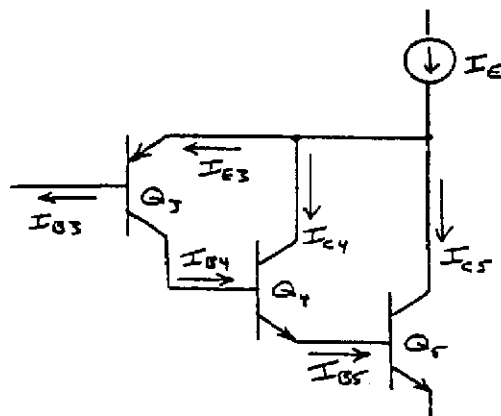

$$\begin{aligned}
 I_E &= I_{E3} + I_{C4} + I_{C5} \\
 &= I_{E3} + I_{C4} + \beta_5 I_{B5} \\
 &= I_{E3} + \beta_4 I_{B4} + \beta_5 (1 + \beta_4) I_{B4} \\
 I_E &= (1 + \beta_3) I_{B3} + \beta_4 \beta_3 I_{B3} + \beta_5 (1 + \beta_4) \beta_3 I_{B3}
 \end{aligned}$$

If β_4 and β_5 are large, then

$$I_E \approx \beta_3 \beta_4 \beta_5 I_{B3}$$

So that composite current gain is

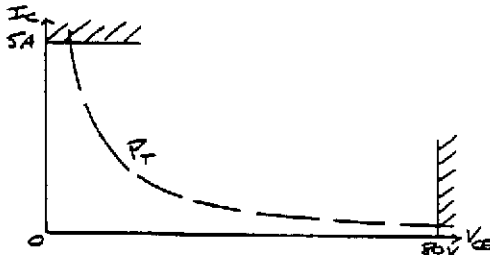
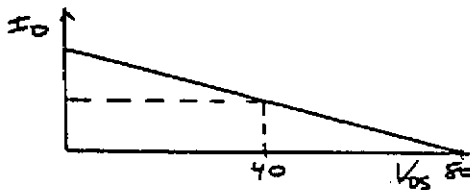
$$\underline{\beta \approx \beta_3 \beta_4 \beta_5}$$

Chapter 8

Problem Solutions


8.1

a.

b. i. $V_{DD} = 80 \text{ V}$ Maximum power at $V_{DS} = \frac{V_{DD}}{2} = 40 \text{ V}$

$$I_D = \frac{P_T}{V_{DS}} = \frac{25}{40} = 0.625 \text{ A}$$

$$R_D = \frac{80 - 40}{0.625} \Rightarrow \underline{R_D = 64 \Omega}$$

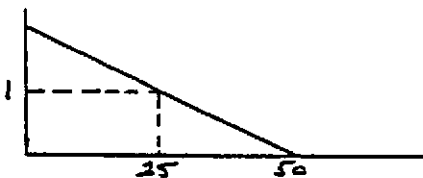ii. $V_{DD} = 50 \text{ V}$ Maximum power at $V_{DS} = \frac{V_{DD}}{2} = 25 \text{ V}$

$$I_D = \frac{P_T}{V_{DS}} = \frac{25}{25} = 1 \text{ A}$$

$$R_D = \frac{50 - 25}{1} \Rightarrow \underline{R_D = 25 \Omega}$$

8.2

$$a. \quad P_Q(\max) = I_{CQ} \cdot \frac{V_{CC}}{2}$$

$$\text{So } I_{CQ} = \frac{2P_Q(\max)}{V_{CC}} = \frac{2(20)}{24} = 1.67 \text{ A}$$

$$R_L = \frac{V_{CC} - (V_{CC}/2)}{I_{CQ}} = \frac{24 - 12}{1.67} \Rightarrow \underline{R_L = 7.2 \Omega}$$

$$I_B = \frac{I_{CQ}}{\beta} = \frac{1.67}{80} \Rightarrow 20.8 \text{ mA}$$

$$R_B = \frac{24 - 0.7}{20.8} \Rightarrow \underline{R_B = 1.12 \text{ k}\Omega}$$

$$b. \quad |A_v| = g_m R_L = \frac{I_{CQ} \cdot R_L}{V_T} = \frac{(1.67)(7.2)}{0.026} = 462$$

$$V_o(\max) = 12 \text{ V} \Rightarrow V_P = \frac{V_o(\max)}{A_v} = \frac{12}{462}$$

$$\Rightarrow \underline{V_P \approx 26 \text{ mV}}$$

8.3

a. For maximum power delivered to the load, set

$$V_{CEQ} = \frac{V_{CC}}{2}$$

$$\text{Set } V_{CC} = 25 \text{ V} = V_{CE(\text{sat})}$$

$$\text{Then } I_{Cm} = \frac{V_{CC}}{R_L} = \frac{25}{0.1}$$

$$I_{Cm} = 250 \text{ mA} < I_{C,\max}$$

$$I_{CQ} = \frac{25 - 12.5}{0.1} = 125 \text{ mA}$$

$$P_Q(\max) = I_{CQ} \cdot \frac{V_{CC}}{2} = (0.125)(12.5)$$

$$= 1.56 \text{ W} < P_{D,\max}$$


$$I_{BQ} = \frac{125}{100} = 1.25 \text{ mA}$$

$$R_B = \frac{25 - 0.7}{1.25} \Rightarrow \underline{R_B = 19.4 \text{ k}\Omega}$$

$$b. \quad P_L(\max) = \frac{1}{2} \cdot I_{CQ}^2 \cdot R_L = \frac{1}{2} (0.125)^2 (100)$$

$$\Rightarrow \underline{P_L(\max) = 0.781 \text{ W}}$$

8.4

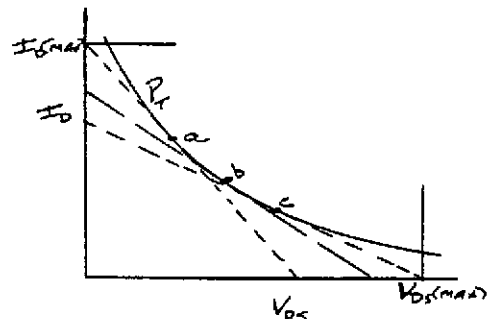


Point (b): Maximum power delivered to load.

Point (a): Will obtain maximum signal current output.

Point (c): Will obtain maximum signal voltage output.

8.5

a.

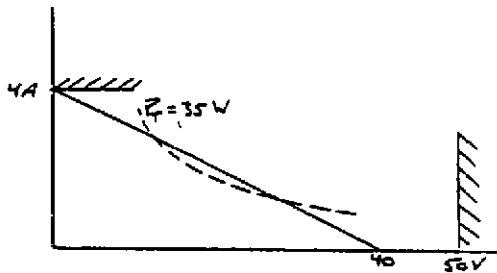

$$b. \quad V_{GG} = 5 \text{ V}, I_D = 0.25(5 - 4)^2 = 0.25 \text{ A},$$

$$V_{DS} = 37.5 \text{ V}, P = 9.375 \text{ W}$$

$$V_{GG} = 6 \text{ V}, I_D = 0.25(6 - 4)^2 = 1.0 \text{ A},$$

$$V_{DS} = 30 \text{ V}, P = 30 \text{ W}$$

$$V_{GG} = 7 \text{ V}, I_D = 0.25(7 - 4)^2 = 2.25 \text{ A},$$

$$V_{DS} = 17.5 \text{ V}, P = 39.375 \text{ W}$$

$$V_{GG} = 8 \text{ V}, I_D = 0.25[2(8 - 4)V_{DS} - V_{DS}^2]$$

$$= \frac{40 - V_{DS}}{10} \Rightarrow V_{DS} = 2.92$$

$$I_D = 3.71 \text{ A}, P = 10.8 \text{ W}$$

$$V_{GG} = 9 \text{ V}, I_D = 0.25[2(9 - 4)V_{DS} - V_{DS}^2]$$

$$= \frac{40 - V_{DS}}{10} \Rightarrow V_{DS} = 1.88 \text{ V}$$

$$I_D = 3.81 \text{ A}, P = 7.16 \text{ W}$$

$$c. \quad \text{Yes, at } V_{GG} = 7 \text{ V}, P = 39.375 \text{ W} > P_{D,\max} = 35 \text{ W}$$

8.6

$$a. \quad \text{Set } V_{DSQ} = \frac{V_{DD}}{2} = 25 \text{ V}$$

$$I_{DQ} = \frac{50 - 25}{20} = 1.25 \text{ A}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$\sqrt{\frac{1.25}{0.2}} + 4 = V_{GS} = 6.5 \text{ V}$$

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$\text{Let } R_1 + R_2 = 100 \text{ k}\Omega$$

$$6.5 = \left(\frac{R_2}{100} \right) (50) \Rightarrow R_2 = 13 \text{ k}\Omega$$

$$R_1 = 87 \text{ k}\Omega$$

$$b. \quad P_D = I_{DQ}V_{DSQ} = (1.25)(25) \Rightarrow P_D = 31.25 \text{ W}$$

$$c. \quad I_{D,\max} = 2I_{DQ} \Rightarrow I_{D,\max} = 2.5 \text{ A}$$

$$V_{DS,\max} = V_{DD} \Rightarrow V_{DS,\max} = 50 \text{ V}$$

$$P_{D,\max} = 31.25 \text{ W}$$

$$d. \quad \left| \frac{V_o}{V_i} \right| = g_m R_L$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(1.25)} = 1 \text{ A/V}$$


$$|V_o| = (1)(20)(0.5) = 10 \text{ V}$$

$$\overline{P_L} = \frac{1}{2} \cdot \frac{V_o^2}{R_L} = \frac{1}{2} \cdot \frac{(10)^2}{20} \Rightarrow \overline{P_L} = 2.5 \text{ W}$$

$$\overline{P_Q} = 31.25 - 2.5 \Rightarrow \overline{P_Q} = 28.75 \text{ W}$$

8.7

(a)

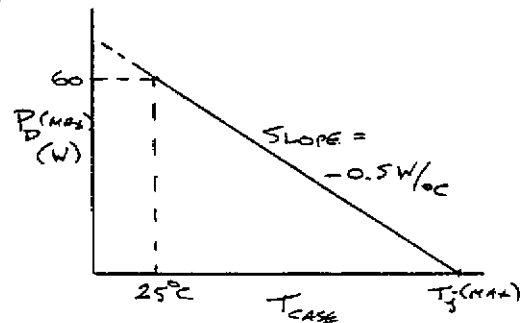

$$(b) \quad P_D = P_{D,\max} - (\text{Slope})(T_J - 25)$$

$$\text{At } P_D = 0, T_{J,\max} = \frac{60}{0.5} + 25 \Rightarrow T_{J,\max} = 145^\circ \text{C}$$

$$(c) \quad P_{D,\max} = \frac{T_{J,\max} - T_{\text{case}}}{\theta_{\text{dev-amb}}}$$

or

$$\theta_{\text{dev-amb}} = \frac{145 - 25}{60} \Rightarrow \theta_{\text{dev-amb}} = 2^\circ \text{C/W}$$

8.8

$$P_{D,\text{rated}} = \frac{T_{J,\max} - T_{\text{amb}}}{\theta_{\text{dev-case}}}$$

or

$$\theta_{\text{dev-case}} = \frac{T_{J,\max} - T_{\text{amb}}}{P_{D,\text{rated}}}$$

$$= \frac{150 - 25}{50} = 2.5^\circ \text{C/W}$$

Then

$$T_{\text{dev}} - T_{\text{amb}} = P_D(\theta_{\text{dev-case}} + \theta_{\text{case-amb}})$$

$$150 - 25 = P_D(2.5 + \theta_{\text{case-amb}})$$

$$\Rightarrow 125 = P_D(2.5 + \theta_{\text{case-amb}})$$

8.9

$$P_D = I_D \cdot V_{DS} = (4)(5) = 20 \text{ W}$$

$$T_{\text{dev}} - T_{\text{amb}} = P_D(\theta_{\text{dev-case}} + \theta_{\text{case-sink}} + \theta_{\text{sink-amb}})$$

$$T_{\text{dev}} - 25 = 20(1.75 + 0.8 + 3) = 111$$

$$\Rightarrow T_{\text{dev}} = 136^\circ\text{C}$$

$$T_{\text{dev}} - T_{\text{case}} = P_D \cdot \theta_{\text{dev-case}} = (20)(1.75) = 35$$

$$T_{\text{case}} = T_{\text{dev}} - 35 = 136 - 35 \Rightarrow T_{\text{case}} = 101^\circ\text{C}$$

$$T_{\text{case}} - T_{\text{sink}} = P_D \cdot \theta_{\text{case-sink}} = (20)(0.8) = 16^\circ\text{C}$$

$$T_{\text{sink}} = T_{\text{case}} - 16 = 101 - 16 \Rightarrow T_{\text{sink}} = 85^\circ\text{C}$$

8.10

$$T_{\text{dev}} - T_{\text{amb}} = P_D(\theta_{\text{dev-case}} + \theta_{\text{case-amb}})$$

$$200 - 25 = 25(3 + \theta_{\text{case-amb}})$$

$$\Rightarrow \theta_{\text{case-amb}} = 4^\circ\text{C/W}$$

8.11

$$\theta_{\text{dev-case}} = \frac{T_{J,\text{max}} - T_{\text{amb}}}{P_{D,\text{rated}}} = \frac{175 - 25}{15} = 10^\circ\text{C/W}$$

$$P_D = \frac{T_{J,\text{max}} - T_{\text{amb}}}{\theta_{\text{dev-case}} + \theta_{\text{case-sink}} + \theta_{\text{sink-amb}}} = \frac{175 - 25}{10 + 1 + 4} \Rightarrow P_D = 10 \text{ W}$$

8.12

$$\eta = \frac{\overline{P}_L}{\overline{P}_S}$$

$$\overline{P}_S = V_{CC} \cdot I_Q$$

$$\overline{P}_L = V_P \cdot I_P = \left(\frac{V_{CC}}{2}\right)(I_Q)$$

$$\eta = \frac{\frac{1}{2} \cdot V_{CC} \cdot I_Q}{V_{CC} \cdot I_Q} \Rightarrow \eta = 50\%$$

8.13

a. Neglect base currents.

$$v_o(\text{max}) = V^+ - V_{CE}(\text{sat}) = 10 - 0.2 = 9.8 \text{ V}$$

$$i_L(\text{max}) = I_Q = \frac{9.8}{R_L} = \frac{9.8}{1} \Rightarrow I_Q = 9.8 \text{ mA}$$

$$R = \frac{0 - 0.7 - (-10)}{9.8} \Rightarrow R = 949 \Omega$$

$$i_{E1}(\text{max}) = 2I_Q \Rightarrow i_{E1}(\text{max}) = 19.6 \text{ mA}$$

$$i_{E1}(\text{min}) = 0$$

$$i_L(\text{max}) = I_Q = 9.8 \text{ mA}$$

$$i_L(\text{min}) = -I_Q = -9.8 \text{ mA}$$

$$\text{b. } \overline{P}_L = \frac{1}{2}(i_L(\text{max}))^2 R_L = \frac{1}{2}(9.8)^2(1)$$

$$\Rightarrow \overline{P}_L = 48.02 \text{ mW}$$

$$\overline{P}_S = I_Q(V^+ - V^-) + I_Q(0 - V^-)$$

$$= 9.8(20) + 9.8(10) \Rightarrow \overline{P}_S = 294 \text{ mW}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{48.02}{294} \Rightarrow \eta = 16.3\%$$

8.14

$$\text{a. } I_Q(\text{min}) = \frac{v_o(\text{max})}{R_L} = \frac{10}{0.1} \Rightarrow I_Q(\text{min}) = 100 \text{ mA}$$

$$R = \frac{0 - 0.7 - (-12)}{100} \Rightarrow R = 113 \Omega$$

$$\text{b. } P_{Q1} = I_Q \cdot V_{CE1} = (100)(12) \Rightarrow P_{Q1} = 1.2 \text{ W}$$

$$P(\text{source}) = 2I_Q(12) = 2.4 \text{ W}$$

$$\text{c. } \overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{(10)^2}{2(100)} = 0.5 \text{ W}$$

$$\overline{P}_S = 1.2 + 2.4 = 3.6 \text{ W}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{0.5}{3.6} \Rightarrow \eta = 13.9\%$$

8.15

$$\overline{P}_L = \frac{V_P^2}{R_L} = \frac{(V^+)^2}{R_L}$$

$$\overline{P}_S = \frac{1}{2} \cdot \frac{(V^+)^2}{R_L} + \frac{1}{2} \cdot \frac{(V^-)^2}{R_L}, \quad V^- = -V^+$$

$$\text{So } \overline{P}_S = \frac{(V^+)^2}{R_L}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} \Rightarrow \eta = 100\%$$

8.16

$$\text{(a) } V_{DS} \geq V_{DS}(\text{sat}) = V_{GS} - V_{TN} = V_{GS}$$

$$V_{DS} = 10 - V_o(\text{max}) \text{ and } I_D = I_L = K_n(V_{GS})^2$$

$$\frac{V_o(\text{max})}{R_L} = K_n(V_{GS})^2$$

$$V_{GS} = \sqrt{\frac{V_o(\text{max})}{R_L \cdot K_n}}$$

So

$$10 - V_o(\text{max}) = \sqrt{\frac{V_o(\text{max})}{R_L \cdot K_n}} = \sqrt{\frac{V_o(\text{max})}{(5)(0.4)}}$$

$$[10 - V_o(\text{max})]^2 = \frac{V_o(\text{max})}{2}$$

$$100 - 20V_o(\text{max}) + V_o^2(\text{max}) = \frac{V_o(\text{max})}{2}$$

$$V_o^2(\max) - 20.5V_o(\max) + 100 = 0$$

$$V_o(\max) = \frac{20.5 \pm \sqrt{(20.5)^2 - 4(100)}}{2}$$

$$\Rightarrow V_o(\max) = 8 \text{ V}$$

$$i_L = \frac{8}{5} \Rightarrow i_L = 1.6 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{i_L}{K_n}} = \sqrt{\frac{1.6}{0.4}} = 2 \text{ V}$$

$$\Rightarrow v_I = 10 \text{ V}$$

$$\text{b. } \overline{P_L} = \frac{1}{2} \cdot \frac{(8)^2}{5} = 6.4 \text{ mW}$$

$$\overline{P_S} = \frac{20(1.6)}{\pi} = 10.2 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{6.4}{10.2} \Rightarrow \eta = 62.7\%$$

8.17

$$v_o = i_L R_L \text{ and } i_L = i_D = K_n(v_{GS} - V_{TN})^2$$

$$\text{or } i_L = K_n(v_{GS})^2 \text{ and } v_{GS} = v_I - v_o$$

Then

$$v_o = K_n R_L (v_I - v_o)^2 \text{ or } v_o = 2(v_I - v_o)^2$$

$$\frac{dv_o}{dv_I} = 2.2(v_I - v_o) \left(1 - \frac{dv_o}{dv_I} \right)$$

$$\frac{dv_o}{dv_I} [1 + 4(v_I - v_o)] = 4(v_I - v_o)$$

$$\text{or } \frac{dv_o}{dv_I} = \frac{4(v_I - v_o)}{1 + 4(v_I - v_o)}$$

$$\text{For } v_I = 10 \text{ V, } v_o = 8 \text{ V} \Rightarrow \frac{dv_o}{dv_I} = \frac{4(10 - 8)}{1 + 4(10 - 8)}$$

$$\Rightarrow \frac{dv_o}{dv_I} = 0.889$$

$$\text{At } v_I = 0, v_o = 0 \Rightarrow \frac{dv_o}{dv_I} = 0$$

$$\text{At } v_I = 1, v_o = 0.5 \Rightarrow \frac{dv_o}{dv_I} = 0.667$$

8.18

$$\text{a. } V_{BE} = V_T \ln \left(\frac{i_C}{I_S} \right) = (0.026) \ln \left(\frac{5 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$V_{BE} = \frac{V_{BB}}{2} = 0.5987 \text{ V}$$

$$\Rightarrow V_{BB} = 1.1973 \text{ V}$$

$$P_Q = i_C \cdot v_{CE} = (5)(10) \Rightarrow P_Q = 50 \text{ mW}$$

$$\text{b. } v_o = -8 \text{ V}$$

$$i_L = \frac{-8}{0.1} \Rightarrow i_L = -80 \text{ mA}$$

$$i_{CP} \approx 80 \text{ mA}$$

$$v_{EB} = V_T \ln \left(\frac{i_{CB}}{I_S} \right) = (0.026) \ln \left(\frac{80 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$v_{EB} = 0.6708 \text{ V}$$

$$v_I = \frac{V_{BB}}{2} - v_{EB} + v_o = 0.5987 - 0.6708 - 8$$

$$\Rightarrow v_I = -8.072 \text{ V}$$

$$v_{BE} = V_{BB} - v_{EB} = 1.1973 - 0.6708 = 0.5265 \text{ V}$$

$$i_{Cn} = I_S \exp \left(\frac{v_{BE}}{V_T} \right) = 5 \times 10^{-13} \exp \left(\frac{0.5265}{0.026} \right)$$

$$\Rightarrow i_{Cn} = 0.311 \text{ mA}$$

$$P_L = i_L^2 R_L = (80)^2 (0.1) \Rightarrow P_L = 640 \text{ mW}$$

$$P_{Qn} = i_{Cn} \cdot v_{CE} = (0.311)(10 - (-8))$$

$$\Rightarrow P_{Qn} = 5.60 \text{ mW}$$

$$P_{QP} = i_{CP} \cdot v_{EC} = (80)(2) \Rightarrow P_{QP} = 160 \text{ mW}$$

8.19

$$\text{(a) } i_{Dn} = K_n (v_{GSn} - V_{TN})^2$$

$$\sqrt{\frac{0.5}{2}} + 2 = v_{GSn} = 2.5 \text{ V} = \frac{V_{BB}}{2}$$

$$\Rightarrow V_{BB} = 5.0 \text{ V}$$

$$P_n = (0.5)(10) \Rightarrow P_n = P_p = 5 \text{ mW}$$

$$\text{(b) } V_{DS} = V_{GS} - V_{TN} \Rightarrow V_{DS} = V_{GS} - 2$$

$$V_{DS} = 10 - v_o(\max)$$

and

$$V_{GS} = \sqrt{\frac{i_L}{K_n}} + V_{TN} = \sqrt{\frac{v_o(\max)}{R_L K_n}} + 2$$

$$= \sqrt{\frac{v_o(\max)}{(2)(1)}} + 2$$

so

$$10 - v_o(\max) = \sqrt{\frac{v_o(\max)}{2}} + 2 - 2 = \sqrt{\frac{v_o(\max)}{2}}$$

$$\text{so } v_o(\max) = 8 \text{ V}$$

$$i_{Dn} = i_L = \frac{8}{1} \Rightarrow i_{Dn} = i_L = 8 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{8}{2}} + 2 \Rightarrow V_{GS} = 4 \text{ V}$$

$$\text{Then } v_I = v_o + V_{GS} - \frac{V_{BB}}{2} = 8 + 4 - 2.5$$

$$\Rightarrow v_I = 9.5 \text{ V}$$

$$v_{SGP} = v_o - \left(v_I - \frac{V_{BB}}{2} \right) = 8 - (9.5 - 2.5)$$

$$v_{SGP} = 1 \text{ V} \Rightarrow M_P \text{ cutoff} \Rightarrow i_{DP} = 0$$

$$P_L = i_L^2 R_L = (8)^2 (1) \Rightarrow \underline{P_L = 64 \text{ mW}}$$

$$P_{Mn} = i_{Dn} \cdot v_{DS} = (8)(10 - 8) \Rightarrow \underline{P_{Mn} = 16 \text{ mW}}$$

$$P_{Mp} = i_{Dp} \cdot v_{SD} \Rightarrow \underline{P_{Mp} = 0}$$

8.20

$$\text{a. } v_0 = 24 \text{ V} \Rightarrow i_L = \frac{24}{8} \Rightarrow \underline{i_L \approx i_N = 3 \text{ A}}$$

$$i_{Bn} = \frac{3}{41} \Rightarrow i_{Bn} = 73.2 \text{ mA}$$

$$\text{For } i_D = 25 \text{ mA} \Rightarrow i_{R1} = 25 + 73.2 = 98.2 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{i_N}{I_S} \right) = (0.026) \ln \left(\frac{3}{6 \times 10^{-12}} \right) \\ = 0.7004 \text{ V}$$

$$\text{Then } 98.2 = \frac{30 - (24 + 0.7)}{R_1} \Rightarrow R_1 = \frac{5.3}{98.2}$$

$$\Rightarrow \underline{R_1 = 53.97 \Omega}$$

$$V_D = (0.026) \ln \left(\frac{25 \times 10^{-3}}{6 \times 10^{-12}} \right) = 0.5759 \text{ V}$$

$$V_{EB} = 2V_D - V_{BE} = 2(0.5759) - 0.7004 \\ = 0.4514 \text{ V}$$

$$i_P = I_S \exp \left(\frac{V_{EB}}{V_T} \right) = (6 \times 10^{-12}) \exp \left(\frac{0.4514}{0.026} \right) \\ \Rightarrow \underline{i_P = 0.208 \text{ mA}}$$

b. Neglecting base current

$$i_D \approx \frac{30 - 0.6}{R_1} = \frac{30 - 0.6}{53.97} \Rightarrow \underline{i_D \approx 545 \text{ mA}}$$

$$V_D = (0.026) \ln \left(\frac{0.545}{6 \times 10^{-12}} \right) = 0.656 \text{ V}$$

Approximation for i_D is okay.

$$\text{Diodes and transistors matched} \Rightarrow \underline{i_N = i_P = 545 \text{ mA}}$$

8.21

$$\text{(a) } I_{D1} = K_1(V_{GS1} - V_{TN})^2$$

$$V_{GS1} = \sqrt{\frac{5}{5}} + 1 = 2 \text{ V}$$

$$I_{D1} = K_3(V_{GS1} - V_{TN})^2$$

$$200 = K_3(2 - 1)^2 \Rightarrow \underline{K_{n3} = K_{p4} = 200 \mu\text{A/V}^2}$$

$$\text{(b) } v_i + V_{SG4} + V_{GS3} - V_{GS1} = v_o$$

$$\text{For } v_o \text{ large, } i_L = i_i = K_{n1}(V_{GS1} - V_{TN})^2$$

$$V_{GS1} = \sqrt{\frac{i_L}{K_{n1}}} + V_{TN} = \sqrt{\frac{v_o}{R_L K_{n1}}} + V_{TN}$$

$$\text{So } v_i + 2 + 2 - \left(\sqrt{\frac{v_o}{(0.5)(5)}} + 1 \right) = v_o$$

$$v_i = v_o + \sqrt{\frac{v_o}{2.5}} - 3$$

$$\frac{dv_i}{dv_i} = 1 = \frac{dv_o}{dv_i} + \frac{1}{2} \cdot \frac{1}{\sqrt{2.5v_o}} \cdot \frac{dv_o}{dv_i}$$

$$1 = \frac{dv_o}{dv_i} \left[1 + \frac{1}{2\sqrt{2.5v_o}} \right]$$

For $v_o = 5 \text{ V}$:

$$1 = \frac{dv_o}{dv_i} \left[1 + \frac{1}{2\sqrt{2.5(5)}} \right] = \frac{dv_o}{dv_i} (1.1414) \\ \Rightarrow \underline{\frac{dv_o}{dv_i} = 0.876}$$

8.22

$$v_o = v_i + \frac{V_{EB}}{2} - V_{GS} \text{ and } V_{GS} = \sqrt{\frac{I_{Dn}}{K_n}} + V_{TN}$$

$$\text{For } v_o = 0, I_{Dn} = I_{DQ} + i_L = I_{DQ} + \frac{v_o}{R_L}$$

Then

$$v_o = v_i + \frac{V_{EB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ} + (v_o/R_L)}{K_n}}$$

or

$$v_o = v_i + \frac{V_{EB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}} \cdot \sqrt{1 + \frac{v_o}{I_{DQ}R_L}}$$

For v_o small,

$$v_o \approx v_i + \frac{V_{EB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}} \cdot \left(1 + \frac{1}{2} \cdot \frac{v_o}{I_{DQ}R_L} \right)$$

$$v_o \left[1 + \frac{1}{2} \cdot \sqrt{\frac{I_{DQ}}{K_n}} \cdot \frac{1}{I_{DQ}R_L} \right]$$

$$= v_i + \frac{V_{EB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}}$$

Now

$$\frac{dv_o}{dv_i} = \frac{1}{\left[1 + \frac{1}{2} \cdot \sqrt{\frac{I_{DQ}}{K_n}} \cdot \frac{1}{I_{DQ}R_L} \right]} = 0.95$$

$$\text{So } \frac{1}{2} \cdot \sqrt{\frac{I_{DQ}}{K_n}} \cdot \frac{1}{I_{DQ}R_L} = \frac{1}{0.95} - 1 = 0.0526$$

$$\text{For } R_L = 0.1 \text{ k}\Omega, \text{ then } \frac{1}{\sqrt{K_n I_{DQ}}} = 0.01052$$

$$\text{Or } \sqrt{K_n I_{DQ}} = 95.1$$

We can write

$$g_m = 2\sqrt{K_n I_{DQ}} = 190 \text{ mA/V}$$

This is the required transconductance for the output transistor. This implies a very large transistor.

8.23

$$A_v = -g_m R_L$$

$$\text{So } -12 = -g_m(2) \Rightarrow g_m = 6 \text{ mA/V} = \frac{I_{CQ}}{V_T}$$

$$I_{CQ} = (6)(0.026) \Rightarrow I_{CQ} = 0.156 \text{ mA}$$

But for maximum symmetrical swing, set

$$I_{CQ} = \frac{V_{CC}}{R_L} = \frac{10}{2} = 5 \text{ mA} \Rightarrow |A_v| > 12$$

Maximum power to the load:

$$\overline{P_L}(\text{max}) = \frac{1}{2} \cdot \frac{V_{CC}^2}{R_L} = \frac{(10)^2}{2(2)} \Rightarrow \overline{P_L}(\text{max}) = 25 \text{ mW}$$

$$\overline{P_S} = V_{CC} \cdot I_{CQ} = (10)(5) = 50 \text{ mW}$$

$$\text{So } \eta = 50\%$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{5}{180} = 0.0278 \text{ mA}$$

$$R_1 = R_{TH} = 6 \text{ k}\Omega$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(\text{on})} + (1 + \beta) I_{BQ} R_E$$

$$\text{Set } R_E = 20 \Omega$$

$$V_{TH} = (0.0278)(6) + 0.7 + (181)(0.0278)(0.020)$$

$$V_{TH} = 0.967 \text{ V}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$0.967 = \frac{1}{R_1}(6)(10) \Rightarrow R_1 = 62.0 \text{ k}\Omega$$

$$R_2 = 6.64 \text{ k}\Omega$$

8.24

$$I_{CQ} = \frac{V_{CC}}{R_L} = \frac{15}{1} = 15 \text{ mA}$$

$$I_{BQ} = \frac{15}{100} = 0.15 \text{ mA}$$

$$\overline{P_L}(\text{max}) = \frac{1}{2} \cdot \frac{V_{CC}^2}{R_L} = \frac{(15)^2}{2(1)} \Rightarrow \overline{P_L}(\text{max}) = 112.5 \text{ mW}$$

$$\text{Let } R_{TH} = 10 \text{ k}\Omega$$

$$\begin{aligned} V_{TH} &= I_{BQ} R_{TH} + V_{BE} + (1 + \beta) I_{BQ} R_E \\ &= (0.15)(10) + 0.7 + (101)(0.15)(0.1) \end{aligned}$$

$$V_{TH} = 3.715 = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} \cdot (10)(15)$$

$$R_1 = 40.4 \text{ k}\Omega$$

$$R_2 = 13.3 \text{ k}\Omega$$

8.25

$$\begin{aligned} V_{TH} &= \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{1.55}{1.55 + 0.73} \right) (10) \\ &= 6.80 \text{ V} \end{aligned}$$

$$R_{TH} = R_1 \| R_2 = 0.73 \| 1.55 = 0.496 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} = \frac{6.80 - 0.70}{0.496 + (26)(0.02)}$$

$$I_{BQ} = 6.0 \text{ mA}, I_{CQ} = 150 \text{ mA}$$

$$A_v = -g_m R'_L \text{ and } R'_L = a^2 R_L = (3)^2(8) = 72 \Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{150}{0.026} \Rightarrow 5.77 \text{ A/V}$$

$$A_v = -(5.77)(72) = -415$$

$$|V_o|' = |A_v| \cdot V_i = (415)(0.017) = 7.06 \text{ V}$$

$$V_o = \frac{7.06}{3} = 2.35 \text{ V}$$

$$\overline{P_L} = \frac{1}{2} \cdot \frac{V_o^2}{R_L} = \frac{(2.35)^2}{2(8)} \Rightarrow \overline{P_L} = 345 \text{ mW}$$

$$\overline{P_S} = I_{CQ} \cdot V_{CC} = (0.15)(10) = 1.5 \text{ W}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{0.345}{1.5} \Rightarrow \eta = 23\%$$

8.26

a. Assuming the maximum power is being delivered, then

$$V_o'(\text{peak}) = 36 \text{ V} \Rightarrow V_o = \frac{36}{4} = 9 \text{ V}$$

$$\Rightarrow V_{\text{rms}} = \frac{9}{\sqrt{2}} \Rightarrow V_{\text{rms}} = 6.36 \text{ V}$$

$$\text{b. } V_o = \frac{36}{\sqrt{2}} \Rightarrow V_o = 25.5 \text{ V}$$

$$\text{c. Secondary } I_{\text{rms}} = \frac{R_L}{V_{\text{rms}}} = \frac{2}{6.36} \Rightarrow I_{\text{rms}} = 0.314 \text{ A}$$


$$\text{Primary } I_P = \frac{0.314}{4} \Rightarrow I_P = 78.6 \text{ mA}$$

$$\text{d. } \overline{P_S} = I_{CQ} \cdot V_{CC} = (0.15)(36) = 5.4 \text{ W}$$

$$\eta = \frac{2}{5.4} \Rightarrow \eta = 37\%$$

8.27

a.

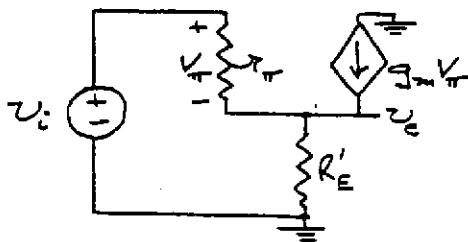

$$v_o = \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) R'_E = V_\pi \left(\frac{1}{r_\pi} + g_m \right) R'_E$$

$$= V_\pi \left(\frac{1 + \beta}{r_\pi} \right) R'_E$$

$$v_i = V_\pi + v_o \Rightarrow V_\pi = v_i - v_o$$

$$v_o = (v_i - v_o) \left(\frac{1 + \beta}{r_\pi} \right) R'_E$$

$$\frac{v_o}{v_i} = \frac{\frac{1 + \beta}{r_\pi} \cdot R'_E}{1 + \frac{1 + \beta}{r_\pi} \cdot R'_E} = \frac{(1 + \beta) R'_E}{r_\pi + (1 + \beta) R'_E} = \frac{v_o}{v_i}$$

$$\text{where } R'_E = \left(\frac{n_1}{n_2} \right)^2 R_L$$

$$v_o = \frac{v_o}{\left(\frac{n_1}{n_2} \right)} \text{ so } v_o = v_o \left(\frac{n_1}{n_2} \right)$$

$$\text{so } \frac{v_o}{v_i} = \frac{1}{\left(\frac{n_1}{n_2} \right)} \cdot \frac{(1 + \beta) R'_E}{r_\pi + (1 + \beta) R'_E}$$

$$\text{b. } \overline{P_L} = \frac{1}{2} \cdot I_P^2 R_L, a = \frac{n_1}{n_2}, I_{CQ} = \frac{I_P}{a}$$

$$\text{so } \overline{P_L} = \frac{1}{2} \cdot a^2 I_{CQ}^2 R_L$$

$$\overline{P_S} = I_{CQ} \cdot V_{CC}$$

For $\eta = 50\%$:

$$\frac{\overline{P_L}}{\overline{P_S}} = 0.5 = \frac{\frac{1}{2} \cdot a^2 I_{CQ}^2 R_L}{I_{CQ} \cdot V_{CC}} = \frac{a^2 I_{CQ} R_L}{2 V_{CC}}$$


$$\text{so } a^2 = \frac{V_{CC}}{I_{CQ} \cdot R_L} = \frac{V_{CC}}{(0.1)(50)} \Rightarrow a^2 = \frac{V_{CC}}{5}$$

$$\text{c. } R_0 = \frac{r_\pi}{1 + \beta} = \frac{\beta V_T}{(1 + \beta) I_{CQ}} = \frac{49(0.026)}{(50)(0.1)}$$

$$\Rightarrow R_0 = 0.255 \Omega$$

8.28

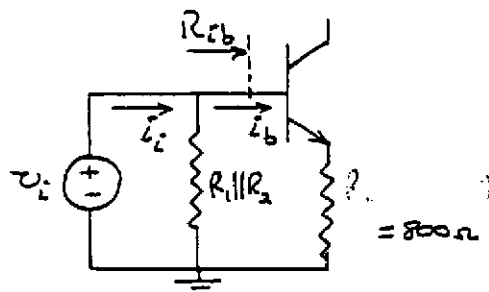- a. With a 10:1 transformer ratio, we need a current gain of 8 through the transistor.



$$i_e = (1 + \beta) i_b \text{ and } i_b = \left(\frac{R_1 || R_2}{R_1 || R_2 + R_{ib}} \right) i_i$$

so we need

$$\frac{i_e}{i_i} = 8 = (1 + \beta) \left(\frac{R_1 || R_2}{R_1 || R_2 + R_{ib}} \right)$$

where

$$R_{ib} = r_\pi + (1 + \beta) R'_E \approx (1 + \beta) R'_E$$

$$= (101)(0.8) = 80.8$$

$$\text{Then } 8 = (101) \left(\frac{R_1 || R_2}{R_1 || R_2 + 80.8} \right)$$

$$\frac{R_1 || R_2}{R_1 || R_2 + 80.8} = 0.0792 \text{ or } R_1 || R_2 = 6.95 \text{ k}\Omega$$

Set

$$\frac{2V_{CC}}{2I_{CQ}} = R'_E \Rightarrow I_{CQ} = \frac{V_{CC}}{R'_E} = \frac{12}{0.8} = 15 \text{ mA}$$

$$I_{BQ} = \frac{15}{100} = 0.15 \text{ mA}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE}$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ} R_{TH} + V_{BE}$$

$$\frac{1}{R_1} (6.95)(12) = (0.15)(6.95) + 0.7$$

$$\Rightarrow R_1 = 47.9 \text{ k}\Omega \text{ then } R_2 = 8.13 \text{ k}\Omega$$

$$\text{b. } I_e = 0.9 I_{CQ} = 13.5 \text{ mA} \approx \frac{I_L}{a} \Rightarrow I_L = 135 \text{ mA}$$

$$\overline{P_L} = \frac{1}{2} (0.135)^2 (8) \Rightarrow \overline{P_L} = 72.9 \text{ mW}$$

$$\overline{P_S} = V_{CC} I_{CQ} = (12)(15) \Rightarrow \overline{P_S} = 180 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} \Rightarrow \eta = 40.5\%$$

8.29

a. $V_P = \sqrt{2R_L P_L}$

$$V_P = \sqrt{2(8)(1)} = 5.66 \text{ V} = \text{peak output voltage}$$

$$I_P = \frac{V_P}{R_L} = \frac{5.66}{8} = 0.708 \text{ A} = \text{peak output current}$$

Set $V_e = 0.9V_{CC} = aV_P$ to minimize distortion

$$\text{Then } a = \frac{(0.9)(18)}{5.66} \Rightarrow a = 2.86$$

b. Now


$$I_{CQ} = \frac{1}{0.9} \left(\frac{I_P}{a} \right) = \frac{1}{0.9} \left(\frac{0.708}{2.86} \right) \Rightarrow I_{CQ} = 0.275 \text{ A}$$

$$\text{Then } P_Q = V_{CC} I_{CQ} = (18)(0.275)$$

$$\Rightarrow P_Q = 4.95 \text{ W Power rating of transistor}$$

8.30

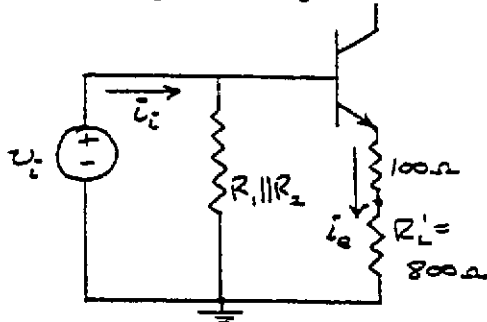a. Need a current gain of 8 through the transistor.



$$\frac{i_b}{i_i} = 8 = (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right)$$

$$\text{where } R_{ib} \approx (1 + \beta)(0.9) = 90.9 \text{ k}\Omega$$

$$\frac{8}{101} = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 90.9} \right) = 0.0792$$

$$\text{or } R_1 \parallel R_2 = 7.82 \text{ k}\Omega$$

Set

$$\frac{2V_{CC}}{2I_{CQ}} = 0.9 \text{ k}\Omega \Rightarrow I_{CQ} = \frac{12}{0.9} = 13.3 \text{ mA}$$

$$I_{BQ} = \frac{13.3}{100} = 0.133 \text{ mA}$$

Then

$$\frac{1}{R_1}(7.82)(12) = (0.133)(7.82) + 0.7$$

$$\Rightarrow R_1 = 53.9 \text{ k}\Omega \text{ and } R_2 = 9.15 \text{ k}\Omega$$

b. $I_e = (0.9)I_{CQ} = 12 \text{ mA} = \frac{I_L}{a} \Rightarrow I_L = 120 \text{ mA}$

$$\overline{P_L} = \frac{1}{2}(0.12)^2(8) \Rightarrow \overline{P_L} = 57.6 \text{ mW}$$

$$\overline{P_S} = V_{CC} I_{CQ} = (12)(13.3) \Rightarrow \overline{P_S} = 159.6 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{57.6}{159.6} \Rightarrow \eta = 36.1\%$$

8.31

a. All transistors are matched.

$$3 \text{ mA} = i_{E1} + i_{B3} = \left(\frac{1 + \beta}{\beta} \right) i_C + \frac{i_C}{\beta}$$

$$3 = \left(\frac{61}{60} + \frac{1}{60} \right) i_C \Rightarrow i_C = 2.90 \text{ mA}$$

b. For $v_o = 6 \text{ V}$, let $R_L = 200 \Omega$.

$$i_o = \frac{6}{200} = 0.03 \text{ A} = 30 \text{ mA} \approx i_{E3}$$

$$i_{B3} = \frac{30}{61} = 0.492 \text{ mA}$$

$$i_{E1} = 3 - 0.492 = 2.508 \text{ mA}$$

$$i_{B1} = \frac{2.508}{61} \Rightarrow i_{B1} = 41.11 \mu\text{A}$$

$$i_{E2} \approx 3 \text{ mA} \Rightarrow i_{B2} = \frac{3}{61} \Rightarrow 49.18 \mu\text{A}$$

$$i_I = i_{B2} - i_{B1} = 49.18 - 41.11 \Rightarrow i_I = 8.07 \mu\text{A}$$

Current gain

$$A_i = \frac{30 \times 10^{-3}}{8.07 \times 10^{-6}} \Rightarrow A_i = 3.72 \times 10^3$$

$$V_{BE3} = V_T \ln \left(\frac{i_{E3}}{I_S} \right) = (0.026) \ln \left(\frac{30 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$V_{BE3} = 0.6453 \text{ V}$$

$$V_{EB1} = V_T \ln \left(\frac{i_{E1}}{I_S} \right) = (0.026) \ln \left(\frac{2.508 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$V_{EB1} = 0.5807 \text{ V}$$

$$v_I = v_o + V_{BE3} - V_{EB1} = 6 + 0.6453 - 0.5807$$

$$v_I = 6.0646 \text{ V}$$

Voltage gain

$$A_v = \frac{v_o}{v_I} = \frac{6}{6.0646} \Rightarrow A_v = 0.989$$

8.32

a. For $i_0 = 1$ A, $I_{B3} \approx \frac{1}{50} \Rightarrow 20$ mA

We can then write

$$\frac{10 - V_{BE1}}{R_1} = 2 \left[\frac{10 - (v_{0,\max} + V_{BE3})}{R_1} - 20 \right]$$

If, for simplicity, we assume $V_{BE1} = V_{BE3} = 0.7$ V, then

$$\frac{10 - V_{BE}}{R_1} = \frac{2v_{0,\max}}{R_1} + 40$$

If we assume $v_{0,\max} = 4$ V, then

$$\frac{9.3}{R_1} = \frac{2(4)}{R_1} + 40$$

which yields $R_1 = R_2 = 32.5 \Omega$

b. For $v_I = 0$,

$$I_{E1} = \frac{9.3}{32.5} \Rightarrow I_{E1} = 0.286 \text{ A} = I_{E2}$$

Since $I_{S3,4} = 10I_{S1,2}$, then

$$I_{E3} = I_{E4} = 2.86 \text{ A}$$

c. We can write

$$R_0 = \frac{1}{2} \left\{ \frac{r_{\pi3} + R_1 \parallel \frac{r_{\pi1}}{1 + \beta_1}}{1 + \beta_3} \right\}$$

$$\text{Now } r_{\pi3} = \frac{\beta_3 V_T}{I_{C3}} = \frac{(50)(0.026)}{2.86} = 0.4545 \Omega$$

$$r_{\pi1} = \frac{\beta_1 V_T}{I_{C1}} = \frac{(120)(0.026)}{0.286} = 10.91 \Omega$$

So

$$R_0 = \frac{1}{2} \left\{ \frac{0.4545 + 32.5 \parallel \frac{10.91}{121}}{51} \right\}$$

$$32.5 \parallel \frac{10.91}{121} = 32.5 \parallel 0.0902 = 0.0900$$

Then

$$R_0 = \frac{1}{2} \left\{ \frac{0.4545 + 0.0900}{51} \right\} \text{ or } R_0 = 0.00534 \Omega$$

8.33

$$R_i = \frac{1}{2} \{ r_{\pi1} + (1 + \beta)[R_1 \parallel (r_{\pi3} + (1 + \beta)R_L)] \}$$

$$i_{C1} \approx 7.2 \text{ mA and } i_{C3} \approx 7.2 \text{ mA}$$

$$\text{Then } r_{\pi} = \frac{(60)(0.026)}{7.2} = 0.217 \text{ k}\Omega$$

So

$$R_i = \frac{1}{2} \{ 0.217 + (61)[2 \parallel (0.217 + (61)(0.1))] \}$$


$$= \frac{1}{2} \{ 0.217 + 61[2 \parallel 6.32] \}$$

or

$$R_i = 46.4 \text{ k}\Omega$$

8.34

a.

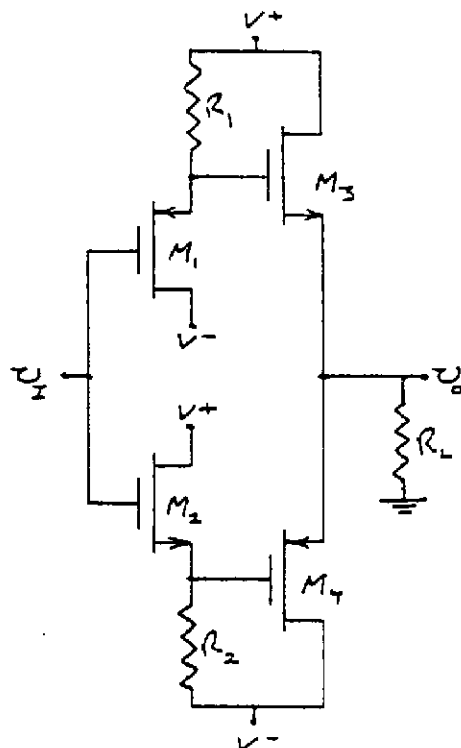

$$\text{b. } I_1 = K_1(V_{SG} + V_{TP})^2 = \frac{V^+ - V_{SG}}{R_1}$$

$$5 = 10(V_{SG} - 2)^2 \Rightarrow V_{SG} = 2.707 \text{ V}$$

$$5 = \frac{10 - 2.707}{R_1} \Rightarrow R_1 = R_2 = 1.46 \text{ k}\Omega$$

Then

$$R_0 = \frac{169 + 25}{1 + (10) + (10)(50) + [10 + (10)(50)](50)}$$

$$R_0 = \frac{194}{26,011} = 0.00746 \text{ k}\Omega$$

$$\text{or } R_0 = 7.46 \Omega$$

8.36

a. Neglect base currents.

$$\begin{aligned} V_{BB} &= 2V_D = 2V_T \ln \left(\frac{I_{B10}}{I_S} \right) \\ &= 2(0.026) \ln \left(\frac{5 \times 10^{-3}}{10^{-13}} \right) \\ &\Rightarrow \underline{V_{BB} = 1.281 \text{ V}} \end{aligned}$$

$$V_{BE1} + V_{EB3} = V_{BB}$$

$$I_{E1} = I_{E3} + I_{C2}$$

$$I_{B2} = I_{C3} = \left(\frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{C2} = \beta_n I_{B2} = \beta_n \left(\frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{E1} = I_{E3} + \beta_n \left(\frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{E1} = I_{E3} \left[1 + \beta_n \left(\frac{\beta_p}{1 + \beta_p} \right) \right]$$

$$\left(\frac{1 + \beta_n}{\beta_n} \right) I_{C1} = \left(\frac{1 + \beta_p}{\beta_p} \right) I_{C3} \left[1 + \beta_n \left(\frac{\beta_p}{1 + \beta_p} \right) \right]$$

$$V_{BE1} = V_T \ln \left[\frac{I_{C1}}{I_S} \right], \quad V_{EB3} = V_T \ln \left[\frac{I_{C3}}{I_S} \right]$$

$$\begin{aligned} (1.01)I_{C1} &= \left(\frac{21}{20} \right) I_{C3} \left[1 + (100) \left(\frac{20}{21} \right) \right] \\ &= I_{C3} \left[\frac{21}{20} + 100 \right] = 101.05 I_{C3} \end{aligned}$$

$$I_{C1} = 100.05 I_{C3}$$

$$V_T \ln \left(\frac{100.05 I_{C3}}{I_S} \right) + V_T \ln \left(\frac{I_{C3}}{I_S} \right) = V_{BB}$$

$$V_T \ln \left(\frac{100.05 I_{C3}^2}{I_S^2} \right) = V_{BB}$$

$$\frac{100.05 I_{C3}^2}{I_S^2} = \exp \left(\frac{V_{BB}}{V_T} \right)$$

$$I_{C3} = \frac{I_S}{\sqrt{100.05}} \sqrt{\exp \left(\frac{V_{BB}}{V_T} \right)} = 0.4997 \text{ mA} = I_{C3}$$

$$\text{Then } I_{E3} = 0.5247 \text{ mA}$$

Now

$$I_{C1} = 100.05 I_{C3} = 50 \text{ mA} = I_{C1}$$

$$I_{C2} = (100) \left(\frac{20}{21} \right) (0.5247) = 49.97 \text{ mA} = I_{C2}$$

$$\text{b. } v_0 = 10 \text{ V} \Rightarrow i_{E1} \approx \frac{10}{100} = 0.10 \text{ A} = i_{C1}$$

$$i_{B1} = \frac{100}{100} = 1 \text{ mA}$$

$$V_{BB} = 2(0.026) \ln \left(\frac{4 \times 10^{-3}}{10^{-13}} \right) = 1.269 \text{ V}$$

$$V_{BE1} = (0.026) \ln \left(\frac{0.1}{10^{-13}} \right) = 0.7184$$

$$V_{EB3} = 1.269 - 0.7184 = 0.5506 \text{ V}$$

$$I_{C3} = 10^{-13} \exp \left(\frac{0.5506}{0.026} \right) = 0.157 \text{ mA}$$

$$\overline{P_L} = \frac{v_0^2}{R_L} = \frac{(10)^2}{100} \Rightarrow \underline{\overline{P_L} = 1 \text{ W}}$$

$$P_{Q1} = i_{C1} \cdot v_{CE1} = (0.1)(12 - 10) \Rightarrow \underline{P_{Q1} = 0.2 \text{ W}}$$

$$\begin{aligned} P_{Q3} &= i_{C3} \cdot v_{EC3} = (0.157)(10 - [0.7 - 12]) \\ &\Rightarrow \underline{P_{Q3} = 3.34 \text{ mW}} \end{aligned}$$

$$i_{C2} = (100)(i_{C3}) = (100)(0.157) = 15.7 \text{ mA}$$

$$\begin{aligned} P_{Q2} &= i_{C2} \cdot v_{CE2} = (15.7)(10 - [-12]) \\ &\Rightarrow \underline{P_{Q2} = 0.345 \text{ W}} \end{aligned}$$

8.37

$$\begin{aligned} \text{a. } V_{BB} &= 3(0.026) \ln \left(\frac{10 \times 10^{-3}}{2 \times 10^{-12}} \right) \\ &\Rightarrow \underline{V_{BB} = 1.74195 \text{ V}} \end{aligned}$$

$$V_{BE1} + V_{BE2} + V_{EB3} = V_{BB}$$

$$I_{C1} \approx \frac{I_{C2}}{\beta_n}, \quad I_{C3} \approx \frac{I_{C2}}{\beta_n^2}$$

$$V_T \ln \left(\frac{I_{C1}}{I_S} \right) + V_T \ln \left(\frac{I_{C2}}{I_S} \right) + V_T \ln \left(\frac{I_{C3}}{I_S} \right) = V_{BB}$$

$$V_T \ln \left[\frac{I_{C2}^3}{\beta_n^3 I_S^3} \right] = V_{BB}$$

$$\begin{aligned} I_{C2} &= \beta_n I_S \sqrt[3]{\exp \left(\frac{V_{BB}}{V_T} \right)} \\ &= (20)(2 \times 10^{-12}) \sqrt[3]{\exp \left(\frac{1.74195}{0.026} \right)} \end{aligned}$$

$$I_{C2} = 0.20 \text{ A}, \quad I_{C1} \approx 10 \text{ mA}, \quad I_{C3} \approx 0.3 \text{ mA}$$

$$\begin{aligned} V_{BE1} &= (0.026) \ln \left(\frac{10 \times 10^{-3}}{2 \times 10^{-12}} \right) \\ &\Rightarrow \underline{V_{BE1} = 0.58065 \text{ V}} \end{aligned}$$

$$V_{BE2} = (0.026) \ln \left(\frac{0.2}{2 \times 10^{-12}} \right)$$

$$\Rightarrow \underline{V_{BE2} = 0.6585 \text{ V}}$$

$$V_{BE3} = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{2 \times 10^{-12}} \right)$$

$$\Rightarrow \underline{V_{BE3} = 0.50276 \text{ V}}$$

$$\text{b. } \overline{P_L} = 10 \text{ W} = \frac{1}{2} \cdot \frac{V_o^2}{R_L} = \frac{1}{2} \cdot \frac{V_o^2}{20}$$

$$\Rightarrow V_o(\text{max}) = 20 \text{ V}$$

For $v_o(\text{max})$:

$$P_L = \frac{v_o^2}{R_L} = \frac{(20)^2}{20} \Rightarrow \underline{P_L = 20 \text{ W}}$$

$$i_o(\text{max}) = -\frac{20}{20} = -1 \text{ A}$$

$$i_{C3} + i_{C4} + i_{E3} = -i_o(\text{max}) = 1 \text{ A}$$

$$i_{C3} + \frac{i_{C3}}{\beta_n} \cdot \left(\frac{1 + \beta_p}{\beta_p} \right) + \frac{i_{C4}}{\beta_n} \cdot \left(\frac{1 + \beta_p}{\beta_p} \right) = 1$$

$$i_{C3} \left[1 + \frac{1}{\beta_n} \cdot \left(\frac{1 + \beta_p}{\beta_p} \right) + \left\{ \frac{1}{\beta_n} \cdot \left(\frac{1 + \beta_p}{\beta_p} \right) \right\}^2 \right] = 1$$

$$i_{C3} \left[1 + \frac{1}{20} \cdot \left(\frac{6}{5} \right) + \left(\frac{1}{20} \cdot \frac{6}{5} \right)^2 \right]$$

$$i_{C3} [1 + 0.06 + 0.0036] = 1 \Rightarrow \underline{i_{C3} = 0.940 \text{ A}}$$

$$\underline{i_{C4} = 0.0564 \text{ A}}$$

$$\underline{i_{E3} = 3.38 \text{ mA}}$$

$$i_{C2} = 2.82 \text{ mA}$$

$$V_{BE3} = (0.026) \ln \left(\frac{2.82 \times 10^{-3}}{2 \times 10^{-12}} \right) = 0.5477 \text{ V}$$

$$V_{BE1} + V_{BE2} = 1.74195 - 0.5477 = 1.1942$$

$$V_T \ln \left(\frac{I_{C2}}{\beta_n I_S} \right) + V_T \ln \left(\frac{I_{C2}}{I_S} \right) = 1.1942$$

$$I_{C2} = \sqrt{\beta_n} \cdot I_S \sqrt{\exp \left(\frac{1.1942}{0.026} \right)}$$

$$= \sqrt{20}(18.83) \text{ mA}$$

$$I_{C2} = 84.2 \text{ mA}$$