

Chapter 5

Exercise Solutions

E5.1

(a) $V_{TN} = 1.2 \text{ V}, V_{GS} = 2 \text{ V}$

$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 2 - 1.2 = 0.8 \text{ V}$

(i) $V_{DS} = 0.4 \Rightarrow$ Nonsaturation

(ii) $V_{DS} = 1 \Rightarrow$ Saturation

(iii) $V_{DS} = 5 \Rightarrow$ Saturation

(b) $V_{TN} = -1.2 \text{ V}, V_{GS} = 2 \text{ V}$

$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 2 - (-1.2) = 3.2 \text{ V}$

(i) $V_{DS} = 0.4 \Rightarrow$ Nonsaturation

(ii) $V_{DS} = 1 \Rightarrow$ Nonsaturation

(iii) $V_{DS} = 5 \Rightarrow$ Saturation

E5.2

(a) $K_n = \frac{W\mu_n C_{ox}}{2L}$

$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}} = 7.67 \times 10^{-8} \text{ F/cm}$

$K_n = \frac{(100)(500)(7.67 \times 10^{-8})}{2(7)} \Rightarrow K_n = 0.274 \text{ mA/V}^2$

(b) $V_{TN} = 1.2 \text{ V}, V_{GS} = 2 \text{ V}$

(i) $V_{DS} = 0.4 \text{ V} \Rightarrow$ Nonsaturation

$I_D = (0.274) \left[2(2 - 1.2)(0.4) - (0.4)^2 \right] \Rightarrow$
 $I_D = 0.132 \text{ mA}$

(ii) $V_{DS} = 1 \text{ V} \Rightarrow$ Saturation

$I_D = (0.274)(2 - 1.2)^2 \Rightarrow I_D = 0.175 \text{ mA}$

(iii) $V_{DS} = 5 \text{ V} \Rightarrow$ Saturation

$I_D = (0.274)(2 - 1.2)^2 \Rightarrow I_D = 0.175 \text{ mA}$

$V_{TN} = -1.2 \text{ V}, V_{GS} = 2 \text{ V}$

(i) $V_{DS} = 0.4 \text{ V} \Rightarrow$ Nonsaturation

$I_D = (0.274) \left[2(2 + 1.2)(0.4) - (0.4)^2 \right] \Rightarrow$
 $I_D = 0.658 \text{ mA}$

(ii) $V_{DS} = 1 \text{ V} \Rightarrow$ Nonsaturation

$I_D = (0.274) \left[2(2 + 1.2)(1) - (1)^2 \right] \Rightarrow I_D = 1.48 \text{ mA}$

(iii) $V_{DS} = 5 \text{ V} \Rightarrow$ Saturation

$I_D = (0.274)(2 + 1.2)^2 \Rightarrow I_D = 2.81 \text{ mA}$

E5.3

$V_{TN} = 1 \text{ V}, V_{GS} = 3 \text{ V}, V_{DS} = 4.5 \text{ V}$

$V_{DS} = 4.5 > V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 3 - 1 = 2 \text{ V}$

Transistor biased in the saturation region

$I_D = K_n(V_{GS} - V_{TN})^2 \Rightarrow 0.8 = K_n(3 - 1)^2 \Rightarrow$

$K_n = 0.2 \text{ mA/V}^2$

(a) $V_{GS} = 2 \text{ V}, V_{DS} = 4.5 \text{ V}$

Saturation region:

$I_D = (0.2)(2 - 1)^2 \Rightarrow I_D = 0.2 \text{ mA}$

(b) $V_{GS} = 3 \text{ V}, V_{DS} = 1 \text{ V}$

Nonsaturation region:

$I_D = (0.2) \left[2(3 - 1)(1) - (1)^2 \right] \Rightarrow I_D = 0.6 \text{ mA}$

E5.4

(a) $V_{TP} = -2 \text{ V}, V_{SG} = 3 \text{ V}$

$V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 3 - 2 = 1 \text{ V}$

(i) $V_{SD} = 0.5 \text{ V} \Rightarrow$ Nonsaturation

(ii) $V_{SD} = 2 \text{ V} \Rightarrow$ Saturation

(iii) $V_{SD} = 5 \text{ V} \Rightarrow$ Saturation

(b) $V_{TP} = 0.5 \text{ V}, V_{SG} = 3 \text{ V}$

$V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 3 + 0.5 = 3.5 \text{ V}$

(i) $V_{SD} = 0.5 \text{ V} \Rightarrow$ Nonsaturation

(ii) $V_{SD} = 2 \text{ V} \Rightarrow$ Nonsaturation

(iii) $V_{SD} = 5 \text{ V} \Rightarrow$ Saturation

E5.5

(a) $\lambda = 0, V_{DS}(\text{sat}) = 2.5 - 0.8 = 1.7 \text{ V}$

For $V_{DS} = 2 \text{ V}, V_{DS} = 10 \text{ V} \Rightarrow$ Saturation Region

$I_D = (0.1)(2.5 - 0.8)^2 \Rightarrow I_D = 0.289 \text{ mA}$

(b) $\lambda = 0.02 \text{ V}^{-1}$

$I_D = K_n(V_{GS} - V_{TN})^2(1 + \lambda V_{DS})$

For $V_{DS} = 2 \text{ V}$

$I_D = (0.1)(2.5 - 0.8)^2 [1 + (0.02)(2)] \Rightarrow$
 $I_D = 0.300 \text{ mA}$

$V_{DS} = 10 \text{ V}$

$I_D = (0.1) \left[(2.5 - 0.8)^2 (1 + (0.02)(10)) \right] \Rightarrow$
 $I_D = 0.347 \text{ mA}$

(c) For part (a), $\lambda = 0 \Rightarrow r_o = \infty$

For part (b), $\lambda = 0.02 \text{ V}^{-1}$,

$r_o = \left[\lambda K_n (V_{GS} - V_{TN})^2 \right]^{-1} = \left[(0.02)(0.1)(2.5 - 0.8)^2 \right]^{-1}$
or $r_o = 173 \text{ k}\Omega$

E5.6

$$V_{TN} = V_{TNO} + \gamma [\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}]$$

$$2\phi_f = 0.70 \text{ V}, \quad V_{TNO} = 1 \text{ V}$$

$$(a) \quad V_{SB} = 0 \Rightarrow V_{TN} = 1 \text{ V}$$

$$(b) \quad V_{SB} = 1 \text{ V},$$

$$V_{TN} = 1 + (0.35) [\sqrt{0.7 + 1} - \sqrt{0.7}] \Rightarrow V_{TN} = 1.16 \text{ V}$$

$$(c) \quad V_{SB} = 4 \text{ V},$$

$$V_{TN} = 1 + (0.35) [\sqrt{0.7 + 4} - \sqrt{0.7}] \Rightarrow V_{TN} = 1.47 \text{ V}$$

E5.7

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5 = \left(\frac{40}{40 + 60} \right) (10) - 5$$

$$V_G = -1 \text{ V}$$

$$V_S = I_D R_S - 5$$

Then

$$V_{GS} = V_G - V_S = -1 - (I_D R_S - 5) = 4 - I_D R_S$$

Assume transistor is biased in saturation region

$$I_D = K_n (V_{GS} - V_{TN})^2 = \frac{4 - V_{GS}}{R_S}$$

$$4 - V_{GS} = (0.5)(0.1)[V_{GS} - 1]^2 \Rightarrow$$

$$0.5V_{GS}^2 - 3.5 = 0 \Rightarrow V_{GS} = 2.65 \text{ V}$$

$$I_D = (0.5)(2.65 - 1)^2 \Rightarrow I_D = 1.36 \text{ mA}$$

$$V_{DS} = 10 - I_D(R_S + R_D) = 10 - (1.36)(1 + 2) \Rightarrow$$

$$V_{DS} = 5.92 \text{ V}$$

$$V_{DS} > V_{DS}(\text{sat}), \text{ Yes}$$

E5.8

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \left(\frac{200}{350} \right) (10) - 5 = 0.714 \text{ V}$$

$$V_S = 5 - I_D R_S = 5 - (1.2)I_D$$

So

$$V_{SG} = V_S - V_G = 5 - (1.2)I_D - 0.714$$

$$= 4.286 - (1.2)I_D$$

$$I_D = \frac{4.286 - V_{SG}}{1.2}$$

$$I_D = K_p (V_{SG} + V_{TP})^2$$

$$4.286 - V_{SG} = (1.2)(0.25) \times$$

$$(V_{SG}^2 - 2V_{SG}(-1) + (-1)^2)$$

$$4.286 - V_{SG} = (0.3)V_{SG}^2 - 0.6V_{SG} + 0.3$$

$$0.3V_{SG}^2 + 0.4V_{SG} - 3.986 = 0$$

$$V_{SG} = \frac{-0.4 \pm \sqrt{(0.4)^2 + 4(0.3)(3.986)}}{2(0.3)}$$

$$\text{Must use + sign} \Rightarrow V_{SG} = 3.04 \text{ V}$$

$$I_D = (0.25)(3.04 - 1)^2 \Rightarrow I_D = 1.04 \text{ mA}$$

$$V_{SD} = 10 - I_D(R_S + R_D) = 10 - (1.04)(1.2 + 4)$$

$$\Rightarrow V_{SD} = 4.59 \text{ V}$$

$$V_{SD} > V_{SD}(\text{sat}), \text{ Yes}$$

E5.9

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$0.4 = 0.25(V_{GS} - 0.8)^2 \Rightarrow V_{GS} = 2.06 \text{ V}$$

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$2.06 = \left(\frac{R_2}{250} \right) (7.5) \Rightarrow R_2 = 68.7 \text{ k}\Omega$$

$$R_1 = 181.3 \text{ k}\Omega$$

$$V_{DS} = 4 = V_{DD} - I_D R_D$$

$$R_D = \frac{7.5 - 4}{0.4} \Rightarrow R_D = 8.75 \text{ k}\Omega$$

$$V_{DS} > V_{DS}(\text{sat}), \text{ Yes}$$

E5.10

$$I_D = \frac{V_S - (-5)}{R_S} \text{ and } V_S = -V_{GS}$$

$$\text{So } R_S = \frac{5 - V_{GS}}{0.1}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$0.1 = (0.080)(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 2.32 \text{ V}$$

$$\text{So } R_S = \frac{5 - 2.32}{0.1} \Rightarrow R_S = 26.8 \text{ k}\Omega$$

$$V_{DS} = V_D - V_S \Rightarrow V_D = V_{DS} + V_S = 4.5 - 2.32$$

$$V_D = 2.18$$

$$R_D = \frac{5 - V_D}{I_D} = \frac{5 - 2.18}{0.1} \Rightarrow R_D = 28.2 \text{ k}\Omega$$

$$V_{DS} > V_{DS}(\text{sat}), \text{ Yes}$$

E5.11

$$I_D = \frac{10 - V_{SG}}{R_S} \text{ and } I_D = K_p (V_{SG} + V_{TP})^2$$

$$0.12 = (0.050)(V_{SG} - 0.8)^2$$

$$V_{SG} = 2.35 \text{ V}$$

$$R_S = \frac{10 - 2.35}{0.12} \Rightarrow R_S = 63.75 \text{ k}\Omega$$

$$V_{SD} = 8 = 20 - I_D(R_S + R_D)$$

$$8 = 20 - (0.12)(63.75) - (0.12)R_D$$

$$R_D = \frac{20 - (0.12)(63.75) - 8}{0.12}$$

$$\Rightarrow R_D = 36.25 \text{ k}\Omega$$

E5.12

$$I_D = \frac{V_{DD} - V_{GS}}{R_S}, \quad I_D = K_n(V_{GS} - V_{TN})^2$$

$$10 - V_{GS} = (10)(0.2)(V_{GS}^2 - 2V_{GS}V_{TN} + V_{TN}^2)$$

$$10 - V_{GS} = 2V_{GS}^2 - 8V_{GS} + 8$$

$$2V_{GS}^2 - 7V_{GS} - 2 = 0$$

$$V_{GS} = \frac{7 \pm \sqrt{(7)^2 + 4(2)(2)}}{2(2)}$$

Use + sign: $V_{GS} = V_{DS} = 3.77 \text{ V}$

$$I_D = \frac{10 - 3.77}{10} \Rightarrow I_D = 0.623 \text{ mA}$$

$$\text{Power} = I_D V_{DS} = (0.623)(3.77)$$

$$\Rightarrow \text{Power} = 2.35 \text{ mW}$$

E5.13

For $V_{DS} = 2.2 \text{ V}$

$$I_D = \frac{5 - 2.2}{5} \Rightarrow I_D = 0.56 \text{ mA}$$

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$0.56 = K_n(2.2 - 1)^2$$

$$K_n = 0.389 \text{ mA/V} = \frac{W}{L} \cdot \frac{\mu_n C_{ox}}{2}$$

$$\frac{W}{L} = \frac{(389)(2)}{(40)} \Rightarrow \frac{W}{L} = 19.5$$

E5.14

(a) The transition point is

$$V_h = \frac{V_{DD} - V_{TNL} + V_{TND}(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$= \frac{5 - 1 + 1(1 + \sqrt{0.05/0.01})}{1 + \sqrt{0.05/0.01}}$$

$$= \frac{7.236}{3.236} \Rightarrow V_{It} = 2.24 \text{ V}$$

$$V_{Ox} = V_h - V_{TND} = 2.24 - 1 \Rightarrow V_{Ox} = 1.24 \text{ V}$$

(b) We may write

$$I_D = K_{nD}(V_{GSD} - V_{TND})^2 = (0.05)(2.24 - 1)^2$$

$$\Rightarrow I_D = 76.9 \mu\text{A}$$

E5.15

$$V_h = \frac{V_{DD} - V_{TNL} + V_{TND}(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$2.5 = \frac{5 - 1 + 1(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$2.5 + 2.5\sqrt{K_{nD}/K_{nL}} = 5 + \sqrt{K_{nD}/K_{nL}} \Rightarrow$$

$$\sqrt{K_{nD}/K_{nL}} = \frac{5 - 2.5}{1.5} = 1.67 \Rightarrow$$

$$K_{nD}/K_{nL} = 2.78$$

b. For $V_i = 5$, driver in nonsaturated region.

$$I_{DD} = I_{DL}$$

$$K_{nD}[2(V_i - V_{TND})V_{Ox} - V_{Ox}^2] = K_{nL}(V_{GSL} - V_{TNL})^2$$

$$\frac{K_{nD}}{K_{nL}}[2(V_i - V_{TND})V_{Ox} - V_{Ox}^2] = [V_{DD} - V_{Ox} - V_{TNL}]^2$$

$$2.78[2(5 - 1)V_{Ox} - V_{Ox}^2] = [5 - V_{Ox} - 1]^2$$

$$22.24V_{Ox} - 2.78V_{Ox}^2 = (4 - V_{Ox})^2$$

$$= 16 - 8V_{Ox} + V_{Ox}^2$$

$$3.78V_{Ox}^2 - 30.24V_{Ox} + 16 = 0$$

$$V_{Ox} = \frac{30.24 \pm \sqrt{(30.24)^2 - 4(3.78)(16)}}{2(3.78)}$$

$$\Rightarrow V_{Ox} = 0.57 \text{ V}$$

E5.16

If the transistor is biased in the saturation region

$$I_D = K_n(V_{GS} - V_{TN})^2 = K_n(-V_{TN})^2$$

$$I_D = (0.25)(2.5)^2 \Rightarrow I_D = 1.56 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_S = 10 - (1.56)(4)$$

$$\Rightarrow V_{DS} = 3.76$$

$$V_{DS} > V_{GS} - V_{TN} = -V_{TN}$$

$$3.76 > -(-2.5)$$

Yes — biased in the saturation region

$$\text{Power} = I_D V_{DS} = (1.56)(3.76)$$

$$\Rightarrow \text{Power} = 5.87 \text{ mW}$$

E5.17

We have $V_{DS} = 1.2 \text{ V} < V_{GS} - V_{TN} = -V_{TN} = 1.8 \text{ V}$
Transistor is biased in the nonsaturation region.

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

and

$$I_D = \frac{V_{DD} - V_{DS}}{R_S} = \frac{5 - 1.2}{8} \Rightarrow$$

$$I_D = 0.475 \text{ mA}$$

$$0.475 = K_n[2(0 - (-1.8))(1.2) - (1.2)^2]$$

$$0.475 = K_n(2.88) \Rightarrow K_n = 0.165 \text{ mA/V}^2$$

$$K_n = \frac{W}{L} \cdot \frac{\mu_n C_{ox}}{2}$$

$$\frac{W}{L} = \frac{(165)(2)}{35} \Rightarrow \frac{W}{L} = 9.43$$

E5.18

- (a) Transition point for the load transistor – Driver is in the saturation region.

$$I_{DD} = I_{DL}$$

$$K_{nD}(V_{GS} - V_{TND})^2 = K_{nL}(V_{GS} - V_{TNL})^2$$

$$V_{DSL}(sat) = V_{GSL} - V_{TNL} = -V_{TNL}$$

$$\Rightarrow V_{DSL} = V_{DD} - V_{OL} = 2V$$

$$\text{Then } V_{OL} = 5 - 2 = 3V, \quad V_{OL} = 3V$$

$$\sqrt{\frac{K_{nD}}{K_{nL}}}(V_H - 1) = (-V_{TNL})$$

$$\sqrt{\frac{0.08}{0.01}}(V_H - 1) = 2 \Rightarrow V_H = 1.89V$$

- (b) For the driver:

$$V_{OL} = V_H - V_{TND}$$

$$V_H = 1.89V, \quad V_{OL} = 0.89V$$

E5.19

- (a) For $V_i = 5V$, Load in saturation and driver in nonsaturation.

$$I_{DD} = I_{DL}$$

$$K_{nD}[2(V_i - V_{TND})V_{OL} - V_{OL}^2] = K_{nL}(-V_{TNL})^2$$

$$\frac{K_{nD}}{K_{nL}}[2(5-1)(0.25) - (0.25)^2] = 4 \Rightarrow$$

$$\frac{K_{nD}}{K_{nL}} = 2.06$$

$$(b) I_{DL} = K_{nL}(-V_{TNL})^2 \Rightarrow 0.2 = K_{nL}[-(-2)]^2$$

$$K_{nL} = 50 \mu A/V^2 \text{ and } K_{nD} = 103 \mu A/V^2$$

E5.20

$$(a) I_{REF} = K_{n3}(V_{GS1} - V_{TN})^2 = K_{n4}(V_{GS4} - V_{TN})^2$$

$$V_{GS3} = 2V \Rightarrow V_{GS4} = 3V$$

$$(2-1)^2 = \frac{K_{n4}}{K_{n3}}(3-1)^2 \Rightarrow \frac{K_{n4}}{K_{n3}} = \frac{1}{4}$$

$$(b) I_Q = K_{n2}(V_{GS2} - V_{TN})^2$$

$$\text{But } V_{GS1} = V_{GS3} = 2V$$

$$0.1 = K_{n2}(2-1)^2 \Rightarrow K_{n2} = 0.1 \text{ mA/V}^2$$

$$(c) 0.2 = K_{n3}(2-1)^2 \Rightarrow K_{n3} = 0.2 \text{ mA/V}^2$$

$$0.2 = K_{n4}(3-1)^2 \Rightarrow K_{n4} = 0.05 \text{ mA/V}^2$$

E5.21

For $R_D = 10 \text{ k}\Omega$, $V_{DD} = 5V$, and $V_o = 1V$

$$I_D = \frac{5-1}{10} = 0.4 \text{ mA}$$

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_D = 0.4 = K_n[2(5-1)(1) - (1)^2] \Rightarrow$$

$$K_n = 0.057 \text{ mA/V}^2$$

$$P = I_D \cdot V_{DS} = (0.4)(1) \Rightarrow P = 0.4 \text{ mW}$$

E5.22

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$= (0.050)[2(10 - 0.7)(0.35) - (0.35)^2]$$

$$I_D = 0.319 \text{ mA}$$

$$R_D = \frac{V_{DD} - V_o}{I_D} = \frac{10 - 0.35}{0.319}$$

$$\Rightarrow R_D = 30.3 \text{ k}\Omega$$

E5.23

- (a) Transistor biased in the nonsaturation region

$$I_D = \frac{5 - 1.5 - V_{DS}}{R} = 12$$

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$12 = 4[2(5 - 0.8)V_{DS} - V_{DS}^2]$$

$$4V_{DS}^2 - 33.6V_{DS} + 12 = 0 \Rightarrow V_{DS} = 0.374V$$

Then

$$R = \frac{5 - 1.5 - 0.374}{12} \Rightarrow R = 261 \Omega$$

E5.24

- a. $V_1 = 5V$, $V_2 = 0$, M_2 cutoff $\Rightarrow I_{D2} = 0$

$$I_D = K_n[2(V_i - V_{TN})V_o - V_o^2] = \frac{5 - V_o}{R_D}$$

$$(0.05)(30)[2(5-1)V_o - V_o^2] = 5 - V_o$$

$$1.5V_o^2 - 13V_o + 5 = 0$$

$$V_o = \frac{13 \pm \sqrt{(13)^2 - 4(1.5)(5)}}{2(1.5)} \Rightarrow V_o = 0.40V$$

$$I_R = I_{D1} = \frac{5 - 0.40}{30} \Rightarrow I_R = I_{D1} = 0.153 \text{ mA}$$

- b. $V_1 = V_2 = 5V$

$$\frac{5 - V_o}{R_D} = 2\{K_n[2(V_i - V_{TN})V_o - V_o^2]\}$$

$$5 - V_o = 2(0.05)(30)[2(5-1)V_o - V_o^2]$$

$$3V_o^2 - 25V_o + 5 = 0$$

$$V_0 = \frac{25 \pm \sqrt{(25)^2 - 4(3)(5)}}{2(3)} \Rightarrow V_0 = 0.205 \text{ V}$$

$$I_R = \frac{5 - 0.205}{30} \Rightarrow I_R = 0.160 \text{ mA}$$

$$I_{D1} = I_{D2} = 0.080 \text{ mA}$$

E5.25

$$(a) I_D = \frac{5 - V_0}{R_D} = K_n [2(V_2 - V_{TN})V_0 - V_0^2]$$

$$\frac{5 - (0.10)}{25} = K_n [2(5 - 1)(0.10) - (0.10)^2] \Rightarrow$$

$$K_n = 0.248 \text{ mA/V}^2$$

$$b. \quad \frac{5 - V_0}{25} = 2(0.248)[2(5 - 1)V_0 - V_0^2]$$

$$5 - V_0 = 12.4[8V_0 - V_0^2]$$

$$12.4V_0^2 - 100.2V_0 + 5 = 0$$

$$V_0 = \frac{100.2 \pm \sqrt{(100.2)^2 - 4(12.4)(5)}}{2(12.4)}$$

$$\Rightarrow V_0 = 0.0502 \text{ V}$$

E5.26

$$V_{DS}(\text{sat}) = V_{GS} - V_P = -1.2 - (-4.5)$$

$$\Rightarrow V_{DS}(\text{sat}) = 3.3 \text{ V}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 12 \left(1 - \frac{(-1.2)}{(-4.5)}\right)^2$$

$$\Rightarrow I_D = 6.45 \text{ mA}$$

E5.27

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$1.2 = 2 \left(1 - \frac{V_{GS}}{(-2.5)}\right)^2 \Rightarrow V_{GS} = -0.564 \text{ V}$$

E5.28

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$3 = I_{DSS} \left(1 - \frac{0.8}{3.8}\right)^2 \Rightarrow I_{DSS} = 4.31 \text{ mA}$$

$$V_{SD}(\text{sat}) = V_P - V_{GS} = 3.8 - 0.8$$

$$V_{SD}(\text{sat}) = 3.0 \text{ V}$$

E5.29

$$I_D = K(V_{GS} - V_{TN})^2$$

$$a. \quad V_{GS} = 0.35 \Rightarrow I_D = 25(0.35 - 0.25)^2$$

$$\Rightarrow I_D = 0.25 \mu\text{A}$$

$$b. \quad V_{GS} = 0.50 \Rightarrow I_D = 25(0.50 - 0.25)^2$$

$$\Rightarrow I_D = 1.56 \mu\text{A}$$

E5.30

Assume the transistor is biased in the saturation region.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$8 = 18 \left(1 - \frac{V_{GS}}{(-3.5)}\right)^2 \Rightarrow V_{GS} = -1.17 \text{ V}$$

$$\Rightarrow V_S = -V_{GS} = 1.17$$

$$V_D = 15 - (8)(0.8) = 8.6$$

$$V_{DS} = 8.6 - (1.17) = 7.43 \text{ V}$$

$$V_{DS} = 7.43 > V_{GS} - V_P = -1.17 - (-3.5) = 2.33$$

Yes, the transistor is biased in the saturation region.

E5.31

$$I_D = 2.5 \text{ mA}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2.5 = 6 \left(1 - \frac{V_{GS}}{(-4)}\right)^2 \Rightarrow V_{GS} = -1.42 \text{ V}$$

$$V_S = I_D R_S - 5 = (2.5)(0.25) - 5$$

$$V_S = -4.375$$

$$V_{DS} = 6 \Rightarrow V_D = 6 - 4.375 = 1.625$$

$$R_D = \frac{5 - 1.625}{2.5} \Rightarrow R_D = 1.35 \text{ k}\Omega$$

$$\frac{(20)^2}{R_1 + R_2} = 2 \Rightarrow R_1 + R_2 = 200 \text{ k}\Omega$$

$$V_G = V_{GS} + V_S = -1.42 - 4.375 = -5.795$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)(20) - 10$$

$$-5.795 = \left(\frac{R_2}{200}\right)(20) - 10 \Rightarrow$$

$$R_2 = 42.05 \text{ k}\Omega \rightarrow 42 \text{ k}\Omega$$

$$R_1 = 157.95 \text{ k}\Omega \rightarrow 158 \text{ k}\Omega$$

E5.32

$$\begin{aligned}
 V_S &= -V_{GS}, \quad I_D = \frac{0 - V_S}{R_S} = \frac{V_{GS}}{R_S} \\
 I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\
 \frac{V_{GS}}{1} &= 6 \left(1 - \frac{V_{GS}}{4} \right)^2 = 6 \left(1 - \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right) \\
 0.375 V_{GS}^2 - 4 V_{GS} + 6 &= 0 \\
 V_{GS} &= \frac{4 \pm \sqrt{16 - 4(0.375)(6)}}{2(0.375)} \\
 \underline{V_{GS} = 8.86} \text{ or } \underline{V_{GS} = 1.81 \text{ V}} \\
 \text{impossible} \\
 I_D &= \frac{V_{GS}}{R_S} = 1.81 \text{ mA} \\
 V_D &= I_D R_D - 5 = (1.81)(0.4) - 5 = -4.276 \\
 V_{SD} &= V_S - V_D = -1.81 - (-4.276) \\
 \Rightarrow \underline{V_{SD} = 2.47 \text{ V}} \\
 V_{SD}(\text{sat}) &= V_P - V_{GS} = 4 - 1.81 = 2.19 \\
 \text{So } V_{SD} &> V_{SD}(\text{sat})
 \end{aligned}$$

E5.33

$$\begin{aligned}
 R_{in} &= R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 100 \text{ k}\Omega \\
 I_{DQ} &= 5 \text{ mA}, \quad V_S = -I_{DQ} R_S = -(5)(1.2) = -6 \text{ V} \\
 V_{SDQ} &= 12 \text{ V} \Rightarrow V_D = V_S - V_{SDQ} \\
 &= -6 - 12 = -18 \text{ V} \\
 R_D &= \frac{-18 - (-20)}{5} \Rightarrow \underline{R_D = 0.4 \text{ k}\Omega} \\
 I_{DQ} &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \Rightarrow 5 = 8 \left(1 - \frac{V_{GS}}{4} \right)^2 \\
 V_{GS} &= 0.838 \text{ V} \\
 V_G &= V_{GS} + V_S = 0.838 - 6 = -5.162 \\
 V_G &= \left(\frac{R_2}{R_1 + R_2} \right) (-20) \\
 -5.162 &= \frac{1}{R_1} (100)(-20) \Rightarrow \underline{R_1 = 387 \text{ k}\Omega} \\
 \frac{R_1 R_2}{R_1 + R_2} &= 100 \Rightarrow (387) R_2 = 100(387) + 100 R_2 \\
 (387 - 100) R_2 &= (100)(387) \\
 \Rightarrow \underline{R_2 = 135 \text{ k}\Omega}
 \end{aligned}$$

E5.34

$$\begin{aligned}
 I_{DQ} &= K(V_{GS} - V_{TN})^2 \Rightarrow 5 = 50(V_{GS} - 0.15)^2 \\
 \Rightarrow \underline{V_{GS} = 0.466 \text{ V}} \\
 V_S &= (0.005)(10) = 0.050 \text{ V} \\
 \Rightarrow V_{GG} &= V_{GS} + V_S = 0.466 + 0.050 \\
 \Rightarrow \underline{V_{GG} = 0.516 \text{ V}} \\
 V_D &= 5 - (0.005)(100) \Rightarrow V_D = 4.5 \text{ V} \\
 V_{DS} &= V_D - V_S = 4.5 - 0.050 \\
 \Rightarrow \underline{V_{DS} = 4.45 \text{ V}}
 \end{aligned}$$

E5.35

$$\begin{aligned}
 I_D &= K[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \\
 &= 100[2(0.7 - 0.2)(0.1) - (0.1)^2] \\
 I_D &= 9 \mu\text{A} \\
 R_D &= \frac{2.5 - 0.1}{0.009} \Rightarrow \underline{R_D = 267 \text{ k}\Omega}
 \end{aligned}$$

Chapter 5

Problem Solutions

5.1

$$(a) V_{DS} = 6V > V_{GS} - V_{TN} = 5 - 1.5 = 3.5V$$

Biased in the saturation region

$$I_D = K_n (V_{GS} - V_{TN})^2 = (0.25)(5 - 1.5)^2 \Rightarrow$$

$$I_D = 3.06 \text{ mA}$$

$$(b) V_{DS} = 2.5V < V_{DS}(\text{sat}) = 3.5V$$

Biased in nonsaturation region

$$I_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_D = (0.25)[2(5 - 1.5)(2.5) - (2.5)^2] \Rightarrow$$

$$I_D = 2.81 \text{ mA}$$

5.2

$$(a) I_D = \frac{k'_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$0.5 = \left(\frac{0.080}{2} \right) (5)(V_{GS} - 0.8)^2$$

$$\sqrt{\frac{0.5}{0.2}} + 0.8 = V_{GS} \Rightarrow V_{GS} = 2.38V$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 2.38 - 0.8 \Rightarrow$$

$$V_{DS}(\text{sat}) = 1.58V$$

$$(b) 1.5 = \left(\frac{0.080}{2} \right) (5)(V_{GS} - 0.8)^2$$

$$\sqrt{\frac{1.5}{0.2}} + 0.8 = V_{GS} \Rightarrow V_{GS} = 3.54V$$

$$V_{DS}(\text{sat}) = 3.54 - 0.8 \Rightarrow V_{DS}(\text{sat}) = 2.74V$$

5.3

$$a. V_{GS} = 0$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 0 - (-2.5) = 2.5V$$

$$i. V_{DS} = 0.5V \Rightarrow \text{Biased in nonsaturation}$$

$$I_D = (1.1)[2(0 - (-2.5))(0.5) - (0.5)^2]$$

$$\Rightarrow I_D = 2.48 \text{ mA}$$

$$ii. V_{DS} = 2.5V \Rightarrow \text{Biased in saturation}$$

$$I_D = (1.1)(0 - (-2.5))^2$$

$$\Rightarrow I_D = 6.88 \text{ mA}$$

$$iii. V_{DS} = 5V \text{ Same as (ii)} \Rightarrow I_D = 6.88 \text{ mA}$$

$$b. V_{GS} = 2V$$

$$V_{DS}(\text{sat}) = 2 - (-2.5) = 4.5V$$

$$i. V_{DS} = 0.5V \Rightarrow \text{Nonsaturation}$$

$$I_D = (1.1)[2(2 - (-2.5))(0.5) - (0.5)^2]$$

$$\Rightarrow I_D = 4.68 \text{ mA}$$

$$ii. V_{DS} = 2.5V \Rightarrow \text{Nonsaturation}$$

$$I_D = (1.1)[2(2 - (-2.5))(2.5) - (2.5)^2]$$

$$\Rightarrow I_D = 17.9 \text{ mA}$$

$$iii. V_{DS} = 5V \Rightarrow \text{Saturation}$$

$$I_D = (1.1)(2 - (-2.5))^2$$

$$\Rightarrow I_D = 22.3 \text{ mA}$$

5.4

$$V_{DS} > V_{GS} - V_{TN} = 0 - (-2) = 2V$$

Biased in the saturation region

$$I_D = \frac{k'_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$1.5 = \left(\frac{0.080}{2} \right) \left(\frac{W}{L} \right) [0 - (-2)]^2 \Rightarrow \frac{W}{L} = 9.375$$

5.5

$$a. C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}}$$

$$\Rightarrow \frac{\epsilon_{ox}}{t_{ox}} = 7.67 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} = \frac{1}{2} (650)(7.67 \times 10^{-8}) \left(\frac{64}{4} \right)$$

$$K_n = 0.399 \text{ mA/V}^2$$

$$b. V_{GS} = V_{DS} = 3V \Rightarrow \text{Saturation}$$

$$I_D = K_n (V_{GS} - V_{TN})^2 = (0.399)(3 - 0.8)^2$$

$$\Rightarrow I_D = 1.93 \text{ mA}$$

5.6

$$a. C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{600 \times 10^{-8}}$$

$$\Rightarrow \frac{\epsilon_{ox}}{t_{ox}} = 5.75 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} = \frac{1}{2} (500)(5.75 \times 10^{-8}) \left(\frac{100}{5} \right) \Rightarrow$$

$$K_n = 0.288 \text{ mA/V}^2$$

b. i. $V_{GS} = 0$, $V_{DS} = 5$ V

$$V_{DS}(\text{sat}) = 0 - (-2) = 2$$
 V

Biased in saturation

$$I_D = (0.288)(0 - (-2))^2 \Rightarrow \underline{I_D = 1.15 \text{ mA}}$$

ii. $V_{GS} = 2$ V, $V_{DS} = 1$ V

$$V_{DS}(\text{sat}) = 2 - (-2) = 4$$
 V

Nonsaturation

$$I_D = (0.288)[2(2 - (-2))(1) - (1)^2]$$

$$\Rightarrow \underline{I_D = 2.02 \text{ mA}}$$

5.7

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{400 \times 10^{-8}} \\ = 8.63 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \\ = \frac{1}{2}(600)(8.63 \times 10^{-8}) \left(\frac{W}{2.5} \right)$$

$$K_n = (1.04 \times 10^{-5})W$$

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$1.2 \times 10^{-3} = (1.04 \times 10^{-5})W(5 - 1)^2$$

$$\Rightarrow \underline{W = 7.21 \text{ } \mu\text{m}}$$

5.8

Biased in the saturation region in both cases.

$$I_D = \frac{k'_p}{2} \cdot \frac{W}{L} (V_{SG} + V_{TP})^2$$

$$(1) 0.225 = \left(\frac{0.040}{2} \right) \left(\frac{W}{L} \right) (3 + V_{TP})^2$$

$$(2) 1.40 = \left(\frac{0.040}{2} \right) \left(\frac{W}{L} \right) (4 + V_{TP})^2$$

Take ratio of (2) to (1):

$$\frac{1.40}{0.225} = 6.222 = \frac{(4 + V_{TP})^2}{(3 + V_{TP})^2}$$

$$\sqrt{6.222} = 2.49 = \frac{4 + V_{TP}}{3 + V_{TP}} \Rightarrow \underline{V_{TP} = -2.33 \text{ V}}$$

Then

$$0.225 = \left(\frac{0.040}{2} \right) \left(\frac{W}{L} \right) (3 - 2.33)^2 \Rightarrow \underline{\frac{W}{L} = 25.1}$$

5.9

$$V_S = 5 \text{ V}, V_G = 0 \Rightarrow V_{SG} = 5 \text{ V}$$

$$V_{TP} = -0.5 \text{ V}$$

$$\Rightarrow V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 5 - 0.5 = 4.5 \text{ V}$$

a. $V_D = 0 \Rightarrow V_{SD} = 5 \text{ V}$

\Rightarrow Biased in saturation

$$I_D = 2(5 - 0.5)^2 \Rightarrow \underline{I_D = 40.5 \text{ mA}}$$

b. $V_D = 2 \text{ V} \Rightarrow V_{SD} = 3 \text{ V}$

\Rightarrow Nonsaturation

$$I_D = 2[2(5 - 0.5)(3) - (3)^2]$$

$$\Rightarrow \underline{I_D = 36 \text{ mA}}$$

c. $V_D = 4 \text{ V} \Rightarrow V_{SD} = 1 \text{ V}$

\Rightarrow Nonsaturation

$$I_D = 2[2(5 - 0.5)(1) - (1)^2]$$

$$\Rightarrow \underline{I_D = 16 \text{ mA}}$$

d. $V_D = 5 \text{ V} \Rightarrow V_{SD} = 0 \Rightarrow \underline{I_D = 0}$

5.10

$$V_{SD}(\text{sat}) = V_{SG} + V_{TP}$$

(a) $V_{SD}(\text{sat}) = -1 + 2 \Rightarrow V_{SD}(\text{sat}) = 1 \text{ V}$

(b) $V_{SD}(\text{sat}) = 0 + 2 \Rightarrow V_{SD}(\text{sat}) = 2 \text{ V}$

(c) $V_{SD}(\text{sat}) = 1 + 2 \Rightarrow V_{SD}(\text{sat}) = 3 \text{ V}$

$$I_D = \frac{k'_p}{2} \cdot \frac{W}{L} (V_{SG} + V_{TP})^2 = \frac{k'_p}{2} \cdot \frac{W}{L} [V_{SD}(\text{sat})]^2$$

(a) $I_D = \left(\frac{0.040}{2} \right) (6)(1)^2 \Rightarrow \underline{I_D = 0.12 \text{ mA}}$

(b) $I_D = \left(\frac{0.040}{2} \right) (6)(2)^2 \Rightarrow \underline{I_D = 0.48 \text{ mA}}$

(c) $I_D = \left(\frac{0.040}{2} \right) (6)(3)^2 \Rightarrow \underline{I_D = 1.08 \text{ mA}}$

5.11

$$V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 0 + 2 = 2 \text{ V}$$

(a) $V_{SD} = 1 \text{ V}$, Nonsaturation

$$I_D = K_p [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2]$$

$$I_D = (0.5)[2(0 + 2)(1) - (1)^2] \Rightarrow \underline{I_D = 1.5 \text{ mA}}$$

(b) $V_{SD} = 2 \text{ V}$, Saturation

$$I_D = K_p (V_{SG} + V_{TP})^2 = (0.5)(0 + 2)^2 \Rightarrow$$

$$\underline{I_D = 2 \text{ mA}}$$

(c) $V_{SD} = 3 \text{ V}$, Saturation

$$\text{Same as (b), } \underline{I_D = 2 \text{ mA}}$$

5.12

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{500 \times 10^{-8}} \\ = 6.90 \times 10^{-6} \text{ F/cm}^2$$

$$k'_n = (\mu_n C_{ox}) = (675)(6.90 \times 10^{-6}) \\ \Rightarrow 46.6 \mu\text{A/V}^2$$

$$k'_p = (\mu_p C_{ox}) = (375)(6.90 \times 10^{-6}) \\ \Rightarrow 25.9 \mu\text{A/V}^2$$

PMOS:

$$I_D = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p (V_{SG} + V_{TP})^2$$

$$0.8 = \left(\frac{0.0259}{2} \right) \left(\frac{W}{L} \right)_p (3 - 0.6)^2$$

$$\Rightarrow \left(\frac{W}{L} \right)_p = 3.19$$

$$L = 4 \mu\text{m} \Rightarrow \underline{W_p = 12.8 \mu\text{m}}$$

$$K_p = \left(\frac{0.0259}{2} \right) (3.19) \Rightarrow \underline{K_p = 41.3 \mu\text{A/V}^2 = K_n}$$

Want $K_n = K_p$

$$\frac{k'_n}{2} \left(\frac{W}{L} \right)_n = \frac{k'_p}{2} \left(\frac{W}{L} \right)_p = 41.3$$

$$\left(\frac{46.6}{2} \right) \left(\frac{W}{L} \right)_n = 41.3 \Rightarrow \left(\frac{W}{L} \right)_n = 1.77$$

$$L = 4 \mu\text{m} \Rightarrow \underline{W_n = 7.08 \mu\text{m}}$$

5.13

$$V_{GS} = 2 \text{ V}, I_D = (0.2)(2 - 1.2)^2 = 0.128 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.128)} \Rightarrow \underline{r_o = 781 \text{ k}\Omega}$$

$$V_{GS} = 4 \text{ V}, I_D = (0.2)(4 - 1.2)^2 = 1.57 \text{ mA}$$

$$r_o = \frac{1}{(0.01)(1.57)} \Rightarrow \underline{r_o = 63.7 \text{ k}\Omega}$$

$$V_A = \frac{1}{\lambda} = \frac{1}{(0.01)} \Rightarrow \underline{V_A = 100 \text{ V}}$$

5.14

$$I_D = \left(\frac{0.080}{2} \right) (4)(3 - 0.8)^2 = (0.16)(3 - 0.8)^2 \Rightarrow$$

$$\underline{I_D = 0.774 \text{ mA}}$$

$$r_o = \frac{1}{\lambda I_D} \Rightarrow \lambda = \frac{1}{r_o I_D} = \frac{1}{(200)(0.774)} \Rightarrow$$

$$\underline{\lambda(\text{max}) = 0.00646 \text{ V}^{-1}}$$

$$V_A(\text{min}) = \frac{1}{\lambda(\text{max})} = \frac{1}{0.00646} \Rightarrow \underline{V_A(\text{min}) = 155 \text{ V}}$$

5.15

$$V_{TN} = V_{TNO} + \gamma \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$\Delta V_{TN} = 2 = (0.8) \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2(0.35)} \right]$$

$$2.5 + 0.837 = \sqrt{2(0.35) + V_{SB}} \Rightarrow \underline{V_{SB} = 10.4 \text{ V}}$$

5.16

$$\Delta V_{TN} = \gamma \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$1.2 = \gamma \left[\sqrt{2(0.37) + 10} - \sqrt{2(0.37)} \right] = \gamma(2.42)$$

$$\text{Then } \gamma = 0.496 \text{ V}^{1/2}$$

5.17

$$\text{a. } V_G = \epsilon_{ox} t_{ox} = (6 \times 10^6)(275 \times 10^{-8})$$

$$\underline{V_G = 16.5 \text{ V}}$$

$$\text{b. } V_G = \frac{16.5}{3} \Rightarrow \underline{V_G = 5.5 \text{ V}}$$

5.18

$$\text{Want } V_G = (3)(24) = \epsilon_{ox} t_{ox} = (6 \times 10^6) t_{ox}$$

$$\underline{t_{ox} = 1.2 \times 10^{-5} \text{ cm} = 1200 \text{ Angstroms}}$$

5.19

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{18}{18 + 32} \right) (10) = 3.6 \text{ V}$$

Assume transistor biased in saturation region

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$3.6 - V_{GS} = (0.5)(2)(V_{GS} - 0.8)^2 \\ = V_{GS}^2 - 1.6V_{GS} + 0.64$$

$$V_{GS}^2 - 0.6V_{GS} - 2.96 = 0$$

$$V_{GS} = \frac{0.6 \pm \sqrt{(0.6)^2 + 4(2.96)}}{2}$$

$$\Rightarrow \underline{V_{GS} = 2.05 \text{ V}}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{3.6 - 2.05}{2} \Rightarrow \underline{I_D = 0.775 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 10 - (0.775)(4 + 2)$$

$$\Rightarrow \underline{V_{DS} = 5.35 \text{ V}}$$

$$\underline{V_{DS} > V_{DS}(\text{sat})}$$

5.20

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left(\frac{6}{14 + 6} \right) (20) - 10 \Rightarrow$$

$$V_G = -4 \text{ V}$$

Assume transistor is biased in saturation region

$$I_D = \frac{V_S - (-10)}{R_S} = \frac{V_G - V_{GS} + 10}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$K_n = \left(\frac{0.060}{2} \right) (60) \Rightarrow 1.8 \text{ mA/V}^2$$

$$\begin{aligned} -4 - V_{GS} + 10 &= (1.8)(0.5)(V_{GS} - 2)^2 \\ &= 0.9V_{GS}^2 - 3.6V_{GS} + 3.6 \end{aligned}$$

$$\text{Then } 0.9V_{GS}^2 - 2.6V_{GS} - 2.4 = 0$$

$$V_{GS} = \frac{2.6 \pm \sqrt{(2.6)^2 + 4(0.9)(2.4)}}{2(0.9)} \Rightarrow \underline{V_{GS} = 3.62 \text{ V}}$$

$$I_D = \frac{V_G - V_{GS} + 10}{R_S} = \frac{-4 - 3.62 + 10}{0.5} \Rightarrow$$

$$\underline{I_D = 4.76 \text{ mA}}$$

$$V_{DS} = 20 - I_D(R_D + R_S) = 20 - (4.76)(1.2 + 0.5) \Rightarrow$$

$$\underline{V_{DS} = 11.9 \text{ V}}$$

$$V_{DS} = 11.9 \text{ V} > V_{GS} - V_{TN} = 3.62 - 2 = 1.62 \text{ V}$$

5.21

$$I_D = \frac{10 - V_S}{R_S} = K_p (V_{SG} + V_{TP})^2$$

Assume transistor biased in saturation region

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (20) - 10$$

$$= \left(\frac{22}{8 + 22} \right) (20) - 10$$

$$\Rightarrow \underline{V_G = 4.67 \text{ V}}$$

$$V_S = V_G + V_{SG}$$

$$10 - (4.67 + V_{SG}) = (1)(0.5)(V_{SG} - 2)^2$$

$$5.33 - V_{SG} = 0.5(V_{SG}^2 - 4V_{SG} + 4)$$

$$0.5V_{SG}^2 - V_{SG} - 3.33 = 0$$

$$V_{SG} = \frac{1 \pm \sqrt{(1)^2 + 4(0.5)(3.33)}}{2(0.5)}$$

$$\Rightarrow \underline{V_{SG} = 3.77 \text{ V}}$$

$$I_D = \frac{10 - (4.67 + 3.77)}{0.5} \Rightarrow \underline{I_D = 3.12 \text{ mA}}$$

$$V_{SD} = 20 - I_D(R_S + R_D)$$

$$= 20 - (3.12)(0.5 + 2)$$

$$\Rightarrow \underline{V_{SD} = 12.2 \text{ V}}$$

$$\underline{V_{SD} > V_{SD}(\text{sat})}$$

5.22

$$V_G = 0, \quad V_{SG} = V_S$$

Assume saturation region

$$I_D = 0.4 = K_p (V_{SG} + V_{TP})^2$$

$$0.4 = (0.2)(V_S - 0.8)^2$$

$$V_S = \sqrt{\frac{0.4}{0.2}} + 0.8 \Rightarrow \underline{V_S = 2.21 \text{ V}}$$

$$V_D = I_D R_D - 5 = (0.4)(5) - 5 = -3 \text{ V}$$

$$V_{SD} = V_S - V_D = 2.21 - (-3)$$

$$\Rightarrow \underline{V_{SD} = 5.21 \text{ V}}$$

$$\underline{V_{SD} > V_{SD}(\text{sat})}$$

5.23

$$V_{DD} = I_{DQ} R_D + V_{DSQ} + I_{DQ} R_S$$

$$(1) \quad 10 = I_{DQ}(5) + 5 + V_{GS} \quad \text{and}$$

$$I_{DQ} = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

$$\text{or (2) } I_{DQ} = \left(\frac{0.060}{2} \right) \left(\frac{W}{L} \right) (V_{GS} - 1.2)^2$$

$$\text{Let } \underline{V_{GS} = 2.5 \text{ V}}$$

$$\text{Then from (1), } 10 = I_{DQ}(5) + 5 + 2.5 \Rightarrow \underline{I_D = 0.5 \text{ mA}}$$

$$\text{Then from (2), } 0.5 = \left(\frac{0.060}{2} \right) \left(\frac{W}{L} \right) (2.5 - 1.2)^2 \Rightarrow$$

$$\underline{\frac{W}{L} = 9.86}$$

$$I_{DQ} R_S = V_{GS} \Rightarrow R_S = \frac{V_{GS}}{I_{DQ}} = \frac{2.5}{0.5} \Rightarrow \underline{R_S = 5 \text{ k}\Omega}$$

$$I_R = \frac{10}{R_1 + R_2} = (0.5)(0.05) = 0.025 \text{ mA}$$

$$\text{Then } R_1 + R_2 = \frac{10}{0.025} = 400 \text{ k}\Omega$$

$$\left(\frac{R_2}{R_1 + R_2} \right) (V_{DD}) = 2V_{GS} \Rightarrow \left(\frac{R_2}{400} \right) (10) = 2(2.5) \Rightarrow$$

$$\underline{R_1 = R_2 = 200 \text{ k}\Omega}$$

5.24

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \left(\frac{5.5}{14.5 + 5.5} \right) (10) - 5 = -2.25 \text{ V}$$

$$I_D = \frac{V_G - V_{GS} - (-5)}{R_S} = K_n (V_{GS} - V_{TN})^2$$

Assume transistor biased in saturation region

$$-2.25 - V_{GS} + 5 = (0.5)(0.6)(V_{GS} - (-1))^2$$

$$2.75 - V_{GS} = (0.3)(V_{GS}^2 + 2V_{GS} + 1)$$

$$0.3V_{GS}^2 + 1.6V_{GS} - 2.45 = 0$$

$$V_{GS} = \frac{-1.6 \pm \sqrt{(1.6)^2 + 4(0.3)(2.45)}}{2(0.3)}$$

$$\Rightarrow V_{GS} = 1.24 \text{ V}$$

$$I_D = \frac{-2.25 - 1.24 + 5}{0.6} \Rightarrow I_D = 2.52 \text{ mA}$$

$$V_{DS} = 10 - I_D(R_S + R_D) \\ = 10 - (2.52)(0.6 + 0.8)$$

$$\Rightarrow V_{DS} = 6.47 \text{ V}$$

$$V_{DS} > V_{DS}(\text{sat})$$

5.25

$$20 = I_{DQ}R_S + V_{SDQ} + I_{DQ}R_D$$

$$(1) 20 = V_{SG} + 10 + I_{DQ}R_D$$

$$I_{DQ} = \left(\frac{k'_p}{2} \right) \left(\frac{W}{L} \right) (V_{SG} + V_{TP})^2$$

$$(2) I_{DQ} = \left(\frac{0.040}{2} \right) \left(\frac{W}{L} \right) (V_{SG} - 2)^2$$

$$\text{For example, let } I_{DQ} = 0.8 \text{ mA and } V_{SG} = 4 \text{ V}$$

$$\text{Then } 0.8 = \left(\frac{0.040}{2} \right) \left(\frac{W}{L} \right) (4 - 2)^2 \Rightarrow \frac{W}{L} = 10$$

$$I_{DQ}R_S = V_{SG} \Rightarrow (0.8)R_S = 4 \Rightarrow R_S = 5 \text{ k}\Omega$$

$$\text{From (1) } 20 = 4 + 10 + (0.8)R_D \Rightarrow R_D = 7.5 \text{ k}\Omega$$

$$I_R = \frac{20}{R_1 + R_2} = (0.8)(0.1) \Rightarrow R_1 + R_2 = 250 \text{ k}\Omega$$

$$\left(\frac{R_1}{R_1 + R_2} \right) (20) = 2V_{SG} = (2)(4)$$

$$\frac{R_1}{250} (20) = 8 \Rightarrow R_1 = 100 \text{ k}\Omega, R_2 = 150 \text{ k}\Omega$$

5.26

$$(a) (i) I_Q = 50 = 500(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 1.516 \text{ V}$$

$$V_{DS} = 5 - (-1.516) \Rightarrow V_{DS} = 6.516 \text{ V}$$

$$(iv) I_Q = 1 = (0.5)(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 2.61 \text{ V}$$

$$V_{DS} = 5 - (-2.61) \Rightarrow V_{DS} = 7.61 \text{ V}$$

$$(b) (i) \text{ Same as (a) } V_{GS} = V_{DS} = 1.516 \text{ V}$$

$$(iv) V_{GS} = V_{DS} = 2.61 \text{ V}$$

5.27

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$0.25 = (0.2)(V_{GS} - 0.6)^2$$

$$V_{GS} = \sqrt{\frac{0.25}{0.2}} + 0.6 \Rightarrow V_{GS} = 1.72 \text{ V}$$

$$\Rightarrow V_S = -1.72 \text{ V}$$

$$V_D = 9 - (0.25)(24) \Rightarrow V_D = 3 \text{ V}$$

5.28

$$I_D = \frac{5 - V_D}{R_D} \Rightarrow 0.8 = \frac{5 - 1}{R_D} \Rightarrow R_D = 5 \text{ k}\Omega$$

$$V_G = 0$$

$$I_D = K_n(V_{GS} - V_{TN})^2 \Rightarrow 0.8 = (0.4)(V_{GS} - 1.7)^2$$

$$V_{GS} = \sqrt{\frac{0.8}{0.4}} + 1.7 \Rightarrow V_{GS} = 3.11 \text{ V}$$

$$\Rightarrow V_S = -3.11 \text{ V}$$

$$I_D = 0.8 = \frac{-3.11 - (-5)}{R_S} \Rightarrow R_S = 2.36 \text{ k}\Omega$$

5.29

$$V_{DD} = V_{SD} + I_{DQ}R$$

$$9 = 2.5 + (0.1)R \Rightarrow R = 65 \text{ k}\Omega$$

$$I_{DQ} = \left(\frac{k'_p}{2} \right) \left(\frac{W}{L} \right) (V_{SG} + V_{TP})^2$$

$$(0.1) = \left(\frac{0.025}{2} \right) \left(\frac{W}{L} \right) (2.5 - 1.5)^2 \Rightarrow \frac{W}{L} = 8$$

$$\text{Then for } L = \mu\text{m}, W = 32 \mu\text{m}$$

5.30

$$5 = I_{DQ}R_S + V_{SDQ} = I_{DQ}(2) + 2.5$$

$$I_{DQ} = 1.25 \text{ mA}$$

$$I_R = \frac{10}{R_1 + R_2} = (1.25)(0.1) \Rightarrow R_1 + R_2 = 80 \text{ k}\Omega$$

$$I_{DQ} = K_p(V_{SG} + V_{TP})^2$$

$$1.25 = 0.5(V_{SG} + 1.5)^2 \Rightarrow \sqrt{\frac{1.25}{0.5}} - 1.5 = V_{SG}$$

$$V_{SG} = 0.0811 \text{ V}$$

$$V_G = V_S - V_{SG} = 2.5 - 0.0811 = 2.42 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$2.42 = \left(\frac{R_2}{80} \right) (10) - 5 \Rightarrow$$

$$R_2 = 59.4 \text{ k}\Omega, R_1 = 20.6 \text{ k}\Omega$$

5.31

$$K_p = \left(\frac{0.030}{2} \right) (20) \Rightarrow 0.30 \text{ mA/V}^2$$

$$I_D = K_p(V_{SG} + V_{TP})^2$$

$$0.5 = 0.30(V_{SG} - 1.2)^2 \Rightarrow V_{SG} = 2.49 \text{ V}$$

$$V_S = V_{SG} = 2.49 \text{ V}$$

$$I_D = \frac{5 - V_S}{R_S} = R_S = \frac{5 - 2.49}{0.5} \Rightarrow R_S = 5.02 \text{ k}\Omega$$

$$R_D = \frac{V_D - (-5)}{I_D} = \frac{5 - 3}{0.5} \Rightarrow R_D = 4 \text{ k}\Omega$$

5.32

$$I_D = \frac{-V_{SD} - (-10)}{R_D} \Rightarrow 5 = \frac{-6 + 10}{R_D}$$

$$\Rightarrow R_D = 0.8 \text{ k}\Omega$$

$$I_D = K_p (V_{SG} + V_{TP})^2 \Rightarrow 5 = 3(V_{SG} - 1.75)^2$$

$$V_{SG} = \sqrt{\frac{5}{3}} + 1.75 = 3.04 \text{ V} \Rightarrow V_G = -3.04$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5 = -3.04$$

$$R_{in} = R_1 \parallel R_2 = 80 \text{ k}\Omega$$

$$\frac{1}{R_1} \cdot (80)(10) = 5 - 3.04 \Rightarrow R_1 = 408 \text{ k}\Omega$$

$$\frac{408 R_2}{408 + R_2} = 80 \Rightarrow R_2 = 99.5 \text{ k}\Omega$$

5.33

(a) $K_{n1} = \left(\frac{60}{2} \right) (4) = 120 \mu\text{A/V}^2$

$$K_{n2} = \left(\frac{60}{2} \right) (1) = 30 \mu\text{A/V}^2$$

For $v_i = 1 \text{ V}$, M_1 Sat. region, M_2 Non-sat. region.

$$I_{D1} = I_{D2}$$

$$30[2(-V_{TNL})(5 - v_o) - (5 - v_o)^2] = 120(1 - 0.8)^2$$

We find $v_o^2 - 6.4v_o + 7.16 = 0 \Rightarrow v_o = 4.955 \text{ V}$

(b) For $v_i = 3 \text{ V}$, M_1 Non-sat. region, M_2 Sat. region. $I_{D1} = I_{D2}$

$$30[-(-1.8)]^2 = 120[2(3 - 0.8)v_o - v_o^2]$$

We find $4v_o^2 - 17.6v_o + 3.24 = 0 \Rightarrow v_o = 0.193 \text{ V}$

(c) For $v_i = 5 \text{ V}$, biasing same as (b)

$$30[-(-1.8)]^2 = 120[2(5 - 0.8)v_o - v_o^2]$$

We find $4v_o^2 - 33.6v_o + 3.24 = 0 \Rightarrow v_o = 0.0976 \text{ V}$

5.34

For $v_i = 5 \text{ V}$, M_1 Non-sat. region, M_2 Sat. region.

$$I_{D1} = I_{D2}$$

$$\left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_1 [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2] =$$

$$\left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN2})^2$$

$$\left(\frac{W}{L} \right)_1 [2(5 - 0.8)(0.15) - (0.15)^2] = (1)[0 - (-2)]^2$$

which yields $\left(\frac{W}{L} \right)_1 = 3.23$

5.35

a. M_1 and M_2 in saturation

$$K_{n1}(V_{GS1} - V_{TN1})^2 = K_{n2}(V_{GS2} - V_{TN2})^2$$

$$K_{n1} = K_{n2}, V_{TN1} = V_{TN2}$$

$$\Rightarrow V_{GS1} = V_{GS2} = 2.5 \text{ V}, V_0 = 2.5 \text{ V}$$

$$I_D = (15)(40)(2.5 - 0.8)^2 \Rightarrow I_D = 1.73 \text{ mA}$$

b. $\left(\frac{W}{L} \right)_1 > \left(\frac{W}{L} \right)_2 \Rightarrow V_{GS1} < V_{GS2}$

$$40(V_{GS1} - 0.8)^2 = (15)(V_{GS2} - 0.8)^2$$

$$V_{GS2} = 5 - V_{GS1}$$

$$1.63(V_{GS1} - 0.8) = (5 - V_{GS1} - 0.8)$$

$$2.63V_{GS1} = 5.50 \Rightarrow V_{GS1} = 2.09 \text{ V}$$

$$V_{GS2} = 2.91 \text{ V}, V_0 = V_{GS1} = 2.09 \text{ V}$$

$$I_D = (15)(15)(2.91 - 0.8)^2 \Rightarrow I_D = 1.0 \text{ mA}$$

5.36

Each transistor biased in saturation.

$$M_1: V_1 = V_{GS1} = 2 \text{ V}$$

$$I_D = 0.5 = 0.018 \left(\frac{W}{L} \right)_1 (2 - 1)^2$$

$$\Rightarrow \left(\frac{W}{L} \right)_1 = 27.8$$

$$M_2: V_{GS2} = V_2 - V_1 = 5 - 2 = 3 \text{ V}$$

$$I_D = 0.5 = 0.018 \left(\frac{W}{L} \right)_2 (3 - 1)^2$$

$$\Rightarrow \left(\frac{W}{L} \right)_2 = 6.94$$

$$M_1: V_{GS1} = 10 - V_2 = 10 - 5 = 5 \text{ V}$$

$$I_D = 0.5 = 0.018 \left(\frac{W}{L} \right)_1 (5 - 1)^2$$

$$\Rightarrow \left(\frac{W}{L} \right)_1 = 1.74$$

5.37

M_L in saturation

M_D in nonsaturation

$$\left(\frac{W}{L} \right)_L (V_{GSL} - V_{TNL})^2$$

$$= \left(\frac{W}{L} \right)_D [2(V_{GSD} - V_{TND})V_{DSD} - V_{DSD}^2]$$

$$(1)(5 - 0.1 - 0.8)^2$$

$$= \left(\frac{W}{L} \right)_D [2(5 - 0.8)(0.1) - (0.1)^2]$$

$$16.81 = \left(\frac{W}{L} \right)_D [0.83]$$

$$\left(\frac{W}{L} \right)_D = 20.3$$

5.38

 M_L in saturation M_D in nonsaturation

$$\left(\frac{W}{L}\right)_L (V_{GS_L} - V_{TN_L})^2 = \left(\frac{W}{L}\right)_D [2(V_{GS_D} - V_{TN_D})V_{DS_D} - V_{DS_D}^2]$$

$$(1)(1.8)^2$$

$$= \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.05) - (0.05)^2]$$

$$3.24 = \left(\frac{W}{L}\right)_D [0.4175]$$

$$\left(\frac{W}{L}\right)_D = 7.76$$

5.39

$$I_{REF} = K_{n4}(V_{GS4} - V_{TN})^2 = K_{n3}(V_{GS3} - V_{TN})^2$$

$$V_{GS4} = 5 - V_{GS3}$$

$$\sqrt{\frac{400}{200}}(5 - V_{GS3} - 1) = (V_{GS3} - 1)$$

$$2.41V_{GS3} = 6.66 \Rightarrow \underline{V_{GS3} = 2.76 \text{ V}}$$

$$\underline{V_{GS4} = 2.24 \text{ V}} \quad \underline{V_{GS2} = V_{GS3} = 2.76 \text{ V}}$$

$$I_{REF} = K_{n3}(V_{GS3} - V_{TN})^2 = (0.2)(2.76 - 1)^2$$

$$\underline{I_{REF} = 0.620 \text{ mA}}$$

$$I_Q = K_{n2}(V_{GS2} - V_{TN})^2 = (0.1)(2.76 - 1)^2$$

$$\underline{I_Q = 0.310 \text{ mA}}$$

$$I_Q = K_{n1}(V_{GS1} - V_{TN})^2$$

$$\Rightarrow 0.310 = (0.08)(V_{GS1} - 1)^2$$

$$\text{Then } V_{GS1} = \sqrt{\frac{0.310}{0.08}} + 1 \Rightarrow \underline{V_{GS1} = 2.97 \text{ V}}$$

5.40

$$I_D = \frac{V_{DD} - V_0}{R_D} = \frac{5 - 0.1}{10} = 0.49 \text{ mA}$$

Transistor biased in nonsaturation

$$I_D = 0.49$$

$$= (0.015) \left(\frac{W}{L}\right) [2(4.2 - 0.8)(0.1) - (0.1)^2]$$

$$0.49 = \left(\frac{W}{L}\right) [0.67] \Rightarrow \underline{\frac{W}{L} = 0.731}$$

5.41

$$5 = I_D R_D + V_T + V_{DS}$$

$$5 = (12)R_D + 1.6 + 0.2 \Rightarrow \underline{R_D = 267 \Omega}$$

$$I_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) (V_{GS} - V_{TN})^2$$

$$12 = \left(\frac{0.040}{2}\right) \left(\frac{W}{L}\right) (5 - 0.8)^2 \Rightarrow \underline{\frac{W}{L} = 34}$$

5.42

$$5 = V_{SD} + I_D R_D + V_T$$

$$5 = 0.15 + (15)R_D + 1.6 \Rightarrow \underline{R_D = 217 \Omega}$$

$$I_D = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right) (V_{SG} + V_{TP})^2$$

$$15 = \left(\frac{0.020}{2}\right) \left(\frac{W}{L}\right) (5 - 0.8)^2 \Rightarrow \underline{\frac{W}{L} = 85}$$

5.43

$$V_{DS}(\text{sat}) = V_{GS} - V_P$$

$$\text{So } \underline{V_{DS} > V_{DS}(\text{sat}) = -V_P, \quad I_D = I_{DSS}}$$

5.44

$$V_{DS}(\text{sat}) = V_{GS} - V_P = V_{GS} + 3 = V_{DS}(\text{sat})$$

$$\text{a. } V_{GS} = 0 \Rightarrow \underline{I_D = I_{DSS} = 6 \text{ mA}}$$

$$\text{b. } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 6 \left(1 - \frac{-1}{-3}\right)^2$$

$$\Rightarrow \underline{I_D = 2.67 \text{ mA}}$$

$$\text{c. } I_D = 6 \left(1 - \frac{-2}{-3}\right)^2 \Rightarrow \underline{I_D = 0.667 \text{ mA}}$$

$$\text{d. } \underline{I_D = 0}$$

5.45

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2.8 = I_{DSS} \left(1 - \frac{1}{V_P}\right)^2$$

$$0.30 = I_{DSS} \left(1 - \frac{3}{V_P}\right)^2$$

$$\frac{2.8}{0.30} = \frac{\left(1 - \frac{1}{V_P}\right)^2}{\left(1 - \frac{3}{V_P}\right)^2} = 9.33$$

$$\frac{\left(1 - \frac{1}{V_P}\right)}{\left(1 - \frac{3}{V_P}\right)} = 3.055$$

$$1 - \frac{1}{V_P} = 3.055 - \frac{9.165}{V_P}$$

$$\frac{8.165}{V_P} = 2.055 \Rightarrow \underline{V_P = 3.97 \text{ V}}$$

$$2.8 = I_{DSS} \left(1 - \frac{1}{3.97}\right)^2 = I_{DSS}(0.560)$$

$$\Rightarrow \underline{I_{DSS} = 5.0 \text{ mA}}$$

5.46

$$V_S = -V_{GS}, \quad V_{SD} = V_S - V_{DD}$$

$$\text{Want } V_{SD} \geq V_{SD}(\text{sat}) = V_P - V_{GS}$$

$$V_S - V_{DD} \geq V_P - V_{GS}$$

$$-V_{GS} - V_{DD} \geq V_P - V_{GS} \Rightarrow \underline{V_{DD} \leq -V_P}$$

$$\text{So } \underline{V_{DD} \leq -2.5 \text{ V}}$$

$$I_D = 2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$2 = 6 \left(1 - \frac{V_{GS}}{2.5} \right)^2 \Rightarrow V_{GS} = 1.06 \text{ V}$$

$$\Rightarrow \underline{V_S = -1.06 \text{ V}}$$

5.47

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$18.5 = K_n (0.35 - V_{TN})^2$$

$$86.2 = K_n (0.5 - V_{TN})^2$$

Then

$$\frac{18.5}{86.2} = 0.2146 = \frac{(0.35 - V_{TN})^2}{(0.50 - V_{TN})^2} \Rightarrow \underline{V_{TN} = 0.221 \text{ V}}$$

$$18.5 = K_n (0.35 - 0.221)^2 \Rightarrow \underline{K_n = 1.11 \text{ mA/V}^2}$$

5.48

$$I_D = K(V_{GS} - V_{TN})^2$$

$$250 = K(0.75 - 0.24)^2 \Rightarrow \underline{K = 0.961 \text{ mA/V}^2}$$

5.49

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = \frac{V_S}{R_S} = -\frac{V_{GS}}{R_S}$$

$$10 \left(1 - \frac{V_{GS}}{-5} \right)^2 = -\frac{V_{GS}}{0.2}$$

$$2 \left(1 + \frac{2V_{GS}}{5} + \frac{V_{GS}^2}{25} \right) = -V_{GS}$$

$$\frac{2}{25} V_{GS}^2 + \frac{9}{5} V_{GS} + 2 = 0$$

$$2V_{GS}^2 + 45V_{GS} + 50 = 0$$

$$V_{GS} = \frac{-45 \pm \sqrt{(45)^2 - 4(2)(50)}}{2(2)}$$

$$\Rightarrow \underline{V_{GS} = -1.17 \text{ V}}$$

$$I_D = -\frac{V_{GS}}{R_S} = \frac{1.17}{0.2} \Rightarrow \underline{I_D = 5.85 \text{ mA}}$$

$$V_D = 20 - (5.85)(2) = 8.3 \text{ V}$$

$$V_{DS} = V_D - V_S = 8.3 - 1.17 \Rightarrow \underline{V_{DS} = 7.13 \text{ V}}$$

5.50

$$V_{DS} = V_{DD} - V_S$$

$$8 = 10 - V_S \Rightarrow V_S = 2 \text{ V} = I_D R_S = (5) R_S$$

$$\Rightarrow \underline{R_S = 0.4 \text{ k}\Omega}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$5 = I_{DSS} \left(1 - \frac{-1}{V_P} \right)^2 \quad \text{Let } \underline{I_{DSS} = 10 \text{ mA}}$$

$$5 = 10 \left(1 - \frac{-1}{V_P} \right)^2 \Rightarrow \underline{V_P = -3.41 \text{ V}}$$

$$V_G = V_{GS} + V_S = -1 + 2 = 1 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$1 = \frac{1}{R_1} (500)(10) \Rightarrow \underline{R_1 = 5 \text{ M}\Omega}$$

$$\frac{5R_2}{5 + R_2} = 0.5 \Rightarrow \underline{R_2 = 0.556 \text{ M}\Omega}$$

5.51

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$5 = 8 \left(1 - \frac{V_{GS}}{4} \right)^2 \Rightarrow \underline{V_{GS} = 0.838 \text{ V}}$$

$$V_{SD} = V_{DD} - I_D(R_S + R_D)$$

$$= 20 - (5)(0.5 + 2) \Rightarrow \underline{V_{SD} = 7.5 \text{ V}}$$

$$V_S = 20 - (5)(0.5) = 17.5 \text{ V}$$

$$V_G = V_S + V_{GS} = 17.5 + 0.838 = 18.3 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$18.3 = \frac{1}{R_1} (100)(20) \Rightarrow \underline{R_1 = 109 \text{ k}\Omega}$$

$$\frac{109R_2}{109 + R_2} = 100 \Rightarrow \underline{R_2 = 1.21 \text{ M}\Omega}$$

5.52

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$5 = 7 \left(1 - \frac{V_{GS}}{3} \right)^2 \Rightarrow \underline{V_{GS} = 0.465 \text{ V}}$$

$$V_{SD} = V_{DD} - I_D(R_S + R_D)$$

$$6 = 12 - (5)(0.3 + R_D) \Rightarrow \underline{R_D = 0.9 \text{ k}\Omega}$$

$$V_S = 12 - (5)(0.3) = 10.5 \text{ V}$$

$$V_G = V_S + V_{GS} = 10.5 + 0.465 = 10.965 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$10.965 = \left(\frac{R_2}{100} \right) (12) \Rightarrow \underline{R_2 = 91.4 \text{ k}\Omega}$$

$$\Rightarrow \underline{R_1 = 8.6 \text{ k}\Omega}$$

5.53

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{60}{140 + 60} \right) (20)$$

$$\Rightarrow \underline{V_G = 6 \text{ V}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$

$$(8)(2) \left(1 - \frac{V_{GS}}{(-4)} \right)^2 = 6 - V_{GS}$$

$$16 \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right) = 6 - V_{GS}$$

$$V_{GS}^2 + 9V_{GS} + 10 = 0$$

$$V_{GS} = \frac{-9 \pm \sqrt{(9)^2 - 4(10)}}{2} \Rightarrow \underline{V_{GS} = -1.30}$$

$$I_D = 8 \left(1 - \frac{(-1.30)}{(-4)} \right)^2 \Rightarrow \underline{I_D = 3.65 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$= 20 - (3.65)(2 + 2.7)$$

$$V_{DS} = 2.85 \text{ V}$$

$$V_{DS} > V_{DS}(\text{sat}) = V_{GS} - V_P$$

$$= -1.30 - (-4)$$

$$= 2.7 \text{ V (Yes)}$$

5.54

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$5 = 12 - I_D(0.5 + 1) \Rightarrow \underline{I_D = 4.67 \text{ mA}}$$

$$V_S = I_D R_S = (4.67)(0.5) \Rightarrow V_S = 2.33 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{20}{450 + 20} \right) (12)$$

$$\Rightarrow \underline{V_G = 0.511 \text{ V}}$$

$$V_{GS} = V_G - V_S = 0.511 - 2.33$$

$$\Rightarrow \underline{V_{GS} = -1.82 \text{ V}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$4.67 = 10 \left(1 - \frac{(-1.82)}{V_P} \right)^2 \Rightarrow \underline{V_P = -6.75 \text{ V}}$$

5.55

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2, \quad V_{GS} = 0$$

$$\underline{I_D = I_{DSS} = 4 \text{ mA}}$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D} = \frac{10 - 3}{4} \Rightarrow \underline{R_D = 1.75 \text{ k}\Omega}$$

5.56

$$V_{SD} = V_{DD} - I_D R_S$$

$$10 = 20 - (1) R_S \Rightarrow \underline{R_S = 10 \text{ k}\Omega}$$

$$R_1 + R_2 = \frac{V_{DD}}{I} = \frac{20}{0.1} = 200 \text{ k}\Omega$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$1 = 2 \left(1 - \frac{V_{GS}}{2} \right)^2 \Rightarrow \underline{V_{GS} = 0.586 \text{ V}}$$

$$V_G = V_S + V_{GS} = 10 + 0.586 = 10.586$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$10.586 = \left(\frac{R_2}{200} \right) (20) \Rightarrow \underline{R_2 = 106 \text{ k}\Omega}$$

$$\underline{R_1 = 94 \text{ k}\Omega}$$

5.57

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$2 = 3 - (0.040)(10 + R_D) \Rightarrow \underline{R_D = 15 \text{ k}\Omega}$$

$$I_D = K(V_{GS} - V_{TN})^2$$

$$40 = 250(V_{GS} - 0.20)^2 \Rightarrow \underline{V_{GS} = 0.60 \text{ V}}$$

$$V_G = V_{GS} + V_S = 0.60 + (0.040)(10) = 1.0 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$1 = \left(\frac{R_2}{150} \right) (3) \Rightarrow \underline{R_2 = 50 \text{ k}\Omega}$$

$$\underline{R_1 = 100 \text{ k}\Omega}$$

5.58

$$\text{For } V_o = 0.70 \text{ V} \Rightarrow$$

$$V_{DS} = 0.70 > V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

$$0.75 - 0.15 = 0.6$$

Biased in the saturation region

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{3 - 0.7}{50} \Rightarrow \underline{I_D = 46 \mu\text{A}}$$

$$I_D = K(V_{GS} - V_{TN})^2 \Rightarrow 46 = K(0.75 - 0.15)^2 \Rightarrow$$

$$\underline{K = 128 \mu\text{A/V}^2}$$