

Chapter 16

Exercise Solutions

E16.1

a. Driver in nonsaturation:

$$i_D = \frac{V_{DD} - v_O}{R_D} = \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right) [2(v_I - V_{TN})v_O - v_O^2]$$

$$\frac{5 - (0.15)}{R_D} = \frac{35}{2}(5) [2(5 - 0.8)(0.15) - (0.15)^2]$$

$$\frac{4.85}{R_D} = 87.5[1.2375]$$

$$\Rightarrow R_D = 44.8 \text{ k}\Omega$$

b. From Equation (16-10):

$$\left(\frac{0.035}{2}\right)(5)(44.8)(V_{It} - 0.8)^2 + (V_{It} - 0.8) - 5 = 0$$

$$3.920(V_{It} - 0.8)^2 + (V_{It} - 0.8) - 5 = 0$$

$$V_{It} - 0.8 = \frac{-1 \pm \sqrt{1 + 4(3.92)(5)}}{2(3.92)}$$

$$V_{It} - 0.8 = 1.0 \Rightarrow V_{It} = 1.8 \text{ V}$$

$$V_{O1} = 1.0 \text{ V}$$

E16.2

a. i. $v_I = 0 \Rightarrow v_O = 4 \text{ V}$ ii. $v_I = 4 \text{ V}$, driver in nonsaturation

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right) (v_{GS} - V_{TN})^2$$

$$= \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right) [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$$

$$2(5 - v_O - 1)^2 = (16) [2(4 - 1)v_O - v_O^2]$$

$$16 - 8v_O + v_O^2 = 8(6v_O - v_O^2)$$

$$9v_O^2 - 56v_O + 16 = 0$$

$$v_O = \frac{56 \pm \sqrt{(56)^2 - 4(9)(16)}}{2(9)}$$

$$v_O = 0.30 \text{ V}$$

b. $P = i_D \cdot V_{DD}$

$$i_D = \frac{35}{2}(2)(5 - 0.30 - 1)^2 = 479 \text{ }\mu\text{A}$$

$$P = (0.479)(5)$$

$$\Rightarrow P = 2.4 \text{ mW}$$

E16.3

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{750}{5} = 150 \text{ }\mu\text{A}$$

$$150 = \frac{35}{2} \left(\frac{W}{L}\right)_L (5 - 0.2 - 0.8)^2$$

$$150 = 280 \left(\frac{W}{L}\right)_L \Rightarrow \left(\frac{W}{L}\right)_L = 0.536$$

$$i_D = \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_I - V_{TN})v_O - v_O^2]$$

$$150 = \frac{35}{2} \left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.2) - (0.2)^2]$$

$$150 = 23.1 \cdot \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 6.49$$

E16.4

a. Load in saturation; driver in nonsaturation:

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (v_{GS} - V_{TN})^2$$

$$= \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$$

$$2(-[-1.5])^2 = (6) [2(5 - 0.7)v_O - v_O^2]$$

$$4.5 = 6(8.6v_O - v_O^2)$$

$$6v_O^2 - 51.6v_O + 4.5 = 0$$

$$v_O = \frac{51.6 \pm \sqrt{(51.6)^2 - 4(6)(4.5)}}{2(6)}$$

$$v_O = 0.0881 \text{ V}$$

b. Load

$$v_{OL} = V_{DD} + V_{TNL} \text{ Equation (16.26(b))}$$

$$= 5 - 1.5 \Rightarrow v_{OL} = 3.5 \text{ V}$$

From Equation (16-28(b)):

$$\sqrt{\frac{K_D}{K_L}} (v_{It} - V_{TND}) = -V_{TNL}$$

$$\sqrt{\frac{6}{2}} (v_{It} - 0.7) = -(-1.5) = 1.5$$

Load:

$$v_{It} = 1.57 \text{ V}$$

$$v_{OL} = 3.5 \text{ V}$$

Driver:

$$v_{It} = 1.57 \text{ V}$$

$$v_{OL} = 0.87 \text{ V}$$

$$c. i_D = \frac{35}{2} \cdot (2)(1.5)^2 = 78.75 \text{ }\mu\text{A}$$

$$P = I_D \cdot V_{DD} = (78.75)(5)$$

$$\Rightarrow P = 394 \text{ }\mu\text{W}$$

E16.5

$$P = i_D \cdot V_{DD} \Rightarrow I_D = \frac{350}{5} = 70 \mu\text{A}$$

$$i_D = \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$70 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (2)^2 \Rightarrow \left(\frac{W}{L}\right)_L = 1$$

$$i_D = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.05) - (0.05)^2]$$

$$70 = 7.31 \cdot \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 9.58$$

E16.6

From Equation (16-35):

$$V_{IH} = 0.85 + \frac{5 - 0.85}{16} \cdot \left\{ \frac{1 + 2(16)}{\sqrt{1 + 3(16)}} - 1 \right\}$$

$$\Rightarrow V_{IH} = 1.81 \text{ V}$$

Then from Equation (16-34):

$$V_{OLU} = \frac{(5 - 0.85) + 16(1.81 - 0.85)}{(1 + 2(16))}$$

$$V_{OLU} = 0.591 \text{ V}$$

$$V_{IL} = 0.85$$

$$V_{OHU} = 4.15$$

So

$$NM_L = V_{IL} - V_{OLU} = 0.85 - 0.591$$

$$\Rightarrow NM_L = 0.259 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 4.15 - 1.81$$

$$\Rightarrow NM_H = 2.34 \text{ V}$$

E16.7

From Equation (16-38):

$$V_{IL} = 1 + \frac{1.7}{\sqrt{(5)(6)}} \Rightarrow V_{IL} = 1.31 \text{ V}$$

Then from Equation (16-37):

$$V_{OHU} = (5 - 1.7) + (5)(1.31 - 1) = 4.85 \text{ V}$$

From Equation (16-41):

$$V_{IH} = 1 + \frac{2(1.7)}{\sqrt{(3)(5)}} \Rightarrow V_{IH} = 1.88 \text{ V}$$

Then from Equation (16-40):

$$V_{OLU} = \frac{1.88 - 1}{2} \Rightarrow V_{OLU} = 0.44 \text{ V}$$

$$NM_L = V_{IL} - V_{OLU} = 1.31 - 0.44$$

$$\Rightarrow NM_L = 0.87 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 4.85 - 1.88$$

$$\Rightarrow NM_H = 2.97 \text{ V}$$

E16.8

- a. i. $A = \text{logic } 1 = 10 \text{ V}$, $B = \text{logic } 0$
 "A" driver in nonsaturation, "B" driver off

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$= \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_i - V_{TND})V_{OL} - V_{OL}^2]$$

$$2(3)^2 = (10)[2(10 - 1.5)V_{OL} - V_{OL}^2]$$

$$9 = 5(17V_{OL} - V_{OL}^2)$$

$$5V_{OL}^2 - 85V_{OL} + 9 = 0$$

$$V_{OL} = \frac{85 \pm \sqrt{(85)^2 - 4(5)(9)}}{2(5)}$$

$$\Rightarrow V_{OL} = 0.107 \text{ V}$$

- ii. $A = B = \text{logic } 1$

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$= 2\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_i - V_{TND})V_{OL} - V_{OL}^2]$$

$$2(3)^2 = (2)(10)[2(10 - 1.5)V_{OL} - V_{OL}^2]$$

$$9 = 10(17V_{OL} - V_{OL}^2)$$

$$10V_{OL}^2 - 170V_{OL} + 9 = 0$$

$$V_{OL} = \frac{170 \pm \sqrt{(170)^2 - 4(10)(9)}}{2(10)}$$

$$\Rightarrow V_{OL} = 0.0531 \text{ V}$$

- b. Both cases.

$$i_D = \frac{35}{2} \cdot (2)(3)^2 = 315 \mu\text{A} \Rightarrow P = i_D \cdot V_{DD}$$

$$\Rightarrow P = 3.15 \text{ mW}$$

E16.9

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{800}{5} = 160 \mu\text{A}$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (1.4)^2 = 34.3 \left(\frac{W}{L}\right)_L$$

$$\Rightarrow \left(\frac{W}{L}\right)_L = 4.66$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.12) - (0.12)^2]$$

$$\Rightarrow \left(\frac{W}{L}\right)_D = 9.20$$

E16.10

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{800}{5} = 160 \mu\text{A}$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (1.4)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_L = 4.66$$

$$i_D = 160 \mu\text{A}$$

$$= \frac{35}{2} \cdot \frac{1}{3} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.12) - (0.12)^2]$$

$$\Rightarrow \left(\frac{W}{L}\right)_D = 27.6$$

E16.11

a. From the load transistor:

$$I_{DL} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (V_{GS} - V_{TN})^2$$

$$= \frac{35}{2} (0.5)(5 - 0.15 - 0.7)^2$$

or

$$I_{DL} = 150.7 \mu\text{A}$$

Maximum v_0 occurs when either A or B is high and C is high. For the two NMOS in series, the effective k_N is cut in half, so

$$I_{DL} = \frac{1}{2} \left[\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_D \right] [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

or

$$150.7 = \frac{1}{2} \left[\frac{35}{2} \cdot \left(\frac{W}{L}\right)_D \right] [2(5 - 0.7)(0.15) - (0.15)^2]$$

which yields

$$\left(\frac{W}{L}\right)_D = 13.6$$

$$\text{b. } P = i_D \cdot V_{DD} = (150.7)(5) \Rightarrow \underline{P = 753 \mu\text{W}}$$

E16.12

a. $v_0(\text{max})$ occurs when $A = B = 1$ and $C = D = 0$ or $A = B = 0$ and $C = D = 1$

$$\left(\frac{W}{L}\right)_L (-V_{TN})^2 = \frac{1}{2} \cdot \left(\frac{W}{L}\right)_D [2(v_i - V_{TN})v_o - v_o^2]$$

$$(0.5)(1.2)^2 = \frac{1}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.7)(0.15) - (0.15)^2]$$

$$0.72 = (0.634) \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 1.14$$

$$\text{b. } i_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (-V_{TN})^2 = \left(\frac{35}{2}\right)(0.5)[(-1.2)^2]$$

$$i_D = 12.6 \mu\text{A}$$

$$P = i_D \cdot V_{DD} = (12.6)(5) \Rightarrow \underline{P = 63 \mu\text{W}}$$

E16.13

a. $K_n/K_p = 1$

$$V_{It} = \frac{10 - 2 + (1)(2)}{1 + 1} \Rightarrow V_{It} = 5 \text{ V}$$

$$V_{OPt} = V_H + |V_{TP}| = 5 + 2 \Rightarrow V_{OPt} = 7 \text{ V}$$

$$V_{ONt} = V_H - V_{TN} = 5 - 2 \Rightarrow V_{ONt} = 3 \text{ V}$$

b. $K_n/K_p = 0.5$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{0.5}(2)}{1 + \sqrt{0.5}} \Rightarrow V_{It} = 5.52 \text{ V}$$

$$V_{OPt} = 7.52 \text{ V}$$

$$V_{ONt} = 3.52 \text{ V}$$

c. $K_n/K_p = 2$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{2}(2)}{1 + \sqrt{2}} \Rightarrow V_{It} = 4.49 \text{ V}$$

$$V_{OPt} = 6.49 \text{ V}$$

$$V_{ONt} = 2.49 \text{ V}$$

E16.14

a. $K_n = K_p = 50 \mu\text{A}/V^2$

$$V_{It} = 2.5 \text{ V}$$

$$i_D(\text{max}) = K_n(V_{It} - V_{TN})^2 = 50(2.5 - 0.8)^2$$

$$\Rightarrow \underline{i_D(\text{max}) = 145 \mu\text{A}}$$

b. $K_n = K_p = 200 \mu\text{A}/V^2$

$$V_{It} = 2.5 \text{ V}$$

$$i_D(\text{max}) = (200)(2.5 - 0.8)^2$$

$$\Rightarrow \underline{i_D(\text{max}) = 578 \mu\text{A}}$$

E16.15

$$P = f \cdot C_L \cdot V_{DD}^2$$

$$(0.10 \times 10^{-6}) = f(0.5 \times 10^{-12})(3)^2$$

$$f = 2.22 \times 10^4 \text{ Hz} \Rightarrow \underline{f = 22.2 \text{ kHz}}$$

E16.16

a. $K_n/K_p = 200/80 = 2.5$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{2.5}(2)}{1 + \sqrt{2.5}} \Rightarrow V_{It} = 4.32 \text{ V}$$

$$V_{OPt} = 6.32 \text{ V}$$

$$V_{ONt} = 2.32 \text{ V}$$

$$\text{b. } V_{IL} = 2 + \frac{10 - 2 - 2}{2.5 - 1} \cdot \left[2\sqrt{\frac{2.5}{2.5 + 3}} - 1 \right]$$

$$\Rightarrow \underline{V_{IL} = 3.39 \text{ V}}$$

$$V_{OHV} = \frac{1}{2} \{ (1 + 2.5)(3.39) + 10 - (2.5)(2) + 2 \}$$

$$V_{OHV} = 9.43 \text{ V}$$

$$V_{IH} = 2 + \frac{10 - 2 - 2}{2.5 - 1} \cdot \left[\frac{2(2.5)}{\sqrt{3(2.5) + 1}} - 1 \right]$$

$$\Rightarrow \underline{V_{IH} = 4.86 \text{ V}}$$

$$V_{OLV} = \frac{(4.86)(1 + 2.5) - 10 - (2.5)(2) + 2}{2(2.5)}$$

$$V_{OLV} = 0.802 \text{ V}$$

$$c. \quad NM_L = V_{IL} - V_{OLU} = 3.39 - 0.802$$

$$\Rightarrow NM_L = 2.59 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 9.43 - 4.86$$

$$\Rightarrow NM_H = 4.57 \text{ V}$$

E16.17

$$a. \quad V_{It} = \frac{5 - 2 + (1)(6.8)}{1 + 1}$$

$$V_{It} = 1.9 \text{ V}$$

$$V_{OPt} = 3.9 \text{ V}$$

$$V_{ONt} = 1.1 \text{ V}$$

$$b. \quad V_{IL} = 0.8 + \frac{3}{8} \cdot [5 - 2 - 0.8]$$

$$\Rightarrow V_{IL} = 1.63 \text{ V}$$

$$V_{OHU} = \frac{1}{2} (2(1.63) + 5 - 0.8 + 2)$$

$$V_{OHU} = 4.73 \text{ V}$$

$$V_{IH} = 0.8 + \frac{5}{8} (5 - 2 - 0.8)$$

$$\Rightarrow V_{IH} = 2.18 \text{ V}$$

$$V_{OLU} = \frac{1}{2} (2(2.18) - 5 - 0.8 + 2)$$

$$V_{OLU} = 0.275 \text{ V}$$

$$c. \quad NM_L = V_{IL} - V_{OLU} = 1.63 - 0.275$$

$$\Rightarrow NM_L = 1.35 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 4.73 - 2.18$$

$$\Rightarrow NM_H = 2.55 \text{ V}$$

E16.18

$$a. \quad A = 0 \Rightarrow M_{PA} \text{ (assume zero resistance)}$$

$$K_n = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_N$$

$$K_p = \left(\frac{k'_p}{2} \right) \left(\frac{W}{L} \right)_P = \frac{1}{2} \cdot \left(\frac{k'_p}{2} \right) \cdot 8 \left(\frac{W}{L} \right)_N$$

$$K_p = 2K_n \Rightarrow \frac{K_n}{K_p} = \frac{1}{2}$$

From Equation (16-55),

$$V_{It} = \frac{5 - 1 + \sqrt{0.5(1)}}{1 + \sqrt{0.5}} \Rightarrow V_{It} = 2.76 \text{ V}$$

$$V_{OPt} = 3.76 \text{ V}$$

$$V_{ONt} = 1.76 \text{ V}$$

$$b. \quad \text{From Equation (16-58(b))}$$

$$i_D(\text{peak}) = K_n (V_{It} - V_{TN})^2$$

$$50 = \frac{35}{2} \left(\frac{W}{L} \right)_N (2.76 - 1)^2 = 54.2 \left(\frac{W}{L} \right)_N$$

$$\Rightarrow \left(\frac{W}{L} \right)_N = 0.923$$

$$\left(\frac{W}{L} \right)_P = (8)(0.923) = 7.38$$

E16.19

$$\text{Want } K_{n,\text{eff}} = K_{p,\text{eff}}$$

$$\left(\frac{k'_n}{2} \right) \cdot \frac{1}{2} \left(\frac{W}{L} \right)_N = \left(\frac{k'_p}{2} \right) \cdot 2 \left(\frac{W}{L} \right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot 2 \left(\frac{W}{L} \right)_P$$

$$\Rightarrow \left(\frac{W}{L} \right)_N = 2 \left(\frac{W}{L} \right)_P$$

E16.20

$$\text{Want } K_{n,\text{eff}} = K_{p,\text{eff}}$$

$$\left(\frac{k'_n}{2} \right) \cdot 3 \left(\frac{W}{L} \right)_N = \left(\frac{k'_p}{2} \right) \cdot \frac{1}{3} \left(\frac{W}{L} \right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot \frac{1}{3} \left(\frac{W}{L} \right)_P$$

$$3 \left(\frac{W}{L} \right)_N = \frac{1}{6} \cdot \left(\frac{W}{L} \right)_P$$

Or

$$\Rightarrow \frac{(W/L)_P}{(W/L)_N} = 18$$

E16.21

$$\text{Want } K_{n,\text{eff}} = K_{p,\text{eff}}$$

$$\left(\frac{k'_n}{2} \right) \cdot \frac{1}{3} \left(\frac{W}{L} \right)_N = \left(\frac{k'_p}{2} \right) \cdot 3 \left(\frac{W}{L} \right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot 3 \left(\frac{W}{L} \right)_P$$

$$\frac{1}{3} \left(\frac{W}{L} \right)_N = \frac{3}{2} \cdot \left(\frac{W}{L} \right)_P$$

Or

$$\Rightarrow \frac{(W/L)_P}{(W/L)_N} = \frac{2}{9}$$

E16.22

NMOS:

$$M_{NA}, M_{NB} \text{ in series} \Rightarrow \left(\frac{W}{L} \right) = 2$$

$$M_{ND}, M_{NE} \text{ in parallel} \Rightarrow \left(\frac{W}{L} \right) = 1$$

$$M_{NC} \text{ in series with } M_{ND} \parallel M_{NE} \Rightarrow \left(\frac{W}{L} \right) = 2$$

$$\text{Effective composite } \left(\frac{W}{L} \right) = 1 \text{ for each side.}$$

PMOS:


Want the effective composite $\left(\frac{W}{L}\right)$ of each side to be 2.

M_{PA}, M_{PC} in series $\Rightarrow \left(\frac{W}{L}\right) = 4$

M_{PA}, M_{PB} in parallel $\Rightarrow \left(\frac{W}{L}\right)_B = 4$


M_{PD}, M_{PE} in series $\Rightarrow \left(\frac{W}{L}\right) = 8$

E16.23

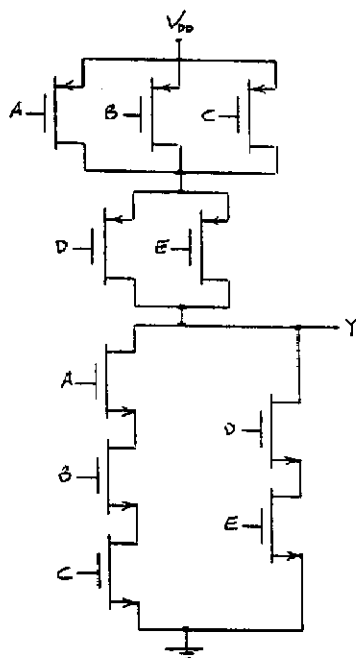


E16.24

The NMOS part of the circuit is:

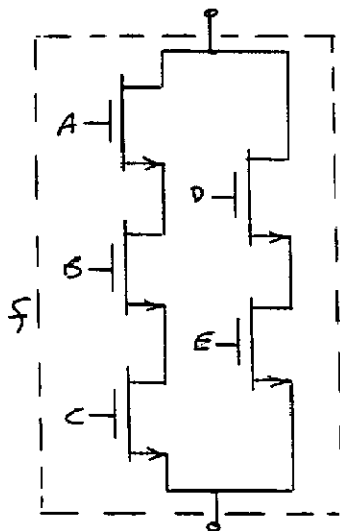

E16.25

The NMOS part of the circuit is:

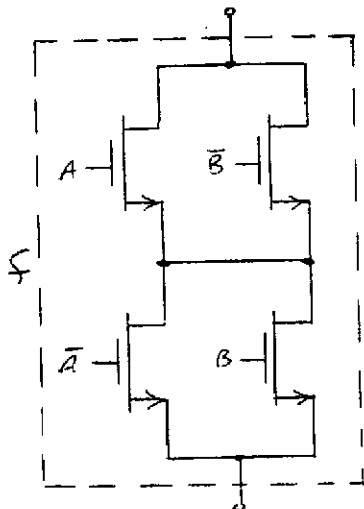

E16.26

- a. $v_I = \phi = 5\text{ V} \Rightarrow v_O = 4\text{ V}$
- b. $v_I = 3\text{ V}, \phi = 5\text{ V} \Rightarrow v_O = 3\text{ V}$
- c. $v_I = 4.2\text{ V}, \phi = 5\text{ V} \Rightarrow v_O = 4\text{ V}$
- d. $v_I = 5\text{ V}, \phi = 3\text{ V} \Rightarrow v_O = 2\text{ V}$

E16.27

(a) $v_I = 8\text{ V}, \phi = 10\text{ V} \Rightarrow v_{OSD} = 8\text{ V}$

M_D in nonsaturation

$K_D[2(v_{OSD} - V_{TND})v_O - v_O^2]$

$K_L[V_{DD} - v_O - V_{TNL}]^2$

$\frac{K_D}{K_L}[2(8 - 2)(0.5) - (0.5)^2] = [10 - 0.5 - 2]^2$

$\Rightarrow \frac{K_D}{K_L} = 9.78$

(b) $v_I = \phi = 8\text{ V} \Rightarrow v_{OSD} = 6\text{ V}$


$\frac{K_D}{K_L}[2(6 - 2)(0.5) - (0.5)^2] = [10 - 0.5 - 2]^2$

$\Rightarrow \frac{K_D}{K_L} = 15$


E16.28

Exclusive-OR

A	B	f
0	0	0
1	0	1
0	1	1
1	1	0

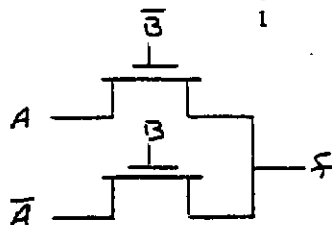

E16.29

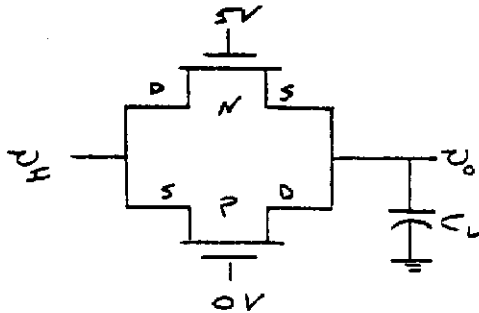

NMOS conducting for $0 \leq v_i \leq 4.2 \text{ V}$


\Rightarrow NMOS Conducting: $0 \leq t \leq 8.4 \text{ s}$

NMOS Cutoff: $8.4 \leq t \leq 10 \text{ s}$

PMOS cutoff for $0 \leq v_i \leq 1.2 \text{ V}$

\Rightarrow PMOS Cutoff: $0 \leq t \leq 2.4 \text{ s}$

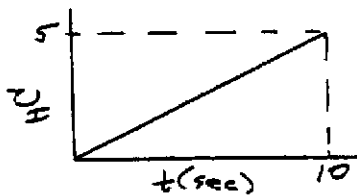PMOS Conducting: $2.4 \leq t \leq 10 \text{ s}$



E16.30

(a) $1 \text{ K} \Rightarrow 32 \times 32$ array

Each row and column requires a 5-bit word \Rightarrow
6 transistors per row and column, \Rightarrow
 $32 \times 6 + 32 \times 6 = 384$ transistors plus buffer transistors.

(b) $4 \text{ K} \Rightarrow 64 \times 64$ array

Each row and column requires a 6-bit word \Rightarrow
7 transistors per row and column \Rightarrow
 $64 \times 7 + 64 \times 7 = 896$ transistors plus buffer transistors.

(c) $16 \text{ K} \Rightarrow 128 \times 128$ array

Each row and column requires a 7-bit word \Rightarrow
8 transistors per row and column \Rightarrow
 $128 \times 8 + 128 \times 8 = 2048$ transistors plus buffer transistors.

E16.31

$16 \text{ K} \Rightarrow 16384$ cells

Total Power = $125 \text{ mW} = (2.5)I_T$

$\Rightarrow I_T = 50 \text{ mA}$

Then, for each cell, $I = \frac{50 \text{ mA}}{16384} \Rightarrow I = 3.05 \mu\text{A}$

Now, $I \equiv \frac{V_{DD}}{R}$ or $R = \frac{V_{DD}}{I} = \frac{2.5}{3.05} \Rightarrow$

$R = 0.82 \text{ M}\Omega$

E16.32

From Equation (16.93)

$$\frac{(W/L)_{n1}}{(W/L)_{n1}} = \frac{2(V_{DD}V_{TN}) - 3V_{TN}^2}{(V_{DD} - 2V_{TN})^2}$$

$$= \frac{2(2.5)(0.4) - 3(0.4)^2}{(2.5 - 2(0.4))^2} = 0.526$$

From Equation (16.95)

$$\frac{(W/L)_p}{(W/L)_{n1}} = \frac{k'_n}{k'_p} \cdot \frac{2(V_{DD}V_{TN}) - 3V_{TN}^2}{(V_{DD} + V_{TP})^2}$$

$$= (2.5) \left[\frac{2(2.5)(0.4) - 3(0.4)^2}{(2.5 - 0.4)^2} \right] = 1.31$$

So $\left(\frac{W}{L}\right)$ of transmission gate device must be

< 0.526 times the $\left(\frac{W}{L}\right)$ of the NMOS transistors in the inverter cell. The $\left(\frac{W}{L}\right)$ of the PMOS transistors must be < 1.31 times the $\left(\frac{W}{L}\right)$ of the transmission gate devices. Then the $\left(\frac{W}{L}\right)$ of the PMOS devices must be < 0.689 times $\left(\frac{W}{L}\right)$ of NMOS devices in cell.

E16.33

Initial voltage across the storage capacitor
 $= V_{DD} - V_{TN} = 3 - 0.5 = 2.5 \text{ V}$.

Now

$$-I = C \frac{dV}{dt} \text{ or } V = -\frac{I}{C} \cdot t + K$$

where $K = 2.5 \text{ V}$, $t = 1.5 \text{ ms}$, $V = \frac{2.5}{2} = 1.25 \text{ V}$, and

$C = 0.05 \text{ pF}$. Then

$$1.25 = 2.5 - \frac{I(1.5 \times 10^{-3})}{(0.05 \times 10^{-12})} \Rightarrow$$

$$I = 4.17 \times 10^{-11} \text{ A} \Rightarrow I = 41.7 \text{ pA}$$

Chapter 16

Problem Solutions

16.1

$$(a) \Delta V_{TN} = \frac{\sqrt{2e \epsilon_s N_a}}{C_{ox}} \left[\sqrt{2\phi_{fp} + V_{SB}} - \sqrt{2\phi_{fp}} \right]$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}} = 7.67 \times 10^{-8}$$

$$\sqrt{2e \epsilon_s N_a}$$

$$= \left[2(1.6 \times 10^{-19})(11.7)(8.85 \times 10^{-14})(8 \times 10^{15}) \right]^{1/2}$$

$$= 5.15 \times 10^{-4}$$

Then

$$\Delta V_{TN} = \frac{5.15 \times 10^{-4}}{7.67 \times 10^{-8}} \left[\sqrt{2(0.343) + V_{SB}} - \sqrt{2(0.343)} \right]$$

For $V_{SB} = 1V$:

$$\Delta V_{TN} = 0.671 \left[\sqrt{1.686} - \sqrt{0.686} \right] \Rightarrow \Delta V_{TN} = 0.316V$$

For $V_{SB} = 2V$:

$$\Delta V_{TN} = 0.671 \left[\sqrt{2.686} - \sqrt{0.686} \right] \Rightarrow \Delta V_{TN} = 0.544V$$

(b) For $V_{GS} = 2.5V$, $V_{DS} = 5V$, transistor biased in the saturation region.

$$I_D = K_n (V_{GS} - V_{TN})^2$$

For $V_{SB} = 0$,

$$I_D = 0.2(2.5 - 0.8)^2 = 0.578 \text{ mA}$$

For $V_{SB} = 1$,

$$I_D = 0.2(2.5 - [0.8 + 0.316])^2 = 0.383 \text{ mA}$$

For $V_{SB} = 2$,

$$I_D = 0.2(2.5 - [0.8 + 0.544])^2 = 0.267 \text{ mA}$$

16.2

$$(a) I_D = \frac{V_{DD} - v_o}{R_D} = K_n [2(V_{GS} - V_{TN})v_o - v_o^2]$$

$$\frac{5 - (0.1)}{40 \times 10^3} = K_n [2(5 - 0.8)(0.1) - (0.1)^2]$$

$$\text{or } K_n = 1.476 \times 10^{-4} \text{ A/V}^2 = \frac{8 \times 10^{-5}}{2} \left(\frac{W}{L} \right)$$

$$\text{So that } \left(\frac{W}{L} \right) = 3.69$$

b. From Equation (16.10),

$$K_n R_D [V_H - V_{TN}]^2 + [V_H - V_{TN}] - V_{DD} = 0$$

$$(0.1476)(40)[V_{IT} - 0.8]^2 + [V_{IT} - 0.8] - 5 = 0$$

$$\text{or } [V_{IT} - 0.8] = \frac{-1 \pm \sqrt{(1)^2 + 4(0.1476)(40)(5)}}{2(0.1476)(40)}$$

$$\text{or } [V_{IT} - 0.8] = 0.839$$

So that $V_{IT} = 1.64V$

$$P = I_D(\text{max}) \cdot V_{DD}$$

$$\text{and } I_D(\text{max}) = \frac{5 - (0.1)}{40} = 0.1225 \text{ mA}$$

$$\text{or } P = 0.6125 \text{ mW}$$

16.3

a. From Equation (16.10), the transistor point is found from

$$K_n R_D (V_H - V_{TN})^2 + (V_H - V_{TN}) - V_{DD} = 0$$

$$K_n = 50 \mu\text{A/V}^2, R_D = 20 \text{ k}\Omega, V_{TN} = 0.8V$$

$$(0.05)(20)(V_H - V_{TN})^2 + (V_H - V_{TN}) - 5 = 0$$

$$V_H - V_{TN} = \frac{-1 \pm \sqrt{1 + 4(0.05)(20)(5)}}{2(0.05)(20)}$$

$$= 1.79V \text{ So } V_{IT} = 2.59V$$

$$V_{Ot} = 1.79V$$

Output voltage for $v_I = 5V$ is determined from Equation (16.12):

$$v_o = 5 - (0.05)(20)[2(5 - 0.8)v_o - v_o^2]$$

$$v_o^2 - 9.4v_o + 5 = 0$$

$$\text{So } v_o = \frac{9.4 \pm \sqrt{(9.4)^2 - 4(1)(5)}}{2(1)} = 0.566V$$

b. For $R_D = 200 \text{ k}\Omega$,

$$(V_H - V_{TN}) = \frac{-1 \pm \sqrt{1 + 4(0.05)(200)(5)}}{2(0.05)(200)}$$


$$= 0.659V \text{ So } V_{IT} = 1.46V$$

$$V_{Ot} = 0.659V$$

$$v_o = 5 - (0.05)(200)[2(5 - 0.8)v_o - v_o^2]$$

$$\text{or } 10v_o^2 - 85v_o + 5 = 0$$
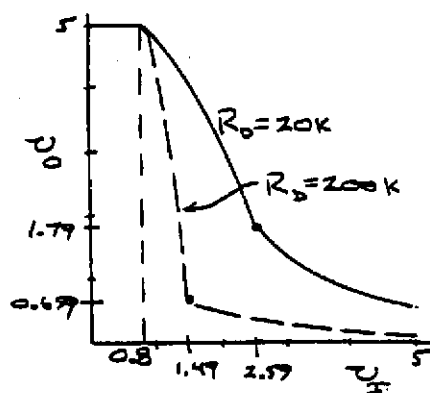
$$v_o = \frac{85 \pm \sqrt{(85)^2 - 4(10)(5)}}{2(10)} = 0.0592V$$



16.4

$$P = i_D \cdot V_{DD}$$

$$1 = i_D(5) \Rightarrow i_D = 0.2 \text{ mA}$$

Now

$$i_D = K_n [2(v_i - V_{TN})v_o - v_o^2]$$

$$0.2 = K_n [2(5 - 0.8)(0.2) - (0.2)^2]$$

$$\text{or } K_n = 0.122 \text{ mA/V}^2 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) \Rightarrow$$

$$\left(\frac{W}{L}\right) = 3.05$$

Also

$$v_o = V_{DD} - K_n R_D [2(v_i - V_{TN})v_o - v_o^2]$$

$$0.2 = 5 - (0.122)R_D [2(5 - 0.8)(0.2) - (0.2)^2] \Rightarrow$$

$$R_D = 24 \text{ k}\Omega$$

16.5

From Equation (16.21):

$$V_{It} = \frac{10 - 2 + 2 \left(1 + \sqrt{\frac{200}{50}}\right)}{1 + \sqrt{\frac{200}{50}}}$$

$$\text{or } V_{It} = 4.67 \text{ V}$$

$$V_{Ox} = V_{It} - V_{TND} = 4.67 - 2 \Rightarrow V_{Ox} = 2.67 \text{ V}$$

From Equation (16.23):

$$200[2(8 - 2)v_o - v_o^2] = 50[10 - v_o - 2]^2$$

$$4[12v_o - v_o^2] = [8 - v_o]^2 = [64 - 16v_o + v_o^2]$$

$$5v_o^2 - 64v_o + 64 = 0$$

$$v_o = \frac{64 \pm \sqrt{(64)^2 - 4(5)(64)}}{2(5)}$$

$$\text{or } v_o = 1.09 \text{ V}$$

16.6

(a) From Equation (16.23)

$$\frac{K_D}{K_L} [2(3 - 0.5)(0.25) - (0.25)^2] = (3 - 0.25 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 4.26$$

$$(b) \frac{K_D}{K_L} [2(2.5 - 0.5)(0.25) - (0.25)^2] = (3 - 0.25 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 5.06$$

$$(c) i_D = K_L (V_{GS} - V_{TNL})^2 = K_L (V_{DD} - v_o - V_{TNL})^2$$

$$= \left(\frac{0.080}{2}\right) (1)(3 - 0.25 - 0.5)^2 \Rightarrow$$

$$i_D = 0.203 \text{ mA}$$

$$P = i_D \cdot V_{DD} = (0.203)(3) \Rightarrow P = 0.608 \text{ mW}$$

for both parts (a) and (b).

16.7

$$(a) P = 0.4 \text{ mW} = i_D \cdot V_{DD} = i_D(3) \Rightarrow$$

$$i_D = 0.133 \text{ mA}$$

$$i_D = K_L (V_{DD} - v_o - V_{TNL})^2$$

$$0.133 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right)_L (3 - 0.1 - 0.5)^2 = (0.2304) \left(\frac{W}{L}\right)_L$$

$$\text{So } \left(\frac{W}{L}\right)_L = 0.577$$

$$\frac{K_D}{K_L} [2(2.5 - 0.5)(0.1) - (0.1)^2] = (3 - 0.1 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 14.8 \text{ so that } \left(\frac{W}{L}\right)_D = 8.54$$

$$V_H = \frac{3 - 0.5 + 0.5(1 + \sqrt{14.8})}{1 + \sqrt{14.8}}$$

or

$$V_H = 1.02 \text{ V}, V_{Ox} = 0.52 \text{ V}$$

$$(b) NM_L = V_{IL} - V_{OLU}$$

$$NM_H = V_{OHU} - V_{IH}$$

From Equation (16.35)

$$V_{IH} = 0.5 + \frac{(3 - 0.5)}{14.8} \left\{ \frac{(1 + 2(14.8))}{\sqrt{1 + 3(14.8)}} - 1 \right\} \Rightarrow$$

$$V_{IH} = 1.10 \text{ V}$$

$$V_{OHU} = 3.0 - 0.5 = 2.5 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 2.5 - 1.10 \Rightarrow NM_H = 1.40 \text{ V}$$

$$V_{IL} = V_{TND} = 0.5 \text{ V}$$

$$V_{OLU} = \frac{(V_{DD} - V_{TNL}) + \frac{K_D}{K_L}(V_i - V_{TND})}{1 + 2\left(\frac{K_D}{K_L}\right)}$$

$$= \frac{(3 - 0.5) + 14.8(1.1 - 0.5)}{1 + 2(14.8)} \Rightarrow$$

$$V_{OLU} = 0.372 \text{ V}$$

$$\text{Then } NM_L = V_{IL} - V_{OLU} = 0.5 - 0.372 \Rightarrow$$

$$NM_L = 0.128 \text{ V}$$

16.8

We have

$$\frac{K_D}{K_L} [2(v_i - V_{TND})v_o - v_o^2] = (V_{DD} - v_o - V_{TNL})^2$$

$$\frac{(W/L)_D}{(W/L)_L} [2(V_{DD} - V_{TN} - V_{TN})(0.08V_{DD}) - (0.08V_{DD})^2]$$

$$= (V_{DD} - 0.08V_{DD} - V_{TN})^2$$

$$\frac{(W/L)_D}{(W/L)_L} [2(V_{DD} - 2(0.2)V_{DD})(0.08V_{DD}) - 0.0064V_{DD}^2]$$

$$= [(0.92 - 0.2)V_{DD}]^2 = 0.5184V_{DD}^2$$

$$\frac{(W/L)_D}{(W/L)_L} [0.096] = 0.5184 \Rightarrow \frac{(W/L)_D}{(W/L)_L} = 5.4$$

16.9

$$V_{OH} = V_s - V_{OS} = \text{Logic 1}$$

So

$$(a) V_s = 4 \text{ V} \Rightarrow V_{OH} = 3 \text{ V}$$

$$(b) V_s = 5 \text{ V} \Rightarrow V_{OH} = 4 \text{ V}$$

$$(c) V_s = 6 \text{ V} \Rightarrow V_{OH} = 5 \text{ V}$$

$$(d) V_s = 7 \text{ V} \Rightarrow V_{OH} = 6 \text{ V}$$

$$\text{For } v_i = V_{OH}$$

$$K_D [2(v_i - V_T)v_o - v_o^2] = K_L [V_s - v_o - V_T]^2$$

Then

$$(a) (1) [2(3 - 1)V_{OL} - V_{OL}^2] = (0.4) [4 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.657 \text{ V}$$

$$(b) (1) [2(4 - 1)V_{OL} - V_{OL}^2] = (0.4) [5 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.791 \text{ V}$$

$$(c) (1) [2(5 - 1)V_{OL} - V_{OL}^2] = (0.4) [6 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.935 \text{ V}$$

$$(d) (1) [2(6 - 1)V_{OL} - V_{OL}^2] = (0.4) [7 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 1.08 \text{ V}$$

16.10

$$a. \text{ For load } V_{OL} = V_{DD} + V_{TNL} = 5 - 2 = 3 \text{ V}$$

$$\sqrt{\frac{K_D}{K_L}} (V_H - V_{TND}) = -V_{TNL}$$

$$\sqrt{\frac{500}{100}} (V_{It} - 0.8) = -(-2)$$

$$\Rightarrow V_{It} = 1.69 \text{ V}$$

$$V_{Or} = 3 \text{ V} \quad \left. \vphantom{\begin{matrix} V_{It} = 1.69 \text{ V} \\ V_{Or} = 3 \text{ V} \end{matrix}} \right\} \text{ Load}$$

$$\text{Driver: } V_{OL} = V_H - V_{TND} = 1.69 - 0.8 = 0.89 \text{ V}$$

$$V_{It} = 1.69 \text{ V}$$

$$V_{Or} = 0.89 \text{ V} \quad \left. \vphantom{V_{It} = 1.69 \text{ V}} \right\} \text{ Driver}$$

b. From Equation (16.29(b)):

$$\frac{500}{100} [2(5 - 0.8)v_o - v_o^2] = [-(-2)]^2$$

$$5v_o^2 - 42v_o + 4 = 0$$

$$v_o = \frac{42 \pm \sqrt{(42)^2 - 4(5)(4)}}{2(5)} \Rightarrow v_o = 0.0963 \text{ V}$$

$$c. i_D = K_L (-V_{TNL})^2 = 100 [-(-2)]^2 \Rightarrow$$

$$i_D = 400 \mu\text{A}$$

16.11

$$\left(\frac{500}{50} \right) [2(3 - 0.5)(0.1) - (0.1)^2] = (-V_{TNL})^2$$

So

$$(-V_{TNL})^2 = 4.9 \Rightarrow V_{TNL} = -2.21 \text{ V}$$

16.12

$$(a) P = i_D \cdot V_{DD}$$

$$150 = i_D \cdot (3) \Rightarrow i_D = 50 \mu\text{A}$$

$$i_D = K_L (-V_{TNL})^2$$

$$50 = \left(\frac{80}{2} \right) \left(\frac{W}{L} \right)_L [-(-1)]^2 \Rightarrow \left(\frac{W}{L} \right)_L = 1.25$$

$$\frac{K_D}{K_L} [2(3 - 0.5)(0.1) - (0.1)^2] = [-(-1)]^2$$

$$\frac{K_D}{K_L} = \frac{(W/L)_D}{(W/L)_L} = 2.04 \Rightarrow \left(\frac{W}{L} \right)_D = 2.55$$

For the Load:

$$V_{OL} = V_{DD} + V_{TNL} = 3 - 1 \Rightarrow V_{OL} = 2 \text{ V}$$

$$\sqrt{2.04} (V_H - 0.5) = [-(-1)] \Rightarrow V_H = 1.20 \text{ V}$$

For the Driver:

$$V_{OL} = V_H - V_{TND} = 1.20 - 0.5 \Rightarrow V_{OL} = 0.70 \text{ V}$$

$$V_H = 1.20 \text{ V}$$

$$(b) \quad NM_L = V_{IL} - V_{OLV}$$

$$NM_H = V_{OHV} - V_{IH}$$

$$V_{IL} = 0.5 + \frac{[-(-1)]}{\sqrt{(2.04)(1+2.04)}} = 0.902 \text{ V}$$

$$V_{IH} = 0.5 + \frac{2[-(-1)]}{\sqrt{3(2.04)}} = 1.31 \text{ V}$$

$$\text{Then } V_{OHV} = (3-1) + (2.04)(0.902-0.5) = 2.82 \text{ V}$$

$$V_{OLV} = \frac{(1.31-0.5)}{2} = 0.405 \text{ V}$$

$$NM_L = 0.902 - 0.405 \Rightarrow NM_L = 0.497 \text{ V}$$

$$NM_H = 2.82 - 1.31 \Rightarrow NM_H = 1.51 \text{ V}$$

16.13

a. From Equation (16.29(b)):

$$\left(\frac{W}{L}\right)_D [2(2.5-0.5)(0.05) - (0.05)^2] = \left(\frac{W}{L}\right)_L [(-(-1))]^2$$

$$\left(\frac{W}{L}\right)_L = 1$$

$$\text{Then } \left(\frac{W}{L}\right)_D = 5.06$$

$$b. \quad i_D = \left(\frac{80}{2}\right)(1)[-(-1)]^2$$

$$\text{or } i_D = 40 \mu\text{A}$$

$$P = i_D \cdot V_{DD} = (40)(2.5)$$

$$\Rightarrow P = 100 \mu\text{W}$$

16.14

$$a. \quad i. \quad v_I = 0.5 \text{ V} \Rightarrow i_D = 0 \Rightarrow P = 0$$

$$ii. \quad v_I = 5 \text{ V, From Equation (16.12),}$$

$$v_0 = 5 - (0.1)(20)[2(5-1.5)v_0 - v_0^2]$$

$$2v_0^2 - 15v_0 + 5 = 0$$

$$v_0 = \frac{15 \pm \sqrt{(15)^2 - 4(2)(5)}}{2(2)} \Rightarrow v_0 = 0.35 \text{ V}$$

$$i_D = \frac{5-0.35}{20} = 0.2325 \text{ mA}$$

$$P = i_D \cdot V_{DD} = (0.2325)(5) \Rightarrow P = 1.16 \text{ mW}$$

$$b. \quad i. \quad v_I = 0.25 \text{ V} \Rightarrow i_D = 0 \Rightarrow P = 0$$

$$ii. \quad v_I = 4.3 \text{ V, From Equation (16.23),}$$

$$100[2(4.3-0.7)v_0 - v_0^2] = 10[5 - v_0 - 0.7]^2$$

$$10[7.2v_0 - v_0^2] = 18.49 - 8.6v_0 + v_0^2$$

Then

$$11v_0^2 - 80.6v_0 + 18.49 = 0$$

$$v_0 = \frac{80.6 \pm \sqrt{(80.6)^2 - 4(11)(18.49)}}{2(11)}$$

$$\Rightarrow v_0 = 0.237 \text{ V}$$

Then

$$i_D = 10[5 - 0.237 - 0.7]^2 = 165 \mu\text{A}$$

$$P = i_D \cdot V_{DD} = (165)(5) \Rightarrow P = 825 \mu\text{W}$$

$$c. \quad i. \quad v_I = 0.03 \text{ V} \Rightarrow i_D = 0 \Rightarrow P = 0$$

$$ii. \quad v_I = 5 \text{ V}$$

$$i_D = K_L(-V_{TNL})^2 = (10)[-(-2)]^2 = 40 \mu\text{A}$$

$$P = i_D \cdot V_{DD} = (40)(5) \Rightarrow P = 200 \mu\text{W}$$

16.15

From Equation (16.35)

$$V_{IH} = 0.8 + \frac{5 - (0.8)}{10} \cdot \left\{ \frac{1 + 2(10)}{\sqrt{1 + 3(10)}} - 1 \right\}$$

$$V_{IH} = 0.8 + 0.42 \cdot \left\{ \frac{21}{5.57} - 1 \right\}$$

or

$$V_{IH} = 1.96 \text{ V}$$

 M_{D2} in non-saturation region. Then

$$K_D[2(v_{GS2} - V_{TN})v_{DS2} - v_{DS2}^2]$$

$$= K_L[V_{DD} - v_{O2} - V_{TN}]^2$$

$$v_{DS2} = v_{O2} \text{ and } v_{GS2} = V_{IH} = 1.96$$

$$10[2(1.96-0.8)v_{O2} - v_{O2}^2] = [5 - v_{O2} - 0.8]^2$$

$$23.2v_{O2} - 10v_{O2}^2 = 17.64 - 8.4v_{O2} + v_{O2}^2$$

or

$$11v_{O2}^2 - 31.6v_{O2} + 17.64 = 0$$

$$v_{O2} = \frac{31.6 \pm \sqrt{(31.6)^2 - 4(11)(17.64)}}{2(11)}$$

$$\Rightarrow v_{O2} = 0.758 \text{ V}$$

Now M_{D1} in saturation region. Then

$$K_D[v_I - V_{TN}]^2 = K_L[V_{DD} - v_{O1} - V_{TN}]^2$$

$$\sqrt{10} \cdot (v_I - 0.8) = 5 - 1.96 - 0.8 = 2.24$$

$$\text{Then } \underline{v_I = 1.51 \text{ V}}$$

16.16

a. From Equation (16.41),

$$V_{IH} = 0.8 + \frac{2(-(-2))}{\sqrt{3(4)}} \Rightarrow \underline{V_{IH} = 1.95 \text{ V} = v_{O1}}$$

M_{D2} in non-saturation and M_{L2} in saturation.

$$K_D[2(v_{O1} - V_{TN0})v_{O2} - v_{O2}^2] = K_L(-V_{TNL})^2$$

$$4[2(1.95 - 0.8)v_{O2} - v_{O2}^2] = (1)[-(-2)]^2$$

$$4v_{O2}^2 - 9.2v_{O2} + 4 = 0$$

$$v_{O2} = \frac{9.2 \pm \sqrt{(9.2)^2 - 4(4)(4)}}{2(4)} \Rightarrow \underline{v_{O2} = 0.582 \text{ V}}$$

Both M_{D1} and M_{L1} in saturation region. From Equation (16.2B(b)).

$$\sqrt{4} \cdot (v_I - 0.8) = -(-2)$$

$$\text{or } \underline{v_I = 1.8 \text{ V}}$$

$$\text{b. } V_{IL} = 0.8 + \frac{(+2)}{\sqrt{4(1+4)}} = 1.25 \text{ V} = v_{O1}$$

M_{D2} in saturation, M_{L2} in non-saturation

$$K_D[v_{O1} - V_{TN0}]^2 = K_L[2(-V_{TNL})(5 - v_{O2}) - (5 - v_{O2})^2]$$

$$4(1.25 - 0.8)^2 = 2(2)(5 - v_{O2}) - (5 - v_{O2})^2$$

$$(5 - v_{O2})^2 - 4(5 - v_{O2}) + 0.81 = 0$$

$$5 - v_{O2} = \frac{4 \pm \sqrt{(4)^2 - 4(1)(0.81)}}{2(1)} = 0.214 \text{ V}$$

so

$$\underline{v_{O2} = 4.786 \text{ V}}$$

To find v_I :

$$4(v_{O1} - 0.8)^2 = (1)(-(-2))^2$$

$$v_{O1} - 0.8 = 1$$

$$\underline{v_{O1} = 1.8 \text{ V}}$$

$$\text{c. } \underline{V_{IH} = 1.95 \text{ V}, V_{IL} = 1.25 \text{ V}}$$

16.17

a. i. Neglecting the body effect,

$$v_O = V_{DD} - V_{TN}$$

$$\text{Assume } V_{DD} = 5 \text{ V, then } \underline{v_O = 4.2 \text{ V}}$$

ii. Taking the body effect into account:
From Problem 16.1,

$$V_{TN} = V_{TN0} + 0.671[\sqrt{0.686 + V_{SB}} - \sqrt{0.686}]$$

$$\text{and } V_{SB} = v_O$$

Then

$$v_O = 5 - [0.8 + 0.671(\sqrt{0.686 + v_O} - \sqrt{0.686})]$$

$$v_O = 4.756 - 0.671\sqrt{0.686 + v_O}$$

$$0.671\sqrt{0.686 + v_O} = 4.756 - v_O$$

$$0.450(0.686 + v_O) = 22.62 - 9.51v_O + v_O^2$$

$$v_O^2 - 9.96v_O + 22.3 = 0$$

$$v_O = \frac{9.96 \pm \sqrt{(9.96)^2 - 4(22.3)}}{2} \Rightarrow \underline{v_O = 3.40 \text{ V}}$$

b. PSpice results similar to Figure 16.18(a).

16.18

Results similar to Figure 16.18(b).

16.19

a. M_X on, M_Y cutoff.

From Equation (16.29(b)):

$$\frac{K_D}{K_L}[2(5 - 0.8)(0.2) - (0.2)^2] = [-(-2)]^2$$

$$\text{or } \underline{\frac{K_D}{K_L} = 2.44}$$

b. For $v_X = v_Y = 5 \text{ V}$

$$2(2.44)[2(5 - 0.8)v_O - v_O^2] = [-(-2)]^2$$

$$4.88v_O^2 - 41.0v_O + 4 = 0$$

$$v_O = \frac{41 \pm \sqrt{(41)^2 - 4(4.88)(4)}}{2(4.88)}$$

or

$$\underline{v_O = 0.0987 \text{ V}}$$

$$\text{c. } i_D = \left(\frac{80}{2}\right)(1)[-(-2)]^2 = 160 \mu\text{A}$$

$$P = (160)(5) \Rightarrow \underline{P = 800 \mu\text{W}}$$

for both parts (a) and (b).

16.20

- (a) Maximum value of v_o in low state- when only one input is high, then,

$$\frac{K_D}{K_L} [2(3-0.5)(0.1) - (0.1)^2] = [-(-1)]^2$$

$$\frac{K_D}{K_L} = 2.04$$

(b) $P = i_D \cdot V_{DD}$

$$0.1 = i_D(3) \Rightarrow i_D = 33.3 \mu A$$

$$i_D = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_L (-V_{TNL})^2$$

$$33.3 = \left(\frac{80}{2} \right) \left(\frac{W}{L} \right)_L [-(-1)]^2 \Rightarrow \left(\frac{W}{L} \right)_L = 0.8325$$

Then $\left(\frac{W}{L} \right)_D = 1.70$

(c) $3(2.04)[2(3-0.5)v_o - v_o^2] = [-(-1)]^2 \Rightarrow$
 $v_o = 0.0329 V$

16.21

a. $P = i_D \cdot V_{DD}$

$$250 = i_D(5) \Rightarrow i_D = 50 \mu A$$

$$i_D = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_{ML1} [-V_{TNL1}]^2$$

$$50 = \left(\frac{60}{2} \right) \left(\frac{W}{L} \right)_{ML1} [-(-2)]^2$$

So that $\left(\frac{W}{L} \right)_{ML1} = 0.417$

$$\frac{K_D}{K_L} [2(v_i - V_{TN0})v_o - v_o^2] = [-V_{TNL}]^2$$

$$\frac{K_D}{K_L} [2(5-0.8)(0.15) - (0.15)^2] = [-(-2)]^2$$

or $\frac{K_D}{K_L} = 3.23 \Rightarrow \left(\frac{W}{L} \right)_{MD1} = 1.35$

b. For $v_X = v_Y = 0 \Rightarrow v_{01} = 5$ and $v_{03} = 4.2$

Then

$$K_{D2} [2(v_{01} - V_{TN0})v_{02} - v_{02}^2]$$

$$+ K_{D3} [2(v_{03} - V_{TN0})v_{02} - v_{02}^2] = K_{L2} [-V_{TNL2}]^2$$

$$K_{D2} \propto 8, K_{D3} \propto 8, K_{L2} \propto 1$$

$$8[2(5-0.8)v_{02} - v_{02}^2] + 8[2(4.2-0.8)v_{02} - v_{02}^2] = (1)[-(-2)]^2$$

$$67.2v_{02} - 8v_{02}^2 + 54.4v_{02} - 8v_{02}^2 = 4$$

Then

$$16v_{02}^2 - 121.6v_{02} + 4 = 0$$

$$v_{02} = \frac{121.6 \pm \sqrt{(121.6)^2 - 4(16)(4)}}{2(16)}$$

So $v_{02} = 0.0330 V$

16.22

- a. We can write

$$\begin{aligned} K_x [2(v_x - V_{TN})v_{DSX} - v_{DSX}^2] \\ = K_y [2(v_y - v_{DSY} - V_{TN})v_{DSY} - v_{DSY}^2] \\ = K_L [V_{DD} - v_o - V_{TN}]^2 \end{aligned}$$

where $v_o = v_{DSX} + v_{DSY}$

We have

$$v_x = v_y = 9.2 V, V_{DD} = 10 V, V_{TN} = 0.8 V$$

As a good first approximation, neglect the v_{DSX}^2 and v_{DSY}^2 terms. Let $v_o \approx 2v_{DSX}$. Then from the first and third terms in the above equation,

$$9[2(9.2 - 0.8)v_{DSX}] \approx (1)(10 - 2v_{DSX} - 0.8)^2$$

$$(151.2)v_{DSX} \approx 84.64 - 36.8v_{DSX}$$

So that $v_{DSX} = 0.450 V$

From the first and second terms of the above equation,

$$9[2(9.2 - 0.8)v_{DSX}] \approx 9[2(9.2 - v_{DSX} - 0.8)v_{DSY}]$$

or

$$(16.8)(0.45) = 2(9.2 - 0.45 - 0.8)v_{DSY}$$

which yields $v_{DSY} = 0.475 V$

Then $v_o = v_{DSX} + v_{DSY} = 0.450 + 0.475$

or $v_o = 0.925 V$

We have $v_{GSX} = 9.2 V$

and $v_{GSY} = 9.2 - v_{DSX} = 9.2 - 0.45$

or $v_{GSY} = 8.75 V$

- b. Since v_o is close to ground potential, the body effect will have minimal effect on the results.

From a PSpice analysis:

For part (a) :

$$v_{DSX} = 0.462 V, v_{DSY} = 0.491 V, v_o = 0.9536 V,$$

$$v_{GSX} = 9.2 V, \text{ and } v_{GSY} = 8.738 V$$

For part (b) :

$$v_{DSX} = 0.441 V, v_{DSY} = 0.475 V, v_o = 0.9154 V,$$

$$v_{GSX} = 9.2 V, \text{ and } v_{GSY} = 8.759 V$$

16.23

a. We can write

$$\begin{aligned} K_x [2(v_x - V_{thx})v_{DSX} - v_{DSX}^2] \\ = K_y [2(v_y - v_{DSY} - V_{thY})v_{DSY} - v_{DSY}^2] \\ = K_L [-V_{thL}]^2 \end{aligned}$$

 From the first and third terms, (neglect v_{DSX}^2).

$$4[2(5 - 0.8)v_{DSX}] = (1)[-(-1.5)]^2$$

$$\text{or } v_{DSX} = 0.067 \text{ V}$$

 From the second and third terms, (neglect v_{DSY}^2).

$$4[2(5 - 0.067 - 0.8)v_{DSY}] = (1)[-(-1.5)]^2$$

$$\text{or } v_{DSY} = 0.068 \text{ V}$$

Now

$$v_{GSX} = 5, v_{GSY} = 5 - 0.067 \Rightarrow v_{GSY} = 4.933 \text{ V}$$

$$\text{and } v_0 = v_{DSX} + v_{DSY} \Rightarrow v_0 = 0.135 \text{ V}$$

 Since v_0 is close to ground potential, the body-effect has little effect on the results.

16.24

$$\text{Complement of (B AND C) OR A} \Rightarrow \overline{(B \cdot C) + A}$$

16.25


Considering a truth table, we find

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

which shows that the circuit performs the exclusive-OR function.

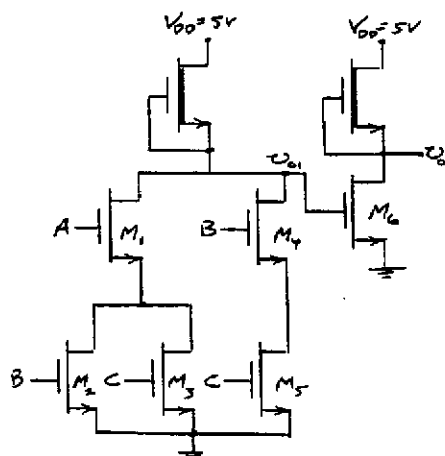16.26

$$(a) \text{ Carry-out} = A \cdot (B + C) + B \cdot C$$



$$(b) \text{ For } v_{01} = \text{Low} = 0.2 \text{ V}$$

$$\frac{K_p}{K_L} [2(5 - 0.8)(0.2) - (0.2)^2] = [-(-1.5)]^2 \Rightarrow$$

$$\text{For } \left(\frac{W}{L} \right)_L = 1, \text{ then } \left(\frac{W}{L} \right)_D = 1.37$$

$$\text{So, for } M_6: \left(\frac{W}{L} \right)_6 = 1.37$$

To achieve the required composite conduction parameter,

$$\text{For } M_1 - M_5: \left(\frac{W}{L} \right)_{1-5} = 2.74$$

16.28

a. From Equation (16.55),

$$v_I = V_{It} = \frac{5 - 0.8 + 0.8}{1 + 1} = V_{It} = 2.5 \text{ V}$$

$$p\text{-channel, } V_{0Pt} = 2.5 - (-0.8) \Rightarrow V_{0Pt} = 3.3 \text{ V}$$

$$n\text{-channel, } V_{0Nt} = 2.5 - 0.8 \Rightarrow V_{0Nt} = 1.7 \text{ V}$$

 c. For $v_I = 2 \text{ V}$, NMOS in saturation and PMOS in nonsaturation. From Equation (16.49),

$$(2 - 0.8)^2 = [2(5 - 2 - 0.8)(5 - v_0) - (5 - v_0)^2]$$

$$1.44 = 4.4(5 - v_0) - (5 - v_0)^2$$

$$\text{So } (5 - v_0)^2 - 4.4(5 - v_0) + 1.44 = 0$$

$$(5 - v_0) = \frac{4.4 \pm \sqrt{(4.4)^2 - 4(1)(1.44)}}{2}$$

or

$$5 - v_0 = 0.356 \Rightarrow v_0 = 4.64 \text{ V}$$

$$\text{By symmetry, for } v_I = 3 \text{ V, } v_0 = 0.356 \text{ V}$$

16.29

$$(a) K_n = \left(\frac{80}{2} \right) (2) = 80 \mu\text{A/V}^2$$

$$K_p = \left(\frac{40}{2} \right) (4) = 80 \mu\text{A/V}^2$$

$$(i) V_n = \frac{V_{DD} + V_{TP} + \sqrt{\frac{K_n}{K_p}} \cdot V_{TN}}{1 + \sqrt{\frac{K_n}{K_p}}} = \frac{3.3 - 0.4 + (1)(0.4)}{1 + 1}$$

$$V_n = 1.65 \text{ V}$$

PMOS:

$$V_{\alpha} = V_n - V_{TP} = 1.65 - (-0.4) \Rightarrow V_{\alpha} = 2.05 \text{ V}$$

NMOS:

$$V_{\alpha} = V_n - V_{TN} = 1.65 - (0.4) \Rightarrow V_{\alpha} = 1.25 \text{ V}$$

(iii) For $v_o = 0.4\text{ V}$: NMOS: Non-sat; PMOS: Sat

$$K_n[2(V_{GSV} - V_{TN})V_{DS} - V_{DS}^2] = K_p[V_{SDP} + V_{TP}]^2$$

$$2(v_i - 0.4)(0.4) - (0.4)^2 = (3.3 - v_i - 0.4)^2 \Rightarrow$$

$$v_i = 1.89\text{ V}$$

For $v_o = 2.9\text{ V}$, By symmetry

$$v_i = 1.65 - (1.89 - 1.65) \Rightarrow v_i = 1.41\text{ V}$$

$$(b) K_n = \left(\frac{80}{2}\right)(2) = 80\ \mu\text{A/V}^2$$

$$K_p = \left(\frac{40}{2}\right)(2) = 40\ \mu\text{A/V}^2$$

$$(i) V_n = \frac{3.3 - 0.4 + \sqrt{\frac{80}{40} \cdot (0.4)}}{1 + \sqrt{\frac{80}{40}}} \Rightarrow V_n = 1.44\text{ V}$$

PMOS:

$$V_{\alpha} = 1.44 - (-0.4) \Rightarrow V_{\alpha} = 1.84\text{ V}$$

NMOS:

$$V_{\alpha} = 1.44 - 0.4 \Rightarrow V_{\alpha} = 1.04\text{ V}$$

(iii) For $v_o = 0.4\text{ V}$

$$(80)[2(v_i - 0.4)(0.4) - (0.4)^2] = (40)[3.3 - v_i - 0.4]^2$$

$$\Rightarrow v_i = 1.62\text{ V}$$

For $v_o = 2.9\text{ V}$: NMOS: Sat, PMOS: Non-sat

$$(80)(v_i - 0.4)^2 = (40)[2(3.3 - v_i - 0.4)(0.4) - (0.4)^2]$$

$$\Rightarrow v_i = 1.16\text{ V}$$

16.30

a. For $v_{o1} = 0.6 < V_{TN} \Rightarrow v_{o2} = 5\text{ V}$ N_1 in nonsaturation and P_1 in saturation. From Equation (16.57),

$$[2(v_i - 0.8)(0.6) - (0.6)^2] = [5 - v_i - 0.8]^2$$

$$1.2v_i - 1.32 = 17.64 - 8.4v_i + v_i^2$$

or

$$v_i^2 - 9.6v_i + 18.96 = 0$$

$$v_i = \frac{9.6 \pm \sqrt{(9.6)^2 - 4(1)(18.96)}}{2}$$

or

$$v_i = 2.78\text{ V}$$

b. $V_{oNt} \leq v_{o2} \leq V_{oPt}$ From symmetry, $V_{It} = 2.5\text{ V}$

$$V_{oPt} = 2.5 + 0.8 = 3.3\text{ V}$$

$$\text{and } V_{oNt} = 2.5 - 0.8 = 1.7\text{ V}$$

$$\text{So } 1.7 \leq v_{o2} \leq 3.3\text{ V}$$

16.31

$$a. V_{oNt} \leq v_{o1} \leq V_{oPt}$$

By symmetry, $V_{It} = 2.5\text{ V}$

$$V_{oPt} = 2.5 + 0.8 = 3.3\text{ V}$$

$$\text{and } V_{oNt} = 2.5 - 0.8 = 1.7\text{ V}$$

$$\text{So } 1.7 \leq v_{o1} \leq 3.3\text{ V}$$

b. For $v_{o2} = 0.6 < V_{TN} \Rightarrow v_{o1} = 5\text{ V}$ N_2 in nonsaturation and P_2 in saturation. From Equation (16.57),

$$[2(v_{i2} - 0.8)(0.6) - (0.6)^2] = [5 - v_{i2} - 0.8]^2$$

$$1.2v_{i2} - 1.32 = 17.64 - 8.4v_{i2} + v_{i2}^2$$

or

$$v_{i2}^2 - 9.6v_{i2} + 18.96 = 0$$

$$\text{So } v_{i2} = v_{o1} = 2.78\text{ V}$$

For $v_{o1} = 2.78$, both N_1 and P_1 in saturation. Then


$$v_i = 2.5\text{ V}$$

16.32

$$a. \sqrt{i_{peak}} = \sqrt{K_n}(v_i - V_{TN})$$

$$\sqrt{i_{peak}} = \sqrt{0.1} \cdot (2.5 - 0.8) = 0.538\text{ (mA)}^{1/2}$$
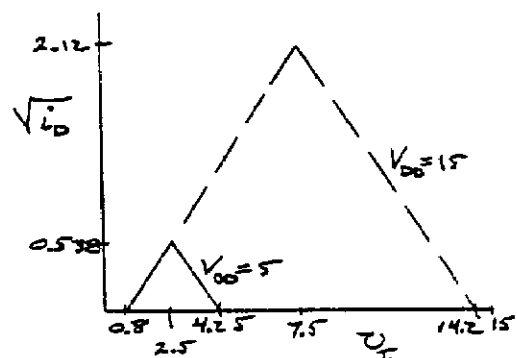
$$b. \sqrt{i_{peak}} = \sqrt{0.1} \cdot (7.5 - 0.8) = 2.12\text{ (mA)}^{1/2}$$



16.33

$$(a) K_n = \left(\frac{50}{2}\right)(2) = 50\ \mu\text{A/V}^2$$

$$K_p = \left(\frac{25}{2}\right)(4) = 50\ \mu\text{A/V}^2$$

$$I_{D,peak} = K_n(v_i - V_{TN})^2 = 50(2.5 - 0.8)^2$$

$$\text{or } I_{D,peak} = 144.5\ \mu\text{A}$$

(b) $K_n = 50 \mu A/V^2$, $K_p = 25 \mu A/V^2$

From Equation (16.55),

$$V_{th} = \frac{5 - 0.8 + \sqrt{\frac{50}{25}(0.8)}}{1 + \sqrt{\frac{50}{25}}} = 2.21 V$$

Then

$$I_{D, peak} = K_n(V_{th} - V_{TN})^2 = 50(2.21 - 0.8)^2$$

$$\text{or } I_{D, peak} = 99.4 \mu A$$

16.34

a. $P = f C_L V_{DD}^2$

For $V_{DD} = 5 V$, $P = (10 \times 10^6)(0.2 \times 10^{-12})(5)^2$

$$\text{or } P = 50 \mu W$$

For $V_{DD} = 15 V$, $P = (10 \times 10^6)(0.2 \times 10^{-12})(15)^2$

$$\text{or } P = 450 \mu W$$

b. For $V_{DD} = 5 V$, $P = (10 \times 10^6)(0.2 \times 10^{-12})(5)^2$

$$\text{or } P = 50 \mu W$$

16.35

(a) $P = f C_L V_{DD}^2 = (150 \times 10^6)(0.4 \times 10^{-12})(5)^2$
 $= 15 \times 10^{-3} \text{ W/inverter}$

Total power: $P_T = (2 \times 10^6)(15 \times 10^{-3}) \Rightarrow$
 $P_T = 3000 \text{ W!!!!}$

(b) For $f = 300 \text{ MHz}$

$$15 \times 10^{-3} = (300 \times 10^6)(0.4 \times 10^{-12})V_{DD}^2 \Rightarrow$$

$$V_{DD} = 3.54 V$$

16.36

(a) For $v_i \equiv V_{DD}$, NMOS in nonsaturation

$$i_D = K_n[2(v_i - V_{TN})v_{DS} - v_{DS}^2] \text{ and } v_{DS} \equiv 0$$

$$\text{So } \frac{1}{r_{ds}} = \frac{di_D}{dv_{DS}} \equiv K_n[2(V_{DD} - V_{TN})]$$

Or

$$r_{ds} = \frac{1}{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_n \cdot 2(V_{DD} - V_{TN})}$$

or

$$r_{ds} = \frac{1}{k'_n\left(\frac{W}{L}\right)_n \cdot (V_{DD} - V_{TN})}$$

For $v_i \equiv 0$, PMOS in nonsaturation

$$i_D = K_p[2(V_{DD} - v_i + V_{TP})v_{SD} - v_{SD}^2]$$

and $v_{SD} \equiv 0$ for $v_i \equiv 0$.

So

$$\frac{1}{r_{sd}} = \frac{di_D}{dv_{SD}} \equiv \left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)_p \cdot 2(V_{DD} + V_{TP})$$

or

$$r_{sd} = \frac{1}{k'_p\left(\frac{W}{L}\right)_p \cdot (V_{DD} + V_{TP})}$$

(b) For $\left(\frac{W}{L}\right)_n = 2$, $\left(\frac{W}{L}\right)_p = 4$

$$r_{sd} = \frac{1}{(50)(2)(5 - 0.8)} \Rightarrow r_{sd} = 2.38 \text{ k}\Omega$$

$$r_{sd} = \frac{1}{(25)(4)(5 - 0.8)} \Rightarrow r_{sd} = 2.38 \text{ k}\Omega$$

For $\left(\frac{W}{L}\right)_p = 2$,

$$r_{sd} = \frac{1}{(25)(2)(5 - 0.8)} \Rightarrow r_{sd} = 4.76 \text{ k}\Omega$$

Now, for NMOS:

$$v_{ds} = i_d r_{ds} \text{ or } i_d = \frac{v_{ds}}{r_{ds}} = \frac{0.5}{2.38} \Rightarrow i_d = 0.21 \text{ mA}$$

For PMOS:

For $r_{sd} = 2.38 \text{ k}\Omega$,

$$i_d = \frac{v_{sd}}{r_{sd}} = \frac{0.5}{2.38} \Rightarrow i_d = 0.21 \text{ mA}$$

For $r_{sd} = 4.76 \text{ k}\Omega$,

$$i_d = \frac{v_{sd}}{r_{sd}} = \frac{0.5}{4.76} \Rightarrow i_d = 0.105 \text{ mA}$$

16.37

From Equation (16.73)

$$V_{IL} = 1.5 + \frac{3}{8} \cdot (10 - 1.5 - 1.5) \Rightarrow V_{IL} = 4.125 V$$

and Equation (16.72)

$$V_{OHV} = \frac{1}{2} \cdot [2(4.125) + 10 - 1.5 + 1.5]$$

$$\text{or } V_{OHV} = 9.125 V$$

From Equation (16.79)

$$V_{IH} = 1.5 + \frac{5}{8} \cdot (10 - 1.5 - 1.5) \Rightarrow V_{IH} = 5.875 V$$

and Equation (16.78)

$$V_{OLV} = \frac{1}{2} \cdot [2(5.875) - 10 - 1.5 + 1.5]$$

$$\text{or } V_{OLV} = 0.875 V$$

Now

$$NM_L = V_{IL} - V_{OLU} = 4.125 - 0.875$$

$$\Rightarrow NM_L = 3.25 \text{ V}$$

$$NM_H = V_{OHU} - V_{TH} = 9.125 - 5.875$$

$$\Rightarrow NM_H = 3.25 \text{ V}$$

16.38

From Equation (16.71)

$$V_{IL} = 1.5 + \frac{(10 - 1.5 - 1.5)}{\left(\frac{100}{50} - 1\right)} \left[2 \sqrt{\frac{\frac{100}{50}}{\frac{100}{50} + 3}} - 1 \right]$$

$$= 1.5 + 7[2(0.632) - 1]$$

or

$$V_{IL} = 3.348 \text{ V}$$

From Equation (16.70)

$$V_{OHU} = \frac{1}{2} \cdot \left\{ \left(1 + \frac{100}{50} \right) (3.348) + 10 \right. \\ \left. - \left(\frac{100}{50} \right) (1.5) + 1.5 \right\}$$

$$\text{or } V_{OHU} = 9.272 \text{ V}$$

From Equation (16.77)

$$V_{IH} = 1.5 + \frac{(10 - 1.5 - 1.5)}{\left(\frac{100}{50} - 1\right)} \left[\frac{2 \left(\frac{100}{50}\right)}{\sqrt{3 \left(\frac{100}{50}\right) + 1}} - 1 \right]$$

$$= 1.5 + 7[1.51 - 1]$$

or

$$V_{IH} = 5.07 \text{ V}$$

From Equation (16.76)

$$V_{OLU} = \frac{(5.07) \left(1 + \frac{100}{50} \right) - 10 - \left(\frac{100}{50} \right) (1.5) + 1.5}{2 \left(\frac{100}{50} \right)}$$

$$\text{or } V_{OLU} = 0.9275 \text{ V}$$

$$\text{Now } NM_L = V_{IL} - V_{OLU} = 3.348 - 0.9275$$

$$\text{or } NM_L = 2.42 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 9.272 - 5.07$$

$$\text{or } NM_H = 4.20 \text{ V}$$

16.39

$$\text{a. } v_A = v_B = 5 \text{ V}$$

$$N_1 \text{ and } N_2 \text{ on, so } v_{DS1} \approx v_{DS2} \approx 0 \text{ V}$$

$$P_1 \text{ and } P_2 \text{ off}$$

So we have a $P_3 - N_3$ CMOS inverter. By symmetry,
 $v_C = 2.5 \text{ V}$ (Transition Point).

$$\text{b. For } v_A = v_B = v_C \equiv v_i$$

$$\text{Want } K_{n, \text{eff}} = K_{p, \text{eff}}$$

$$\frac{k'_n}{2} \cdot \left(\frac{W}{3L} \right)_n = \frac{k'_p}{2} \cdot \left(\frac{3W}{L} \right)_p$$

With $k'_n = 2k'_p$, then

$$\frac{2}{2} \cdot \frac{1}{3} \cdot \left(\frac{W}{L} \right)_n = \frac{1}{2} \cdot 3 \cdot \left(\frac{W}{L} \right)_p$$

$$\text{Or } \left(\frac{W}{L} \right)_n = \frac{9}{2} \cdot \left(\frac{W}{L} \right)_p$$

c. We have

$$K_n = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right)_n = \left(\frac{2k'_p}{2} \right) \left(\frac{9}{2} \right) \left(\frac{W}{L} \right)_p$$

$$K_p = \left(\frac{k'_p}{2} \right) \left(\frac{W}{L} \right)_p$$

Then from Equation (16.55)

$$V_n = \frac{5 + (-0.8) + \sqrt{\frac{K_n}{K_p}} \cdot (0.8)}{1 + \sqrt{\frac{K_n}{K_p}}}$$

Now

$$\frac{K_n}{K_p} = (2) \left(\frac{9}{2} \right) = 9$$

Then

$$V_n = \frac{5 + (-0.8) + 3(0.8)}{1 + 3} \Rightarrow V_n = 1.65 \text{ V}$$

16.40

By definition, NMOS is on if gate voltage is 5 V and is off if gate voltage is 0 V.


State	N_1	N_2	N_3	N_4	N_5	v_o
1	off	on	off	on	on	0
2	off	off	on	on	off	0
3	on	on	off	off	on	5
4	on	on	off	on	on	0

Logic function $(v_X \text{ OR } v_Y) \otimes (v_X \text{ AND } v_Z)$

Exclusive OR of $(v_X \text{ OR } v_Y)$ with $(v_X \text{ AND } v_Z)$

16.41

(a) A classic design is shown:

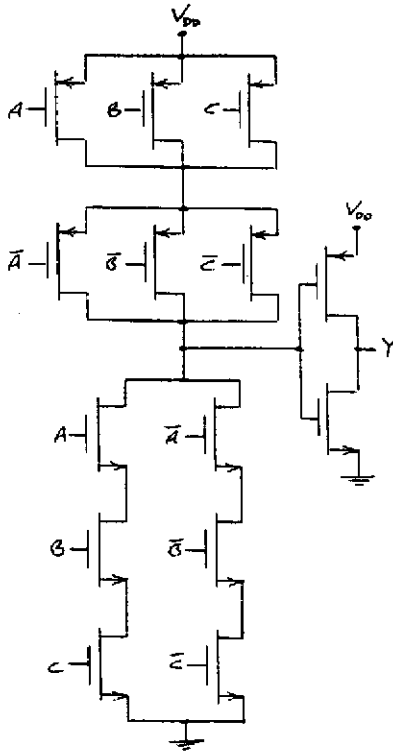

$\bar{A}, \bar{B}, \bar{C}$ signals supplied through inverters.


(b) For Inverters, $\left(\frac{W}{L}\right)_n = 1$ and $\left(\frac{W}{L}\right)_p = 2$

For PMOS in Logic function, let $\left(\frac{W}{L}\right)_p = 1$, then

for NMOS in Logic function, $\left(\frac{W}{L}\right)_n = 2.25$

16.42

(a) A classic design is shown:

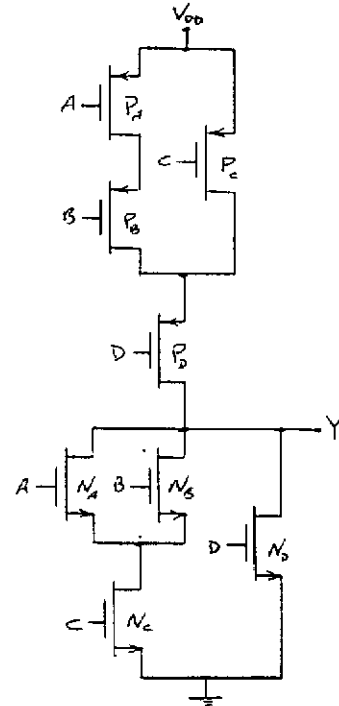

(b) $\left(\frac{W}{L}\right)_{ND} = 1$, $\left(\frac{W}{L}\right)_{NA, NB, NC} = 2$

$\left(\frac{W}{L}\right)_{PA, PB} = 8$, $\left(\frac{W}{L}\right)_{PC, PD} = 4$

16.43

$$\overline{(A \text{ OR } B) \text{ AND } C}$$

16.44

Let $\left(\frac{W}{L}\right)_p = 1$ for each PMOS: Composite PMOS

$\left(\frac{W}{L}\right)_n = 5$. Want composite $\left(\frac{W}{L}\right)_n = 2.5$ for NMOS,

So that $\left(\frac{W}{L}\right)_n = 5(2.5) = 12.5$ for each NMOS.

16.45

(a) Let $\left(\frac{W}{L}\right)_n = 1$ for each NMOS. Composite $\left(\frac{W}{L}\right)$

of NMOS = 6. Want composite $\left(\frac{W}{L}\right)$ of PMOS =

12. Then $\left(\frac{W}{L}\right)_p = 6(12) = 72$ for each PMOS. Let

$\left(\frac{W}{L}\right)_n = 1$ and $\left(\frac{W}{L}\right)_p = 2$ for each transistor in

inverter.

(a) For 3-input NOR:

Let $\left(\frac{W}{L}\right)_n = 1$ for each NMOS. Composite $\left(\frac{W}{L}\right)$ of

NMOS = 3. Want composite $\left(\frac{W}{L}\right)$ of PMOS = 6.

Then $\left(\frac{W}{L}\right)_p = 3(6) = 18$ for each PMOS.

For 2-input NAND:

Let $\left(\frac{W}{L}\right)_p = 1$ for each PMOS. Composite $\left(\frac{W}{L}\right)$ of

PMOS = 2. Want composite $\left(\frac{W}{L}\right)$ of NMOS = 1.

Then $\left(\frac{W}{L}\right)_n = 2$ for each NMOS.

Sizes of PMOS transistors in (b) are substantially less than those in (a).

16.46

By definition:

NMOS off if gate voltage = 0

NMOS on if gate voltage = 5 V

PMOS off if gate voltage = 5 V

PMOS on if gate voltage = 0

State	N_1	P_1	N_A	N_B	N_C	v_{01}	N_2	P_2	v_{02}
1	off	on	off	off	off	5	on	off	0
2	on	off	on	off	off	5	on	off	0
3	off	on	off	off	off	5	on	off	0
4	on	off	off	off	on	5	on	off	0
5	off	on	off	off	off	5	on	off	0
6	on	off	off	on	on	0	off	on	5

Logic function is

$$v_{02} = (v_A \text{ OR } v_B) \text{ AND } v_C$$


16.47

State	v_{01}	v_{02}	v_{03}
1	5	5	0
2	0	0	5
3	5	5	0
4	5	0	5
5	5	5	0
6	0	5	0


Logic function:

$$v_{03} = (v_X \text{ OR } v_Z) \text{ AND } v_Y$$


16.48

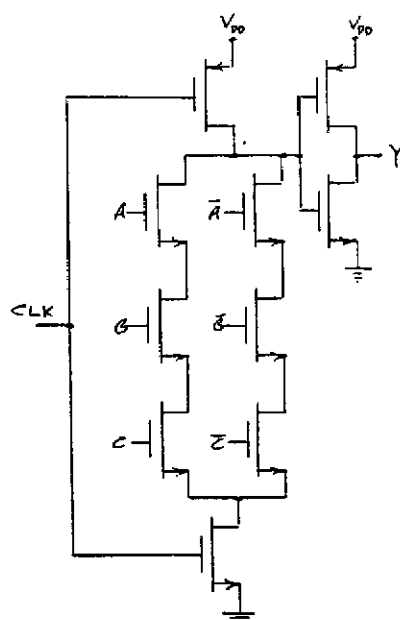

16.49

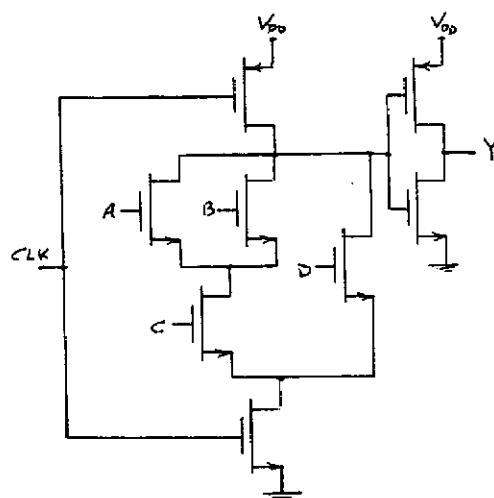

16.50

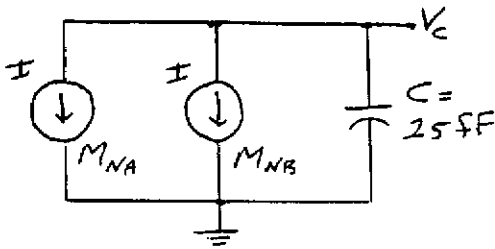

$$2I = -C \frac{dV_c}{dt}$$

So

$$\Delta V_c = -\frac{1}{C}(2I) \cdot t$$

$$\text{For } \Delta V_c = -0.5 \text{ V}$$

$$-0.5 = -\frac{2(2 \times 10^{-12}) \cdot t}{25 \times 10^{-15}} \Rightarrow t = 3.125 \text{ ms}$$

16.51

- (a)
 (i) $v_o = 0$
 (ii) $v_o = 4.2 \text{ V}$
 (iii) $v_o = 2.5 \text{ V}$

- (b)
 (i) $v_o = 0$
 (ii) $v_o = 3.2 \text{ V}$
 (iii) $v_o = 2.5 \text{ V}$

16.52

Neglect the body effect.

$$\text{a. } v_{o1}(\text{logic 1}) = 4.2 \text{ V, } v_{o2}(\text{logic 1}) = 5 \text{ V}$$

$$\text{b. } v_I = 5 \text{ V} \Rightarrow v_{GS1} = 4.2 \text{ V}$$

M_1 in nonsaturation and M_2 in saturation. From Equation (16.23)

$$\left(\frac{W}{L}\right)_D [2(v_{GS1} - V_{TND})v_{o1} - v_{o1}^2] = \left(\frac{W}{L}\right)_L (V_{DD} - v_{o1} - V_{TnL})^2$$

$$\left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.1) - (0.1)^2] = (1)[5 - 0.1 - 0.8]^2$$

Or

$$\left(\frac{W}{L}\right)_D (0.67) = 16.81 \Rightarrow \left(\frac{W}{L}\right)_D = 25.1$$

Now

$$v_{o1} = 4.2 \text{ V} \Rightarrow v_{GS2} = 4.2 \text{ V}$$

M_3 in nonsaturation and M_4 in saturation. From Equation (16.29(b)).

$$\left(\frac{W}{L}\right)_D [2(v_{GS3} - V_{TND})v_{o2} - v_{o2}^2] = \left(\frac{W}{L}\right)_L [-V_{TnL}]^2$$

$$\left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.1) - (0.1)^2] = (2)[-(-1.5)]^2$$

$$\left(\frac{W}{L}\right)_D (0.67) = 2.25$$

$$\text{Or } \left(\frac{W}{L}\right)_D = 3.36$$

16.53

For $\phi = 1$, $\bar{\phi} = 0$, then $Y = B$. And for $\phi = 0$, $\bar{\phi} = 1$, then $Y = A$.

A multiplexer.

16.54

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0, 1 \Rightarrow indeterminate

Without the top transistor, the circuit performs the exclusive-NOR function.

16.55

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	0

Exclusive-OR function.

16.56

This circuit is referred to as a ratioless circuit. Identical minimum-sized transistors can be used throughout.

When ϕ_1 is low, C_3 is charged to V_{DD} . Then when ϕ_1 is high and ϕ_2 is low, M_6 turns on. If $A = B = 0$, then M_3 and M_4 are off so C_3 remains charged and v_{o1} is high. When ϕ_2 goes high, then v_{o1} is applied to the gates of M_9 and M_{10} . The circuit performs the OR logic function.

16.57

This circuit is referred to as a two-phase ratioed circuit. The same width-to-length ratios between the driver and load transistors must be maintained as discussed previously with the enhancement load inverter.

When ϕ_1 is high, v_{o1} becomes the complement of v_I . When ϕ_2 goes high, then v_o becomes the complement of v_{o1} or is the same as v_I . The circuit is a shift register.

16.58

Let $Q = 0$ and $\bar{Q} = 1$; as S increases, \bar{Q} decreases.

When \bar{Q} reaches the transition point of the $M_3 - M_6$ inverter, the flip-flop will change state.

From Equation (16.28(b)),

$$V_H = \sqrt{\frac{K_L}{K_D}} \cdot (-V_{TNL}) + V_{TND}$$

where $K_L = K_6$ and $K_D = K_3$.

Then

$$V_H = \sqrt{\frac{30}{100}} \cdot [-(-2)] + 1 \Rightarrow V_H = \bar{Q} = 2.095 \text{ V}$$

This is the region where both M_1 and M_3 are biased in the saturation region. Then


$$S = \sqrt{\frac{K_3}{K_1}} \cdot (-V_{TNL}) + V_{TND} = \sqrt{\frac{30}{200}} \cdot [-(-2)] + 1$$

or $S = 1.77 \text{ V}$

This analysis neglects the effect of M_2 starting to turn on at the same time.

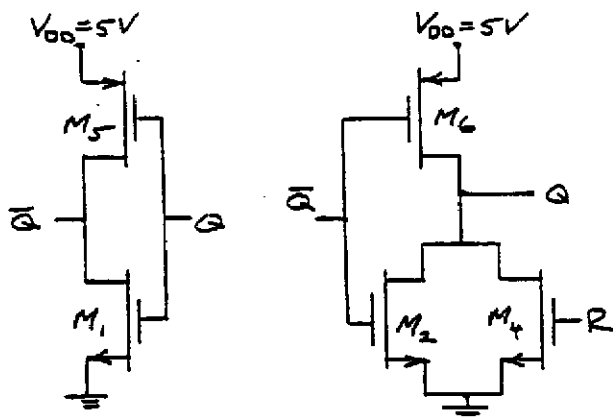16.59

Let $v_Y = R$, $v_X = S$, $v_{01} = Q$, and $v_{02} = \bar{Q}$. Assume $V_{TNH} = 0.5 \text{ V}$ and $V_{THP} = -0.5 \text{ V}$. For $S = 0$, we have the following:



If we want the switching to occur for $R = 2.5 \text{ V}$, then because of the nonsymmetry between the two circuits, we cannot have Q and \bar{Q} both equal to 2.5 V .

Set $R = Q = 2.5 \text{ V}$ and assume \bar{Q} goes low.

For the $M_1 - M_5$ inverter, M_1 in nonsaturation and M_5 in saturation. Then

$$K_n [2(2.5 - 0.5)\bar{Q} - \bar{Q}^2] = K_p [2.5 - 0.5]^2$$

Or

$$4\bar{Q} - \bar{Q}^2 = 4\left(\frac{K_p}{K_n}\right)$$


For the other circuit, $M_2 - M_4$ in saturation and M_6 in nonsaturation. Then

$$K_n (2.5 - 0.5)^2 + K_n (\bar{Q} - 0.5)^2 = K_p [2(2.5 - \bar{Q} - 0.5)(2.5) - (2.5)^2]$$

Combining these equations and neglecting the \bar{Q}^3 term, we find

$$\bar{Q} = 1.4 \text{ V} \quad \text{and} \quad \frac{K_p}{K_n} = 0.9$$

16.60

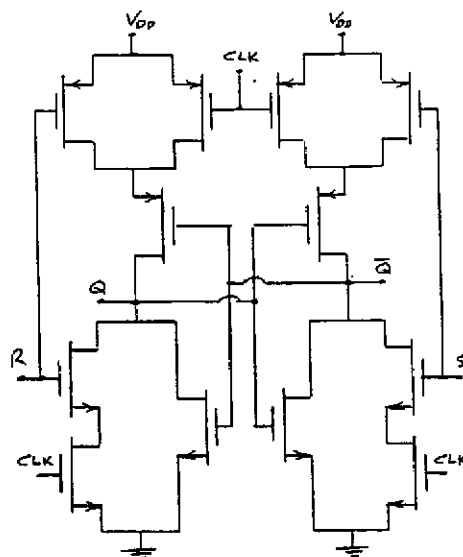

16.61

- Positive edge triggered flip-flop when $\text{CLK} = 1$, output of first inverter is \bar{D} and then $Q = \bar{\bar{D}} = D$.
- For example, put a CMOS transmission gate between the output and the gate of M_1 driven by a CLK pulse.

16.62

For $J = 1$, $K = 0$, and $\text{CLK} = 1$; this makes $Q = 1$ and $\bar{Q} = 0$.

For $J = 0$, $K = 1$, and $\text{CLK} = 1$, and if $Q = 1$, then the circuit is driven so that $Q = 0$ and $\bar{Q} = 1$.

If initially, $Q = 0$, then the circuit is driven so that there is no change and $Q = 0$ and $\bar{Q} = 1$.

$J = 1$, $K = 1$, and $\text{CLK} = 1$, and if $Q = 1$, then the circuit is driven so that $Q = 0$.

If initially, $Q = 0$, then the circuit is driven so that $Q = 1$.

So if $J = K = 1$, the output changes state.

16.63

For $J = \nu_X = 1$, $K = \nu_Y = 0$, and $\text{CLK} = \nu_Z = 1$, then $\nu_0 = 0$.

For $J = \nu_X = 0$, $K = \nu_Y = 1$, and $\text{CLK} = \nu_Z = 1$, then $\nu_0 = 1$.

Now consider $J = K = \text{CLK} = 1$. With $\nu_X = \nu_Z = 1$, the output is always $\nu_0 = 0$. So the output does not change state when $J = K = \text{CLK} = 1$. This is not actually a $J - K$ flip-flop.

16.64

64 $K \Rightarrow 65,536$ transistors arranged in a 256×256 array.

(a) Each column and row decoder required 8 inputs.

(b)

(i) Address = 01011110 so input = $a_7\bar{a}_6\bar{a}_5\bar{a}_4\bar{a}_3\bar{a}_2\bar{a}_1\bar{a}_0$

(ii) Address = 11101111 so input = $\bar{a}_7\bar{a}_6\bar{a}_5\bar{a}_4\bar{a}_3\bar{a}_2\bar{a}_1\bar{a}_0$

(c)

(i) Address = 00100111 so input = $a_7\bar{a}_6\bar{a}_5\bar{a}_4\bar{a}_3\bar{a}_2\bar{a}_1\bar{a}_0$

(ii) Address = 01111011 so input = $a_7\bar{a}_6\bar{a}_5\bar{a}_4\bar{a}_3\bar{a}_2\bar{a}_1\bar{a}_0$

16.65

Put 128 words in a 8×16 array, which means 8 row (or column) address lines and 16 column (or row) address lines.

16.66

Assume the address line is initially uncharged, then

$$I = C \frac{dV_c}{dt} \text{ or } V_c = \frac{1}{C} \int I dt = \frac{I}{C} \cdot t$$

$$\text{Then } t = \frac{V_c \cdot C}{I} = \frac{(2.7)(5.8 \times 10^{-12})}{250 \times 10^{-6}} \Rightarrow$$

$$t = 6.26 \times 10^{-8} \text{ s} \Rightarrow 62.6 \text{ ns}$$

16.67

$$(a) \frac{5 - 0.1}{1} = \left(\frac{35}{2} \right) \left(\frac{W}{L} \right) [2(5 - 0.7)(0.1) - (0.1)^2]$$

$$\text{or } \left(\frac{W}{L} \right) = 0.329$$

(b) $16 K \Rightarrow 16,384$ cells

$$i_D \approx \frac{2}{1} = 2 \mu\text{A}$$

$$\text{Power per cell} = (2 \mu\text{A})(2 \text{ V}) = 4 \mu\text{W}$$

$$\text{Total Power} = P_T = (4 \mu\text{W})(16,384) \Rightarrow$$

$$P_T = 65.5 \text{ mW}$$

$$\text{Standby current} = (2 \mu\text{A})(16,384) \Rightarrow I_T = 32.8 \text{ mA}$$

16.68

$16 K \Rightarrow 16,384$ cells

$$P_T = 200 \text{ mW} \Rightarrow \text{Power per cell}$$

$$= \frac{200}{16,384} \Rightarrow 12.2 \mu\text{W}$$

$$i_D = \frac{P}{V_{DD}} = \frac{12.2}{2.5} = 4.88 \mu\text{A} \approx \frac{V_{DD}}{R} = \frac{2.5}{R} \Rightarrow$$

$$R = 0.512 \text{ M}\Omega$$

If we want $v_o = 0.1 \text{ V}$ for a logic 0, then

$$i_D = \left(\frac{k'_n}{2} \right) \left(\frac{W}{L} \right) [2(V_{DD} - V_{TN})v_o - v_o^2]$$

$$4.88 = \left(\frac{35}{2} \right) \left(\frac{W}{L} \right) [2(2.5 - 0.7)(0.1) - (0.1)^2]$$

$$\text{So } \left(\frac{W}{L} \right) = 0.797$$

16.69

$$Q = 0, \bar{Q} = 1$$

$$\text{So } \bar{D} = \text{Logic 1} = 5 \text{ V}$$

A very short time after the row has been addressed, D remains charged at $V_{DD} = 5 \text{ V}$. Then M_{P3} , M_{A1} , and M_{N1} begin to conduct and D decreases. In steady-state, all three transistors are biased in the nonsaturation region. Then

$$\begin{aligned} K_{P3} [2(V_{SD3} + V_{TP3})V_{SD3} - V_{SD3}^2] \\ = K_{N1} [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2] \\ = K_{A1} [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2] \end{aligned}$$

Or

$$\begin{aligned} K_{P3} [2(V_{DD} + V_{TP3})(V_{DD} - D) - (V_{DD} - D)^2] \\ = K_{N1} [2(V_{DD} - Q - V_{TN1})(D - Q) - (D - Q)^2] \\ = K_{A1} [2(V_{DD} - V_{TN1})Q - Q^2] \quad (1) \end{aligned}$$

Equating the first and third terms:

$$\left(\frac{20}{2}\right)(1)[2(5-0.8)(5-D)-(5-D)^2] \\ = \left(\frac{40}{2}\right)(2)[2(5-0.8)Q-Q^2] \quad (2)$$

As a first approximation, neglect the $(5-D)^2$ and Q^2 terms. We find

$$Q = 1.25 - 0.25D \quad (3)$$

Then, equating the first and second terms of Equation (1):

$$\left(\frac{20}{2}\right)(1)[2(5-0.8)(5-D)-(5-D)^2] \\ = \left(\frac{40}{2}\right)(1)[2(5-Q-0.8)(D-Q)-(D-Q)^2]$$

Substituting Equation (3), we find as a first approximation: $D = 2.14 V$

Substituting this value of D into equation (2), we find

$$8.4(5-2.14)-(5-2.14)^2 = 4[8.4Q-Q^2]$$

We find $Q = 0.50 V$

Using this value of Q , we can find a second approximation for D by equating the second and third terms of equation (1). We have

$$20[2(4.2-Q)(D-Q)-(D-Q)^2] \\ = 40[2(4.2Q)-Q^2]$$

Using $Q = 0.50 V$, we find $D = 1.79 V$

16.70

Initially M_{N1} and M_A turn on.

M_{N1} , Nonsat; M_A , sat.

$$K_{n1}[V_{DD}-Q-V_{TN}]^2 = K_{n1}[2(V_{DD}-V_{TN1})Q-Q^2]$$

$$\left(\frac{40}{2}\right)(1)[5-Q-0.8]^2 = \left(\frac{40}{2}\right)(2)[2(5-0.8)Q-Q^2]$$

which yields

$$Q = 0.771 V$$

Initially M_{P2} and M_B turn on

Both biased in nonsaturation region

$$K_{p2}[2(V_{DD}+V_{TP3})(V_{DD}-\bar{Q})-(V_{DD}-\bar{Q})^2] \\ = K_{nB}[2(V_{DD}-V_{TNB})\bar{Q}-\bar{Q}^2]$$

$$\left(\frac{20}{2}\right)(4)[2(5-0.8)(5-\bar{Q})-(5-\bar{Q})^2]$$

$$= \left(\frac{40}{2}\right)(1)[2(5-0.8)\bar{Q}-\bar{Q}^2]$$

which yields $\bar{Q} = 3.78 V$

Note: (W/L) ratios do not satisfy Equation (16.95)

16.71

For Logic 1, v_1 :

$$(5)(0.05) + (4)(1) = (1+0.05)v_1 \Rightarrow \underline{v_1 = 4.0476 V}$$

v_2 :

$$(5)(0.025) + (4)(1) = (1+0.025)v_2 \Rightarrow \underline{v_2 = 4.0244 V}$$

For Logic 0, v_1 :

$$(0)(0.05) + (4)(1) = (1+0.05)v_1 \Rightarrow \underline{v_1 = 3.8095 V}$$

v_2 :

$$(0)(0.025) + (4)(1) = (1+0.025)v_2 \Rightarrow \underline{v_2 = 3.9024 V}$$