

# Chapter 11

## Exercise Solutions

E11.1

$$\begin{aligned}
 V_d &= V_1 - V_2 \\
 &= 2 + 0.005 \sin \omega t - (0.5 - 0.005 \sin \omega t) \\
 \Rightarrow V_d &= 1.5 + 0.010 \sin \omega t \text{ (V)} \\
 V_{cm} &= \frac{V_1 + V_2}{2} \\
 &= \frac{2 + 0.005 \sin \omega t + 0.5 - 0.005 \sin \omega t}{2} \\
 \Rightarrow V_{cm} &= 1.25 \text{ V}
 \end{aligned}$$

E11.2

$$\begin{aligned}
 v_E &= -V_{BE(\text{on})} \Rightarrow v_E = -0.7 \text{ V} \\
 I_{C1} &= I_{C2} = 0.5 \text{ mA} \\
 v_{C1} &= v_{C2} = 10 - (0.5)(10) \\
 \Rightarrow v_{C1} &= v_{C2} = 5 \text{ V}
 \end{aligned}$$

E11.3

$$\begin{aligned}
 \text{For } v_1 &= v_2 = +4 \text{ V} \\
 \Rightarrow \text{Minimum } v_{C1} &= v_{C2} = 4 \text{ V} \\
 I_{C1} &= I_{C2} = \frac{I_Q}{2} = 1 \text{ mA} \\
 R_C &= \frac{10 - 4}{1} \Rightarrow R_C = 6 \text{ k}\Omega
 \end{aligned}$$

E11.4

$$\begin{aligned}
 \frac{i_{C2}}{I_Q} &= \frac{1}{1 + \exp\left(\frac{v_d}{V_T}\right)} = 0.99 \\
 1 + \exp\left(\frac{v_d}{V_T}\right) &= \frac{1}{0.99} \\
 \exp\left(\frac{v_d}{V_T}\right) &= \frac{1}{0.99} - 1 \\
 v_d &= V_T \ln \left[ \frac{1}{0.99} - 1 \right] \\
 \Rightarrow v_d &= -119.5 \text{ mV}
 \end{aligned}$$

E11.6

$$\begin{aligned}
 \text{a. } v_1 &= v_2 = 0 \Rightarrow v_E = 0.7 \text{ V} \\
 \Delta V_{RC} &= (0.25)(8) = 2 \text{ V} \\
 \Rightarrow v_{C1} &= v_{C2} = -3 \text{ V} \\
 \Rightarrow v_{EC1} &= 3.7 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{b. } v_1 &= v_2 = 2.5 \text{ V} \Rightarrow v_E = 3.2 \text{ V} \\
 \Rightarrow v_{EC1} &= 6.2 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{c. } v_1 &= v_2 = -2.5 \text{ V} \Rightarrow v_E = -1.8 \text{ V} \\
 \Rightarrow v_{EC1} &= 1.2 \text{ V}
 \end{aligned}$$

E11.7

$$\text{Let } I_Q = 1 \text{ mA, then } I_{CQ1} = I_{CQ2} = 0.5 \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

At  $v_{C2}$ ,

$$A_d = \frac{v_{c2}}{v_d} = \frac{1}{2} g_m R_{C2}$$

$$\text{So, } 150 = \frac{1}{2} (19.23) R_{C2} \Rightarrow R_{C2} = 15.6 \text{ k}\Omega$$

At  $v_{C1}$ ,

$$A_d = \frac{v_{c1}}{v_d} = -\frac{1}{2} g_m R_{C1}$$

$$\text{So, } -100 = -\frac{1}{2} (19.23) R_{C1} \Rightarrow R_{C1} = 10.4 \text{ k}\Omega$$

If  $V^+ = +10 \text{ V}$  and  $V^- = -10 \text{ V}$ , dc biasing is OK.

E11.8

$$\text{a. Diff. Gain } A_d = \frac{I_Q R_C}{4V_T}$$

$$\text{For } v_1 = v_2 = 5 \text{ V} \Rightarrow \text{Minimum collector voltage } v_{C2} = 5 \text{ V}$$

$$\Rightarrow \frac{I_Q}{2} \cdot R_C = 15 - 5 = 10 \text{ V}$$

$$\text{or } I_Q R_C = 20 \text{ V for max. } A_d$$

Then

$$A_d = \frac{20}{2(0.026)} \Rightarrow A_d(\text{max}) = 192$$

$$\text{b. If } I_Q = 0.5 \text{ mA, } R_C = 40 \text{ k}\Omega$$

$$A_{cm} = \frac{-\left(\frac{I_Q R_C}{2V_T}\right)}{\left[1 + \frac{(1 + \beta) I_Q R_Q}{V_T \beta}\right]} = \frac{-\left(\frac{20}{2(0.026)}\right)}{\left[1 + \frac{(201)(0.5)(100)}{(0.026)(200)}\right]}$$

$$\text{Then } A_{cm} = \frac{-0.199}{\left[1 + \frac{(201)(0.5)(100)}{(0.026)(200)}\right]}$$

$$\Rightarrow A_{cm} = -0.199$$

$$\text{and } CMRR_{dB} = 20 \log_{10} \left( \frac{192}{0.199} \right)$$

$$\Rightarrow CMRR_{dB} = 59.7 \text{ dB}$$

## E11.9

$$\text{For } v_1 = v_2 = 5 \text{ V} \Rightarrow \min v_{C1} = v_{C2} = 5 \text{ V}$$

$$\text{So } I_{C1} R_C = 10 - 5 = 0.25 R_C \Rightarrow R_C = 20 \text{ k}\Omega$$

$$A_d = \frac{I_Q R_C}{4V_T} = \frac{(0.5)(20)}{4(0.026)} \Rightarrow A_d = 96.2 \quad \text{Let } I_Q = 0.5 \text{ mA}$$

$$CMRR_{dB} = 95 \text{ dB} \Rightarrow CMRR = 5.62 \times 10^4$$

$$\Rightarrow A_{cm} = \frac{96.2}{5.62 \times 10^4} \Rightarrow |A_{cm}| = 1.71 \times 10^{-3}$$

$$|A_{cm}| = \frac{\left( \frac{I_Q R_C}{2V_T} \right)}{\left[ 1 + \frac{(1+\beta)I_Q R_0}{V_T \beta} \right]} = 1.71 \times 10^{-3}$$

$$\frac{\left[ \frac{(0.5)(20)}{2(0.026)} \right]}{\left[ 1 + \frac{(201)(0.5)R_0}{(0.026)(200)} \right]} = 1.71 \times 10^{-3}$$

$$1 + 19.3 R_0 = 1.12 \times 10^5 \Rightarrow R_0 = 5.83 \times 10^3 \text{ k}\Omega$$

$$= 5.83 \text{ M}\Omega$$

$$\text{We have } R_0 = r_{o4} [1 + g_{m2} (R_2 \| r_{\pi 2})]$$

$$r_{o4} = \frac{V_A}{I_Q} = \frac{125}{0.5} = 250 \text{ k}\Omega$$

$$g_{m2} = \frac{I_Q}{V_T} = \frac{0.5}{0.026} = 19.2 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_Q} = \frac{(200)(0.026)}{0.5} = 10.4 \text{ k}\Omega$$

$$5830 = 250[1 + g_{m2} (R_2 \| r_{\pi 2})]$$

$$19.2(R_2 \| r_{\pi 2}) = 22.3$$

$$(R_2 \| r_{\pi 2}) = 1.16 \text{ k}\Omega$$

$$\frac{R_2(10.4)}{R_2 + 10.4} = 1.16$$

$$R_2(10.4 - 1.16) = (1.16)(10.4)$$

$$\Rightarrow R_2 = 1.31 \text{ k}\Omega$$

$$I_Q R_2 - I_1 R_3 = V_T \ln \left( \frac{I_1}{I_Q} \right) \quad \text{Let } I_1 = 1 \text{ mA}$$

$$(0.5)(1.31) - (1)R_3 = (0.026) \ln \left( \frac{1}{0.5} \right)$$

$$\Rightarrow R_3 = 0.637 \text{ k}\Omega$$

$$\text{If } V_{BE}(Q_3) \approx 0.7 \text{ V}$$

$$R_1 + R_3 = \frac{10 - 0.7 - (-10)}{1} = 19.3$$

$$\Rightarrow R_1 \approx 18.7 \text{ k}\Omega$$

## E11.10

$$\text{a. } v_o = A_d v_d + A_{cm} v_{cm}$$

$$v_d = v_1 - v_2 = 0.505 \sin \omega t - 0.495 \sin \omega t$$

$$= 0.01 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2} = \frac{0.505 \sin \omega t + 0.495 \sin \omega t}{2}$$

$$= 0.50 \sin \omega t$$

$$v_o = (60)(0.01 \sin \omega t) + (0.5)(0.5 \sin \omega t)$$

$$\Rightarrow v_o = 0.85 \sin \omega t \text{ (V)}$$

b.

$$v_d = v_1 - v_2$$

$$= 0.5 + 0.005 \sin \omega t - (0.5 - 0.005 \sin \omega t)$$

$$= 0.01 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2}$$

$$= \frac{0.5 + 0.005 \sin \omega t + 0.5 - 0.005 \sin \omega t}{2}$$

$$= 0.5$$

$$v_o = (60)(0.01 \sin \omega t) + (0.5)(0.5)$$

$$\Rightarrow v_o = 0.25 + 0.6 \sin \omega t \text{ (V)}$$

## E11.11

$$\text{a. } I_{B1} = I_{B2} = \frac{I_Q/2}{(1+\beta)} = \frac{1}{151}$$

$$\Rightarrow I_{B1} = I_{B2} = 6.62 \text{ }\mu\text{A}$$

$$\text{b. } r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(150)(0.026)}{1} = 3.9 \text{ k}\Omega$$

$$R_{id} = 2r_{\pi} = 2(3.9) = 7.8 \text{ k}\Omega$$

$$I_b = \frac{V_d}{R_{id}} = \frac{10 \sin \omega t \text{ (mV)}}{7.8 \text{ k}\Omega}$$

$$\Rightarrow I_b = 1.28 \sin \omega t \text{ (}\mu\text{A)}$$

$$\text{c. } R_{icm} \approx 2(1+\beta)R_0 = 2(151)(50) \Rightarrow 15.1 \text{ M}\Omega$$

$$I_b = \frac{V_{cm}}{R_{icm}} = \frac{3 \sin \omega t}{15.1 \text{ M}\Omega} \Rightarrow I_b = 0.199 \sin \omega t \text{ (}\mu\text{A)}$$

## E11.12

$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left( \frac{K_n}{2I_Q} \right) v_d^2}$$

Using the parameters in Example 11.11,

 $K_n = 0.5 \text{ mA/V}^2$ ,  $I_Q = 1 \text{ mA}$ , then

$$\frac{i_{D1}}{I_Q} = 0.90 = \frac{1}{2} + \sqrt{\frac{0.5}{2(1)}} \cdot v_d \sqrt{1 - \left( \frac{0.5}{2(1)} \right) v_d^2}$$

By trial and error,

$$v_d = 0.894 \text{ V}$$

## E11.13

$$I_1 = \frac{10 - V_{GS4}}{R_1} = K_n (V_{GS4} - V_{TN})^2$$

$$10 - V_{GS4} = (0.1)(80)(V_{GS4} - 0.8)^2$$

$$10 - V_{GS4} = 8(V_{GS4}^2 - 1.6V_{GS4} + 0.64)$$

$$8V_{GS4}^2 - 11.8V_{GS4} - 4.88 = 0$$

$$V_{GS4} = \frac{11.8 \pm \sqrt{(11.8)^2 + 4(8)(4.88)}}{2(8)} = 1.81 \text{ V}$$

$$I_1 = I_Q = \frac{10 - 1.81}{80} = 0.102 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{0.102}{2} = 0.051 \text{ mA}$$

$$= K_n (V_{GS1} - V_{TN})^2$$

$$0.051 = 0.050 (V_{GS1} - 0.8)^2 \Rightarrow V_{GS1} = 1.81 \text{ V}$$

$$v_{o1} = v_{o2} = 5 - (0.051)(40) = 2.96 \text{ V}$$

$$\begin{aligned} \text{Max } v_{cm}: V_{DS1}(\text{sat}) &= V_{GS1} - V_{TN} \\ &= 1.81 - 0.8 = 1.01 \text{ V} \end{aligned}$$

$$\begin{aligned} v_{cm}(\text{max}) &= v_{o1} - V_{DS1}(\text{sat}) + V_{GS1} \\ &= 2.96 - 1.01 + 1.81 \end{aligned}$$

$$v_{cm}(\text{max}) = 3.76 \text{ V}$$

$$\begin{aligned} \text{Min } v_{cm}: V_{DS4}(\text{sat}) &= V_{GS4} - V_{TN} \\ &= 1.81 - 0.8 = 1.01 \text{ V} \end{aligned}$$

$$\begin{aligned} v_{cm}(\text{min}) &= V_{GS1} + V_{DS4}(\text{sat}) - 5 \\ &= 1.81 + 1.01 - 5 \end{aligned}$$

$$v_{cm}(\text{min}) = -2.18 \text{ V}$$

$$-2.18 \leq v_{cm} \leq 3.76 \text{ V}$$

E11.14

$$g_f(\text{max}) = \sqrt{\frac{K_n I_Q}{2}} = \sqrt{\frac{(1)(2)}{(2)}} \Rightarrow$$

$$g_f(\text{max}) = 1 \text{ mA/V}$$

$$A_d = g_f R_D = (1)(5) \Rightarrow \underline{A_d = 5}$$

E11.15

$$A_d = g_f R_D$$

$$8 = g_f(4) \Rightarrow g_f(\text{max}) = 2 \text{ mA/V}$$

$$g_f(\text{max}) = \sqrt{\frac{K_n I_Q}{2}}$$

$$(2)^2 = K_n \left( \frac{4}{2} \right) \Rightarrow \underline{K_n = 2 \text{ mA/V}^2}$$

E11.16

From Example 11-10,  $I_Q = 0.588 \text{ mA}$ 

$$A_d = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D = \sqrt{\frac{(0.1)(0.588)}{2}} \cdot (16)$$

$$\Rightarrow \underline{A_d = 2.74}$$

$$\text{For } M_4, R_o = \frac{1}{\lambda_4 I_Q} = \frac{1}{(0.02)(0.588)} \Rightarrow R_o = 85 \text{ k}\Omega$$

$$\begin{aligned} g_m &= 2K_n (V_{GS2} - V_{TN}) = 2(0.1)(2.71 - 1) \\ &= 0.342 \text{ mA/V} \end{aligned}$$

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_o} = \frac{-(0.342)(16)}{1 + 2(0.342)(85)}$$

$$\Rightarrow \underline{A_{cm} = -0.0925}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{2.74}{0.0925} \right)$$

$$\Rightarrow \underline{CMRR_{dB} = 29.4 \text{ dB}}$$

E11.17

$$CMRR = \frac{1}{2} \left[ 1 + 2\sqrt{2K_n I_Q} \cdot R_o \right]$$

$$CMRR_{dB} = 60 \text{ dB} \Rightarrow CMRR = 1000$$

$$1000 = \frac{1}{2} \left[ 1 + 2\sqrt{2(0.1)(0.2)} \cdot R_o \right]$$

$$2000 = 1 + 0.4 R_o$$

$$\Rightarrow \underline{R_o \approx 5 \text{ M}\Omega}$$

E11.18

$$R_o = r_{o4} + r_{o2}(1 + g_{m4} r_{o4})$$

$$\text{Assume } I_{REF} = I_Q = 100 \mu\text{A} \text{ and } \lambda = 0.01 \text{ V}^{-1}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.1)} \Rightarrow 1 \text{ M}\Omega$$

$$\text{Let } K_n (\text{all devices}) = 0.1 \text{ mA/V}^2$$

Then

$$g_{m4} = 2\sqrt{K_n I_D} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$R_o = 1000 + 1000(1 + (0.2)(1000)) \Rightarrow 202 \text{ M}\Omega$$

Now

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.05}{0.1}} + 1 = 1.71 \text{ V}$$

$$V_{DS1}(\text{sat}) = V_{GS1} - V_{TN} = 1.71 - 1 = 0.71 \text{ V}$$

So

$$v_{o1}(\text{min}) = +4 - V_{GS1} + V_{DS1}(\text{sat}) = 4 - 1.71 + 0.71$$

$$v_{o1}(\text{min}) = 3 \text{ V} = 10 - I_D R_D = 10 - (0.05)R_D \Rightarrow$$

$$\underline{R_D = 140 \text{ k}\Omega}$$

For a one-sided output, the differential gain is:

$$A_d = \frac{1}{2} g_{m1} R_D \text{ where } g_{m1} = 2\sqrt{K_n I_D}$$

$$= 2\sqrt{(0.1)(0.05)} = 0.141 \text{ mA/V}$$

$$A_d = \frac{1}{2} (0.141)(140) \Rightarrow \underline{A_d = 9.87}$$

The common-mode gain is:

$$A_{cm} = \frac{\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o} = \frac{\sqrt{2(0.1)(0.1)} \cdot (140)}{1 + 2\sqrt{2(0.1)(0.1)} \cdot (202000)}$$

$$\Rightarrow \underline{A_{cm} = 0.000347}$$

Then

$$CMRR_{dB} = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| \Rightarrow \underline{CMRR_{dB} = 89.1 \text{ dB}}$$

E11.19

$$a. \quad I_{B5} = \frac{I_Q}{\beta(1+\beta)} = \frac{0.5}{(180)(181)} \Rightarrow 15.3 \text{ nA}$$

$$\text{So } I_Q = 15.3 \text{ nA}$$

b. For a balanced condition

$$V_{EC4} = V_{EC3} = V_{EB3} \Rightarrow V_{EC4} = 0.7 \text{ V}$$

$$V_{CE2} = V_{C2} - V_{E2} = (10 - 0.7) - (-0.7)$$

$$\Rightarrow V_{CE2} = 10 \text{ V}$$

E11.20

$$a. \quad g_f = \frac{I_Q}{4V_T} = \frac{0.5}{4(0.026)} = 4.81 \text{ mA/V}$$

$$r_{02} = \frac{V_{A2}}{I_{C2}} = \frac{125}{0.25} = 500 \text{ k}\Omega$$

$$r_{04} = \frac{V_{A4}}{I_{C4}} = \frac{85}{0.25} = 340 \text{ k}\Omega$$

$$A_d = 2g_f(r_{02} \parallel r_{04}) = 2(4.81)(500 \parallel 340)$$

$$\Rightarrow A_d = 1947$$

$$b. \quad A_d = 2g_f(r_{02} \parallel r_{04} \parallel R_L)$$

$$A_d = 2(4.81)[500 \parallel 340 \parallel 100]$$

$$\Rightarrow A_d = 644$$

$$c. \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(150)(0.026)}{0.25} = 15.6 \text{ k}\Omega$$

$$R_{id} = 2r_\pi \Rightarrow R_{id} = 31.2 \text{ k}\Omega$$

$$d. \quad R_o = r_{02} \parallel r_{04} = 500 \parallel 340 \Rightarrow R_o = 202 \text{ k}\Omega$$

E11.21

$$A_d = 2g_f(r_{02} \parallel r_{04})$$

$$g_f = \frac{I_Q}{4V_T} = \frac{0.2}{4(0.026)} = 1.92 \text{ mA/V}$$

$$r_{02} = \frac{V_{A2}}{I_{C2}} = \frac{120}{0.1} = 1200 \text{ k}\Omega$$

$$r_{04} = \frac{V_{A4}}{I_{C4}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$A_d = 2(1.92)(1200 \parallel 800) \Rightarrow A_d = 1843$$

E11.22

$$P = (I_Q + I_{REF})(5 - (-5))$$

$$10 = (0.1 + I_{REF})(10) \Rightarrow I_{REF} = 0.9 \text{ mA}$$

$$R_1 = \frac{5 - 0.7 - (-5)}{I_{REF}} = \frac{9.3}{0.9} \Rightarrow R_1 = 10.3 \text{ k}\Omega$$

$$I_Q R_E = V_T \ln \left( \frac{I_{REF}}{I_Q} \right)$$

$$R_E = \frac{0.026}{0.1} \ln \left( \frac{0.9}{0.1} \right) \Rightarrow R_E = 0.571 \text{ k}\Omega$$

$$r_{02} = \frac{V_{A2}}{I_{C2}} = \frac{125}{0.05} \Rightarrow 2.5 \text{ M}\Omega$$

$$r_{04} = \frac{V_{A4}}{I_{C4}} = \frac{85}{0.05} \Rightarrow 1.7 \text{ M}\Omega$$

$$g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

$$A_d = g_m(r_{02} \parallel r_{04} \parallel R_L) = (1.923)(2500 \parallel 1700 \parallel 90) \Rightarrow$$

$$A_d = 159$$

E11.23

$$a. \quad R_o = r_{02} \parallel r_{04}$$

$$r_{02} = \frac{120}{0.1} = 1.2 \text{ M}\Omega$$

$$r_{04} = \frac{80}{0.1} = 0.8 \text{ M}\Omega$$

$$R_o = 1.2 \parallel 0.8 \Rightarrow R_o = 0.48 \text{ M}\Omega$$

$$b. \quad A_d(\text{open circuit}) = 2g_f(r_{02} \parallel r_{04})$$

$$A_d(\text{with load}) = 2g_f(r_{02} \parallel r_{04} \parallel R_L)$$

$$\text{For } A_d(\text{with load}) = \frac{1}{2} A_d(\text{open circuit})$$

$$\Rightarrow R_L = (r_{02} \parallel r_{04}) \Rightarrow R_L = 0.48 \text{ M}\Omega$$

E11.24

$$A_d = 2 \sqrt{\frac{2K_n}{I_Q}} \cdot \frac{1}{(\lambda_2 + \lambda_4)}$$

$$= 2 \sqrt{\frac{2(0.1)}{0.1}} \cdot \frac{1}{(0.01 + 0.015)} \Rightarrow$$

$$A_d = 113$$

E11.25

$$\text{For the MOSFET, } I_D = 25 \text{ }\mu\text{A}$$

$$25 = 20(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.12 \text{ V}$$

$$g_{m1} = 2K_{n1}(V_{GS} - V_{TN}) = 2(20)(2.12 - 1)$$

$$\Rightarrow g_{m1} = 44.8 \text{ }\mu\text{A/V, } r_{02} = \infty$$

$$\text{For the Bipolar, } I_Q = 100 - 25 = 75 \text{ }\mu\text{A}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.075} \Rightarrow r_{\pi 2} = 34.7 \text{ k}\Omega$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{75}{0.026}$$

$$\Rightarrow g_{m2} = 2.88 \text{ mA/V, } r_{02} = \infty$$

$$g_m^C = \frac{g_{m1}(1 + g_{m2}r_\pi)}{(1 + g_{m1}r_\pi)}$$

$$= \frac{(44.8)[1 + (2.88)(34.7)]}{1 + (0.0448)(34.7)}$$

$$= \frac{(44.8)(100.9)}{2.55}$$

$$\Rightarrow g_m^C = 1.77 \text{ mA/V}$$

E11.26

From Figure 11.41

$$r_{o4} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

$$R_o = \beta r_{o4} = (150)(160) \text{ k}\Omega \Rightarrow \underline{R_o = 24 \text{ M}\Omega}$$

From Figure 11.42

$$r_{o6} = \frac{1}{\lambda I_D} = \frac{1}{(0.0125)(0.5)} \Rightarrow \underline{r_{o6} = 160 \text{ k}\Omega}$$

$$0.5 = 0.5(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2 \text{ V}$$

$$g_{m6} = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2 - 1) = 1 \text{ mA/V}$$

$$r_{o4} = 160 \text{ k}\Omega$$

$$R_o = (g_{m6})(r_{o6})(\beta r_{o4}) = (1)(160)(150)(160) \\ \Rightarrow \underline{R_o = 3.840 \text{ M}\Omega}$$

E11.27

From Equation (11.103)

$$R_i = \frac{2(1 + \beta)\beta V_T}{I_Q} = \frac{2(121)(120)(0.026)}{0.5} \\ \Rightarrow \underline{R_i = 1.51 \text{ M}\Omega}$$

$$r_{\pi 11} = \frac{\beta V_T}{I_Q} = \frac{(120)(0.026)}{0.5} = 6.24 \text{ k}\Omega$$

$$R'_E = r_{\pi 11} \parallel R_3 = 6.24 \parallel 0.1 = 0.0984 \text{ k}\Omega$$

$$g_{m11} = \frac{I_Q}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{o11} = \frac{V_A}{I_Q} = \frac{120}{0.5} = 240 \text{ k}\Omega$$

Then

$$R_{C11} = r_{o11}(1 + g_{m11}R'_E) \\ = 240[1 + (19.23)(0.0984)] \\ = 694 \text{ k}\Omega$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{(120)(0.026)}{2} = 1.56 \text{ k}\Omega$$

$$R_{o6} = r_{\pi 6} + (1 + \beta)R_4 = 1.56 + (121)(5) \\ = 607 \text{ k}\Omega$$

Then

$$R_{L7} = R_{C11} \parallel R_{o6} = 694 \parallel 607 = 324 \text{ k}\Omega$$

Then

$$A_v = \left( \frac{I_Q}{2V_T} \right) R_{L7} = \left[ \frac{0.5}{2(0.026)} \right] (324) \\ \Rightarrow \underline{A_v = 3115}$$

$$R_o = R_4 \parallel \left( \frac{r_{\pi 6} + Z}{1 + \beta} \right)$$

$$Z = R_{C11} \parallel R_{C7}$$

$$R_{C7} = \frac{V_A}{I_Q} = \frac{120}{0.5} = 240 \text{ k}\Omega$$

$$Z = 694 \parallel 240 = 178 \text{ k}\Omega$$

$$R_o = 5 \parallel \left( \frac{1.56 + 178}{121} \right) = 5 \parallel 1.48 \\ \Rightarrow \underline{R_o = 1.14 \text{ k}\Omega}$$

E11.28

$$A_v = \left( \frac{I_Q}{2V_T} \right) R_{L7}$$

$$10^3 = \left( \frac{0.5}{2(0.026)} \right) R_{L7} \\ \Rightarrow \underline{R_{L7} = 104 \text{ k}\Omega}$$

## E11.29

$$a. \quad R_1 = \frac{10 - 0.7 - (-10)}{I_1} = \frac{19.3}{0.6} \Rightarrow \underline{R_1 = 32.2 \text{ k}\Omega}$$

$$I_{C1} = I_{C2} = 0.1 \text{ mA} \Rightarrow I_Q \approx 0.2 \text{ mA}$$

$$R_2 = \frac{V_T}{I_Q} \cdot \ln\left(\frac{I_1}{I_Q}\right) = \frac{0.026}{0.2} \cdot \ln\left(\frac{0.6}{0.2}\right)$$

$$\Rightarrow \underline{R_2 = 143 \text{ }\Omega}$$

$$I_{R6} = I_1 = 0.6 \text{ mA} \Rightarrow \underline{R_3 = 0}$$

$$V_{O2} = V_{CE2} + V_B = 4 - 0.7 = 3.3 \text{ V}$$

$$R_C = \frac{10 - 3.3}{I_{C2}} = \frac{6.7}{0.1} \Rightarrow \underline{R_C = 67 \text{ k}\Omega}$$

$$V_{E4} = V_{O2} - 2V_{BE} = 3.3 - 2(0.7) = 1.9 \text{ V}$$

$$R_4 = \frac{1.9}{I_{R4}} = \frac{1.9}{0.6} \Rightarrow \underline{R_4 = 3.17 \text{ k}\Omega}$$

$$V_{O3} = V_{CE4} + V_{E4} = 3 + 1.9 = 4.9$$

$$R_5 = \frac{10 - 4.9}{I_{R4}} = \frac{5.1}{0.6} \Rightarrow \underline{R_5 = 8.5 \text{ k}\Omega}$$

$$V_{E5} = V_{O3} - V_{BE} = 4.9 - 0.7 = 4.2$$

$$R_6 = \frac{4.2 - 0.7}{I_{R6}} = \frac{3.5}{0.6} \Rightarrow \underline{R_6 = 5.83 \text{ k}\Omega}$$

$$R_7 = \frac{0 - (-10)}{I_{R7}} = \frac{10}{5} \Rightarrow \underline{R_7 = 2 \text{ k}\Omega}$$

$$b. \quad R_{i2} = r_{\pi3} + (1 + \beta)r_{\pi4}$$

$$r_{\pi4} = \frac{\beta V_T}{I_{R4}} = \frac{(100)(0.026)}{0.6} = 4.33 \text{ k}\Omega$$

$$r_{\pi3} \approx \frac{\beta^2 V_T}{I_{R4}} = \frac{(100)^2(0.026)}{0.6} = 433 \text{ k}\Omega$$

$$R_{i2} = 433 + (101)(4.33) \Rightarrow \underline{R_{i2} = 870 \text{ k}\Omega}$$

$$R_{i3} = r_{\pi5} + (1 + \beta)[R_6 + r_{\pi6} + (1 + \beta)R_7]$$

$$r_{\pi5} = \frac{\beta V_T}{I_{R6}} = \frac{(100)(0.026)}{0.6} = 4.33 \text{ k}\Omega$$

$$r_{\pi6} = \frac{\beta V_T}{I_{R7}} = \frac{(100)(0.026)}{5} = 0.52 \text{ k}\Omega$$

$$R_{i3} = 4.33 + (101)[5.83 + 0.52 + (101)(2)]$$

$$\Rightarrow \underline{R_{i3} = 21.0 \text{ M}\Omega}$$

$$c. \quad A_d = A_{d1} \cdot A_2 \cdot A_3$$

$$A_{d1} = g_f(R_C \parallel R_{i2})$$

$$g_f = \frac{I_Q}{4V_T} = \frac{0.2}{4(0.026)} = 1.92 \text{ mA/V}$$

$$A_{d1} = (1.92)(67 \parallel 870) = 119$$

$$A_2 = \left(\frac{I_{R4}}{2V_T}\right) R_5 = \frac{0.6}{2(0.026)}(8.5) = 98.1$$

$$A_3 \approx 1$$

$$A_d = (119)(98.1)(1)$$

$$\Rightarrow \underline{A_d = 11,674}$$

## Chapter 11

## Problem Solutions

11.1

$$a. \quad I_E = I_{C1} + I_{C2} = 4 \text{ mA} = \frac{-0.7 - (-8.7)}{R_E}$$

$$\text{So } R_E = \frac{8.0}{4} = 2 \text{ k}\Omega = R_E$$

Then


$$R_C = \frac{16 - V_{CE2}}{I_{C2}} = \frac{16 - 8}{2} \Rightarrow R_C = 4 \text{ k}\Omega$$

b. Neglecting base currents

$$16 = I_C R_C + V_{CE2} + 2I_C R_E - 8.7$$

$$V_{CE2} = 24.7 - I_C(R_C + 2R_E) = 24.7 - I_C(8)$$
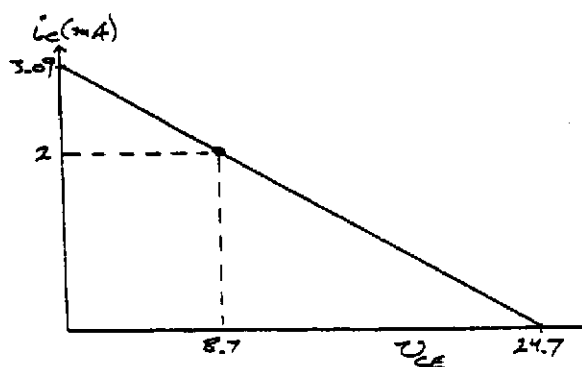
$$\text{For } I_C = 2 \text{ mA}, V_{CEQ} = 8.7 \text{ V}$$



$$c. \quad v_{cm}(\text{max}) \text{ for } V_{CB} = 0 \Rightarrow v_{cm}(\text{max}) = 8 \text{ V}$$

$$v_{cm}(\text{min}) \text{ for } Q_1 \text{ and } Q_2 \text{ at edge of cutoff}$$

$$\Rightarrow v_{cm}(\text{min}) = -8 \text{ V}$$

11.2

$$P = (I_1 + I_{C4})(V^+ - V^-)$$

$$I_1 \approx I_{C4} \text{ so}$$

$$1.2 = 2I_1(6) \Rightarrow I_1 = I_{C4} = 0.1 \text{ mA}$$

$$R_1 = \frac{3 - 0.7 - (-3)}{0.1} \Rightarrow R_1 = 53 \text{ k}\Omega$$

$$\text{For } v_{CM} = +1 \text{ V} \Rightarrow V_{C1} = V_{C2} = 1 \text{ V} \Rightarrow$$

$$R_C = \frac{3 - 1}{0.05} \Rightarrow R_C = 40 \text{ k}\Omega$$

One-sided output

$$A_d = \frac{1}{2} g_m R_C \text{ where } g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

Then

$$A_d = \frac{1}{2} (1.923)(40) \Rightarrow A_d = 38.5$$

11.3

$$a. \quad I_1 = \frac{10 - 2(0.7)}{8.5} \Rightarrow I_1 = 1.01 \text{ mA}$$

$$I_{C2} = \frac{I_1}{1 + \frac{\beta}{\beta(1+\beta)}} = \frac{1.01}{1 + \frac{101}{(100)(101)}}$$

$$\Rightarrow I_{C2} \approx 1.01 \text{ mA}$$

$$I_{C4} = \left(\frac{100}{101}\right) \left(\frac{1.01}{2}\right) \Rightarrow I_{C4} \approx 0.50 \text{ mA}$$

$$V_{CE2} = (0 - 0.7) - (-5) \Rightarrow V_{CE2} = 4.3 \text{ V}$$

$$V_{CE4} = [5 - (0.5)(2)] - (-0.7) \Rightarrow V_{CE4} = 4.7 \text{ V}$$

$$b. \quad \text{For } V_{CE4} = 2.5 \text{ V} \Rightarrow V_{C4} = -0.7 + 2.5 = 1.8 \text{ V}$$

$$I_{C4} = \frac{5 - 1.8}{2} \Rightarrow I_{C4} = 1.6 \text{ mA}$$

$$I_{C2} + \left(\frac{1+\beta}{\beta}\right) (2I_{C4}) = \left(\frac{101}{100}\right) (2)(1.6)$$

$$\Rightarrow I_{C2} = 3.23 \text{ mA}$$

$$I_1 \approx I_{C2} = 3.23 \text{ mA}$$

$$R_1 = \frac{10 - 2(0.7)}{3.23} \Rightarrow R_1 = 2.66 \text{ k}\Omega$$

11.4

$$a. \quad 0 = 0.7 + \frac{I_E}{2}(2) + I_E(85) - 5$$

$$I_E = \frac{5 - 0.7}{85 + 1} \Rightarrow I_E = 0.050 \text{ mA}$$

$$I_{C1} = I_{C2} = \left(\frac{\beta}{1+\beta}\right) \left(\frac{I_E}{2}\right) = \left(\frac{100}{101}\right) \left(\frac{0.050}{2}\right)$$

$$\text{Or } I_{C1} = I_{C2} = 0.0248 \text{ mA}$$

$$V_{CE1} = V_{CE2} = [5 - I_{C1}(100)] - (-0.7)$$

$$\text{So } V_{CE1} = V_{CE2} = 3.22 \text{ V}$$

$$b. \quad v_{cm}(\text{max}) \text{ for } V_{CB} = 0 \text{ and}$$

$$V_C = 5 - I_{C1}(100) = 2.52 \text{ V}$$

$$\text{So } v_{cm}(\text{max}) = 2.52 \text{ V}$$

$$v_{cm}(\text{min}) \text{ for } Q_1 \text{ and } Q_2 \text{ at the edge of cutoff}$$

$$\Rightarrow v_{cm}(\text{min}) = -4.3 \text{ V}$$

(c) Differential-mode half circuits

$$-\frac{v_d}{2} = V_x + \left(\frac{V_x}{r_x} + g_m V_x\right) \cdot R_E$$

$$= V_x \left[1 + \frac{(1+\beta)}{r_x} R_E\right]$$

Then

$$V_s = \frac{-(v_d/2)}{\left[1 + \frac{(1+\beta)R_E}{r_s}\right]}$$

$$v_o = -g_m V_s R_C \Rightarrow A_d = \frac{1}{2} \cdot \frac{\beta R_C}{r_s + (1+\beta)R_E}$$

$$r_s = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.0248} = 105 \text{ k}\Omega$$

Then

$$A_d = \frac{1}{2} \cdot \frac{(100)(100)}{105 + (101)(2)} \Rightarrow A_d = 16.3$$

11.5

a. i.  $(v_{o1} - v_{o2}) = 0$

ii.  $I_{C1} = I_{C2} = 1 \text{ mA}$

$$\begin{aligned} v_{o1} - v_{o2} &= [V^+ - I_{C1}R_{C1}] - [V^+ - I_{C2}R_{C2}] \\ &= I_C(R_{C2} - R_{C1}) = (1)(7.9 - 8) \\ \Rightarrow v_{o1} - v_{o2} &= -0.1 \text{ V} \end{aligned}$$

b.  $I_0 = (I_{S1} + I_{S2}) \exp\left(\frac{v_{BE}}{V_T}\right)$

$$\begin{aligned} \text{So } \exp\left(\frac{v_{BE}}{V_T}\right) &= \frac{2 \times 10^{-3}}{10^{-13} + 1.1 \times 10^{-13}} \\ &= 9.524 \times 10^9 \end{aligned}$$

$$I_{C1} = I_{S1} \exp\left(\frac{v_{BE}}{V_T}\right) = (10^{-13})(9.524 \times 10^9)$$

$$\Rightarrow I_{C1} = 0.952 \text{ mA}$$

$$I_{C2} = (1.1 \times 10^{-13})(9.524 \times 10^9)$$

$$\Rightarrow I_{C2} = 1.048 \text{ mA}$$

i.  $v_{o1} - v_{o2} = I_{C2}R_{C2} - I_{C1}R_{C1}$

$$\Rightarrow v_{o1} - v_{o2} = (1.048 - 0.952)(8)$$

$$\Rightarrow v_{o1} - v_{o2} = 0.768 \text{ V}$$

ii.  $v_{o1} - v_{o2} = (1.048)(7.9) - (0.952)(8)$

$$v_{o1} - v_{o2} = 8.279 - 7.616$$

$$\Rightarrow v_{o1} - v_{o2} = 0.663 \text{ V}$$

11.6

From Equation (11.12(b))

$$i_{C2} = \frac{I_Q}{1 + e^{v_d/V_T}}$$

$$0.90 = \frac{1}{1 + e^{v_d/V_T}}$$

$$\text{So } e^{v_d/V_T} = \frac{1}{0.90} - 1 = 0.111$$

$$v_d = V_T \ln(0.111) = (0.026) \ln(0.111)$$

$$\Rightarrow v_d = -0.0571 \text{ V}$$

11.7

For  $v_{CM} = 3.5 \text{ V}$  and a maximum peak-to-peak swing in the output voltage of  $2 \text{ V}$ , we need the quiescent collector voltage to be

$$V_C = 3.5 + 1 = 4.5 \text{ V}$$

Assume the bias is  $\pm 10 \text{ V}$ , and  $I_Q = 0.5 \text{ mA}$ .

Then  $I_C = 0.25 \text{ mA}$

$$\text{Now } R_C = \frac{10 - 4.5}{0.25} \Rightarrow R_C = 22 \text{ k}\Omega$$

$$\text{In this case, } r_s = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

Then

$$A_d = \frac{(100)(22)}{2(10.4 + 0.5)} = 101 \text{ So gain specification is met.}$$

For  $CMRR_{dB} = 80 \text{ dB} \Rightarrow$

$$\begin{aligned} CMRR &= 10^4 = \frac{1}{2} \left[ 1 + \frac{(1+\beta)I_Q R_o}{V_T \beta} \right] \\ &= \frac{1}{2} \left[ 1 + \frac{(101)(0.5)R_o}{(0.026)(100)} \right] \Rightarrow \end{aligned}$$

$$R_o = 103 \text{ M}\Omega$$

Need to use a Modified Widlar current source.

$$R_o = r_o \left[ 1 + g_m (R_{E1} \parallel r_s) \right]$$

$$\text{If } V_A = 100 \text{ V, then } r_o = \frac{100}{0.5} = 200 \text{ k}\Omega$$

$$r_s = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

Then

$$1030 = 200 \left[ 1 + (19.23)(R_{E1} \parallel r_s) \right] \Rightarrow$$

$$R_{E1} \parallel r_s = 0.216 \text{ k}\Omega = R_{E1} \parallel 5.2 \Rightarrow$$

$$R_{E1} = 225 \Omega$$

Also let  $R_{E2} = 225 \Omega$  and  $I_{REF} \cong 0.5 \text{ mA}$



11.8

a. For  $v_1 = v_2 = 0$  and neglecting base currents

$$R_E = \frac{-0.7 - (-10)}{0.15} \Rightarrow R_E = 62 \text{ k}\Omega$$

b. Using the small-signal equivalent circuit shown in Figure 11.8, but including the  $R_B$  resistors, we have

$$\frac{V_{\pi 1}}{r_\pi} + g_m V_{\pi 1} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_\pi} = \frac{V_e}{R_E}$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1 + \beta}{r_\pi} \right) = \frac{V_e}{R_E}$$

$$\text{Now } \frac{v_1 - V_e}{R_B + r_\pi} = \frac{V_{\pi 1}}{r_\pi} \text{ and } \frac{v_2 - V_e}{R_B + r_\pi} = \frac{V_{\pi 2}}{r_\pi}$$

Then

$$V_{\pi 1} = \left( \frac{r_\pi}{R_B + r_\pi} \right) (v_1 - V_e)$$

$$\text{and } V_{\pi 2} = \left( \frac{r_\pi}{R_B + r_\pi} \right) (v_2 - V_e)$$

Substituting, we find

$$(v_1 + v_2 - 2V_e) \left( \frac{r_\pi}{R_B + r_\pi} \right) \left( \frac{1 + \beta}{r_\pi} \right) = \frac{V_e}{R_E}$$

or

$$(v_1 + v_2 - 2V_e) \left( \frac{1 + \beta}{R_B + r_\pi} \right) = \frac{V_e}{R_E}$$

Solving for  $V_e$ ,

$$V_e = \frac{v_1 + v_2}{2 + \frac{R_B + r_\pi}{(1 + \beta)R_E}}$$

$$\text{Now } v_{o2} = -g_m V_{\pi 2} R_C$$

$$= -g_m R_C \left( \frac{r_\pi}{R_B + r_\pi} \right) (v_2 - V_e)$$

Substituting for  $V_e$ ,

$$\begin{aligned} v_{o2} &= \frac{-\beta R_C}{R_B + r_\pi} \left[ v_2 - \frac{v_1 + v_2}{2 + \frac{R_B + r_\pi}{(1 + \beta)R_E}} \right] \\ &= \frac{-\beta R_C}{R_B + r_\pi} \left[ \frac{v_2 \left( 1 + \frac{R_B + r_\pi}{(1 + \beta)R_E} \right) - v_1}{2 + \frac{R_B + r_\pi}{(1 + \beta)R_E}} \right] \end{aligned}$$

$$\text{Now } v_1 = v_{cm} + \frac{v_d}{2}$$

$$v_2 = v_{cm} - \frac{v_d}{2}$$

Substituting and rearranging terms, we obtain

$$v_{o2} = \frac{-\beta R_C}{R_B + r_\pi} \left\{ \frac{v_d}{2} - v_{cm} \left[ \frac{1}{1 + \frac{2R_E(1 + \beta)}{R_B + r_\pi}} \right] \right\}$$

$$A_d = \frac{v_{o2}}{v_d} = \frac{\beta R_C}{2(r_\pi + R_B)}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.075} = 34.7 \text{ k}\Omega$$

$$A_d = \frac{(100)(50)}{2(34.7 + 0.5)} \Rightarrow A_d = 71.0$$

$$\begin{aligned} A_{cm} &= -\frac{\beta R_C}{r_\pi + R_B} \left[ \frac{1}{1 + \frac{2R_E(1 + \beta)}{r_\pi + R_B}} \right] \\ &= -\frac{(100)(50)}{34.7 + 0.5} \left[ \frac{1}{1 + \frac{2(62)(101)}{34.7 + 0.5}} \right] \end{aligned}$$

$$\Rightarrow A_{cm} = -0.398$$

$$CMRR_{dB} = 20 \log_{10} \left| \frac{71.0}{0.398} \right| \Rightarrow CMRR_{dB} = 45.0 \text{ dB}$$

$$\text{c. } R_{id} = 2(r_\pi + R_B)$$


$$R_{id} = 2(34.7 + 0.5) \Rightarrow R_{id} = 70.4 \text{ k}\Omega$$

Common-mode input resistance

$$\begin{aligned} R_{icm} &= \frac{1}{2} [r_\pi + R_B + 2(1 + \beta)R_E] \\ &= \frac{1}{2} [34.7 + 0.5 + 2(101)(62)] \\ &\Rightarrow R_{icm} = 6.28 \text{ M}\Omega \end{aligned}$$

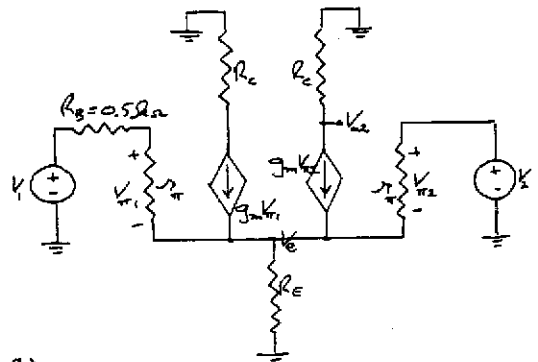11.9

$$\text{(a) } R_E = \frac{-0.7 - (-10)}{0.25} \Rightarrow R_E = 37.2 \text{ k}\Omega$$



(b)

$$\frac{V_{\pi 1}}{r_\pi} + g_m V_{\pi 1} + \frac{V_{\pi 2}}{r_\pi} + g_m V_{\pi 2} = \frac{V_e}{R_E}$$

$$\text{or (1) } \left( \frac{1 + \beta}{r_\pi} \right) (V_{\pi 1} + V_{\pi 2}) = \frac{V_e}{R_E}$$

$$\frac{V_{\pi 1}}{r_\pi} = \frac{V_1 - V_e}{R_B + r_\pi} \Rightarrow V_{\pi 1} = \left( \frac{r_\pi}{R_B + r_\pi} \right) (V_1 - V_e)$$

$$V_{e2} = V_2 - V_e$$

Then

$$(1) \left( \frac{1+\beta}{r_\pi} \right) \left[ \frac{r_\pi}{r_\pi + R_B} (V_1 - V_e) + (V_2 - V_e) \right] = \frac{V_e}{R_E}$$

From this, we find

$$V_e = \frac{V_1 + \frac{r_\pi + R_B}{r_\pi} V_2}{\left[ \frac{r_\pi + R_B}{R_E(1+\beta)} + 1 + \frac{r_\pi + R_B}{r_\pi} \right]}$$

Now

$$V_e = -g_m V_{e2} R_C = -g_m R_C (V_2 - V_e)$$

We have

$$r_\pi = \frac{(120)(0.026)}{0.125} \approx 25 \text{ k}\Omega, \quad g_m = \frac{0.125}{0.026} = 4.81 \text{ mA/V}$$

$$(i) \quad \text{Set } V_1 = \frac{V_d}{2} \text{ and } V_2 = -\frac{V_d}{2}$$

Then

$$V_e = \frac{\frac{V_d}{2} \left( 1 - \left( \frac{25+0.5}{25} \right) \right)}{\left[ \frac{25+0.5}{(37.2)(121)} + 1 + \frac{25+0.5}{25} \right]} = \frac{\frac{V_d}{2} (-0.02)}{2.026}$$

So

$$V_e = -0.00494 V_d$$

Now

$$V_o = -(4.81)(50) \left( -\frac{V_d}{2} - (-0.00494) V_d \right) \Rightarrow$$

$$A_d = \frac{V_o}{V_d} = 119$$

$$(ii) \quad \text{Set } V_1 = V_2 = V_{cm}$$

Then

$$V_e = \frac{V_{cm} \left( 1 + \frac{25+0.5}{25} \right)}{\left[ \frac{25+0.5}{(37.2)(121)} + 1 + \frac{25+0.5}{25} \right]} = \frac{V_{cm}(2.02)}{2.02567}$$

$$V_e = V_{cm}(0.9972)$$

Then

$$V_o = -(4.81)(50) [V_{cm} - V_{cm}(0.9972)]$$

or

$$A_{cm} = \frac{V_o}{V_{cm}} = -0.673$$

11.10

a. Neglecting base currents

$$I_1 = I_3 = 400 \mu\text{A} \Rightarrow R_1 = \frac{30 - 0.7}{0.4}$$

$$\Rightarrow R_1 = 73.25 \text{ k}\Omega$$

$$V_{CB1} = 10 \text{ V} \Rightarrow V_{C1} = 9.3 \text{ V}$$

$$R_C = \frac{15 - 9.3}{0.2} \Rightarrow R_C = 28.5 \text{ k}\Omega$$

$$b. \quad r_\pi = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$r_o(Q_3) = \frac{50}{0.4} = 125 \text{ k}\Omega$$

Using the results from problem 11.9, we have

$$A_d = \frac{\beta R_C}{2(r_\pi + R_B)} = \frac{(100)(28.5)}{2(13 + 10)} \Rightarrow A_d = 62$$

$$A_{cm} = -\frac{\beta R_C}{r_\pi + R_B} \left\{ \frac{1}{1 + \frac{2r_o(1+\beta)}{r_\pi + R_B}} \right\}$$

$$= -\frac{(100)(28.5)}{13 + 10} \left\{ \frac{1}{1 + \frac{2(125)(101)}{13 + 10}} \right\}$$

$$\Rightarrow A_{cm} = -0.113$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{62}{0.113} \right)$$

$$\Rightarrow CMRR_{dB} = 54.8 \text{ dB}$$

$$c. \quad R_{id} = 2(r_\pi + R_B) = 2(13 + 10) \Rightarrow R_{id} = 46 \text{ k}\Omega$$

$$R_{icm} = \frac{1}{2} [r_\pi + R_B + 2(1+\beta)r_o]$$

$$= \frac{1}{2} [13 + 10 + 2(101)(125)]$$

$$\Rightarrow R_{icm} = 12.6 \text{ M}\Omega$$

11.11

From Equation (11.18)

$$v_o = v_{C2} - v_{C1} = g_m R_C v_d$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$\text{For } I_Q = 2 \text{ mA}, \quad I_{CQ} = 1 \text{ mA}$$

$$\text{Then } g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Now

$$2 = (38.46) R_C (0.015)$$

$$\text{So } R_C = 3.47 \text{ k}\Omega$$


$$\text{Now } V_C = V^+ - I_C R_C = 10 - (1)(3.47)$$

$$= 6.53 \text{ V}$$

$$\text{For } V_{CB} = 0 \Rightarrow v_{cm}(\text{max}) = 6.53 \text{ V}$$

11.12

The small-signal equivalent circuit is

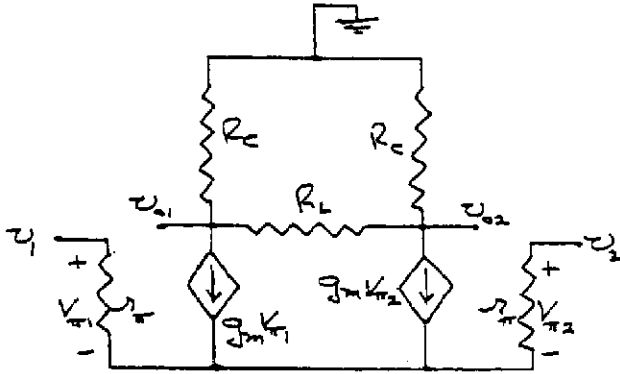
 A KVL equation:  $v_1 = V_{\pi 1} - V_{\pi 2} + v_2$ 

$$v_1 - v_2 = V_{\pi 1} - V_{\pi 2}$$

A KCL equation

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + \frac{V_{\pi 2}}{r_{\pi}} + g_m V_{\pi 2} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1}{r_{\pi}} + g_m \right) = 0 \Rightarrow V_{\pi 1} = -V_{\pi 2}$$

$$\text{Then } v_1 - v_2 = 2V_{\pi 1} \Rightarrow V_{\pi 1} = \frac{1}{2}(v_1 - v_2)$$

$$\text{and } V_{\pi 2} = -\frac{1}{2}(v_1 - v_2)$$

 At the  $v_{o1}$  node:

$$\frac{v_{o1}}{R_C} + \frac{v_{o1} - v_{o2}}{R_L} + g_m V_{\pi 1} = 0$$

$$v_{o1} \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - v_{o2} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_2 - v_1) \quad (1)$$

 At the  $v_{o2}$  node:

$$\frac{v_{o2}}{R_C} + \frac{v_{o2} - v_{o1}}{R_L} + g_m V_{\pi 2} = 0$$

$$v_{o2} \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - v_{o1} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_1 - v_2) \quad (2)$$

From (1):

$$v_{o2} = v_{o1} \left( 1 + \frac{R_L}{R_C} \right) - \frac{1}{2} g_m R_L (v_2 - v_1)$$

Substituting into (2)

$$\begin{aligned} v_{o1} \left( 1 + \frac{R_L}{R_C} \right) \left( \frac{1}{R_C} + \frac{1}{R_L} \right) \\ - \frac{1}{2} g_m R_L (v_2 - v_1) \left( \frac{1}{R_C} + \frac{1}{R_L} \right) \\ - v_{o1} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_1 - v_2) \end{aligned}$$

$$\begin{aligned} v_{o1} \left( \frac{1}{R_C} + \frac{R_L}{R_C^2} + \frac{1}{R_C} \right) \\ = \frac{1}{2} g_m (v_1 - v_2) \left[ 1 - \left( \frac{R_L}{R_C} + 1 \right) \right] \\ \frac{v_{o1}}{R_C} \left( 2 + \frac{R_L}{R_C} \right) = -\frac{1}{2} g_m \left( \frac{R_L}{R_C} \right) (v_1 - v_2) \end{aligned}$$

 For  $v_1 - v_2 = v_d$ 


$$A_{v1} = \frac{v_{o1}}{v_d} = \frac{-\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$$

$$\text{From symmetry: } A_{v2} = \frac{v_{o2}}{v_d} = \frac{\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$$

$$\text{Then } A_v = \frac{v_{o2} - v_{o1}}{v_d} = \frac{g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$$

11.13

The small-signal equivalent circuit is

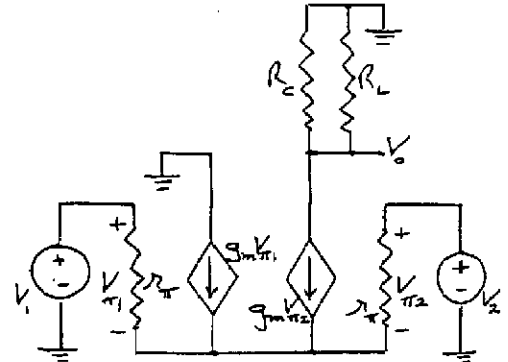
 KVL equation:  $v_1 = V_{\pi 1} - V_{\pi 2} + v_2$  or

$$v_1 - v_2 = V_{\pi 1} - V_{\pi 2}$$

KCL equation:

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi}} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1}{r_{\pi}} + g_m \right) = 0 \Rightarrow V_{\pi 1} = -V_{\pi 2}$$

$$\text{Then } v_1 - v_2 = -2V_{\pi 2} \text{ or } V_{\pi 2} = -\frac{1}{2}(v_1 - v_2)$$

 Now  $v_o = -g_m V_{\pi 2} (R_C \parallel R_L)$ 

$$= \frac{1}{2} g_m (R_C \parallel R_L) (v_1 - v_2)$$

 For  $v_1 - v_2 \equiv v_d$ 

$$\Rightarrow A_d = \frac{v_o}{v_d} = \frac{1}{2} g_m (R_C \parallel R_L)$$

11.14

We have

$$V_{C2} = -g_m V_{\pi 2} R_C = -g_m (V_{b2} - V_e) R_C$$

and

$$V_{C1} = -g_m V_{\pi 1} R_C = -g_m (V_{b1} - V_e) R_C$$

Then

$$\begin{aligned} V_0 &= V_{C2} - V_{C1} \\ &= -g_m (V_{b2} - V_e) R_C - [-g_m (V_{b1} - V_e) R_C] \\ &= g_m R_C (V_{b1} - V_{b2}) \end{aligned}$$

Differential gain

$$A_d = \frac{V_0}{V_{b1} - V_{b2}} = g_m R_C$$

Common-mode gain

$$A_{cm} = 0$$

11.15

$$(a) v_{cm} = 3V \Rightarrow V_{C1} = V_{C2} = 3V$$

$$\text{Then } R_C = \frac{10-3}{0.1} \Rightarrow R_C = 70 \text{ k}\Omega$$

$$(b) CMRR_{dB} = 75 \text{ dB} \Rightarrow CMRR = 5623$$

Now

$$CMRR = \frac{1}{2} \left[ 1 + \frac{(1+\beta)I_Q R_o}{\beta V_T} \right]$$

$$5623 = \frac{1}{2} \left[ 1 + \frac{(151)(0.2)R_o}{(150)(0.026)} \right] \Rightarrow R_o = 1.45 \text{ M}\Omega$$

Use a Widlar current source.

$$R_o = r_o [1 + g_m R'_g]$$

Let  $V_A$  of current source transistor be  $100V$ .

Then

$$r_o = \frac{100}{0.2} = 500 \text{ k}\Omega, \quad g_m = \frac{0.2}{0.026} = 7.69 \text{ mA/V}$$

$$r_s = \frac{(150)(0.026)}{0.2} = 19.5 \text{ k}\Omega$$

So

$$1450 = 500 [1 + (7.69)R'_g] \Rightarrow R'_g = 0.247 \text{ k}\Omega$$

Now

$$R'_g = R_g \parallel r_s \Rightarrow 0.247 = R_g \parallel 19.5 \Rightarrow R_g = 250 \Omega$$

Then

$$I_Q R_g = V_T \ln \left( \frac{I_{REF}}{I_Q} \right)$$

$$(0.2)(0.250) = (0.026) \ln \left( \frac{I_{REF}}{(0.2)} \right) \Rightarrow I_{REF} = 137 \text{ mA}$$

Then

$$R_1 = \frac{10 - 0.7 - (-10)}{137} \Rightarrow R_1 = 14.1 \text{ k}\Omega$$

11.16

$$A_d = 180, \quad CMRR_{dB} = 85 \text{ dB}$$

$$CMRR = 17,783 = \left| \frac{A_d}{A_{cm}} \right| = \frac{180}{A_{cm}}$$

$$\Rightarrow |A_{cm}| = 0.01012$$

Assume the common-mode gain is negative.

$$v_0 = A_d v_d + A_{cm} v_{cm}$$

$$= 180 v_d - 0.01012 v_{cm}$$

$$v_0 = 180(2 \sin \omega t) \text{ mV} - (0.01012)(2 \sin \omega t) \text{ V}$$

$$v_0 = 0.36 \sin \omega t - 0.02024 \sin \omega t$$

$$\text{Ideal Output: } v_0 = 0.360 \sin \omega t \text{ (V)}$$

$$\text{Actual Output: } v_0 = 0.340 \sin \omega t \text{ (V)}$$

11.17

At terminal A.

$$R_{THA} = R_A \parallel R = \frac{R(1+\delta) \cdot R}{R(1+\delta) + R} = \frac{R(1+\delta)}{2+\delta} \cong \frac{R}{2} = 5 \text{ k}\Omega$$

Variation in  $R_{TH}$  is not significant

$$V_{THA} = \left( \frac{R_A}{R_A + R} \right) V^* = \frac{R(1+\delta)(5)}{R(1+\delta) + R} = \frac{5(1+\delta)}{2+\delta}$$

At terminal B.

$$R_{THB} = R \parallel R = \frac{R}{2} = 5 \text{ k}\Omega$$

$$V_{THB} = \left( \frac{R}{R+R} \right) V^* = 2.5V$$

From Eq. (11.27)

$$V_o = \frac{-\beta R_C (V_2 - V_1)}{2(r_s + R_B)} \quad \text{where } V_2 = V_{THB} \text{ and } V_1 = V_{THA}$$

$$R_B = 5 \text{ k}\Omega, \quad r_s = \frac{(120)(0.026)}{0.25} = 12.5 \text{ k}\Omega$$

So

$$V_o = \frac{-(120)(3)(V_2 - V_1)}{2(12.5 + 5)} = -10.3(V_2 - V_1)$$

We can find  $V_2 - V_1 = V_{THB} - V_{THA}$ 

$$\begin{aligned} V_{THB} - V_{THA} &= 2.5 - \left[ \frac{5(1+\delta)}{2+\delta} \right] \\ &= \frac{2.5(2+\delta) - 5(1+\delta)}{2+\delta} = \frac{2.5\delta - 5\delta}{2+\delta} \\ &\cong \frac{-2.5\delta}{2} = -1.25\delta \end{aligned}$$

Then

$$V_o = -(10.3)(-1.25)\delta = 12.9\delta$$

So for  $-0.01 \leq \delta \leq 0.01$ 

We have

$$-0.129 \leq V_o \leq 0.129 \text{ V}$$

11.18

a.  $R_{id} = 2r_\pi$

$$r_\pi = \frac{(180)(0.026)}{0.2} = 23.4 \text{ k}\Omega$$

So

$$\underline{R_{id} = 46.8 \text{ k}\Omega}$$

b. Assuming  $r_\mu \rightarrow \infty$ , then

$$R_{icm} \approx [(1 + \beta)R_0] \parallel \left[ (1 + \beta) \left( \frac{r_o}{2} \right) \right]$$

$$r_o = \frac{125}{0.2} = 625 \text{ k}\Omega$$

$$\begin{aligned} R_{icm} &= [(181)(1)] \parallel [(181)(0.3125)] \\ &= 181 \parallel 56.56 \\ \Rightarrow \underline{R_{icm} = 43.1 \text{ M}\Omega} \end{aligned}$$

11.19

a. For  $I_1 = 1 \text{ mA}$ ,  $V_{BE3} = 0.7 \text{ V}$

$$R_1 = \frac{20 - 0.7}{1} \Rightarrow \underline{R_1 = 19.3 \text{ k}\Omega}$$

$$\begin{aligned} R_2 &= \frac{V_T}{I_Q} \cdot \ln \left( \frac{I_1}{I_Q} \right) = \frac{0.026}{0.1} \cdot \ln \left( \frac{1}{0.1} \right) \\ \Rightarrow \underline{R_2 = 0.599 \text{ k}\Omega} \end{aligned}$$

b.  $r_{\pi 4} = \frac{(180)(0.026)}{0.1} = 46.8 \text{ k}\Omega$

$$g_m = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$r_{o4} = \frac{100}{0.1} \Rightarrow 1 \text{ M}\Omega$$

From Chapter 10

$$R_0 = r_{o4} [1 + g_m (R_E \parallel r_{\pi 4})]$$

$$R_E \parallel r_{\pi 4} = 0.599 \parallel 46.8 = 0.591$$

$$R_0 = (1) [1 + (3.846)(0.591)] = 3.27 \text{ M}\Omega$$

$$r_{o1} = \frac{100}{0.05} \Rightarrow 2 \text{ M}\Omega$$

$$R_{icm} \approx [(1 + \beta)R_0] \parallel \left[ (1 + \beta) \left( \frac{r_{o1}}{2} \right) \right]$$

$$= [(181)(3.27)] \parallel [(181)(1)]$$

$$= 592 \parallel 181$$

$$\Rightarrow \underline{R_{icm} = 139 \text{ M}\Omega}$$

(c) From Eq. (11.32(b))

$$A_{cm} = \frac{-g_m R_c}{1 + \frac{2(1 + \beta)R_o}{r_x + R_B}}$$

$$g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

$$r_x = \frac{(180)(0.026)}{0.05} = 93.6 \text{ k}\Omega$$

$$R_B = 0$$

Then

$$A_{cm} = \frac{-(1.923)(50)}{1 + \frac{2(181)(3270)}{93.6}} \Rightarrow \underline{A_{cm} = -0.00760}$$

11.20

$$A_{d1} = g_{m1} (R_1 \parallel r_{\pi 3})$$

$$g_{m1} = \frac{I_{Q1}/2}{V_T} = 19.23 I_{Q1}$$

$$r_{\pi 3} = \frac{\beta V_T}{I_{Q2}/2} = \frac{2(100)(0.026)}{I_{Q2}} = \frac{5.2}{I_{Q2}}$$

$$A_{d2} = \frac{g_{m3} R_2}{2}, \quad g_{m3} = \frac{I_{Q2}/2}{V_T} = 19.23 I_{Q2}$$

Then

$$30 = \frac{(19.23)I_{Q2}}{2} \cdot R_2 \Rightarrow I_{Q2} R_2 = 3.12 \text{ V}$$

Maximum  $v_{o2} - v_{o1} = \pm 18 \text{ mV}$  for linearity

$$v_{o3}(\text{max}) = (\pm 18)(30) \text{ mV} \Rightarrow \pm 0.54 \text{ V}$$

so  $I_{Q2} R_2 = 3.12 \text{ V}$  is OK.From  $A_{d1}$ :

$$20 = 19.23 I_{Q1} (R_1 \parallel r_{\pi 3})$$

$$= 19.23 I_{Q1} \left( \frac{R_1 \left( \frac{5.2}{I_{Q2}} \right)}{R_1 + \left( \frac{5.2}{I_{Q2}} \right)} \right)$$

$$20 = \frac{19.23 I_{Q1} R_1 (5.2)}{I_{Q2} R_1 + 5.2}$$

$$\text{Let } \frac{I_{Q1}}{2} \cdot R_1 = 5 \text{ V} \Rightarrow I_{Q1} R_1 = 10 \text{ V}$$

Then

$$20 = \frac{19.23(10)(5.2)}{I_{Q2} R_1 + 5.2} \Rightarrow I_{Q2} R_1 = 44.8 \text{ V}$$

Now

$$I_{Q1} R_1 = 10 \Rightarrow R_1 = \frac{10}{I_{Q1}}$$

So

$$I_{Q2} \left( \frac{10}{I_{Q1}} \right) = 44.8 \Rightarrow \frac{I_{Q2}}{I_{Q1}} = 4.48$$

$$\text{Let } I_{Q1} = 100 \mu\text{A}, \quad I_{Q2} = 448 \mu\text{A}$$

Then

$$I_{Q2} R_2 = 3.12 \Rightarrow \underline{R_2 = 6.96 \text{ k}\Omega}$$

$$I_{Q1} R_1 = 10 \Rightarrow \underline{R_1 = 100 \text{ k}\Omega}$$

11.21

$$a. \quad I_1 = \frac{20 - V_{GS3}}{50} = 0.25(V_{GS3} - 2)^2$$

$$20 - V_{GS3} = 12.5(V_{GS3}^2 - 4V_{GS3} + 4)$$

$$12.5V_{GS3}^2 - 49V_{GS3} + 30 = 0$$

$$V_{GS3} = \frac{49 \pm \sqrt{(49)^2 - 4(12.5)(30)}}{2(12.5)}$$

$$\Rightarrow V_{GS3} = 3.16 \text{ V}$$

$$I_1 = \frac{20 - 3.16}{50} \Rightarrow I_1 = I_Q = 0.337 \text{ mA}$$

$$I_{D1} = \frac{I_Q}{2} \Rightarrow I_{D1} = 0.168 \text{ mA}$$


$$0.168 = 0.25(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 2.82 \text{ V}$$

$$V_{DS4} = -2.82 - (-10) \Rightarrow V_{DS4} = 7.18 \text{ V}$$

$$V_{D1} = 10 - (0.168)(24) = 5.97 \text{ V}$$

$$V_{DS1} = 5.97 - (-2.82) \Rightarrow V_{DS1} = 8.79 \text{ V}$$

(b)

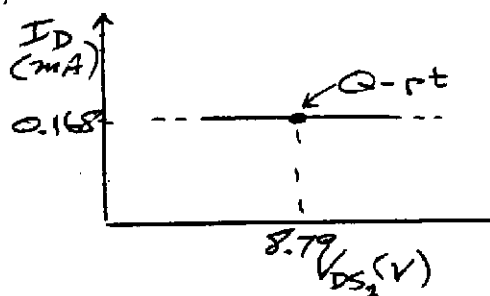

$$(c) \text{Max } v_{CM} \Rightarrow V_{DS1} = V_{DS2} = V_{DS}(\text{sat}) = V_{GS1} - V_{TN}$$

$$2.82 - 2 = 0.82 \text{ V}$$

$$\text{Now } V_{D1} = 10 - (0.168)(24) = 5.97 \text{ V}$$

$$V_s(\text{max}) = 5.97 - V_{DS1}(\text{sat}) = 5.97 - 0.82$$

$$V_s(\text{max}) = 5.15 \text{ V}$$

$$v_{CM}(\text{max}) = V_s(\text{max}) + V_{GS1} = 5.15 + 2.82$$

$$v_{CM}(\text{max}) = 7.97 \text{ V}$$

$$v_{CM}(\text{min}) = V^- + V_{DS4}(\text{sat}) + V_{GS1}$$

$$V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 3.16 - 2 = 1.16 \text{ V}$$

Then

$$v_{CM}(\text{min}) = -10 + 1.16 + 2.82 \Rightarrow$$

$$v_{CM}(\text{min}) = -6.02 \text{ V}$$

11.22

$$a. \quad I_{D1} = I_{D2} = 120 \mu\text{A} = 100(V_{GS1} - 1.2)^2$$

$$\Rightarrow V_{GS1} = V_{GS2} = 2.30 \text{ V}$$

$$\text{For } v_1 = v_2 = -5.4 \text{ V and } V_{DS1} = V_{DS2} = 12 \text{ V}$$

$$\Rightarrow V_0 = -5.4 - 2.30 + 12 = 4.3 \text{ V}$$

$$R_D = \frac{10 - 4.3}{0.12} \Rightarrow R_D = 47.5 \text{ k}\Omega$$

$$I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = I_1 = 240 \mu\text{A}$$

$$I_1 = 240 = 200(V_{GS1} - 1.2)^2 \Rightarrow V_{GS1} = 2.30 \text{ V}$$

$$R_1 = \frac{20 - 2.3}{0.24} \Rightarrow R_1 = 73.75 \text{ k}\Omega$$

$$b. \quad r_{o4} = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.24)} = 416.7 \text{ k}\Omega$$

$$\Delta I_Q = \frac{1}{r_{o4}} \cdot \Delta V_{DS} = \frac{5.4}{416.7} \Rightarrow \Delta I_Q \approx 13 \mu\text{A}$$

11.23

$$a. \quad R_D = \frac{10 - 7}{0.5} \Rightarrow R_D = 6 \text{ k}\Omega$$


$$I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = 1 \text{ mA}$$

$$b. \quad 10 = I_D(6) + V_{DS} - V_{GS}$$

$$\text{and } V_{GS} = \sqrt{\frac{I_D}{K_n}} + V_{TN}$$

$$\text{For } I_D = 0.5 \text{ mA, } V_{GS} = \sqrt{\frac{0.5}{0.4}} + 2 = 3.12 \text{ V}$$

$$\text{and } V_{DS} = 10.12$$

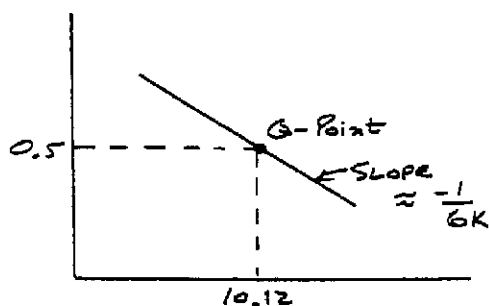

Load line is actually nonlinear.

c. Maximum common-mode voltage when  $M_1$  and  $M_2$  reach the transition point, or

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 3.12 - 2 = 1.12 \text{ V}$$

Then

$$v_{cm} = v_{02} - v_{DS}(\text{sat}) + V_{GS} = 7 - 1.12 + 3.12$$

$$\text{Or } v_{cm}(\text{max}) = 9 \text{ V}$$

Minimum common-mode voltage, voltage across  $I_Q$  becomes zero.

$$\text{So } v_{cm}(\text{min}) = -10 + 3.12$$

$$\Rightarrow v_{cm}(\text{min}) = -6.88 \text{ V}$$

11.24

$$a. \quad I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$$v_{01} - v_{02} = [V^+ - I_{D1}R_{D1}] - [V^+ - I_{D2}R_{D2}]$$

$$v_{01} - v_{02} = I_{D2}R_{D2} - I_{D1}R_{D1} = I_D(R_{D2} - R_{D1})$$

i.  $R_{D1} - R_{D2} = 6 \text{ k}\Omega$ ,  $v_{01} - v_{02} = 0$

ii.  $R_{D1} = 6 \text{ k}\Omega$ ,  $R_{D2} = 5.9 \text{ k}\Omega$

$$v_{01} - v_{02} = (0.5)(5.9 - 6)$$

$$\Rightarrow v_{01} - v_{02} = -0.05 \text{ V}$$

b.  $K_{n1} = 0.4 \text{ mA/V}^2$ ,  $K_{n2} = 0.44 \text{ mA/V}^2$

$$V_{GS1} = V_{GS2}$$

$$I_Q = (K_{n1} + K_{n2})(V_{GS} - V_{TN})^2$$

$$1 = (0.4 + 0.44)(V_{GS} - V_{TN})^2$$

$$\Rightarrow (V_{GS} - V_{TN})^2 = 1.19$$

$$I_{D1} = (0.4)(1.19) = 0.476 \text{ mA}$$

$$I_{D2} = (0.44)(1.19) = 0.524 \text{ mA}$$

i.  $R_{D1} = R_{D2} = 6 \text{ k}\Omega$

$$v_{01} - v_{02} = (0.524 - 0.476)(6)$$

$$\Rightarrow v_{01} - v_{02} = 0.288 \text{ V}$$

ii.  $R_{D1} = 6 \text{ k}\Omega$ ,  $R_{D2} = 5.9 \text{ k}\Omega$

$$v_{01} - v_{02} = (0.524)(5.9) - (0.476)(6)$$

$$= 3.0916 - 2.856$$

$$\Rightarrow v_{01} - v_{02} = 0.236 \text{ V}$$

11.25

(a) From Equation (11.51)

$$\frac{v_{D2}}{I_Q} = \frac{1}{2} - \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2}$$

$$0.90 = 0.50 - \sqrt{\frac{0.1}{2(0.25)}} \cdot v_d \sqrt{1 - \left[\frac{0.1}{2(0.25)}\right] v_d^2}$$

$$-0.40 = -(0.4472)v_d \sqrt{1 - (0.2)v_d^2}$$

$$0.8945 = v_d \sqrt{1 - (0.2)v_d^2}$$

Square both sides

$$0.80 = v_d^2 (1 - [0.2]v_d^2)$$

$$(0.2)(v_d^2)^2 - v_d^2 + 0.80 = 0$$

$$v_d^2 = \frac{1 \pm \sqrt{1 - 4(0.2)(0.80)}}{2(0.2)} = 4V^2 \text{ or } 1V^2$$

Then  $v_d = 2 \text{ V}$  or  $1 \text{ V}$ 

$$\text{But } |v_d|_{\max} = \sqrt{\frac{I_Q}{k_n}} = \sqrt{\frac{0.25}{0.1}} = 1.58$$

So  $v_d = 1 \text{ V}$ b. From part (a),  $v_{d,\max} = 1.58 \text{ V}$ 

11.26

$$A_d = \frac{g_m R_D}{2}$$

$$\text{For } v_{cm} = 2.5 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{I_Q}{2} = 0.25 \text{ mA}$$

$$\text{Let } V_{D1} = V_{D2} = 3 \text{ V, then } R_D = \frac{10 - 3}{0.25} \Rightarrow$$

$$R_D = 28 \text{ k}\Omega$$

$$\text{Then } 100 = \frac{g_m(28)}{2} \Rightarrow g_m = 7.14 \text{ mA/V}$$

$$\text{And } g_m = 2 \sqrt{\frac{k'_n}{2} \left(\frac{W}{L}\right) I_D}$$

$$7.14 = 2 \sqrt{\left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (0.25)} \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 1274 \text{ (Extremely large transistors to meet the gain requirement.)}$$

$$\text{Need } |A_{cm}| = 0.10$$

From Eq. (11.64(b))

$$|A_{cm}| = \frac{g_m R_D}{1 + 2g_m R_o}$$

$$\text{So } 0.10 = \frac{(7.14)(28)}{1 + 2(7.14)R_o} \Rightarrow R_o = 140 \text{ k}\Omega$$

For the basic 2-transistor current source

$$R_o = r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.5)} = 200 \text{ k}\Omega$$

This current source is adequate to meet common-mode gain requirement.

11.27

a.  $I_S = \frac{-V_{GS1} - (-5)}{R_S}$

$$\text{and } I_S = 2I_D = 2K_n(V_{GS1} - V_{TN})^2$$

$$\frac{5 - V_{GS1}}{20} = 2(0.050)(V_{GS1} - 1)^2$$

$$5 - V_{GS1} = 2(V_{GS1}^2 - 2V_{GS1} + 1)$$

$$2V_{GS1}^2 - 3V_{GS1} - 3 = 0$$

$$V_{GS1} = \frac{3 \pm \sqrt{(3)^2 + 4(2)(3)}}{2(2)} \Rightarrow V_{GS1} = 2.186 \text{ V}$$

$$I_S = \frac{5 - 2.186}{20} \Rightarrow I_S = 0.141 \text{ mA}$$


$$I_{D1} = I_{D2} = \frac{I_S}{2} \Rightarrow I_{D1} = I_{D2} = 0.0704 \text{ mA}$$

$$v_{02} = 5 - (0.0704)(25) \Rightarrow v_{02} = 3.24 \text{ V}$$

$$b. \quad g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.05)(2.186 - 1)$$

$$g_m = 0.119 \text{ mA/V}$$
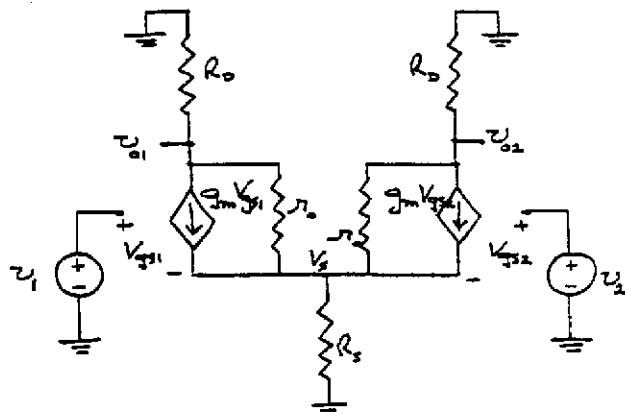
$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(0.0704)} = 710 \text{ k}\Omega$$



$$V_{gs1} = v_1 - V_S, \quad V_{gs2} = v_2 - V_S$$

$$\frac{v_{o1}}{R_D} + g_m V_{gs1} + \frac{v_{o1} - V_S}{r_o} = 0$$

$$v_{o1} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m(v_1 - V_S) - \frac{V_S}{r_o} = 0 \quad (1)$$

$$\frac{v_{o2}}{R_D} + g_m V_{gs2} + \frac{v_{o2} - V_S}{r_o} = 0$$

$$v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m(v_2 - V_S) - \frac{V_S}{r_o} = 0 \quad (2)$$

$$g_m V_{gs1} + \frac{v_{o1} - V_S}{r_o} + \frac{v_{o2} - V_S}{r_o} + g_m V_{gs2} = \frac{V_S}{R_S}$$

$$g_m(v_1 - V_S) + \frac{v_{o1}}{r_o} + \frac{v_{o2}}{r_o} - \frac{2V_S}{r_o} + g_m(v_2 - V_S) = \frac{V_S}{R_S}$$

$$g_m(v_1 + v_2) + \frac{v_{o1}}{r_o} + \frac{v_{o2}}{r_o} = V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\} \quad (3)$$

From (1)

$$v_{o1} = \frac{V_S \left( g_m + \frac{1}{r_o} \right) - g_m v_1}{\left( \frac{1}{R_D} + \frac{1}{r_o} \right)}$$

Then

$$g_m(v_1 + v_2) + \frac{V_S \left( g_m + \frac{1}{r_o} \right) - g_m v_1}{r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right)} + \frac{v_{o2}}{r_o} = V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\} \quad (3)$$

$$g_m(v_1 + v_2) r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + V_S \left( g_m + \frac{1}{r_o} \right) - g_m v_1 + v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) = V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\} \cdot r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$$

$$g_m(v_1 + v_2) \left( 1 + \frac{r_o}{R_D} \right) - g_m v_1 + v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) = V_S \left\{ \left( 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right) \left( 1 + \frac{r_o}{R_D} \right) - \left( g_m + \frac{1}{r_o} \right) \right\}$$

$$g_m \left( v_1 \cdot \frac{r_o}{R_D} + v_2 + v_2 \cdot \frac{r_o}{R_D} \right) + v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) = V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} + 2g_m \cdot \frac{r_o}{R_D} + \frac{2}{R_D} + \frac{r_o}{R_S R_D} - g_m - \frac{1}{r_o} \right\}$$

$$g_m \left( v_1 \cdot \frac{r_o}{R_D} + v_2 + v_2 \cdot \frac{r_o}{R_D} \right) + v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) = V_S \left\{ 2g_m + \frac{1}{r_o} + \frac{1}{R_S} \left( 1 + \frac{r_o}{R_D} \right) + \frac{2}{R_D} (1 + g_m r_o) \right\} \quad (4)$$

Then substituting into (2),

$$v_{o2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m v_2 = V_S \left( g_m + \frac{1}{r_o} \right)$$

Substitute numbers:

$$(0.119) \left[ v_1 \frac{710}{25} + v_2 + v_2 \frac{710}{25} \right] + v_{o2} \left[ \frac{1}{25} + \frac{1}{710} \right] = V_S \left\{ 0.119 + \frac{1}{710} + \frac{1}{20} \left( 1 + \frac{710}{25} \right) + \frac{2}{25} [1 + (0.119)(710)] \right\} \quad (4)$$

$$(0.119)[28.4v_1 + 29.4v_2] + (0.0414)v_{o2} = V_S \{ 0.1204 + 1.470 + 6.8392 \} = V_S(8.4296)$$

or

$$V_S = 0.4010v_1 + 0.4150v_2 + 0.00491v_{o2}$$

Then

$$v_{o2} \left( \frac{1}{25} + \frac{1}{710} \right) + (0.119)v_2 = V_S \left( 0.119 + \frac{1}{710} \right) \quad (2)$$

$$v_{o2}(0.0414) + v_2(0.119) = (0.1204)[0.4010v_1 + 0.4150v_2 + 0.00491v_{o2}]$$

$$v_{o2}(0.0408) = (0.04828)v_1 - (0.0690)v_2$$

$$v_{o2} = (1.183)v_1 - (1.691)v_2$$



$$\begin{aligned}\text{Now } v_1 &= v_{cm} + \frac{v_d}{2} \\ v_2 &= v_{cm} - \frac{v_d}{2}\end{aligned}$$

So

$$v_{o2} = (1.183)\left(v_{cm} + \frac{v_d}{2}\right) - (1.691)\left(v_{cm} - \frac{v_d}{2}\right)$$


$$\text{Or } v_{o2} = 1.437v_d - 0.508v_{cm}$$

$$\Rightarrow A_d = 1.437, \quad A_{cm} = -0.508$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{1.437}{0.508} \right)$$

$$\Rightarrow CMRR_{dB} = 9.03 \text{ dB}$$

11.28

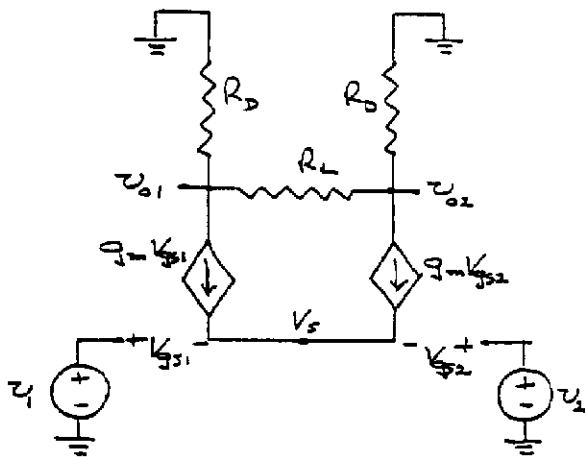

KVL:

$$v_1 = V_{gs1} - V_{gs2} + v_2$$

$$\text{So } v_1 - v_2 = V_{gs1} - V_{gs2}$$

KCL:

$$g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$$

$$\text{So } V_{gs1} = \frac{1}{2}(v_1 - v_2), \quad V_{gs2} = -\frac{1}{2}(v_1 - v_2)$$

Now

$$\begin{aligned}\frac{v_{o2}}{R_D} + \frac{v_{o2} - v_{o1}}{R_L} &= -g_m V_{gs2} \\ &= v_{o2} \left( \frac{1}{R_D} + \frac{1}{R_L} \right) - \frac{v_{o1}}{R_L}\end{aligned}$$

$$\begin{aligned}\frac{v_{o1}}{R_D} + \frac{v_{o1} - v_{o2}}{R_L} &= -g_m V_{gs1} \\ &= v_{o1} \left( \frac{1}{R_D} + \frac{1}{R_L} \right) - \frac{v_{o2}}{R_L}\end{aligned}$$

$$\text{From (1): } v_{o1} = v_{o2} \left( 1 + \frac{R_L}{R_D} \right) + g_m R_L V_{gs2}$$

Substitute into (2):

$$\begin{aligned}-g_m V_{gs1} &= v_{o2} \left( 1 + \frac{R_L}{R_D} \right) \left( \frac{1}{R_D} + \frac{1}{R_L} \right) \\ &\quad + g_m R_L \left( \frac{1}{R_D} + \frac{1}{R_L} \right) V_{gs2} - \frac{v_{o2}}{R_L} \\ -g_m (v_1 - v_2) + g_m \left( 1 + \frac{R_L}{R_D} \right) \left( \frac{1}{2} \right) (v_1 - v_2) \\ &= v_{o2} \left( \frac{1}{R_D} + \frac{R_L}{R_D^2} + \frac{1}{R_D} \right)\end{aligned}$$

$$\frac{1}{2} g_m \left( \frac{R_L}{R_D} \right) (v_1 - v_2) = \frac{v_{o2}}{R_D} \left( 2 + \frac{R_L}{R_D} \right)$$

$$\Rightarrow A_{d2} = \frac{v_{o2}}{v_1 - v_2} = \frac{\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$


From symmetry

$$A_{d1} = \frac{v_{o1}}{v_1 - v_2} = \frac{-\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

Then

$$A_v = \frac{v_{o2} - v_{o1}}{v_1 - v_2} = \frac{g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

11.29

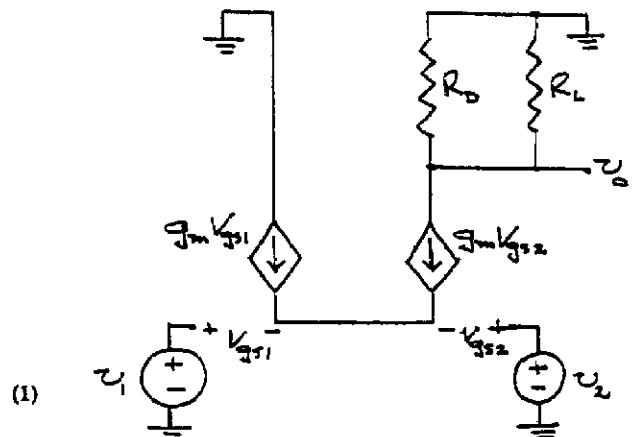

(1)

$$v_1 - v_2 = V_{gs1} - V_{gs2}$$

(2)

$$\text{and } g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$$

$$\text{Then } v_1 - v_2 = -2V_{gs2}$$

$$\text{Or } V_{gs2} = -\frac{1}{2}(v_1 - v_2)$$

$$v_o = -g_m V_{gs2} (R_D \parallel R_L) = \frac{g_m}{2} (R_D \parallel R_L) (v_1 - v_2)$$

$$\text{Or } A_d = \frac{g_m}{2} (R_D \parallel R_L)$$

11.30

$$\text{From Equation (11.64(a)), } A_d = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D$$

$$\text{We need } A_d = \frac{2}{0.2} = 10$$

$$\text{Then } 10 = \sqrt{\frac{K_n (0.5)}{2}} \cdot R_D \text{ or } \sqrt{K_n} \cdot R_D = 20$$

$$\text{If we set } R_D = 20 \text{ k}\Omega, \text{ then } K_n = 1 \text{ mA/V}^2$$

$$\text{For this case } V_D = 10 - (0.25)(20) = 5 \text{ V}$$

$$V_{GS} = \sqrt{\frac{0.25}{1}} + 1 = 1.5 \text{ V}$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 1.5 - 1 = 0.5 \text{ V}$$

$$\begin{aligned} \text{Then } v_{cm}(\text{max}) &= V_D - V_{DS}(\text{sat}) + V_{GS} \\ &= 5 - 0.5 + 1.5 \end{aligned}$$

$$\text{Or } v_{cm}(\text{max}) = 6 \text{ V}$$

11.31

$$V_{d1} = -g_m V_{gs1} R_D = -g_m R_D (V_1 - V_2)$$

$$V_{d2} = -g_m V_{gs2} R_D = -g_m R_D (V_2 - V_1)$$

Now

$$V_o = V_{d2} - V_{d1} = -g_m R_D (V_2 - V_1) - (-g_m R_D (V_1 - V_2))$$

$$V_o = g_m R_D (V_1 - V_2)$$

$$\text{Define } V_1 - V_2 = V_d$$

Then

$$A_d = \frac{V_o}{V_d} = g_m R_D$$

and

$$A_{cm} = 0$$

11.32

$$(a) K_{n1} = K_{n2} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) = \left(\frac{0.080}{2}\right) (10) = 0.40 \text{ mA/V}^2$$

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.1}{0.4}} + 1 = 1.5 \text{ V}$$

$$V_{DS1}(\text{sat}) = 1.5 - 1 = 0.5 \text{ V}$$

$$\begin{aligned} \text{For } v_{CM} = +3 \text{ V} \Rightarrow V_{D1} = V_{D2} = v_{CM} - V_{GS1} + V_{DS1}(\text{sat}) \\ = 3 - 1.5 + 0.5 \Rightarrow V_{D1} = V_{D2} = 2 \text{ V} \end{aligned}$$

$$R_D = \frac{10 - 2}{0.1} \Rightarrow R_D = 80 \text{ k}\Omega$$

$$(b) A_d = \frac{1}{2} g_m R_D \text{ and } g_m = 2\sqrt{(0.4)(0.1)} = 0.4 \text{ mA/V}$$

$$\text{Then } A_d = \frac{1}{2} (0.4)(80) = 16$$

$$CMRR_{dB} = 45 \Rightarrow CMRR = 177.8 = \frac{16}{A_{cm}}$$

$$\text{So } |A_{cm}| = 0.090$$

$$|A_{cm}| = \frac{g_m R_D}{1 + 2g_m R_o}$$

$$0.090 = \frac{(0.4)(80)}{1 + 2(0.4)R_o} \Rightarrow R_o = 443 \text{ k}\Omega$$

If we assume  $\lambda = 0.01 \text{ V}^{-1}$  for the current source transistor, then

$$r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

So the CMRR specification can be met by a 2-transistor current source.

$$\text{Let } \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 1$$

$$\text{Then } K_{n3} = K_{n4} = \left(\frac{0.080}{2}\right) (1) = 0.040 \text{ mA/V}^2$$

$$\text{and } V_{GS3} = \sqrt{\frac{I_Q}{K_{n3}}} + V_{TN} = \sqrt{\frac{0.2}{0.04}} + 1 = 3.24 \text{ V}$$

$$\begin{aligned} \text{For } v_{CM} = -3 \text{ V}, V_{D3} = -3 - V_{GS1} = -3 - 1.5 = -4.5 \text{ V} \\ \Rightarrow V_{DS3}(\text{min}) = -4.5 - (-10) = 5.5 \text{ V} > V_{DS3}(\text{sat}) \end{aligned}$$


So design is OK.

$$\text{On reference side: For } \left(\frac{W}{L}\right) \geq 1, V_{GS}(\text{max}) = 3.24 \text{ V}$$

$$20 - V_{GS3} = 20 - 3.24 = 16.76 \text{ V}$$

Then
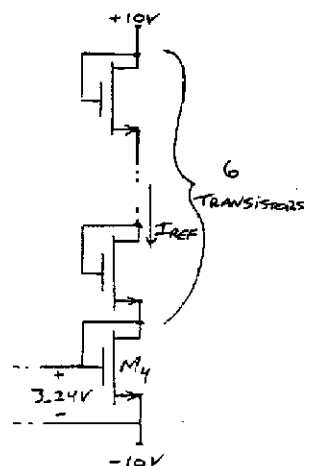
$$\frac{16.67}{3.24} = 5.17 \Rightarrow \text{We need six transistors in series.}$$




$$V_{GS} = \frac{20 - 3.24}{6} = 2.793 \text{ V}$$

$$I_{REF} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) (V_{GS} - V_{TN})^2$$

$$0.2 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (2.793 - 1)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right) = 156 \text{ for each of the 6 transistors.}$$

11.33

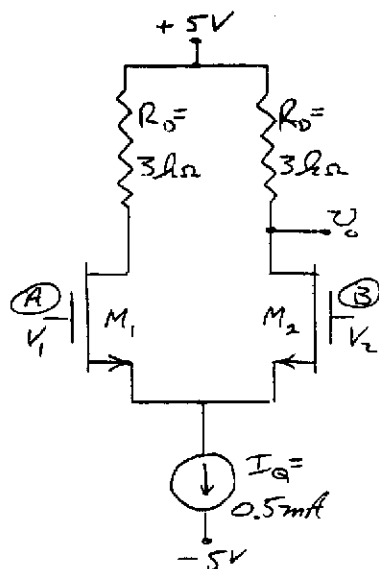

$$A_d = \frac{1}{2} g_m R_D$$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.25)(0.25)} = 0.50 \text{ mA/V}$$

$$A_d = \frac{1}{2} (0.50)(3) = 0.75$$

From Problem 11.17

$$V_1 = V_A = \frac{5(1+\delta)}{2+\delta}, \quad V_2 = V_B = 2.5 \text{ V}$$

$$\text{and } V_1 - V_2 = 1.25\delta$$

Then

$$V_{o2} = A_d \cdot (V_1 - V_2) = (0.75)(1.25\delta) = 0.9375\delta$$

$$\text{So for } -0.01 \leq \delta \leq 0.01$$

$$-9.375 \leq V_{o2} \leq 9.375 \text{ mV}$$

11.34

From previous results

$$A_{d1} = \frac{v_{o2} - v_{o1}}{v_1 - v_2} = g_{m1} R_1 = \sqrt{2K_n I_{Q1}} \cdot R_1 = 20$$

and

$$A_{d2} = \frac{v_{o2}}{v_{o2} - v_{o1}} = \frac{1}{2} g_{m2} R_2 = \frac{1}{2} \sqrt{2K_n I_{Q2}} \cdot R_2 = 30$$

$$\text{Set } \frac{I_{Q1} R_1}{2} = 5 \text{ V and } \frac{I_{Q2} R_2}{2} = 2.5 \text{ V}$$

$$\text{Let } I_{Q1} = I_{Q2} = 0.1 \text{ mA}$$

$$\text{Then } R_1 = 100 \text{ k}\Omega, \quad R_2 = 50 \text{ k}\Omega$$

Then

$$2\left(\frac{0.06}{2}\right)\left(\frac{W}{L}\right)_1 (0.1) = \left(\frac{20}{100}\right)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 6.67$$

and

$$2\left(\frac{0.060}{2}\right)\left(\frac{W}{L}\right)_3 (0.1) = \left(\frac{2(30)}{50}\right)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 240$$

11.35

$$\text{a. } i_{D1} = I_{DSS} \left(1 - \frac{v_{GS1}}{V_P}\right)^2$$

$$i_{D2} = I_{DSS} \left(1 - \frac{v_{GS2}}{V_P}\right)^2$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}}$$

$$= \sqrt{I_{DSS}} \left(1 - \frac{v_{GS1}}{V_P}\right) - \sqrt{I_{DSS}} \left(1 - \frac{v_{GS2}}{V_P}\right)$$

$$= \frac{\sqrt{I_{DSS}}}{V_P} (v_{GS2} - v_{GS1})$$

$$= -\frac{\sqrt{I_{DSS}}}{V_P} \cdot v_d = \frac{\sqrt{I_{DSS}}}{(-V_P)} \cdot v_d$$

$$i_{D1} + i_{D2} = I_Q \Rightarrow i_{D2} = I_Q - i_{D1}$$

$$\left(\sqrt{i_{D1}} - \sqrt{I_Q - i_{D1}}\right)^2 = \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2$$

$$i_{D1} - 2\sqrt{i_{D1}(I_Q - i_{D1})} + (I_Q - i_{D1}) = \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2$$

Then

$$\sqrt{i_{D1}(I_Q - i_{D1})} = \frac{1}{2} \left[ I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right]$$

Square both sides

$$i_{D1}^2 - i_{D1} I_Q + \frac{1}{4} \left[ I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right]^2 = 0$$

$$i_{D1} = \frac{I_Q \pm \sqrt{I_Q^2 - 4\left(\frac{1}{4}\right)\left[I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2\right]^2}}{2}$$

$$i_{D1} =$$

$$\frac{I_Q}{2} \pm \frac{1}{2} \sqrt{I_Q^2 - \left[ I_Q^2 - \frac{2I_Q I_{DSS} v_d^2}{(-V_P)^2} + \left( \frac{I_{DSS} v_d^2}{(-V_P)^2} \right)^2 \right]}$$

Use + sign

$$i_{D1} = \frac{I_Q}{2} + \frac{1}{2} \sqrt{\frac{2I_Q I_{DSS}}{(-V_P)^2} \cdot v_d^2 - \left( \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right)^2}$$

$$i_{D1} = \frac{I_Q}{2} + \frac{1}{2} \frac{I_Q}{(-V_P)} v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

Or

$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \left( \frac{1}{-2V_P} \right) \cdot v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

We had

$$i_{D2} = I_Q - i_{D1}$$

Then

$$\frac{i_{D2}}{I_Q} = \frac{1}{2} - \left( \frac{1}{-2V_P} \right) \cdot v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

b. If  $i_{D1} = I_Q$ , then

$$1 = \frac{1}{2} + \left( \frac{1}{-2V_P} \right) \cdot v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

$$|V_P| = v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

Square both sides

$$|V_P|^2 = v_d^2 \left[ \frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2 \right]$$

$$\left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{1}{V_P} \right)^2 (v_d^2)^2 - \frac{2I_{DSS}}{I_Q} \cdot v_d^2 + |V_P|^2 = 0$$

$$v_d^2 =$$

$$\frac{\frac{2I_{DSS}}{I_Q} \pm \sqrt{\left( \frac{2I_{DSS}}{I_Q} \right)^2 - 4 \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{1}{V_P} \right)^2 (V_P)^2}}{2 \left( \frac{2I_{DSS}}{I_Q} \right)^2 \left( \frac{1}{V_P} \right)^2}$$

$$v_d^2 = (V_P)^2 \left( \frac{I_Q}{I_{DSS}} \right)$$

$$\text{Or } |v_d| = |V_P| \left( \frac{I_Q}{I_{DSS}} \right)^{1/2}$$

c. For  $v_d$  small,

$$i_{D1} \approx \frac{I_Q}{2} + \frac{1}{2} \cdot \frac{I_Q}{(-V_P)} \cdot v_d \sqrt{\frac{2I_{DSS}}{I_Q}}$$

$$g_f = \left. \frac{di_{D1}}{dv_d} \right|_{v_d=0} = \frac{1}{2} \cdot \frac{I_Q}{(-V_P)} \cdot \sqrt{\frac{2I_{DSS}}{I_Q}}$$

Or

$$\Rightarrow g_f(\text{max}) = \left( \frac{1}{-V_P} \right) \sqrt{\frac{I_Q I_{DSS}}{2}}$$

11.36

$$\text{a. } I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = 1 \text{ mA}$$

$$v_0 = 7 = 10 - (0.5)R_D \Rightarrow R_D = 6 \text{ k}\Omega$$

$$\text{b. } g_f(\text{max}) = \left( \frac{1}{-V_P} \right) \sqrt{\frac{I_Q \cdot I_{DSS}}{2}}$$

$$g_f(\text{max}) = \left( \frac{1}{4} \right) \sqrt{\frac{(1)(2)}{2}}$$

$$\Rightarrow g_f(\text{max}) = 0.25 \text{ mA/V}$$

$$\text{c. } A_d = \frac{g_m R_D}{2} = g_f(\text{max}) \cdot R_D$$

$$A_d = (0.25)(6) \Rightarrow A_d = 1.5$$

11.37

$$\text{a. } I_S = \frac{-V_{GS} - (-5)}{R_S} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$5 - V_{GS} = (0.8)(20) \left( 1 - \frac{V_{GS}}{(-2)} \right)^2$$

$$5 - V_{GS} = 16 \left( 1 + V_{GS} + \frac{1}{4} V_{GS}^2 \right)$$

$$4V_{GS}^2 + 17V_{GS} + 11 = 0$$

$$V_{GS} = \frac{-17 \pm \sqrt{(17)^2 - 4(4)(11)}}{2(4)}$$

$$V_{GS} = -0.796 \text{ V}$$

$$I_S = \frac{5 - (-0.796)}{20} \Rightarrow I_S = 0.290 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{I_S}{2} \Rightarrow I_{D1} = I_{D2} = 0.145 \text{ mA}$$

$$v_{02} = 5 - (0.145)(25) \Rightarrow v_{02} = 1.375 \text{ V}$$

b. Taking into account the  $r_o$  parameters of  $Q_1$  and  $Q_2$ , the analysis is identical to that in problem 11.34.

11.38

Equivalent circuit and analysis is identical to that in problem 11.36.

$$A_{d2} = \frac{\frac{1}{2} \cdot g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

$$A_{d1} = \frac{-\frac{1}{2} \cdot g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

$$A_v = \frac{v_{02} - v_{01}}{v_d} = \frac{g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

11.39

a. Using the results of problem 10.59, the resistance from the base of  $Q_4$  looking toward  $Q_3$ :

$$\frac{1}{R_0'} = \frac{1}{r_{01}} + \frac{\left( \frac{1}{r_{\pi3}} + g_{m3} + \frac{1}{r_{03}} \right)}{\left[ 1 + \left( \frac{1}{r_{\pi3}} + g_{m3} + \frac{1}{r_{03}} \right) R_E \right]}$$

$$r_{01} = \frac{120}{0.1} = 1200 \text{ k}\Omega, \quad r_{03} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

Assume  $\beta = 100$ 

$$r_{\pi3} = \frac{(100)(0.026)}{0.1} = 26 \text{ k}\Omega$$

$$g_{m3} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$\begin{aligned}\frac{1}{R'_0} &= \frac{1}{1200} + \frac{\left(\frac{1}{26} + 3.846 + \frac{1}{800}\right)}{\left[1 + \left(\frac{1}{26} + 3.846 + \frac{1}{800}\right)(1)\right]} \\ &= \frac{1}{1200} + \frac{3.886}{1 + (3.886)(1)} \Rightarrow R'_0 = 1.256 \text{ k}\Omega\end{aligned}$$

$$\begin{aligned}R_0 &= r_{02} \left[ 1 + \frac{R_E \parallel (r_{\pi 2} + R'_0)}{r_{02}} \right. \\ &\quad \left. + g_{m2} \left( \frac{r_{\pi 2}}{r_{\pi 2} + R'_0} \right) \{ R_E \parallel (r_{\pi 2} + R'_0) \} \right] \\ R_E \parallel (r_{\pi 2} + R'_0) &= (1) \parallel (26 + 1.256) \\ &= (1) \parallel (27.256) \\ &= 0.965 \text{ k}\Omega\end{aligned}$$

$$\begin{aligned}R_0 &= 1200 \left[ 1 + \frac{0.965}{1200} + (3.846) \left( \frac{26}{26 + 1.256} \right) (0.965) \right] \\ \Rightarrow R_0 &= 5.45 \text{ M}\Omega\end{aligned}$$

Then

$$\begin{aligned}A_v &= -g_m(r_{02} \parallel R_0) \\ r_{02} &= \frac{120}{0.1} = 1200 \text{ k}\Omega \\ g_m &= \frac{0.1}{0.026} = 3.846 \text{ mA/V}\end{aligned}$$

$$\begin{aligned}A_v &= -(3.846)[1200 \parallel 5450] \\ \Rightarrow A_v &= -3782\end{aligned}$$

b. For  $R = 0$ ,  $r_{04} = \frac{80}{0.1} = 800 \text{ k}\Omega$

$$\begin{aligned}A_v &= -g_m(r_{02} \parallel r_{04}) \\ &= -(3.846)[1200 \parallel 800] \\ \Rightarrow A_v &= -1846\end{aligned}$$

(c) For part (a),  $R_o = (5.45 \parallel 12) = 0.983 \text{ M}\Omega$

For part (b),  $R_o = (12 \parallel 0.8) = 0.48 \text{ M}\Omega$

11.40

$$I_{B3} = \frac{I_{B3}}{1 + \beta} = \frac{I_{B3} + I_{B4}}{1 + \beta} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)}$$

Now  $I_{C3} + I_{C4} \approx I_Q$

So  $I_{B3} \approx \frac{I_Q}{\beta(1 + \beta)}$

$$I_{B4} = \frac{I_{B4}}{1 + \beta} = \frac{I_{Q1}}{\beta(1 + \beta)}$$

For balance, we want  $I_{B3} = I_{B4}$

So that  $I_{Q1} = I_Q$

11.41

a.  $A_d = g_m(r_{02} \parallel r_{04})$

$$r_{02} = \frac{V_{A2}}{I_{C2}} = \frac{150}{0.4} = 375 \text{ k}\Omega$$

$$r_{04} = \frac{V_{A4}}{I_{C4}} = \frac{100}{0.4} = 250 \text{ k}\Omega$$

$$g_m = \frac{I_{C2}}{V_T} = \frac{0.4}{0.026} = 15.38 \text{ mA/V}$$

$$A_d = (15.38)(375 \parallel 250)$$


$$\Rightarrow A_d = 2307$$

b.  $R_L = r_{02} \parallel r_{04} = 375 \parallel 250$

$$\Rightarrow R_L = 150 \text{ k}\Omega$$

11.42

(a) For  $Q_2, Q_4$

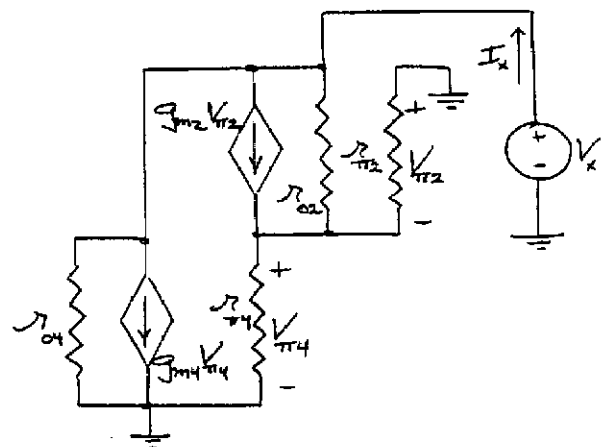

$$(1) I_x = \frac{V_x - V_{x4}}{r_{02}} + g_{m2}V_{x2} + g_{m4}V_{x4} + \frac{V_x}{r_{04}}$$

$$(2) g_{m2}V_{x2} + \frac{V_x - V_{x4}}{r_{02}} = \frac{V_{x4}}{r_{04} \parallel r_{x2}}$$

$$(3) V_{x4} = -V_{x2}$$

From (2)

$$\frac{V_x}{r_{02}} = V_{x4} \left[ \frac{1}{r_{04} \parallel r_{x2}} + \frac{1}{r_{02}} + g_{m2} \right]$$

Now

$$I_{C4} = \left( \frac{\beta}{1 + \beta} \right) \left( \frac{I_Q}{2} \right) = \left( \frac{120}{121} \right) (0.5) = 0.496 \text{ mA}$$

$$I_{C2} = \left( \frac{I_Q}{2} \right) \left( \frac{1}{1 + \beta} \right) \left( \frac{\beta}{1 + \beta} \right) = (0.5) \left( \frac{120}{(121)^2} \right) \Rightarrow$$

$$I_{C2} = 0.0041 \text{ mA}$$

So

$$r_{\pi 2} = \frac{(120)(0.026)}{0.0041} = 761 \text{ k}\Omega$$

$$g_{m2} = \frac{0.0041}{0.026} = 0.158 \text{ mA/V}$$

$$r_{o2} = \frac{100}{0.0041} \Rightarrow 24.4 \text{ M}\Omega$$

$$r_{\pi 4} = \frac{(120)(0.026)}{0.496} = 6.29 \text{ k}\Omega$$

$$g_{m4} = \frac{0.496}{0.026} = 19.08 \text{ mA/V}$$

$$r_{o4} = \frac{100}{0.496} = 202 \text{ k}\Omega$$

Now

$$\frac{V_x}{r_{o2}} = V_{\pi 4} \left[ \frac{1}{6.29 \parallel 761} + \frac{1}{24400} + 0.158 \right] \Rightarrow$$

which yields

$$V_{\pi 4} = \frac{V_x}{(0.318)r_{o2}}$$

From (1),

$$I_x = \frac{V_x}{r_{o2}} + \frac{V_x}{r_{o4}} + V_{\pi 4} \left( g_{m4} - g_{m2} - \frac{1}{r_{o2}} \right)$$

$$\frac{I_x}{V_x} = \left[ \frac{1}{24400} + \frac{1}{202} + \frac{\left( 19.08 - 0.158 - \frac{1}{24400} \right)}{(0.318)(24400)} \right]$$

which yields

$$R_{o2} = \frac{V_x}{I_x} = 135 \text{ k}\Omega$$


Now

$$r_{o6} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

Then

$$R_o = R_{o2} \parallel r_{o6} = 135 \parallel 160 \Rightarrow R_o = 73.2 \text{ k}\Omega$$
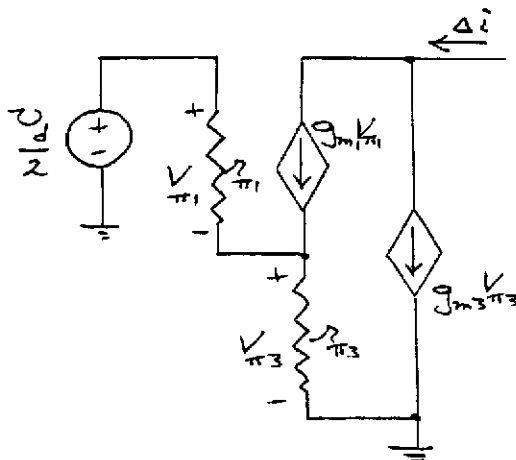
$$(b) A_d = g_m^c R_o \text{ where } g_m^c = \frac{\Delta i}{v_d/2}$$



$$\Delta i = g_{m1} V_{\pi 1} + g_{m3} V_{\pi 3} \text{ and } V_{\pi 1} + V_{\pi 3} = \frac{v_d}{2}$$

$$\text{Also } \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} \right) r_{\pi 3} = V_{\pi 3}$$

$$\text{So } V_{\pi 1} \left( \frac{1+\beta}{r_{\pi 1}} \right) r_{\pi 3} = V_{\pi 3}$$

Or

$$V_{\pi 1} \left( \frac{121}{761} \right) (6.29) = V_{\pi 3} \equiv V_{\pi 1}$$

$$\text{Then } 2V_{\pi 1} = \frac{v_d}{2} \Rightarrow V_{\pi 1} = \frac{v_d}{4}$$

So

$$\Delta i = (g_{m1} + g_{m3}) V_{\pi 1} = (0.158 + 19.08) \left( \frac{v_d}{4} \right) = 9.62 \left( \frac{v_d}{2} \right)$$

So

$$g_m^c = \frac{\Delta i}{v_d/2} = 9.62 \Rightarrow A_d = (9.62)(73.2) \Rightarrow$$

$$A_d = 704$$

Now


$$R_{id} = 2R_i \text{ where } R_i = r_{\pi 1} + (1+\beta)r_{\pi 3}$$

$$R_i = 761 + (121)(6.29) = 1522 \text{ k}\Omega$$

Then

$$R_{id} = 3.044 \text{ M}\Omega$$

11.43

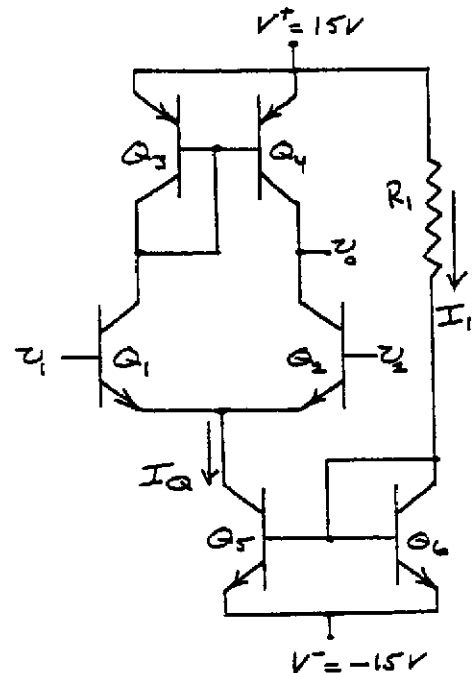

$$a. \quad g_f = \frac{I_Q}{4V_T} \Rightarrow I_Q = g_f(4V_T) = (8)(4)(0.026) \\ \Rightarrow I_Q = 0.832 \text{ mA}$$

Neglecting base currents,

$$R_1 = \frac{30 - 0.7}{0.832} \Rightarrow \underline{R_1 = 35.2 \text{ k}\Omega}$$

$$\text{b. } r_{o4} = r_{o2} = \frac{V_A}{I_{CQ}} = \frac{100}{0.416} = 240 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.416}{0.026} = 16 \text{ mA/V}$$

$$A_d = g_m(r_{o2} \parallel r_{o4}) = 16(240 \parallel 240)$$

$$\Rightarrow \underline{A_d = 1920}$$

$$R_{id} = 2r_{\pi}, \quad r_{\pi} = \frac{(180)(0.026)}{0.416} = 11.25 \text{ k}\Omega$$

$$\Rightarrow \underline{R_{id} = 22.5 \text{ k}\Omega}$$

$$R_o = r_{o2} \parallel r_{o4} \Rightarrow \underline{R_o = 120 \text{ k}\Omega}$$

c. Max. common-mode voltage when

$$V_{CB} = 0 \text{ for } Q_1 \text{ and } Q_2.$$

Therefore

$$v_{cm}(\text{max}) = V^+ - V_{EB}(Q_3) = 15 - 0.7$$

$$v_{cm}(\text{max}) = 14.3 \text{ V}$$

Min. common-mode voltage when

$$V_{CB} = 0 \text{ for } Q_3.$$

Therefore

$$v_{cm}(\text{min}) = 0.7 + 0.7 + (-15) = -13.6 \text{ V}$$

$$\text{So } \underline{-13.6 \leq v_{cm} \leq 14.3 \text{ V}}$$

$$R_{icm} \approx \frac{1}{2}(1 + \beta)(2R_o)$$

$$R_o = \frac{V_A}{I_Q} = \frac{100}{0.832} = 120 \text{ k}\Omega$$

$$R_{icm} = (181)(120) \Rightarrow \underline{R_{icm} = 21.7 \text{ M}\Omega}$$

11.44

$$\text{a. } I_o = I_{B3} + I_{B4} \approx 2 \left( \frac{I_Q}{2} \right) \left( \frac{1}{\beta} \right)$$

$$I_o = \frac{I_Q}{\beta} = \frac{0.2}{100} \Rightarrow \underline{I_o = 2 \mu\text{A}}$$

$$\text{b. } r_{o2} = r_{o4} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1} = 1000 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$A_d = g_m(r_{o2} \parallel r_{o4}) = (3.846)(1000 \parallel 1000)$$

$$\Rightarrow \underline{A_d = 1923}$$


$$\text{c. } A_d = g_m(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$A_d = (3.846)(1000 \parallel 1000 \parallel 250)$$

$$\Rightarrow \underline{A_d = 641}$$

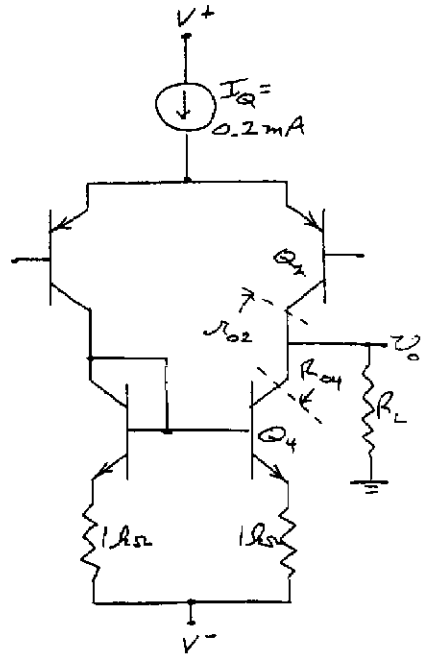11.45

$$\text{Let } \beta = 100, \quad V_A = 100 \text{ V}$$



$$r_{o2} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1} = 1000 \text{ k}\Omega$$

$$R_{o4} = r_{o4} [1 + g_m R'_g] \text{ where } R'_g = r_{\pi} \parallel R_g$$

Now

$$r_{\pi} = \frac{(100)(0.026)}{0.1} = 26 \text{ k}\Omega$$

$$g_m = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$R'_g = 26 \parallel 1 = 0.963 \text{ k}\Omega$$

Then

$$R_{o4} = 1000 [1 + (3.846)(0.963)] = 4704 \text{ k}\Omega$$

$$A_d = g_m(r_{o2} \parallel R_{o4}) = 3.846(1000 \parallel 4704) \Rightarrow$$

$$\underline{A_d = 3172}$$

11.46

$$\text{a. } A_d = g_m(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{I_Q}{2V_T}$$

$$r_{o2} = \frac{V_{A2}}{I_{CQ}} = \frac{125}{I_{CQ}}$$

$$r_{o4} = \frac{V_{A4}}{I_{CQ}} = \frac{80}{I_{CQ}}$$

If  $I_Q = 2 \text{ mA}$ , then  $g_m = 38.46 \text{ mA/V}$

$$r_{o2} = 125 \text{ k}\Omega, r_{o4} = 80 \text{ k}\Omega$$

$$\text{So } A_d = 38.46[125 \parallel 80 \parallel 200]$$

$$\text{Or } A_d = 1508$$

For each gain of 1000, lower the current level

For  $I_Q = 0.60 \text{ mA}$ ,  $I_{CQ} = 0.30 \text{ mA}$

$$g_m = \frac{0.3}{0.026} = 11.54 \text{ mA/V}$$

$$r_{o2} = \frac{125}{0.3} = 417 \text{ k}\Omega$$

$$r_{o4} = \frac{80}{0.3} = 267 \text{ k}\Omega$$

$$A_d = 11.54[417 \parallel 267 \parallel 200] = 1036$$

So  $I_Q = 0.60 \text{ mA}$  is adequate

$$\text{b. For } V^+ = 10 \text{ V}, V_{BE} = V_{EB} = 0.6 \text{ V}$$

For  $V_{CB} = 0$ ,

$$v_{cm}(\text{max}) = V^+ - 2V_{BE} = 10 - 2(0.6)$$

$$\text{Or } v_{cm}(\text{max}) = 8.8 \text{ V}$$

11.48

a. From symmetry,

$$V_{GS3} = V_{GS4} = V_{DS3} = V_{DS4} = \sqrt{\frac{0.1}{0.1}} + 1$$

$$\text{Or } V_{DS3} = V_{DS4} = 2 \text{ V}$$

$$V_{SG1} = V_{SG2} = \sqrt{\frac{0.1}{0.1}} + 1 = 2 \text{ V}$$

$$V_{SD1} = V_{SD2} = V_{SG1} - (V_{DS3} - 10) \\ = 2 - (2 - 10)$$

$$\text{Or } V_{SD1} = V_{SD2} = 10 \text{ V}$$

$$\text{b. } r_{on} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.01)(0.1)} \Rightarrow 1 \text{ M}\Omega$$

$$r_{op} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.015)(0.1)} \Rightarrow 0.667 \text{ M}\Omega$$

$$g_m = 2K_p(V_{GS} + V_{TP}) \\ = 2(0.1)(2 - 1) = 0.2 \text{ mA/V}$$

$$A_d = g_m(r_{on} \parallel r_{op}) = (0.2)(1000 \parallel 667)$$

$$\Rightarrow A_d = 80$$

$$\text{(c) } I_{D2} = I_{D1} = \frac{I_Q}{2} = 0.1 \text{ mA}$$

$$r_{on} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.01)(0.1)} = 1000 \text{ k}\Omega$$

$$r_{op} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$R_o = r_{on} \parallel r_{op} = 667 \parallel 1000 = 400 \text{ k}\Omega$$

11.49

$$A_d = g_m(r_{o2} \parallel r_{o4})$$

$$g_m = 2\sqrt{k_n I_{DQ}} = 2\sqrt{(0.12)(0.075)} \\ = 0.1897 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.015)(0.075)} = 889 \text{ k}\Omega$$


$$r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.075)} = 667 \text{ k}\Omega$$

$$A_d = (0.1897)(889 \parallel 667)$$

$$\Rightarrow A_d = 72.3$$

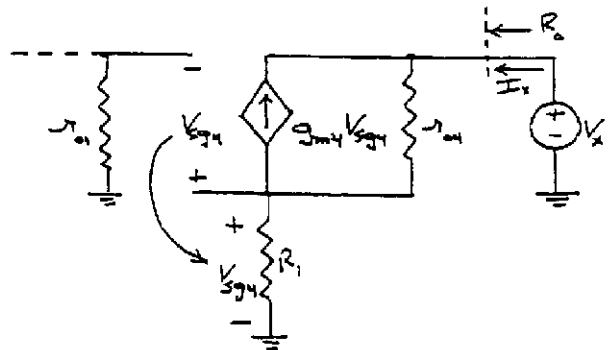11.50

Resistance looking into drain of  $M_1$ .



$$V_{sg4} = I_X R_1$$

$$I_X = g_{m4} V_{sg4} = \frac{V_X - V_{sg4}}{r_{o4}}$$

$$I_X \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right] = \frac{V_X}{r_{o4}}$$

$$\text{Or } R_o = r_{o4} \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right]$$

$$\text{a. } A_d = g_{m2}(r_{o2} \parallel R_o)$$

$$g_{m2} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.080)(0.1)} \\ = 0.179 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$g_{m4} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.080)(0.1)} \\ = 0.179 \text{ mA/V}$$

$$r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$R_o = 500 \left[ 1 + (0.179)(1) + \frac{1}{500} \right] = 590.5 \text{ k}\Omega$$

$$A_d = (0.179)[667 \parallel 590.5]$$

$$\Rightarrow A_d = 56.06$$



b. When  $R_1 = 0$ ,  $R_o = r_{o4} = 500 \text{ k}\Omega$

$$A_d = (0.179)[667\|500]$$

$$\Rightarrow A_d = 51.15$$

(c) For part (a),  $R_o = r_{o2}\|R_o = 667\|590.5 \Rightarrow$

$$R_o = 313 \text{ k}\Omega$$

For part (b),  $R_o = r_{o2}\|r_{o4} = 667\|500 \Rightarrow$

$$R_o = 286 \text{ k}\Omega$$

11.51

$$(a) A_d = 100 = g_m(r_{o2}\|r_{o4})$$

$$\text{Let } I_Q = 0.5 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.02)(0.25)} = 200 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.025)(0.25)} = 160 \text{ k}\Omega$$

Then

$$100 = g_m(200\|160) \Rightarrow g_m = 1.125 \text{ mA/V}$$

$$g_m = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$1.125 = 2\sqrt{\left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.25)} \Rightarrow \left(\frac{W}{L}\right)_n = 31.6$$

$$\text{Now } \left(\frac{W}{L}\right)_p \text{ somewhat arbitrary. Let } \left(\frac{W}{L}\right)_p = 31.6$$

11.52

$$A_d = g_m(r_{o2}\|r_{o4})$$

$$P = (I_Q + I_{REF})(V^+ - V^-)$$

$$\text{Let } I_Q = I_{REF}$$

$$\text{Then } 0.5 = 2I_Q(3 - (-3)) \Rightarrow I_Q = I_{REF} = 0.0417 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.015)(0.0208)} = 3205 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.02)(0.0208)} = 2404 \text{ k}\Omega$$

Then

$$A_d = 80 = g_m(3205\|2404) \Rightarrow g_m = 0.0582 \text{ mA/V}$$

$$g_m = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$0.0582 = 2\sqrt{\left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.0208)} \Rightarrow$$

$$\left(\frac{W}{L}\right)_n = 1.02$$

11.53

$$A_d = g_m(r_{o2}\|R_o)$$

$$\text{Want } A_d = 400$$

From Example 11.15,  $r_{o2} = 1 \text{ M}\Omega$

Assuming that  $g_m = 0.283 \text{ mA/V}$  for the PMOS from Example 11.15, then  $R_o = 285 \text{ M}\Omega$ .

So

$$400 = g_m(1000\|285000) \Rightarrow$$

$$g_m = 0.4014 \text{ mA/V} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{DQ}}$$

$$0.4014 = \left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.1) \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 10.1$$

11.54

$$A_d = g_m(R_{o4}\|R_{o6})$$

where

$$R_{o4} = r_{o4} + r_{o2}[1 + g_{m4}r_{o4}]$$

$$R_{o6} = r_{o6} + r_{o8}[1 + g_{m6}r_{o6}]$$

We have

$$r_{o2} = r_{o4} = \frac{1}{(0.015)(0.040)} = 1667 \text{ k}\Omega$$

$$r_{o6} = r_{o8} = \frac{1}{(0.02)(0.040)} = 1250 \text{ k}\Omega$$

$$g_{m4} = 2\sqrt{\left(\frac{0.060}{2}\right)(15)(0.040)} = 0.268 \text{ mA/V}$$

$$g_{m6} = 2\sqrt{\left(\frac{0.025}{2}\right)(10)(0.040)} = 0.141 \text{ mA/V}$$

Then

$$R_{o4} = 1667 + 1667[1 + (0.268)(1667)] \Rightarrow 748 \text{ M}\Omega$$

$$R_{o6} = 1250 + 1250[1 + (0.141)(1250)] \Rightarrow 222.8 \text{ M}\Omega$$

(a)

$$R_o = R_{o4}\|R_{o6} = 748\|222.8 \Rightarrow R_o = 172 \text{ M}\Omega$$

(b)

$$A_d = g_{m4}(R_{o4}\|R_{o6}) = (0.268)(172000) \Rightarrow A_d = 46096$$


11.55

$$g_{m1} = 2\sqrt{K_n I_{B1}} = 2\sqrt{(0.2)(0.25)}$$

$$= 0.447 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.75}{0.026} = 28.85 \text{ mA/V}$$
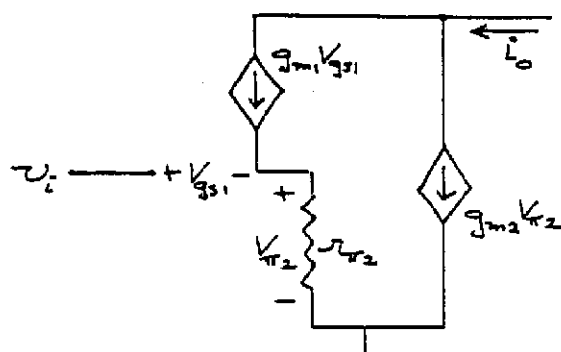
$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{0.75} = 4.16 \text{ k}\Omega$$



$$i_o = g_{m1}V_{gs1} + g_{m2}V_{\pi2}$$

$$V_{\pi2} = g_{m1}V_{gs1}r_{o2} \text{ and } v_i = V_{gs1} + V_{\pi2}$$

$$i_o = V_{gs1}(g_{m1} + g_{m2} \cdot g_{m1}r_{o2})$$

$$v_i = V_{gs1} + g_{m1}V_{gs1}r_{o2}$$

$$\text{and } V_{gs1} = \frac{v_i}{1 + g_{m1}r_{o2}}$$

$$i_o = v_i \cdot \frac{g_{m1}(1 + \beta)}{1 + g_{m1}r_{o2}}$$

$$g_m^C = \frac{i_o}{v_i} = \frac{g_{m1}(1 + \beta)}{1 + g_{m1}r_{o2}}$$

$$= \frac{(0.447)(121)}{1 + (0.447)(4.16)}$$

$$\Rightarrow g_m^C = 18.9 \text{ mA/V}$$

11.56

$$r_o(M_2) = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

$$r_o(Q_2) = \frac{V_A}{I_{CQ}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

$$g_m(M_2) = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(0.2)}$$

$$= 0.4 \text{ mA/V}$$

$$A_d = g_m(M_2)[r_o(M_2) \parallel r_o(Q_2)]$$


$$= 0.4[500 \parallel 400]$$

$$\Rightarrow A_d = 88.9$$

If the  $I_Q$  current source is ideal,

$$A_{cm} = 0 \text{ and } CMRR_{dB} = \infty$$

11.57

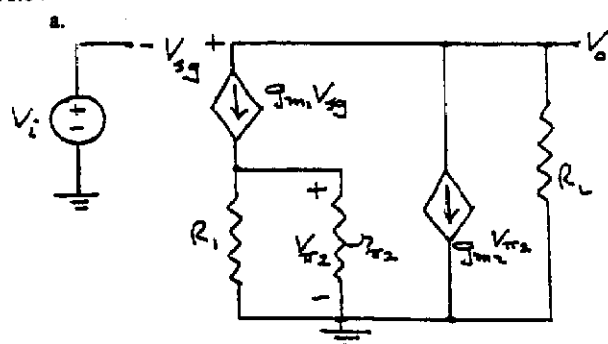

b. Assume  $R_L$  is capacitively coupled. Then

$$I_{CQ} + I_{DQ} = I_Q$$

$$I_{DQ} = \frac{V_{BE}}{R_1} = \frac{0.7}{8} = 0.0875 \text{ mA}$$

$$I_{CQ} = 0.9 - 0.0875 = 0.8125 \text{ mA}$$

$$g_{m1} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.0875)}$$

$$\Rightarrow g_{m1} = 0.592 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.8125}{0.026} \Rightarrow g_{m2} = 31.25 \text{ mA/V}$$

$$r_{\pi2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.8125} \Rightarrow r_{\pi2} = 3.2 \text{ k}\Omega$$

$$c. V_o = (-g_{m1}V_{gs1} - g_{m2}V_{\pi2})R_L$$

$$V_i + V_{gs1} = V_o \Rightarrow V_{gs1} = V_o - V_i$$

$$V_{\pi2} = (g_{m1}V_{gs1})(R_1 \parallel r_{\pi2})$$

$$V_o = -[g_{m1}V_{gs1} + g_{m2}g_{m1}V_{gs1}(R_1 \parallel r_{\pi2})]R_L$$

$$V_o = -(V_o - V_i)[g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi2})]R_L$$

$$A_v = \frac{V_o}{V_i} = \frac{[g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi2})]R_L}{1 + [g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi2})]R_L}$$

We find

$$g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi2})$$

$$= 0.592 + (31.25)(0.592)(8 \parallel 3.2)$$

$$= 42.88$$

$$\text{Then } A_v = \frac{(42.88)(R_L)}{1 + (42.88)(R_L)}$$

11.58

a. Assume  $R_L$  is capacitively coupled.

$$I_{DQ} = \frac{0.7}{8} = 0.0875 \text{ mA}$$

$$I_{CQ} = 1.2 - 0.0875 = 1.11 \text{ mA}$$


$$g_{m1} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.0875)}$$

$$\Rightarrow g_{m1} = 0.592 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{1.11}{0.026} \Rightarrow g_{m2} = 42.7 \text{ mA/V}$$

$$r_{\pi2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.11} \Rightarrow r_{\pi2} = 2.34 \text{ k}\Omega$$

b.

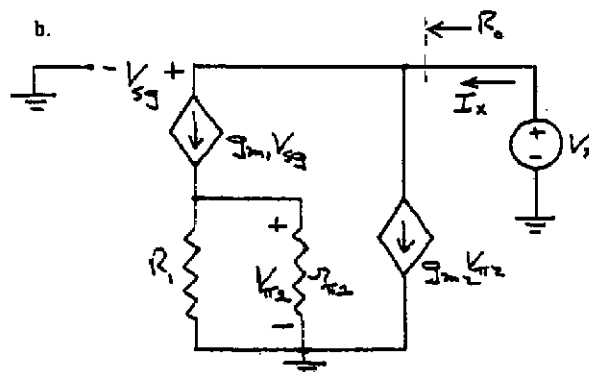

$$V_{sg} = V_X$$

$$I_X = g_{m2}V_{\pi 2} + g_{m1}V_{sg}$$

$$(g_{m1}V_{sg})(R_1 \parallel r_{\pi 2}) = V_{\pi 2}$$

$$I_X = V_X [g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})]$$


$$R_0 = \frac{V_X}{I_X} = \frac{1}{g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})}$$

$$= \frac{1}{0.592 + (0.592)(42.7)(8 \parallel 2.34)}$$

$$\Rightarrow R_0 = 21.6 \, \Omega$$

11.59

(a)

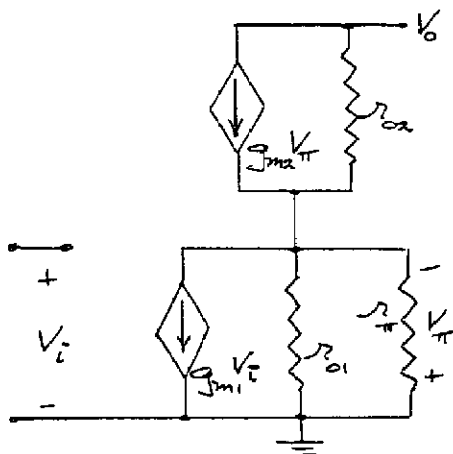

$$(1) \quad g_{m2}V_{\pi} + \frac{V_o - (-V_s)}{r_{o2}} = 0$$

$$(2) \quad g_{m2}V_{\pi} + \frac{V_o - (-V_s)}{r_{o2}} = g_{m1}V_i + \frac{-V_s}{r_{o1}} + \frac{-V_s}{r_s}$$

or

$$0 = g_{m1}V_i - V_s \left( \frac{1}{r_{o1}} + \frac{1}{r_s} \right)$$

Then

$$V_s = \frac{g_{m1}V_i}{\left( \frac{1}{r_{o1}} + \frac{1}{r_s} \right)}$$

From (1)

$$\left( g_{m2} + \frac{1}{r_{o1}} \right) V_{\pi} + \frac{V_o}{r_{o2}} = 0$$

$$V_o = -r_{o2} \left( g_{m2} + \frac{1}{r_{o1}} \right) V_{\pi} = -r_{o2} g_{m1} V_i \left( \frac{g_{m2} + \frac{1}{r_{o2}}}{\left( \frac{1}{r_{o1}} + \frac{1}{r_s} \right)} \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_{m1}r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)}{\left( \frac{1}{r_{o1}} + \frac{1}{r_s} \right)}$$

Now

$$g_{m1} = 2\sqrt{K_n I_Q} = 2\sqrt{(0.25)(0.025)} = 0.158 \text{ mA/V}$$

$$g_{m2} = \frac{I_Q}{V_T} = \frac{0.025}{0.026} = 0.9615 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda I_Q} = \frac{1}{(0.02)(0.025)} = 2000 \text{ k}\Omega$$


$$r_{o2} = \frac{V_A}{I_Q} = \frac{50}{0.025} = 2000 \text{ k}\Omega$$

$$r_s = \frac{\beta V_T}{I_Q} = \frac{(100)(0.026)}{0.025} = 104 \text{ k}\Omega$$

Then

$$A_v = \frac{-(0.158)(2000) \left( 0.9615 + \frac{1}{2000} \right)}{\left( \frac{1}{2000} + \frac{1}{104} \right)} \Rightarrow$$

$$A_v = -30039$$

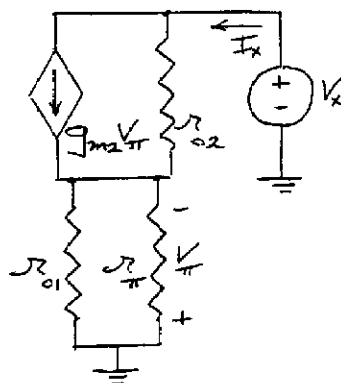To find  $R_0$ ; set  $V_i = 0 \Rightarrow g_{m1}V_i = 0$ 

$$I_x = g_{m2}V_{\pi} + \frac{V_x - (-V_s)}{r_{o2}}$$

$$V_s = -I_x(r_{o1} \parallel r_s)$$

Then

$$I_x = \left( g_{m2} + \frac{1}{r_{o2}} \right) (-I_x)(r_{o1} \parallel r_s) + \frac{V_x}{r_{o2}}$$


Combining terms,

$$R_0 = \frac{V_x}{I_x} = r_{o2} \left[ 1 + (r_{o1} \parallel r_s) \left( g_{m2} + \frac{1}{r_{o2}} \right) \right]$$

$$= 2000 \left[ 1 + (2000 \parallel 104) \left( 0.9615 + \frac{1}{2000} \right) \right] \Rightarrow$$

$$R_0 = 192.2 \text{ M}\Omega$$

(b)

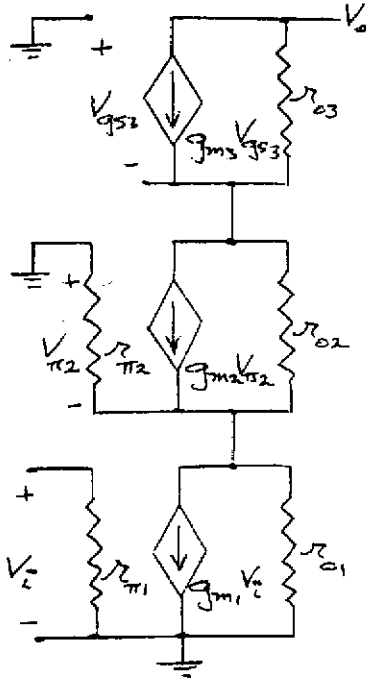

$$(1) \quad g_{m3}V_{o3} + \frac{V_o - (-V_{o3})}{r_{o3}} = 0$$

$$(2) \quad g_{m3}V_{o3} + \frac{V_o - (-V_{o3})}{r_{o3}} = g_{m2}V_{o2} + \frac{-V_{o3} - (-V_{o2})}{r_{o2}}$$

or

$$0 = V_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right) - \frac{V_{o3}}{r_{o2}}$$

$$(3) \quad \frac{V_{o2}}{r_{o2}} + g_{m2}V_{o2} + \frac{-V_{o3} - (-V_{o2})}{r_{o2}} = g_{m1}V_i + \frac{(-V_{o2})}{r_{o1}}$$

$$\text{From (2), } V_{o2} = \frac{V_{o3}}{r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)}$$

Then

$$(3) \quad V_{o2} \left( \frac{1}{r_{o2}} + g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right) = g_{m1}V_i + \frac{V_{o3}}{r_{o2}}$$

or

$$\begin{aligned} \frac{V_{o3}}{r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)} \left[ \frac{1}{r_{o2}} + g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right] &= g_{m1}V_i + \frac{V_{o3}}{r_{o2}} \\ \frac{V_{o3}}{2000 \left( 0.9615 + \frac{1}{2000} \right)} \left[ \frac{1}{104} + 0.9615 + \frac{1}{2000} + \frac{1}{2000} \right] &= 0.9615V_i + \frac{V_{o3}}{2000} \end{aligned}$$

$$\text{Then } V_{o3} = 1.83 \times 10^5 V_i$$


From (1),

$$\left( g_{m3} + \frac{1}{r_{o3}} \right) V_{o3} = \frac{-V_o}{r_{o3}}$$

or

$$V_o = -2000 \left( 0.158 + \frac{1}{2000} \right) (1.83 \times 10^5) V_i$$

$$A_v = \frac{V_o}{V_i} = -5.80 \times 10^7$$

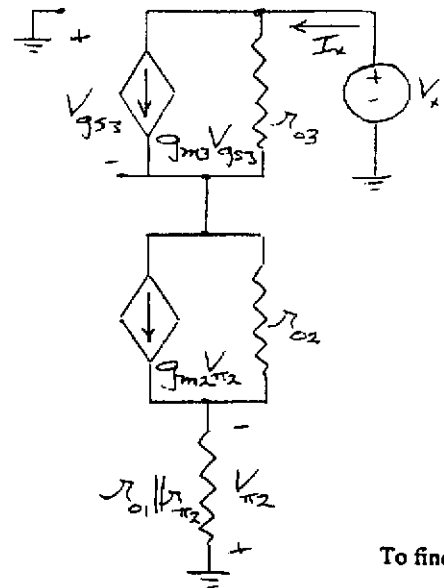To find  $R_o$ ,

$$(1) \quad I_x = g_{m3}V_{gs3} + \frac{V_x - (-V_{gs3})}{r_{o3}}$$

$$(2) \quad g_{m3}V_{gs3} + \frac{V_x - (-V_{gs3})}{r_{o3}} = g_{m2}V_{gs2} + \frac{-V_{gs3} - (-V_{gs2})}{r_{o2}}$$

$$(3) \quad V_{gs2} = -I_x(r_{o1} \parallel r_{o2})$$

$$\text{From (1) } I_x = V_{gs3} \left( g_{m3} + \frac{1}{r_{o3}} \right) + \frac{V_x}{r_{o3}}$$

$$I_x = V_{gs3} \left( 0.158 + \frac{1}{2000} \right) + \frac{V_x}{2000}$$

So

$$V_{gs3} = \frac{I_x - \frac{V_x}{2000}}{0.1585}$$

From (2),

$$V_{gs3} \left[ g_{m3} + \frac{1}{r_{o3}} + \frac{1}{r_{o2}} \right] + \frac{V_x}{r_{o3}} = V_{gs2} \left( g_{m2} + \frac{1}{r_{o2}} \right)$$

$$\begin{aligned} V_{gs3} \left[ 0.158 + \frac{1}{2000} + \frac{1}{2000} \right] + \frac{V_x}{2000} &= V_{gs2} \left( 0.9615 + \frac{1}{2000} \right) \end{aligned}$$

Then

$$\left[ \frac{I_x - V_x/2000}{0.1585} \right] (0.159) + \frac{V_x}{2000} = -I_x (2000 \parallel 104) (0.962)$$

We find

$$R_o = \frac{V_x}{I_x} = 6.09 \times 10^{10} \Omega$$

11.60

Assume emitter of  $Q_1$  is capacitively coupled to signal ground.

$$I_{CQ} = 0.2 \left( \frac{80}{81} \right) = 0.1975 \text{ mA}$$


$$I_{DQ} = \frac{0.2}{81} = 0.00247 \text{ mA}$$

$$r_\pi = \frac{(80)(0.026)}{0.1975} = 10.5 \text{ k}\Omega$$

$$g_m(Q_1) = \frac{0.1975}{0.026} = 7.60 \text{ mA/V}$$

$$g_m(M_1) = 2\sqrt{K_n I_D} = 2\sqrt{(0.2)(0.00247)}$$

$$g_m(M_1) = 0.0445 \text{ mA/V}$$

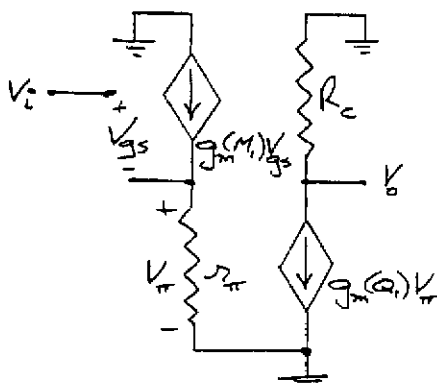

$$V_i = V_{gs} + V_{\pi} \text{ and } V_{\pi} = g_m(M_1) V_{gs} r_\pi$$

or

$$V_{gs} = \frac{V_i}{g_m(M_1) r_\pi}$$

Then

$$V_i = V_{\pi} \left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)$$

or

$$V_{\pi} = \frac{V_i}{\left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)}$$

$$V_o = -g_m(Q_1) V_{\pi} R_C \Rightarrow$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m(Q_1) R_C}{\left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)}$$

Then

$$A_v = \frac{-(7.60)(20)}{\left( 1 + \frac{1}{(0.0445)(10.5)} \right)} \Rightarrow$$

$$A_v = -48.4$$

11.61

Using the results from Chapter 4 for the emitter-follower:

$$R_o = R_s \parallel \left[ \frac{r_{\pi 8} + \frac{r_{\pi 9} + r_{o7} + R_{o11}}{1 + \beta}}{1 + \beta} \right]$$

$$r_{\pi 8} = \frac{\beta V_T}{I_{C8}} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$I_{C9} \approx \frac{I_{C8}}{\beta} = \frac{1}{100} = 0.01 \text{ mA}$$

$$r_{\pi 9} = \frac{(100)(0.026)}{0.01} = 260 \text{ k}\Omega$$

$$r_{o7} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$r_{o11} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$R_{o11} = r_{o11} [1 + g_m R'_E], \quad g_m = \frac{0.2}{0.026} = 7.69$$

$$r_{\pi 11} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$R'_E = 0.2 \parallel 13 = 0.197 \text{ k}\Omega$$

$$R_{o11} = 500 [1 + (7.69)(0.197)] = 1257 \text{ k}\Omega$$

Then

$$R_o = 5 \parallel \left[ \frac{2.6 + \frac{260 + 500 + 1257}{101}}{101} \right]$$

$$= 5 \parallel 0.223$$

$$\Rightarrow R_o = 0.213 \text{ k}\Omega$$

11.62

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$


$$r_{\pi 2} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$r_{\pi 1} = \frac{(100)(0.026)}{(0.5/100)} = \frac{(100)^2(0.026)}{0.5} = 520 \text{ k}\Omega$$

$$R_i = 520 + (101)(5.2) \Rightarrow R_i \approx 1.05 \text{ M}\Omega$$

$$R_o = 5 \parallel \frac{r_{\pi 3} + 50}{101}, \quad r_{\pi 3} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$
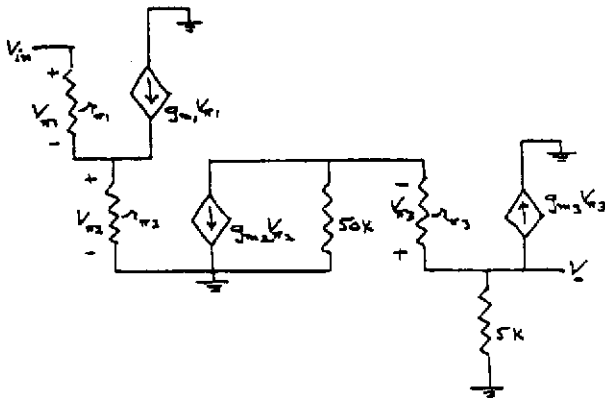
$$R_o = 5 \parallel \frac{2.6 + 50}{101} = 5 \parallel 0.521 \Rightarrow R_o = 0.472 \text{ k}\Omega$$



$$V_0 = -\left(\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3}\right)(5) \quad (1)$$

$$V_0 = -V_{\pi 3} \left(\frac{1 + \beta}{r_{\pi 3}}\right)(5)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} = g_{m2} V_{\pi 2} + \frac{(V_0 - V_{\pi 3})}{50}$$

$$g_{m2} V_{\pi 2} = V_{\pi 3} \left(\frac{1}{r_{\pi 3}} + \frac{1}{50}\right) - \frac{V_0}{50}$$

$$V_{\pi 2} = \left(\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1}\right) r_{\pi 2}$$

$$= V_{\pi 1} \left(\frac{1 + \beta}{r_{\pi 1}}\right) r_{\pi 2}$$

and

$$V_{in} = V_{\pi 1} + V_{\pi 2} \quad (2)$$

$$g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

Then

$$V_0 = -V_{\pi 3} \left(\frac{101}{2.6}\right)(5) \quad (1)$$

$$\Rightarrow V_{\pi 3} = -V_0(0.005149)$$

And

$$19.23 V_{\pi 2} = -V_0(0.005149) \left(\frac{1}{2.6} + \frac{1}{50}\right) - \frac{V_0}{50} \quad (2)$$

$$= -V_0(0.02208)$$

$$\text{Or } V_{\pi 2} = -V_0(0.001148)$$

And

$$V_{\pi 1} = V_{in} - V_{\pi 2} = V_{in} + V_0(0.001148) \quad (4)$$

So

$$-V_0(0.001148) = [V_{in} + V_0(0.001148)] \left(\frac{101}{520}\right)(5.2) \quad (3)$$

$$-V_0(0.001148) - V_0(0.001159) = V_{in}(1.01)$$

$$\Rightarrow A_v = \frac{V_0}{V_{in}} = -438$$

11.63

$$I_2 = \frac{5}{5} = 1 \text{ mA}$$


$$V_{GS2} = \sqrt{\frac{1}{0.5}} + 0.8 = 2.21 \text{ V}$$

$$I_1 = \frac{2.21 - (-5)}{35} = 0.206 \text{ mA}$$

(1)

(2)

(3)

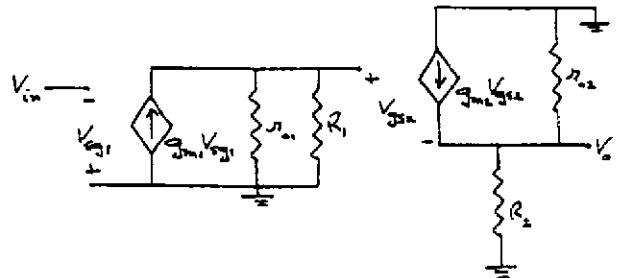

$$V_0 = (g_{m2} V_{gs2})(R_2 \parallel r_{o2})$$

$$V_{gs2} = (g_{m1} V_{gs1})(r_{o1} \parallel R_1) - V_0$$

$$\text{and } V_{gs1} = -V_{in}$$

So

$$V_{gs2} = -(g_{m1} V_{in})(r_{o1} \parallel R_1) - V_0$$

Then

$$V_0 = g_{m2} (R_2 \parallel r_{o2}) [-(g_{m1} V_{in})(r_{o1} \parallel R_1) - V_0]$$

$$A_v = \frac{V_0}{V_{in}} = \frac{-g_{m2} (R_2 \parallel r_{o2}) g_{m1} (r_{o1} \parallel R_1)}{1 + g_{m2} (R_2 \parallel r_{o2})}$$

$$g_{m2} = 2\sqrt{K_{n2} I_{D2}} = 2\sqrt{(0.5)(1)} = 1.414 \text{ mA/V}$$

$$g_{m1} = 2\sqrt{K_{p1} I_{D1}} = 2\sqrt{(0.2)(0.206)} = 0.406 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{(0.01)(0.206)} = 485 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} = \frac{1}{(0.01)(1)} = 100 \text{ k}\Omega$$

$$R_2 \parallel r_{o2} = 5 \parallel 100 = 4.76 \text{ k}\Omega$$

$$R_1 \parallel r_{o1} = 35 \parallel 485 = 32.6 \text{ k}\Omega$$

Then

$$A_v = \frac{-(1.414)(4.76)(0.406)(32.6)}{1 + (1.414)(4.76)}$$

So

$$\Rightarrow A_v = -11.5$$

Output Resistance—From the results for a source follower in Chapter 6.

$$R_o = \frac{1}{g_{m2}} \parallel R_2 \parallel r_{o2} = \frac{1}{1.414} \parallel 5 \parallel 100$$

$$= 0.707 \parallel 4.76$$

$$\text{So } R_o = 0.616 \text{ k}\Omega$$

11.64

$$\text{a. } R_2 = \frac{5}{0.5} \Rightarrow R_2 = 10 \text{ k}\Omega$$

$$V_{SG2} = \sqrt{\frac{I_{D2}}{K_{p2}}} - V_{TP2} = \sqrt{\frac{0.5}{0.25}} + 1 = 2.41 \text{ V}$$

$$R_1 = \frac{5 - (-2.41)}{0.1} \Rightarrow R_1 = 74.1 \text{ k}\Omega$$

b.



$$V_o = -(g_{m2} V_{gs2})(r_{o2} \parallel R_2)$$

$$V_{gs2} = V_o - [-(g_{m1} V_{gs1})(r_{o1} \parallel R_1)]$$

$$\text{and } V_{gs1} = V_{in}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{-(g_{m2})(r_{o2} \parallel R_2)(g_{m1})(r_{o1} \parallel R_1)}{1 + (g_{m2})(r_{o2} \parallel R_2)}$$

$$g_{m1} = 2\sqrt{K_{n1}I_{D1}} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_{p2}I_{D2}} = 2\sqrt{(0.25)(0.5)} = 0.707 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{(0.01)(0.1)} = 1000 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} = \frac{1}{(0.01)(0.5)} = 200 \text{ k}\Omega$$

$$r_{o2} \parallel R_2 = 200 \parallel 10 = 9.52 \text{ k}\Omega$$

$$r_{o1} \parallel R_1 = 1000 \parallel 74.1 = 69.0 \text{ k}\Omega$$

Then

$$A_v = \frac{-(0.707)(9.52)(0.2)(69)}{1 + (0.707)(9.52)}$$

So

$$\Rightarrow A_v = -12.0$$

$$R_o = \frac{1}{g_{m2}} \parallel R_2 \parallel r_{o2} = \frac{1}{0.707} \parallel 10 \parallel 200$$

$$= 1.414 \parallel 9.52$$

$$\text{Or } R_o = 1.23 \text{ k}\Omega$$

11.65

$$\text{a. } I_{C2} = 0.25 \text{ mA}$$

$$R = \frac{5 - 2}{0.25} \Rightarrow R = 12 \text{ k}\Omega$$

$$I_{C3} = \frac{v_{o2} - V_{BE(on)}}{R_{E1}} \Rightarrow R_{E1} = \frac{2 - 0.7}{0.5}$$

$$\Rightarrow R_{E1} = 2.6 \text{ k}\Omega$$

$$R_C = \frac{5 - v_{o3}}{I_{C3}} = \frac{5 - 3}{0.5} \Rightarrow R_C = 4 \text{ k}\Omega$$

$$I_{C4} = \frac{[v_{o3} - V_{BE(on)}] - (-5)}{R_{E2}}$$

$$R_{E2} = \frac{3 - 0.7 + 5}{3} \Rightarrow R_{E2} = 2.43 \text{ k}\Omega$$

b. Input resistance to base of  $Q_1$ .

$$R_{i3} = r_{\pi3} + (1 + \beta)R_{E1}$$

$$r_{\pi3} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$R_{i3} = 5.2 + (101)(2.6) = 267.8 \text{ k}\Omega$$

$$A_{d1} = \frac{v_{o2}}{v_d} = \frac{1}{2}g_{m2}(R \parallel R_{i3})$$

$$g_{m2} = \frac{0.25}{0.026} = 9.62 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2}(9.62)(12 \parallel 267.8) \Rightarrow A_{d1} = 55.2$$

$$\text{Now } \frac{v_{o3}}{v_{o2}} = \frac{-\beta(R_C \parallel R_{i4})}{r_{\pi3} + (1 + \beta)R_{E1}}$$

$$\text{where } R_{i4} = r_{\pi4} + (1 + \beta)R_{E2}$$

$$\text{and } \frac{v_o}{v_{o3}} = \frac{(1 + \beta)R_{E2}}{r_{\pi4} + (1 + \beta)R_{E2}}$$

$$r_{\pi4} = \frac{(100)(0.026)}{3} = 0.867 \text{ k}\Omega$$

$$\frac{v_o}{v_{o3}} = \frac{(101)(2.43)}{0.867 + (101)(2.43)} = 0.9965$$

$$R_{i4} = 0.867 + (101)(2.43) = 246.3 \text{ k}\Omega$$

$$r_{\pi3} = 5.2 \text{ k}\Omega$$

So

$$\frac{v_{o3}}{v_{o2}} = \frac{-(100)(4 \parallel 246.3)}{5.2 + (101)(2.6)} = -1.47$$

So

$$A_d = \frac{v_o}{v_d} = (55.2)(0.9965)(-1.47)$$

$$\Rightarrow A_d = -80.9$$

c. Using Equation (11.32b)

$$A_{cm1} = \frac{-g_{m2}(R \parallel R_{i3})}{1 + \frac{2(1 + \beta)R_o}{r_{\pi2}}}$$

$$r_{\pi2} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$A_{cm1} = \frac{-(9.62)(12 \parallel 267.8)}{1 + \frac{2(101)(100)}{10.4}} = \frac{-0.0569}{10.4} = A_{cm1}$$

Then

$$A_{cm} = \left( \frac{v_o}{v_{o3}} \right) \left( \frac{v_{o3}}{v_{o2}} \right) \cdot A_{cm1}$$

$$= (0.9965)(-1.47)(-0.0569)$$

$$\Rightarrow A_{cm} = 0.08335$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{80.9}{0.08335} \right)$$

$$\Rightarrow CMRR_{dB} = 59.7 \text{ dB}$$

11.66

$$a. \quad R_{C1} = \frac{10 - v_{o1}}{I_{C1}} = \frac{10 - 2}{0.1} \Rightarrow R_{C1} = 80 \text{ k}\Omega$$

$$R_{C2} = \frac{10 - v_{o4}}{I_{C4}} = \frac{10 - 6}{0.2} \Rightarrow R_{C2} = 20 \text{ k}\Omega$$

$$b. \quad A_{d1} = \frac{v_{o1} - v_{o2}}{v_d} = -g_{m1}(R_{C1} \parallel r_{\pi3})$$

$$g_{m1} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$r_{\pi3} = \frac{(180)(0.026)}{0.2} = 23.4 \text{ k}\Omega$$

$$A_{d1} = -(3.846)(80 \parallel 23.4) \Rightarrow A_{d1} = -59.5$$

$$A_{d2} = \frac{v_{o4}}{v_{o1} - v_{o2}} = \frac{1}{2} g_{m4} R_{C2}$$

$$g_{m4} = \frac{0.2}{0.026} = 7.692 \text{ mA/V}$$

$$A_{d2} = \frac{1}{2}(7.692)(20) = 76.9$$

$$\text{Then } A_d = (76.9)(-59.5)$$

$$\Rightarrow A_d = -5352$$

11.67

- a. Neglect the effect of  $r_o$  in determining the differential-mode gain.

$$A_{d1} = \frac{v_{o1}}{v_d} = \frac{1}{2} g_{m1}(R_C \parallel R_{i3})$$

$$\text{where } R_{i3} = r_{\pi3} + (1 + \beta)R_E$$

$$A_2 = \frac{-\beta R_{C2}}{r_{\pi3} + (1 + \beta)R_E}$$

$$I_1 = \frac{12 - 0.7 - (-12)}{R_1} = \frac{23.3}{12} = 1.94 \text{ mA} \approx I_{C3}$$

$$g_{m2} = \frac{\frac{1}{2}(1.94)}{0.026} = 37.3 \text{ mA/V}$$

$$r_{\pi3} = \frac{(200)(0.026)}{I_{C3}}$$

$$v_{o2} = 12 - \frac{1}{2}(1.94)(8) = 4.24 \text{ V}$$

$$I_{C3} = \frac{4.24 - 0.7}{3.3} = 1.07 \text{ mA}$$

$$r_{\pi3} = \frac{(200)(0.026)}{1.07} = 4.86 \text{ k}\Omega$$

$$R_{i3} = 4.86 + (201)(3.3) = 668 \text{ k}\Omega$$

$$A_{d1} = \frac{1}{2}(37.3)(8 \parallel 668) = 147.4$$

$$A_2 = \frac{-(200)(4)}{4.86 + (201)(3.3)} = -1.197$$

Then

$$A_d = A_{d1} \cdot A_2 = (147.4)(-1.197) \Rightarrow A_d = -176$$

$$R_o = r_{o5} = \frac{V_A}{I_{C5}} = \frac{80}{1.94} = 41.2 \text{ k}\Omega$$

$$A_{cm1} = \frac{-g_{m2}(R_C \parallel R_{i3})}{1 + \frac{2(1 + \beta)R_o}{r_{\pi2}}}$$

$$r_{\pi2} = \frac{(200)(0.026)}{\frac{1}{2}(1.94)} = 5.36 \text{ k}\Omega$$

$$A_{cm1} = \frac{-(37.3)(8 \parallel 668)}{1 + \frac{2(201)(41.2)}{5.36}} = -0.09539$$

$$A_2 = -1.197$$

$$A_{cm} = (-0.09539)(-1.197) \Rightarrow A_{cm} = 0.114$$

$$b. \quad v_d = v_1 - v_2 = 2.015 \sin \omega t - 1.985 \sin \omega t$$

$$v_d = 0.03 \sin \omega t \text{ (V)}$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 2.0 \sin \omega t$$

$$v_{o3} = A_d v_d + A_{cm} v_{cm}$$

$$= (-176)(0.03) + (0.114)(2)$$

Or

$$v_{o3} = -5.052 \sin \omega t$$

$$\text{Ideal, } A_{cm} = 0$$

So

$$v_{o3} = A_d v_d = (-176)(0.03)$$

$$v_{o3} = -5.28 \sin \omega t$$

$$c. \quad R_{id} = 2r_{\pi2} = 2(5.36) \Rightarrow R_{id} = 10.72 \text{ k}\Omega$$

$$2R_{icm} \approx 2(1 + \beta)R_o \parallel (1 + \beta)r_o$$

$$r_o = \frac{V_A}{I_{C2}} = \frac{80}{\frac{1}{2}(1.94)} = 82.5 \text{ k}\Omega$$

$$2R_{icm} = [2(201)(41.2)] \parallel [(201)(82.5)]$$

$$= 16.6 \text{ M}\Omega \parallel 16.6 \text{ M}\Omega$$

So

$$\Rightarrow R_{icm} = 4.15 \text{ M}\Omega$$



11.68

$$a. \quad I_1 = \frac{24 - V_{GS4}}{R_1} = k_n(V_{GS4} - V_{Th})^2$$

$$24 - V_{GS4} = (55)(0.2)(V_{GS4} - 2)^2$$

$$24 - V_{GS4} = 11(V_{GS4}^2 - 4V_{GS4} + 4)$$

$$11V_{GS4}^2 - 43V_{GS4} + 20 = 0$$

$$V_{GS4} = \frac{43 \pm \sqrt{(43)^2 - 4(11)(20)}}{2(11)} = 3.37 \text{ V}$$

$$I_1 = \frac{24 - 3.37}{55} = 0.375 \text{ mA} = I_Q$$

$$v_{o2} = 12 - \left(\frac{0.375}{2}\right)(40) = 4.5 \text{ V}$$

$$\frac{v_{o2} - V_{GS3}}{R_5} = I_{D3} = k_n(V_{GS3} - V_{Th})^2$$

$$4.5 - V_{GS3} = (0.2)(6)(V_{GS3}^2 - 4V_{GS3} + 4)$$

$$1.2V_{GS3}^2 - 3.8V_{GS3} + 0.3 = 0$$

$$V_{GS3} = \frac{3.8 \pm \sqrt{(3.8)^2 - 4(1.2)(0.3)}}{2(1.2)} = 3.09 \text{ V}$$

$$I_{D3} = \frac{4.5 - 3.09}{6} = 0.235 \text{ mA}$$

$$g_{m2} = 2\sqrt{K_n I_{D2}} = 2\sqrt{(0.2)\left(\frac{0.375}{2}\right)}$$

$$= 0.387 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2}g_{m2}R_D = \frac{1}{2}(0.387)(40)$$

$$\Rightarrow A_{d1} = 7.74$$

$$A_2 = \frac{-g_{m3}R_{D2}}{1 + g_{m3}R_5}$$

$$g_{m3} = 2\sqrt{K_n I_{D3}} = 2\sqrt{(0.2)(0.235)}$$

$$= 0.434 \text{ mA/V}$$

$$A_2 = \frac{-(0.434)(4)}{1 + (0.434)(6)} = -0.482$$

$$\text{So } A_d = A_{d1} \cdot A_2 = (7.74)(-0.482)$$

$$\Rightarrow A_d = -3.73$$

$$R_o = r_{o5} = \frac{1}{\lambda I_Q} = \frac{1}{(0.02)(0.375)} = 133 \text{ k}\Omega$$

$$A_{cm1} = \frac{-g_{m2}R_D}{1 + 2g_{m2}R_o} = \frac{-(0.387)(40)}{1 + 2(0.387)(133)}$$

$$= -0.149$$

$$A_{cm} = (-0.149)(-0.482) \Rightarrow A_{cm} = 0.0718$$

$$b. \quad v_d = v_1 - v_2 = 0.3 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 2 \sin \omega t$$

$$v_{o3} = A_d v_d + A_{cm} v_{cm}$$

$$= (-3.73)(0.3) + (0.0718)(2)$$

$$\Rightarrow v_{o3} = -0.975 \sin \omega t \text{ (V)}$$

$$\text{Ideal, } A_{cm} = 0$$

$$v_{o3} = A_d v_d = (-3.73)(0.3)$$

Or

$$\Rightarrow v_{o3} = -1.12 \sin \omega t \text{ (V)}$$

11.69

The low-frequency, one-sided differential gain is

$$A_{v2} = \frac{v_{o2}}{v_d} = \frac{1}{2}g_m R_C \left( \frac{r_\pi}{r_\pi + R_B} \right)$$

$$= \frac{\frac{1}{2}\beta R_C}{r_\pi + R_B}$$

$$r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$A_{v2} = \frac{\frac{1}{2}(100)(10)}{5.2 + 0.5} \Rightarrow A_{v2} = 87.7$$

$$C_M = C_\mu(1 + g_m R_C)$$

$$g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$C_M = 2[1 + (19.23)(10)] \Rightarrow C_M = 387 \text{ pF}$$

$$f_H = \frac{1}{2\pi[r_\pi \| R_B](C_\pi + C_M)}$$

$$= \frac{1}{2\pi[5.2 \| 0.5] \times 10^3 \times (8 + 387) \times 10^{-12}}$$

So

$$\Rightarrow f_H = 883 \text{ kHz}$$

11.70

a. From Equation (11.117),

$$f_z = \frac{1}{2\pi R_o C_o} = \frac{1}{2\pi(5 \times 10^4)(0.8 \times 10^{-12})}$$

$$\text{Or } f_z = 39.8 \text{ kHz}$$

b. From Problem 11.69,  $f_H = 883 \text{ kHz}$ . From Equation (11.116(b)), the low-frequency common-mode gain is

$$A_{cm} = \frac{-g_m R_C}{\left[ \left( 1 + \frac{R_B}{r_\pi} \right) + \frac{2(1 + \beta)R_o}{r_\pi} \right]}$$

$$r_\pi = 5.2 \text{ k}\Omega, g_m = 19.23 \text{ mA/V}$$

So


$$A_{cm} = \frac{-(19.23)(10)}{\left[ \left( 1 + \frac{0.5}{5.2} \right) + \frac{2(101)(5 \times 10^4)}{5.2 \times 10^3} \right]}$$

$$= -9.9 \times 10^{-4}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{87.7}{9.9 \times 10^{-4}} \right) = 98.9 \text{ dB}$$

11.72

The differential-mode half circuit is:

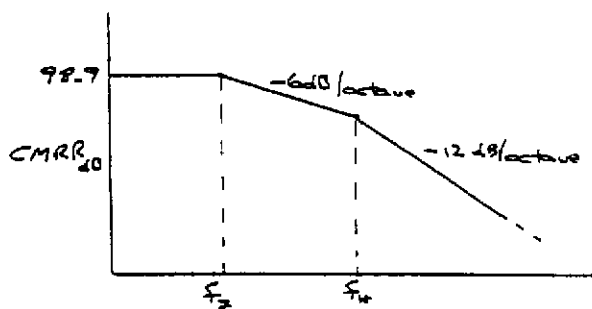

11.71

a. From Equation (7.72),

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Then

$$800 \times 10^6 = \frac{38.46 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

Or

$$C_\pi + C_\mu = 7.65 \times 10^{-12} \text{ F} = 7.65 \text{ pF}$$

And  $C_\pi = 6.65 \text{ pF}$ 

$$C_M = C_\mu(1 + g_m R_C) = 1[1 + (38.46)(10)]$$

$$= 386 \text{ pF}$$

$$f_H = \frac{1}{2\pi[r_\pi \| R_B](C_\pi + C_M)}$$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi[3.12 \| 1] \times 10^3 \times (6.65 + 386) \times 10^{-12}}$$

Or


$$f_H = 535 \text{ kHz}$$

b. From Equation (11.117),

$$f_Z = \frac{1}{2\pi R_O C_O} = \frac{1}{2\pi(10 \times 10^6)(10^{-12})}$$

Or

$$f_Z = 15.9 \text{ kHz}$$

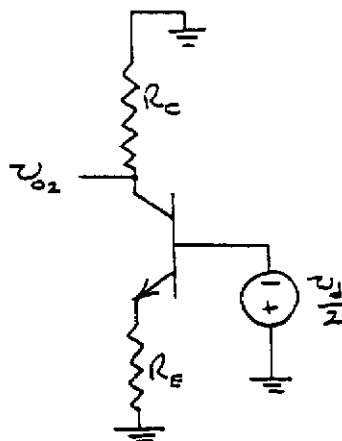

$$v_{o2} = \frac{g_m \left( \frac{v_d}{2} \right) R_C}{1 + \left( \frac{1 + \beta}{r_\pi} \right) R_E} \text{ or } A_v = \frac{\left( \frac{1}{2} \right) \beta R_C}{r_\pi + (1 + \beta) R_E}$$

$$r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$A_v = \frac{\left( \frac{1}{2} \right) (100)(10)}{5.2 + (101)R_E} = \frac{500}{5.2 + (101)R_E}$$

a. For  $R_E = 0.1 \text{ k}\Omega$ :  $A_v = 32.7$

b. For  $R_E = 0.25 \text{ k}\Omega$ :  $A_v = 16.4$