

### Chapter 9, Solution 1.

- (a) angular frequency  $\omega = \underline{10^3 \text{ rad/s}}$
- (b) frequency  $f = \frac{\omega}{2\pi} = \underline{159.2 \text{ Hz}}$
- (c) period  $T = \frac{1}{f} = \underline{6.283 \text{ ms}}$
- (d) Since  $\sin(A) = \cos(A - 90^\circ)$ ,  
 $v_s = 12 \sin(10^3 t + 24^\circ) = 12 \cos(10^3 t + 24^\circ - 90^\circ)$   
 $v_s$  in cosine form is  $v_s = \underline{12 \cos(10^3 t - 66^\circ) \text{ V}}$
- (e)  $v_s(2.5 \text{ ms}) = 12 \sin((10^3)(2.5 \times 10^{-3}) + 24^\circ)$   
 $= 12 \sin(2.5 + 24^\circ) = 12 \sin(143.24^\circ + 24^\circ)$   
 $= \underline{2.65 \text{ V}}$

### Chapter 9, Solution 2.

- (a) amplitude = 8 A
- (b)  $\omega = 500\pi = \underline{1570.8 \text{ rad/s}}$
- (c)  $f = \frac{\omega}{2\pi} = \underline{250 \text{ Hz}}$
- (d)  $I_s = 8 \angle -25^\circ \text{ A}$   
 $I_s(2 \text{ ms}) = 8 \cos((500\pi)(2 \times 10^{-3}) - 25^\circ)$   
 $= 8 \cos(\pi - 25^\circ) = 8 \cos(155^\circ)$   
 $= \underline{-7.25 \text{ A}}$

### Chapter 9, Solution 3.

- (a)  $4 \sin(\omega t - 30^\circ) = 4 \cos(\omega t - 30^\circ - 90^\circ) = \underline{4 \cos(\omega t - 120^\circ)}$
- (b)  $-2 \sin(6t) = \underline{2 \cos(6t + 90^\circ)}$
- (c)  $-10 \sin(\omega t + 20^\circ) = 10 \cos(\omega t + 20^\circ + 90^\circ) = \underline{10 \cos(\omega t + 110^\circ)}$

#### Chapter 9, Solution 4.

$$(a) \quad v = 8 \cos(7t + 15^\circ) = 8 \sin(7t + 15^\circ + 90^\circ) = \underline{8 \sin(7t + 105^\circ)}$$

$$(b) \quad i = -10 \sin(3t - 85^\circ) = 10 \cos(3t - 85^\circ + 90^\circ) = \underline{10 \cos(3t + 5^\circ)}$$

#### Chapter 9, Solution 5.

$$v_1 = 20 \sin(\omega t + 60^\circ) = 20 \cos(\omega t + 60^\circ - 90^\circ) = 20 \cos(\omega t - 30^\circ)$$

$$v_2 = 60 \cos(\omega t - 10^\circ)$$

This indicates that the phase angle between the two signals is 20° and that v<sub>1</sub> lags v<sub>2</sub>.

#### Chapter 9, Solution 6.

$$(a) \quad v(t) = 10 \cos(4t - 60^\circ)$$

$$i(t) = 4 \sin(4t + 50^\circ) = 4 \cos(4t + 50^\circ - 90^\circ) = 4 \cos(4t - 40^\circ)$$

Thus, i(t) leads v(t) by 20°.

$$(b) \quad v_1(t) = 4 \cos(377t + 10^\circ)$$

$$v_2(t) = -20 \cos(377t) = 20 \cos(377t + 180^\circ)$$

Thus, v<sub>2</sub>(t) leads v<sub>1</sub>(t) by 170°.

$$(c) \quad x(t) = 13 \cos(2t) + 5 \sin(2t) = 13 \cos(2t) + 5 \cos(2t - 90^\circ)$$

$$\mathbf{X} = 13 \angle 0^\circ + 5 \angle -90^\circ = 13 - j5 = 13.928 \angle -21.04^\circ$$

$$x(t) = 13.928 \cos(2t - 21.04^\circ)$$

$$y(t) = 15 \cos(2t - 11.8^\circ)$$

$$\text{phase difference} = -11.8^\circ + 21.04^\circ = 9.24^\circ$$

Thus, y(t) leads x(t) by 9.24°.

#### Chapter 9, Solution 7.

$$\text{If } f(\phi) = \cos \phi + j \sin \phi,$$

$$\frac{df}{d\phi} = -\sin \phi + j \cos \phi = j(\cos \phi + j \sin \phi) = j f(\phi)$$

$$\frac{df}{f} = j d\phi$$

Integrating both sides

$$\ln f = j\phi + \ln A$$

$$f = Ae^{j\phi} = \cos\phi + j \sin\phi$$

$$f(0) = A = 1$$

$$\text{i.e. } \underline{f(\phi) = e^{j\phi} = \cos\phi + j \sin\phi}$$

### Chapter 9, Solution 8.

$$\begin{aligned} \text{(a)} \quad \frac{15\angle 45^\circ}{3-j4} + j2 &= \frac{15\angle 45^\circ}{5\angle -53.13^\circ} + j2 \\ &= 3\angle 98.13^\circ + j2 \\ &= -0.4245 + j2.97 + j2 \\ &= \underline{\underline{-0.4243 + j4.97}} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad \frac{(2+j)(3-j4)}{8\angle -20^\circ} + \frac{10}{-5+j12} &= \frac{8\angle -20^\circ}{11.18\angle -26.57^\circ} + \frac{(-5-j12)(10)}{25+144} \\ &= 0.7156\angle 6.57^\circ - 0.2958 \\ &\quad -j0.71 \\ &= 0.7109 + j0.08188 - \\ &\quad 0.2958 - j0.71 \\ &= \underline{\underline{0.4151 - j0.6281}} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad 10 + (8\angle 50^\circ)(13\angle -68.38^\circ) &= 10 + 104\angle -17.38^\circ \\ &= \underline{\underline{109.25 - j31.07}} \end{aligned}$$

### Chapter 9, Solution 9.

$$\begin{aligned} \text{(a)} \quad 2 + \frac{3+j4}{5-j8} &= 2 + \frac{(3+j4)(5+j8)}{25+64} \\ &= 2 + \frac{15 + j24 + j20 - 32}{89} \\ &= \underline{\underline{1.809 + j0.4944}} \end{aligned}$$

$$\text{(b)} \quad 4\angle -10^\circ + \frac{1-j2}{3\angle 6^\circ} = 4\angle -10^\circ + \frac{2.236\angle -63.43^\circ}{3\angle 6^\circ}$$

$$\begin{aligned}
&= 4\angle -10^\circ + 0.7453\angle -69.43^\circ \\
&= 3.939 - j0.6946 + 0.2619 - j0.6978 \\
&= \underline{\underline{4.201 - j1.392}}
\end{aligned}$$

$$\begin{aligned}
(c) \quad \frac{8\angle 10^\circ + 6\angle -20^\circ}{9\angle 80^\circ - 4\angle 50^\circ} &= \frac{7.879 + j1.3892 + 5.638 - j2.052}{1.5628 + j8.863 - 2.571 - j3.064} \\
&= \frac{13.517 - j0.6629}{-1.0083 + j5.799} = \frac{13.533\angle -2.81^\circ}{5.886\angle 99.86^\circ} \\
&= 2.299\angle -102.67^\circ \\
&= \underline{\underline{-0.5043 - j2.243}}
\end{aligned}$$

### Chapter 9, Solution 10.

$$\begin{aligned}
(a) \quad z_1 &= 6 - j8, \quad z_2 = 8.66 - j5, \quad \text{and} \quad z_3 = -4 - j6.9282 \\
z_1 + z_2 + z_3 &= \underline{\underline{10.66 - j19.93}}
\end{aligned}$$

$$(b) \quad \frac{z_1 z_2}{z_3} = \underline{\underline{9.999 + j7.499}}$$

### Chapter 9, Solution 11.

$$\begin{aligned}
(a) \quad z_1 z_2 &= (-3 + j4)(12 + j5) \\
&= -36 - j15 + j48 - 20 \\
&= \underline{\underline{-56 + j33}}
\end{aligned}$$

$$(b) \quad \frac{z_1}{z_2^*} = \frac{-3 + j4}{12 - j5} = \frac{(-3 + j4)(12 + j5)}{144 + 25} = \underline{\underline{-0.3314 + j0.1953}}$$

$$\begin{aligned}
(c) \quad z_1 + z_2 &= (-3 + j4) + (12 + j5) = 9 + j9 \\
z_1 - z_2 &= (-3 + j4) - (12 + j5) = -15 - j \\
\frac{z_1 + z_2}{z_1 - z_2} &= \frac{9(1 + j)}{-(15 + j)} = \frac{-9(1 + j)(15 - j)}{15^2 - 1^2} = \frac{-9(16 + j14)}{226} \\
&= \underline{\underline{-0.6372 - j0.5575}}
\end{aligned}$$

**Chapter 9, Solution 12.**

$$\begin{aligned}
 \text{(a)} \quad z_1 z_2 &= (-3 + j4)(12 + j5) \\
 &= -36 - j15 + j48 - 20 \\
 &= \underline{\underline{-56 + j33}}
 \end{aligned}$$

$$\text{(b)} \quad \frac{z_1}{z_2^*} = \frac{-3 + j4}{12 - j5} = \frac{(-3 + j4)(12 + j5)}{144 + 25} = \underline{\underline{-0.3314 + j0.1953}}$$

$$\begin{aligned}
 \text{(c)} \quad z_1 + z_2 &= (-3 + j4) + (12 + j5) = 9 + j9 \\
 z_1 - z_2 &= (-3 + j4) - (12 + j5) = -15 - j \\
 \frac{z_1 + z_2}{z_1 - z_2} &= \frac{9(1 + j)}{-(15 + j)} = \frac{-9(1 + j)(15 - j)}{15^2 - 1^2} = \frac{-9(16 + j14)}{226} \\
 &= \underline{\underline{-0.6372 - j0.5575}}
 \end{aligned}$$

**Chapter 9, Solution 13.**

$$\text{(a)} \quad (-0.4324 + j0.4054) + (-0.8425 - j0.2534) = \underline{\underline{-1.2749 + j0.1520}}$$

$$\text{(b)} \quad \frac{50 \angle -30^\circ}{24 \angle 150^\circ} = \underline{\underline{-2.0833}}$$

$$\text{(c)} \quad (2 + j3)(8 - j5) - (-4) = \underline{\underline{35 + j14}}$$

**Chapter 9, Solution 14.**

$$\text{(a)} \quad \frac{3 - j14}{-15 + j11} = \underline{\underline{-0.5751 + j0.5116}}$$

$$\text{(b)} \quad \frac{(62.116 + j231.82 + 138.56 - j80)(60 - j80)}{(67 + j84)(16.96 + j10.5983)} = \frac{24186 - 6944.9}{246.06 + j2134.7} = \underline{\underline{-1.922 - j11.55}}$$

$$\text{(c)} \quad (-2 + j4)^2 \sqrt{(260 - j120)} = \underline{\underline{-256.4 - j200.89}}$$

**Chapter 9, Solution 15.**

$$(a) \quad \begin{vmatrix} 10+j6 & 2-j3 \\ -5 & -1+j \end{vmatrix} = -10-j6+j10-6+10-j15 \\ = \underline{\underline{-6-j11}}$$

$$(b) \quad \begin{vmatrix} 20\angle -30^\circ & -4\angle -10^\circ \\ 16\angle 0^\circ & 3\angle 45^\circ \end{vmatrix} = 60\angle 15^\circ + 64\angle -10^\circ \\ = 57.96 + j15.529 + 63.03 - j11.114 \\ = \underline{\underline{120.99 - j4.415}}$$

$$(c) \quad \begin{vmatrix} 1-j & -j & 0 \\ j & 1 & -j \\ 1 & j & 1+j \\ 1-j & -j & 0 \\ j & 1 & -j \end{vmatrix} = 1+1+0-1-0+j^2(1-j)+j^2(1+j) \\ = 1-1(1-j+1+j) \\ = 1-2 = \underline{\underline{-1}}$$

**Chapter 9, Solution 16.**

$$(a) \quad -10 \cos(4t + 75^\circ) = 10 \cos(4t + 75^\circ - 180^\circ) \\ = 10 \cos(4t - 105^\circ)$$

The phasor form is **10∠-105°**

$$(b) \quad 5 \sin(20t - 10^\circ) = 5 \cos(20t - 10^\circ - 90^\circ) \\ = 5 \cos(20t - 100^\circ)$$

The phasor form is **5∠-100°**

$$(c) \quad 4 \cos(2t) + 3 \sin(2t) = 4 \cos(2t) + 3 \cos(2t - 90^\circ)$$

The phasor form is  $4\angle 0^\circ + 3\angle -90^\circ = 4 - j3 = \underline{\underline{5\angle -36.87^\circ}}$

**Chapter 9, Solution 17.**

$$(a) \quad \text{Let } \mathbf{A} = 8\angle -30^\circ + 6\angle 0^\circ \\ = 12.928 - j4 \\ = 13.533\angle -17.19^\circ \\ a(t) = \underline{\underline{13.533 \cos(5t + 342.81^\circ)}}$$

- (b) We know that  $-\sin\alpha = \cos(\alpha + 90^\circ)$ .  
 Let  $\mathbf{B} = 20\angle 45^\circ + 30\angle(20^\circ + 90^\circ)$   
 $= 14.142 + j14.142 - 10.261 + j28.19$   
 $= 3.881 + j42.33$   
 $= 42.51\angle 84.76^\circ$   
 $b(t) = \underline{\underline{42.51 \cos(120\pi t + 84.76^\circ)}}$
- (c) Let  $\mathbf{C} = 4\angle -90^\circ + 3\angle(-10^\circ - 90^\circ)$   
 $= -j4 - 0.5209 - j2.954$   
 $= 6.974\angle 265.72^\circ$   
 $c(t) = \underline{\underline{6.974 \cos(8t + 265.72^\circ)}}$

### Chapter 9, Solution 18.

- (a)  $v_1(t) = \underline{\underline{60 \cos(t + 15^\circ)}}$
- (b)  $\mathbf{V}_2 = 6 + j8 = 10\angle 53.13^\circ$   
 $v_2(t) = \underline{\underline{10 \cos(40t + 53.13^\circ)}}$
- (c)  $i_1(t) = \underline{\underline{2.8 \cos(377t - \pi/3)}}$
- (d)  $\mathbf{I}_2 = -0.5 - j1.2 = 1.3\angle 247.4^\circ$   
 $i_2(t) = \underline{\underline{1.3 \cos(10^3t + 247.4^\circ)}}$

### Chapter 9, Solution 19.

- (a)  $3\angle 10^\circ - 5\angle -30^\circ = 2.954 + j0.5209 - 4.33 + j2.5$   
 $= -1.376 + j3.021$   
 $= 3.32\angle 114.49^\circ$   
 Therefore,  $3 \cos(20t + 10^\circ) - 5 \cos(20t - 30^\circ) = \underline{\underline{3.32 \cos(20t + 114.49^\circ)}}$
- (b)  $4\angle -90^\circ + 3\angle -45^\circ = -j40 + 21.21 - j21.21$   
 $= 21.21 - j61.21$   
 $= 64.78\angle -70.89^\circ$   
 Therefore,  $40 \sin(50t) + 30 \cos(50t - 45^\circ) = \underline{\underline{64.78 \cos(50t - 70.89^\circ)}}$
- (c) Using  $\sin\alpha = \cos(\alpha - 90^\circ)$ ,  
 $20\angle -90^\circ + 10\angle 60^\circ - 5\angle -110^\circ = -j20 + 5 + j8.66 + 1.7101 + j4.699$   
 $= 6.7101 - j6.641$   
 $= 9.44\angle -44.7^\circ$   
 Therefore,  $20 \sin(400t) + 10 \cos(400t + 60^\circ) - 5 \sin(400t - 20^\circ) = \underline{\underline{9.44 \cos(400t - 44.7^\circ)}}$

**Chapter 9, Solution 20.**

$$(a) \quad V = 4\angle -60^\circ - 90^\circ - 5\angle 40^\circ = -3.464 - j2 - 3.83 - j3.2139 = 8.966\angle -4.399^\circ$$

Hence,

$$\underline{v = 8.966 \cos(377t - 4.399^\circ)}$$

$$(b) \quad I = 10\angle 0^\circ + j\omega 8\angle 20^\circ - 90^\circ, \quad \omega = 5, \text{ i.e. } I = 10 + 40\angle 20^\circ = 49.51\angle 16.04^\circ$$

$$\underline{i = 49.51 \cos(5t + 16.04^\circ)}$$

**Chapter 9, Solution 21.**

$$(a) \quad F = 5\angle 15^\circ - 4\angle -30^\circ - 90^\circ = 6.8296 + j4.758 = 8.3236\angle 34.86^\circ$$

$$\underline{f(t) = 8.324 \cos(30t + 34.86^\circ)}$$

$$(b) \quad G = 8\angle -90^\circ + 4\angle 50^\circ = 2.571 - j4.9358 = 5.565\angle -62.49^\circ$$

$$\underline{g(t) = 5.565 \cos(t - 62.49^\circ)}$$

$$(c) \quad H = \frac{1}{j\omega} (10\angle 0^\circ + 5\angle -90^\circ), \quad \omega = 40$$

$$\text{i.e. } H = 0.25\angle -90^\circ + 0.125\angle -180^\circ = -j0.25 - 0.125 = 0.2795\angle -116.6^\circ$$

$$\underline{h(t) = 0.2795 \cos(40t - 116.6^\circ)}$$

**Chapter 9, Solution 22.**

$$\text{Let } f(t) = 10v(t) + 4\frac{dv}{dt} - 2\int_{-\infty}^t v(t)dt$$

$$F = 10V + j\omega 4V - \frac{2V}{j\omega}, \quad \omega = 5, \quad V = 20\angle -30^\circ$$

$$F = 10V + j20V - j0.4V = (10 - j19.6)(17.32 - j10) = 440.1\angle -92.97^\circ$$

$$\underline{f(t) = 440.1 \cos(5t - 92.97^\circ)}$$

**Chapter 9, Solution 23.**

(a)  $v(t) = \underline{40 \cos(\omega t - 60^\circ)}$

(b)  $V = -30\angle 10^\circ + 50\angle 60^\circ$   
 $= -4.54 + j38.09$   
 $= 38.36\angle 96.8^\circ$   
 $v(t) = \underline{38.36 \cos(\omega t + 96.8^\circ)}$

(c)  $I = j6\angle -10^\circ = 6\angle(90^\circ - 10^\circ) = 6\angle 80^\circ$   
 $i(t) = \underline{6 \cos(\omega t + 80^\circ)}$

(d)  $I = \frac{2}{j} + 10\angle -45^\circ = -j2 + 7.071 - j7.071$   
 $= 11.5\angle -52.06^\circ$   
 $i(t) = \underline{11.5 \cos(\omega t - 52.06^\circ)}$

**Chapter 9, Solution 24.**

(a)

$$V + \frac{V}{j\omega} = 10\angle 0^\circ, \quad \omega = 1$$
$$V(1 - j) = 10$$
$$V = \frac{10}{1 - j} = 5 + j5 = 7.071\angle 45^\circ$$

Therefore,  $v(t) = \underline{7.071 \cos(t + 45^\circ)}$

(b)

$$j\omega V + 5V + \frac{4V}{j\omega} = 20\angle(10^\circ - 90^\circ), \quad \omega = 4$$
$$V\left(j4 + 5 + \frac{4}{j4}\right) = 20\angle -80^\circ$$
$$V = \frac{20\angle -80^\circ}{5 + j3} = 3.43\angle -110.96^\circ$$

Therefore,  $v(t) = \underline{3.43 \cos(4t - 110.96^\circ)}$

**Chapter 9, Solution 25.**

(a)

$$2j\omega\mathbf{I} + 3\mathbf{I} = 4\angle -45^\circ, \quad \omega = 2$$

$$\mathbf{I}(3 + j4) = 4\angle -45^\circ$$

$$\mathbf{I} = \frac{4\angle -45^\circ}{3 + j4} = \frac{4\angle -45^\circ}{5\angle 53.13^\circ} = 0.8\angle -98.13^\circ$$

$$\text{Therefore, } i(t) = \underline{\mathbf{0.8 \cos(2t - 98.13^\circ)}}$$

(b)

$$10\frac{\mathbf{I}}{j\omega} + j\omega\mathbf{I} + 6\mathbf{I} = 5\angle 22^\circ, \quad \omega = 5$$

$$(-j2 + j5 + 6)\mathbf{I} = 5\angle 22^\circ$$

$$\mathbf{I} = \frac{5\angle 22^\circ}{6 + j3} = \frac{5\angle 22^\circ}{6.708\angle 26.56^\circ} = 0.745\angle -4.56^\circ$$

$$\text{Therefore, } i(t) = \underline{\mathbf{0.745 \cos(5t - 4.56^\circ)}}$$

**Chapter 9, Solution 26.**

$$j\omega\mathbf{I} + 2\mathbf{I} + \frac{\mathbf{I}}{j\omega} = 1\angle 0^\circ, \quad \omega = 2$$

$$\mathbf{I}\left(j2 + 2 + \frac{1}{j2}\right) = 1$$

$$\mathbf{I} = \frac{1}{2 + j1.5} = 0.4\angle -36.87^\circ$$

$$\text{Therefore, } i(t) = \underline{\mathbf{0.4 \cos(2t - 36.87^\circ)}}$$

**Chapter 9, Solution 27.**

$$j\omega\mathbf{V} + 50\mathbf{V} + 100\frac{\mathbf{V}}{j\omega} = 110\angle -10^\circ, \quad \omega = 377$$

$$\mathbf{V}\left(j377 + 50 - \frac{j100}{377}\right) = 110\angle -10^\circ$$

$$\mathbf{V}(380.6\angle 82.45^\circ) = 110\angle -10^\circ$$

$$\mathbf{V} = 0.289\angle -92.45^\circ$$

$$\text{Therefore, } v(t) = \underline{\mathbf{0.289 \cos(377t - 92.45^\circ)}}.$$

**Chapter 9, Solution 28.**

$$i(t) = \frac{v_s(t)}{R} = \frac{110 \cos(377t)}{8} = \underline{\underline{13.75 \cos(377t) \text{ A}}}.$$

**Chapter 9, Solution 29.**

$$Z = \frac{1}{j\omega C} = \frac{1}{j(10^6)(2 \times 10^{-6})} = -j0.5$$

$$V = IZ = (4 \angle 25^\circ)(0.5 \angle -90^\circ) = 2 \angle -65^\circ$$

Therefore  $v(t) = \underline{\underline{2 \sin(10^6 t - 65^\circ) \text{ V}}}.$

**Chapter 9, Solution 30.**

$$Z = j\omega L = j(500)(4 \times 10^{-3}) = j2$$

$$I = \frac{V}{Z} = \frac{60 \angle -65^\circ}{2 \angle 90^\circ} = 30 \angle -155^\circ$$

Therefore,  $i(t) = \underline{\underline{30 \cos(500t - 155^\circ) \text{ A}}}.$

**Chapter 9, Solution 31.**

$$i(t) = 10 \sin(\omega t + 30^\circ) = 10 \cos(\omega t + 30^\circ - 90^\circ) = 10 \cos(\omega t - 60^\circ)$$

Thus,  $I = 10 \angle -60^\circ$

$$v(t) = -65 \cos(\omega t + 120^\circ) = 65 \cos(\omega t + 120^\circ - 180^\circ) = 65 \cos(\omega t - 60^\circ)$$

Thus,  $V = 65 \angle -60^\circ$

$$Z = \frac{V}{I} = \frac{65 \angle -60^\circ}{10 \angle -60^\circ} = 6.5 \Omega$$

Since  $V$  and  $I$  are in phase, the element is a resistor with  $R = \underline{\underline{6.5 \Omega}}.$

**Chapter 9, Solution 32.**

$$\mathbf{V} = 180\angle 10^\circ, \quad \mathbf{I} = 12\angle -30^\circ, \quad \omega = 2$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{180\angle 10^\circ}{12\angle -30^\circ} = 15\angle 40^\circ = 11.49 + j9.642 \, \Omega$$

One element is a resistor with  $R = \underline{\mathbf{11.49 \, \Omega}}$ .

The other element is an inductor with  $\omega L = 9.642$  or  $L = \underline{\mathbf{4.821 \, H}}$ .

**Chapter 9, Solution 33.**

$$\begin{aligned} 110 &= \sqrt{v_R^2 + v_L^2} \\ v_L &= \sqrt{110^2 - v_R^2} \\ v_L &= \sqrt{110^2 - 85^2} = \underline{\mathbf{69.82 \, V}} \end{aligned}$$

**Chapter 9, Solution 34.**

$$v_o = 0 \text{ if } \omega L = \frac{1}{\omega C} \longrightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{(5 \times 10^{-3})(2 \times 10^{-3})}} = \underline{\mathbf{100 \, \text{rad/s}}}$$

**Chapter 9, Solution 35.**

$$\begin{aligned} \mathbf{V}_s &= 5\angle 0^\circ \\ j\omega L &= j(2)(1) = j2 \\ \frac{1}{j\omega C} &= \frac{1}{j(2)(0.25)} = -j2 \end{aligned}$$

$$\mathbf{V}_o = \frac{j2}{2 - j2 + j2} \mathbf{V}_s = \frac{j2}{2} 5\angle 0^\circ = (1\angle 90^\circ)(5\angle 0^\circ) = 5\angle 90^\circ$$

Thus,  $v_o(t) = 5 \cos(2t + 90^\circ) = \underline{\mathbf{-5 \sin(2t) \, V}}$

### Chapter 9, Solution 36.

Let  $Z$  be the input impedance at the source.

$$100 \text{ mH} \longrightarrow j\omega L = j200 \times 100 \times 10^{-3} = j20$$

$$10 \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j10 \times 10^{-6} \times 200} = -j500$$

$$1000 // -j500 = 200 - j400$$

$$1000 // (j20 + 200 - j400) = 242.62 - j239.84$$

$$Z = 242.62 - j239.84 = 225.5 \angle -6.104^\circ$$

$$I = \frac{60 \angle -10^\circ}{225.5 \angle -6.104^\circ} = 26.61 \angle -3.896^\circ \text{ mA}$$

$$i = \underline{266.1 \cos(200t - 3.896^\circ)}$$

### Chapter 9, Solution 37.

$$j\omega L = j(5)(1) = j5$$

$$\frac{1}{j\omega C} = \frac{1}{j(5)(0.2)} = -j$$

$$\text{Let } \mathbf{Z}_1 = -j, \quad \mathbf{Z}_2 = 2 \parallel j5 = \frac{(2)(j5)}{2 + j5} = \frac{j10}{2 + j5}$$

$$\text{Then, } \mathbf{I}_x = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}_s, \quad \text{where } \mathbf{I}_s = 2 \angle 0^\circ$$

$$\mathbf{I}_x = \frac{\frac{j10}{2 + j5}}{-j + \frac{j10}{2 + j5}} (2) = \frac{j20}{5 + j8} = 2.12 \angle 32^\circ$$

$$\text{Therefore, } i_x(t) = \underline{2.12 \sin(5t + 32^\circ) \text{ A}}$$

**Chapter 9, Solution 38.**

$$(a) \quad \frac{1}{6} \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(3)(1/6)} = -j2$$

$$\mathbf{I} = \frac{-j2}{4-j2}(10\angle 45^\circ) = 4.472\angle -18.43^\circ$$

$$\text{Hence, } i(t) = \underline{\mathbf{4.472 \cos(3t - 18.43^\circ) \text{ A}}}$$

$$\mathbf{V} = 4\mathbf{I} = (4)(4.472\angle -18.43^\circ) = 17.89\angle -18.43^\circ$$

$$\text{Hence, } v(t) = \underline{\mathbf{17.89 \cos(3t - 18.43^\circ) \text{ V}}}$$

$$(b) \quad \frac{1}{12} \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(4)(1/12)} = -j3$$

$$3 \text{ H} \longrightarrow j\omega L = j(4)(3) = j12$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{50\angle 0^\circ}{4-j3} = 10\angle 36.87^\circ$$

$$\text{Hence, } i(t) = \underline{\mathbf{10 \cos(4t + 36.87^\circ) \text{ A}}}$$

$$\mathbf{V} = \frac{j12}{8+j12}(50\angle 0^\circ) = 41.6\angle 33.69^\circ$$

$$\text{Hence, } v(t) = \underline{\mathbf{41.6 \cos(4t + 33.69^\circ) \text{ V}}}$$

**Chapter 9, Solution 39.**

$$\mathbf{Z} = 8 + j5 \parallel (-j10) = 8 + \frac{(j5)(-j10)}{j5 - j10} = 8 + j10$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{40\angle 0^\circ}{8+j10} = \frac{20}{6.403\angle 51.34^\circ} = 3.124\angle -51.34^\circ$$

$$\mathbf{I}_1 = \frac{-j10}{j5-j10}\mathbf{I} = 2\mathbf{I} = 6.248\angle -51.34^\circ$$

$$\mathbf{I}_2 = \frac{j5}{-j5}\mathbf{I} = -\mathbf{I} = 3.124\angle 128.66^\circ$$

$$\text{Therefore, } i_1(t) = \underline{\mathbf{6.248 \cos(120\pi t - 51.34^\circ) \text{ A}}}$$

$$i_2(t) = \underline{\mathbf{3.124 \cos(120\pi t + 128.66^\circ) \text{ A}}}$$

### Chapter 9, Solution 40.

(a) For  $\omega = 1$ ,

$$1 \text{ H} \longrightarrow j\omega L = j(1)(1) = j$$

$$0.05 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(1)(0.05)} = -j20$$

$$\mathbf{Z} = j + 2 \parallel (-j20) = j + \frac{-j40}{2 - j20} = 1.98 + j0.802$$

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{4\angle 0^\circ}{1.98 + j0.802} = \frac{4\angle 0^\circ}{2.136\angle 22.05^\circ} = 1.872\angle -22.05^\circ$$

$$\text{Hence, } i_o(t) = \underline{\underline{1.872 \cos(t - 22.05^\circ) \text{ A}}}$$

(b) For  $\omega = 5$ ,

$$1 \text{ H} \longrightarrow j\omega L = j(5)(1) = j5$$

$$0.05 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(5)(0.05)} = -j4$$

$$\mathbf{Z} = j5 + 2 \parallel (-j4) = j5 + \frac{-j4}{1 - j2} = 1.6 + j4.2$$

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{4\angle 0^\circ}{1.6 + j4} = \frac{4\angle 0^\circ}{4.494\angle 69.14^\circ} = 0.89\angle -69.14^\circ$$

$$\text{Hence, } i_o(t) = \underline{\underline{0.89 \cos(5t - 69.14^\circ) \text{ A}}}$$

(c) For  $\omega = 10$ ,

$$1 \text{ H} \longrightarrow j\omega L = j(10)(1) = j10$$

$$0.05 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(0.05)} = -j2$$

$$\mathbf{Z} = j10 + 2 \parallel (-j2) = j10 + \frac{-j4}{2 - j2} = 1 + j9$$

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{4\angle 0^\circ}{1 + j9} = \frac{4\angle 0^\circ}{9.055\angle 83.66^\circ} = 0.4417\angle -83.66^\circ$$

$$\text{Hence, } i_o(t) = \underline{\underline{0.4417 \cos(10t - 83.66^\circ) \text{ A}}}$$

**Chapter 9, Solution 41.**

$$\omega = 1, \\ 1 \text{ H} \longrightarrow j\omega L = j(1)(1) = j$$

$$1 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(1)(1)} = -j$$

$$\mathbf{Z} = 1 + (1 + j) \parallel (-j) = 1 + \frac{-j+1}{1} = 2 - j$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10}{2 - j}, \quad \mathbf{I}_c = (1 + j)\mathbf{I}$$

$$\mathbf{V} = (-j)(1 + j)\mathbf{I} = (1 - j)\mathbf{I} = \frac{(1 - j)(10)}{2 - j} = 6.325 \angle -18.43^\circ$$

Thus,  $v(t) = \underline{\underline{6.325 \cos(t - 18.43^\circ) \text{ V}}}$

**Chapter 9, Solution 42.**

$$\omega = 200 \\ 50 \text{ } \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(200)(50 \times 10^{-6})} = -j100$$

$$0.1 \text{ H} \longrightarrow j\omega L = j(200)(0.1) = j20$$

$$50 \parallel -j100 = \frac{(50)(-j100)}{50 - j100} = \frac{-j100}{1 - j2} = 40 - j20$$

$$\mathbf{V}_o = \frac{j20}{j20 + 30 + 40 - j20} (60 \angle 0^\circ) = \frac{j20}{70} (60 \angle 0^\circ) = 17.14 \angle 90^\circ$$

Thus,  $v_o(t) = \underline{\underline{17.14 \sin(200t + 90^\circ) \text{ V}}}$

or  $v_o(t) = \underline{\underline{17.14 \cos(200t) \text{ V}}}$

**Chapter 9, Solution 43.**

$$\omega = 2$$
$$1 \text{ H} \longrightarrow j\omega L = j(2)(1) = j2$$

$$1 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(1)} = -j0.5$$

$$\mathbf{I}_o = \frac{j2 - j0.5}{j2 - j0.5 + 1} \mathbf{I} = \frac{j1.5}{1 + j1.5} 4 \angle 0^\circ = 3.328 \angle 33.69^\circ$$

Thus,  $i_o(t) = \underline{\underline{3.328 \cos(2t + 33.69^\circ) \text{ A}}}$

**Chapter 9, Solution 44.**

$$\omega = 200$$
$$10 \text{ mH} \longrightarrow j\omega L = j(200)(10 \times 10^{-3}) = j2$$

$$5 \text{ mF} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(200)(5 \times 10^{-3})} = -j$$

$$\mathbf{Y} = \frac{1}{4} + \frac{1}{j2} + \frac{1}{3 - j} = 0.25 - j0.5 + \frac{3 + j}{10} = 0.55 - j0.4$$


$$\mathbf{Z} = \frac{1}{\mathbf{Y}} = \frac{1}{0.55 - j0.4} = 1.1892 + j0.865$$

$$\mathbf{I} = \frac{6 \angle 0^\circ}{5 + \mathbf{Z}} = \frac{6 \angle 0^\circ}{6.1892 + j0.865} = 0.96 \angle -7.956^\circ$$

Thus,  $i(t) = \underline{\underline{0.96 \cos(200t - 7.956^\circ) \text{ A}}}$
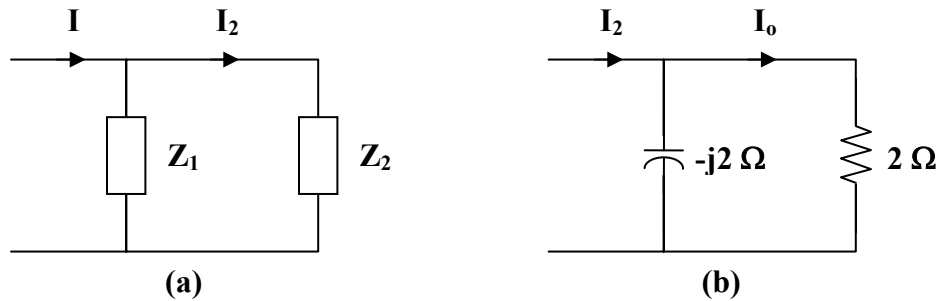
### Chapter 9, Solution 45.

We obtain  $I_o$  by applying the principle of current division twice.



$$Z_1 = -j2, \quad Z_2 = j4 + (-j2) \parallel 2 = j4 + \frac{-j4}{2 - j2} = 1 + j3$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} I = \frac{-j2}{-j2 + 1 + j3} (5 \angle 0^\circ) = \frac{-j10}{1 + j}$$

$$I_o = \frac{-j2}{2 - j2} I_2 = \left( \frac{-j}{1 - j} \right) \left( \frac{-j10}{1 + j} \right) = \frac{-10}{1 + 1} = \underline{\underline{-5\text{ A}}}$$

### Chapter 9, Solution 46.

$$i_s = 5 \cos(10t + 40^\circ) \longrightarrow I_s = 5 \angle 40^\circ$$

$$0.1\text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(0.1)} = -j$$

$$0.2\text{ H} \longrightarrow j\omega L = j(10)(0.2) = j2$$

$$\text{Let } Z_1 = 4 \parallel j2 = \frac{j8}{4 + j2} = 0.8 + j1.6, \quad Z_2 = 3 - j$$


$$I_o = \frac{Z_1}{Z_1 + Z_2} I_s = \frac{0.8 + j1.6}{3.8 + j0.6} (5 \angle 40^\circ)$$

$$I_o = \frac{(1.789 \angle 63.43^\circ)(5 \angle 40^\circ)}{3.847 \angle 8.97^\circ} = 2.325 \angle 94.46^\circ$$

$$\text{Thus, } i_o(t) = \underline{\underline{2.325 \cos(10t + 94.46^\circ)\text{ A}}}$$
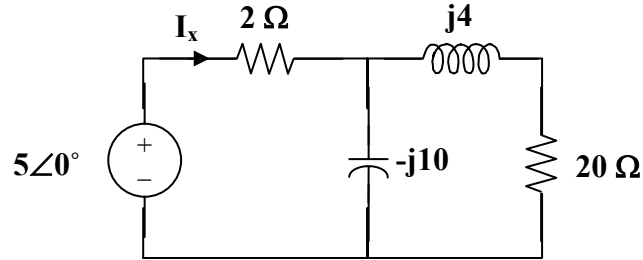
### Chapter 9, Solution 47.

First, we convert the circuit into the frequency domain.




$$I_x = \frac{5}{2 + \frac{-j10(20 + j4)}{-j10 + 20 + j4}} = \frac{5}{2 + 4.588 - j8.626} = \frac{5}{10.854\angle -52.63^\circ} = 0.4607\angle 52.63^\circ$$

$$i_s(t) = \underline{\underline{0.4607\cos(2000t + 52.63^\circ)\text{ A}}}$$
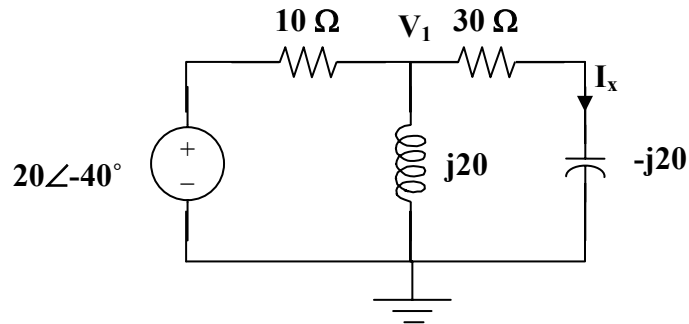
### Chapter 9, Solution 48.

Converting the circuit to the frequency domain, we get:



We can solve this using nodal analysis.

$$\frac{V_1 - 20\angle -40^\circ}{10} + \frac{V_1 - 0}{j20} + \frac{V_1 - 0}{30 - j20} = 0$$

$$V_1(0.1 - j0.05 + 0.02307 + j0.01538) = 2\angle -40^\circ$$


$$V_1 = \frac{2\angle 40^\circ}{0.12307 - j0.03462} = 15.643\angle -24.29^\circ$$

$$I_x = \frac{15.643\angle -24.29^\circ}{30 - j20} = 0.4338\angle 9.4^\circ$$

$$i_x = \underline{0.4338\sin(100t + 9.4^\circ) \text{ A}}$$
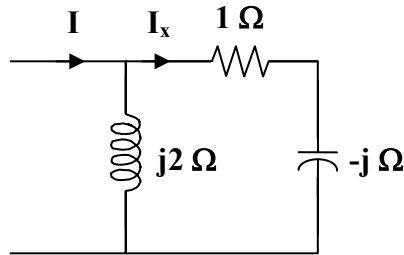
### Chapter 9, Solution 49.

$$Z_T = 2 + j2 \parallel (1 - j) = 2 + \frac{(j2)(1 - j)}{1 + j} = 4$$



$$I_x = \frac{j2}{j2 + 1 - j} I = \frac{j2}{1 + j} I, \quad \text{where } I_x = 0.5\angle 0^\circ = \frac{1}{2}$$


$$I = \frac{1 + j}{j2} I_x = \frac{1 + j}{j4}$$

$$V_s = I Z_T = \frac{1 + j}{j4} (4) = \frac{1 + j}{j} = 1 - j = 1.414\angle -45^\circ$$

$$v_s(t) = \underline{1.414 \sin(200t - 45^\circ) \text{ V}}$$
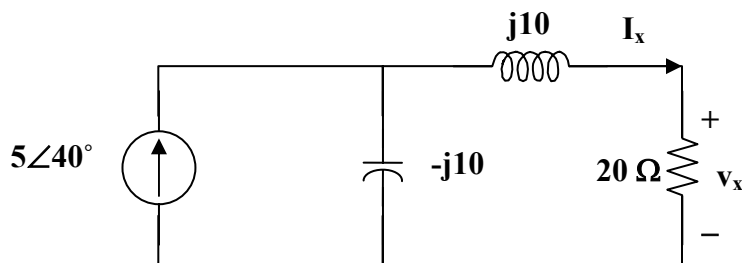
### Chapter 9, Solution 50.

Since  $\omega = 100$ , the inductor  $= j100 \times 0.1 = j10 \Omega$  and the capacitor  $= 1/(j100 \times 10^{-3}) = -j10 \Omega$ .



Using the current dividing rule:

$$I_x = \frac{-j10}{-j10 + 20 + j10} 5\angle 40^\circ = -j2.5\angle 40^\circ = 2.5\angle -50^\circ$$

$$V_x = 20I_x = 50\angle -50^\circ$$

$$v_x = \underline{50\cos(100t - 50^\circ) \text{ V}}$$

### Chapter 9, Solution 51.

$$0.1 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(0.1)} = -j5$$

$$0.5 \text{ H} \longrightarrow j\omega L = j(2)(0.5) = j$$

The current  $\mathbf{I}$  through the  $2\text{-}\Omega$  resistor is

$$\mathbf{I} = \frac{1}{1 - j5 + j + 2} \mathbf{I}_s = \frac{\mathbf{I}_s}{3 - j4},$$

where  $\mathbf{I} = 10\angle 0^\circ$

$$\mathbf{I}_s = (10)(3 - j4) = 50\angle -53.13^\circ$$


Therefore,

$$i_s(t) = \underline{50 \cos(2t - 53.13^\circ) \text{ A}}$$
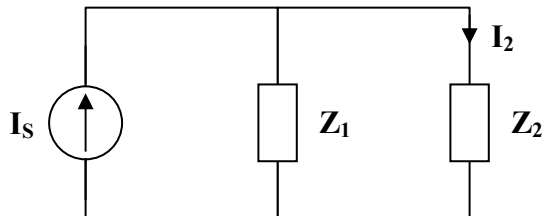
### Chapter 9, Solution 52.

$$5 \parallel j5 = \frac{j25}{5 + j5} = \frac{j5}{1 + j} = 2.5 + j2.5$$

$$\mathbf{Z}_1 = 10, \quad \mathbf{Z}_2 = -j5 + 2.5 + j2.5 = 2.5 - j2.5$$



$$\mathbf{I}_2 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}_s = \frac{10}{12.5 - j2.5} \mathbf{I}_s = \frac{4}{5 - j} \mathbf{I}_s$$


$$\mathbf{V}_o = \mathbf{I}_2 (2.5 + j2.5)$$

$$8 \angle 30^\circ = \left( \frac{4}{5 - j} \right) \mathbf{I}_s (2.5)(1 + j) = \frac{10(1 + j)}{5 - j} \mathbf{I}_s$$

$$\mathbf{I}_s = \frac{(8 \angle 30^\circ)(5 - j)}{10(1 + j)} = \underline{\underline{2.884 \angle -26.31^\circ \text{ A}}}$$
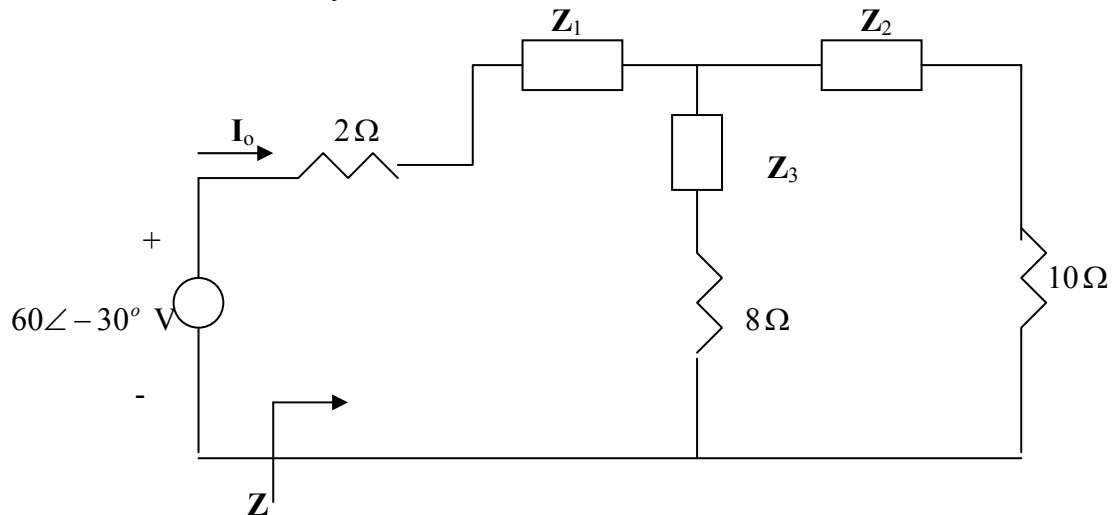
### Chapter 9, Solution 53.

Convert the delta to wye subnetwork as shown below.



$$Z_1 = \frac{-j2 \times 4}{10 - j2} = 0.1532 - j0.7692, \quad Z_2 = \frac{j6 \times 4}{10 - j2} = -0.4615 + j2.3077,$$

$$Z_3 = \frac{12}{10 - j2} = 1.1538 + j0.2308$$


$$(Z_3 + 8) \parallel (Z_2 + 10) = (9.1538 + j0.2308) \parallel (9.5385 + j2.3077) = 4.726 + j0.6062$$

$$Z = 2 + Z_1 + 4.726 + j0.6062 = 6.878 - j0.163$$

$$\mathbf{I}_o = \frac{60 \angle -30^\circ}{Z} = \frac{60 \angle -30^\circ}{6.88 \angle -1.3575^\circ} = \underline{\underline{8.721 \angle -28.64^\circ \text{ A}}}$$

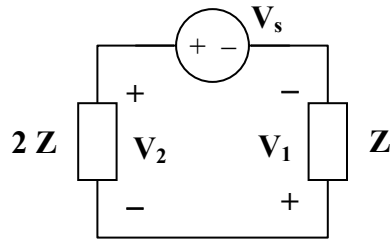**Chapter 9, Solution 54.**

Since the left portion of the circuit is twice as large as the right portion, the equivalent circuit is shown below.




$$V_1 = I_o(1 - j) = 2(1 - j)$$

$$V_2 = 2V_1 = 4(1 - j)$$

$$V_s = V_1 + V_2 = 6(1 - j)$$

$$V_s = \underline{8.485 \angle -45^\circ \text{ V}}$$

**Chapter 9, Solution 55.**

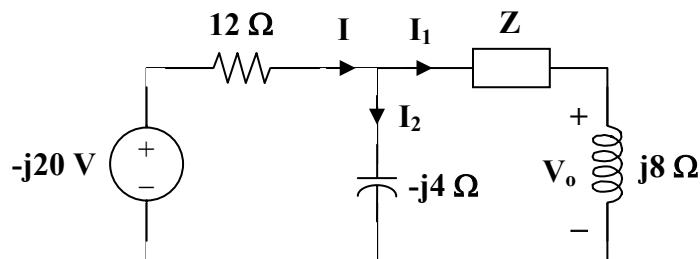

$$I_1 = \frac{V_o}{j8} = \frac{4}{j8} = -j0.5$$

$$I_2 = \frac{I_1(Z + j8)}{-j4} = \frac{(-j0.5)(Z + j8)}{-j4} = \frac{Z}{8} + j$$

$$I = I_1 + I_2 = -j0.5 + \frac{Z}{8} + j = \frac{Z}{8} + j0.5$$

$$-j20 = 12I + I_1(Z + j8)$$

$$-j20 = 12\left(\frac{Z}{8} + \frac{j}{2}\right) + \frac{-j}{2}(Z + j8)$$

$$-4 - j26 = \mathbf{Z} \left( \frac{3}{2} - j\frac{1}{2} \right)$$

$$\mathbf{Z} = \frac{-4 - j26}{\frac{3}{2} - j\frac{1}{2}} = \frac{26.31 \angle 261.25^\circ}{1.5811 \angle -18.43^\circ} = 16.64 \angle 279.68^\circ$$

$$\mathbf{Z} = \underline{\underline{2.798 - j16.403 \, \Omega}}$$

### Chapter 9, Solution 56.

$$3H \longrightarrow j\omega L = j30$$

$$3F \longrightarrow \frac{1}{j\omega C} = -j/30$$

$$1.5F \longrightarrow \frac{1}{j\omega C} = -j/15$$

$$j30 // (-j/15) = \frac{j30 \times \frac{-j}{15}}{j30 - \frac{j}{15}} = -j0.06681$$

$$\mathbf{Z} = \frac{-j}{30} // (2 - j0.06681) = \frac{-j0.033(2 - j0.06681)}{-j0.033 + 2 - j0.06681} = \underline{\underline{6 - j333 \, \text{m}\Omega}}$$

### Chapter 9, Solution 57.

$$2H \longrightarrow j\omega L = j2$$

$$1F \longrightarrow \frac{1}{j\omega C} = -j$$

$$\mathbf{Z} = 1 + j2 // (2 - j) = 1 + \frac{j2(2 - j)}{j2 + 2 - j} = 2.6 + j1.2$$

$$\mathbf{Y} = 1/\mathbf{Z} = \underline{\underline{0.3171 - j0.1463 \, \text{S}}}$$

**Chapter 9, Solution 58.**

$$(a) \quad 10 \text{ mF} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(50)(10 \times 10^{-3})} = -j2$$

$$10 \text{ mH} \longrightarrow j\omega L = j(50)(10 \times 10^{-3}) = j0.5$$

$$\mathbf{Z}_{in} = j0.5 + 1 \parallel (1 - j2)$$

$$\mathbf{Z}_{in} = j0.5 + \frac{1 - j2}{2 - j2}$$

$$\mathbf{Z}_{in} = j0.5 + 0.25(3 - j)$$

$$\mathbf{Z}_{in} = \mathbf{0.75 + j0.25 \Omega}$$

$$(b) \quad 0.4 \text{ H} \longrightarrow j\omega L = j(50)(0.4) = j20$$

$$0.2 \text{ H} \longrightarrow j\omega L = j(50)(0.2) = j10$$

$$1 \text{ mF} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(50)(1 \times 10^{-3})} = -j20$$

For the parallel elements,

$$\frac{1}{\mathbf{Z}_p} = \frac{1}{20} + \frac{1}{j10} + \frac{1}{-j20}$$

$$\mathbf{Z}_p = 10 + j10$$

Then,

$$\mathbf{Z}_{in} = 10 + j20 + \mathbf{Z}_p = \mathbf{20 + j30 \Omega}$$

**Chapter 9, Solution 59.**

$$\mathbf{Z}_{eq} = 6 + (1 - j2) \parallel (2 + j4)$$

$$\mathbf{Z}_{eq} = 6 + \frac{(1 - j2)(2 + j4)}{(1 - j2) + (2 + j4)}$$

$$\mathbf{Z}_{eq} = 6 + 2.308 - j1.5385$$

$$\mathbf{Z}_{eq} = \mathbf{8.308 - j1.5385 \Omega}$$

**Chapter 9, Solution 60.**

$$\mathbf{Z} = (25 + j15) + (20 - j50) \parallel (30 + j10) = 25 + j15 + 26.097 - j5.122 = \mathbf{51.1 + j9.878 \Omega}$$

### Chapter 9, Solution 61.

All of the impedances are in parallel.

$$\frac{1}{\mathbf{Z}_{\text{eq}}} = \frac{1}{1-j} + \frac{1}{1+j2} + \frac{1}{j5} + \frac{1}{1+j3}$$


$$\frac{1}{\mathbf{Z}_{\text{eq}}} = (0.5 + j0.5) + (0.2 - j0.4) + (-j0.2) + (0.1 - j0.3) = 0.8 - j0.4$$

$$\mathbf{Z}_{\text{eq}} = \frac{1}{0.8 - j0.4} = \underline{\underline{1 + j0.5 \, \Omega}}$$
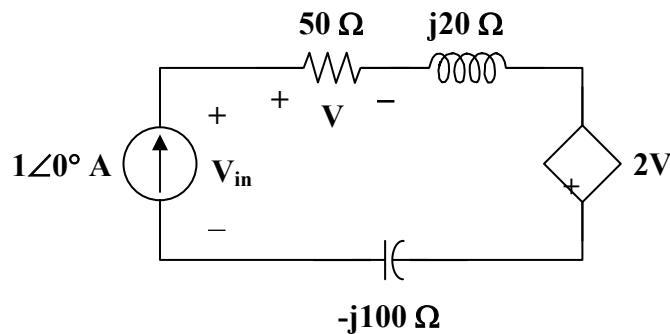
### Chapter 9, Solution 62.

$$2 \text{ mH} \longrightarrow j\omega L = j(10 \times 10^3)(2 \times 10^{-3}) = j20$$

$$1 \, \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10 \times 10^3)(1 \times 10^{-6})} = -j100$$



$$\mathbf{V} = (1\angle 0^\circ)(50) = 50$$

$$\mathbf{V}_{\text{in}} = (1\angle 0^\circ)(50 + j20 - j100) + (2)(50)$$

$$\mathbf{V}_{\text{in}} = 50 - j80 + 100 = 150 - j80$$


$$\mathbf{Z}_{\text{in}} = \frac{\mathbf{V}_{\text{in}}}{1\angle 0^\circ} = \underline{\underline{150 - j80 \, \Omega}}$$

### Chapter 9, Solution 63.

First, replace the wye composed of the 20-ohm, 10-ohm, and j15-ohm impedances with the corresponding delta.

$$z_1 = \frac{200 + j150 + j300}{10} = 20 + j45$$
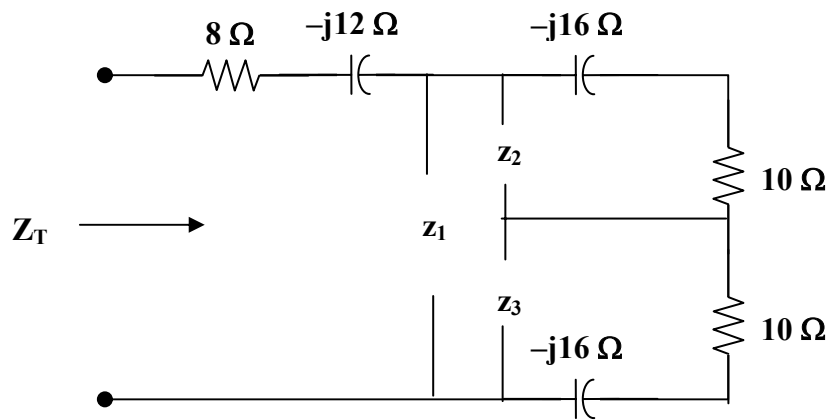
$$z_2 = \frac{200 + j450}{j15} = 30 - j13.333, \quad z_3 = \frac{200 + j450}{20} = 10 + j22.5$$



Now all we need to do is to combine impedances.

$$z_2 \parallel (10 - j16) = \frac{(30 - j13.333)(10 - j16)}{40 - j29.333} = 8.721 - j8.938$$

$$z_3 \parallel (10 - j16) = 21.70 - j3.821$$

$$Z_T = 8 - j12 + z_1 \parallel (8.721 - j8.938 + 21.7 - j3.821) = \underline{34.69 - j6.93\ \Omega}$$

### Chapter 9, Solution 64.

$$Z_T = 4 + \frac{-j10(6 + j8)}{6 - j2} = \underline{19 - j5\ \Omega}$$

$$I = \frac{30 \angle 90^\circ}{Z_T} = -0.3866 + j1.4767 = \underline{1.527 \angle 104.7^\circ\ \text{A}}$$

**Chapter 9, Solution 65.**

$$\mathbf{Z_T} = 2 + (4 - j6) \parallel (3 + j4)$$

$$\mathbf{Z_T} = 2 + \frac{(4 - j6)(3 + j4)}{7 - j2}$$

$$\mathbf{Z_T} = \underline{\mathbf{6.83 + j1.094\ \Omega}} = 6.917\angle 9.1^\circ\ \Omega$$


$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z_T}} = \frac{120\angle 10^\circ}{6.917\angle 9.1^\circ} = \underline{\mathbf{17.35\angle 0.9^\circ\ A}}$$

**Chapter 9, Solution 66.**

$$\mathbf{Z_T} = (20 - j5) \parallel (40 + j10) = \frac{(20 - j5)(40 + j10)}{60 + j5} = \frac{170}{145}(12 - j)$$

$$\mathbf{Z_T} = \underline{\mathbf{14.069 - j1.172\ \Omega}} = 14.118\angle -4.76^\circ$$
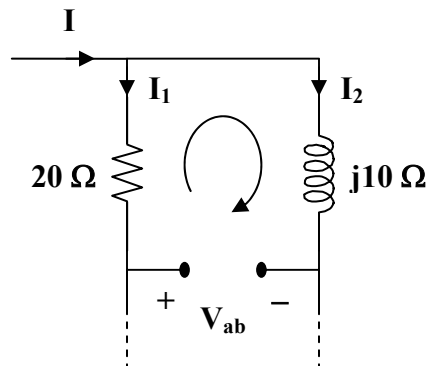
$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z_T}} = \frac{60\angle 90^\circ}{14.118\angle -4.76^\circ} = 4.25\angle 94.76^\circ$$



$$\mathbf{I_1} = \frac{40 + j10}{60 + j5} \mathbf{I} = \frac{8 + j2}{12 + j} \mathbf{I}$$

$$\mathbf{I_2} = \frac{20 - j5}{60 + j5} \mathbf{I} = \frac{4 - j}{12 + j} \mathbf{I}$$

$$\mathbf{V_{ab}} = -20\mathbf{I_1} + j10\mathbf{I_2}$$

$$V_{ab} = \frac{-(160 + j40)}{12 + j} \mathbf{I} + \frac{10 + j40}{12 + j} \mathbf{I}$$

$$V_{ab} = \frac{-150}{12 + j} \mathbf{I} = \frac{(-12 + j)(150)}{145} \mathbf{I}$$

$$V_{ab} = (12.457 \angle 175.24^\circ)(4.25 \angle 97.76^\circ)$$

$$V_{ab} = \underline{\underline{52.94 \angle 273^\circ \text{ V}}}$$

### Chapter 9, Solution 67.

$$\begin{aligned} \text{(a)} \quad 20 \text{ mH} &\longrightarrow j\omega L = j(10^3)(20 \times 10^{-3}) = j20 \\ 12.5 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10^3)(12.5 \times 10^{-6})} = -j80 \end{aligned}$$

$$Z_{in} = 60 + j20 \parallel (60 - j80)$$

$$Z_{in} = 60 + \frac{(j20)(60 - j80)}{60 - j60}$$

$$Z_{in} = 63.33 + j23.33 = 67.494 \angle 20.22^\circ$$

$$Y_{in} = \frac{1}{Z_{in}} = \underline{\underline{0.0148 \angle -20.22^\circ \text{ S}}}$$

$$\begin{aligned} \text{(b)} \quad 10 \text{ mH} &\longrightarrow j\omega L = j(10^3)(10 \times 10^{-3}) = j10 \\ 20 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10^3)(20 \times 10^{-6})} = -j50 \\ 30 \parallel 60 &= 20 \end{aligned}$$

$$Z_{in} = -j50 + 20 \parallel (40 + j10)$$

$$Z_{in} = -j50 + \frac{(20)(40 + j10)}{60 + j10}$$

$$Z_{in} = 13.5 - j48.92 = 50.75 \angle -74.56^\circ$$

$$Y_{in} = \frac{1}{Z_{in}} = \underline{\underline{0.0197 \angle 74.56^\circ \text{ S}}} = 5.24 + j18.99 \text{ mS}$$

**Chapter 9, Solution 68.**

$$Y_{eq} = \frac{1}{5-j2} + \frac{1}{3+j} + \frac{1}{-j4}$$

$$Y_{eq} = (0.1724 + j0.069) + (0.3 - j0.1) + (j0.25)$$

$$Y_{eq} = \underline{\underline{0.4724 + j0.219 \text{ S}}}$$

**Chapter 9, Solution 69.**

$$\frac{1}{Y_o} = \frac{1}{4} + \frac{1}{-j2} = \frac{1}{4}(1 + j2)$$

$$Y_o = \frac{4}{1+j2} = \frac{(4)(1-j2)}{5} = 0.8 - j1.6$$

$$Y_o + j = 0.8 - j0.6$$

$$\frac{1}{Y_o'} = \frac{1}{1} + \frac{1}{-j3} + \frac{1}{0.8 - j0.6} = (1) + (j0.333) + (0.8 + j0.6)$$

$$\frac{1}{Y_o'} = 1.8 + j0.933 = 2.028 \angle 27.41^\circ$$

$$Y_o' = 0.4932 \angle -27.41^\circ = 0.4378 - j0.2271$$

$$Y_o' + j5 = 0.4378 + j4.773$$


$$\frac{1}{Y_{eq}} = \frac{1}{2} + \frac{1}{0.4378 + j4.773} = 0.5 + \frac{0.4378 - j4.773}{22.97}$$

$$\frac{1}{Y_{eq}} = 0.5191 - j0.2078$$

$$Y_{eq} = \frac{0.5191 - j0.2078}{0.3126} = \underline{\underline{1.661 + j0.6647 \text{ S}}}$$
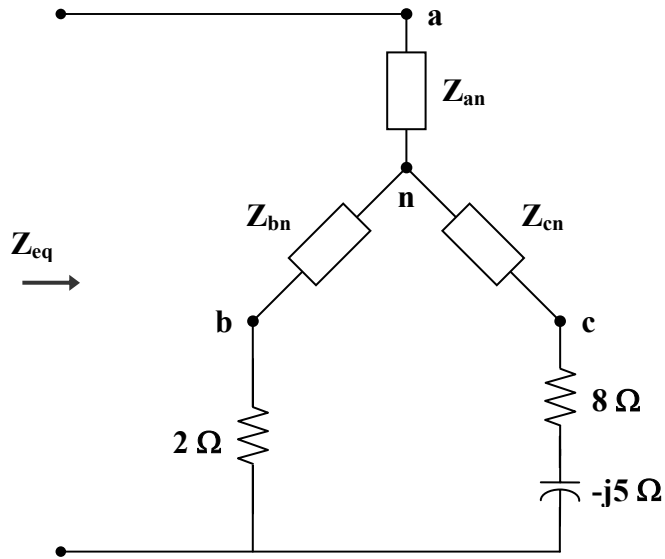
# Chapter 9, Solution 70.

Make a delta-to-wye transformation as shown in the figure below.



$$Z_{an} = \frac{(-j10)(10 + j15)}{5 - j10 + 10 + j15} = \frac{(10)(15 - j10)}{15 + j5} = 7 - j9$$

$$Z_{bn} = \frac{(5)(10 + j15)}{15 + j5} = 4.5 + j3.5$$

$$Z_{cn} = \frac{(5)(-j10)}{15 + j5} = -1 - j3$$

$$Z_{eq} = Z_{an} + (Z_{bn} + 2) \parallel (Z_{cn} + 8 - j5)$$

$$Z_{eq} = 7 - j9 + (6.5 + j3.5) \parallel (7 - j8)$$


$$Z_{eq} = 7 - j9 + \frac{(6.5 + j3.5)(7 - j8)}{13.5 - j4.5}$$

$$Z_{eq} = 7 - j9 + 5.511 - j0.2$$

$$Z_{eq} = 12.51 - j9.2 = \underline{\underline{15.53 \angle -36.33^\circ \Omega}}$$

# Chapter 9, Solution 71.

We apply a wye-to-delta transformation.

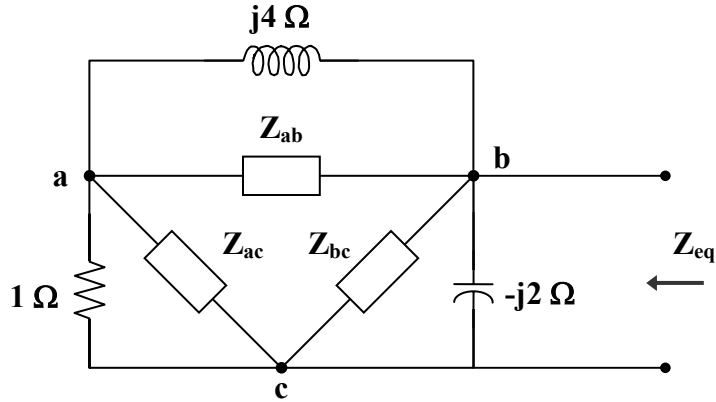

$$Z_{ab} = \frac{2 - j2 + j4}{j2} = \frac{2 + j2}{j2} = 1 - j$$

$$Z_{ac} = \frac{2 + j2}{2} = 1 + j$$

$$Z_{bc} = \frac{2 + j2}{-j} = -2 + j2$$

$$j4 \parallel Z_{ab} = j4 \parallel (1 - j) = \frac{(j4)(1 - j)}{1 + j3} = 1.6 - j0.8$$

$$1 \parallel Z_{ac} = 1 \parallel (1 + j) = \frac{(1)(1 + j)}{2 + j} = 0.6 + j0.2$$

$$j4 \parallel Z_{ab} + 1 \parallel Z_{ac} = 2.2 - j0.6$$

$$\frac{1}{Z_{eq}} = \frac{1}{-j2} + \frac{1}{-2 + j2} + \frac{1}{2.2 - j0.6}$$


$$= j0.5 - 0.25 - j0.25 + 0.4231 + j0.1154$$

$$= 0.173 + j0.3654 = 0.4043 \angle 64.66^\circ$$

$$Z_{eq} = 2.473 \angle -64.66^\circ \Omega = \underline{\underline{1.058 - j2.235 \Omega}}$$

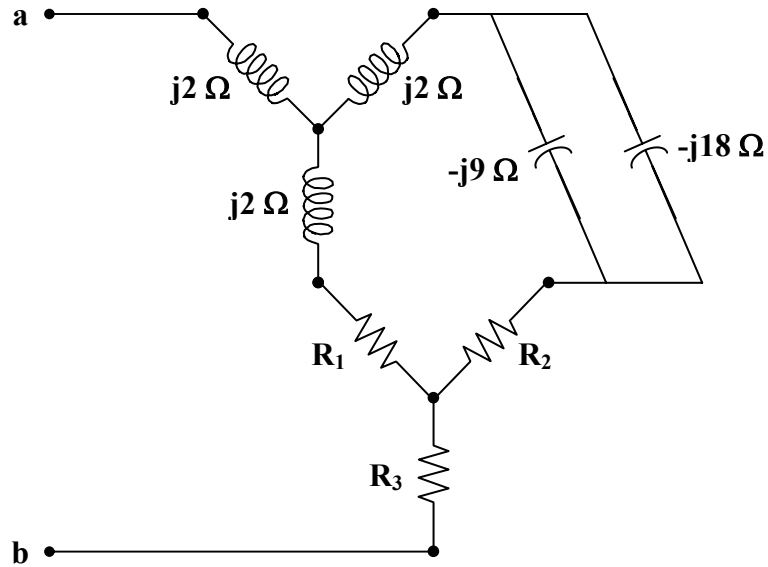**Chapter 9, Solution 72.**

Transform the delta connections to wye connections as shown below.



$$-j9 \parallel -j18 = -j6,$$

$$R_1 = \frac{(20)(20)}{20 + 20 + 10} = 8 \Omega, \quad R_2 = \frac{(20)(10)}{50} = 4 \Omega, \quad R_3 = \frac{(20)(10)}{50} = 4 \Omega$$

$$Z_{ab} = j2 + (j2 + 8) \parallel (j2 - j6 + 4) + 4$$

$$Z_{ab} = 4 + j2 + (8 + j2) \parallel (4 - j4)$$


$$Z_{ab} = 4 + j2 + \frac{(8 + j2)(4 - j4)}{12 - j2}$$

$$Z_{ab} = 4 + j2 + 3.567 - j1.4054$$

$$Z_{ab} = \underline{\underline{7.567 + j0.5946 \Omega}}$$
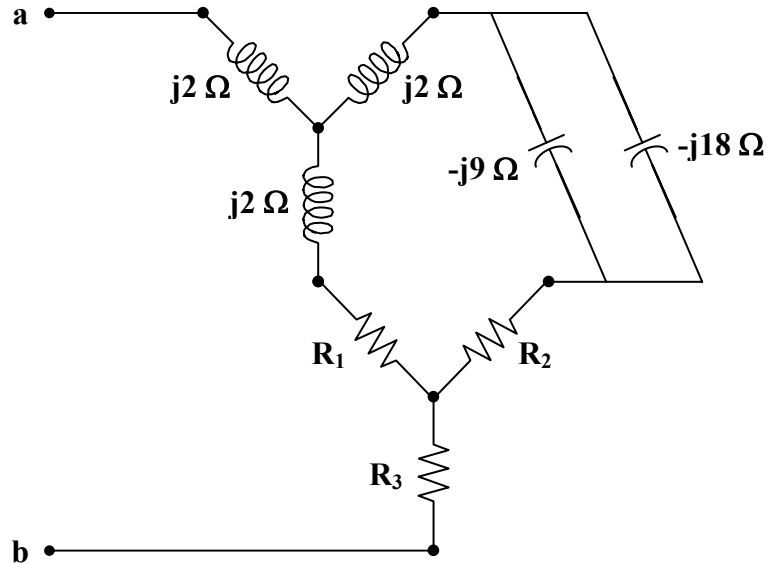
### Chapter 9, Solution 73.

Transform the delta connection to a wye connection as in Fig. (a) and then transform the wye connection to a delta connection as in Fig. (b).



$$\mathbf{Z}_1 = \frac{(j8)(-j6)}{j8 + j8 - j6} = \frac{48}{j10} = -j4.8$$

$$\mathbf{Z}_2 = \mathbf{Z}_1 = -j4.8$$

$$\mathbf{Z}_3 = \frac{(j8)(j8)}{j10} = \frac{-64}{j10} = j6.4$$

$$\begin{aligned} (2 + \mathbf{Z}_1)(4 + \mathbf{Z}_2) + (4 + \mathbf{Z}_2)(\mathbf{Z}_3) + (2 + \mathbf{Z}_1)(\mathbf{Z}_3) = \\ (2 - j4.8)(4 - j4.8) + (4 - j4.8)(j6.4) + (2 - j4.8)(j6.4) = 46.4 + j9.6 \end{aligned}$$

$$\mathbf{Z}_a = \frac{46.4 + j9.6}{j6.4} = 1.5 - j7.25$$

$$\mathbf{Z}_b = \frac{46.4 + j9.6}{4 - j4.8} = 3.574 + j6.688$$

$$\mathbf{Z}_c = \frac{46.4 + j9.6}{2 - j4.8} = 1.727 + j8.945$$

$$j6 \parallel \mathbf{Z}_b = \frac{(6 \angle 90^\circ)(7.583 \angle 61.88^\circ)}{3.574 + j12.688} = 0.7407 + j3.3716$$

$$-j4 \parallel \mathbf{Z}_a = \frac{(-j4)(1.5 - j7.25)}{1.5 - j11.25} = 0.186 - j2.602$$

$$j12 \parallel \mathbf{Z}_c = \frac{(12\angle 90^\circ)(9.11\angle 79.07^\circ)}{1.727 + j20.945} = 0.5634 + j5.1693$$


$$\mathbf{Z}_{eq} = (j6 \parallel \mathbf{Z}_b) \parallel (-j4 \parallel \mathbf{Z}_a + j12 \parallel \mathbf{Z}_c)$$

$$\mathbf{Z}_{eq} = (0.7407 + j3.3716) \parallel (0.7494 + j2.5673)$$

$$\mathbf{Z}_{eq} = 1.508\angle 75.42^\circ \Omega = \underline{\underline{0.3796 + j1.46 \Omega}}$$

#### Chapter 9, Solution 74.

One such RL circuit is shown below.

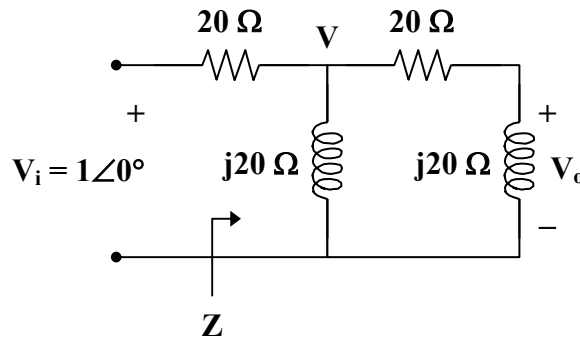

We now want to show that this circuit will produce a  $90^\circ$  phase shift.

$$\mathbf{Z} = j20 \parallel (20 + j20) = \frac{(j20)(20 + j20)}{20 + j40} = \frac{-20 + j20}{1 + j2} = 4(1 + j3)$$


$$\mathbf{V} = \frac{\mathbf{Z}}{\mathbf{Z} + 20} \mathbf{V}_i = \frac{4 + j12}{24 + j12} (1\angle 0^\circ) = \frac{1 + j3}{6 + j3} = \frac{1}{3}(1 + j)$$

$$\mathbf{V}_o = \frac{j20}{20 + j20} \mathbf{V} = \left( \frac{j}{1 + j} \right) \left( \frac{1}{3}(1 + j) \right) = \frac{j}{3} = 0.3333\angle 90^\circ$$

This shows that the output leads the input by  $90^\circ$ .
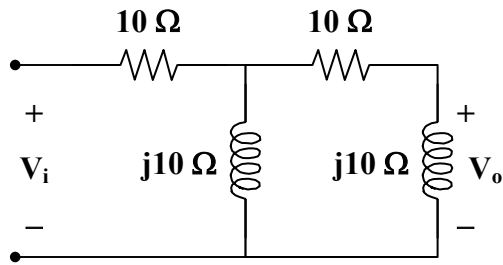
#### Chapter 9, Solution 75.

Since  $\cos(\omega t) = \sin(\omega t + 90^\circ)$ , we need a phase shift circuit that will cause the output to lead the input by  $90^\circ$ . **This is achieved by the RL circuit shown below, as explained in the previous problem.**



This can also be obtained by an RC circuit.

### Chapter 9, Solution 76.

$$\text{Let } Z = R - jX, \text{ where } X = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

$$|Z| = \sqrt{R^2 + X^2} \longrightarrow X = \sqrt{|Z|^2 - R^2} = \sqrt{116^2 - 66^2} = 95.394$$

$$C = \frac{1}{2\pi fX} = \frac{1}{2\pi \times 60 \times 95.394} = \underline{27.81 \mu\text{F}}$$

### Chapter 9, Solution 77.

$$(a) \quad V_o = \frac{-jX_c}{R - jX_c} V_i$$

$$\text{where } X_c = \frac{1}{\omega C} = \frac{1}{(2\pi)(2 \times 10^6)(20 \times 10^{-9})} = 3.979$$

$$\frac{V_o}{V_i} = \frac{-j3.979}{5 - j3.979} = \frac{3.979}{\sqrt{5^2 + 3.979^2}} \angle (-90^\circ + \tan^{-1}(3.979/5))$$


$$\frac{V_o}{V_i} = \frac{3.979}{\sqrt{25 + 15.83}} \angle (-90^\circ - 38.51^\circ)$$

$$\frac{V_o}{V_i} = 0.6227 \angle -51.49^\circ$$

Therefore, the phase shift is **51.49° lagging**

$$\begin{aligned}
 \text{(b)} \quad \theta &= -45^\circ = -90^\circ + \tan^{-1}(X_c/R) \\
 45^\circ &= \tan^{-1}(X_c/R) \longrightarrow R = X_c = \frac{1}{\omega C} \\
 \omega &= 2\pi f = \frac{1}{RC} \\
 f &= \frac{1}{2\pi RC} = \frac{1}{(2\pi)(5)(20 \times 10^{-9})} = \underline{\underline{1.5915 \text{ MHz}}}
 \end{aligned}$$

**Chapter 9, Solution 78.**

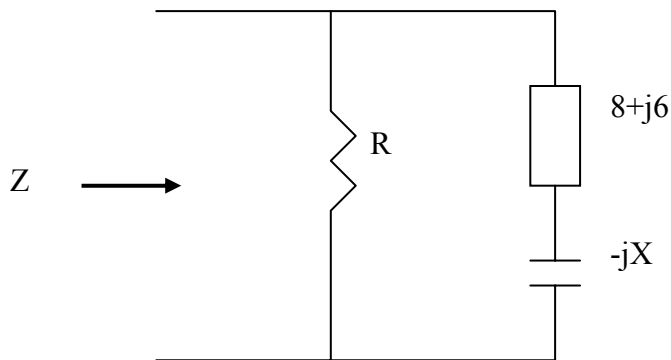

$$Z = R // [8 + j(6 - X)] = \frac{R[8 + j(6 - X)]}{R + 8 + j(6 - X)} = 5$$


$$\text{i.e. } 8R + j6R - jXR = 5R + 40 + j30 - j5X$$

Equating real and imaginary parts:

$$\begin{aligned}
 8R &= 5R + 40 \quad \text{which leads to} \quad \underline{\underline{R=13.33\Omega}} \\
 6R - XR &= 30 - 5 \quad \text{which leads to} \quad \underline{\underline{X=4.125\Omega}}
 \end{aligned}$$

**Chapter 9, Solution 79.**

(a) Consider the circuit as shown.

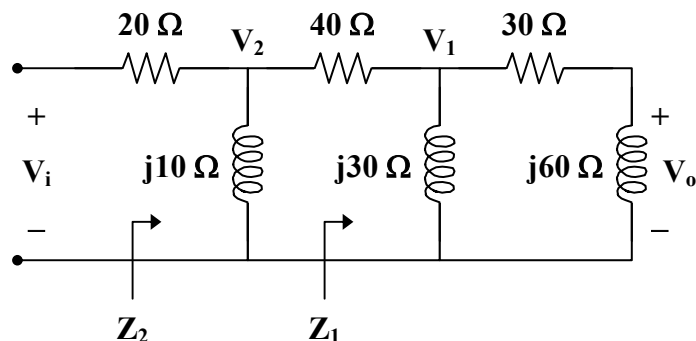

$$\mathbf{Z}_1 = j30 \parallel (30 + j60) = \frac{(j30)(30 + j60)}{30 + j90} = 3 + j21$$

$$\mathbf{Z}_2 = j10 \parallel (40 + \mathbf{Z}_1) = \frac{(j10)(43 + j21)}{43 + j31} = 1.535 + j8.896 = 9.028 \angle 80.21^\circ$$

Let  $\mathbf{V}_i = 1 \angle 0^\circ$ .

$$\mathbf{V}_2 = \frac{\mathbf{Z}_2}{\mathbf{Z}_2 + 20} \mathbf{V}_i = \frac{(9.028 \angle 80.21^\circ)(1 \angle 0^\circ)}{21.535 + j8.896}$$

$$\mathbf{V}_2 = 0.3875 \angle 57.77^\circ$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + 40} \mathbf{V}_2 = \frac{3 + j21}{43 + j21} \mathbf{V}_2 = \frac{(21.213 \angle 81.87^\circ)(0.3875 \angle 57.77^\circ)}{47.85 \angle 26.03^\circ}$$

$$\mathbf{V}_1 = 0.1718 \angle 113.61^\circ$$

$$\mathbf{V}_o = \frac{j60}{30 + j60} \mathbf{V}_1 = \frac{j2}{1 + j2} \mathbf{V}_1 = \frac{2}{5} (2 + j) \mathbf{V}_1$$

$$\mathbf{V}_o = (0.8944 \angle 26.56^\circ)(0.1718 \angle 113.6^\circ)$$

$$\mathbf{V}_o = 0.1536 \angle 140.2^\circ$$

Therefore, the phase shift is **140.2°**

(b) The phase shift is **leading**.

(c) If  $\mathbf{V}_i = 120 \text{ V}$ , then

$$\mathbf{V}_o = (120)(0.1536 \angle 140.2^\circ) = 18.43 \angle 140.2^\circ \text{ V}$$

and the magnitude is **18.43 V**.

## Chapter 9, Solution 80.

$$200 \text{ mH} \longrightarrow j\omega L = j(2\pi)(60)(200 \times 10^{-3}) = j75.4 \Omega$$

$$\mathbf{V}_o = \frac{j75.4}{R + 50 + j75.4} \mathbf{V}_i = \frac{j75.4}{R + 50 + j75.4} (120 \angle 0^\circ)$$

(a) When  $R = 100 \Omega$ ,

$$\mathbf{V}_o = \frac{j75.4}{150 + j75.4} (120 \angle 0^\circ) = \frac{(75.4 \angle 90^\circ)(120 \angle 0^\circ)}{167.88 \angle 26.69^\circ}$$

$$\mathbf{V}_o = \mathbf{53.89 \angle 63.31^\circ V}$$

(b) When  $R = 0 \Omega$ ,

$$V_o = \frac{j75.4}{50 + j75.4} (120 \angle 0^\circ) = \frac{(75.4 \angle 90^\circ)(120 \angle 0^\circ)}{90.47 \angle 56.45^\circ}$$

$$V_o = \underline{\underline{100 \angle 33.55^\circ \text{ V}}}$$

(c) To produce a phase shift of  $45^\circ$ , the phase of  $V_o = 90^\circ + 0^\circ - \alpha = 45^\circ$ .

Hence,  $\alpha = \text{phase of } (R + 50 + j75.4) = 45^\circ$ .

For  $\alpha$  to be  $45^\circ$ ,  $R + 50 = 75.4$

Therefore,  $R = \underline{\underline{25.4 \Omega}}$

### Chapter 9, Solution 81.

$$\text{Let } Z_1 = R_1, \quad Z_2 = R_2 + \frac{1}{j\omega C_2}, \quad Z_3 = R_3, \text{ and } Z_x = R_x + \frac{1}{j\omega C_x}.$$

$$Z_x = \frac{Z_3}{Z_1} Z_2$$

$$R_x + \frac{1}{j\omega C_x} = \frac{R_3}{R_1} \left( R_2 + \frac{1}{j\omega C_2} \right)$$

$$R_x = \frac{R_3}{R_1} R_2 = \frac{1200}{400} (600) = \underline{\underline{1.8 \text{ k}\Omega}}$$

$$\frac{1}{C_x} = \left( \frac{R_3}{R_1} \right) \left( \frac{1}{C_2} \right) \longrightarrow C_x = \frac{R_1}{R_3} C_2 = \left( \frac{400}{1200} \right) (0.3 \times 10^{-6}) = \underline{\underline{0.1 \mu\text{F}}}$$

### Chapter 9, Solution 82.

$$C_x = \frac{R_1}{R_2} C_s = \left( \frac{100}{2000} \right) (40 \times 10^{-6}) = \underline{\underline{2 \mu\text{F}}}$$

### Chapter 9, Solution 83.

$$L_x = \frac{R_2}{R_1} L_s = \left( \frac{500}{1200} \right) (250 \times 10^{-3}) = \underline{\underline{104.17 \text{ mH}}}$$

**Chapter 9, Solution 84.**

$$\text{Let } \mathbf{Z}_1 = R_1 \parallel \frac{1}{j\omega C_s}, \quad \mathbf{Z}_2 = R_2, \quad \mathbf{Z}_3 = R_3, \text{ and } \mathbf{Z}_x = R_x + j\omega L_x.$$

$$\mathbf{Z}_1 = \frac{\frac{R_1}{j\omega C_s}}{R_1 + \frac{1}{j\omega C_s}} = \frac{R_1}{j\omega R_1 C_s + 1}$$

$$\text{Since } \mathbf{Z}_x = \frac{\mathbf{Z}_3}{\mathbf{Z}_1} \mathbf{Z}_2,$$

$$R_x + j\omega L_x = R_2 R_3 \frac{j\omega R_1 C_s + 1}{R_1} = \frac{R_2 R_3}{R_1} (1 + j\omega R_1 C_s)$$

Equating the real and imaginary components,

$$\underline{\mathbf{R}_x = \frac{\mathbf{R}_2 \mathbf{R}_3}{\mathbf{R}_1}}$$

$$\omega L_x = \frac{R_2 R_3}{R_1} (\omega R_1 C_s) \text{ implies that}$$

$$\underline{\mathbf{L}_x = \mathbf{R}_2 \mathbf{R}_3 \mathbf{C}_s}$$

Given that  $R_1 = 40 \text{ k}\Omega$ ,  $R_2 = 1.6 \text{ k}\Omega$ ,  $R_3 = 4 \text{ k}\Omega$ , and  $C_s = 0.45 \text{ }\mu\text{F}$

$$R_x = \frac{R_2 R_3}{R_1} = \frac{(1.6)(4)}{40} \text{ k}\Omega = 0.16 \text{ k}\Omega = \underline{\mathbf{160 \Omega}}$$

$$L_x = R_2 R_3 C_s = (1.6)(4)(0.45) = \underline{\mathbf{2.88 \text{ H}}}$$

**Chapter 9, Solution 85.**

$$\text{Let } \mathbf{Z}_1 = R_1, \quad \mathbf{Z}_2 = R_2 + \frac{1}{j\omega C_2}, \quad \mathbf{Z}_3 = R_3, \text{ and } \mathbf{Z}_4 = R_4 \parallel \frac{1}{j\omega C_4}.$$

$$\mathbf{Z}_4 = \frac{R_4}{j\omega R_4 C_4 + 1} = \frac{-jR_4}{\omega R_4 C_4 - j}$$

$$\text{Since } \mathbf{Z}_4 = \frac{\mathbf{Z}_3}{\mathbf{Z}_1} \mathbf{Z}_2 \longrightarrow \mathbf{Z}_1 \mathbf{Z}_4 = \mathbf{Z}_2 \mathbf{Z}_3,$$

$$\frac{-jR_4R_1}{\omega R_4C_4 - j} = R_3 \left( R_2 - \frac{j}{\omega C_2} \right)$$

$$\frac{-jR_4R_1(\omega R_4C_4 + j)}{\omega^2 R_4^2 C_4^2 + 1} = R_3 R_2 - \frac{jR_3}{\omega C_2}$$

Equating the real and imaginary components,

$$\frac{R_1 R_4}{\omega^2 R_4^2 C_4^2 + 1} = R_2 R_3 \quad (1)$$

$$\frac{\omega R_1 R_4^2 C_4}{\omega^2 R_4^2 C_4^2 + 1} = \frac{R_3}{\omega C_2} \quad (2)$$

Dividing (1) by (2),

$$\frac{1}{\omega R_4 C_4} = \omega R_2 C_2$$

$$\omega^2 = \frac{1}{R_2 C_2 R_4 C_4}$$

$$\omega = 2\pi f = \frac{1}{\sqrt{R_2 C_2 R_4 C_4}}$$

$$\underline{\underline{f = \frac{1}{2\pi \sqrt{R_2 R_4 C_2 C_4}}}}$$

### Chapter 9, Solution 86.

$$\mathbf{Y} = \frac{1}{240} + \frac{1}{j95} + \frac{1}{-j84}$$

$$\mathbf{Y} = 4.1667 \times 10^{-3} - j0.01053 + j0.0119$$

$$\mathbf{Z} = \frac{1}{\mathbf{Y}} = \frac{1000}{4.1667 + j1.37} = \frac{1000}{4.3861 \angle 18.2^\circ}$$

$$\mathbf{Z} = \underline{\underline{228 \angle -18.2^\circ \Omega}}$$

**Chapter 9, Solution 87.**

$$\mathbf{Z}_1 = 50 + \frac{1}{j\omega C} = 50 + \frac{-j}{(2\pi)(2 \times 10^3)(2 \times 10^{-6})}$$

$$\mathbf{Z}_1 = 50 - j39.79$$

$$\mathbf{Z}_2 = 80 + j\omega L = 80 + j(2\pi)(2 \times 10^3)(10 \times 10^{-3})$$

$$\mathbf{Z}_2 = 80 + j125.66$$

$$\mathbf{Z}_3 = 100$$

$$\frac{1}{\mathbf{Z}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3}$$

$$\frac{1}{\mathbf{Z}} = \frac{1}{100} + \frac{1}{50 - j39.79} + \frac{1}{80 + j125.66}$$

$$\frac{1}{\mathbf{Z}} = 10^{-3} (10 + 12.24 + j9.745 + 3.605 - j5.663)$$

$$= (25.85 + j4.082) \times 10^{-3}$$

$$= 26.17 \times 10^{-3} \angle 8.97^\circ$$

$$\mathbf{Z} = \underline{\underline{38.21 \angle -8.97^\circ \Omega}}$$

**Chapter 9, Solution 88.**

$$(a) \quad \mathbf{Z} = -j20 + j30 + 120 - j20$$

$$\mathbf{Z} = \underline{\underline{120 - j10 \Omega}}$$

- (b) If the frequency were halved,  $\frac{1}{\omega C} = \frac{1}{2\pi f C}$  would cause the capacitive impedance to double, while  $\omega L = 2\pi f L$  would cause the inductive impedance to halve. Thus,

$$\mathbf{Z} = -j40 + j15 + 120 - j40$$

$$\mathbf{Z} = \underline{\underline{120 - j65 \Omega}}$$

**Chapter 9, Solution 89.**

$$\begin{aligned} \mathbf{Z}_{\text{in}} &= j\omega L \parallel \left( R + \frac{1}{j\omega C} \right) \\ \mathbf{Z}_{\text{in}} &= \frac{j\omega L \left( R + \frac{1}{j\omega C} \right)}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + j\omega L R}{R + j \left( \omega L - \frac{1}{\omega C} \right)} \\ \mathbf{Z}_{\text{in}} &= \frac{\left( \frac{L}{C} + j\omega L R \right) \left( R - j \left( \omega L - \frac{1}{\omega C} \right) \right)}{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2} \end{aligned}$$

To have a resistive impedance,  $\text{Im}(\mathbf{Z}_{\text{in}}) = 0$ . Hence,

$$\omega L R^2 - \left( \frac{L}{C} \right) \left( \omega L - \frac{1}{\omega C} \right) = 0$$

$$\omega R^2 C = \omega L - \frac{1}{\omega C}$$

$$\omega^2 R^2 C^2 = \omega^2 LC - 1$$

$$L = \frac{\omega^2 R^2 C^2 + 1}{\omega^2 C} \quad (1)$$

Ignoring the +1 in the numerator in (1),

$$L = R^2 C = (200)^2 (50 \times 10^{-9}) = \underline{\underline{2 \text{ mH}}}$$

**Chapter 9, Solution 90.**

$$\text{Let } \mathbf{V}_s = 145 \angle 0^\circ, \quad X = j\omega L = j(2\pi)(60)L = j377L$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{80 + R + jX} = \frac{145 \angle 0^\circ}{80 + R + jX}$$

$$V_1 = 80\mathbf{I} = \frac{(80)(145)}{80 + R + jX}$$

$$50 = \left| \frac{(80)(145)}{80 + R + jX} \right| \quad (1)$$

$$V_o = (R + jX)\mathbf{I} = \frac{(R + jX)(145\angle 0^\circ)}{80 + R + jX}$$

$$110 = \left| \frac{(R + jX)(145)}{80 + R + jX} \right| \quad (2)$$

From (1) and (2),

$$\frac{50}{110} = \frac{80}{|R + jX|}$$

$$|R + jX| = (80)\left(\frac{11}{5}\right)$$

$$R^2 + X^2 = 30976 \quad (3)$$

From (1),

$$|80 + R + jX| = \frac{(80)(145)}{50} = 232$$

$$6400 + 160R + R^2 + X^2 = 53824$$

$$160R + R^2 + X^2 = 47424 \quad (4)$$

Subtracting (3) from (4),

$$160R = 16448 \longrightarrow R = \underline{\underline{102.8 \, \Omega}}$$

From (3),

$$X^2 = 30976 - 10568 = 20408$$

$$X = 142.86 = 377L \longrightarrow L = \underline{\underline{0.3789 \, H}}$$

**Chapter 9, Solution 91.**

$$\mathbf{Z}_{\text{in}} = \frac{1}{j\omega C} + R \parallel j\omega L$$

$$\begin{aligned}\mathbf{Z}_{\text{in}} &= \frac{-j}{\omega C} + \frac{j\omega LR}{R + j\omega L} \\ &= \frac{-j}{\omega C} + \frac{\omega^2 L^2 R + j\omega LR^2}{R^2 + \omega^2 L^2}\end{aligned}$$

To have a resistive impedance,  $\text{Im}(\mathbf{Z}_{\text{in}}) = 0$ .

Hence,

$$\frac{-1}{\omega C} + \frac{\omega LR^2}{R^2 + \omega^2 L^2} = 0$$

$$\frac{1}{\omega C} = \frac{\omega LR^2}{R^2 + \omega^2 L^2}$$

$$C = \frac{R^2 + \omega^2 L^2}{\omega^2 LR^2}$$

where  $\omega = 2\pi f = 2\pi \times 10^7$

$$C = \frac{9 \times 10^4 + (4\pi^2 \times 10^{14})(400 \times 10^{-12})}{(4\pi^2 \times 10^{14})(20 \times 10^{-6})(9 \times 10^4)}$$

$$C = \frac{9 + 16\pi^2}{72\pi^2} \text{ nF}$$

$$C = \underline{\underline{235 \text{ pF}}}$$

**Chapter 9, Solution 92.**

$$(a) \ Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{100 \angle 75^\circ}{450 \angle 48^\circ \times 10^{-6}}} = \underline{\underline{471.4 \angle 13.5^\circ \Omega}}$$

$$(b) \ \gamma = \sqrt{ZY} = \sqrt{100 \angle 75^\circ \times 450 \angle 48^\circ \times 10^{-6}} = \underline{\underline{0.2121 \angle 61.5^\circ}}$$

**Chapter 9, Solution 93.**

$$\mathbf{Z} = \mathbf{Z}_s + 2\mathbf{Z}_\ell + \mathbf{Z}_L$$

$$\mathbf{Z} = (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$\mathbf{Z} = 25 + j20$$

$$\mathbf{I}_L = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{115\angle 0^\circ}{32.02\angle 38.66^\circ}$$

$$\mathbf{I}_L = \underline{\underline{3.592\angle -38.66^\circ \text{ A}}}$$