

- (b) At the point *SWR*: $S = 1.64$.
 (c) Z_{in} is 0.350λ from the load, which is at 0.144λ on the wavelengths to generator scale. So point *Z-IN* is at $0.144\lambda + 0.350\lambda = 0.494\lambda$ on the WTG scale. At point *Z-IN*:

$$Z_{in} = z_{in}Z_0 = (0.61 - j0.022) \times 50 \Omega = (30.5 - j1.09) \Omega.$$

- (d) At the point on the *SWR* circle opposite *Z-IN*,

$$Y_{in} = \frac{y_{in}}{Z_0} = \frac{(1.64 + j0.06)}{50 \Omega} = (32.7 + j1.17) \text{ mS}.$$

(e) Traveling from the point *Z-LOAD* in the direction of the generator (clockwise), the *SWR* circle crosses the $x_L = 0$ line first at the point *SWR*. To travel from *Z-LOAD* to *SWR* one must travel $0.250\lambda - 0.144\lambda = 0.106\lambda$. (Readings are on the wavelengths to generator scale.) So the shortest line length would be 0.106λ .

(f) The voltage max occurs at point *SWR*. From the previous part, this occurs at $z = -0.106\lambda$.

Problem 2.39 A lossless $50\text{-}\Omega$ transmission line is terminated in a short circuit. Use the Smith chart to find

- (a) the input impedance at a distance 2.3λ from the load,
 (b) the distance from the load at which the input admittance is $Y_{in} = -j0.04 \text{ S}$.

Solution: Refer to Fig. P2.39.

(a) For a short, $z_{in} = 0 + j0$. This is point *Z-SHORT* and is at 0.000λ on the WTG scale. Since a lossless line repeats every $\lambda/2$, traveling 2.3λ toward the generator is equivalent to traveling 0.3λ toward the generator. This point is at *A : Z-IN*, and

$$Z_{in} = z_{in}Z_0 = (0 - j3.08) \times 50 \Omega = -j154 \Omega.$$

(b) The admittance of a short is at point *Y-SHORT* and is at 0.250λ on the WTG scale:

$$y_{in} = Y_{in}Z_0 = -j0.04 \text{ S} \times 50 \Omega = -j2,$$

which is point *B : Y-IN* and is at 0.324λ on the WTG scale. Therefore, the line length is $0.324\lambda - 0.250\lambda = 0.074\lambda$. Any integer half wavelengths farther is also valid.

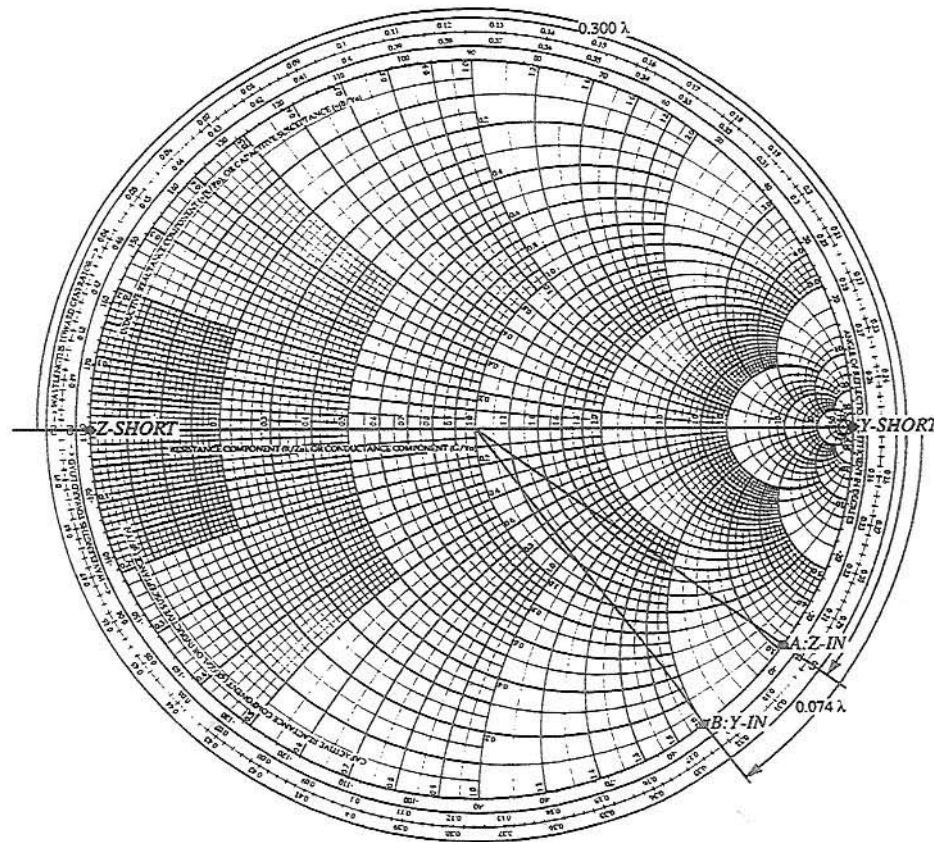


Figure P2.39: Solution of Problem 2.39.

Problem 2.40 Use the Smith chart to find y_L if $z_L = 1.5 - j0.7$.

Solution: Refer to Fig. P2.40. The point Z represents $1.5 - j0.7$. The reciprocal of point Z is at point Y , which is at $0.55 + j0.26$.

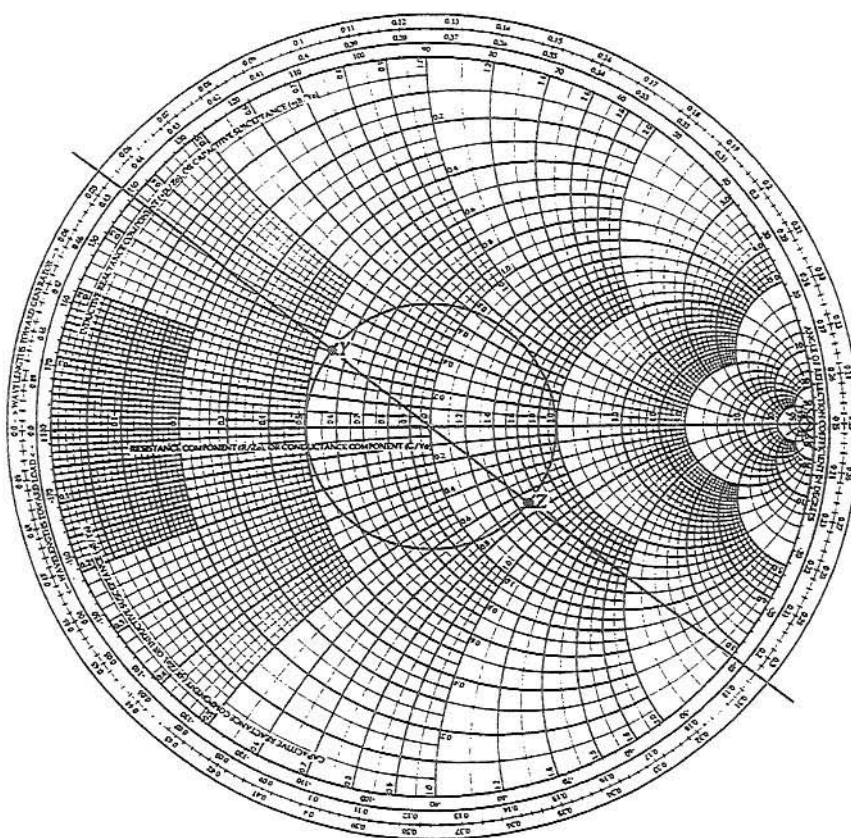


Figure P2.40: Solution of Problem 2.40.

Problem 2.41 A lossless $100\text{-}\Omega$ transmission line $3\lambda/8$ in length is terminated in an unknown impedance. If the input impedance is $Z_{\text{in}} = -j2.5\text{ }\Omega$,

- use the Smith chart to find Z_L .
- What length of open-circuit line could be used to replace Z_L ?

Solution: Refer to Fig. P2.41. $z_{\text{in}} = Z_{\text{in}}/Z_0 = -j2.5\text{ }\Omega/100\text{ }\Omega = 0.0 - j0.025$ which is at point *Z-IN* and is at 0.004λ on the wavelengths to load scale.

(a) Point *Z-LOAD* is 0.375λ toward the load from the end of the line. Thus, on the wavelength to load scale, it is at $0.004\lambda + 0.375\lambda = 0.379\lambda$.

$$Z_L = z_L Z_0 = (0 + j0.95) \times 100\text{ }\Omega = j95\text{ }\Omega.$$

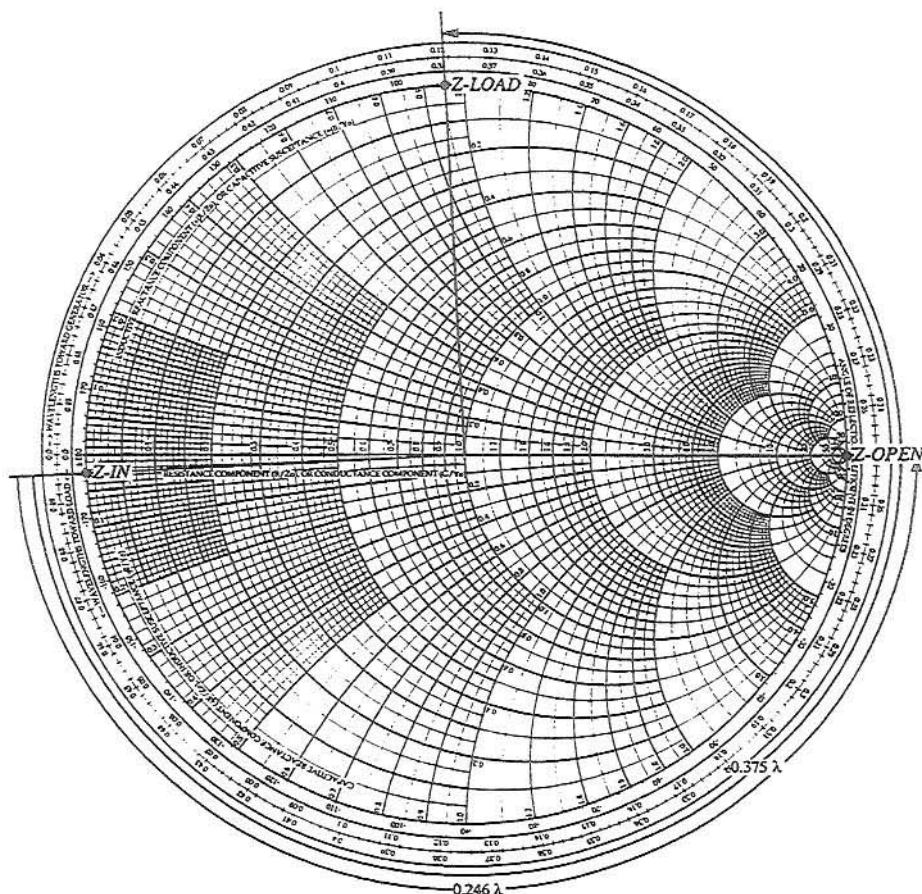


Figure P2.41: Solution of Problem 2.41.

(b) An open circuit is located at point *Z-OPEN*, which is at 0.250λ on the wavelength to load scale. Therefore, an open circuited line with $Z_{in} = -j0.025$ must have a length of $0.250\lambda - 0.004\lambda = 0.246\lambda$.

Problem 2.42: A $75\text{-}\Omega$ lossless line is 0.6λ long. If $S = 1.8$ and $\theta_r = -60^\circ$, use the Smith chart to find $|\Gamma|$, Z_L , and Z_{in} .

Solution: Refer to Fig. P2.42. The SWR circle must pass through $S = 1.8$ at point *SWR*. A circle of this radius has

$$|\Gamma| = \frac{S-1}{S+1} = 0.29.$$

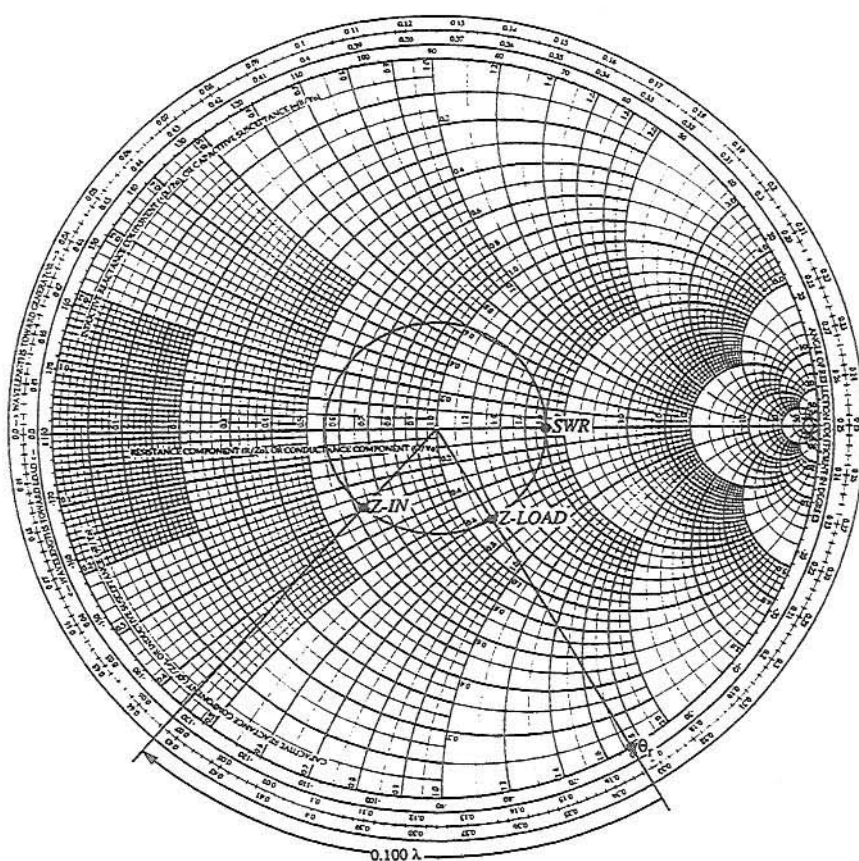


Figure P2.42: Solution of Problem 2.42.

The load must have a reflection coefficient with $\theta_r = -60^\circ$. The angle of the reflection coefficient is read off that scale at the point θ_r . The intersection of the circle of constant $|\Gamma|$ and the line of constant θ_r is at the load, point *Z-LOAD*, which has a value $z_L = 1.15 - j0.62$. Thus,

$$Z_L = z_L Z_0 = (1.15 - j0.62) \times 75 \, \Omega = (86.5 - j46.6) \, \Omega.$$

A 0.6λ line is equivalent to a 0.1λ line. On the WTG scale, *Z-LOAD* is at 0.333λ , so *Z-IN* is at $0.333\lambda + 0.100\lambda = 0.433\lambda$ and has a value

$$z_{in} = 0.63 - j0.29.$$

Therefore $Z_{in} = z_{in}Z_0 = (0.63 - j0.29) \times 75 \Omega = (47.0 - j21.8) \Omega$.

Problem 2.43 Using a slotted line on a $50\text{-}\Omega$ air-spaced lossless line, the following measurements were obtained: $S = 1.6$, $|\tilde{V}|_{\max}$ occurred only at 10 cm and 24 cm from the load. Use the Smith chart to find Z_L .

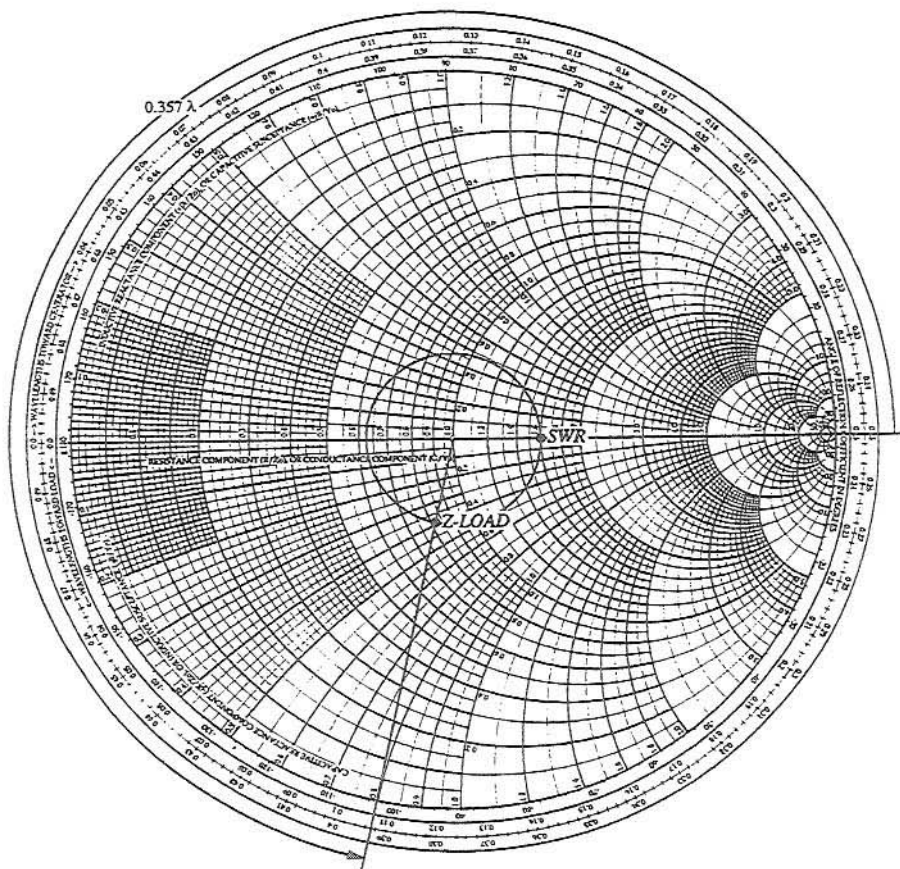


Figure P2.43: Solution of Problem 2.43.

Solution: Refer to Fig. P2.43. The point SWR denotes the fact that $S = 1.6$. This point is also the location of a voltage maximum. From the knowledge of the locations of adjacent maxima we can determine that $\lambda = 2(24\text{ cm} - 10\text{ cm}) = 28\text{ cm}$. Therefore, the load is $\frac{10\text{ cm}}{28\text{ cm}}\lambda = 0.357\lambda$ from the first voltage maximum, which is at 0.250λ on the WTL scale. Traveling this far on the SWR circle we find point $Z\text{-LOAD}$.

at $0.250\lambda + 0.357\lambda - 0.500\lambda = 0.107\lambda$ on the WTL scale, and here

$$z_L = 0.82 - j0.39.$$

Therefore $Z_L = z_L Z_0 = (0.82 - j0.39) \times 50 \Omega = (41.0 - j19.5) \Omega$.

Problem 2.44 At an operating frequency of 5 GHz, a 50- Ω lossless coaxial line with insulating material having a relative permittivity $\epsilon_r = 2.25$ is terminated in an antenna with an impedance $Z_L = 75 \Omega$. Use the Smith chart to find Z_{in} . The line length is 30 cm.

Solution: To use the Smith chart the line length must be converted into wavelengths. Since $\beta = 2\pi/\lambda$ and $u_p = \omega/\beta$,

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi u_p}{\omega} = \frac{c}{\sqrt{\epsilon_r} f} = \frac{3 \times 10^8 \text{ m/s}}{\sqrt{2.25} \times (5 \times 10^9 \text{ Hz})} = 0.04 \text{ m}.$$

Hence, $l = \frac{0.30 \text{ m}}{0.04 \text{ m}} \lambda = 7.5\lambda$. Since this is an integral number of half wavelengths,

$$Z_{in} = Z_L = 75 \Omega.$$

Section 2-10: Impedance Matching

Problem 2.45 A 50- Ω lossless line 0.6λ long is terminated in a load with $Z_L = (50 + j25) \Omega$. At 0.3λ from the load, a resistor with resistance $R = 30 \Omega$ is connected as shown in Fig. 2-43 (P2.45(a)). Use the Smith chart to find Z_{in} .

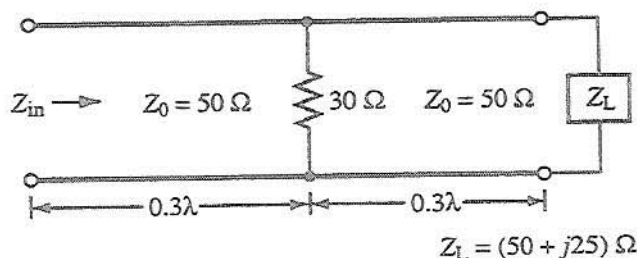


Figure P2.45: (a) Circuit for Problem 2.45.

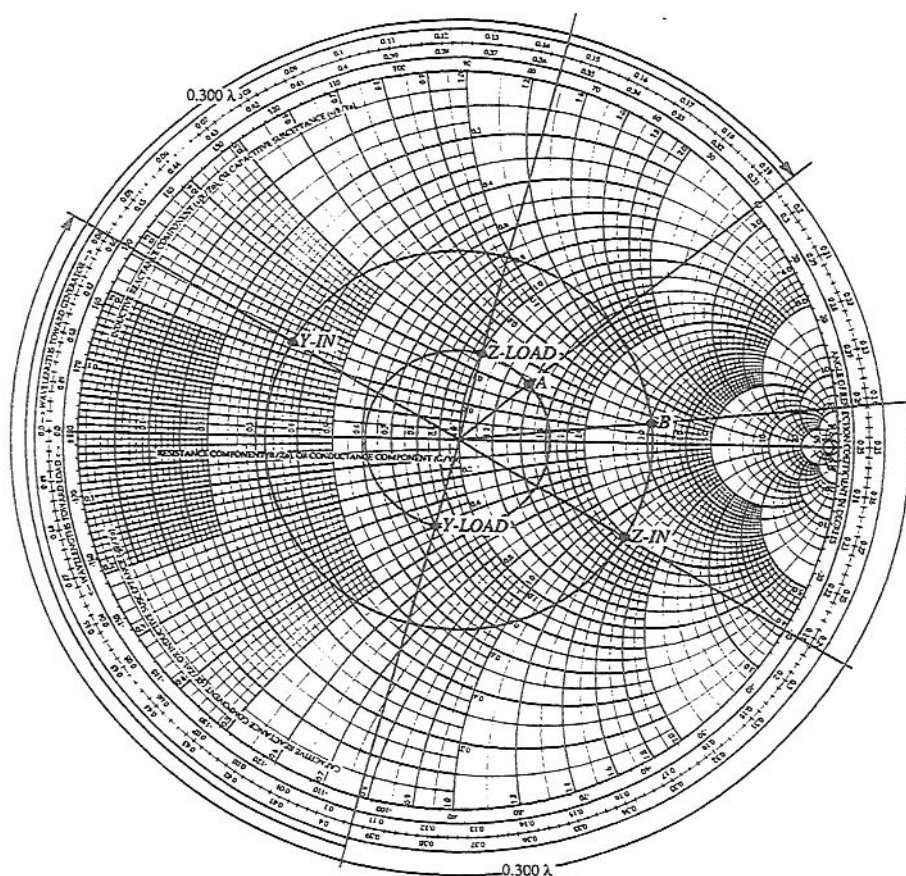


Figure P2.45: (b) Solution of Problem 2.45.

Solution: Refer to Fig. P2.45(b). Since the $30\text{-}\Omega$ resistor is in parallel with the input impedance at that point, it is advantageous to convert all quantities to admittances.

$$z_L = \frac{Z_L}{Z_0} = \frac{(50 + j25)\ \Omega}{50\ \Omega} = 1 + j0.5$$

and is located at point *Z-LOAD*. The corresponding normalized load admittance is at point *Y-LOAD*, which is at 0.394λ on the WTG scale. The input admittance of the load only at the shunt conductor is at $0.394\lambda + 0.300\lambda - 0.500\lambda = 0.194\lambda$ and is denoted by point *A*. It has a value of

$$y_{inA} = 1.37 + j0.45.$$

The shunt conductance has a normalized conductance

$$g = \frac{50 \Omega}{30 \Omega} = 1.67.$$

The normalized admittance of the shunt conductance in parallel with the input admittance of the load is the sum of their admittances:

$$y_{inB} = g + y_{inA} = 1.67 + 1.37 + j0.45 = 3.04 + j0.45$$

and is located at point *B*. On the WTG scale, point *B* is at 0.242λ . The input admittance of the entire circuit is at $0.242\lambda + 0.300\lambda - 0.500\lambda = 0.042\lambda$ and is denoted by point *Y-IN*. The corresponding normalized input impedance is at *Z-IN* and has a value of

$$z_{in} = 1.9 - j1.4.$$

Thus,

$$Z_{in} = z_{in}Z_0 = (1.9 - j1.4) \times 50 \Omega = (95 - j70) \Omega.$$

Problem 2.46 A $50\text{-}\Omega$ lossless line is to be matched to an antenna with

$$Z_L = (75 - j20) \Omega$$

using a shorted stub. Use the Smith chart to determine the stub length and the distance between the antenna and the stub.

Solution: Refer to Fig. P2.46(a) and Fig. P2.46(b), which represent two different solutions.

$$z_L = \frac{Z_L}{Z_0} = \frac{(75 - j20) \Omega}{50 \Omega} = 1.5 - j0.4$$

and is located at point *Z-LOAD* in both figures. Since it is advantageous to work in admittance coordinates, y_L is plotted as point *Y-LOAD* in both figures. *Y-LOAD* is at 0.041λ on the WTG scale.

For the first solution in Fig. P2.46(a), point *Y-LOAD-IN-1* represents the point at which $g = 1$ on the SWR circle of the load. *Y-LOAD-IN-1* is at 0.145λ on the WTG scale, so the stub should be located at $0.145\lambda - 0.041\lambda = 0.104\lambda$ from the load (or some multiple of a half wavelength further). At *Y-LOAD-IN-1*, $b = 0.52$, so a stub with an input admittance of $y_{stub} = 0 - j0.52$ is required. This point is *Y-STUB-IN-1* and is at 0.423λ on the WTG scale. The short circuit admittance

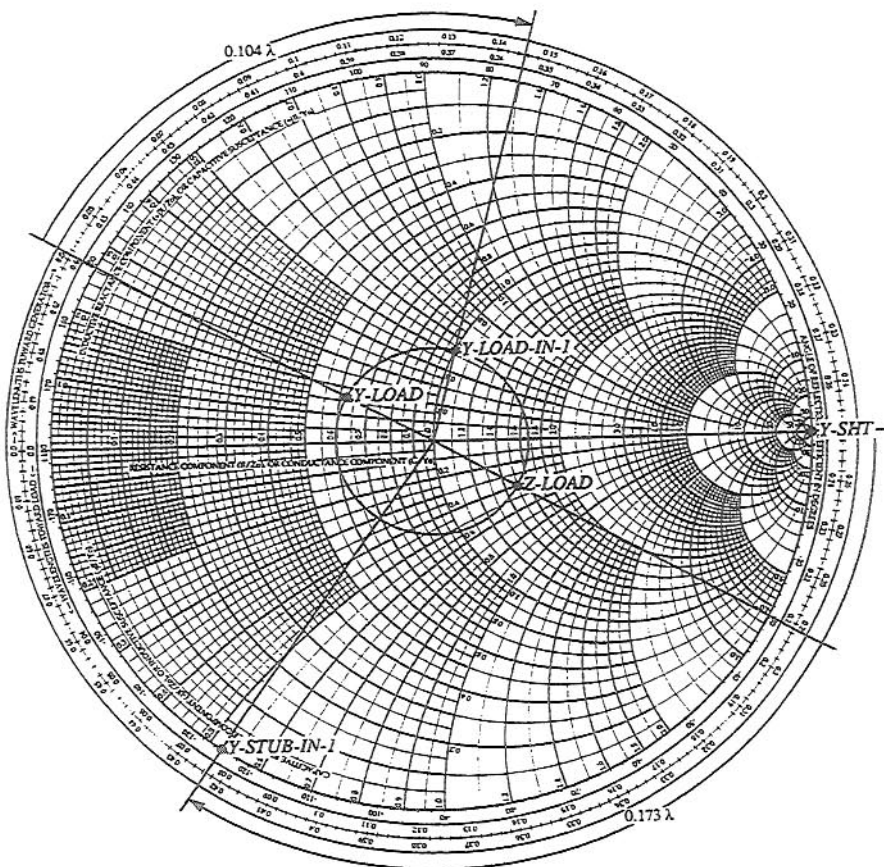


Figure P2.46: (a) First solution to Problem 2.46.

is denoted by point $Y-SHT$, located at 0.250λ . Therefore, the short stub must be $0.423\lambda - 0.250\lambda = 0.173\lambda$ long (or some multiple of a half wavelength longer).

For the second solution in Fig. P2.46(b), point $Y-LOAD-IN-2$ represents the point at which $g = 1$ on the SWR circle of the load. $Y-LOAD-IN-2$ is at 0.355λ on the WTG scale, so the stub should be located at $0.355\lambda - 0.041\lambda = 0.314\lambda$ from the load (or some multiple of a half wavelength further). At $Y-LOAD-IN-2$, $b = -0.52$, so a stub with an input admittance of $y_{stub} = 0 + j0.52$ is required. This point is $Y-STUB-IN-2$ and is at 0.077λ on the WTG scale. The short circuit admittance is denoted by point $Y-SHT$, located at 0.250λ . Therefore, the short stub must be $0.077\lambda - 0.250\lambda + 0.500\lambda = 0.327\lambda$ long (or some multiple of a half wavelength

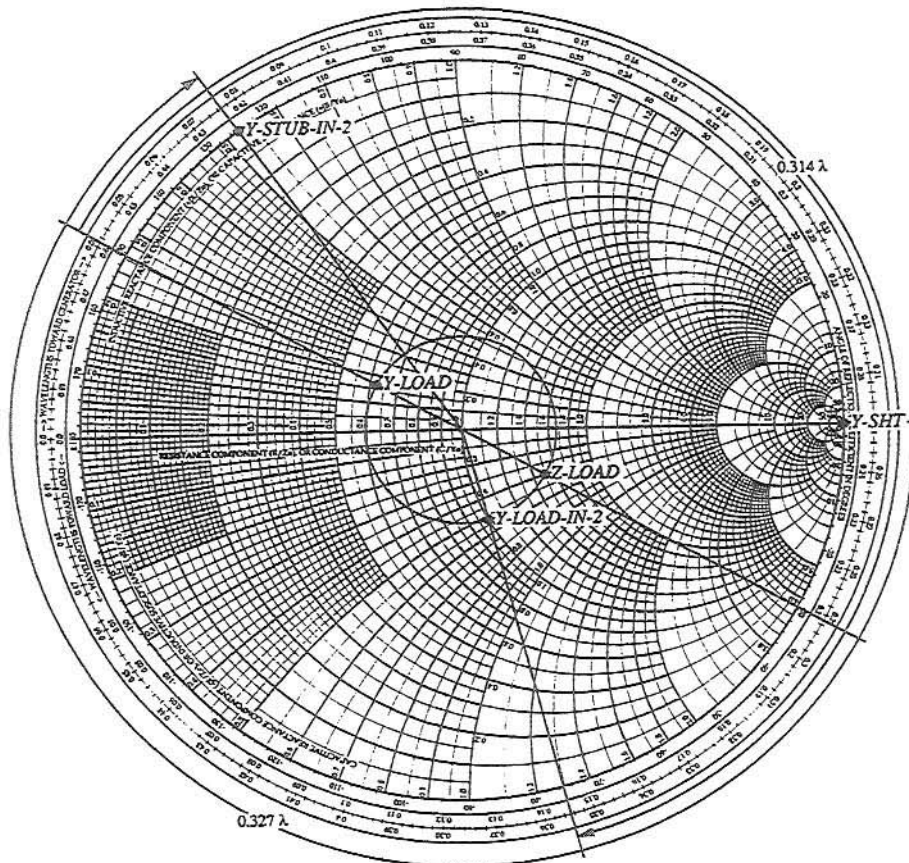


Figure P2.46: (b) Second solution to Problem 2.46.

longer).

Problem 2.47 Repeat Problem 2.46 for a load with $Z_L = (100 + j50) \Omega$.

Solution: Refer to Fig. P2.47(a) and Fig. P2.47(b), which represent two different solutions.

$$z_L = \frac{Z_L}{Z_0} = \frac{100 + j50 \Omega}{50 \Omega} = 2 + j1$$

and is located at point $Z\text{-LOAD}$ in both figures. Since it is advantageous to work in admittance coordinates, y_L is plotted as point $Y\text{-LOAD}$ in both figures. $Y\text{-LOAD}$ is at 0.463λ on the WTG scale.

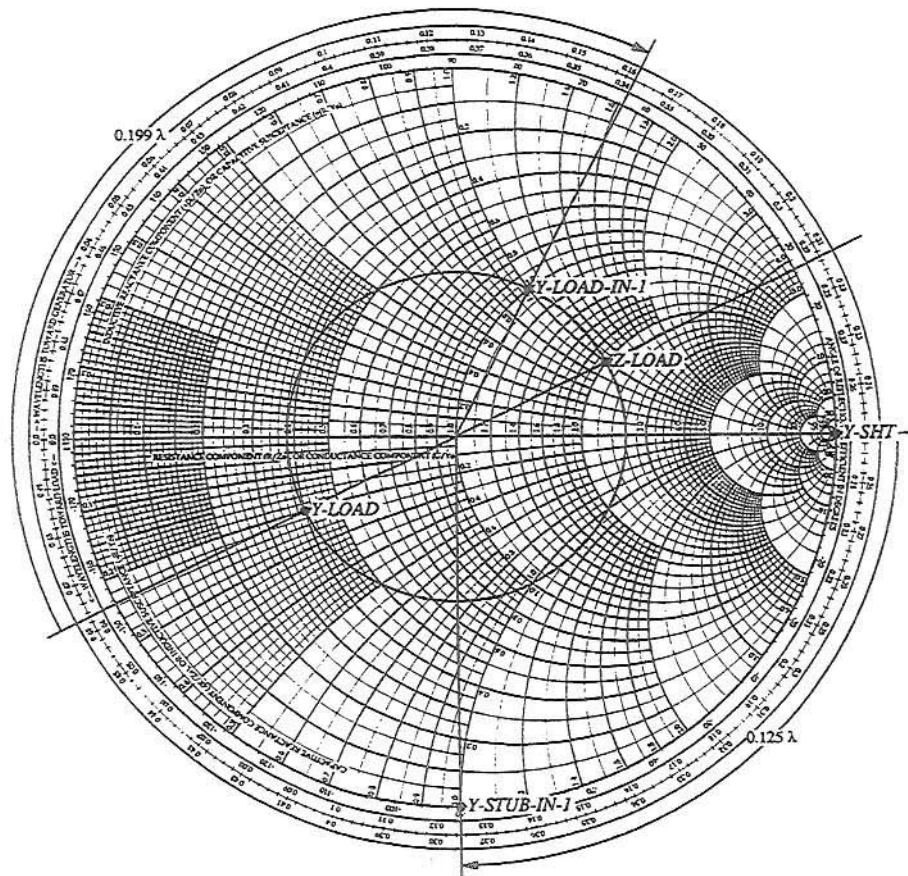


Figure P2.47: (a) First solution to Problem 2.47.

For the first solution in Fig. P2.47(a), point *Y-LOAD-IN-1* represents the point at which $g = 1$ on the SWR circle of the load. *Y-LOAD-IN-1* is at 0.162λ on the WTG scale, so the stub should be located at $0.162\lambda - 0.463\lambda + 0.500\lambda = 0.199\lambda$ from the load (or some multiple of a half wavelength further). At *Y-LOAD-IN-1*, $b = 1$, so a stub with an input admittance of $y_{\text{stub}} = 0 - j1$ is required. This point is *Y-STUB-IN-1* and is at 0.375λ on the WTG scale. The short circuit admittance is denoted by point *Y-SHT*, located at 0.250λ . Therefore, the short stub must be $0.375\lambda - 0.250\lambda = 0.125\lambda$ long (or some multiple of a half wavelength longer).

For the second solution in Fig. P2.47(b), point *Y-LOAD-IN-2* represents the point at which $g = 1$ on the SWR circle of the load. *Y-LOAD-IN-2* is at 0.338λ on the

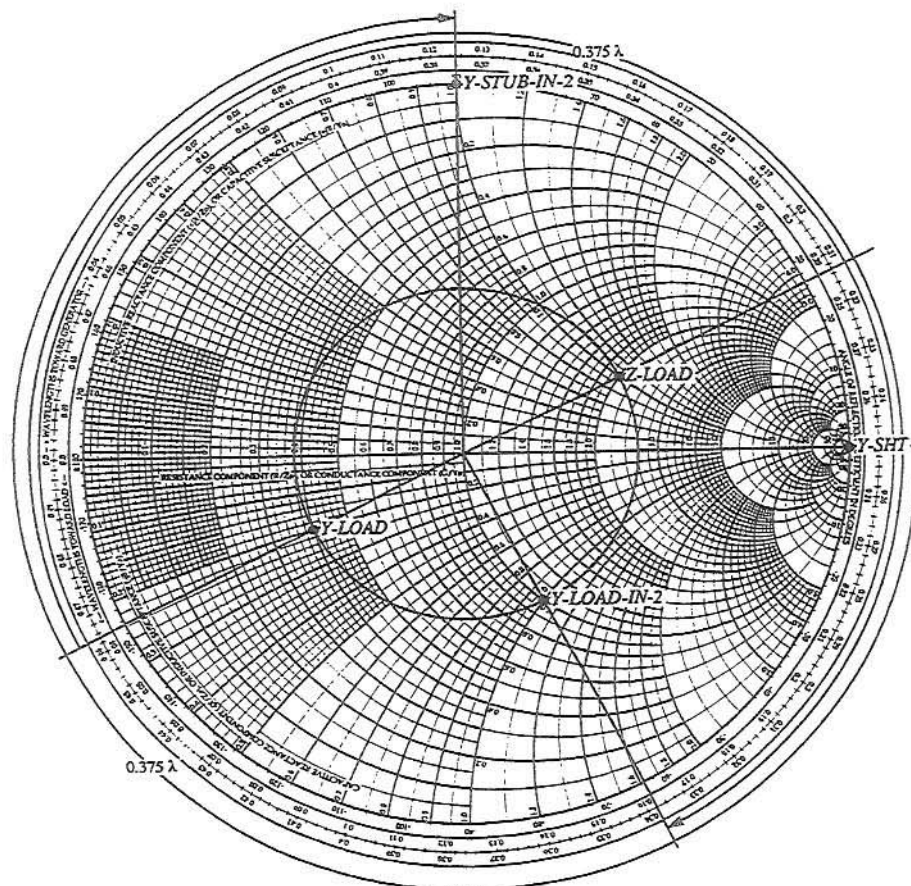


Figure P2.47: (b) Second solution to Problem 2.47.

WTG scale, so the stub should be located at $0.338\lambda - 0.463\lambda + 0.500\lambda = 0.375\lambda$ from the load (or some multiple of a half wavelength further). At $Y\text{-LOAD-IN-2}$, $b = -1$, so a stub with an input admittance of $y_{\text{stub}} = 0 + j1$ is required. This point is $Y\text{-STUB-IN-2}$ and is at 0.125λ on the WTG scale. The short circuit admittance is denoted by point $Y\text{-SHT}$, located at 0.250λ . Therefore, the short stub must be $0.125\lambda - 0.250\lambda + 0.500\lambda = 0.375\lambda$ long (or some multiple of a half wavelength longer).

Problem 2.48 Use the Smith chart to find Z_{in} of the feed line shown in Fig. 2-44 (P2.48(a)). All lines are lossless with $Z_0 = 50 \Omega$.

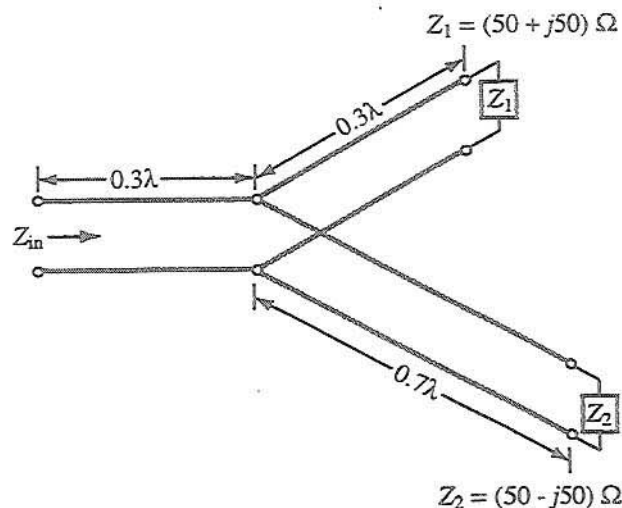


Figure P2.48: (a) Circuit of Problem 2.48.

Solution: Refer to Fig. P2.48(b).

$$z_1 = \frac{Z_1}{Z_0} = \frac{50 + j50 \Omega}{50 \Omega} = 1 + j1$$

and is at point *Z-LOAD-1*.

$$z_2 = \frac{Z_2}{Z_0} = \frac{50 - j50 \Omega}{50 \Omega} = 1 - j1$$

and is at point *Z-LOAD-2*. Since at the junction the lines are in parallel, it is advantageous to solve the problem using admittances. y_1 is point *Y-LOAD-1*, which is at 0.412λ on the WTG scale. y_2 is point *Y-LOAD-2*, which is at 0.088λ on the WTG scale. Traveling 0.300λ from *Y-LOAD-1* toward the generator one obtains the input admittance for the upper feed line, point *Y-IN-1*, with a value of $1.97 + j1.02$. Since traveling 0.700λ is equivalent to traveling 0.200λ on any transmission line, the input admittance for the lower line feed is found at point *Y-IN-2*, which has a value of $1.97 - j1.02$. The admittance of the two lines together is the sum of their admittances: $1.97 + j1.02 + 1.97 - j1.02 = 3.94 + j0$ and is denoted *Y-JUNCT*. 0.300λ from *Y-JUNCT* toward the generator is the input admittance of the entire feed line, point *Y-IN*, from which *Z-IN* is found.

$$Z_{in} = z_{in}Z_0 = (1.65 - j1.79) \times 50 \Omega = (82.5 - j89.5) \Omega.$$

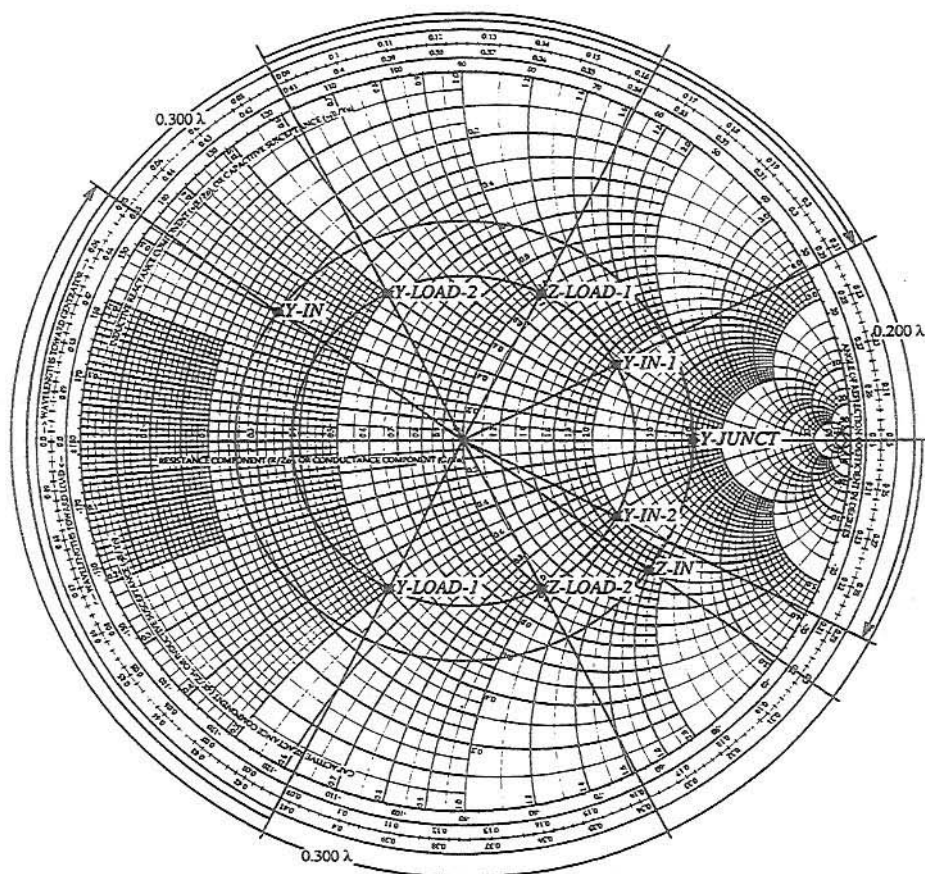


Figure P2.48: (b) Solution of Problem 2.48.

Problem 2.49 Repeat Problem 2.48 for the case where all three transmission lines are $\lambda/4$ in length.

Solution: Since the transmission lines are in parallel, it is advantageous to express loads in terms of admittances. In the upper branch, which is a quarter wave line,

$$Y_{1\text{ in}} = \frac{Y_0^2}{Y_1} = \frac{Z_1}{Z_0^2},$$

and similarly for the lower branch,

$$Y_{2\text{ in}} = \frac{Y_0^2}{Y_2} = \frac{Z_2}{Z_0^2}.$$

Thus, the total load at the junction is

$$Y_{\text{JCT}} = Y_{1\text{ in}} + Y_{2\text{ in}} = \frac{Z_1 + Z_2}{Z_0^2}.$$

Therefore, since the common transmission line is also quarter-wave,

$$Z_{\text{in}} = Z_0^2 / Z_{\text{JCT}} = Z_0^2 Y_{\text{JCT}} = Z_1 + Z_2 = (50 + j50) \Omega + (50 - j50) \Omega = 100 \Omega.$$

Section 2-11: Transients on Transmission Lines

Problem 2.50 Generate a bounce diagram for the voltage $V(z, t)$ for a 1-m long lossless line characterized by $Z_0 = 50 \Omega$ and $u_p = 2c/3$ (where c is the velocity of light) if the line is fed by a step voltage applied at $t = 0$ by a generator circuit with $V_g = 60 \text{ V}$ and $R_g = 100 \Omega$. The line is terminated in a load $Z_L = 25 \Omega$. Use the bounce diagram to plot $V(t)$ at a point midway along the length of the line from $t = 0$ to $t = 25 \text{ ns}$.

Solution:

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = \frac{1}{3},$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = \frac{-25}{75} = -\frac{1}{3}.$$

From Eq. (2.124b),

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0} = \frac{60 \times 50}{100 + 50} = 20 \text{ V}.$$

Also,

$$T = \frac{l}{u_p} = \frac{l}{2c/3} = \frac{3}{2 \times 3 \times 10^8} = 5 \text{ ns}.$$

The bounce diagram is shown in Fig. P2.50(a) and the plot of $V(t)$ in Fig. P2.50(b).

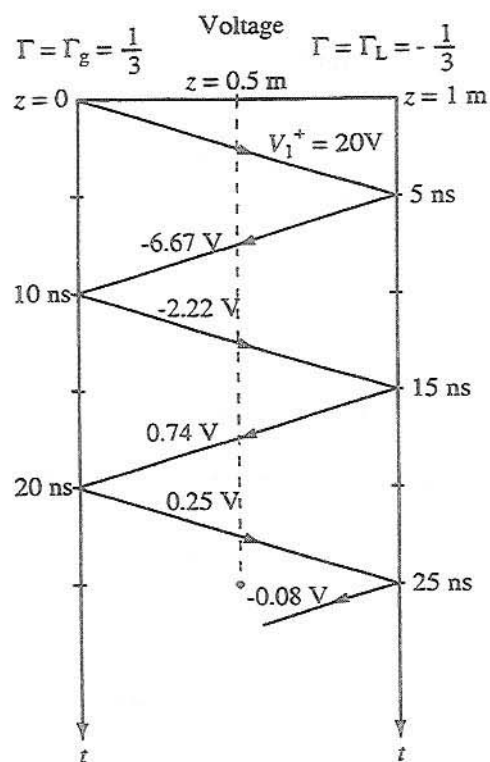


Figure P2.50: (a) Bounce diagram for Problem 2.50.

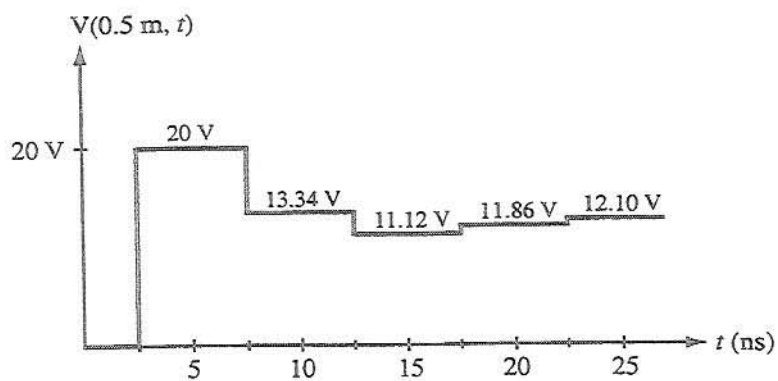


Figure P2.50: (b) Time response of voltage.

Problem 2.51 Repeat Problem 2.50 for the current I on the line.

Solution:

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3},$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3}.$$

From Eq. (2.124a),

$$I_1^+ = \frac{V_g}{R_g + Z_0} = \frac{60}{100 + 50} = 0.4 \text{ A}.$$

The bounce diagram is shown in Fig. P2.51(a) and $I(t)$ in Fig. P2.51(b).

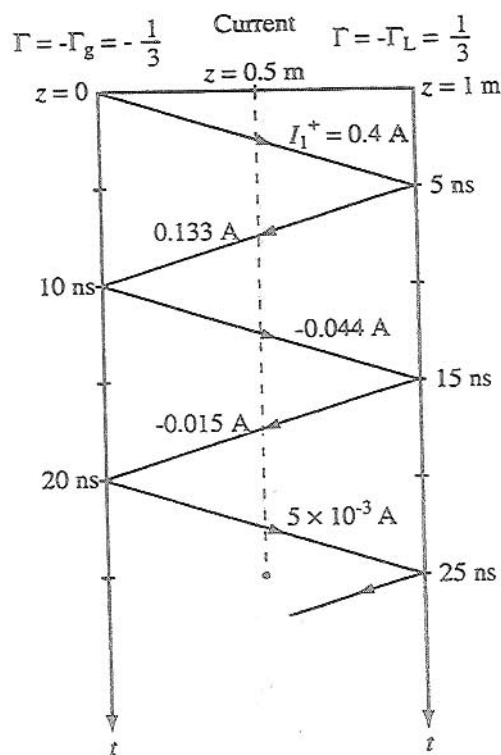


Figure P2.51: (a) Bounce diagram for Problem 2.51.

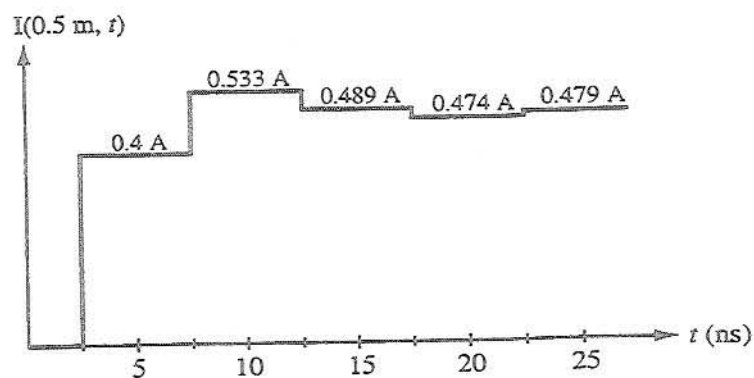


Figure P2.51: (b) Time response of current.

Problem 2.52 In response to a step voltage, the voltage waveform shown in Fig. 2-45 (P2.52) was observed at the sending end of a lossless transmission line with $R_g = 50 \Omega$, $Z_0 = 50 \Omega$, and $\epsilon_r = 2.25$. Determine (a) the generator voltage, (b) the length of the line, and (c) the load impedance.

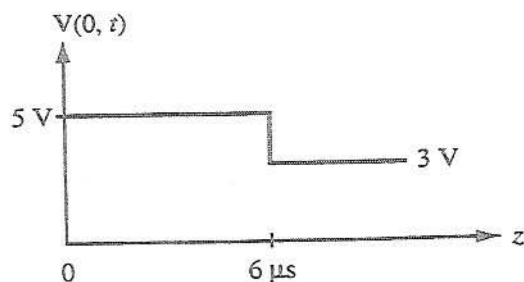


Figure P2.52: Observed voltage at sending end.

Solution:

(a) From the figure, $V_1^+ = 5 \text{ V}$. Applying Eq. (2.124b),

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0} = \frac{V_g Z_0}{Z_0 + Z_0} = \frac{V_g}{2},$$

which gives $V_g = 2V_1^+ = 10 \text{ V}$.

(b) $u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.25}} = 2 \times 10^8$ m/s. The first change in the waveform occurs at $\Delta t = 6 \mu\text{s}$. But $\Delta t = 2l/u_p$. Hence,

$$l = \frac{\Delta t u_p}{2} = \frac{6 \times 10^{-6}}{2} \times 2 \times 10^8 = 600 \text{ m.}$$

(c) The change in level from 5 V down to 3 V means that $V_1^- = -2$ V. But

$$V_1^- = \Gamma_L V_1^+, \quad \text{or} \quad \Gamma_L = \frac{V_1^-}{V_1^+} = \frac{-2}{5} = -0.4.$$

From

$$Z_L = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) = 50 \left(\frac{1 - 0.4}{1 + 0.4} \right) = 21.43 \Omega.$$

Problem 2.53 In response to a step voltage, the voltage waveform shown in Fig. 2.46 (P2.53) was observed at the sending end of a shorted line with $Z_0 = 50 \Omega$ and $\epsilon_r = 4$. Determine V_g , R_g , and the line length.

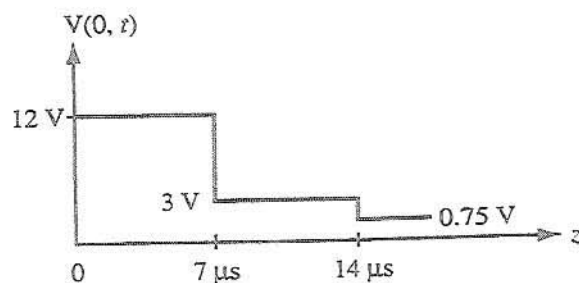


Figure P2.53: Observed voltage at sending end.

Solution:

$$u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{4}} = 1.5 \times 10^8 \text{ m/s,}$$

$$7 \mu\text{s} = 7 \times 10^{-6} \text{ s} = \frac{2l}{u_p} = \frac{2l}{1.5 \times 10^8}.$$

Hence, $l = 525 \text{ m.}$

From the voltage waveform, $V_1^+ = 12$ V. At $t = 7\mu\text{s}$, the voltage at the sending end is

$$V(z=0, t=7\mu\text{s}) = V_1^+ + \Gamma_L V_1^+ + \Gamma_g \Gamma_L V_1^+ = -\Gamma_g V_1^+ \quad (\text{because } \Gamma_L = -1).$$

Hence, $3\text{ V} = -\Gamma_g \times 12\text{ V}$, or $\Gamma_g = -0.25$. From Eq. (2.128),

$$R_g = Z_0 \left(\frac{1 + \Gamma_g}{1 - \Gamma_g} \right) = 50 \left(\frac{1 - 0.25}{1 + 0.25} \right) = 30\ \Omega.$$

Also,

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0}, \quad \text{or} \quad 12 = \frac{V_g \times 50}{30 + 50},$$

which gives $V_g = 19.2$ V.

Problem 2.54 Suppose the voltage waveform shown in Fig. 2-45 was observed at the sending end of a $50\text{-}\Omega$ transmission line in response to a step voltage introduced by a generator with $V_g = 15$ V and an unknown series resistance R_g . The line is 1 km in length, its velocity of propagation is 1×10^8 m/s, and it is terminated in a load $Z_L = 100\ \Omega$.

- Determine R_g .
- Explain why the drop in level of $V(0, t)$ at $t = 6\ \mu\text{s}$ cannot be due to reflection from the load.
- Determine the shunt resistance R_f and the location of the fault responsible for the observed waveform.

Solution:

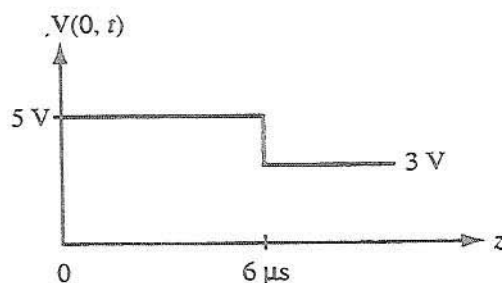


Figure P2.54: Observed voltage at sending end.

(a)

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0}.$$

From Fig. 2-45, $V_1^+ = 5$ V. Hence,

$$5 = \frac{15 \times 50}{R_g + 50},$$

which gives $R_g = 100 \Omega$.

(b) Roundtrip time delay of pulse return from the load is

$$2T = \frac{2l}{u_p} = \frac{2 \times 10^3}{1 \times 10^8} = 20 \mu\text{s},$$

which is much longer than $6 \mu\text{s}$, the instance at which $V(0, t)$ drops in level.

(c) $V_1^+ = 5$ V. The new level of 3 V is equal to V_1^+ plus V_1^- due to shunt resistance:

$$V_1^+ + V_1^- = 5 + 5\Gamma = 3 \quad (\text{V}),$$

or $\Gamma = -\frac{2}{5} = -0.4$. But

$$\Gamma = \frac{R_f - Z_0}{R_f + Z_0} = -0.4,$$

which gives $R_f = 21.43 \Omega$.

Problem 2.55 A generator circuit with $V_g = 200$ V and $R_g = 25 \Omega$ was used to excite a $75\text{-}\Omega$ lossless line with a rectangular pulse of duration $\tau = 0.4 \mu\text{s}$. The line is 200 m long, its $u_p = 2 \times 10^8$ m/s, and it is terminated in a load $Z_L = 125 \Omega$.

- Synthesize the voltage pulse exciting the line as the sum of two step functions, $V_{g1}(t)$ and $V_{g2}(t)$.
- For each voltage step function, generate a bounce diagram for the voltage on the line.
- Use the bounce diagrams to plot the total voltage at the sending end of the line.

Solution:

(a) pulse length = $0.4 \mu\text{s}$.

$$V_g(t) = V_{g1}(t) + V_{g2}(t),$$

with

$$V_{g1}(t) = 200 U(t) \quad (\text{V}),$$

$$V_{g2}(t) = -200 U(t - 0.4 \mu\text{s}) \quad (\text{V}).$$

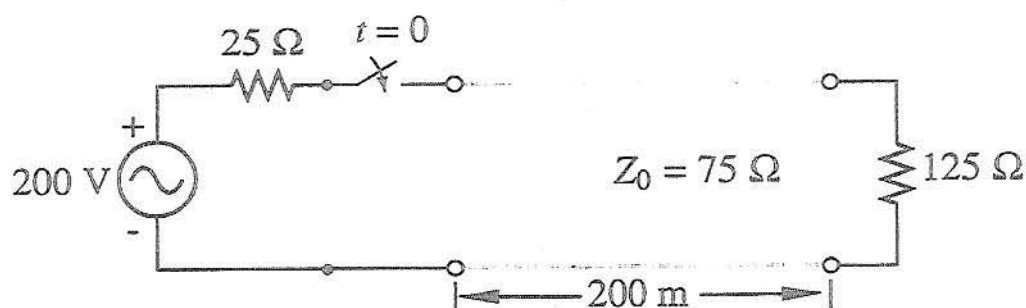


Figure P2.55: (a) Circuit for Problem 2.55.

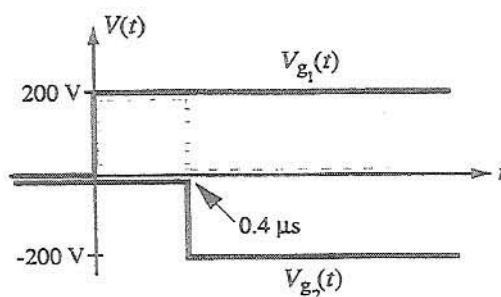


Figure P2.55: (b) Solution of part (a).

(b)

$$T = \frac{l}{u_p} = \frac{200}{2 \times 10^8} = 1 \mu\text{s}.$$

We will divide the problem into two parts, one for $V_{g1}(t)$ and another for $V_{g2}(t)$ and then we will use superposition to determine the solution for the sum. The solution for $V_{g2}(t)$ will mimic the solution for $V_{g1}(t)$, except for a reversal in sign and a delay by $0.4 \mu\text{s}$.

For $V_{g1}(t) = 200 U(t)$:

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{25 - 75}{25 + 75} = -0.5,$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{125 - 75}{125 + 75} = 0.25,$$

$$V_1^+ = \frac{V_1 Z_0}{R_g + Z_0} = \frac{200 \times 75}{25 + 75} = 150 \text{ V},$$

$$V_\infty = \frac{V_g Z_L}{R_g + Z_L} = \frac{200 \times 125}{25 + 125} = 166.67 \text{ V}.$$

(i) $V_1(0, t)$ at sending end due to $V_{g_1}(t)$:

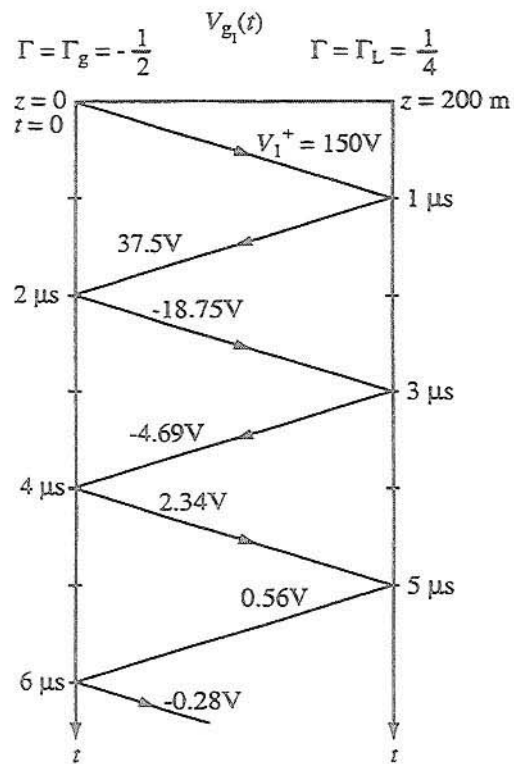


Figure P2.55: (c) Bounce diagram for voltage in reaction to $V_{g_1}(t)$.

(ii) $V_2(0, t)$ at sending end due to $V_{g_2}(t)$:

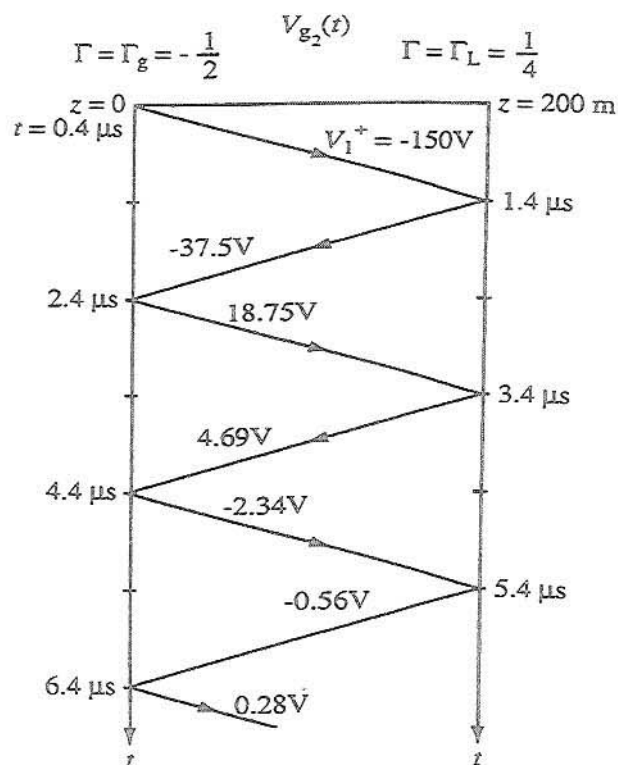
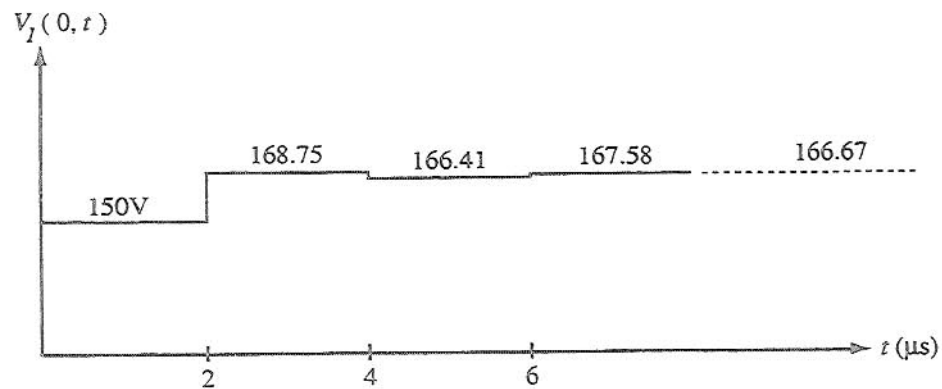
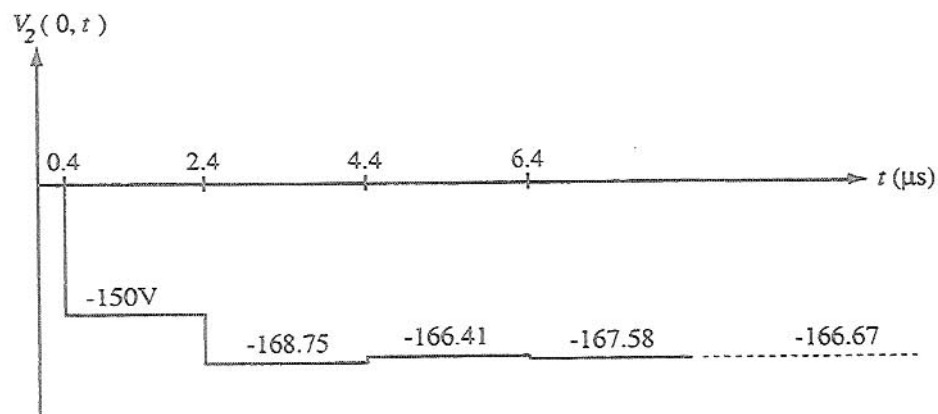


Figure P2.55: (d) Bounce diagram for voltage in reaction to $V_{g_2}(t)$.

(b)

(i) $V_1(0, t)$ at sending end due to $V_{g_1}(t)$:Figure P2.55: (e) $V_1(0, t)$.(ii) $V_2(0, t)$ at sending end:Figure P2.55: (f) $V_2(0, t)$.

(iii) Net voltage $V(0,t) = V_1(0,t) + V_2(0,t)$:

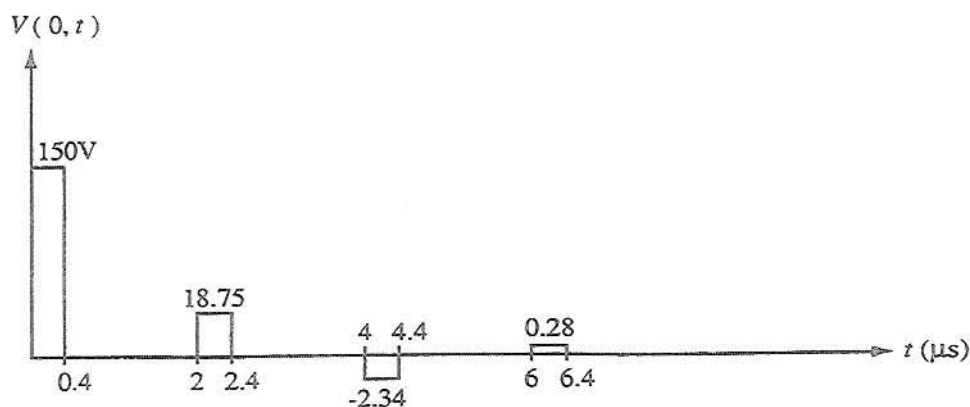


Figure P2.55: (g) Net voltage $V(0,t)$.

Problem 2.56 For the circuit of Problem 2.55, generate a bounce diagram for the current and plot its time history at the middle of the line.

Solution: Using the values for Γ_g and Γ_L calculated in Problem 2.55, we reverse their signs when using them to construct a bounce diagram for the current.

$$I_1^+ = \frac{V_1^+}{Z_0} = \frac{150}{75} = 2 \text{ A},$$

$$I_2^+ = \frac{V_2^+}{Z_0} = \frac{-150}{75} = -2 \text{ A},$$

$$I_\infty^+ = \frac{V_\infty}{Z_L} = 1.33 \text{ A}.$$

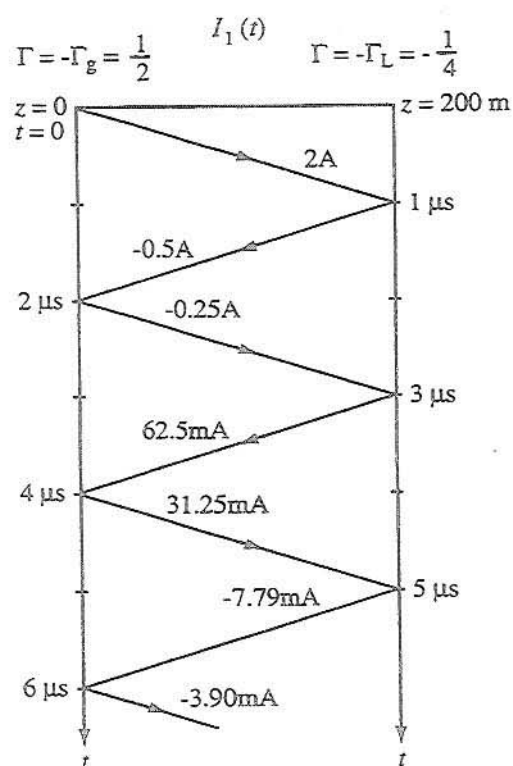


Figure P2.56: (a) Bounce diagram for $I_1(t)$ in reaction to $V_{g1}(t)$.

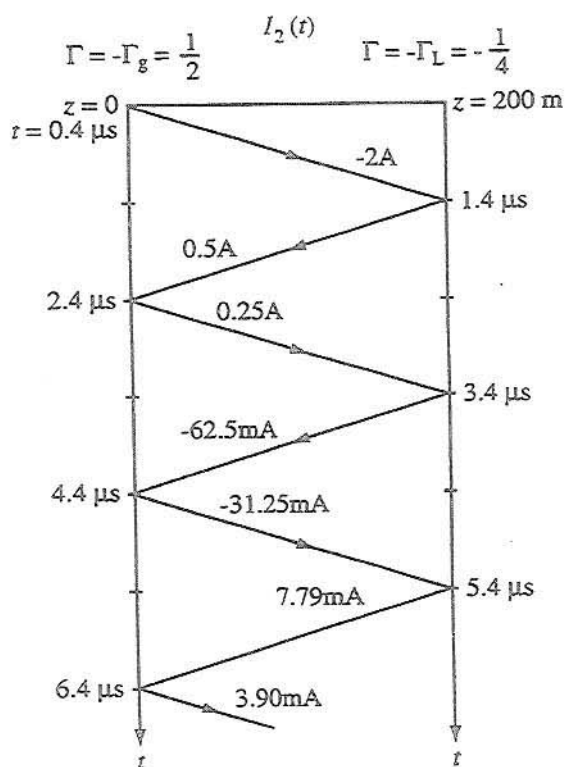


Figure P2.56: (b) Bounce diagram for current $I_2(t)$ in reaction to $V_{g2}(t)$.

(i) $I_1(l/2, t)$ due to $V_{g1}(t)$:

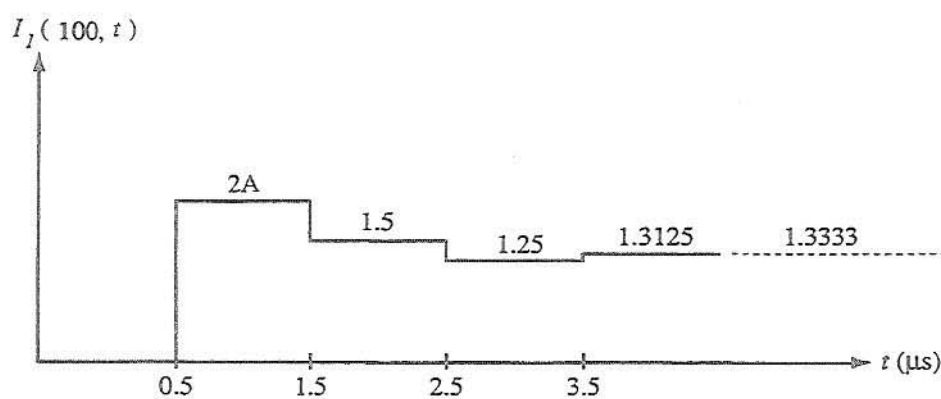


Figure P2.56: (c) $I_1(l/2, t)$.

(ii) $I_2(l/2, t)$ due to $V_{g2}(t)$:

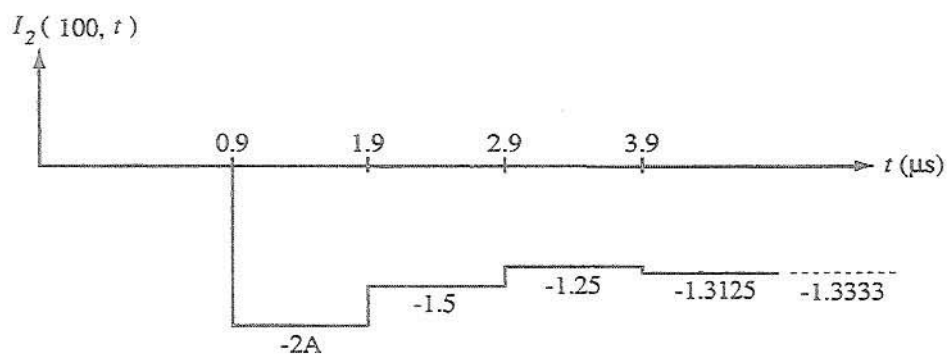


Figure P2.56: (d) $I_2(l/2, t)$.

(iii) Net current $I(l/2, t) = I_1(l/2, t) + I_2(l/2, t)$:

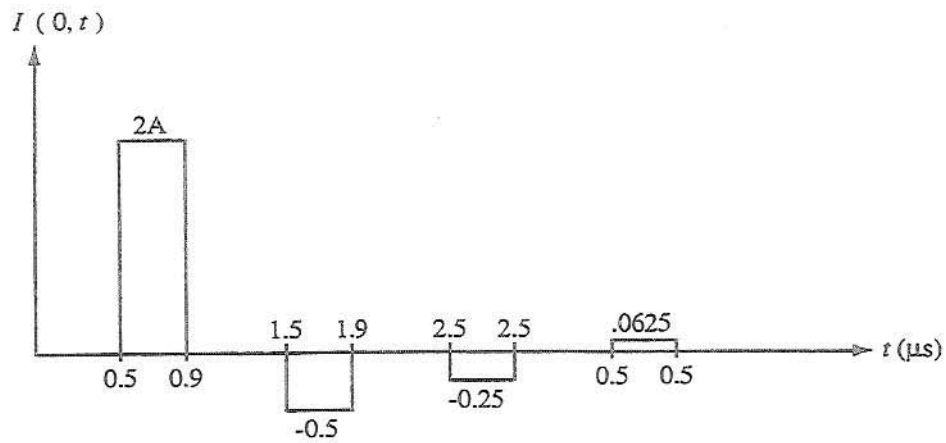


Figure P2.56: (e) Total $I(l/2, t)$.