


# Chapter Three:

## Nodal and Loop Analysis Techniques



**3.1** Find  $I_o$  in the circuit in Fig. P3.1 using nodal analysis.


**CS**

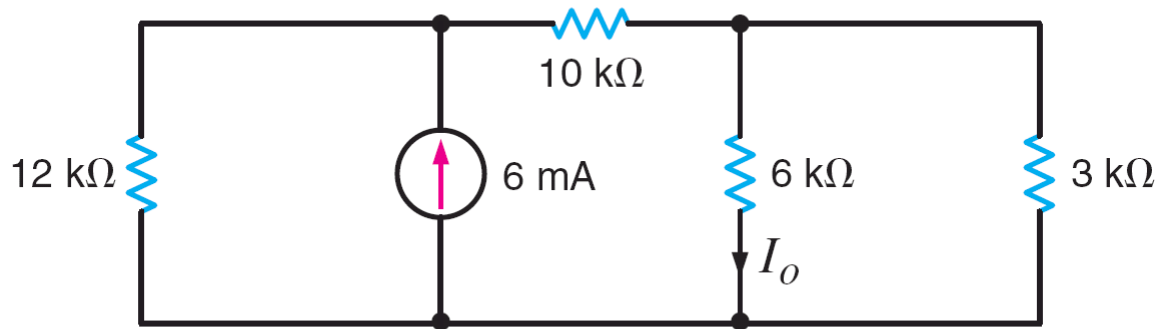

**Figure P3.1**

**SOLUTION:**

3.1  $I_o$  via nodal.

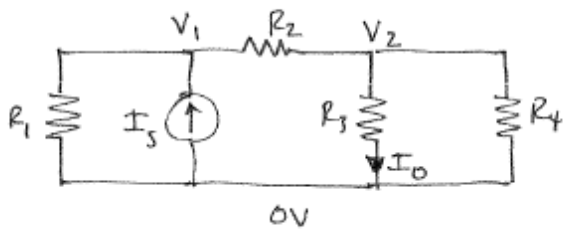

$$R_1 = 12 \text{ k}\Omega \quad R_2 = 10 \text{ k}\Omega \quad R_3 = 6 \text{ k}\Omega$$

$$R_4 = 3 \text{ k}\Omega \quad I_s = 6 \text{ mA}$$


$$@ V_1: \quad \frac{V_1}{R_1} - I_s + \frac{V_1 - V_2}{R_2} = 0$$

$$@ V_2: \quad \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = 0$$

$$\# : I_o = V_2 / R_3$$

$$I_o = 1 \text{ mA}$$


**3.2** Use nodal analysis to find  $V_1$  in the circuit in Fig. P3.2.

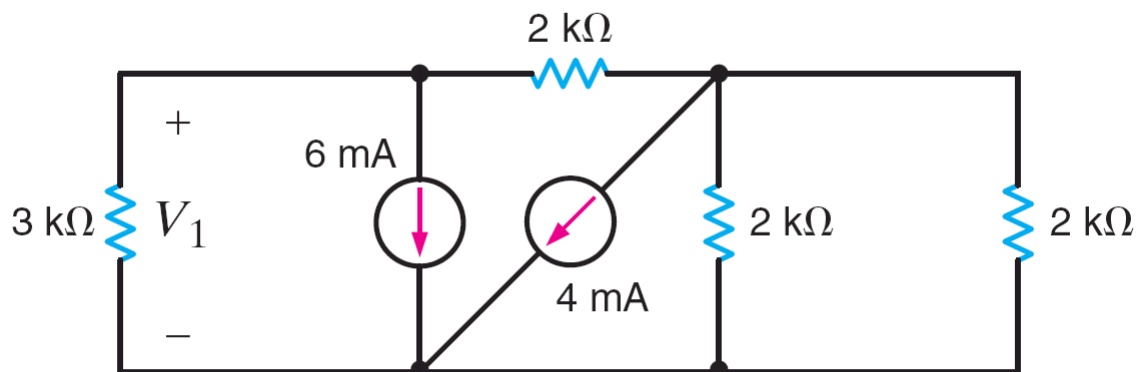

**Figure P3.2**

SOLUTION:

3.2 Find  $V_1$  via nodal.

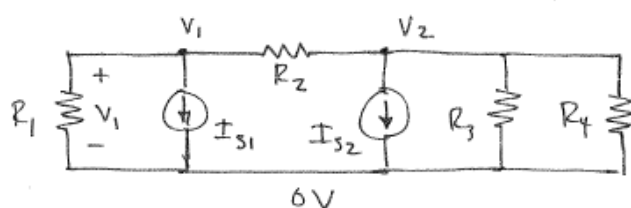

$$R_1 = 3\text{ k}\Omega \quad R_2 = R_3 = R_4 = 2\text{ k}\Omega$$


$$I_{s1} = 6\text{ mA} \quad I_{s2} = 4\text{ mA}$$

$$@ V_1: \frac{V_1}{R_1} + I_{s1} + \frac{V_1 - V_2}{R_2} = 0$$

$$@ V_2: \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} + I_{s2} = 0$$

$$\boxed{V_1 = -11\text{ V}}$$


**3.3** Use nodal analysis to find both  $V_1$  and  $V_o$  in the circuit in Fig. P3.3. **PSV**

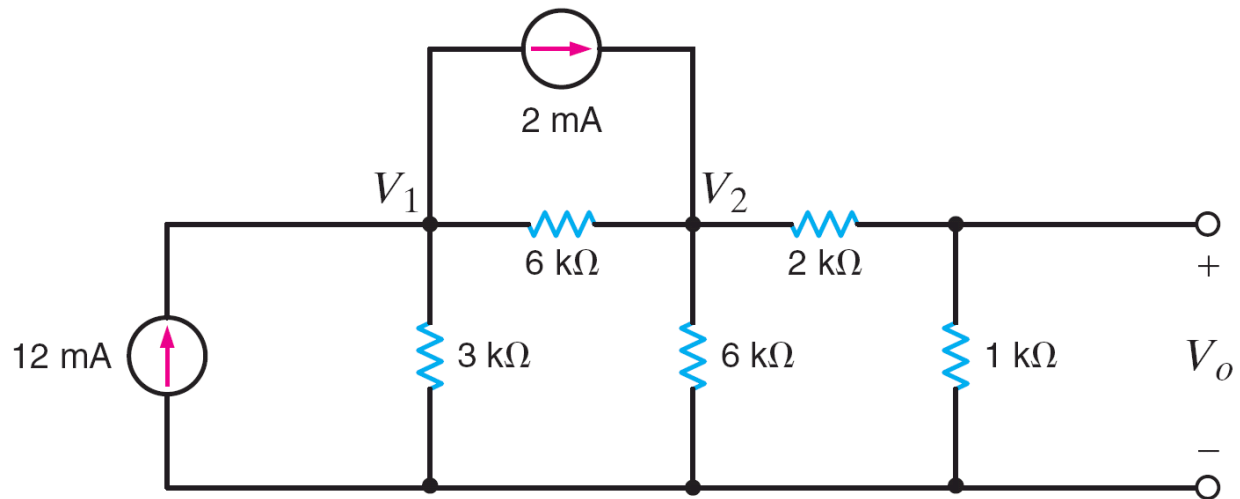

**Figure P3.3**

**SOLUTION:**

3.3 Find  $V_o$  &  $V_1$  by nodal.

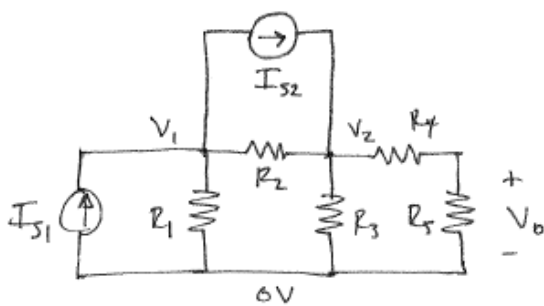

$$R_1 = 3\text{ k}\Omega \quad R_2 = R_3 = 6\text{ k}\Omega \quad R_4 = 2\text{ k}\Omega$$

$$R_5 = 1\text{ k}\Omega \quad I_{s1} = 12\text{ mA} \quad I_{s2} = 2\text{ mA}$$


$$@ V_1: I_{s2} - I_{s1} + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$@ V_2: -I_{s2} + \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2 - V_o}{R_4} = 0$$

$$@ V_o: \frac{V_2 - V_o}{R_4} = \frac{V_o}{R_5}$$

$$V_o = 2.91\text{ V} \quad V_1 = 22.9\text{ V}$$


**3.4** Find  $V_1$  and  $V_2$  in the circuit in Fig. P3.4 using nodal analysis. Then solve the problem using MATLAB and compare your answers.

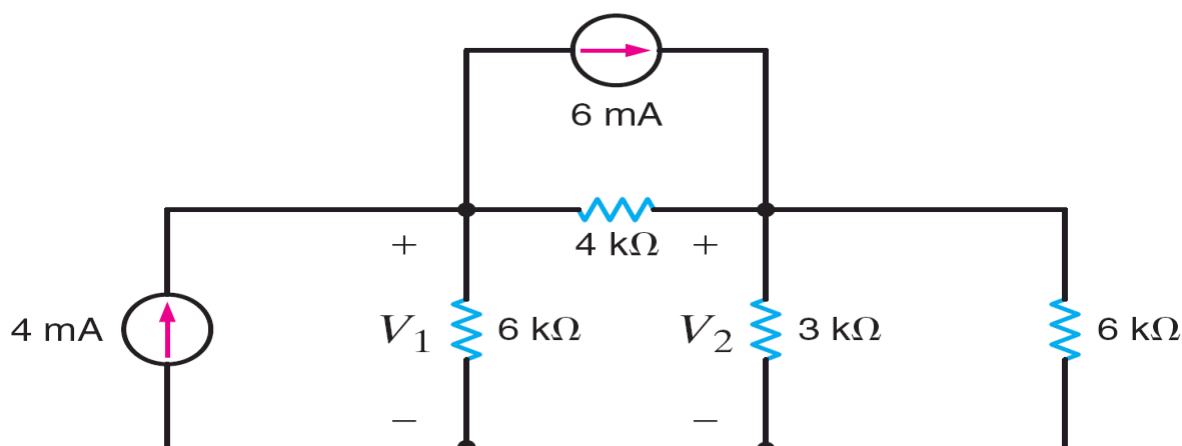

**Figure P3.4**

SOLUTION:

3.4 Find  $V_1$  &  $V_2$  by nodal

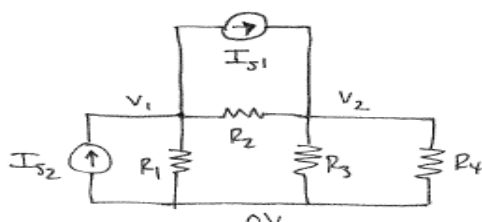

$$R_1 = R_4 = 6 \text{ k}\Omega \quad R_2 = 4 \text{ k}\Omega \quad R_3 = 3 \text{ k}\Omega$$

$$I_{S1} = 6 \text{ mA} \quad I_{S2} = 4 \text{ mA}$$

$$\text{@ } V_1: I_{S1} - I_{S2} + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\text{@ } V_2: -I_{S1} + \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = 0$$

$$\boxed{V_1 = 0 \text{ V} \quad V_2 = 8 \text{ V}}$$

matrix Format

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{S2} - I_{S1} \\ I_{S1} \end{bmatrix}$$

Continued on the next page.

3\_4.txt

MATLAB WORK

Factor 1/24000 out of conductance matrix.

EDU&gt; g=[12,-6;-6,18]

g =

$$\begin{bmatrix} 12 & -6 \\ -6 & 18 \end{bmatrix}$$

EDU&gt; i=[-0.002;0.006]

i =

$$\begin{bmatrix} -0.0020 \\ 0.0060 \end{bmatrix}$$


EDU&gt; 24000\*inv(g)\*i

ans =

$$\begin{bmatrix} 0 \\ 8 \end{bmatrix}$$

**3.5** Find  $I_o$  in the circuit in Fig. P3.5 using nodal analysis.


**CS**

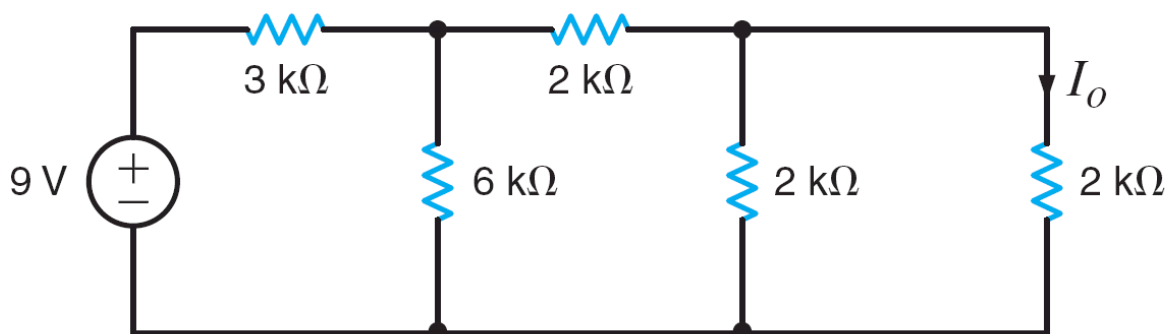

**Figure P3.5**

SOLUTION:

3.5 Find  $I_o$  by nodal.

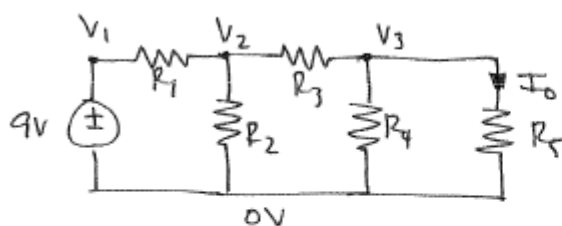

$$R_1 = 3\text{ k}\Omega \quad R_2 = 6\text{ k}\Omega \quad R_3 = R_4 = R_5 = 2\text{ k}\Omega$$

$$\text{@ } V_1: V_1 = 9\text{ V}$$

$$\text{@ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$


$$\text{@ } V_3: \frac{V_3 - V_2}{R_3} + \frac{V_3}{R_4} + \frac{V_3}{R_5} = 0$$

$$\text{and } I_o = V_3 / R_5$$

$$\boxed{I_o = 0.6\text{ mA}}$$




**3.6** Find  $I_o$  in the network in Fig. P3.6 using nodal analysis.

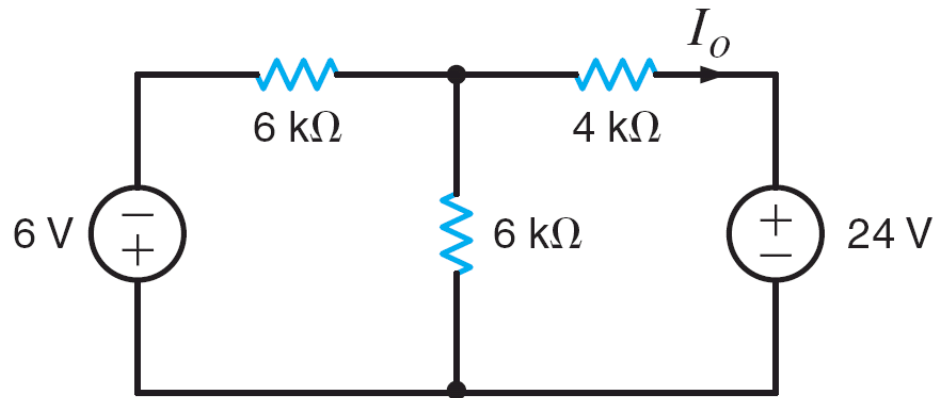

**Figure P3.6**

SOLUTION:

3.6 Find  $I_o$  by nodal.

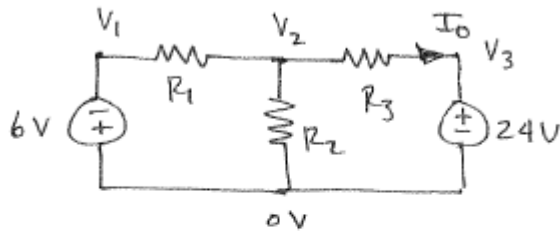

$$R_1 = R_2 = 6 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

$$\textcircled{V}_1: V_1 = -6 \text{ V}$$

$$\textcircled{V}_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$\textcircled{V}_3: V_3 = 24 \text{ V}$$


$$\text{and } I_o = (V_2 - V_3) / R_3$$

$$V_2 = 8.57 \text{ V}$$

$$I_o = -3.86 \text{ mA}$$

**3.7** Find  $V_o$  in the network in Fig. P3.7 using nodal analysis.


**CS**

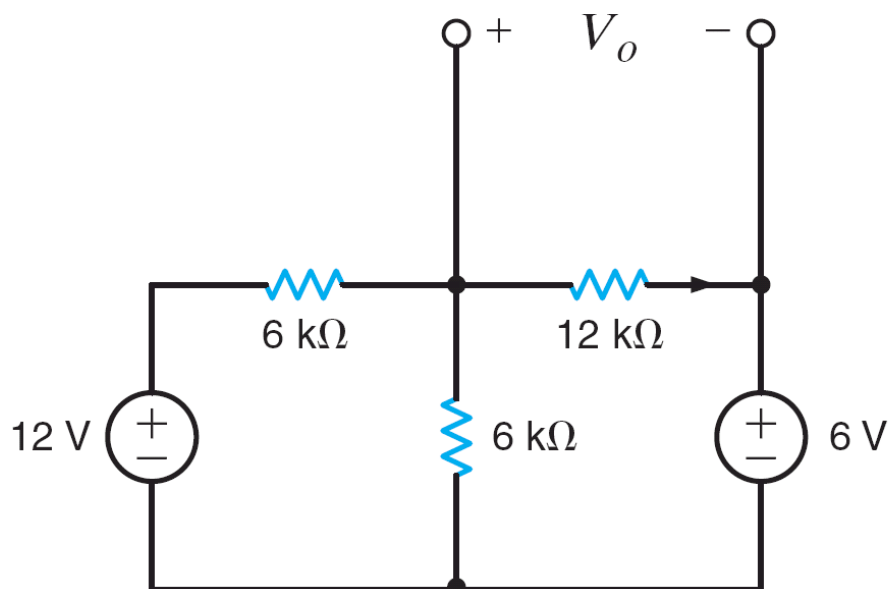

**Figure P3.7**

**SOLUTION:**

3.7 Find  $V_o$  by nodal.

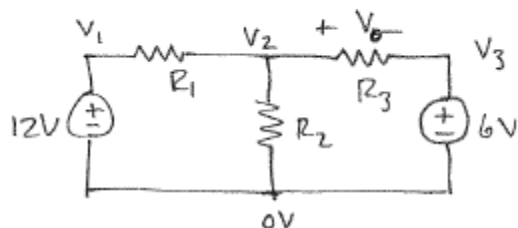

$$R_1 = R_2 = 6 \text{ k}\Omega$$

$$R_3 = 12 \text{ k}\Omega$$

$$@ V_1: V_1 = 12 \text{ V}$$

$$@ V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$@ V_3: V_3 = 6 \text{ V}$$


$$\text{and } V_o = V_2 - V_3$$

$$V_2 = 6 \text{ V}$$

$$V_o = 0 \text{ V}$$

**3.8** Find  $V_o$  in the circuit in Fig. P3.8 using nodal analysis.


**PSV**

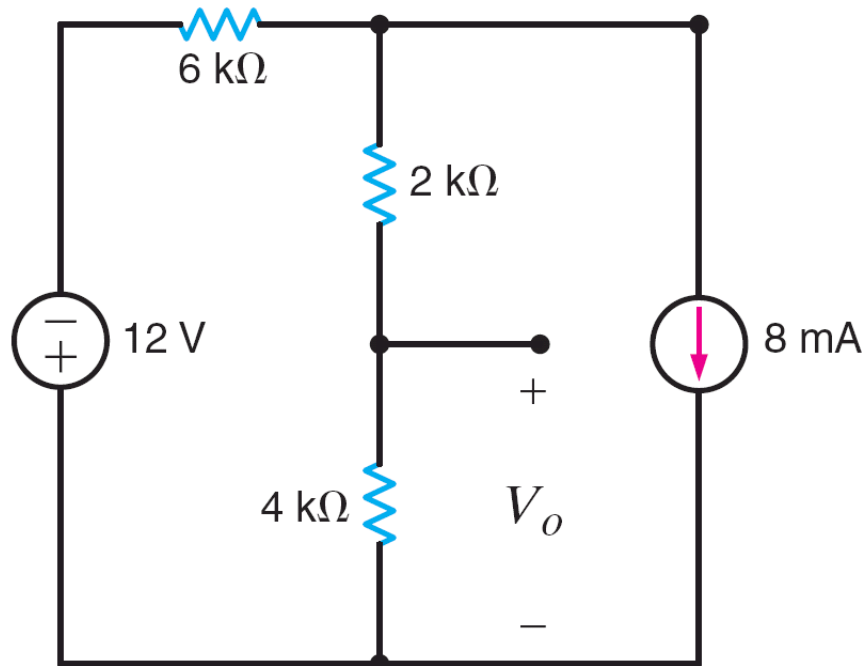

**Figure P3.8**

**SOLUTION:**

3.8 Find  $V_o$  by nodal.

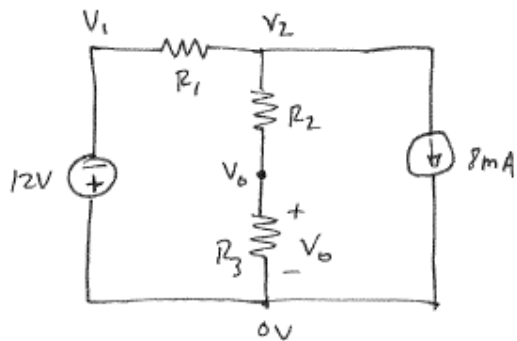

$$R_1 = 6\text{ k}\Omega \quad R_2 = 2\text{ k}\Omega \quad R_3 = 4\text{ k}\Omega$$


$$V_1 = -12\text{ V}$$

$$\text{@ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_o}{R_2} + 8 \times 10^{-3} = 0$$

$$\text{@ } V_o: \frac{V_2 - V_o}{R_2} = \frac{V_o}{R_3}$$

$$\boxed{V_o = -20\text{ V}}$$


**3.9** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.9.

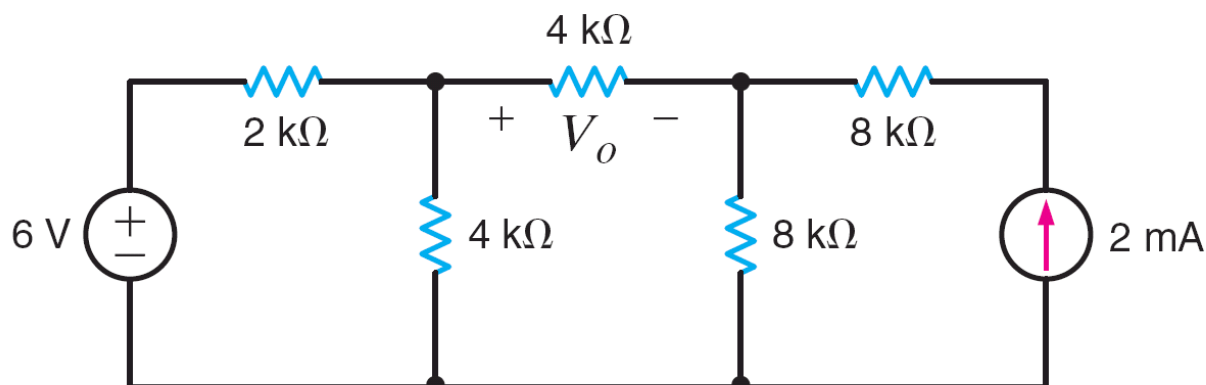

**Figure P3.9**

SOLUTION:

3.9 Find  $V_o$  by nodal.

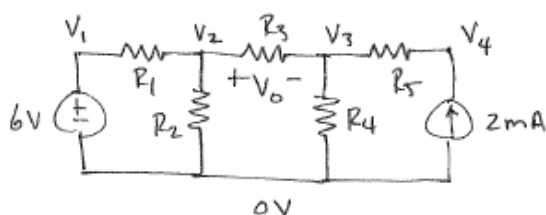

$$R_1 = 2\text{ k}\Omega \quad R_2 = R_3 = 4\text{ k}\Omega$$

$$R_4 = R_5 = 8\text{ k}\Omega$$

$$V_1 = 6\text{ V}$$

$$\text{@ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$


$$\text{@ } V_3: \frac{V_3 - V_2}{R_3} + \frac{V_3}{R_4} + \frac{V_3 - V_4}{R_5} = 0$$

$$\text{@ } V_4: \frac{V_4 - V_3}{R_5} = 2 \times 10^{-3}$$

$$\text{and } V_o = V_2 - V_3$$

$$V_2 = 5.2\text{ V}, \quad V_3 = 8.8\text{ V} \quad \boxed{V_o = -3.6\text{ V}}$$


**3.10** Find  $I_o$  in the circuit in Fig. P3.10 using nodal analysis.

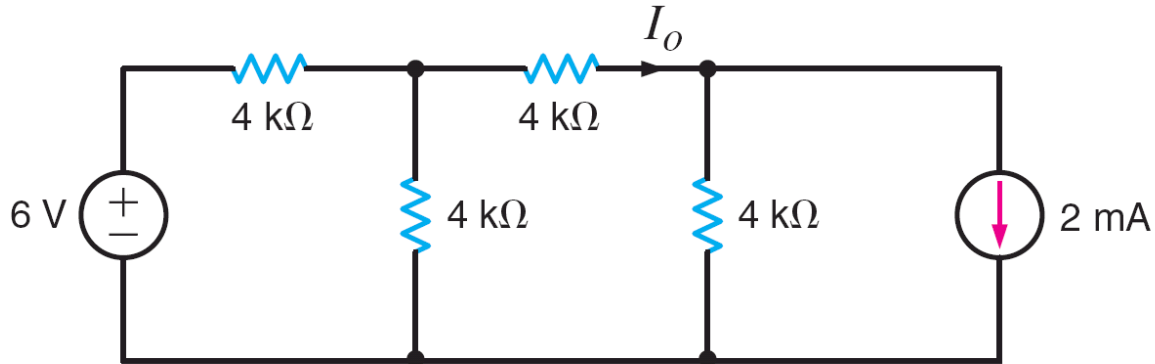

**Figure P3.10**

**SOLUTION:**

3.10 Find  $I_o$  by nodal.

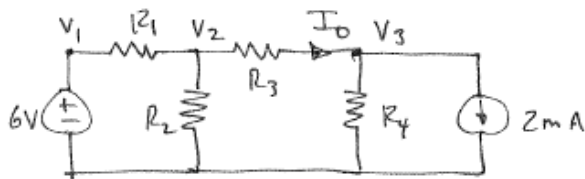

all  $R = 4\text{ k}\Omega$

$$V_1 = 6\text{ V}$$

$$\textcircled{a} \text{ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$


$$\textcircled{b} \text{ } V_3: \frac{V_3 - V_2}{R_3} + \frac{V_3}{R_4} + 2 \times 10^{-3} = 0$$

$$\text{and } I_o = \frac{V_2 - V_3}{R_3}$$

$$V_2 = 0.8\text{ V} \quad V_3 = -3.6\text{ V}$$

$$\boxed{I_o = 1.1\text{ mA}}$$


**3.11** Use nodal analysis to find  $V_o$  in the network in Fig. P3.11. Then solve the problem using MATLAB and compare your answers.

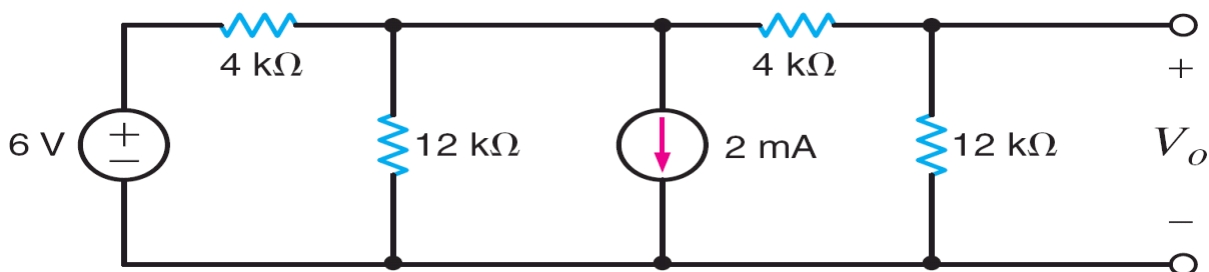

**Figure P3.11**

SOLUTION:

3.11 Find  $V_o$  by nodal. & MATLAB

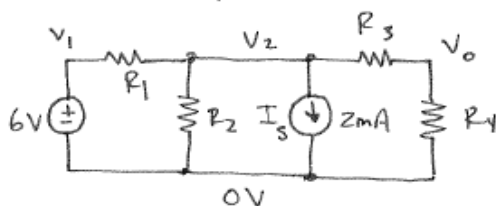

$$R_1 = 4k\Omega \quad R_2 = 12k\Omega \quad R_3 = 4k\Omega$$

$$R_4 = 12k\Omega$$

$$V_1 = 6V$$

$$\textcircled{V_2}: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_o}{R_3} + I_s = 0$$

$$\textcircled{V_o}: \frac{V_o - V_2}{R_3} + \frac{V_o}{R_4} = 0$$

$$\boxed{V_o = -0.95V}$$

In matrix form:

$$\begin{bmatrix} 1 & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ 0 & -\frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_o \end{bmatrix} = \begin{bmatrix} 6 \\ -2 \times 10^{-3} \\ 0 \end{bmatrix}$$

Continued on the next page.

3\_11.txt

MATLAB WORK

Factor out 1/12000 from the conductance matrix

EDU&gt; g=[12000,0,0;-3,7,-3;0,-3,4]

g =

12000	0	0
-3	7	-3
0	-3	4

EDU&gt; i=[6;-0.002;0]

i =


6.0000
-0.0020
0

EDU&gt; v=12000\*inv(g)\*i

v =


6.0000
-1.2632
-0.9474

**3.12** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.12.

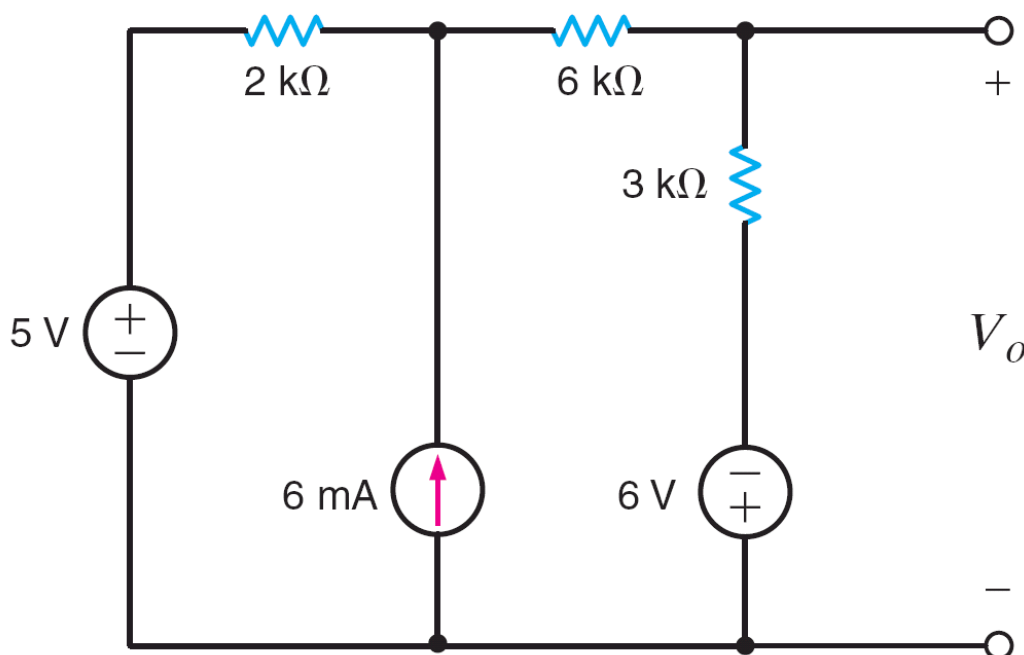

**Figure P3.12**

SOLUTION:

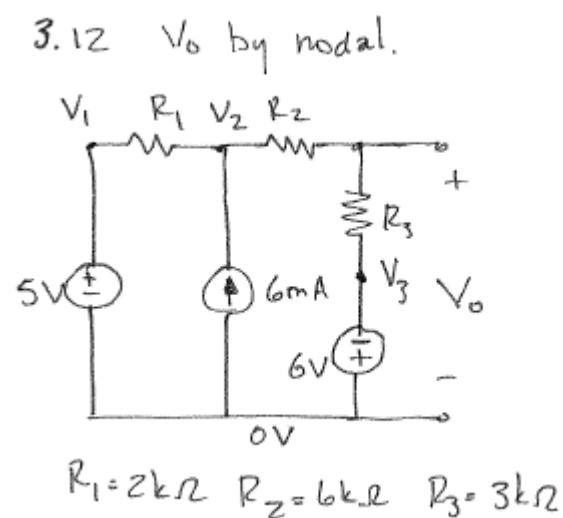

$$V_1 = 5V \quad \& \quad V_3 = -6V$$


$$@ V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_o}{R_2} - 6 \times 10^{-3} = 0$$

$$@ V_o: \frac{V_o - V_2}{R_2} + \frac{V_o - V_3}{R_3} = 0$$

$$\boxed{V_o = 0.27V}$$




**3.13** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.13.

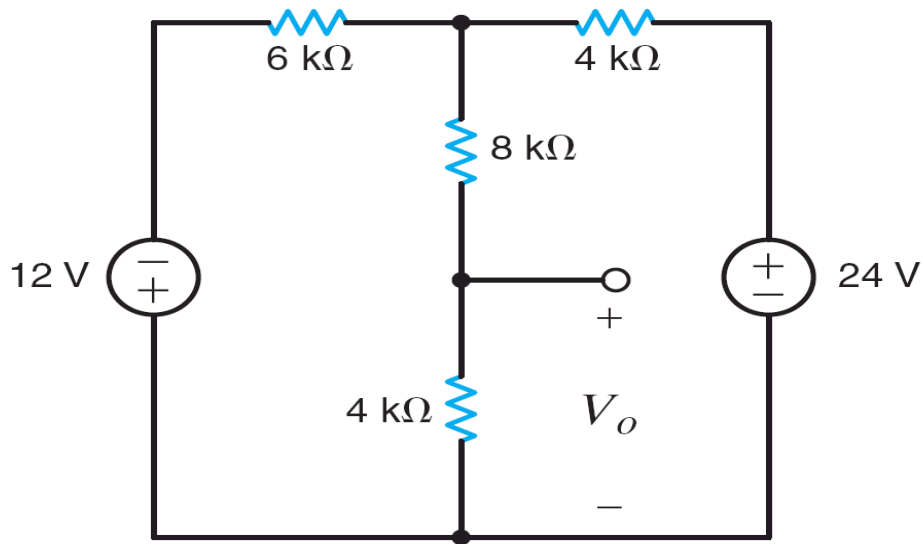

**Figure P3.13**

SOLUTION:

3.13 Find  $V_o$  by nodal.

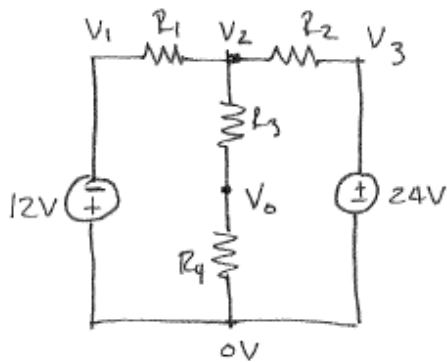

$$R_1 = 6 \text{ k}\Omega \quad R_2 = R_4 = 4 \text{ k}\Omega$$

$$R_3 = 8 \text{ k}\Omega$$

$$V_1 = -12 \text{ V} \quad V_3 = 24 \text{ V}$$


$$\text{@ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + \frac{V_2 - V_o}{R_3} = 0$$

$$\text{@ } V_o: \quad \frac{V_o - V_2}{R_3} + \frac{V_o}{R_4} = 0$$

$$V_o = 2.67 \text{ V}$$

**3.14** Find  $I_o$  in the network in Fig. P3.14.


**CS**

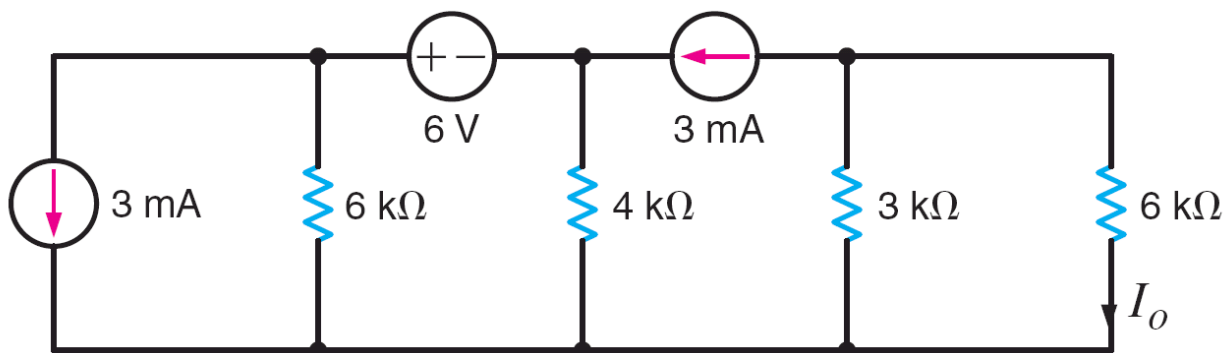

**Figure P3.14**

**SOLUTION:**

3.14 Find  $I_o$ .

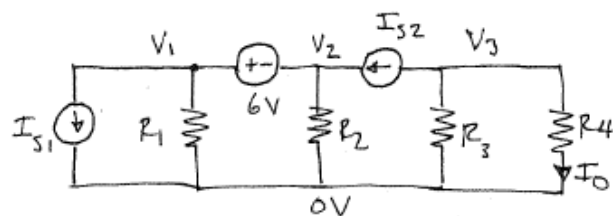

$$R_1 = R_4 = 6 \text{ k}\Omega \quad R_2 = 4 \text{ k}\Omega \quad R_3 = 3 \text{ k}\Omega$$

$$I_{s1} = 3 \text{ mA} \quad I_{s2} = 3 \text{ mA}$$

$$V_1 - V_2 = 6 \text{ V}$$


$$\text{@ } V_3: I_{s2} + \frac{V_3}{R_3} + \frac{V_3}{R_4} = 0$$

$$\text{@ ref: } I_{s1} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_3}{R_4} = 0$$

$$\text{also, } I_o = V_3 / R_4$$

$$I_o = -1 \text{ mA}$$


**3.15** Find  $I_1$  in the network in Fig. P3.15. CS

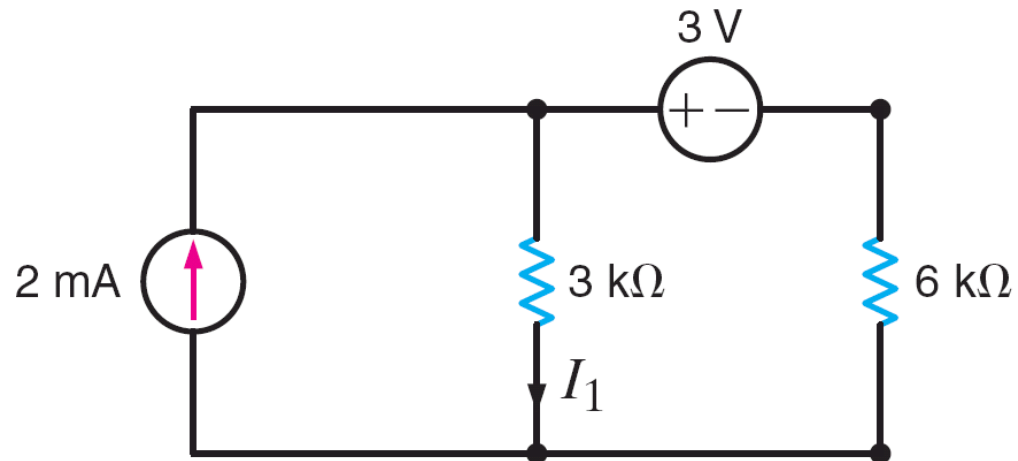

**Figure P3.15**

SOLUTION:

3.15 Find  $I_1$ .

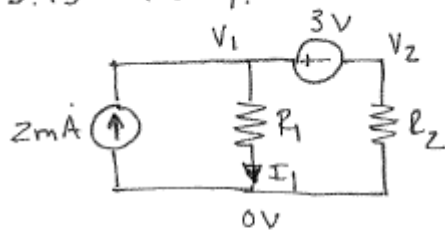

$$R_1 = 3 \text{ k}\Omega \quad R_2 = 6 \text{ k}\Omega$$


$$V_1 - V_2 = 3 \text{ V}$$

$$\text{@ ref: } \frac{V_1}{R_1} + \frac{V_2}{R_2} - 2 \times 10^{-3} = 0$$

$$\text{and, } I_1 = V_1 / R_1$$

$$\boxed{I_1 = 1.67 \text{ mA}}$$


**3.16** Find  $I_o$  in the network in Fig. P3.16.

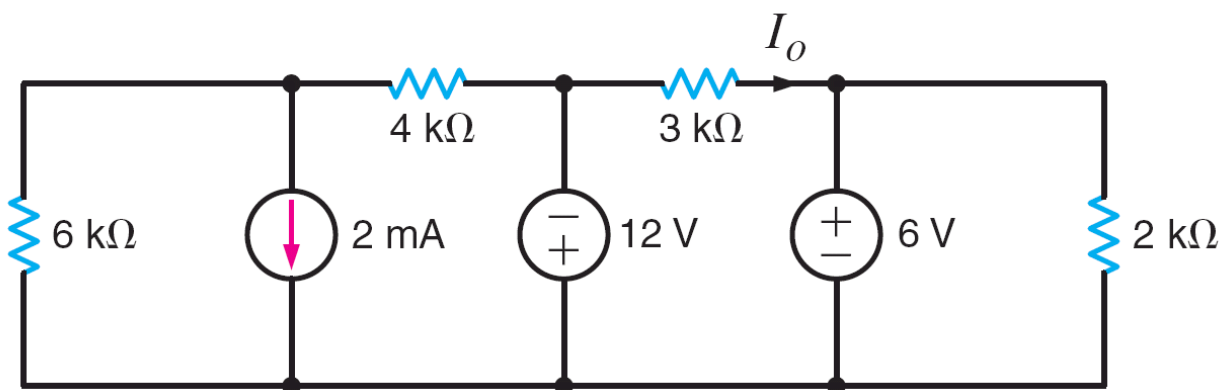

**Figure P3.16**

SOLUTION:

3.16 Find  $I_o$ .

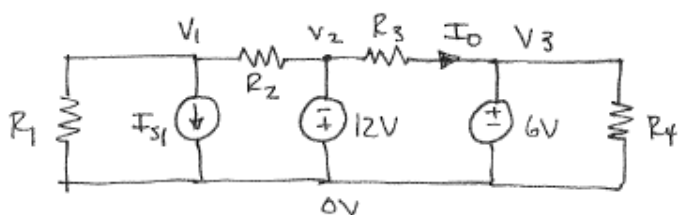

$$R_1 = 6\text{ k}\Omega \quad R_2 = 4\text{ k}\Omega \quad R_3 = 3\text{ k}\Omega \quad R_4 = 2\text{ k}\Omega$$

$$I_{s1} = 2\text{ mA}$$


$$V_2 = -12\text{ V} \quad V_3 = 6\text{ V}$$

$$\text{@ } V_1: \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + I_{s1} = 0$$

$$\text{and } I_o = \frac{V_2 - V_3}{R_3}$$

$$I_o = -6\text{ mA}$$


**3.17** Use nodal analysis to find  $V_x$  and  $V_y$  in the circuit in Fig. P3.17.

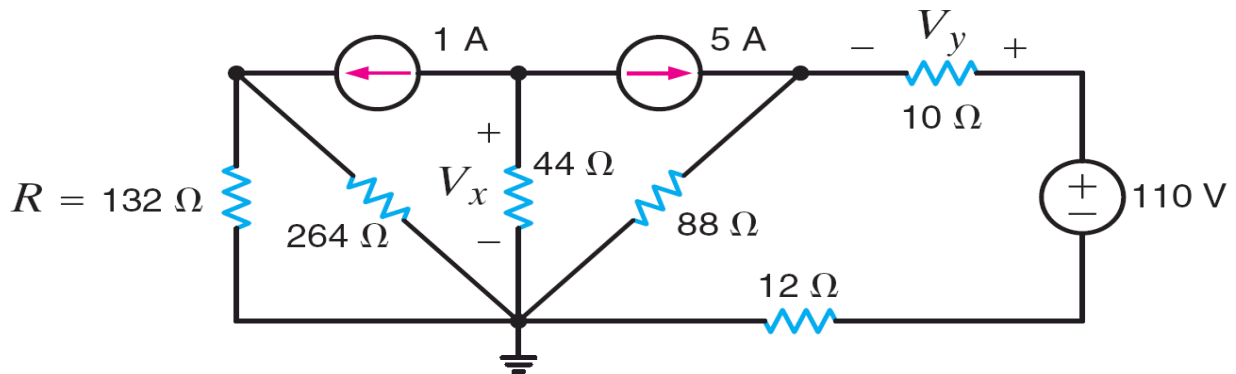

**Figure P3.17**

**SOLUTION:**

3.17 Find  $V_x$  and  $V_y$  by nodal.

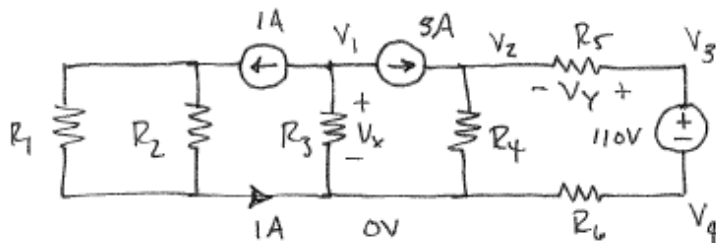

$$R_1 = 132\Omega \quad R_2 = 264\Omega$$

$$R_3 = 44\Omega \quad R_4 = 88\Omega$$

$$R_5 = 10\Omega \quad R_6 = 12\Omega$$

$$\text{@ } V_1: \quad 1 + 5 + \frac{V_x}{R_3} = 0 \Rightarrow \boxed{V_x = -264\text{V}}$$

$$\text{@ } V_2: \quad 5 = \frac{V_2}{R_4} + \frac{V_2 - V_3}{R_5}$$

$$\text{@ ref:} \quad 1 + \frac{V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_4}{R_6}$$

$$V_3 - V_4 = 110\text{V}$$

$$V_y = V_3 - V_2$$


$$\boxed{V_y = 30\text{V}}$$

**3.18** For the network in Fig P3.17, explain why the resistor  $R$  plays no role in determining  $V_x$  and  $V_y$ .

SOLUTION:

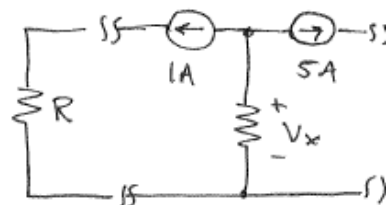3.18 As shown in the simple circuit here the 1-A current source fixes the current in its branch, independent of the value of  $R$ .

Since  $V_x$  &  $V_y$  depend only on the branch's current, the value of  $R$  does not impact  $V_x$  or  $V_y$ .



### 3.19 Use nodal analysis to find $V_o$ in the network in Fig P3.19.


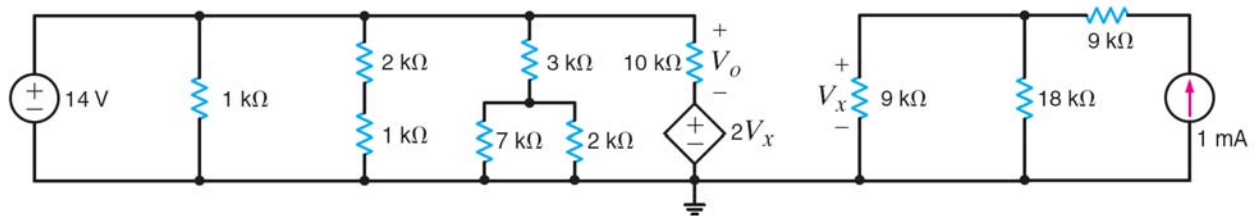


Figure P3.19

SOLUTION:

3.19 Find  $V_o$  by nodal

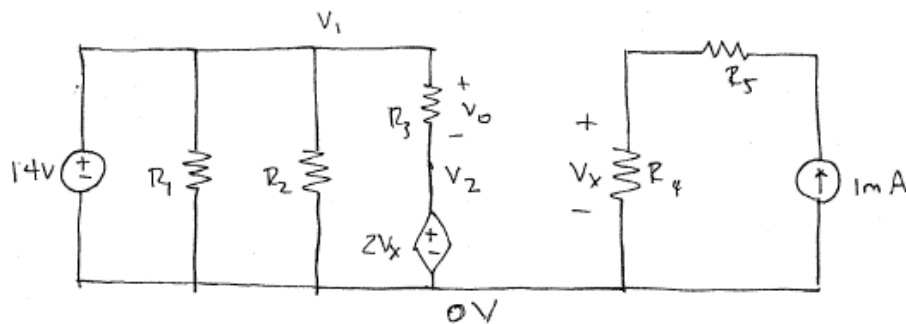

$$R_1 = 1000 \parallel (2000 + 1000) = 750\Omega \quad R_3 = 10k\Omega \quad R_5 = 9k\Omega$$


$$R_4 = 9000 \parallel 18000 = 6k\Omega \quad R_2 = 3000 + (7000 \parallel 2000) = 4.55k\Omega$$

$$V_1 = 14V \quad V_2 = 2V_x \quad V_x = 1 \times 10^{-3} (R_4) = 6V$$

$$V_o = V_1 - V_2$$

$$V_o = 2V$$


**3.20** Use nodal analysis to find  $V_A$  and  $V_B$  in the network in Fig. P3.20. Simplify the analysis by making an insightful choice for the reference node.

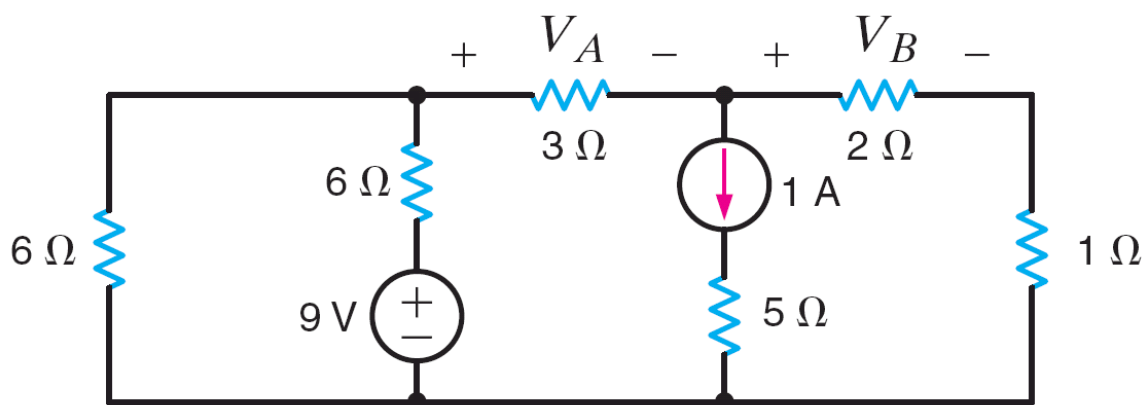

**Figure P3.20**

SOLUTION:

3.20 Find  $V_A$  &  $V_B$  by nodal

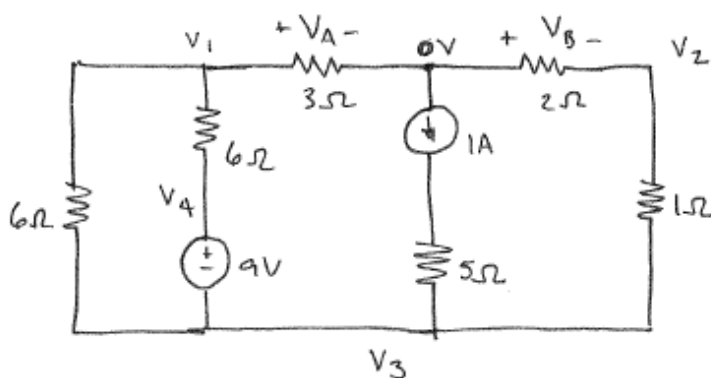

$$V_A = V_1$$

$$V_B = -V_2$$

$$V_A = 2.5 \text{ V}$$

$$V_B = -0.33 \text{ V}$$

$$V_4 - V_3 = 9$$


$$\frac{V_1 - V_4}{6} + \frac{V_1}{3} + \frac{V_1 - V_3}{6} = 0$$

$$\frac{V_1}{3} + \frac{V_2}{2} = 1$$

$$\frac{V_2}{2} + \frac{V_2 - V_3}{1} = 0$$




**3.21** Find  $I_o$  in the circuit in Fig. P3.21.

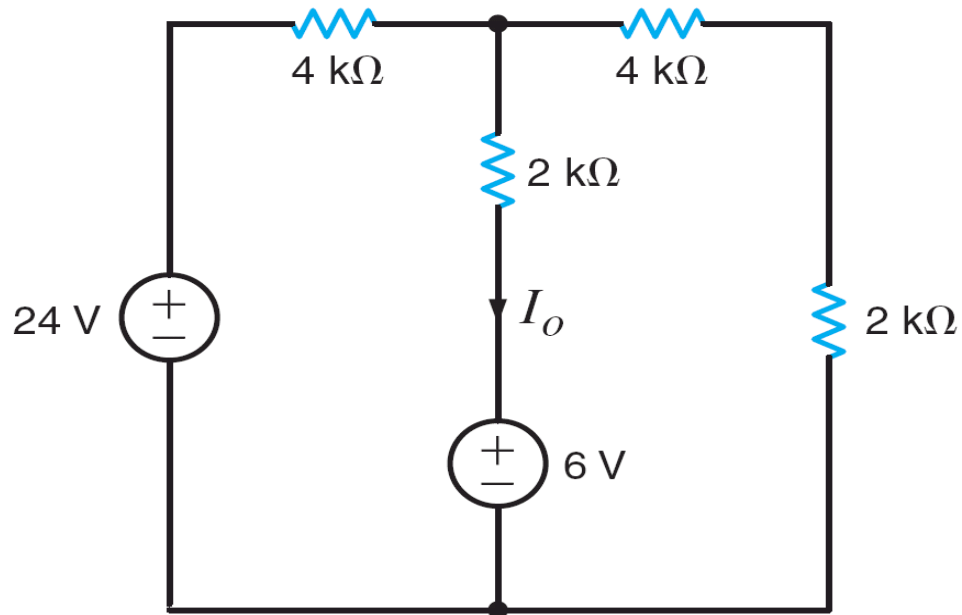

**Figure P3.21**

SOLUTION:

3.21 Find  $I_o$ .

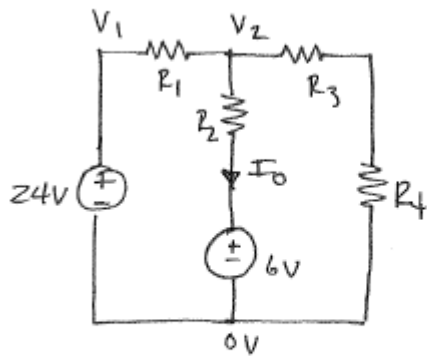

$$V_1 = 24V$$

$$\frac{V_2 - V_1}{R_1} + \frac{V_2 - 6}{R_2} + \frac{V_2}{R_3 + R_4} = 0$$


$$I_o = \frac{V_2 - 6}{R_2}$$

$$\boxed{I_o = 1.91 \text{ mA}}$$

$$R_1 = R_3 = 4 \text{ k}\Omega$$

$$R_2 = R_4 = 2 \text{ k}\Omega$$


**3.22** Use nodal analysis to find  $I_o$  and  $I_s$  in the circuit in Fig. P3.22.

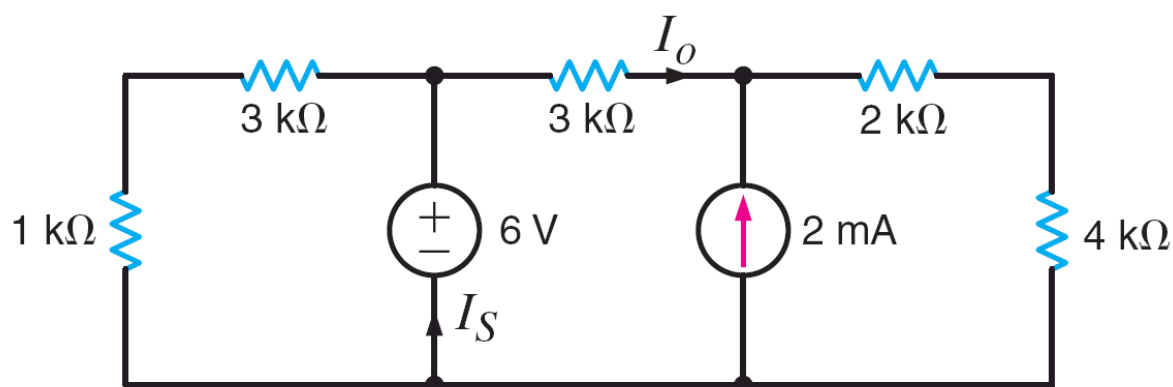

**Figure P3.22**

SOLUTION:

3.22 Find  $I_o$  and  $I_s$  by nodal.

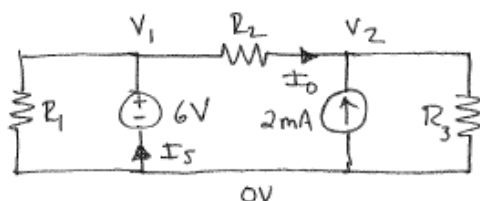

$$I_o = (V_1 - V_2) / R_2$$

$$I_o = -0.67 \text{ mA}$$

$$R_1 = 1000 + 3000 = 4000 \Omega$$


$$R_3 = 2000 + 4000 = 6 \text{ k}\Omega$$

$$V_1 = 6 \text{ V}$$

$$\frac{V_1 - V_2}{R_2} + 2 \times 10^{-3} = V_2 / R_3$$

$$I_s = \frac{V_1}{R_1} + I_o \Rightarrow I_s = 0.83 \text{ mA}$$


**3.23** Use nodal analysis to find  $V_o$  in the network in Fig. P3.23.

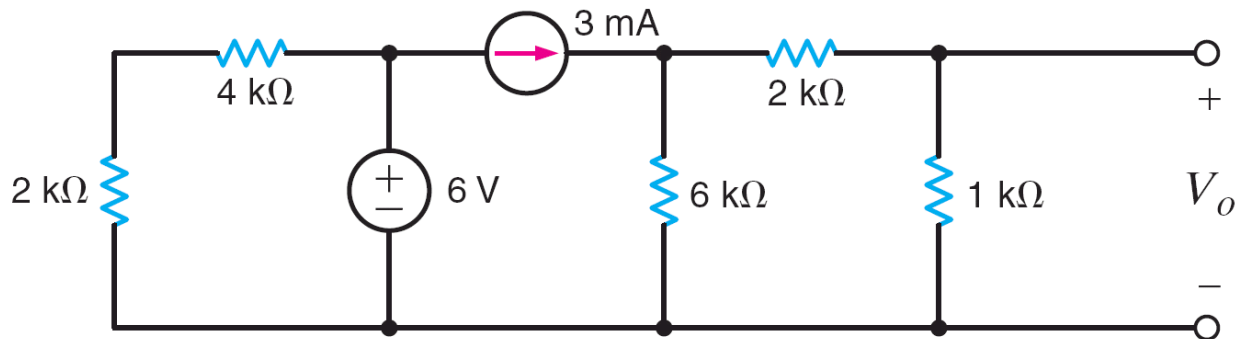

**Figure P3.23**

**SOLUTION:**

3.23 Find  $V_o$  by nodal.

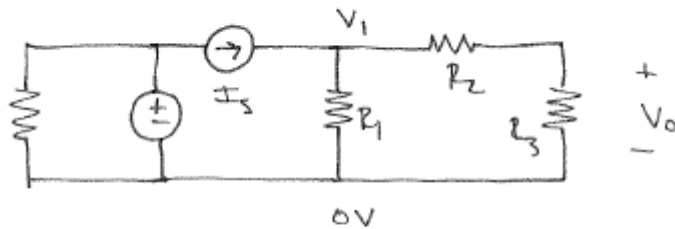

$$R_1 = 6 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega \quad R_3 = 1 \text{ k}\Omega$$


$$I_s = 3 \text{ mA}$$

$$I_s = \frac{V_1}{R_1} + \frac{V_1}{R_2 + R_3}$$

$$V_o = V_1 \left( \frac{R_3}{R_2 + R_3} \right)$$

$$\boxed{V_o = 2 \text{ V}}$$


**3.24** Use nodal analysis to find  $I_o$  in the circuit in Fig. P3.24.

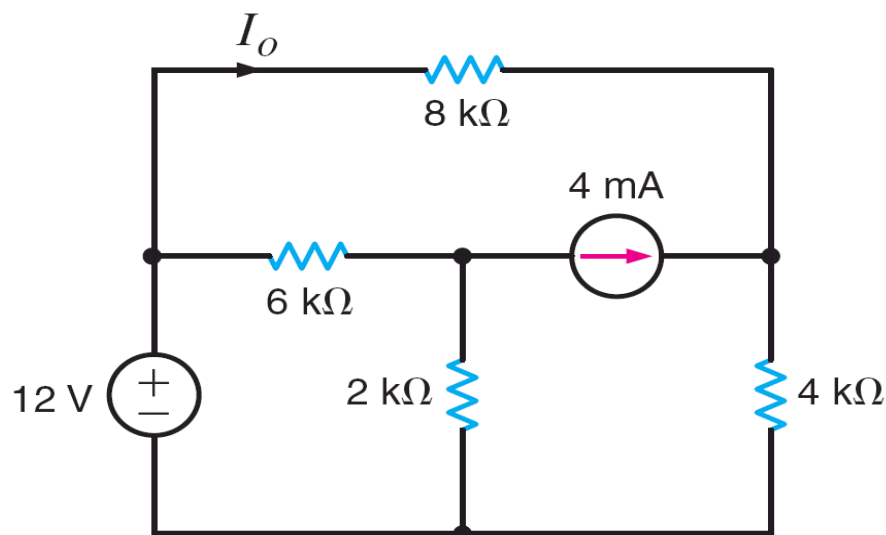

**Figure P3.24**

SOLUTION:

3.24 Find  $I_o$  by nodal.

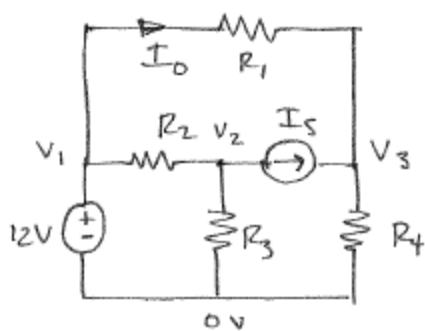

$$R_1 = 8\text{ k}\Omega \quad R_2 = 6\text{ k}\Omega$$

$$R_3 = 2\text{ k}\Omega \quad R_4 = 4\text{ k}\Omega$$

$$I_s = 4\text{ mA}$$

$$V_1 = 12\text{ V}$$


$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + I_s = 0$$

$$\frac{V_3 - V_1}{R_1} + \frac{V_3}{R_4} = I_s$$

$$\text{and, } I_o = \frac{V_1 - V_3}{R_1}$$

$$I_o = -0.33\text{ mA}$$


**3.25** Find  $I_o$  in the network in Fig. P3.25 using nodal analysis.

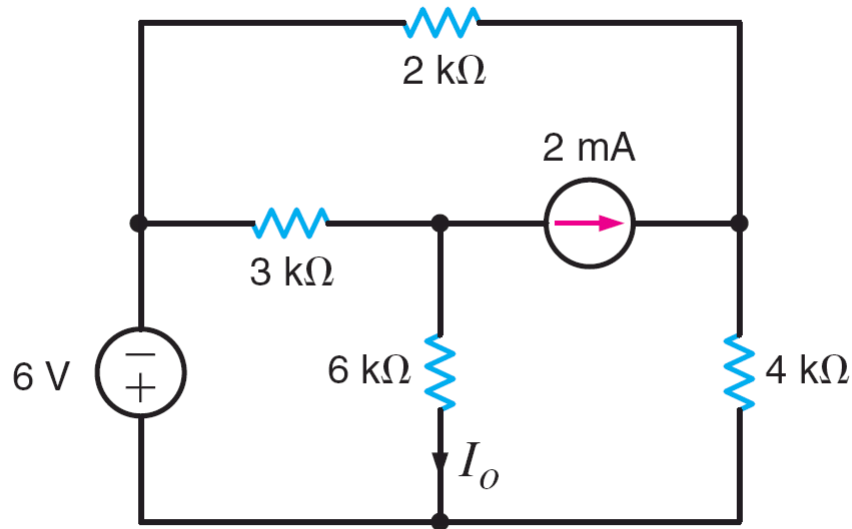

**Figure P3.25**

**SOLUTION:**

3.25 Find  $I_o$  by nodal.

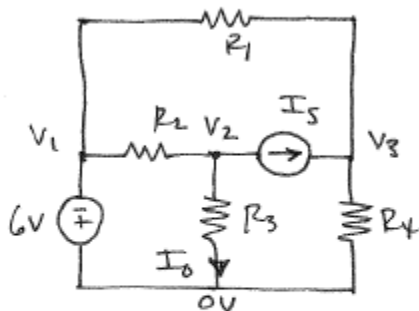

$$R_1 = 2\text{ k}\Omega \quad R_2 = 3\text{ k}\Omega$$

$$R_3 = 6\text{ k}\Omega \quad R_4 = 4\text{ k}\Omega$$

$$I_5 = 2\text{ mA}$$


$$V_1 = -6\text{ V}$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + I_5 = 0$$

$$I_o = V_2 / R_3$$

$$\boxed{I_o = 0\text{ A}}$$


**3.26** Use nodal analysis to find  $I_o$  in the network in Fig. P3.26.

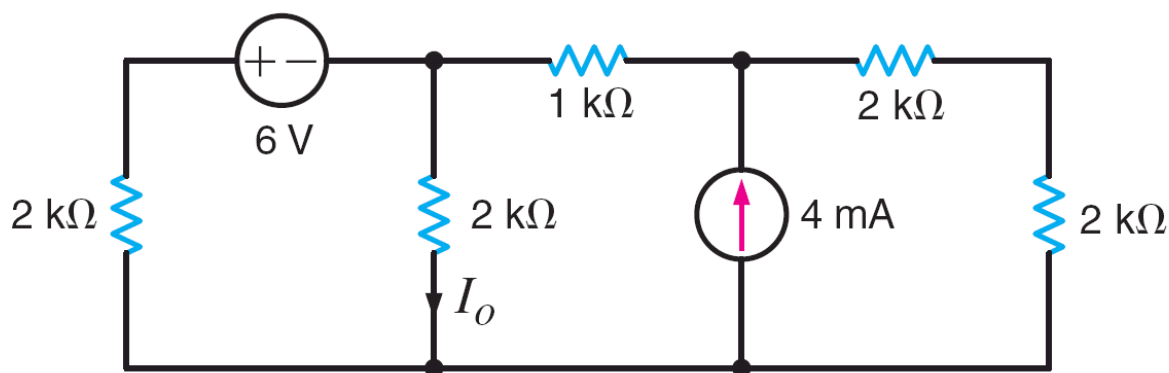

**Figure P3.26**

**SOLUTION:**

3.26 Find  $I_o$  by nodal.

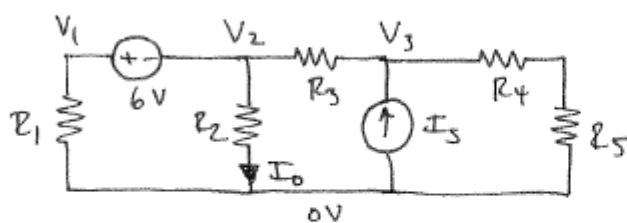

$$R_1 = R_2 = R_4 = R_5 = 2\text{ k}\Omega$$

$$R_3 = 1\text{ k}\Omega \quad I_s = 4\text{ mA}$$

$$V_1 - V_2 = 6\text{ V}$$


$$\text{@ } V_3: \frac{V_3 - V_2}{R_3} + \frac{V_3}{R_4 + R_5} = I_s$$

$$\text{@ ref: } \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_4 + R_5} = I_s$$

$$\text{and } I_o = V_2 / R_2$$

$$\boxed{I_o = 83.3\text{ }\mu\text{A}}$$


**3.27** Use nodal analysis to find  $V_o$  in the network in Fig. P3.27. Then solve this problem using MATLAB and compare your answers. **CS**

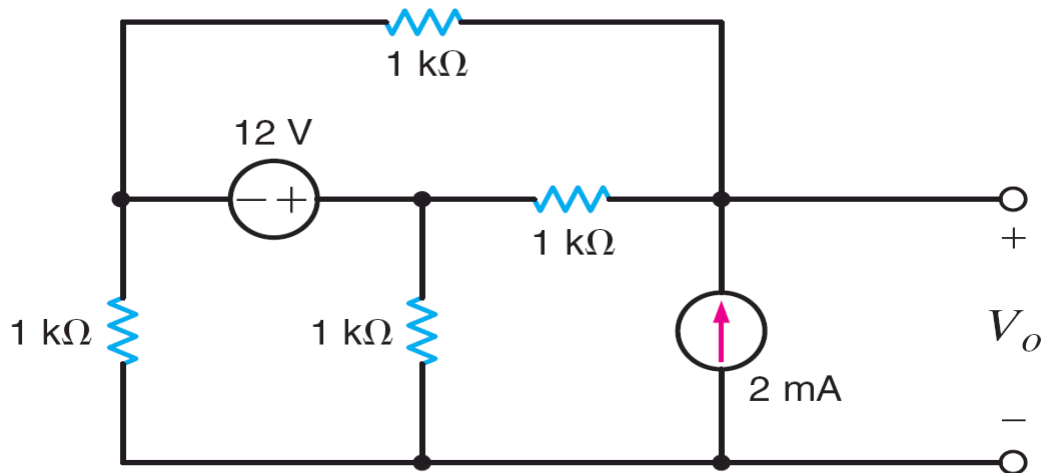

**Figure P3.27**

**SOLUTION:**

3.27 Find  $V_o$  by model and MATLAB.

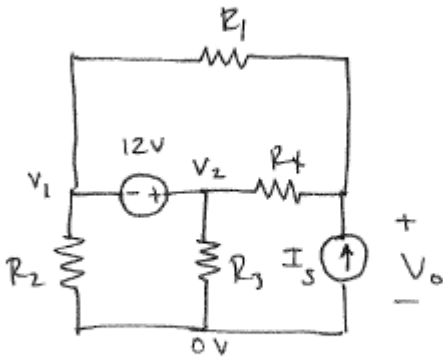

$$R_1 = R_2 = R_3 = R_4 = 1\text{ k}\Omega$$

$$I_s = 2\text{ mA}$$

$$V_2 - V_1 = 12\text{ V}$$


$$\text{at } V_o: \frac{V_o - V_2}{R_4} + \frac{V_o - V_1}{R_1} = I_s$$

$$\text{e ref: } \frac{V_1}{R_2} + \frac{V_2}{R_3} = I_s$$

$$\boxed{V_o = 2\text{ V}}$$

**3.28** Find  $V_o$  in the circuit in Fig. P3.28 using nodal analysis.


**PSV**

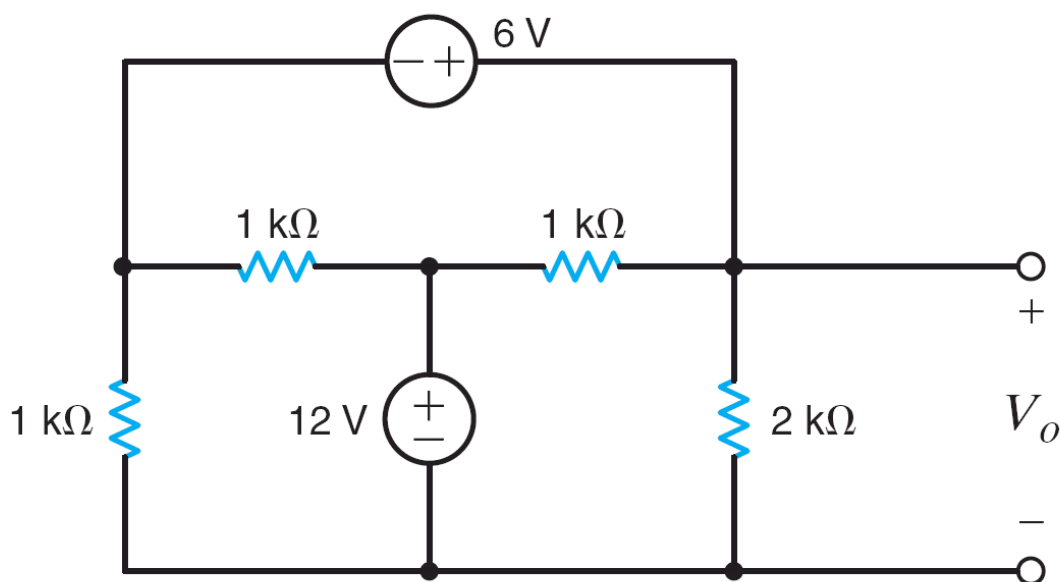

**Figure P3.28**

**SOLUTION:**

3.28 Find  $V_o$  by nodal.

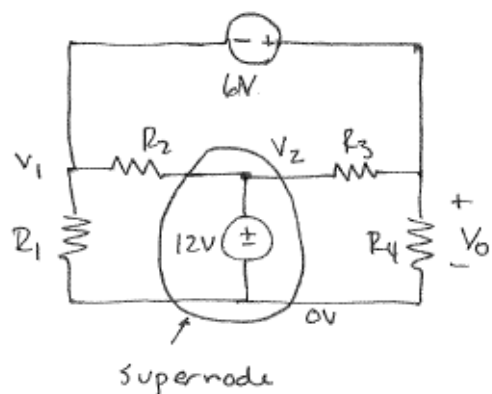

$$R_1 = R_2 = R_3 = 1\text{k}\Omega \quad R_4 = 2\text{k}\Omega$$

$$V_o - V_1 = 6\text{V} \quad V_2 = 12\text{V}$$

at supernode,


$$\frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1} + \frac{V_o - V_2}{R_3} + \frac{V_o}{R_4} = 0$$

$$V_o = 10.3\text{V}$$



**3.29** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.29.


**CS**

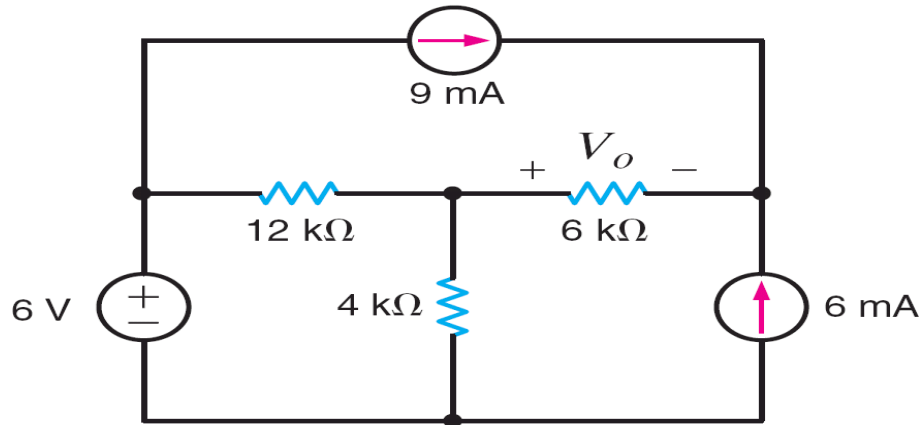

**Figure P3.29**

SOLUTION:

3.29 Find  $V_o$  by nodal.

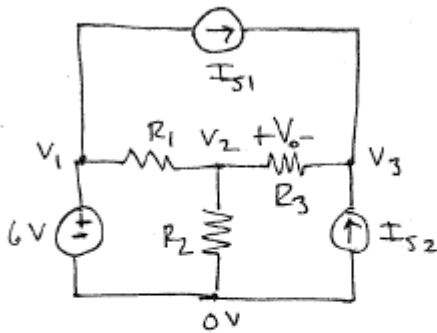

$$R_1 = 12 \text{ k}\Omega \quad R_2 = 4 \text{ k}\Omega$$

$$R_3 = 6 \text{ k}\Omega \quad I_{S1} = 9 \text{ mA}$$

$$I_{S2} = 6 \text{ mA}$$

$$V_1 = 6 \text{ V}$$


$$\text{@ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$\text{@ } V_3: \quad \frac{V_3 - V_2}{R_3} = I_{S1} + I_{S2}$$

$$\text{and} \quad V_o = V_2 - V_3$$

$$\boxed{V_o = -90 \text{ V}}$$


**3.30** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.30.

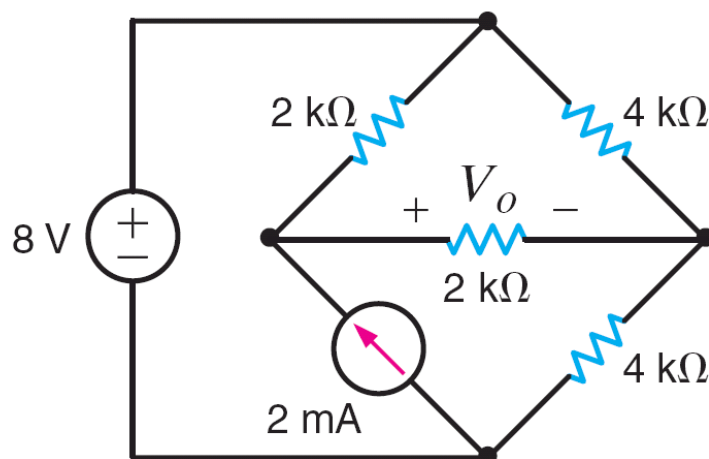

**Figure P3.30**

**SOLUTION:**

3.30 Find  $V_o$  by nodal

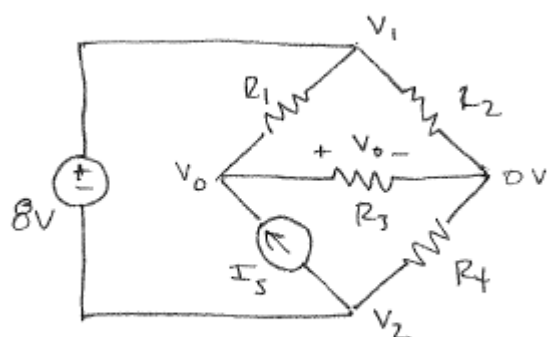

$$R_1 = 2k\Omega \quad R_2 = 4k\Omega \quad R_3 = 2k\Omega$$

$$R_4 = 4k\Omega \quad I_5 = 2mA$$


$$V_1 - V_2 = 8V$$

$$@ V_0: \frac{V_0 - V_1}{R_1} + \frac{V_0}{R_3} = I_5$$

$$@ \text{ref: } \frac{V_1}{R_2} + \frac{V_0}{R_3} + \frac{V_2}{R_4} = 0$$

$$\boxed{V_o = 2.67V}$$


**3.31** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.31.

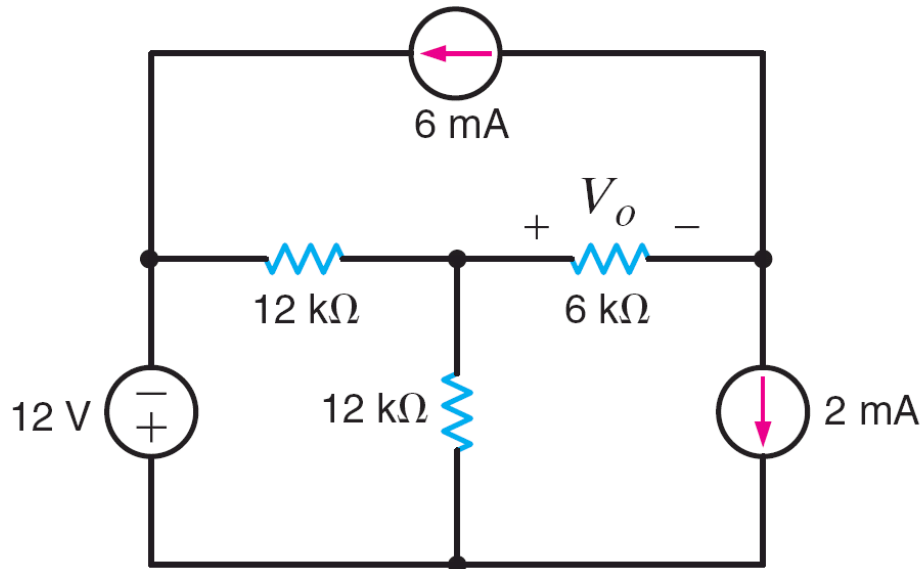

**Figure P3.31**

**SOLUTION:**

3.31 Find  $V_o$  by nodal.

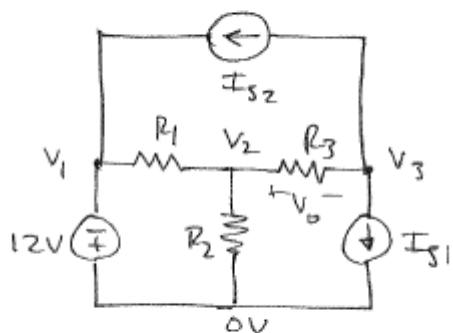

$$R_1 = R_2 = 12\text{ k}\Omega \quad R_3 = 6\text{ k}\Omega$$

$$I_{s1} = 2\text{ mA} \quad I_{s2} = 6\text{ mA}$$

$$V_1 = -12\text{ V}$$

$$\text{@ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$


$$\text{@ } V_3: \frac{V_3 - V_2}{R_3} + I_{s1} + I_{s2} = 0$$

$$V_o = V_2 - V_3$$

$$V_o = 48\text{ V}$$

**3.32** Find  $V_o$  in the network in Fig. P3.32 using nodal analysis.


**CS**

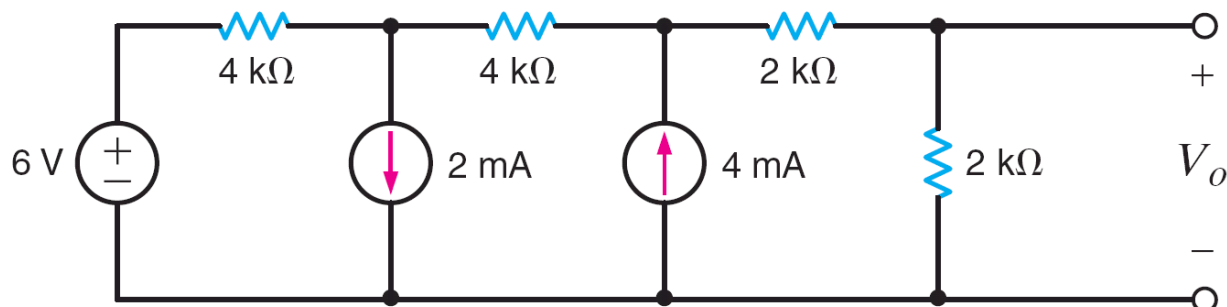

**Figure P3.32**

**SOLUTION:**

3.32 Find  $V_o$  by nodal.

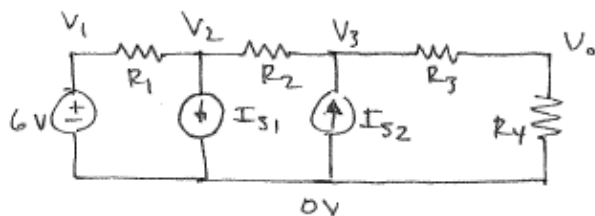

$$R_1 = R_2 = 4 \text{ k}\Omega \quad R_3 = R_4 = 2 \text{ k}\Omega$$

$$I_{s1} = 2 \text{ mA} \quad I_{s2} = 4 \text{ mA}$$

$$V_1 = 6 \text{ V}$$


$$\text{@ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + I_{s1} = 0$$

$$\text{@ } V_3: \frac{V_3 - V_2}{R_2} + \frac{V_3 - V_o}{R_3} = I_{s2}$$

$$\text{@ } V_o: \frac{V_o - V_3}{R_3} + \frac{V_o}{R_4} = 0$$

$$\boxed{V_o = 5 \text{ V}}$$


**3.33** Use nodal analysis to find  $V_o$  in the network in Fig. P3.33.

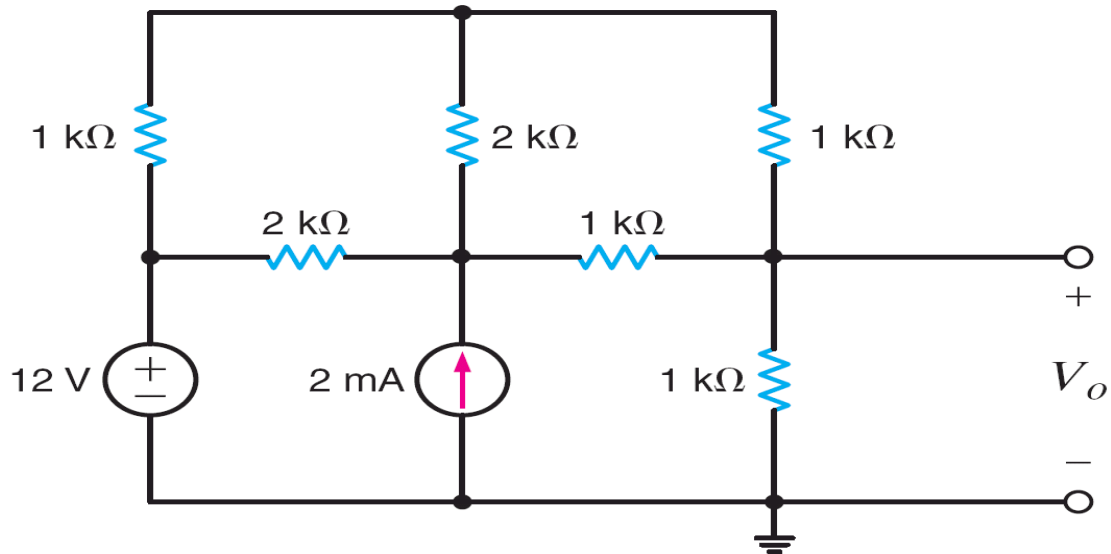

**Figure P3.33**

SOLUTION:

3.33 Find  $V_o$  by nodal.

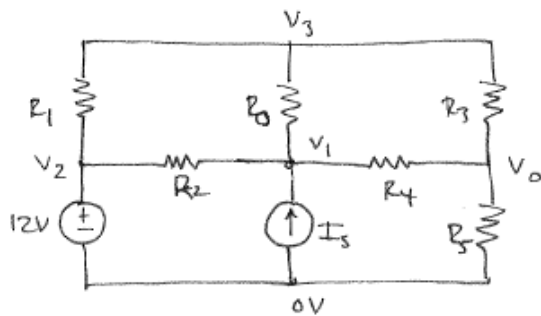

$$R_1 = R_3 = R_4 = R_5 = 1\text{ k}\Omega \quad R_2 = R_0 = 2\text{ k}\Omega$$

$$I_5 = 2\text{ mA}$$

$$V_2 = 12\text{ V}$$


$$\text{@ } V_3: \frac{V_3 - V_2}{R_1} + \frac{V_3 - V_1}{R_0} + \frac{V_3 - V_o}{R_3} = 0$$

$$\text{@ } V_1: I_5 = \frac{V_1 - V_3}{R_0} + \frac{V_1 - V_o}{R_4} + \frac{V_1 - V_2}{R_2}$$

$$\text{@ } V_o: \frac{V_o - V_1}{R_4} + \frac{V_o}{R_5} + \frac{V_o - V_3}{R_3} = 0$$

$$\boxed{V_o = 6.17\text{ V}}$$


**3.34** Find  $V_o$  in the circuit in Fig. P3.34 using nodal analysis.

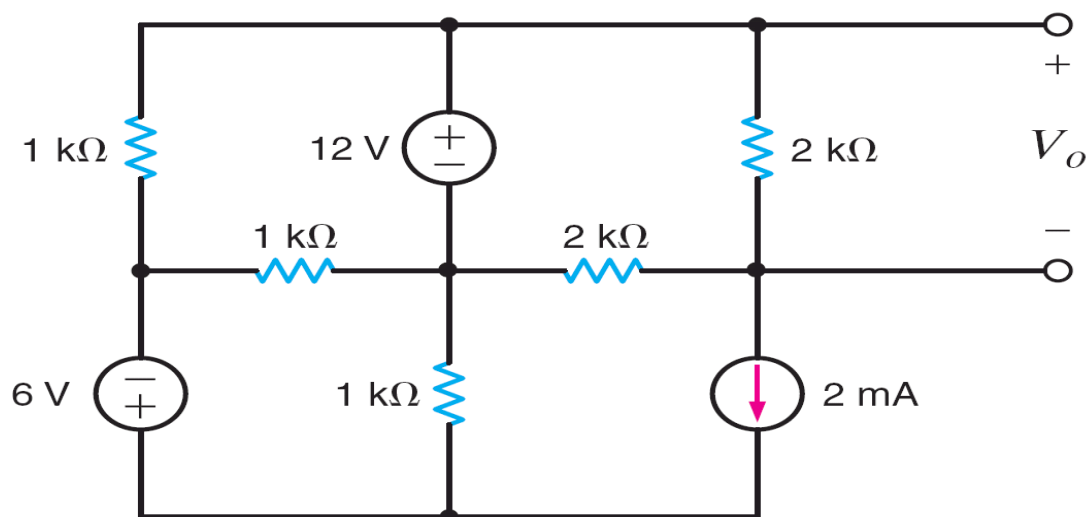

**Figure P3.34**

**SOLUTION:**

3.34 Find  $V_o$  by nodal.

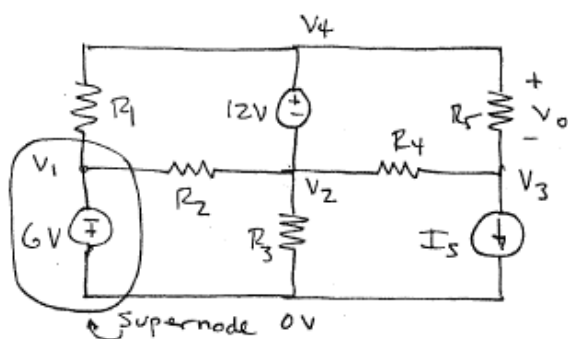

$$R_1 = R_2 = R_3 = 1\text{ k}\Omega \quad I_S = 2\text{ mA}$$

$$R_4 = R_5 = 2\text{ k}\Omega$$

$$V_1 = -6\text{ V} \quad V_4 - V_2 = 12\text{ V}$$

$$\text{@ } V_3: \frac{V_3 - V_2}{R_4} + \frac{V_3 - V_4}{R_5} + I_S = 0$$


@ supernode:

$$\frac{V_4 - V_1}{R_1} + \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + I_S = 0$$

$$V_o = V_4 - V_3$$

$$\boxed{V_o = 8\text{ V}}$$


**3.35** Use nodal analysis to find  $V_o$  in the network in Fig. P3.35.

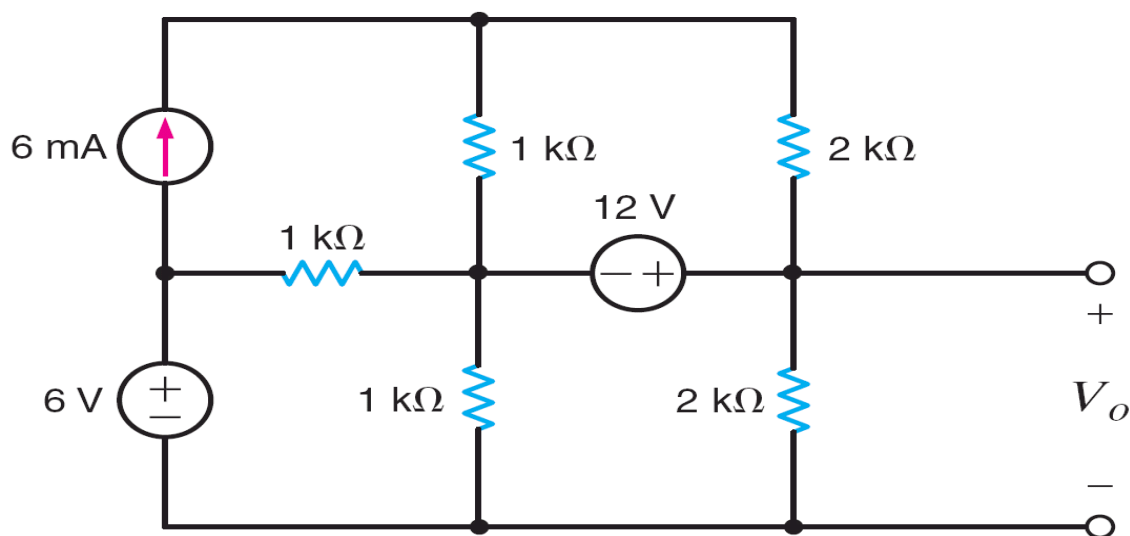

**Figure P3.35**

SOLUTION:

3.35 Use nodal to find  $V_o$

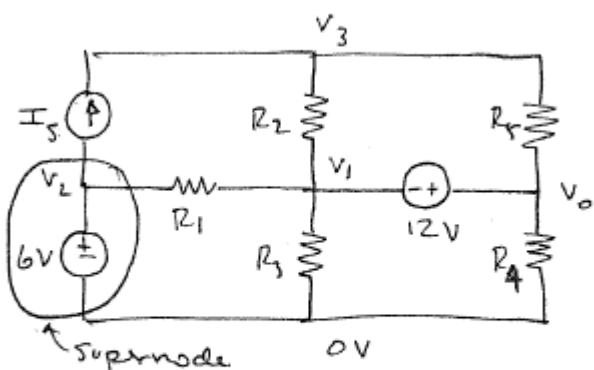

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega \quad I_S = 6 \text{ mA}$$

$$R_4 = R_5 = 2 \text{ k}\Omega$$

$$V_2 = 6 \text{ V} \quad V_o - V_1 = 12 \text{ V}$$


$$\text{@ } V_3: I_S = \frac{V_3 - V_1}{R_2} + \frac{V_3 - V_o}{R_5}$$

@ supernode:

$$\frac{V_1 - V_2}{R_1} + \frac{V_1}{R_3} + \frac{V_o}{R_4} = I_S$$

$$\boxed{V_o = 14.4 \text{ V}}$$


**3.36** Use MATLAB to find the node voltages in the network in Fig. P3.36. **CS**

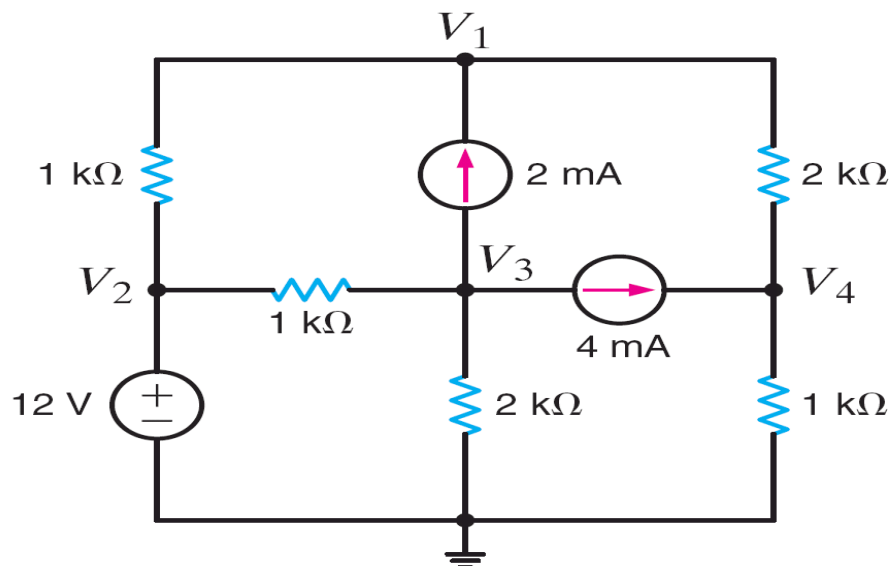

**Figure P3.36**

SOLUTION:

3.36 Use MATLAB to Find node voltages.

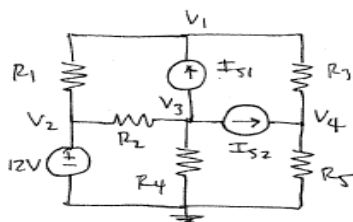

$$R_1 = R_2 = R_5 = 1\text{ k}\Omega$$

$$R_4 = R_3 = 2\text{ k}\Omega$$

$$I_{S1} = 2\text{ mA} \quad I_{S2} = 4\text{ mA}$$

$$V_2 = 12\text{ V}$$

$$\text{@ } V_1: \quad \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_4}{R_3} = I_{S1}$$

$$\text{@ } V_3: \quad \frac{V_3 - V_2}{R_2} + \frac{V_3}{R_4} + I_{S1} + I_{S2} = 0$$

$$\text{@ } V_4: \quad \frac{V_4 - V_1}{R_3} + \frac{V_4}{R_5} = I_{S2}$$

matrix form:

$$\begin{bmatrix} 0 & 1 & 0 & 0 \\ \frac{1}{R_1} + \frac{1}{R_3} & -\frac{1}{R_1} & 0 & -\frac{1}{R_3} \\ 0 & -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_4} & 0 \\ -\frac{1}{R_3} & 0 & 0 & \frac{1}{R_3} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 12 \\ I_{S1} \\ -I_{S1} - I_{S2} \\ I_{S2} \end{bmatrix}$$

MATLAB:

Continued on the next page.



MATLAB WORK

Factor 1/1000 out of the conductance matrix.

```
EDU> g=[0,1000,0,0;1.5,-1,0,-0.5;0,-1,1.5,0;-0.5,0,0,1.5]
```

g =

1.0e+003 \*

0	1.0000	0	0
0.0015	-0.0010	0	-0.0005
0	-0.0010	0.0015	0
-0.0005	0	0	0.0015

```
EDU> i=[12;0.002;-0.006;0.004]
```

i =


12.0000
0.0020
-0.0060
0.0040

```
EDU> v=1000*inv(g)*i
```

v =

11.5000
12.0000
4.0000
6.5000


**3.37** Determine  $V_o$  in the network in Fig. P3.37 using nodal analysis.

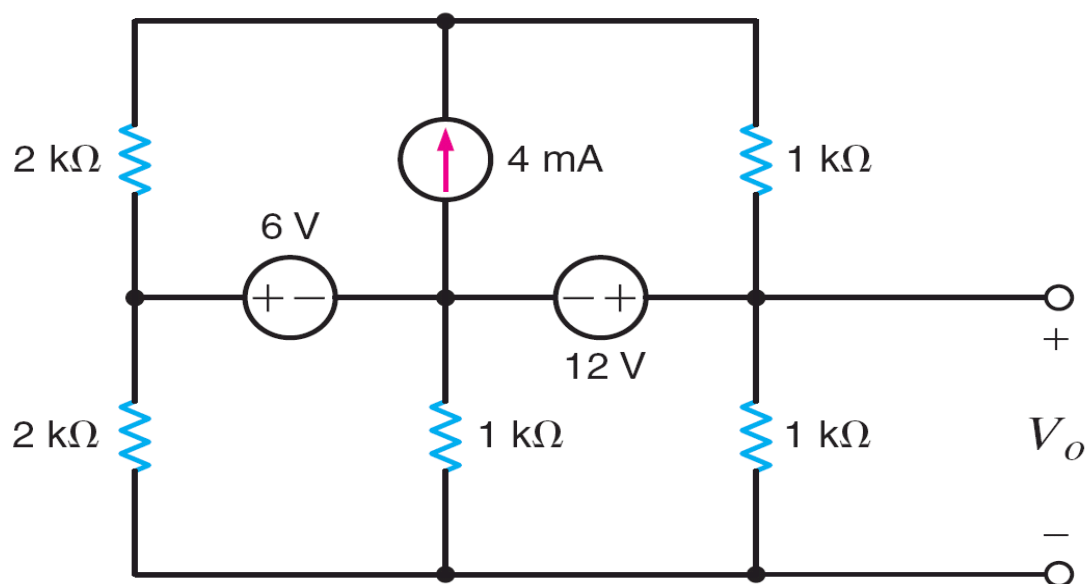

**Figure P3.37**

SOLUTION:

3.37 Find  $V_o$  by nodal.

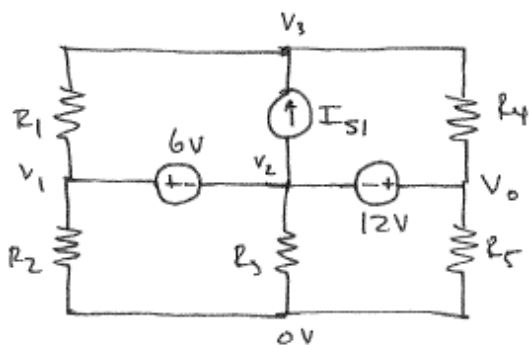

$$R_1 = R_2 = 2\text{ k}\Omega \quad I_{S1} = 4\text{ mA}$$

$$R_3 = R_4 = R_5 = 1\text{ k}\Omega$$


$$V_1 - V_2 = 6\text{ V} \quad V_o - V_2 = 12\text{ V}$$

$$\text{@ } V_3: \quad \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_o}{R_4} = I_{S1}$$

$$\text{@ ref:} \quad \frac{V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_o}{R_5} = 0$$

$$\boxed{V_o = 6\text{ V}}$$


**3.38** Find  $V_o$  in the circuit in Fig. P3.38.

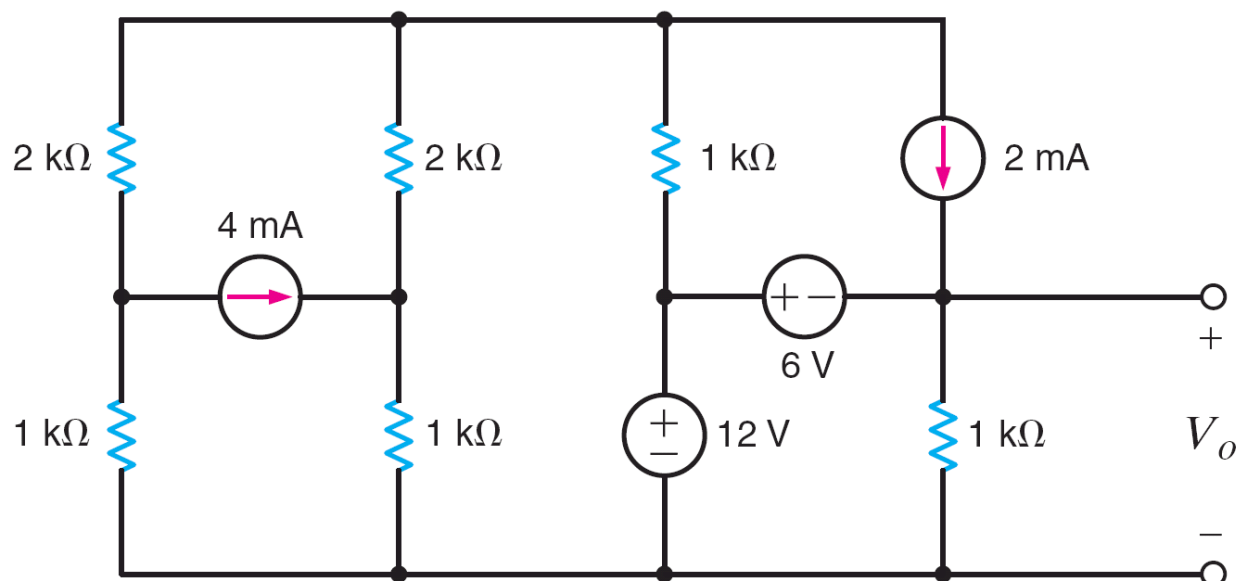

**Figure P3.38**

**SOLUTION:**

3.38 Find  $V_o$

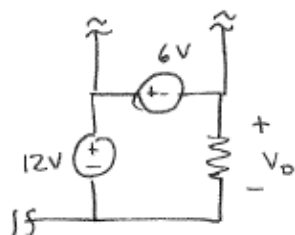


Rest of circuit is of no consequence to  $V_o$

$$V_o = 12 - 6$$

$$\boxed{V_o = 6V}$$


**3.39** Find  $V_o$  in the network in Fig. P3.39.

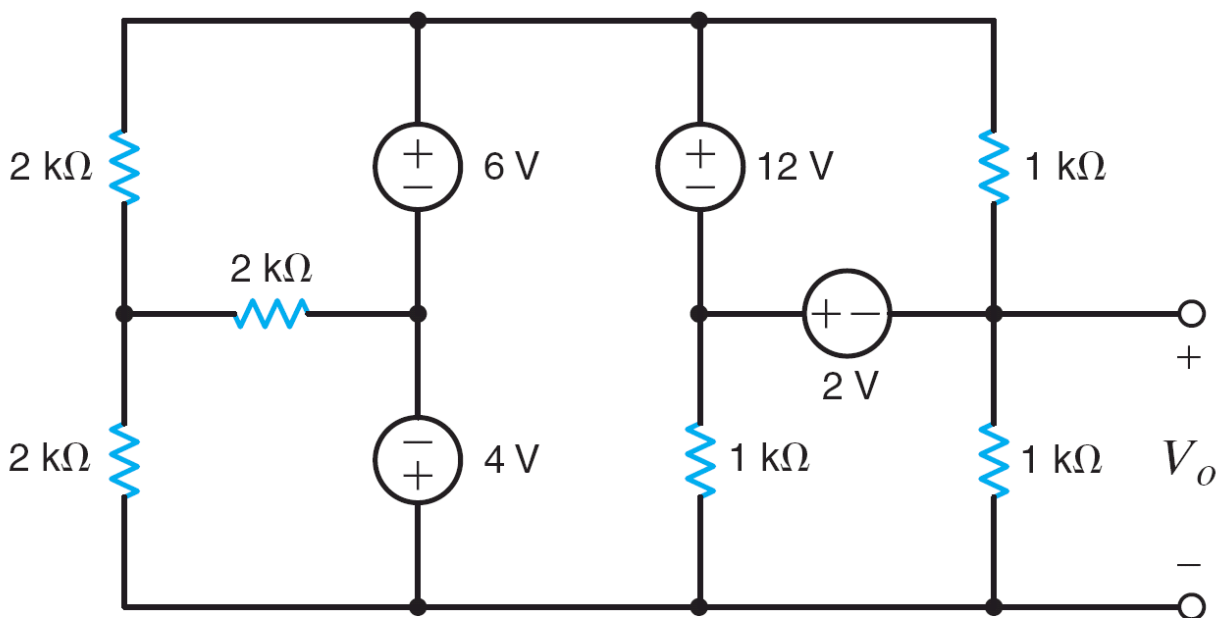

**Figure P3.39**

SOLUTION:

3.39 Find  $V_o$

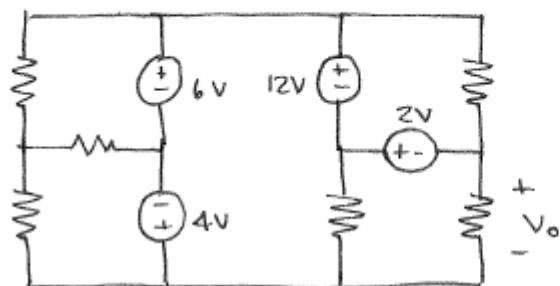


By KVL:

$$4 - 6 + 12 + 2 + V_o = 0$$

$$\boxed{V_o = -12}$$


**3.40** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.40.

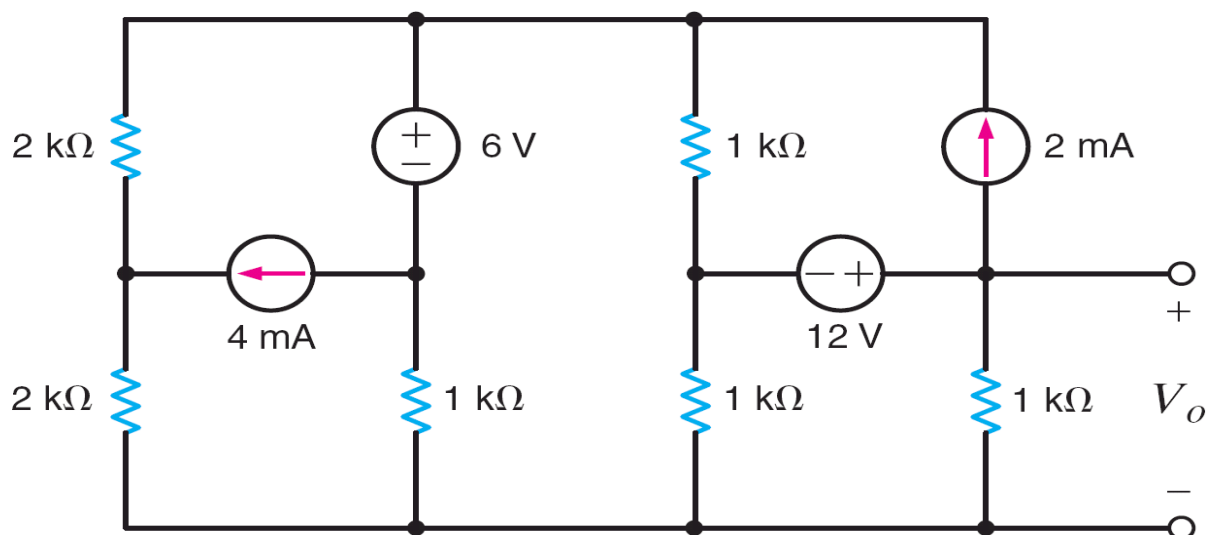

**Figure P3.40**

**SOLUTION:**

3.40 Find  $V_o$  by nodal.

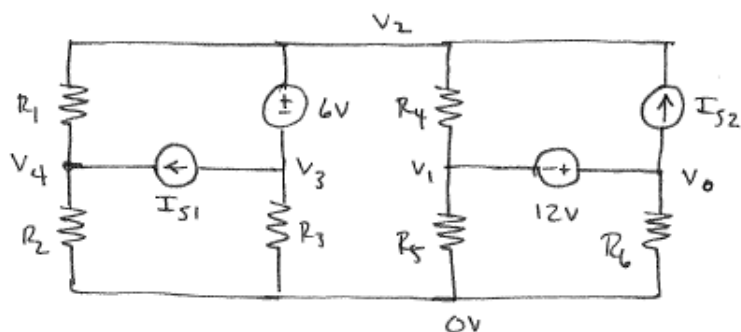

$$R_1 = R_2 = 2 \text{ k}\Omega$$

$$R_3 = R_4 = R_5 = R_6 = 1 \text{ k}\Omega$$

$$I_{S1} = 4 \text{ mA}$$

$$I_{S2} = 2 \text{ mA}$$


$$V_2 - V_3 = 6 \text{ V} \quad V_0 - V_1 = 12 \text{ V}$$

$$\text{@ } V_4: \quad \frac{V_4 - V_2}{R_1} + \frac{V_4}{R_2} = I_{S1}$$

$$\text{@ ref:} \quad \frac{V_4}{R_2} + \frac{V_3}{R_3} + \frac{V_1}{R_5} + \frac{V_0}{R_6} = 0$$

$$V_o = 7.57 \text{ V}$$


**3.41** Determine  $V_o$  in the network in Fig. P3.41.

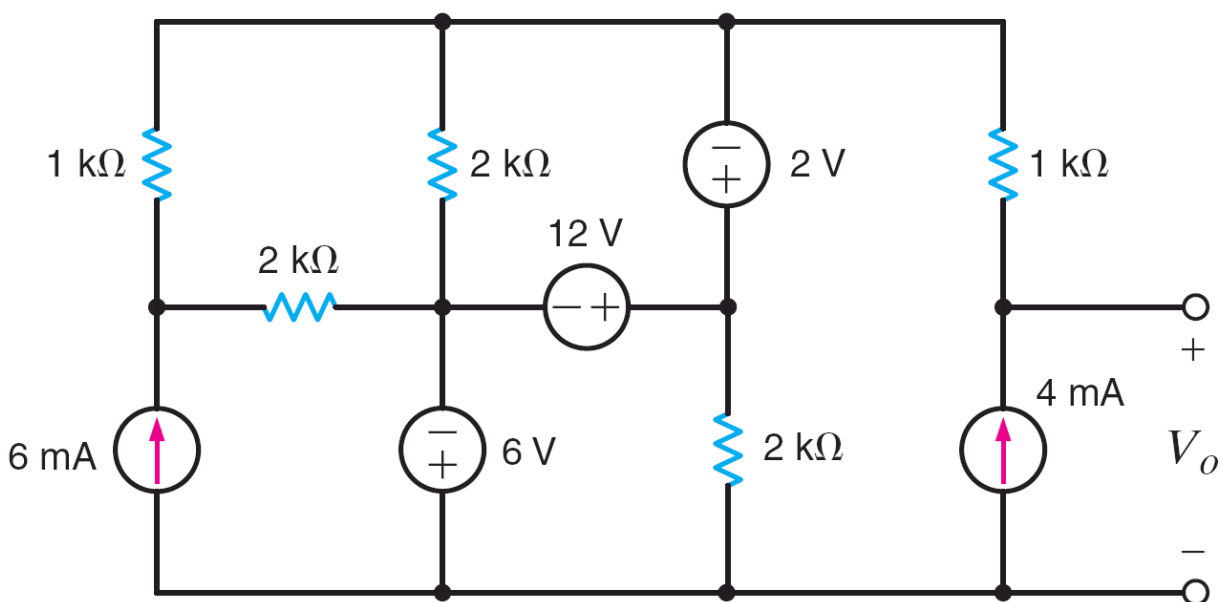

**Figure P3.41**

SOLUTION:

3.41 Find  $V_o$

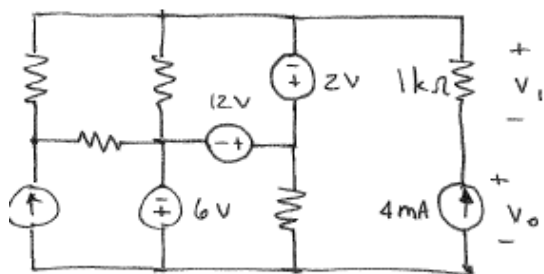


$$\text{KVL: } 6 - 12 + 2 + V_1 + V_o = 0$$

$$V_1 = (-4 \times 10^{-3})(10^3) = -4\text{V}$$

$$V_o = 8\text{V}$$


**3.42** Find  $V_o$  in the circuit in Fig. P3.42.

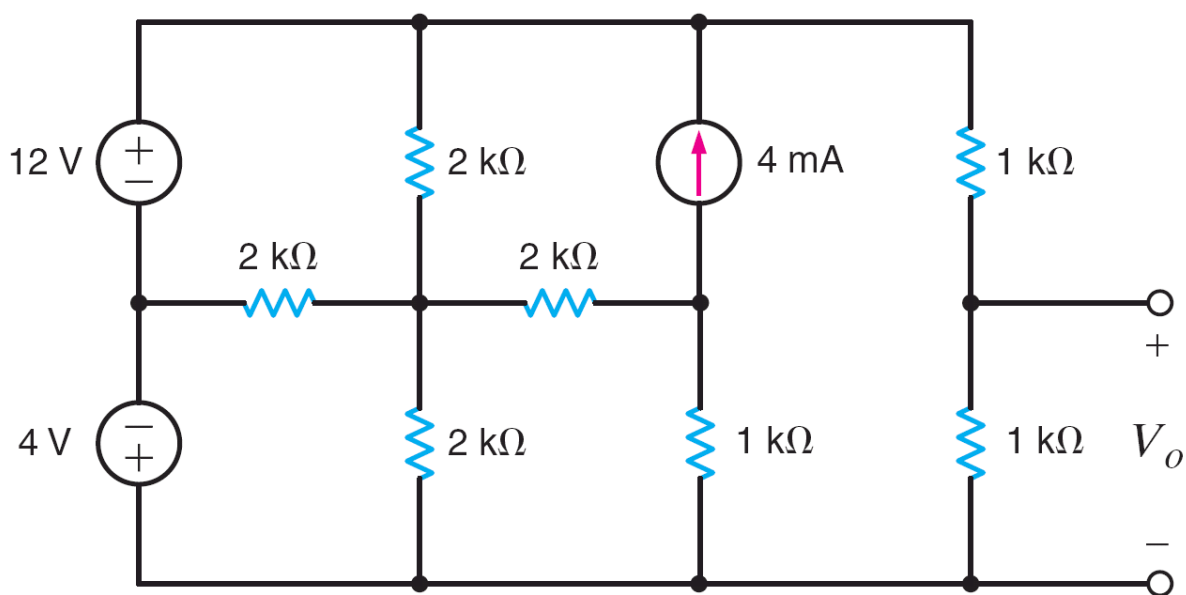

**Figure P3.42**

**SOLUTION:**

3.42 Find  $V_o$

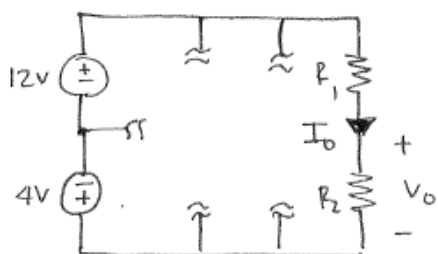

$$R_1 = R_2 = 1k\Omega$$

Rest of circuit has no effect on  $V_o$ !


$$\text{KVL: } 4 - 12 + I_o R_1 + I_o R_2 = 0$$

$$I_o = 4\text{mA}$$

$$V_o = R_2 I_o$$

$$\boxed{V_o = 4\text{V}}$$


**3.43** Find  $I_o$  in the circuit in Fig. P3.43 using nodal analysis.

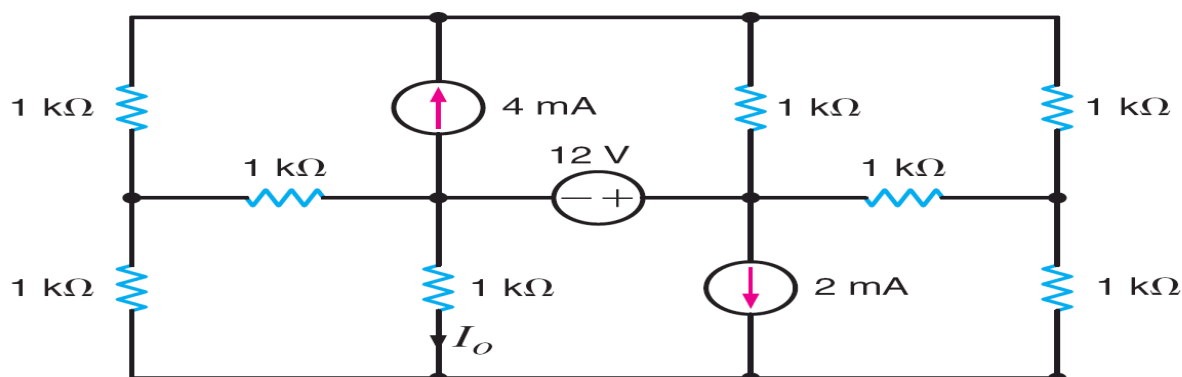

**Figure P3.43**

**SOLUTION:**

3.43 Find  $I_o$  by nodal.

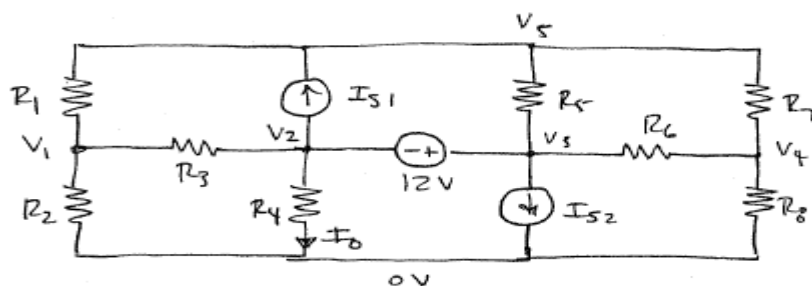

all  $R = 1\text{ k}\Omega$

$I_{S1} = 4\text{ mA}$

$I_{S2} = 2\text{ mA}$

$$V_3 - V_2 = 12$$

$$\text{@ } V_1: \frac{V_1 - V_5}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$

$$\text{@ } V_4: \frac{V_4 - V_3}{R_6} + \frac{V_4 - V_5}{R_7} + \frac{V_4}{R_8} = 0$$

$$\text{@ } V_5: \frac{V_5 - V_1}{R_1} + \frac{V_5 - V_3}{R_5} + \frac{V_5 - V_4}{R_7} = I_{S1}$$


$$\text{@ ref: } \frac{V_1}{R_2} + \frac{V_2}{R_4} + \frac{V_4}{R_8} + I_{S2} = 0$$

$$I_o = V_2 / R_4$$

$$I_o = -5.47\text{ mA}$$




**3.44** Use nodal analysis to find  $V_o$  in Fig. P3.44.

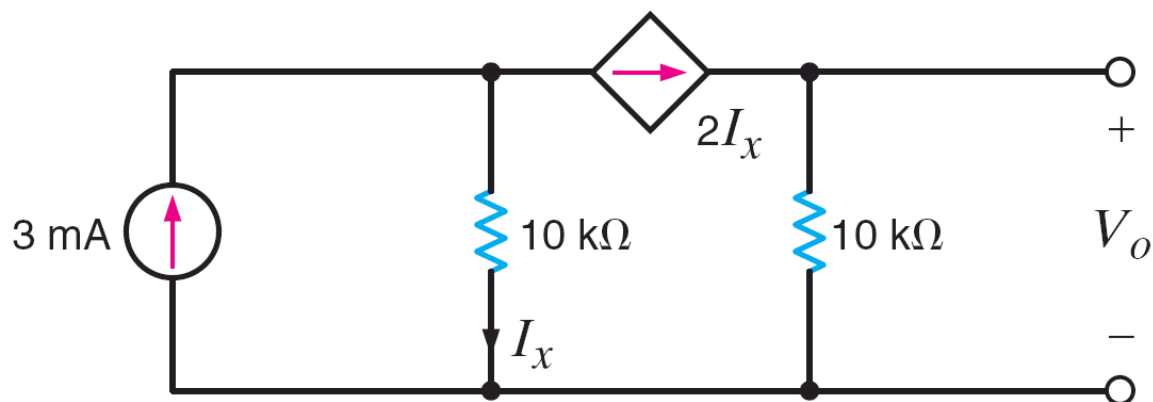

**Figure P3.44**

**SOLUTION:**

3.44 Find  $V_o$  by nodal.

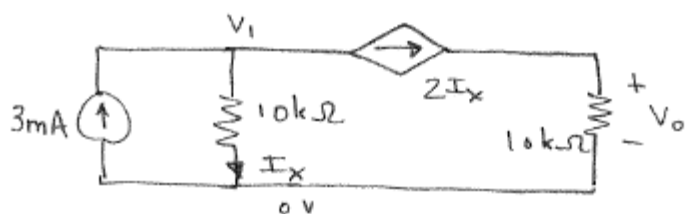


$$\text{@ } V_1: \quad 3 \times 10^{-3} = \frac{V_1}{10^4} + 2I_x \quad I_x = \frac{V_1}{10^4}$$

$$\text{@ } V_o: \quad 2I_x = \frac{V_o}{10^4}$$

$$\boxed{V_o = 20 \text{ V}}$$


**3.45** Find  $V_o$  in the circuit in Fig. P3.45 using nodal analysis.

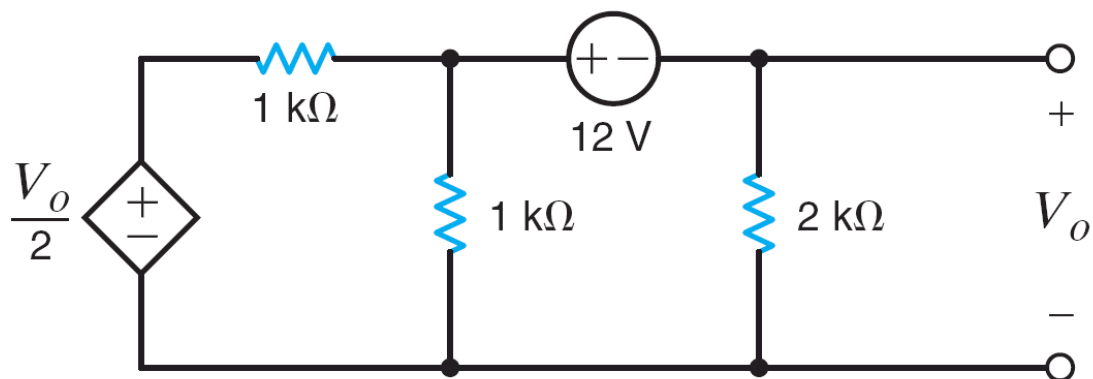


**Figure P3.45**

**SOLUTION:**

3.45 Find  $V_o$  by nodal.

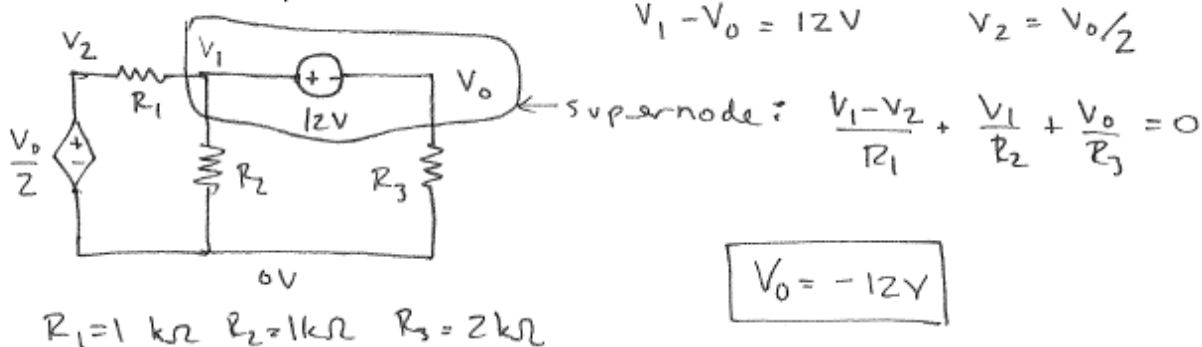


**3.46** Find  $V_o$  in the circuit in Fig. P3.46 using nodal analysis. Then solve the problem using MATLAB and compare your answers. **CS**

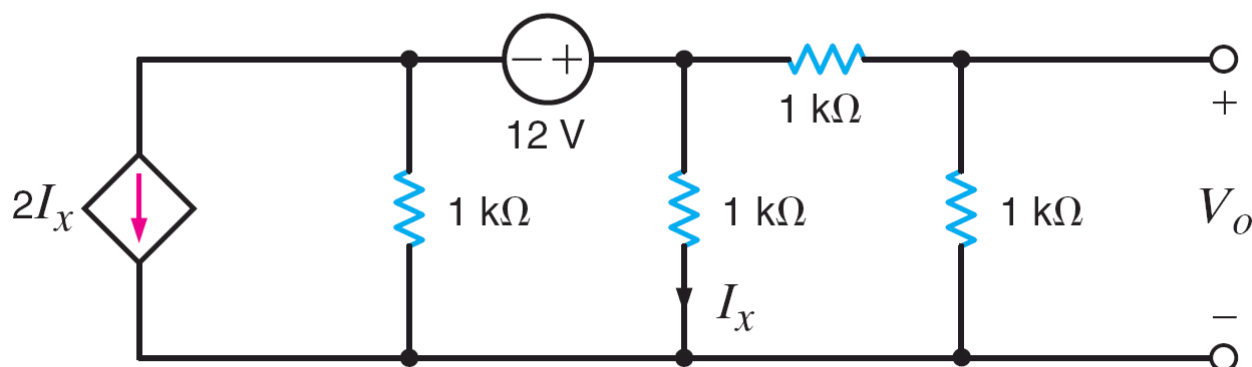

**Figure P3.46**

**SOLUTION:**

3.46 Find  $V_o$  by nodal & MATLAB

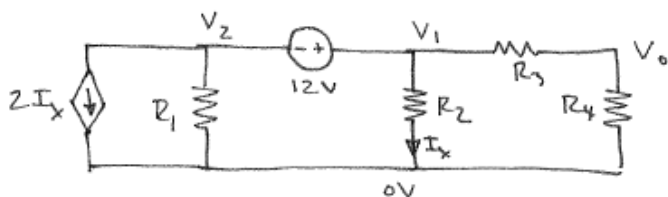

All  $R = 1k\Omega$

$$V_1 - V_2 = 12$$


$$@ V_o: \frac{V_o - V_1}{R_3} + \frac{V_o}{R_4} = 0$$

$$@ \text{ref}: 2I_x + \frac{V_2}{R_1} + \frac{V_1}{R_2} + \frac{V_o}{R_4} = 0$$

$$I_x = V_1 / R_2$$

$$V_o = 1.33V$$


**3.47** Find  $I_o$  in the network in Fig. P3.47. **PSV**

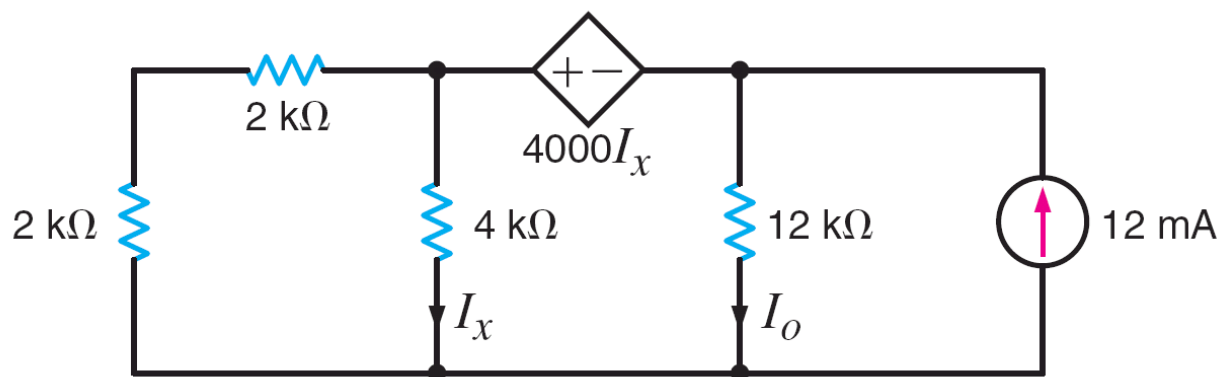

**Figure P3.47**

SOLUTION:

3.47 Find  $I_o$ .

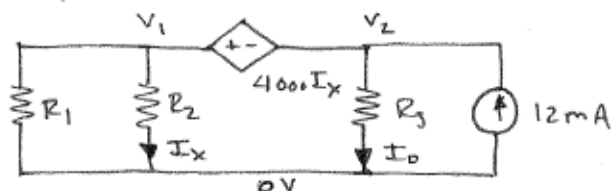

$$R_1 = R_2 = 4 \text{ k}\Omega \quad R_3 = 12 \text{ k}\Omega$$

$$V_1 - V_2 = 4000 I_x$$


$$I_x = V_1 / R_2$$

$$\frac{V_1}{R_1} + \frac{V_1}{R_2} + \frac{V_2}{R_3} = 12 \times 10^{-3}$$

$$I_o = V_2 / R_3$$

$$\boxed{I_o = 0 \text{ A}}$$


**3.48** Find  $I_o$  in the circuit in Fig. P3.48 using nodal analysis.

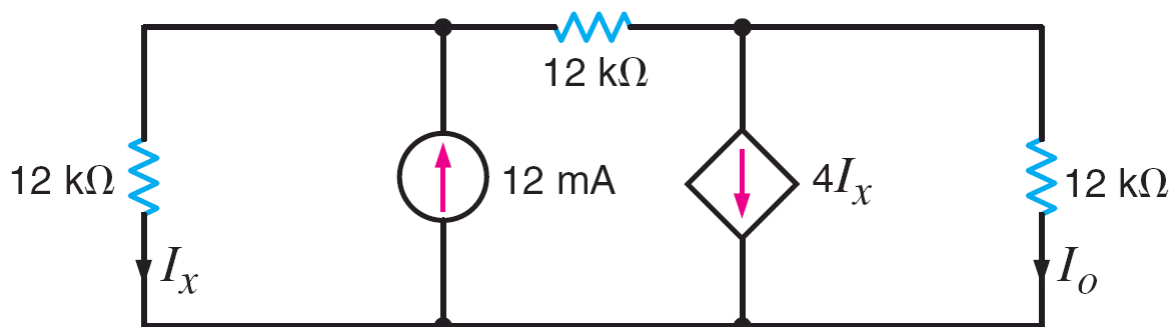

**Figure P3.48**

**SOLUTION:**

3.48 Find  $I_o$  by nodal.

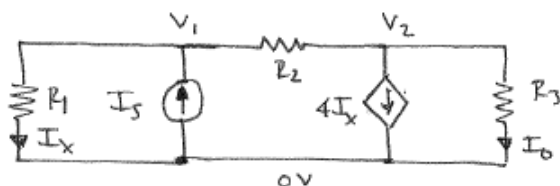

All  $R = 12\text{ k}\Omega$   $I_s = 12\text{ mA}$

$$\text{@ } V_1: I_s = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$\text{@ } V_2: \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + 4I_x = 0$$


$$I_x = V_1 / R_1$$

$$I_o = V_2 / R_3$$

$$\boxed{I_o = 5.14\text{ mA}}$$

**3.49** Find  $V_o$  in the network in Fig. P3.49 using nodal analysis.


**CS**

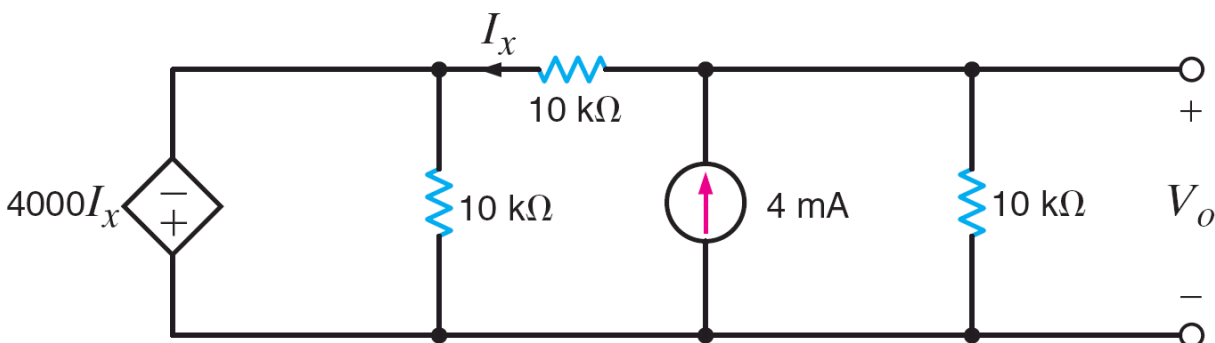

**Figure P3.49**

**SOLUTION:**

3.49 Find  $V_o$  by nodal.

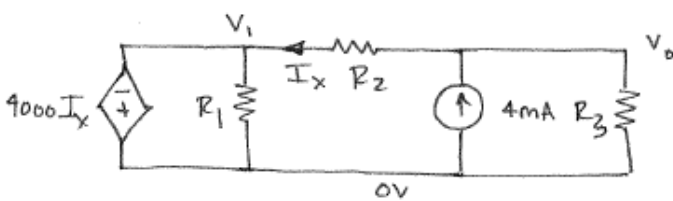

$$R_1 = R_2 = R_3 = 10 \text{ k}\Omega$$


$$V_1 = -4000 I_x$$

$$I_x = (V_o - V_1) / R_2$$

$$\text{@ } V_o: \frac{V_o}{R_3} + \frac{V_o - V_1}{R_2} = 4 \times 10^{-3}$$

$$\boxed{V_o = 15 \text{ V}}$$


**3.50** Find  $V_o$  in the circuit in Fig. P3.50. **PSV**

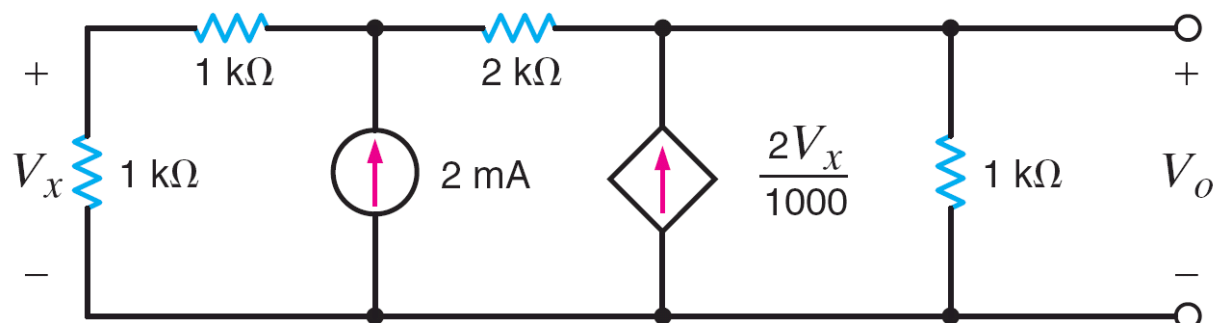

**Figure P3.50**

**SOLUTION:**

3.50 Find  $V_o$

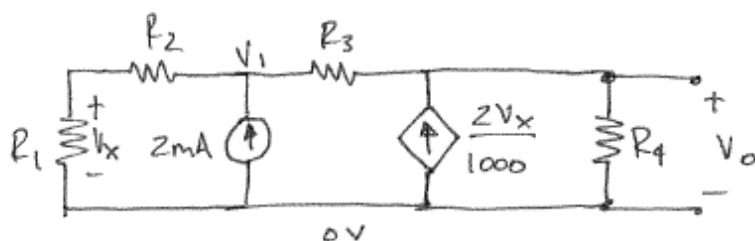

$$R_1 = R_2 = R_4 = 1\text{ k}\Omega$$

$$R_3 = 2\text{ k}\Omega$$

Nodal Analysis: 
$$2 \times 10^{-3} = \frac{V_1 - V_o}{R_3} + \frac{V_1}{R_1 + R_2}$$

Voltage Division


$$V_x = V_1 \left[ \frac{R_1}{R_1 + R_2} \right]$$

$$\frac{2V_x}{1000} = \frac{V_o - V_1}{R_3} + \frac{V_o}{R_4}$$

$$V_x = V_1 / 2$$

$$\boxed{V_o = 4\text{ V}}$$


**3.51** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.51. In addition, find all branch currents and check your answers using KCL at every node.

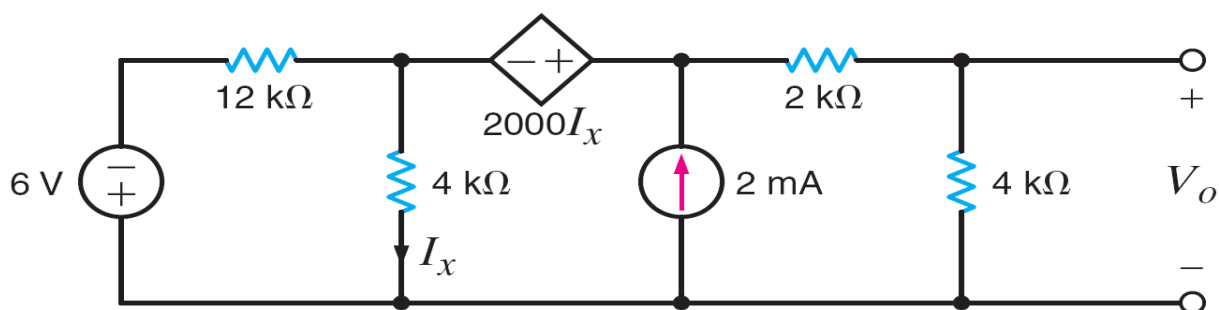

**Figure P3.51**

SOLUTION:

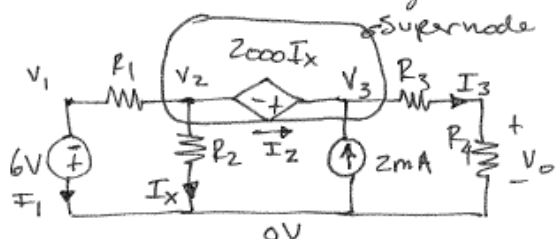3.51 Use nodal analysis to find  $V_o$  & check via KCL.



$$R_1 = 12k\Omega \quad R_2 = 4k\Omega$$

$$R_3 = 2k\Omega \quad R_4 = 4k\Omega$$

$$V_1 = -6V \quad V_2 - V_3 = -2000I_x \quad I_x = V_2/R_2$$

$$\frac{V_3 - V_o}{R_3} = \frac{V_o}{R_4} \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3 - V_o}{R_3} = 2 \times 10^{-3}$$

Solve for  $V_o$ :

$$V_o = 2.57V$$

$$I_1 = 714\mu A \quad I_x = 643\mu A \quad I_2 = -1357\mu A \quad I_3 = 643\mu A$$

@  $V_2$      $I_1 + I_2 + I_x = 0?$      $714 + 643 - 1357 = 0$     ✓

@  $V_3$      $I_2 + 2 \times 10^{-3} = I_3$      $-1357 + 2000 = 643$     ✓

@ ref:     $I_1 + I_x + I_3 = 2 \times 10^{-3}$      $714 + 643 + 643 - 2000 = 0$     ✓



**3.52** Find the power supplied by the 2-A current source in the network in Fig. P3.52 using nodal analysis.


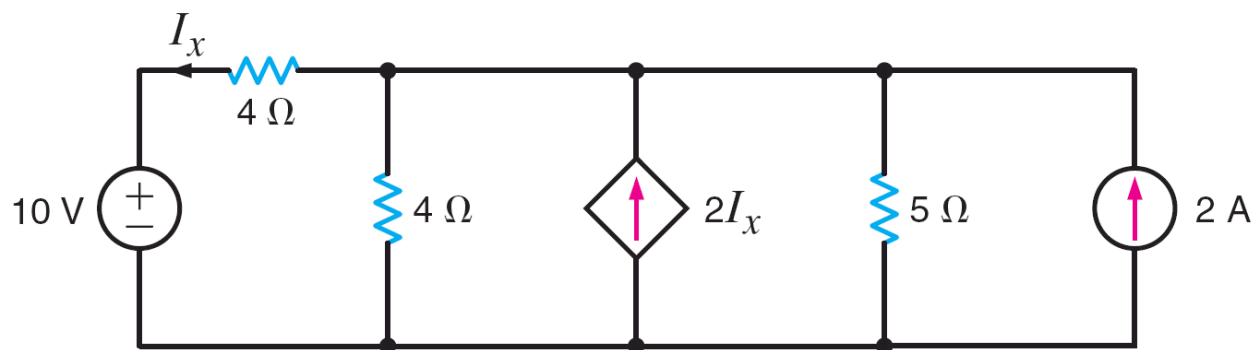


Figure P3.52

SOLUTION:

3.52 Find  $P_{2A}$  by nodal analysis.

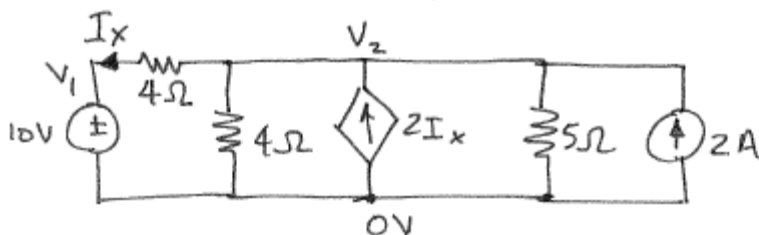

$$V_1 = 10V$$

$$I_x = \frac{V_2 - V_1}{4}$$

$$2 + 2I_x = \frac{V_2}{4} + \frac{V_2}{5} + \frac{V_2 - V_1}{4} \Rightarrow V_2 =$$

$$P_{2A} = (2)(V_2) = -5 \text{ W supplied}$$

2A - source absorbs 5W

**3.53** Use nodal equations for the circuit in Fig. P3.53 to determine  $V_o$ .


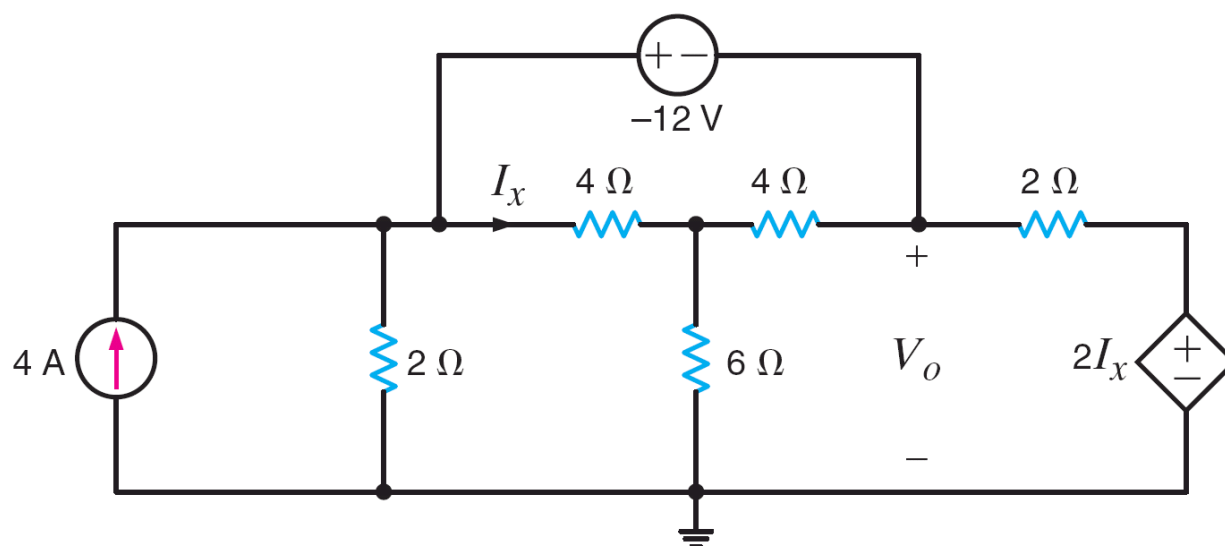


Figure P3.53

SOLUTION:

3.53

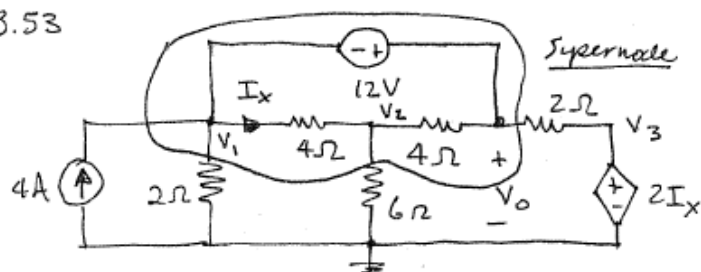

Find  $V_o$  by nodal analysis.

$$12 = V_o - V_1$$

$$2I_x = V_3$$

$$I_x = (V_1 - V_2) / 4$$


$$\text{at } V_2: \frac{V_1 - V_2}{4} + \frac{V_o - V_2}{4} = \frac{V_2}{6}$$

$$\text{at supernode: } 4 = \frac{V_1}{2} + \frac{V_2}{6} + \frac{V_o - V_3}{2}$$

Solve for  $V_o$ :

$$V_o = 8.35 \text{ V}$$


**3.54** Determine  $V_o$  in the network in Fig. P3.54 using nodal analysis.

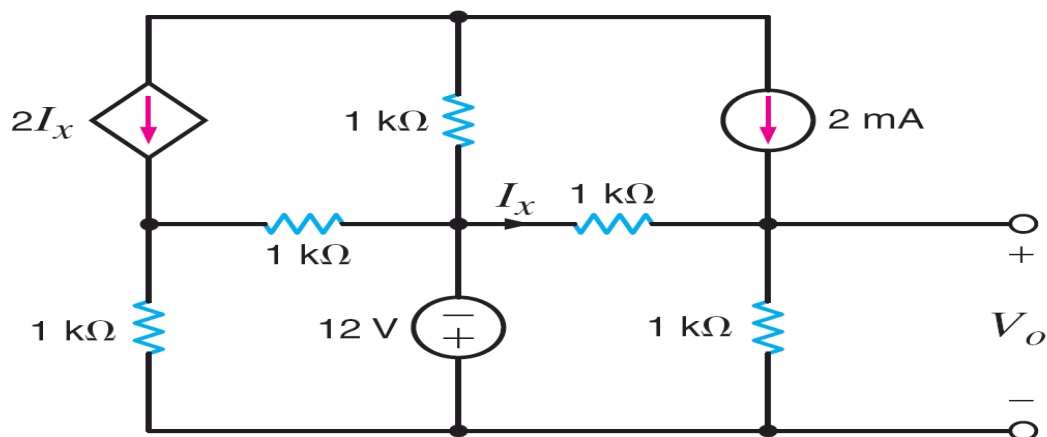

**Figure P3.54**

**SOLUTION:**

3.54 Find  $V_o$  by nodal analysis.

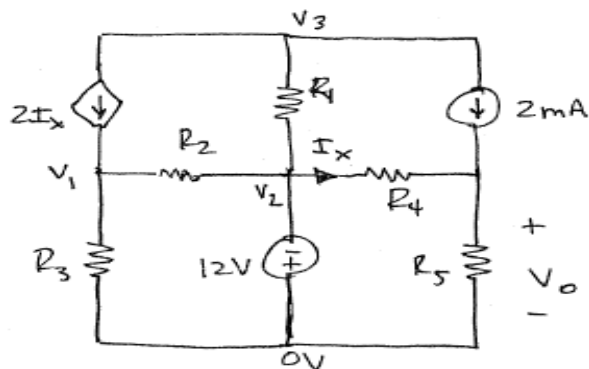

All  $R$ 's =  $1\text{ k}\Omega$

$$V_2 = -12$$

$$I_x = \frac{V_2 - V_o}{R_4}$$

$$\text{at } v_3: 2I_x + 2 \times 10^{-3} + \frac{V_3 - V_2}{R_1} = 0$$


$$\text{at } v_1: 2I_x + \frac{V_2 - V_1}{R_2} = \frac{V_1}{R_3}$$

$$\text{at } v_o: 2 \times 10^{-3} + \frac{V_2 - V_o}{R_4} = \frac{V_o}{R_5}$$

Solve for  $V_o$ :

$$\boxed{V_o = -5\text{ V}}$$


**3.55** Calculate  $V_o$  in the circuit in Fig. P3.55 using nodal analysis.

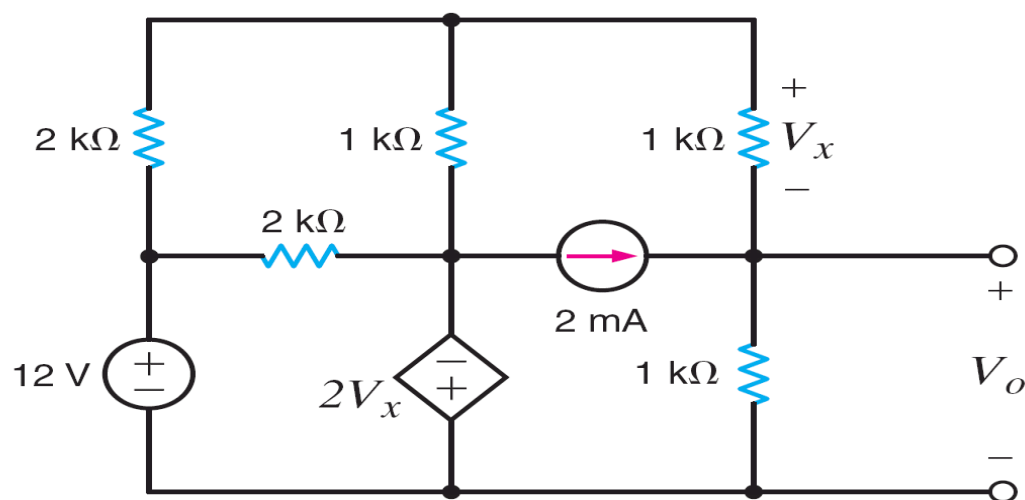

**Figure P3.55**

SOLUTION:

3.55 Find  $V_o$  by nodal analysis.

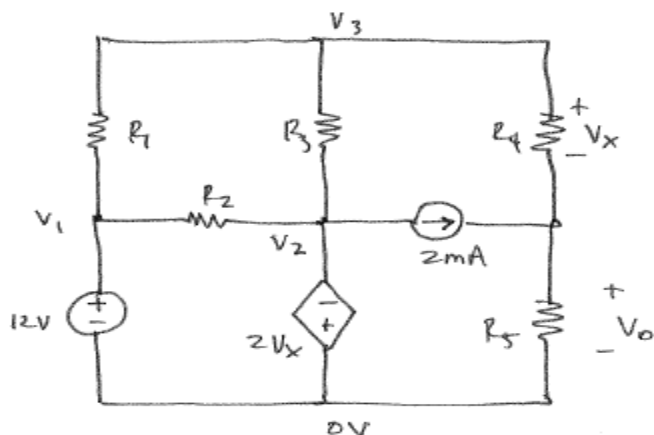

$$R_1 = R_2 = 2\text{ k}\Omega$$

$$R_3 = R_4 = R_5 = 1\text{ k}\Omega$$

$$V_x = V_3 - V_o$$

$$V_1 = 12\text{ V}$$

$$V_2 = -2V_x$$


$$\text{at } V_3: \quad \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_o}{R_4} = 0$$

$$\text{at } V_o: \quad \frac{V_3 - V_o}{R_4} + 2 \times 10^{-3} = \frac{V_o}{R_5}$$

Solve for  $V_o$ :

$$\boxed{V_o = 2.5\text{ V}}$$


**3.56** Using nodal analysis, find  $V_o$  in the network in Fig. P3.56.

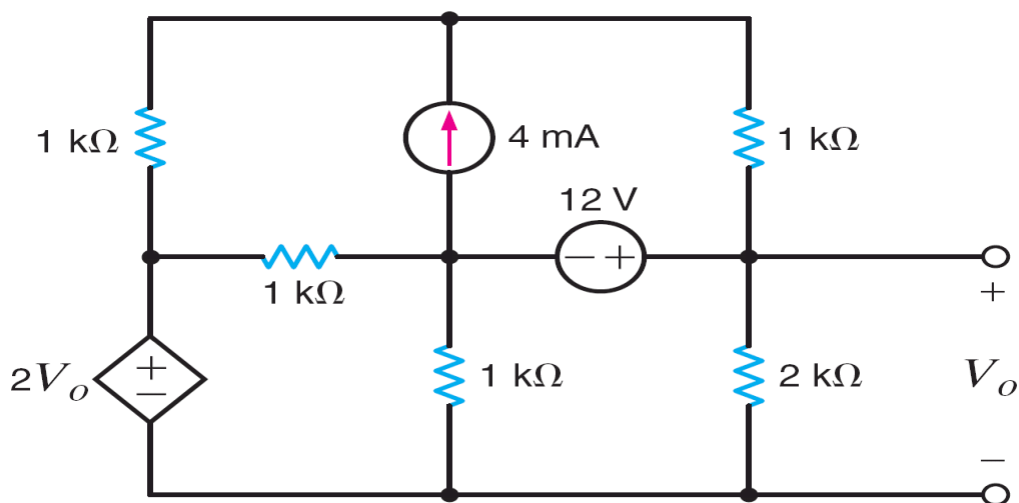

**Figure P3.56**

**SOLUTION:**

3.56 Find  $V_o$  by nodal analysis.

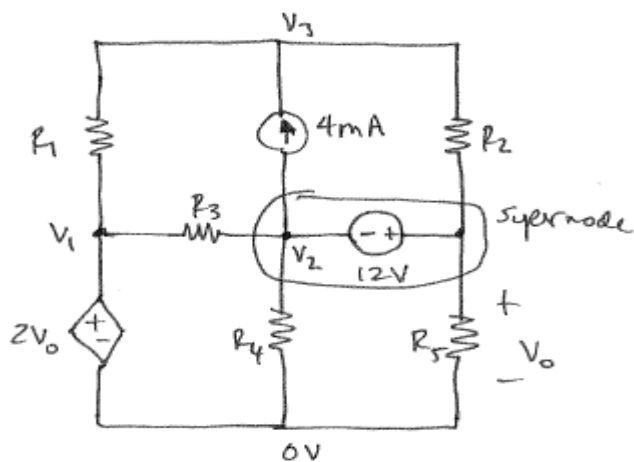

$$R_1 = R_2 = R_3 = R_4 = 1 \text{ k}\Omega$$

$$R_5 = 2 \text{ k}\Omega$$

$$V_1 = 2V_o$$

$$V_o - V_2 = 12 \text{ V}$$


$$\text{at } V_3: \quad 4 \times 10^{-3} = \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_o}{R_2}$$

$$\text{at supernode:} \quad \frac{V_o}{R_5} + \frac{V_2}{R_4} + \frac{V_o - V_3}{R_2} + \frac{V_2 - V_1}{R_3} + 4 \times 10^{-3} = 0$$

Solve for  $V_o$ :

$$\boxed{V_o = \infty \text{ V}}$$


**3.57** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.57.

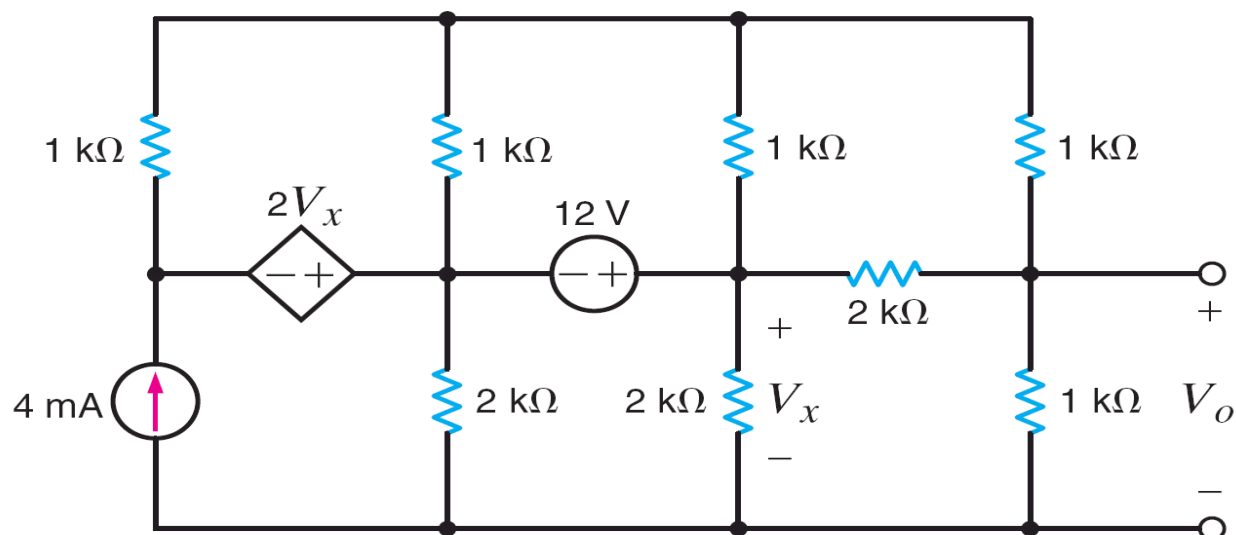

**Figure P3.57**

**SOLUTION:**

3.57 Find  $V_o$  by nodal analysis.

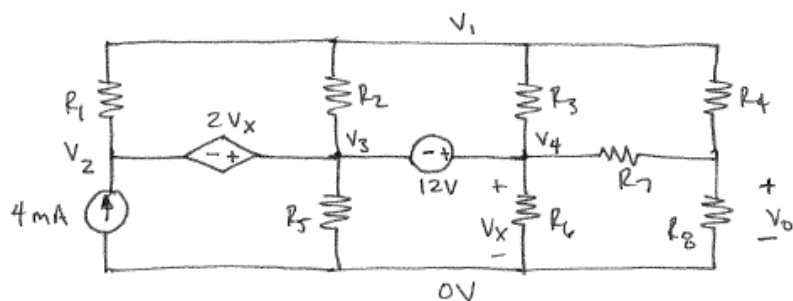

$$R_1 = R_2 = R_3 = R_4 = R_8 = 1\text{ k}\Omega$$

$$R_5 = R_6 = R_7 = 2\text{ k}\Omega$$

$$V_4 - V_3 = 12$$

$$V_3 - V_2 = 2V_x$$


$$V_x = V_4$$

At  $V_1$  
$$\frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_2} + \frac{V_1 - V_4}{R_3} + \frac{V_1 - V_0}{R_4} = 0$$

At  $V_0$  
$$\frac{V_3}{R_5} + \frac{V_4}{R_6} + \frac{V_0}{R_8} = 4 \times 10^{-3}$$

Solve for  $V_o$ : 
$$V_o = 0.5\text{ V}$$


**3.58** Use nodal analysis to determine  $I_o$  in the circuit in Fig. P3.58.

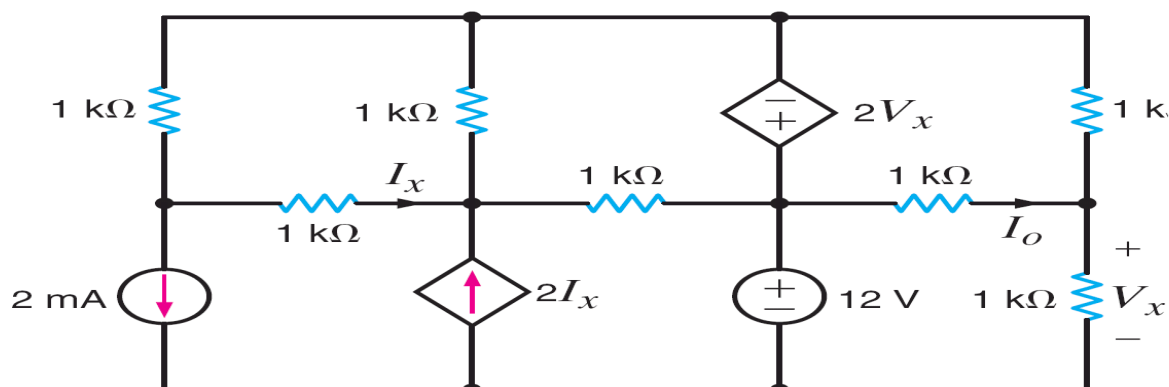

**Figure P3.58**

**SOLUTION:**

3.58 Use nodal to find  $I_o$

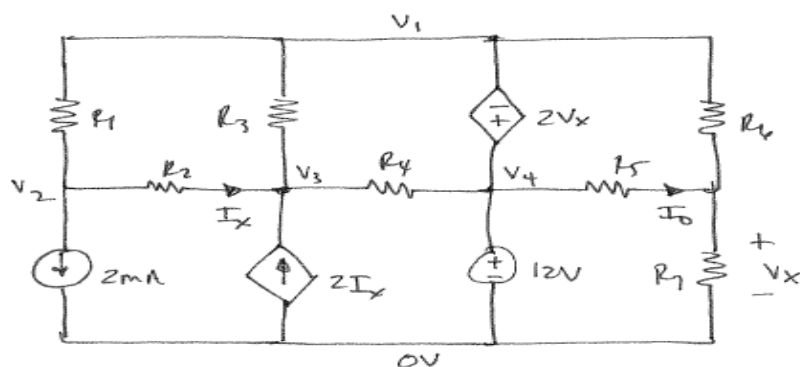

All  $R$ 's =  $1\text{ k}\Omega$

$$V_4 - V_1 = 2V_x$$

$$V_4 = 12\text{ V}$$

$$I_x = (V_2 - V_3) / R_2$$

at  $V_2$  
$$\frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + 2 \times 10^{-3} = 0$$

at  $V_3$  
$$\frac{V_3 - V_2}{R_2} + \frac{V_3 - V_1}{R_3} + \frac{V_3 - V_4}{R_4} = 2I_x$$

at  $V_x$  
$$\frac{V_x}{R_6} + \frac{V_x - V_4}{R_5} + \frac{V_x - V_1}{R_6} = 0$$


Finally, 
$$I_o = (V_4 - V_x) / R_5$$

$$V_4 = 12\text{ V}$$

$$V_x = 4.8\text{ V}$$

$$I_o = 7.2\text{ mA}$$


**3.59** Find  $I_o$  in the network in Fig. P3.59 using nodal analysis.

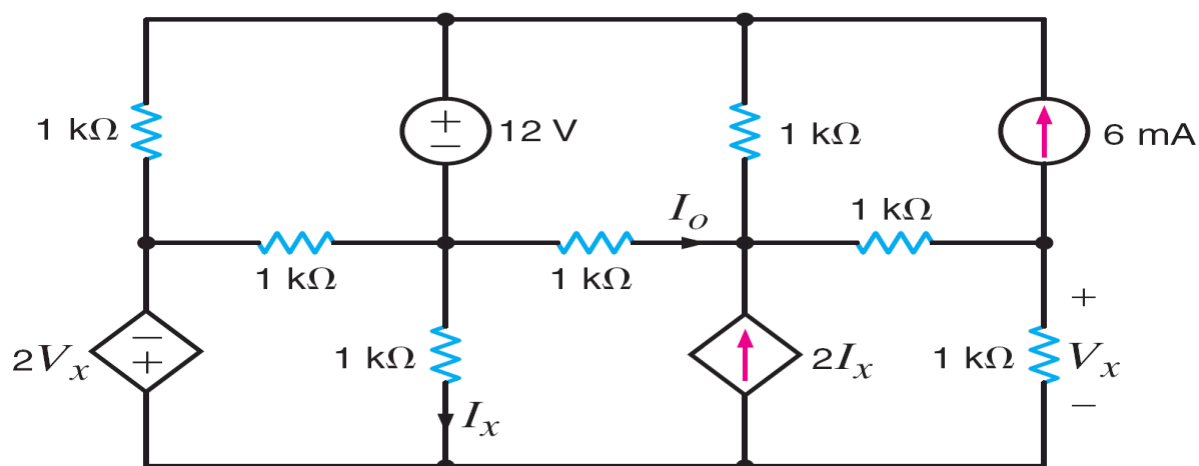

**Figure P3.59**

**SOLUTION:**

3.59 Find  $I_o$  by nodal analysis

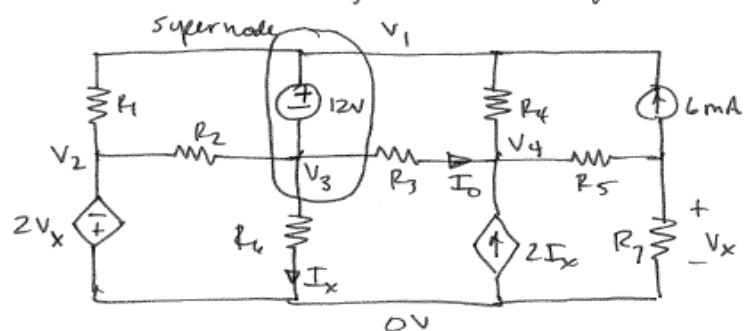

$$\text{All } R\text{'s} = 1\text{ k}\Omega$$

$$12 = V_1 - V_3$$

$$2V_x + V_2 = 0$$

$$I_x = V_3 / R_6$$

At  $V_4$

$$\frac{V_4 - V_1}{R_4} + \frac{V_4 - V_x}{R_5} + \frac{V_4 - V_3}{R_3} = 2I_x$$

At supernode:

$$\frac{V_1 - V_2}{R_1} + \frac{V_1 - V_4}{R_4} - 6 \times 10^{-3} + \frac{V_3 - V_2}{R_2} + \frac{V_3 - V_4}{R_3} + \frac{V_3}{R_6} = 0$$

$$\text{And } I_o = \frac{V_3 - V_4}{R_3}$$

$$V_3 = -1.2\text{ V}$$

$$V_4 = 1.68\text{ V}$$

$$I_o = 2.88\text{ mA}$$



**3.60** Given the network in Fig. P3.60, we wish to determine the power dissipated in the resistor  $R_3$ .

- Is mesh or nodal analysis the most efficient approach? Why?
- For a nodal analysis, comment on the advantages of selecting node 1 as the reference node. Repeat for nodes 2, 3, and 4.
- Based on your results in (b), write the node equations.

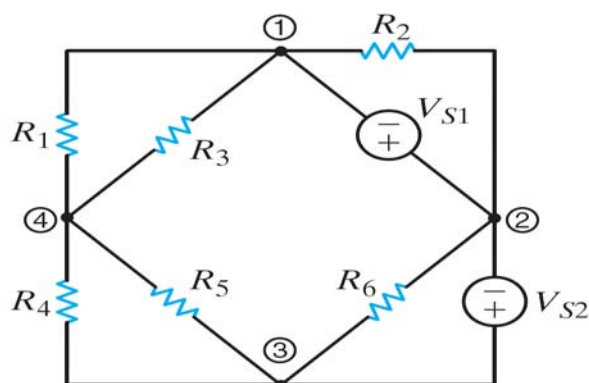


Figure P3.60

SOLUTION:

3.60 Find power absorbed by  $R_3$ .

a) Mesh or nodal?

5 mesh vs. 3 non-ref nodes  $\Rightarrow$  nodal.

b) Justify ref node choice

Node 1 - Great choice.  $V_{R3}$  will be  $V_4$ .


Node 4 - Just as good as choosing node 1.  $V_{R3}$  will be  $V_1$ .

Node 2 - Poor choice.  $V_{R3} = V_1 - V_4$  requiring 2 calculations  
But  $V_{S1}$  &  $V_{S2}$  will be simple to write in terms of node voltages

Node 3 - Worst choice of all.

Continued on the next page.

c) Choose  $V_1$  as reference.

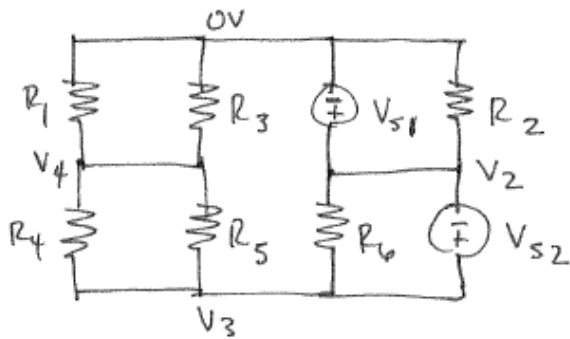

$$V_{s1} = V_2$$

$$V_{s2} = V_3 - V_2$$

$$\frac{V_4}{R_1} + \frac{V_4}{R_3} + \frac{V_4 - V_3}{R_4} + \frac{V_4 - V_3}{R_5} = 0$$

**3.61** In the circuit in Fig. P3.61, use Gaussian elimination to determine  $V_o$ .

- (a) Would mesh or nodal analysis be the most efficient approach? Why?
- (b) If mesh analysis is used, are any supermeshes required? Write the mesh equations. If nodal analysis is used, are any supernodes required? If so, how many? What is the best location for the reference node and why? Write the node equations.

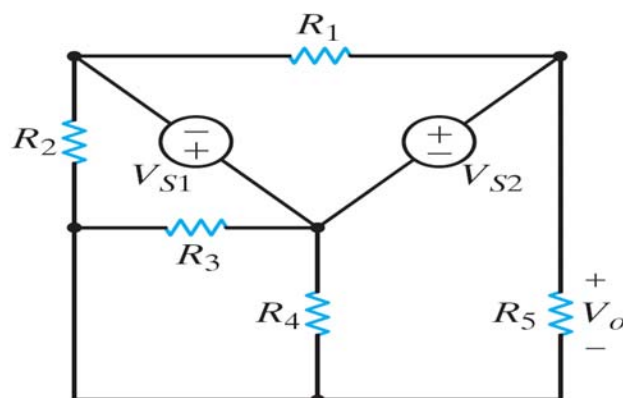


Figure P3.61

SOLUTION:

3.61 Find  $V_o$


2) Mesh or nodal?

4 meshes, 3 non-ref. nodes, 2 voltage sources  $\Rightarrow$  nodal

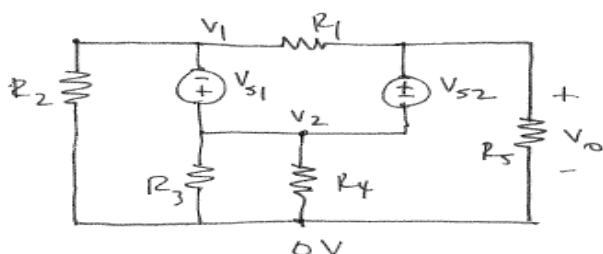b) No supermeshes required because there are no current sources

No supernodes are needed because the 2 voltage sources connect at only 3 of the nodes, leaving the 4th node free for application of KCL.

Best location for ref node is at bottom of schematic.




$$V_1 - V_2 = -V_{S1}$$

$$V_o - V_2 = V_{S2}$$

$$\frac{V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} + \frac{V_o}{R_5} = 0$$


**3.62** Use mesh equations to find  $V_o$  in the circuit in Fig. P3.62.

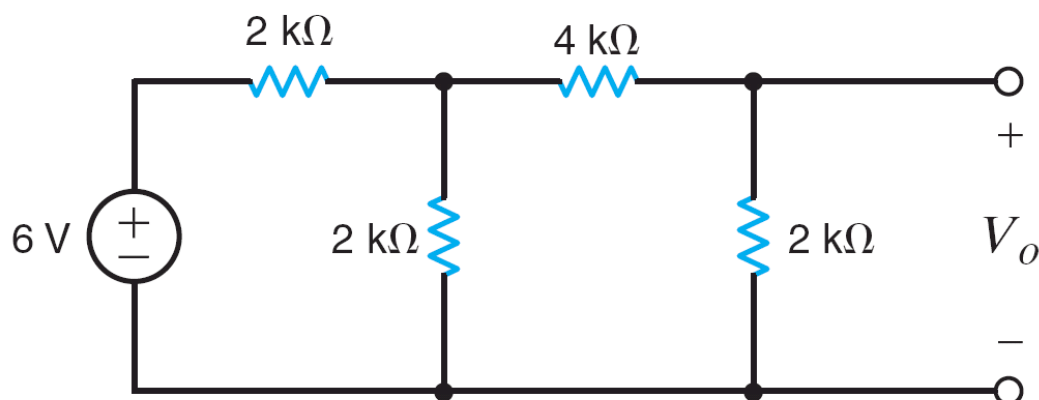

**Figure P3.62**

SOLUTION:

3.62 Use mesh analysis to find  $V_o$ .

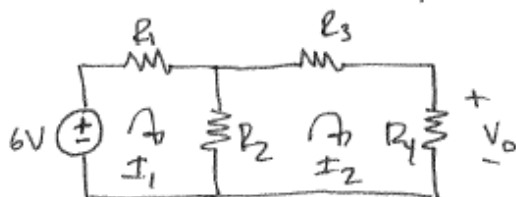

$$R_1 = R_2 = R_4 = 2\text{ k}\Omega \quad R_3 = 4\text{ k}\Omega$$

$$6 = I_1 R_1 + (I_1 - I_2) R_2$$


$$0 = -R_2 I_1 + I_2 (R_2 + R_3 + R_4)$$

$$V_o = I_2 R_4$$

$$I_2 = 429\text{ }\mu\text{A}$$

$$\boxed{V_o = 858\text{ mV}}$$


**3.63** Find  $V_o$  in the network in Fig. P3.63 using mesh equations. **PSV**

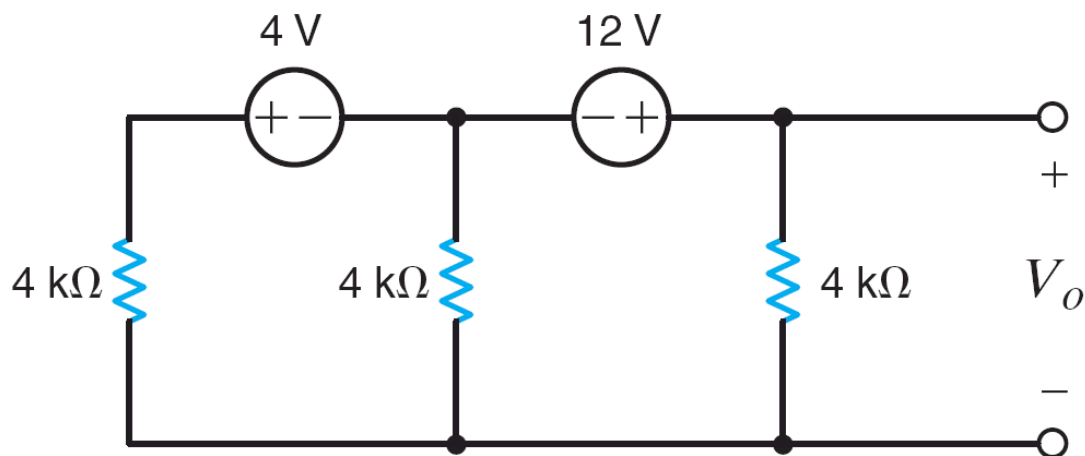

**Figure P3.63**

**SOLUTION:**

3.63 Use mesh analysis to find  $V_o$ .

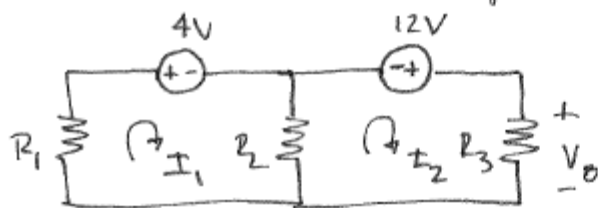

all  $R$ 's =  $4k\Omega$

$$I_1 R_1 + (I_1 - I_2) R_2 + 4 = 0$$


$$I_2 R_3 + (I_2 - I_1) R_2 = 12$$

$$V_o = I_2 R_3$$

$$I_2 = 1.67 \text{ mA}$$

$$V_o = 6.67 \text{ V}$$

**3.64** Use mesh analysis to find  $V_o$  in the circuit in Fig. P3.64.

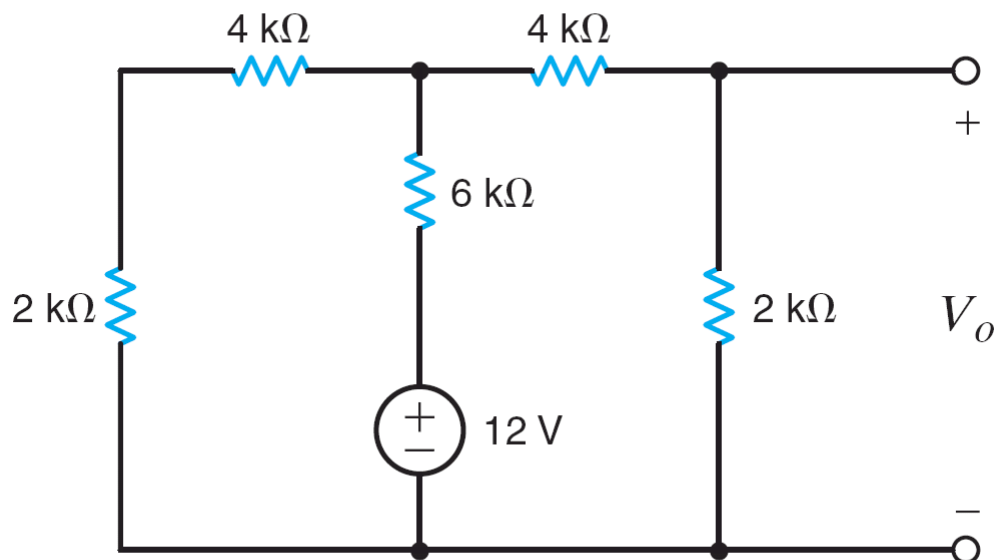


**Figure P3.64**

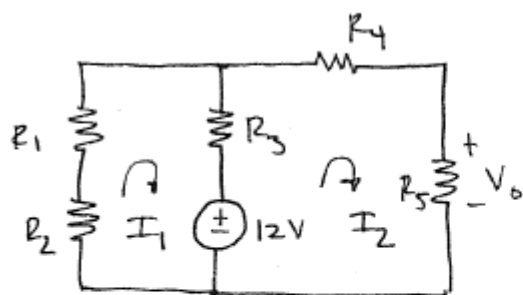---

SOLUTION:

3.64 Use mesh to find  $V_o$



$$R_1 = 4k\Omega \quad R_2 = 2k\Omega \quad R_3 = 6k\Omega$$

$$R_4 = 4k\Omega \quad R_5 = 2k\Omega$$

$$V_o = I_2 R_5$$


$$I_1 R_1 + I_1 R_2 + (I_1 - I_2) R_3 + 12 = 0$$

$$I_2 R_4 + I_2 R_5 + (I_2 - I_1) R_3 = 12$$

$$I_2 = 0.67 \text{ mA}$$


$$V_o = 1.33 \text{ V}$$

**3.65** Use mesh analysis to find  $V_o$  in the circuit in Fig. P3.65.

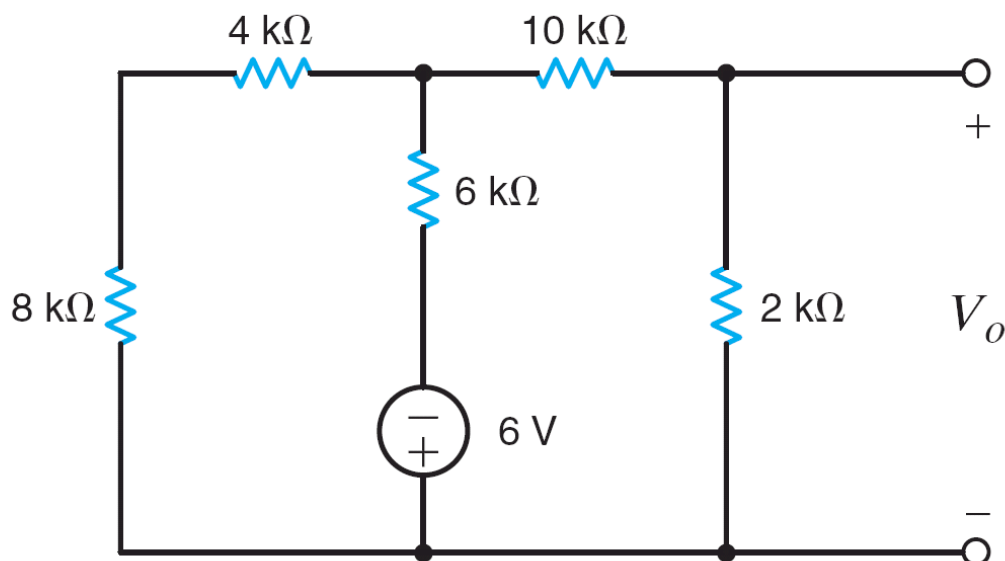

**Figure P3.65**

**SOLUTION:**

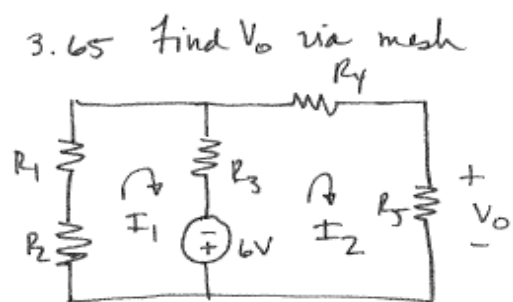

$$R_1 = 4\text{ k}\Omega \quad R_2 = 8\text{ k}\Omega \quad R_3 = 6\text{ k}\Omega$$

$$R_4 = 10\text{ k}\Omega \quad R_5 = 2\text{ k}\Omega$$

$$V_o = I_2 R_5$$

$$I_1 R_1 + I_1 R_2 + (I_1 - I_2) R_3 = 6$$


$$I_2 R_4 + I_2 R_5 + (I_2 - I_1) R_3 = -6$$

$$I_2 = -250\text{ }\mu\text{A}$$

$$V_o = -0.5\text{ V}$$




**3.66** Use mesh analysis to find  $V_o$  in the network in Fig. P3.66. **CS**

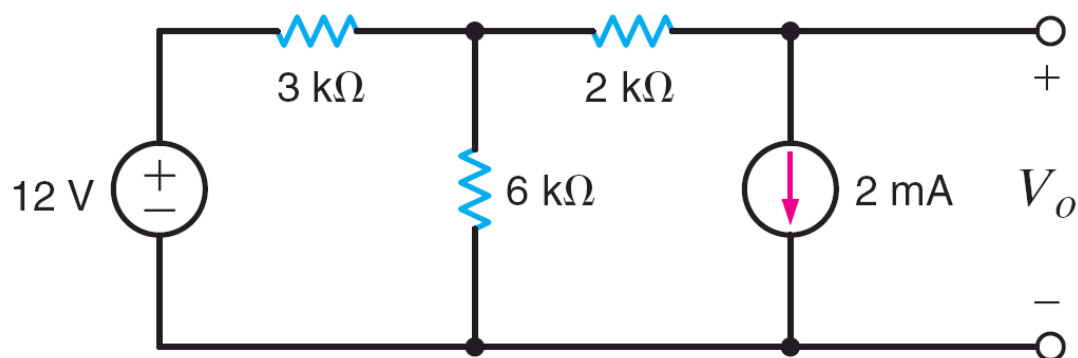

**Figure P3.66**

**SOLUTION:**

3.66 Find  $V_o$  using mesh analysis.

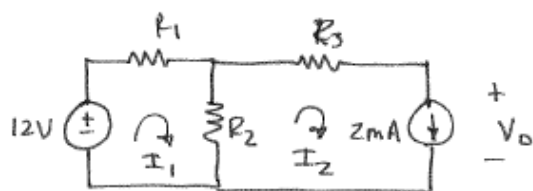

$$R_1 = 3\text{ k}\Omega \quad R_2 = 6\text{ k}\Omega \quad R_3 = 2\text{ k}\Omega$$

$$I_2 = 2\text{ mA}$$


$$12 = I_1 R_1 + (I_1 - I_2) R_2$$

$$V_o = 12 - I_1 R_1 - I_2 R_3$$

$$I_1 = 2.67\text{ mA}$$

$$\boxed{V_o = 0\text{ V}}$$


**3.67** Use loop analysis to find  $V_o$  in the circuit in Fig. P3.67.

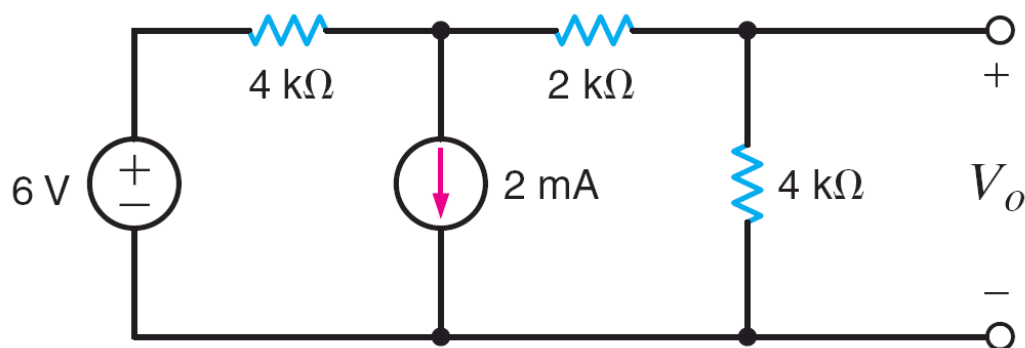

**Figure P3.67**

**SOLUTION:**

3.67 Find  $V_o$  using loop analysis.

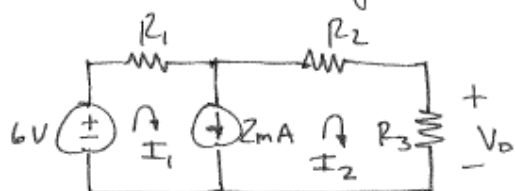

$$R_1 = 4\text{ k}\Omega \quad R_2 = 2\text{ k}\Omega \quad R_3 = 4\text{ k}\Omega$$

$$2\text{ mA} = I_1 - I_2$$

$$6 = I_1 R_1 + I_2 R_2 + I_2 R_3$$


$$V_o = I_2 R_3$$

$$I_2 = -200\text{ }\mu\text{A}$$

$$\boxed{V_o = -0.8\text{ V}}$$

**3.68** Use loop analysis to find  $V_o$  in the network in Fig. P3.68.


**PSV**

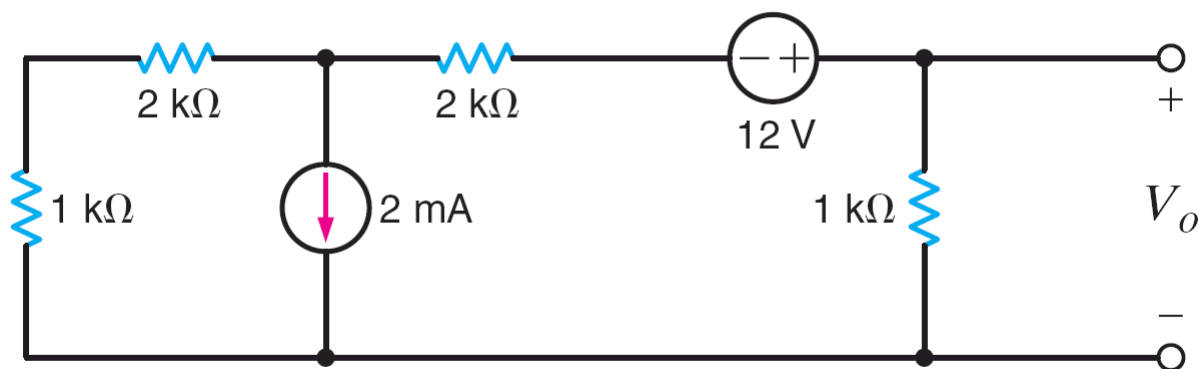

**Figure P3.68**

**SOLUTION:**

3.68 Find  $V_o$  using loop analysis.

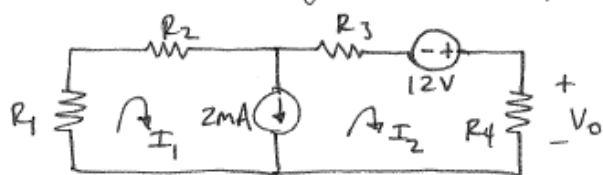

$$R_1 = R_4 = 1 \text{ k}\Omega \quad R_2 = R_3 = 2 \text{ k}\Omega$$

$$V_o = I_2 R_4$$

$$I_1 - I_2 = 2 \text{ mA}$$


$$I_1 R_1 + I_1 R_2 + I_2 R_3 + I_2 R_4 = 12$$

$$I_2 = 1 \text{ mA}$$

$$\boxed{V_o = 1 \text{ V}}$$

**3.69** Find  $I_o$  in the network in Fig. P3.69 using mesh analysis.


**CS**

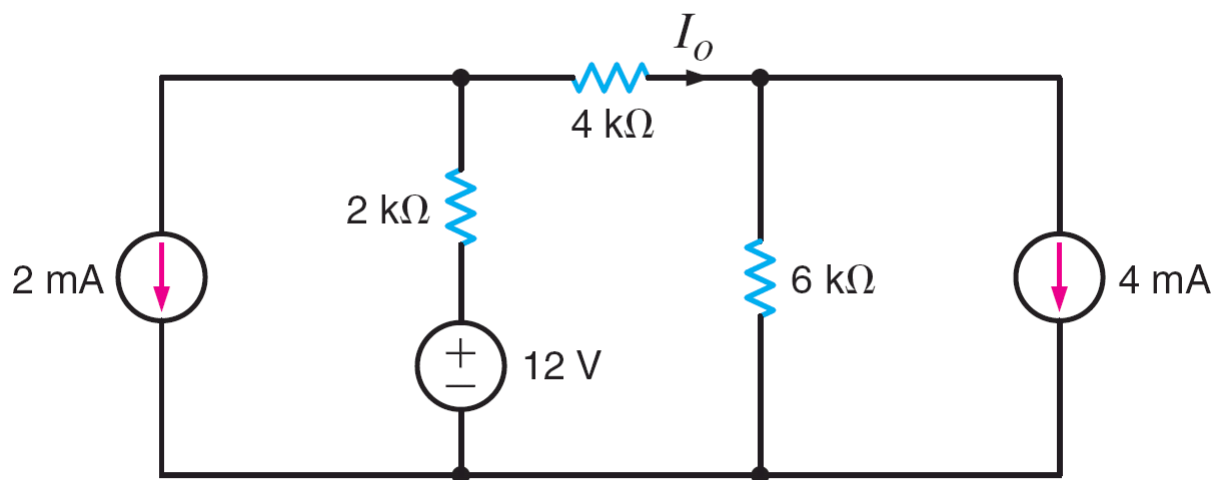

**Figure P3.69**

**SOLUTION:**

3.69 Use mesh analysis to find  $I_o$ .

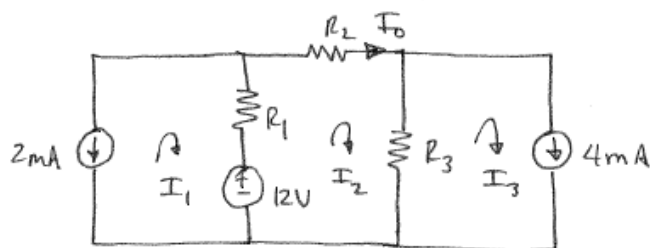

$$R_1 = 2\text{ k}\Omega \quad R_2 = 4\text{ k}\Omega \quad R_3 = 6\text{ k}\Omega$$

$$I_o = I_2$$


$$I_1 = -2\text{ mA}$$

$$I_3 = 4\text{ mA}$$

$$12 = (I_2 - I_1)R_1 + I_2 R_2 + (I_2 - I_3)R_3 \Rightarrow I_2 = 2.67\text{ mA}$$

$$\boxed{I_o = 2.67\text{ mA}}$$


**3.70** Use both nodal analysis and mesh analysis to find  $I_o$  in the circuit in Fig. P3.70.

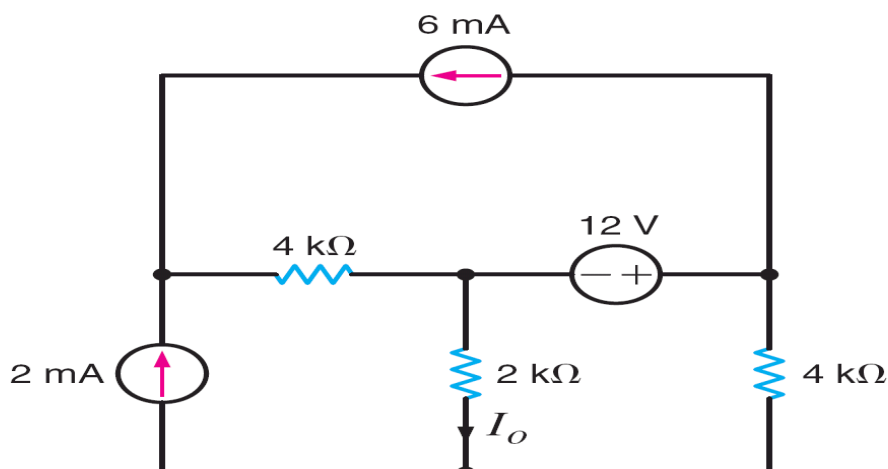

**Figure P3.70**

**SOLUTION:**

3.70 Use nodal & mesh to find  $I_o$ .

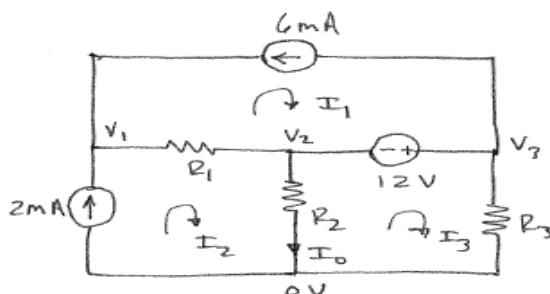

Mesh

$$I_1 = -6 \text{ mA}$$

$$I_2 = 2 \text{ mA}$$

$$12 = I_3 R_3 + (I_3 - I_2) R_2$$

$$I_o = I_2 - I_3$$

$$I_2 = 2 \text{ mA}$$

$$I_3 = 2.67 \text{ mA}$$

$$I_o = -0.67 \text{ mA}$$

$$R_1 = 4 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

Nodal

$$V_3 - V_2 = 12$$

$$6 \times 10^{-3} + 2 \times 10^{-3} + \frac{V_2 - V_1}{R_1} = 0$$


$$V_2 / R_2 + V_3 / R_3 = 2 \times 10^{-3}$$

$$I_o = V_2 / R_2$$

$$V_2 = -1.33 \text{ V}$$

$$I_o = -0.67 \text{ mA}$$


**3.71** Find  $I_o$  in the network in Fig. P3.71 using loop analysis. Then solve the problem using MATLAB and compare your answers. **CS**

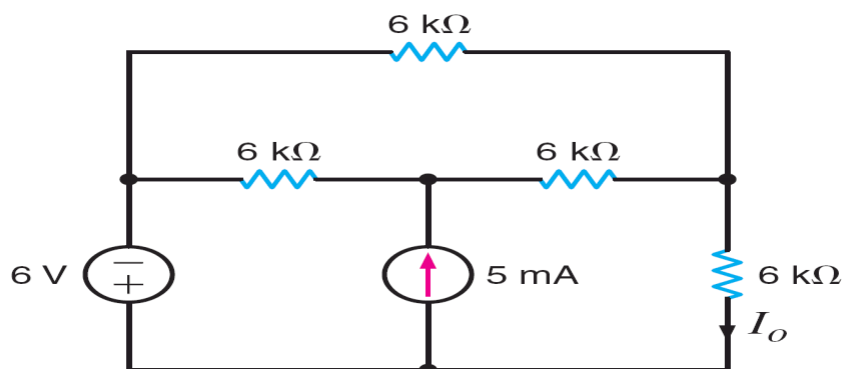

**Figure P3.71**

**SOLUTION:**

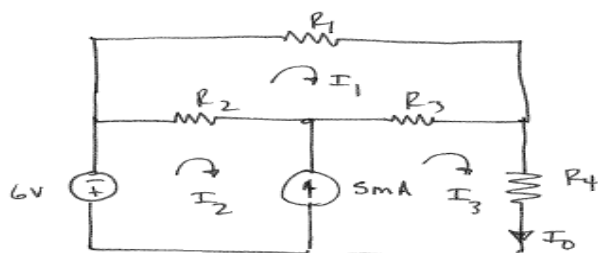3.71 Find  $I_o$  using loop analysis. Verify with MATLAB.



$$\text{All } R's = 6k\Omega$$

$$I_3 - I_2 = 5\text{mA}$$

$$I_o = I_3$$

$$I_1 R_1 + (I_1 - I_3) R_3 + (I_1 - I_2) R_2 = 0$$

$$6 + (I_2 - I_1) R_2 + (I_3 - I_1) R_3 + I_3 R_4 = 0$$

$$I_3 = 0.4\text{mA}$$

$$I_o = 0.4\text{mA}$$

Format for MATLAB

$$I_1 (R_1 + R_2 + R_3) - R_2 I_2 - R_3 I_3 = 0$$

$$-I_1 (R_2 + R_3) + R_2 I_2 + I_3 (R_3 + R_4) = -6$$

$$-I_2 + I_3 = 5 \times 10^{-3}$$

$$\begin{bmatrix} 18 \times 10^3 & -6 \times 10^3 & -6 \times 10^3 \\ -12 \times 10^3 & +6 \times 10^3 & 12 \times 10^3 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -6 \\ 5 \times 10^{-3} \end{bmatrix}$$

Continued on the next page.

3\_71.txt

MATLAB WORK

Factor 1000 out of the resistance matrix.

EDU&gt; r=[18,-6,-6;-12,6,12;0,-0.001,0.001]

r =

18.0000	-6.0000	-6.0000
-12.0000	6.0000	12.0000
0	-0.0010	0.0010

EDU&gt; v=[0;-6;0.005]

v =


0
-6.0000
0.0050

EDU&gt; 0.001\*inv(r)\*v

ans =

-0.0014
-0.0046
0.0004


**3.72** Find  $V_o$  in the network in Fig. P3.72 using both mesh and nodal analysis. **PSV**

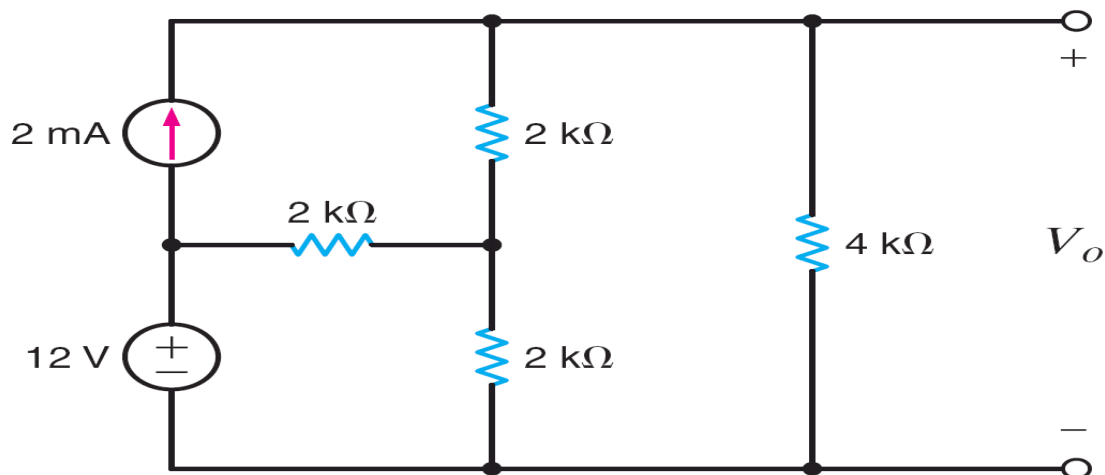

**Figure P3.72**

**SOLUTION:**

3.72 Find  $V_o$  using mesh & nodal.

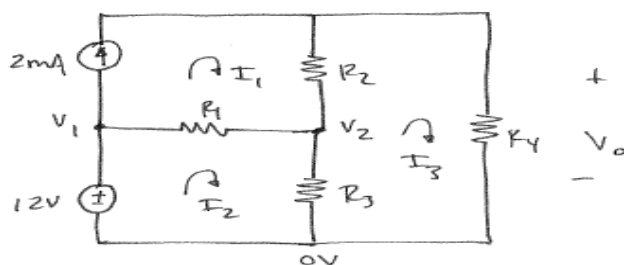

$$R_1 = R_2 = R_3 = 2 \text{ k}\Omega$$

$$R_4 = 4 \text{ k}\Omega$$

Mesh

$$I_1 = 2 \text{ mA}$$

$$12 = (I_2 - I_1) R_1 + (I_2 - I_3) R_3$$

$$0 = (I_3 - I_2) R_3 + (I_3 - I_1) R_2 + I_3 R_4$$

$$V_o = R_4 I_3$$

$$I_3 = 1.71 \text{ mA}$$

$$V_o = 6.86 \text{ V}$$

Nodal

$$V_1 = 12 \text{ V}$$

$$2 \times 10^{-3} = \frac{V_o - V_2}{R_2} + \frac{V_o}{R_4}$$


$$\frac{V_o - V_2}{R_2} + \frac{V_1 - V_2}{R_1} + \frac{0 - V_2}{R_3} = 0$$

$$V_o = 6.86 \text{ V}$$



**3.73** Use loop analysis to find  $I_o$  in the network in Fig. P3.73.


**CS**

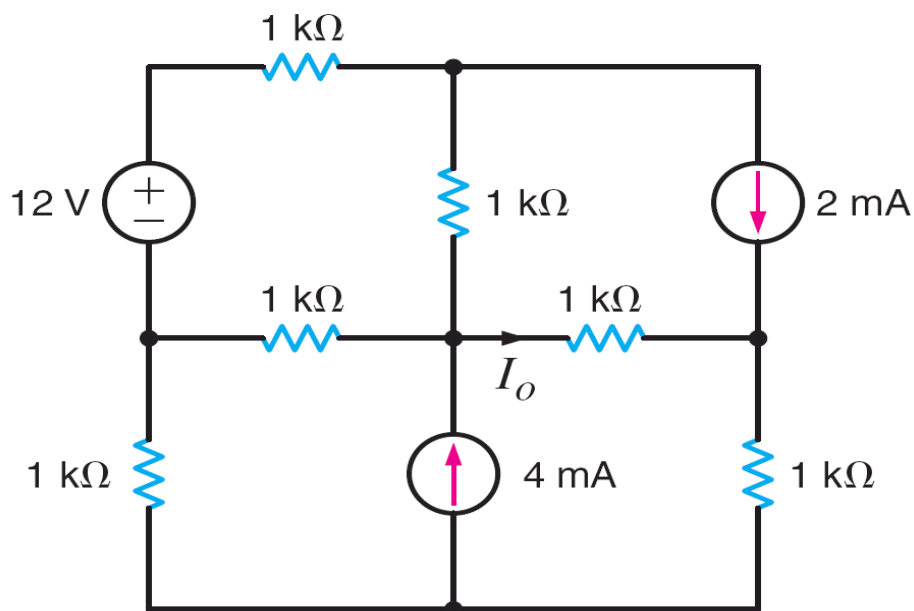

**Figure P3.73**

**SOLUTION:**

3.73 Use loop to find  $I_o$ .

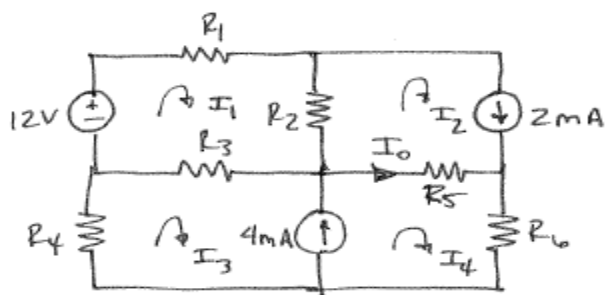

all  $R$ 's =  $1k\Omega$

$$I_2 = 2\text{mA}$$

$$I_4 - I_3 = 4\text{mA}$$

$$I_o = I_4 - I_2$$

$$12 = I_1 R_1 + R_2 (I_1 - I_2) + R_3 (I_1 - I_3)$$


$$0 = I_3 R_4 + R_3 (I_3 - I_1) + R_5 (I_4 - I_2) + I_4 R_6$$

$$I_4 = 3.64\text{mA}$$

$$I_o = 1.64\text{mA}$$

**3.74** Find  $I_o$  in the circuit in Fig. P3.74.


**CS**

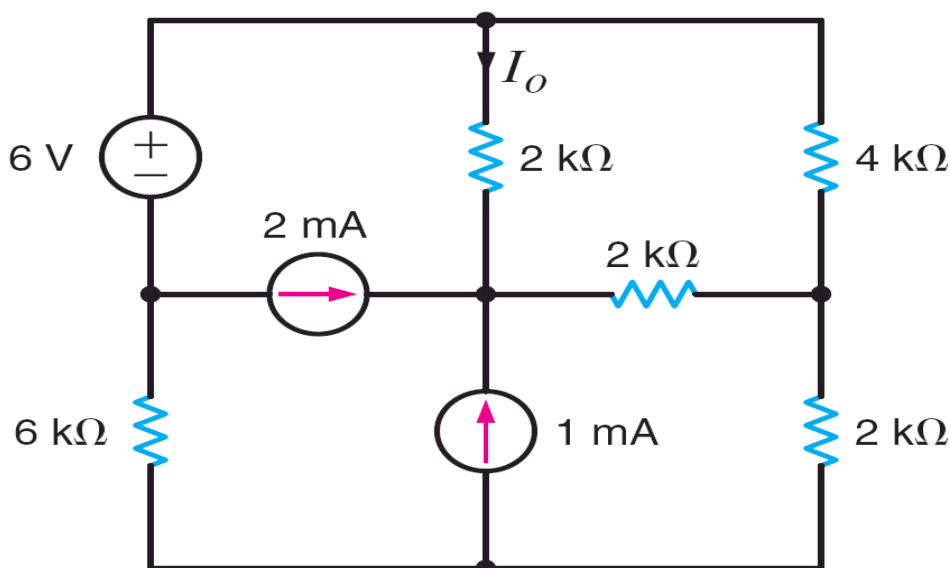

**Figure P3.74**

**SOLUTION:**

3.74 Find  $I_o$

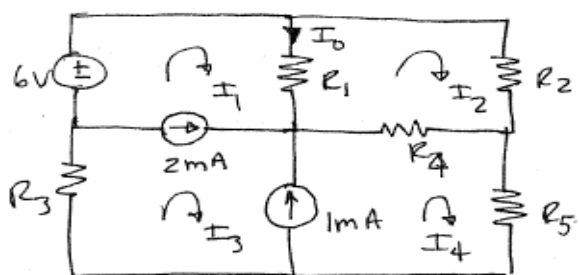

$$R_1 = R_5 = R_4 = 2\text{ k}\Omega$$

$$R_2 = 4\text{ k}\Omega \quad R_3 = 6\text{ k}\Omega$$

$$I_3 - I_1 = 2\text{ mA}$$

$$I_4 - I_3 = 1\text{ mA}$$

$$I_2 R_2 + (I_2 - I_4) R_4 + (I_2 - I_1) R_1 = 0$$

$$6 = I_2 R_2 + I_4 R_5 + I_3 R_3$$

$$I_o = I_1 - I_2$$

$$I_1 = -1.5\text{ mA}$$


$$I_2 = 0\text{ A}$$

$$I_o = -1.5\text{ mA}$$

### 3.75 Solve Problem 3.33 using loop analysis.

SOLUTION:

3.75 Find  $V_o$  by loop analysis.

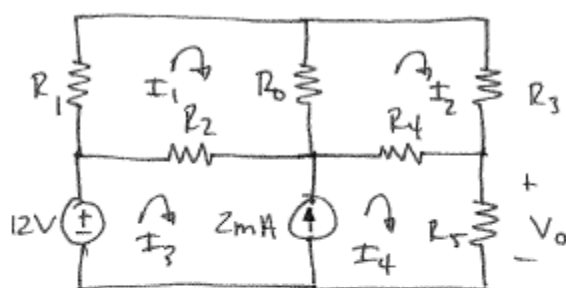

$$R_1 = R_3 = R_4 = R_5 = 1\text{ k}\Omega$$

$$R_2 = R_6 = 2\text{ k}\Omega$$

$$V_o = I_4 R_5$$

$$I_4 - I_3 = 2\text{ mA}$$

$$I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_2 = 0$$

$$I_2 R_3 + (I_2 - I_4) R_4 + (I_2 - I_1) R_2 = 0$$

$$12 = (I_3 - I_1) R_2 + (I_4 - I_2) R_4 + I_4 R_5$$


$$I_4 = 6.17\text{ mA}$$

$$V_o = 6.17\text{ V}$$

### 3.76 Solve Problem 3.34 using loop analysis.

SOLUTION:

3.76 Find  $V_o$  by loop analysis.

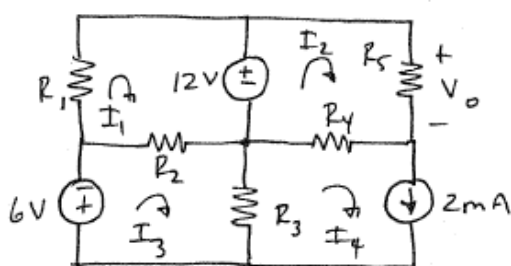

$$R_1 = R_2 = R_3 = 1\text{ k}\Omega \quad R_4 = R_5 = 2\text{ k}\Omega$$

$$I_4 = 2\text{ mA} \quad V_o = I_2 R_5$$

$$6 + (I_3 - I_1) R_2 + (I_3 - I_4) R_3 = 0$$

$$I_1 R_1 + (I_1 - I_3) R_2 + 12 = 0$$

$$I_2 R_5 + (I_2 - I_4) R_4 = 12$$


$$I_2 = 4\text{ mA}$$

$$V_o = 8\text{ V}$$

### 3.77 Solve Problem 3.35 using loop analysis.

SOLUTION:

3.77 Find  $V_o$  using loop analysis.

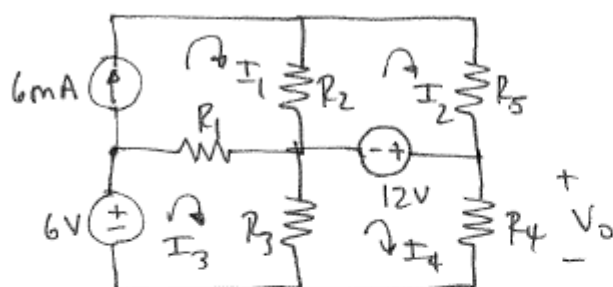

$$R_1 = R_2 = R_3 = 1\text{ k}\Omega$$

$$R_4 = R_5 = 2\text{ k}\Omega$$

$$I_1 = 6\text{ mA}$$

$$I_4 R_4 = V_o$$

$$6 = (I_3 - I_1)R_1 + (I_3 - I_4)R_3$$

$$-12 = (I_2 - I_1)R_2 + I_2 R_5$$

$$12 = I_4 R_4 + (I_4 - I_3)R_3$$


$$I_4 = 7.2\text{ mA}$$

$$V_o = 14.4\text{ V}$$

### 3.78 Solve Problem 3.37 using loop analysis.

SOLUTION:

3.78 Find  $V_o$  by loop analysis.

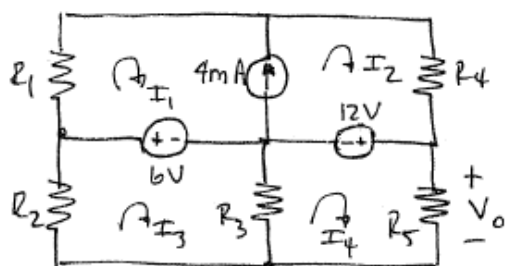

$$R_1 = R_2 = 2\text{ k}\Omega \quad R_3 = R_4 = R_5 = 1\text{ k}\Omega$$

$$V_o = I_4 R_5$$

$$I_2 - I_1 = 4\text{ mA}$$

$$-6 = R_3 (I_3 - I_4) + R_2 (I_3)$$

$$6 = I_1 R_1 + I_2 R_4 + 12$$

$$12 = I_4 R_5 + (I_4 - I_3) R_3$$


$$I_4 = 6\text{ mA}$$

$$V_o = 6\text{ V}$$

### 3.79 Solve Problem 3.40 using loop analysis.

SOLUTION:

3.79 Find  $V_o$  by loop analysis.

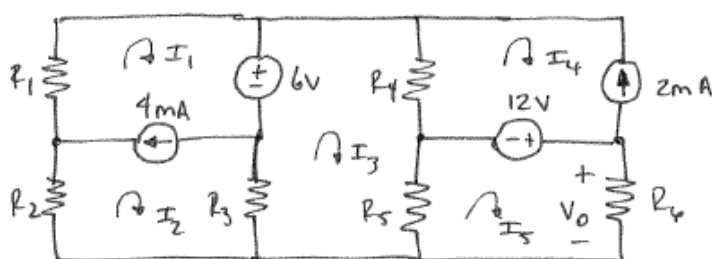

$$R_1 = R_2 = 2\text{ k}\Omega$$

$$R_3 = R_4 = R_5 = R_6 = 1\text{ k}\Omega$$

$$I_4 = -2\text{ mA}$$

$$I_1 - I_2 = 4\text{ mA}$$

$$-6 = R_3(I_2 - I_3) + I_2 R_2 + I_1 R_1$$

$$6 = R_4(I_3 - I_4) + R_5(I_3 - I_5) + R_3(I_3 - I_2)$$

$$12 = R_6 I_5 + R_5(I_5 - I_3)$$

$$V_o = I_5 R_6$$


$$I_5 = 7.57\text{ mA}$$

$$V_o = 7.57\text{ V}$$

### 3.80 Solve Problem 3.43 using loop analysis.

SOLUTION:

3.80 find  $I_o$  using loop analysis.

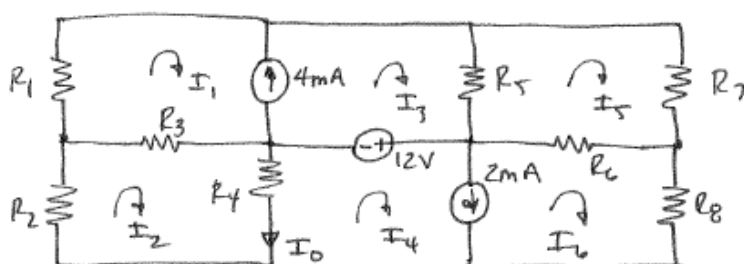

all  $R$ 's =  $1\text{ k}\Omega$

$$I_3 - I_1 = 4\text{ mA}$$

$$I_4 - I_6 = 2\text{ mA}$$

$$I_o = I_2 - I_4$$

$$0 = I_2 R_2 + (I_2 - I_1) R_3 + (I_2 - I_4) R_4$$

$$0 = I_5 R_7 + (I_5 - I_6) R_6 + (I_5 - I_3) R_5$$

$$-12 = I_1 R_1 + (I_3 - I_5) R_5 + (I_1 - I_2) R_3$$

$$12 = (I_6 - I_5) R_6 + I_6 R_8 + I_2 R_2 + (I_2 - I_1) R_3$$


$$I_2 = 267\text{ }\mu\text{A}$$

$$I_4 = 5.74\text{ mA}$$

$$I_o = -5.47\text{ mA}$$




**3.81** Use MATLAB to find the mesh currents in the network in Fig. P3.81. **CS**

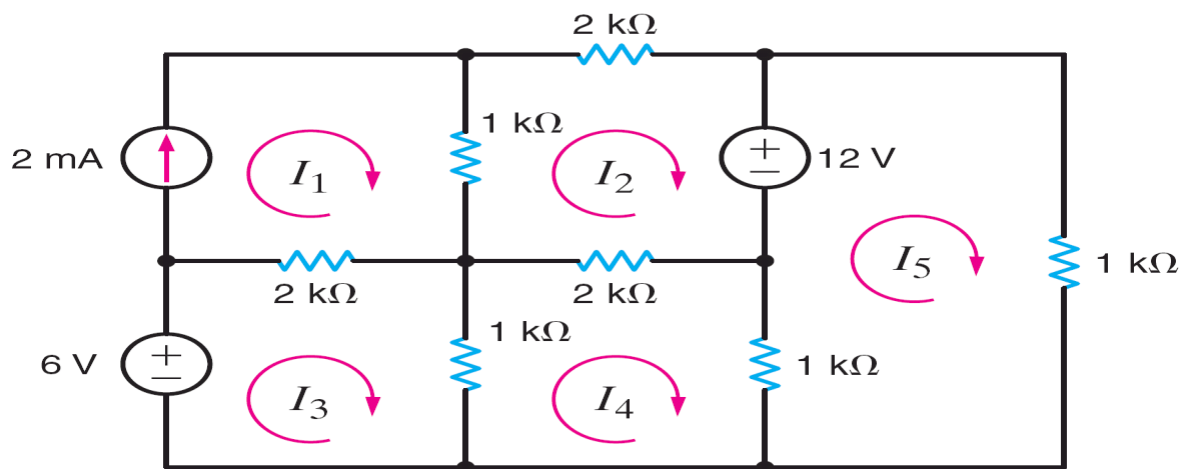

**Figure P3.81**

**SOLUTION:**

3.81 Find mesh currents using MATLAB.

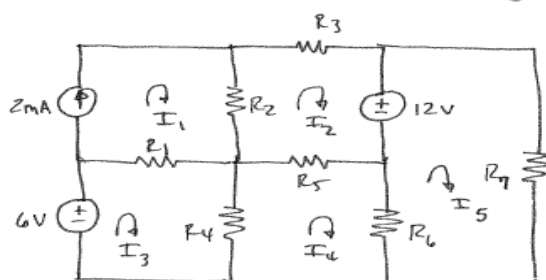

$$R_1 = R_3 = R_5 = 2 \text{ k}\Omega$$

$$R_2 = R_4 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_1 = 2 \text{ mA}$$

$$0 = (I_3 - I_1)R_1 + (I_3 - I_4)R_4$$

$$0 = (I_4 - I_3)R_4 + (I_4 - I_2)R_5 + (I_4 - I_5)R_6$$

$$-12 = I_2 R_3 + (I_2 - I_4)R_5 + (I_2 - I_1)R_2$$

$$12 = I_5 R_7 + (I_5 - I_4)R_6$$

In matrix form,

$$\begin{bmatrix} -2000 & 0 & 3000 & -1000 & 0 \\ 0 & -2000 & -1000 & 4000 & -1000 \\ -1000 & 5000 & 0 & -2000 & 0 \\ 0 & 0 & 0 & -1000 & 2000 \\ 1 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ -12 \\ 12 \\ 2 \times 10^{-3} \end{bmatrix}$$

Continued on the next page.

```
3_81.txt

MATLAB WORK

r*i = v

EDU>
r=[-2000,0,3000,-1000,0;0,-2000,-1000,4000,-1000;-1000,5000,0,-2000,0;0,0,0,-1000,20
00;1,0,0,0,0]

r =

    -2000         0     3000    -1000         0
         0    -2000    -1000     4000    -1000
   -1000     5000         0    -2000         0
         0         0         0    -1000     2000
         1         0         0         0         0

EDU> v=[6;0;-12;12;0.002]

v =


    6.0000
         0
   -12.0000
    12.0000
     0.0020

EDU> i=1000*inv(r)*v

i =

    2.0000
   -1.0986
    4.0845
    2.2535
    7.1268
```


**3.82** Write mesh equations for the circuit in Fig. P3.82 using the assigned currents.

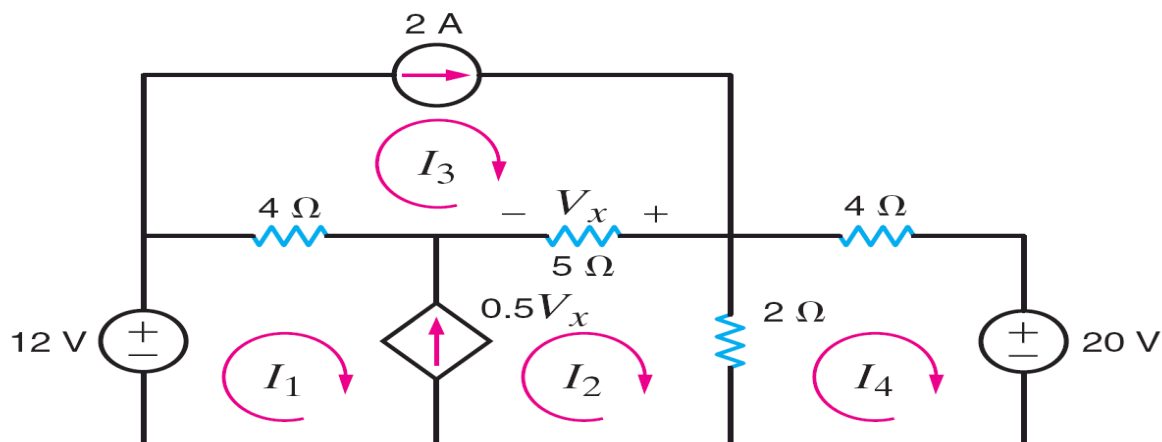

**Figure P3.82**

SOLUTION:

3.82 Write mesh equations.

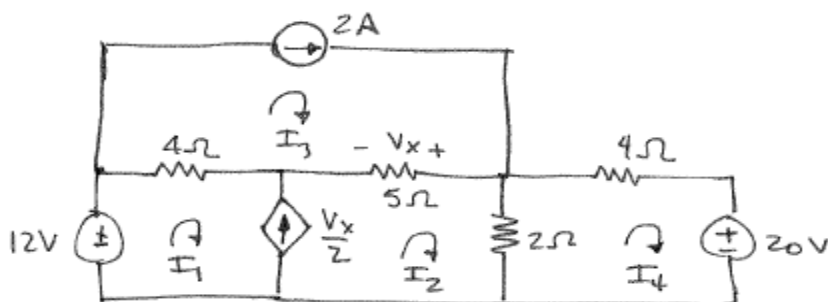

$$V_x = (I_3 - I_2) 5$$

①  $I_3 = 2 \text{ A}$

$$I_2 - I_1 = \frac{V_x}{2} = \frac{(I_3 - I_2) 5}{2}$$


②  $3.5 I_2 - I_1 - 2.5 I_3 = 0$

③  $4 I_4 + 2(I_4 - I_2) = -20$

④  $(I_1 - I_3) 4 + (I_2 - I_3) 5 + 2 I_2 = 12$

**3.83** Use mesh analysis to find  $V_o$  in the circuit in Fig. P3.83.


**PSV**

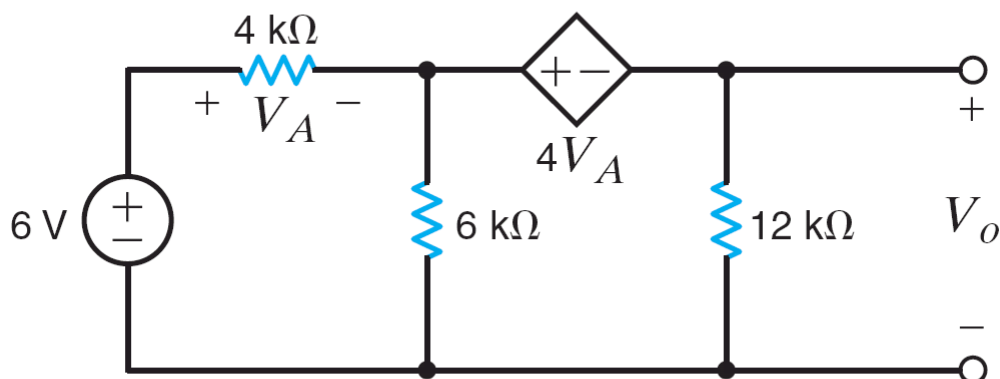

**Figure P3.83**

**SOLUTION:**

3.83 Find  $V_o$  using mesh analysis.

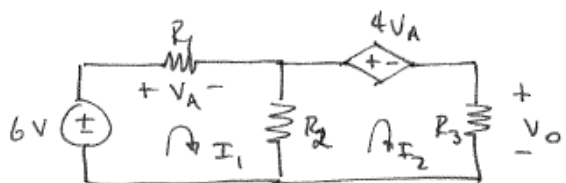

$$R_1 = 4\text{ k}\Omega \quad R_2 = 6\text{ k}\Omega \quad R_3 = 12\text{ k}\Omega$$

$$V_A = I_1 R_1 \quad V_o = I_2 R_3$$

$$6 = I_1 R_1 + (I_1 - I_2) R_2$$

$$I_2 R_3 + (I_2 - I_1) R_2 + 4V_A = 0$$

$$6 = I_1 (R_1 + R_2) - I_2 R_2$$


$$I_2 (R_2 + R_3) + I_1 (4R_1 - R_2) = 0$$

$$I_2 = -0.25\text{ mA}$$

$$V_o = -3\text{ V}$$

**3.84** Find  $V_o$  in the circuit in Fig. P3.84 using mesh analysis.


**CS**

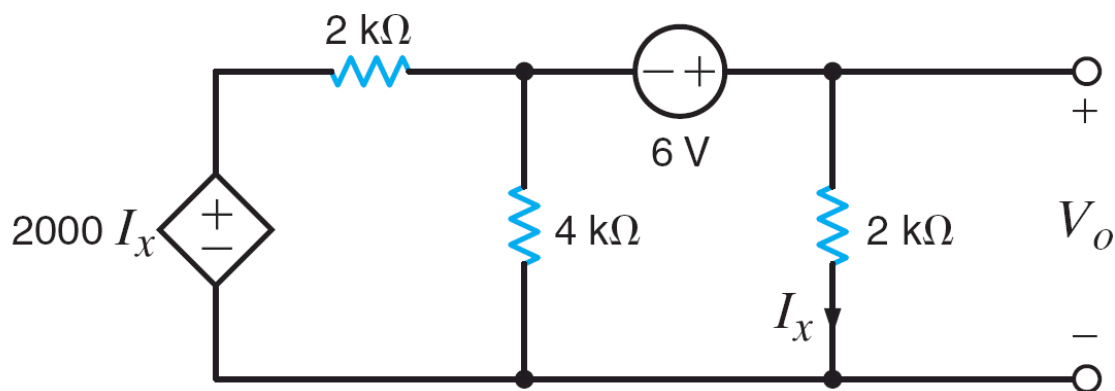

**Figure P3.84**

**SOLUTION:**

3.84 Find  $V_o$  using mesh analysis.

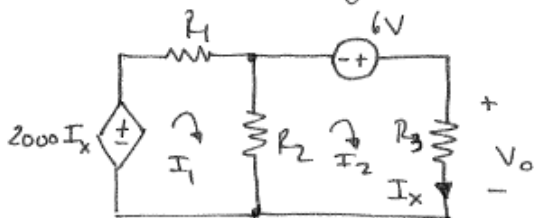

$$R_1 = 2 \text{ k}\Omega \quad R_2 = 4 \text{ k}\Omega \quad R_3 = 2 \text{ k}\Omega$$

$$I_x = I_2 \quad V_o = R_3 I_2$$


$$2000 I_x = I_1 R_1 + (I_1 - I_2) R_2$$

$$6 = I_2 R_3 + (I_2 - I_1) R_2$$

$$I_2 = 3 \text{ mA}$$

$$V_o = 6 \text{ V}$$


**3.85** Use loop analysis to find  $V_o$  in the network in Fig. P3.85.

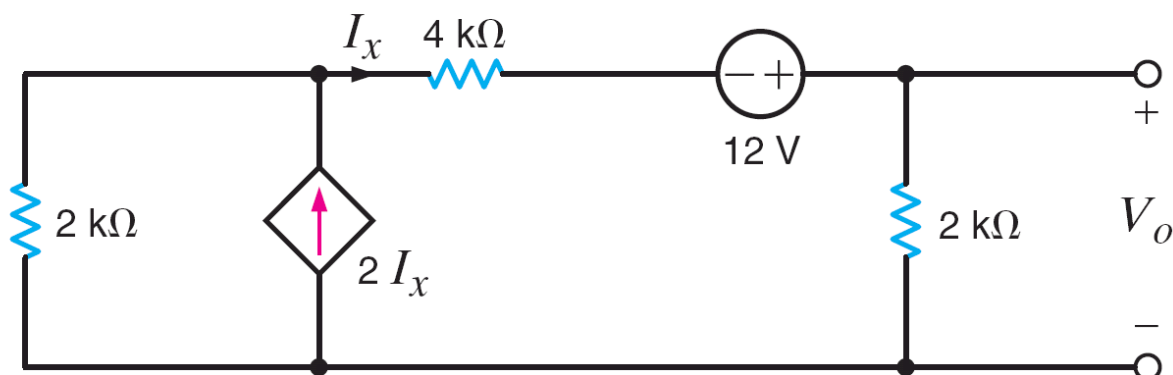

**Figure P3.85**

SOLUTION:

3.85 Find  $V_o$  using loop analysis.

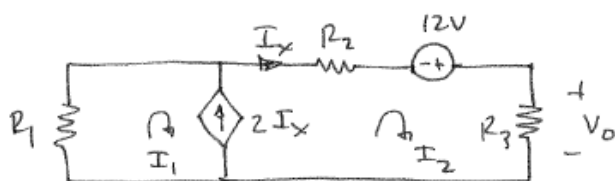

$$R_1 = 2\text{ k}\Omega \quad R_2 = 4\text{ k}\Omega \quad R_3 = 2\text{ k}\Omega$$

$$I_x = I_2 \quad V_o = R_3 I_2$$


$$I_1 R_1 + I_2 R_2 + I_2 R_3 = 12$$

$$2I_x = I_2 - I_1$$

$$I_2 = 3\text{ mA}$$

$$V_o = 6\text{ V}$$


**3.86** Use loop analysis to find  $V_o$  in the circuit in Fig. P3.86.

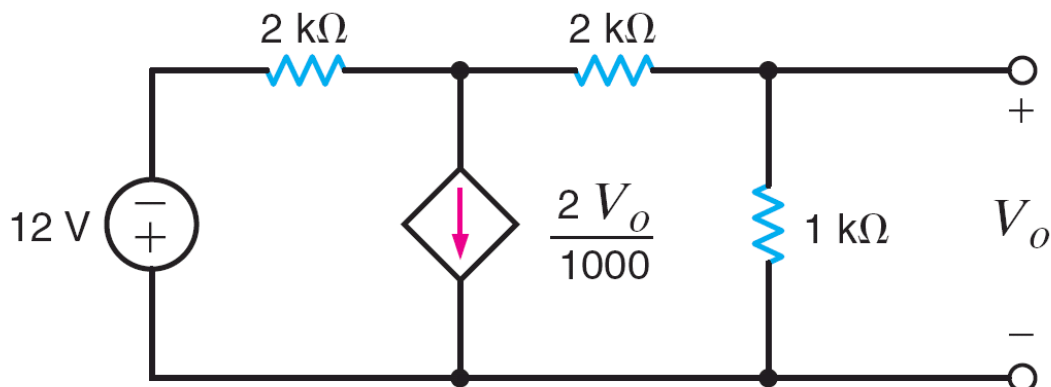

**Figure P3.86**

**SOLUTION:**

3.86 Find  $V_o$  using loop analysis.

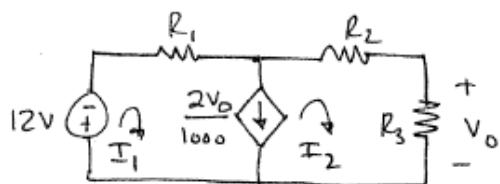

$$R_1 = 2\text{ k}\Omega \quad R_2 = 2\text{ k}\Omega \quad R_3 = 1\text{ k}\Omega$$

$$V_o = R_3 I_2$$


$$\frac{2V_o}{1000} = I_1 - I_2$$

$$-12 = I_1 R_1 + I_2 R_2 + I_2 R_3$$

$$I_2 = -1.33\text{ mA}$$

$$V_o = -1.33\text{ V}$$


**3.87** Use both nodal analysis and mesh analysis to find  $V_o$  in the circuit in Fig. P3.87.

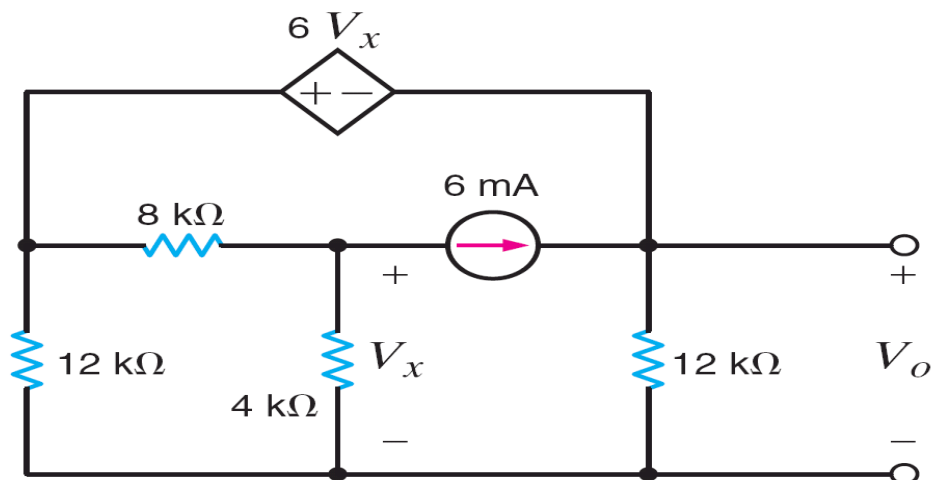

**Figure P3.87**

**SOLUTION:**

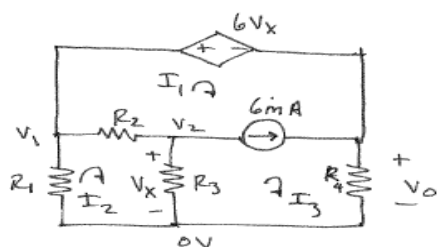3.87 Use both nodal & mesh to find  $V_o$ .



$$R_1 = 12 \text{ k}\Omega \quad R_2 = 8 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega \quad R_4 = 12 \text{ k}\Omega$$

Mesh

$$I_3 - I_1 = 6 \text{ mA}$$

$$6V_x + R_4 I_3 + R_1 I_2 = 0$$

$$0 = I_2 R_2 + (I_2 - I_1) R_2 + (I_2 - I_3) R_3$$

$$V_x = (I_2 - I_3) R_3$$

$$V_o = I_3 R_4$$

$$I_3 = 12 \text{ mA}$$

$$V_o = 144 \text{ V}$$

Nodal

$$V_1 - V_o = 6V_x$$

$$V_x = V_2$$


$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + 6 \times 10^{-3} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_3} + \frac{V_o}{R_4} = 0$$

$$V_o = 144 \text{ V}$$




**3.88** Using mesh analysis, find  $V_o$  in the circuit in Fig. P3.88.

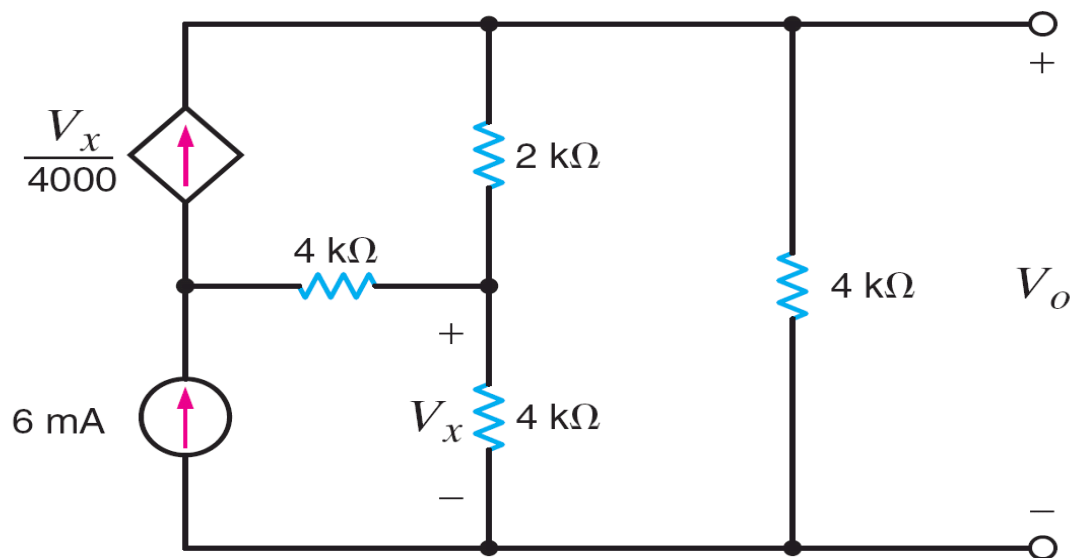

**Figure P3.88**

**SOLUTION:**

3.88 find  $V_o$  using mesh analysis.

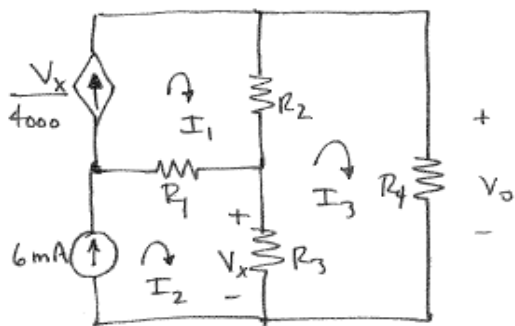

$$R_1 = R_3 = R_4 = 4 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega$$

$$V_x = R_3 (I_2 - I_3)$$

$$V_o = R_4 I_3$$

$$I_2 = 6 \text{ mA}$$


$$\frac{V_x}{4000} = I_1$$

$$0 = I_3 R_4 + (I_3 - I_1) R_2 + (I_3 - I_2) R_3$$

$$I_3 = 3 \text{ mA}$$

$$V_o = 12 \text{ V}$$


**3.89** Find  $V_o$  in the network in Fig. P3.89. **PSV**

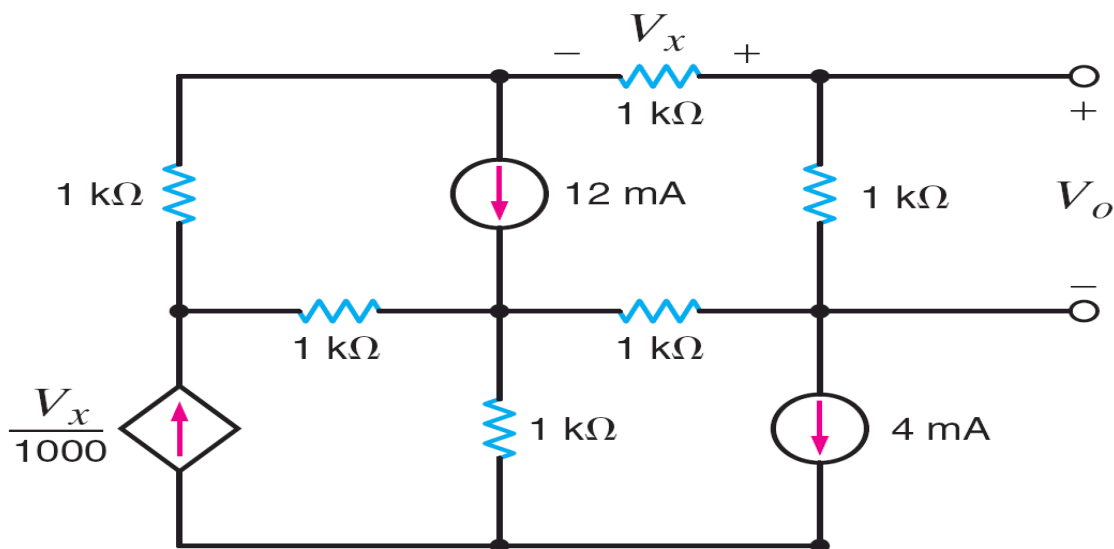

**Figure P3.89**

**SOLUTION:**

3.89 find  $V_o$ .

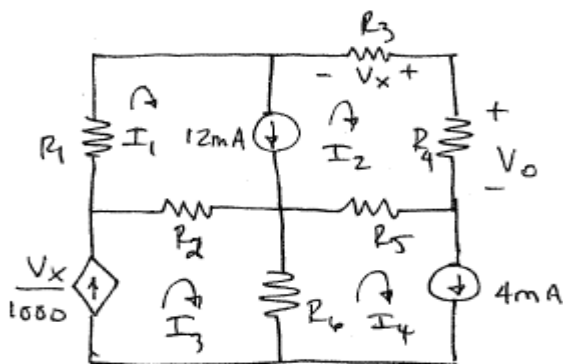

All  $R$ 's =  $1k\Omega$

$$I_4 = 4\text{mA}$$

$$I_1 - I_2 = 12\text{mA}$$

$$\frac{V_x}{1000} = I_3 \quad V_x = -I_2 R_3$$

$$0 = I_1 R_1 + I_2 R_3 + I_2 R_4 + (I_2 - I_4) R_5 + (I_1 - I_3) R_2$$

$$V_o = I_2 R_4$$


$$I_2 = -3.33\text{mA}$$

$$V_o = -3.33\text{V}$$

### 3.90 Solve Problem 3.54 using loop analysis.

SOLUTION:

3.90 Find  $V_o$  by loop analysis.

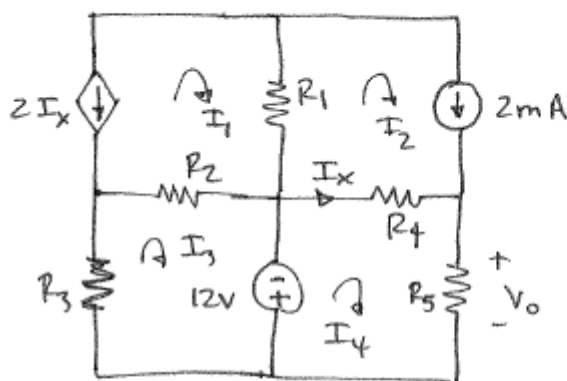

all  $R$ 's =  $1\text{ k}\Omega$

$$I_2 = 2\text{ mA}$$

$$2I_x = -I_1$$

$$I_x = I_4 - I_2$$

$$V_o = I_4 R_5$$

$$12 = I_3 R_3 + (I_3 - I_1) R_2$$

$$-12 = I_4 R_5 + (I_4 - I_2) R_4$$


$$I_4 = -5\text{ mA}$$

$$V_o = -5\text{ V}$$

### 3.91 Solve Problem 3.55 using loop analysis.

SOLUTION:

3.91 Find  $V_o$  using loop analysis.

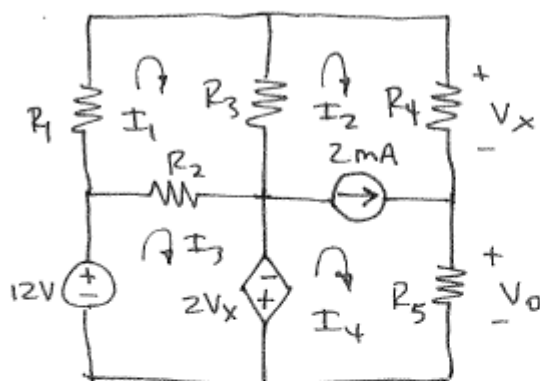

$$R_1 = R_2 = 2\text{ k}\Omega$$

$$R_3 = R_4 = R_5 = 1\text{ k}\Omega$$

$$I_4 - I_2 = 2\text{ mA}$$

$$V_o = I_4 R_5$$

$$V_x = R_4 I_2$$

$$12 = I_3 R_2 - 2V_x$$

$$0 = I_1 R_1 + (I_1 - I_2) R_3 + (I_1 - I_3) R_2$$

$$12 = I_1 R_1 + I_2 R_4 + I_4 R_5$$


$$I_4 = 2.5\text{ mA}$$

$$V_o = 2.5\text{ V}$$

### 3.92 Solve Problem 3.56 using loop analysis.

SOLUTION:

3.92 Find  $V_o$  using loop analysis.

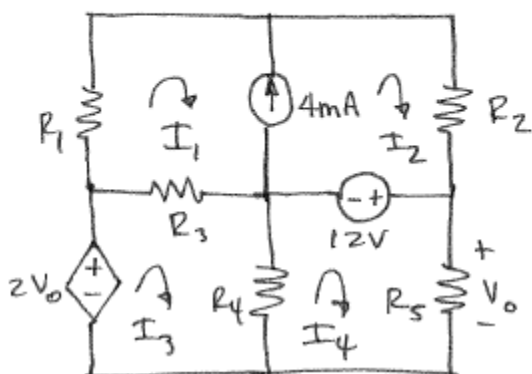

$$R_1 = R_2 = R_3 = R_4 = 1\text{ k}\Omega$$

$$R_5 = 2\text{ k}\Omega$$

$$I_2 - I_1 = 4\text{ mA}$$

$$V_o = R_5 I_4$$

$$2V_o = (I_3 - I_1)R_3 + (I_3 - I_4)R_4$$

$$12 = I_4 R_5 + (I_4 - I_3)R_4$$

$$+2V_o = I_1 R_1 + I_2 R_2 + I_4 R_5$$


$$I_4 = \infty$$

$$V_o = \infty\text{ V}$$

### 3.93 Solve Problem 3.57 using loop analysis.

SOLUTION:

3.93 Find  $v_o$  using loop analysis.

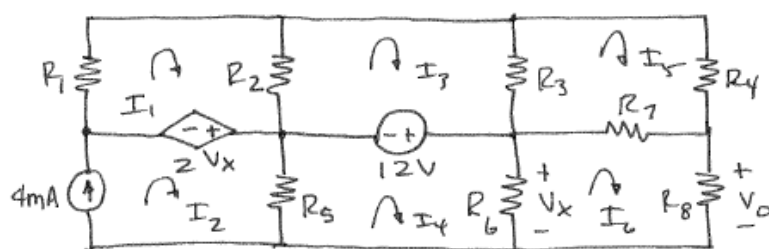

$$R_1 = R_2 = R_3 = R_4 = R_8 = 1\text{ k}\Omega$$

$$R_5 = R_6 = R_7 = 2\text{ k}\Omega$$

$$v_o = R_8 I_6$$

$$I_2 = 4\text{ mA}$$

$$I_1 R_1 + (I_1 - I_3) R_2 + 2V_x = 0 \quad V_x = (I_4 - I_6) R_6$$

$$12 = (I_4 - I_6) R_6 + (I_4 - I_2) R_5$$

$$-12 = (I_3 - I_1) R_2 + (I_3 - I_5) R_3$$

$$0 = I_5 R_4 + (I_5 - I_6) R_7 + (I_5 - I_3) R_3$$

$$0 = I_6 R_8 + (I_6 - I_4) R_6 + (I_6 - I_5) R_7$$


$$I_6 = 500\text{ }\mu\text{A}$$

$$v_o = 0.5\text{ V}$$

### 3.94 Solve Problem 3.58 using loop analysis.

SOLUTION:

3.94 Find  $I_o$  using loop analysis.

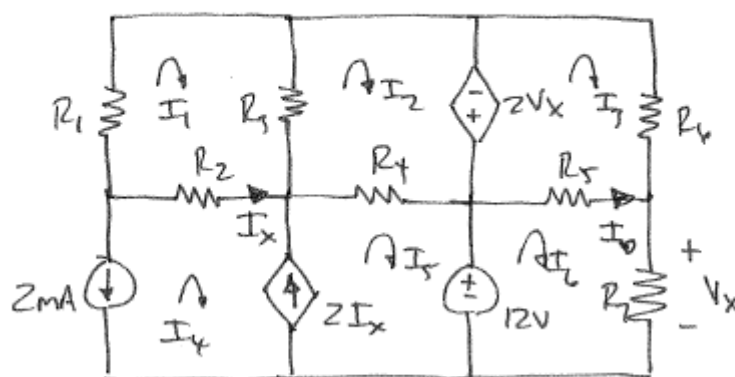

$$\text{All } R's = 1k\Omega$$

$$I_4 = -2\text{mA}$$

$$I_5 - I_4 = 2I_x$$

$$I_x = I_4 - I_1$$

$$I_o = I_6 - I_3$$

$$0 = I_1 R_1 + (I_1 - I_2) R_3 + R_2 (I_1 - I_4)$$

$$2V_x = (I_2 - I_5) R_4 + (I_2 - I_1) R_3$$

$$V_x = I_6 R_7$$

$$-2V_x = I_3 R_6 + (I_3 - I_6) R_5$$


$$12 = (I_6 - I_3) R_5 + I_6 R_7$$

$$I_o = 7.2\text{mA}$$

### 3.95 Solve Problem 3.59 using loop analysis.

SOLUTION:

3.95 Find  $I_o$  using loop analysis

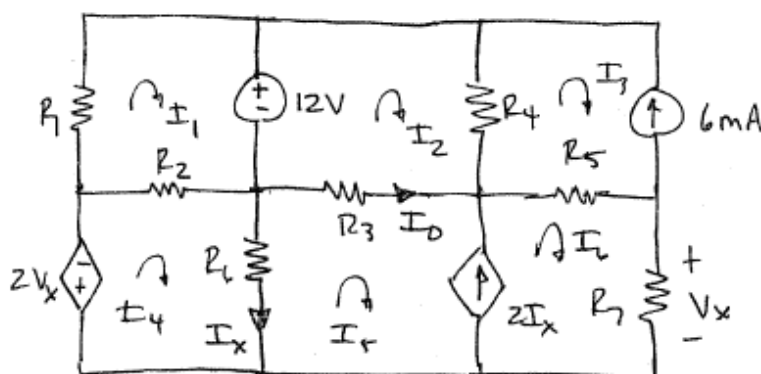

$$\text{All } R\text{'s} = 1\text{k}\Omega$$

$$I_3 = -6\text{mA}$$

$$2I_x = I_6 - I_5$$

$$I_x = I_4 - I_5$$

$$I_o = I_5 - I_2$$

$$V_x = I_6 R_7$$

$$-2V_x = (I_4 - I_1)R_2 + (I_4 - I_5)R_6$$

$$-12 = I_1 R_1 + (I_1 - I_4) R_2$$


$$12 = (I_2 - I_3) R_4 + (I_2 - I_5) R_3$$

$$0 = (I_5 - I_4) R_6 + (I_5 - I_2) R_3 + (I_6 - I_3) R_5 + I_6 R_7$$

$$\boxed{I_o = -2.88\text{mA}}$$




**3.96** Use mesh analysis to determine the power delivered by the independent 3-V source in the network in Fig. P3.96.

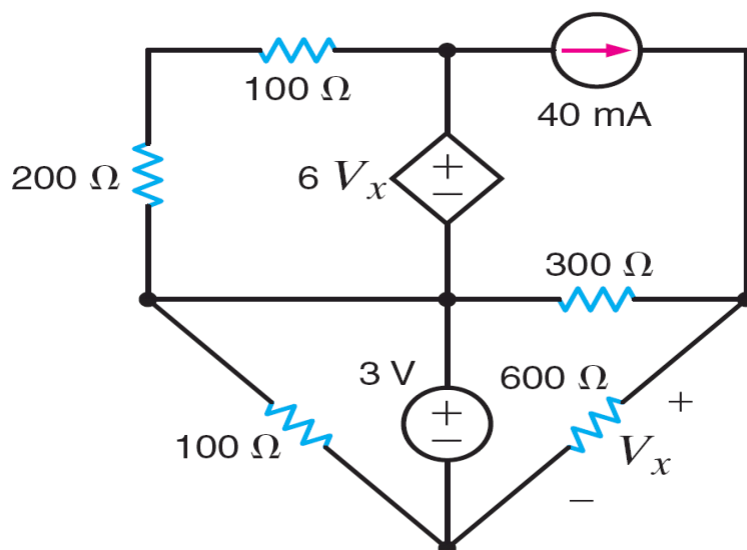

**Figure P3.96**

**SOLUTION:**

3.96 Find power delivered by 3-V source.

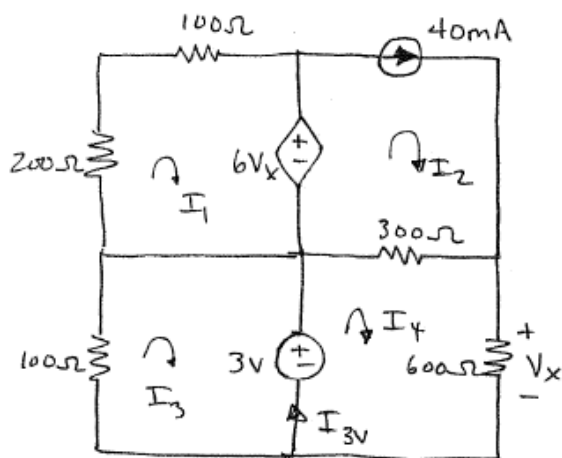

$$I_2 = 40 \text{ mA}$$

$$-6V_x = 300 I_1$$

$$V_x = 600 I_4$$

$$3 = 300 (I_4 - I_2) + 600 I_4$$


$$-3 = 100 I_3$$

$$I_{3V} = I_4 - I_3 = 46.67 \text{ mA}$$

$$P_{3V} = 3 I_{3V}$$

$$P_{3V} = 140 \text{ mW}$$


**3.97** Use mesh analysis to find the power delivered by the current-controlled voltage source in the circuit in Fig. P3.97.

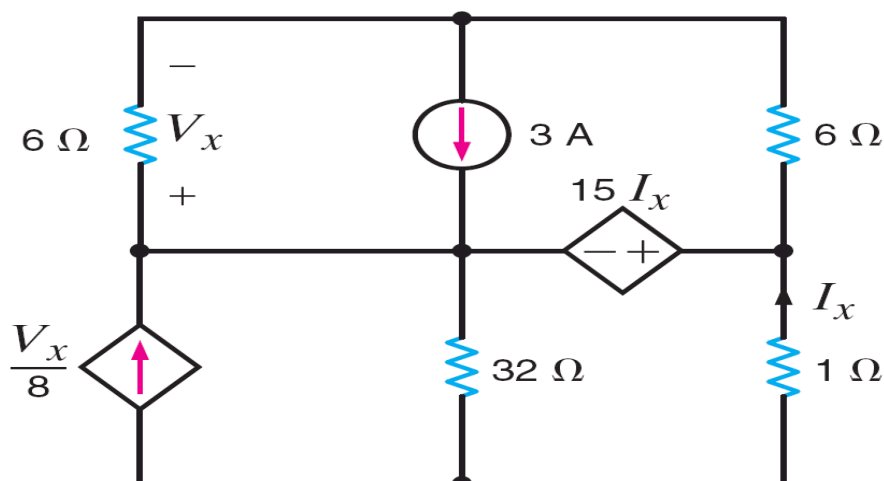

**Figure P3.97**

SOLUTION:

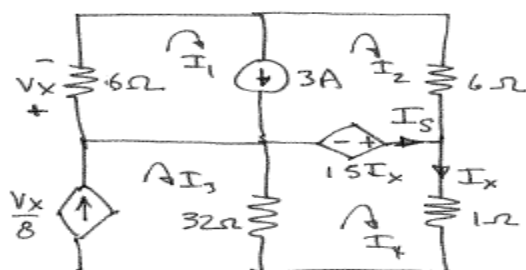3.97 Find power delivered by the voltage source.



$$I_1 - I_2 = 3$$

$$I_3 = V_x / 8$$

$$V_x = 6 I_1$$

$$I_x = I_4$$

$$I_5 = I_4 - I_2$$

$$15 I_x = I_4 + 32(I_4 - I_3)$$


$$-15 I_x = 6 I_1 + 6 I_2$$

$$I_4 = 2 \text{ A} \quad I_2 = 1 \text{ A} \quad I_5 = 1 \text{ A}$$

$$P_{ccvs} = (15 I_x) I_5 = 15 I_4 I_5$$

$$P_{ccvs} = 30 \text{ W}$$


**3FE-1** Find  $V_o$  in the circuit in Fig. 3PFE-1. CS

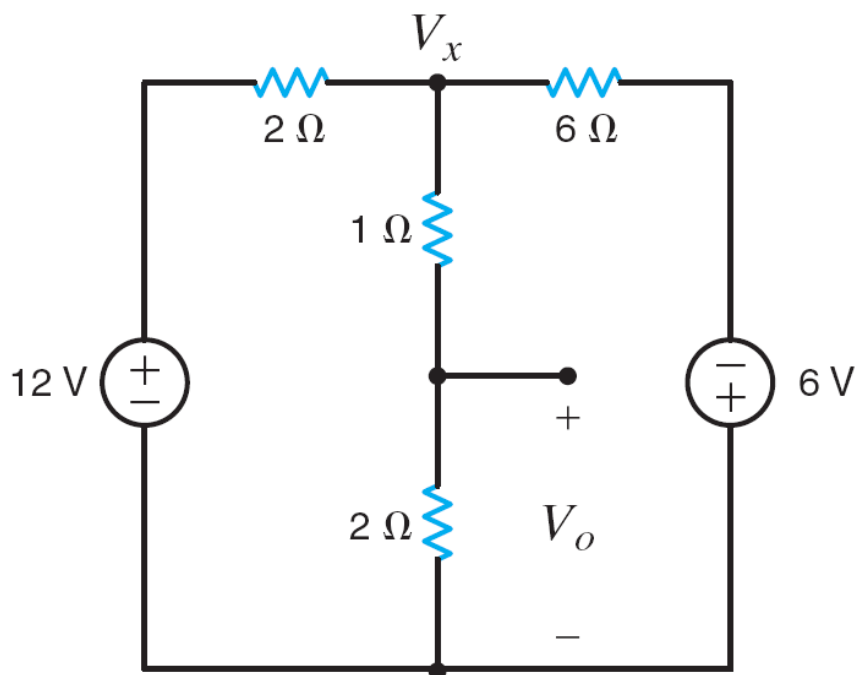

**Figure 3PFE-1**

### SOLUTION

3FE-1 Find  $V_o$ .

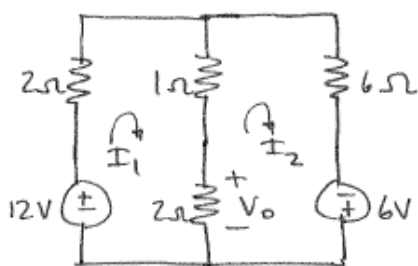

$$12 = 2I_1 + (I_1 - I_2) + 2(I_1 - I_2)$$


$$6 = 2(I_2 - I_1) + (I_2 - I_1) + 6I_2$$

$$V_o = 2(I_1 - I_2)$$

Results:  $I_1 = 3.5 \text{ A}$  ,  $I_2 = 1.83 \text{ A}$

$$V_o = 3.33 \text{ V}$$


**3FE-2** Determine the power dissipated in the 6-ohm resistor in the network in Fig. 3PFE-2.

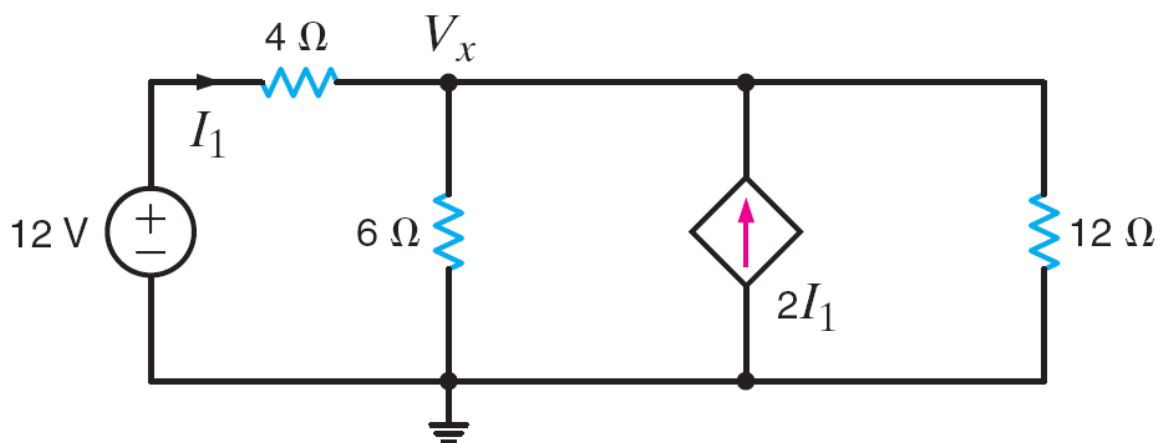

**Figure 3PFE-2**

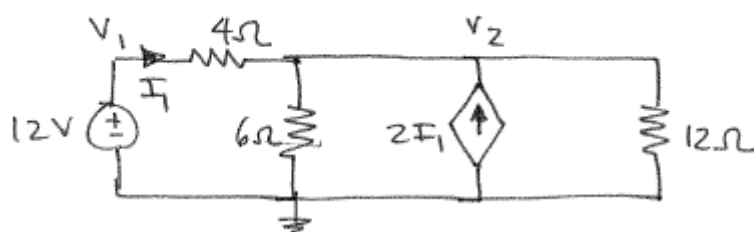**SOLUTION**

3FE-2 find power absorbed by 6-Ω resistor.



$$I_1 = (V_1 - V_2) / 4$$

$$V_1 = 12V$$


$$\frac{V_2}{6} + \frac{V_2}{12} + \frac{V_2 - V_1}{4} = 2I_1$$

Results:  $V_2 = 9V$

$$P_{6\Omega} = \frac{V_2^2}{6}$$

$$P_{6\Omega} = 13.5W$$


**3FE-3** Find the current  $I_x$  in the 4-ohm resistor in the circuit in Fig. 3PFE-3. **CS**

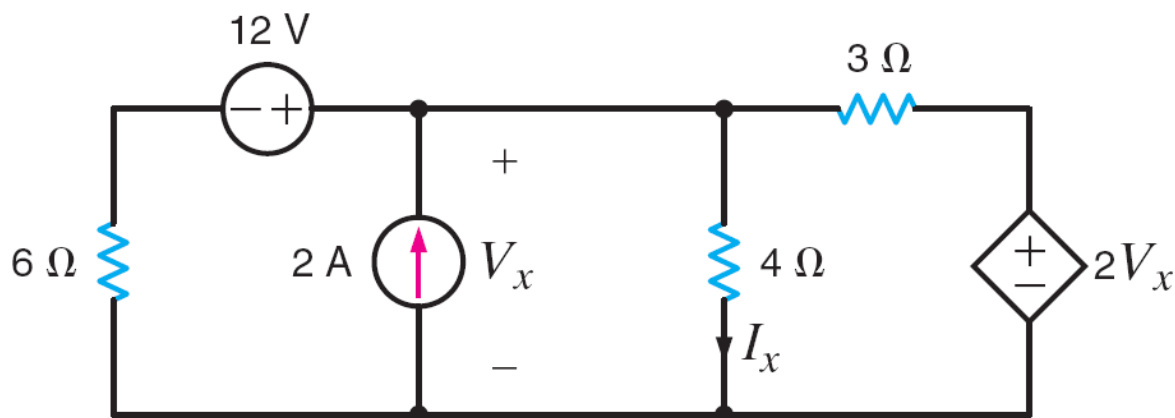

**Figure 3PFE-3**

**SOLUTION**

3FE-3 Find  $I_x$ .

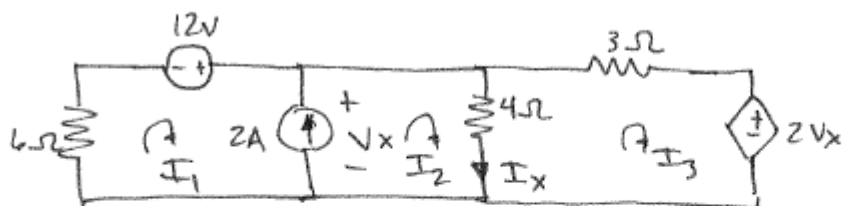

$$V_x = 4 I_x$$

$$I_x = I_2 - I_3$$

$$I_2 - I_1 = 2$$


$$12 = 4(I_2 - I_3) + 6I_1$$

$$-2V_x = 4(I_3 - I_2) + 3I_3$$

$$\text{Results: } I_2 = -4A, \quad I_3 = -16A$$

$$\boxed{I_x = 12A}$$


**3FE-4** Determine the voltage  $V_o$  in the circuit in Fig. 3PFE-4.

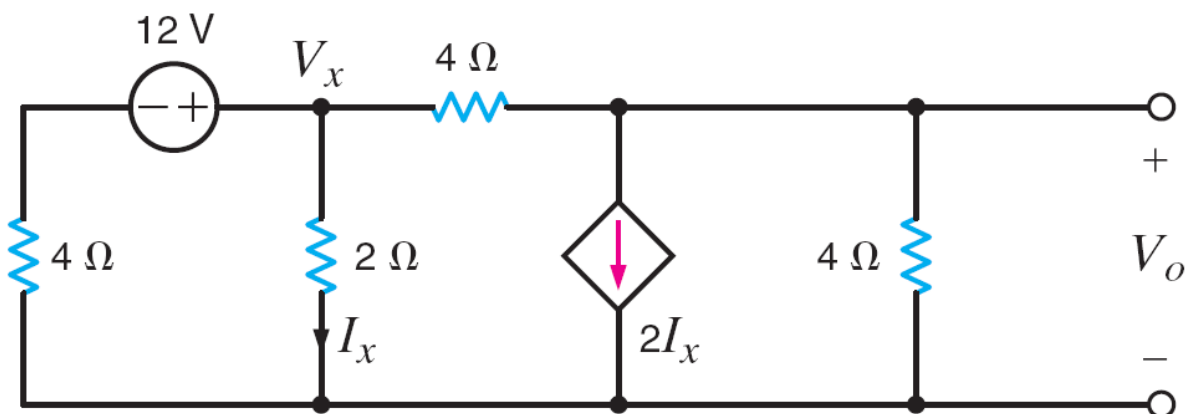

**Figure 3PFE-4**

**SOLUTION**

3FE-4 Find  $V_o$ .

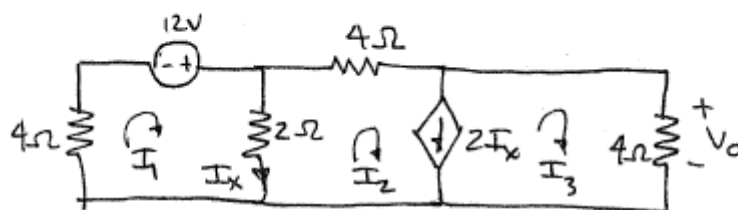

$$12 = 4I_1 + 2(I_1 - I_2)$$

Result:  $I_3 = -0.818\text{ A}$

$$I_x = I_1 - I_2$$

$$V_o = 4I_3$$

$$2I_x = I_2 - I_3$$

$$4I_1 + 4I_2 + 4I_3 = 12$$

$$V_o = -3.27\text{ V}$$