
 


# Chapter Twelve:

# Variable-Frequency Network Performance

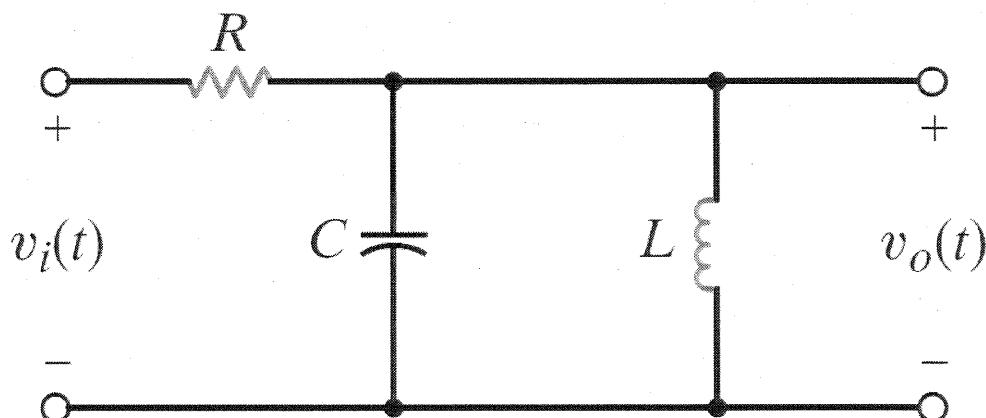


- 12.1** Determine the driving point impedance at the input terminals of the network shown in Fig. P12.1 as a function of  $s$ . **CS**



**Figure P12.1**

**SOLUTION:**

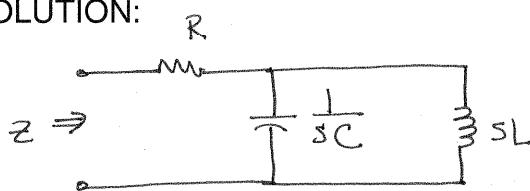

$$Z = R \left[ \frac{s^2 + \frac{1}{RC} + \frac{1}{LC}}{s^2 + \frac{1}{LC}} \right]$$

$$\begin{aligned} Z &= R + \frac{(sL)(1/sC)}{sL + 1/sC} \\ &= R + \frac{sL}{s^2LC + 1} = \frac{s^2LCR + R + sL}{s^2LC + 1} \end{aligned}$$

**12.2** Determine the voltage transfer function  $V_o(s)/V_i(s)$  as a function of  $s$  for the network shown in Fig. P12.2.

**P S V**

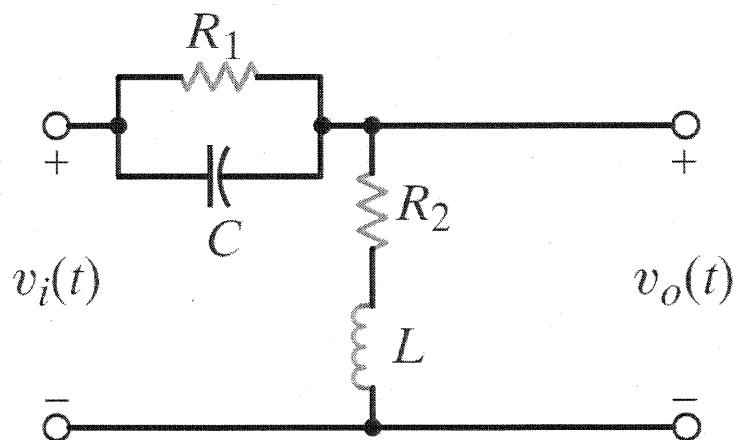


Figure P12.2

**SOLUTION:**

Let  $Z_1 = \frac{R_1 / sC}{R_1 + 1/sC} = \frac{R_1}{sR_1 C + 1}$

$Z_2 = sL + R_2$

$\frac{V_o(s)}{V_i(s)} = \frac{Z_2}{Z_1 + Z_2} = \frac{sL + R_2}{sL + R_2 + \frac{R_1}{sR_1 C + 1}}$

$$\frac{V_o(s)}{V_i(s)} = \frac{s^2 + s \left[ \frac{R_2}{L} + \frac{1}{R_1 C} \right] + \frac{R_2/R_1}{LC}}{s^2 + s \left[ \frac{R_2}{L} + \frac{1}{R_1 C} \right] + \frac{(R_1+R_2)/R_1}{LC}}$$

- 12.3 Determine the driving point impedance at the input terminals of the network shown in Fig. P12.3 as a function of  $s$ .

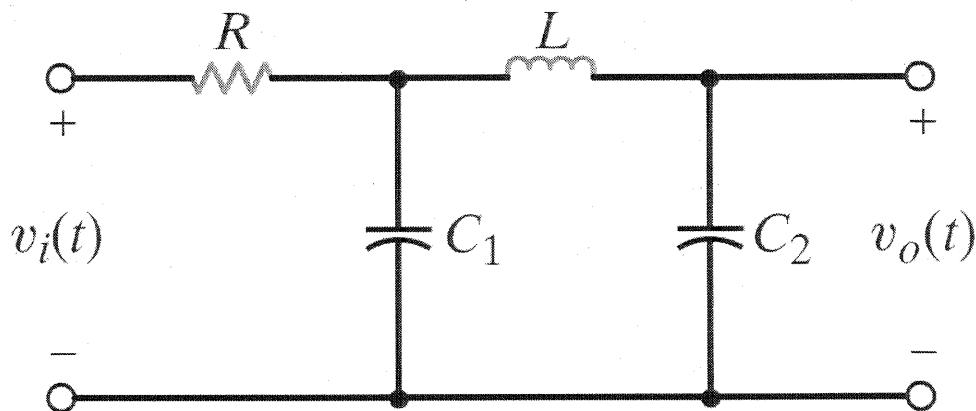


Figure P12.3

SOLUTION:

$$\begin{aligned}
 & \text{Circuit diagram: } Z = R + \frac{s^2 + \frac{1}{LC_2}}{SC_1 \left[ s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right]} \\
 & z \rightarrow \quad \quad \quad z_1 = sL + \frac{1}{SC_2} \\
 & \quad \quad \quad z_2 = \left( \frac{1}{SC_1} \right) z_1 / \left( \frac{1}{SC_1} + z_1 \right) \\
 & \quad \quad \quad z_2 = \frac{s^2 + \frac{1}{LC_2}}{SC_1 \left[ s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right]}
 \end{aligned}$$

$$Z = R + \frac{s^2 + \frac{1}{LC_2}}{SC_1 \left[ s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right]}$$

$$\boxed{Z = R \left\{ \frac{\frac{s^3}{C_1 R} + \frac{s^2}{C_1 C_2} + \frac{(C_1 + C_2)}{LC_1 C_2} s + \frac{1}{RLC_1 C_2}}{s \left( s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right)} \right\}}$$

- 12.4 Find the transfer impedance  $V_o(s)/I_s(s)$  for the network shown in Fig. P12.4.

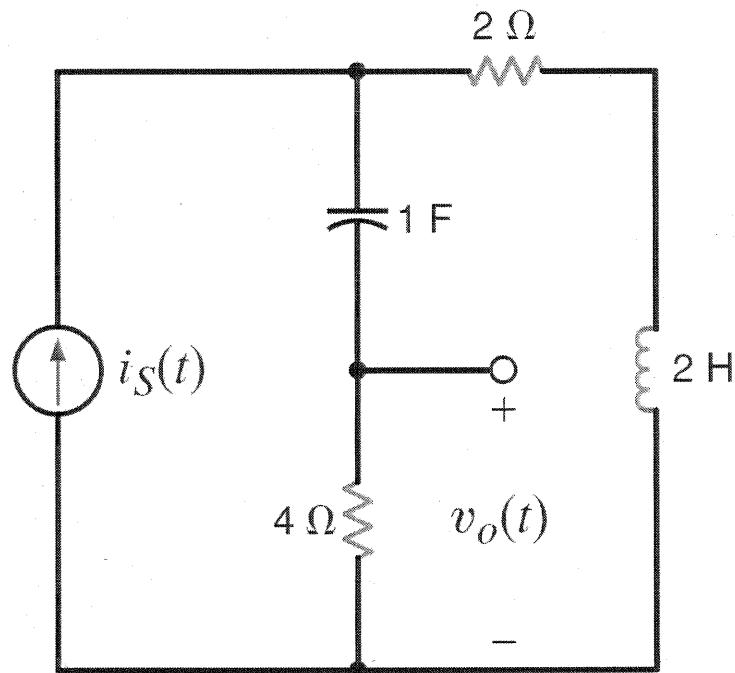


Figure P12.4

SOLUTION:


Let  $Z_1 = 4 + 1/s = \frac{4s+1}{s} \Omega$

$$Z_2 = 2s + 2 \Omega$$

$$\frac{I_o}{I_s} = \frac{Z_2}{Z_1 + Z_2} = \frac{2s(s+1)}{2s^2 + 6s + 1}$$


$$\frac{V_o}{I_s} = \frac{4 I_o}{I_s} = \boxed{\frac{8s(s+1)}{2s^2 + 6s + 1}} = \frac{V_o}{I_s}$$

**12.5** Find the driving point impedance at the input terminals of the circuit in Fig. P12.5 as a function of  $s$ . cs

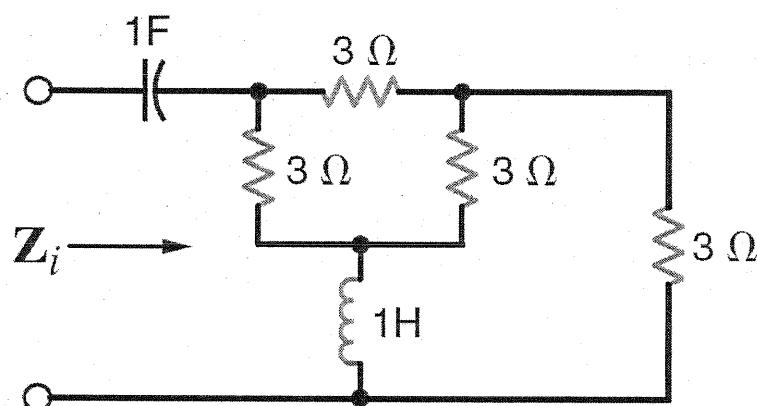

**Figure P12.5**

**SOLUTION:**

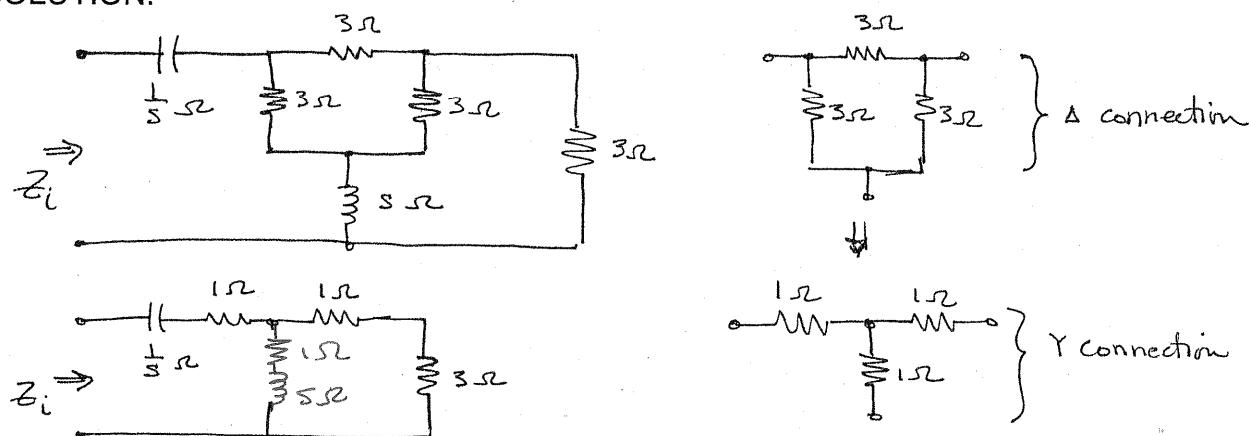

$$Z_1 = 1 + 3 = 4\Omega \quad Z_2 = (s+1)(Z_1) / (s+1+Z_1) = 4(s+1) / (s+5)$$

$$Z_i = Z_2 + 1 + \frac{1}{s} = \frac{5(s^2 + 2s + 1)}{s(s+5)}$$


$$Z_i = \frac{s(s^2 + 2s + 1)}{s(s+5)} \Omega$$

## 12.6 Draw the Bode plot for the network function

$$H(j\omega) = \frac{j\omega 4 + 1}{j\omega 20 + 1}$$

SOLUTION:
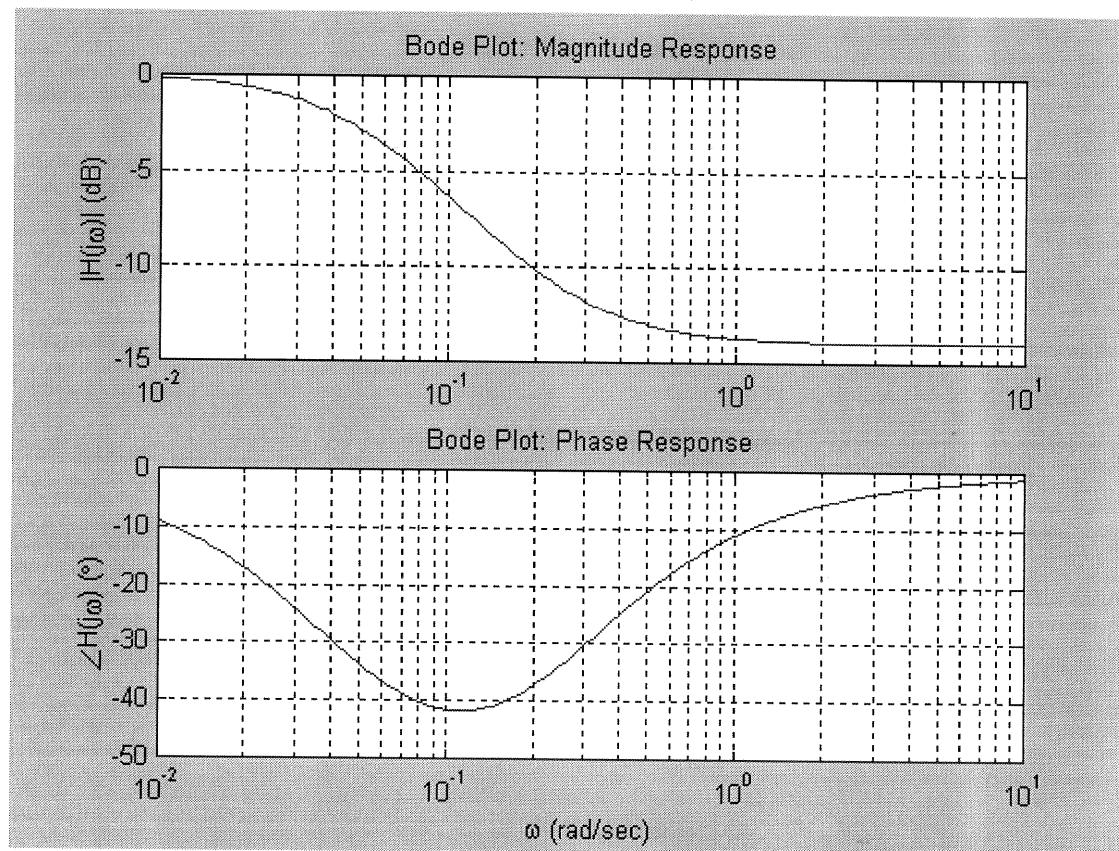
$$H(j\omega) = \frac{1}{5} \frac{j\omega + 1/4}{j\omega + 1/20}$$




12.7 Draw the Bode plot for the network function

$$H(j\omega) = \frac{j\omega 5 + 1}{j\omega 10 + 1}$$

SOLUTION:
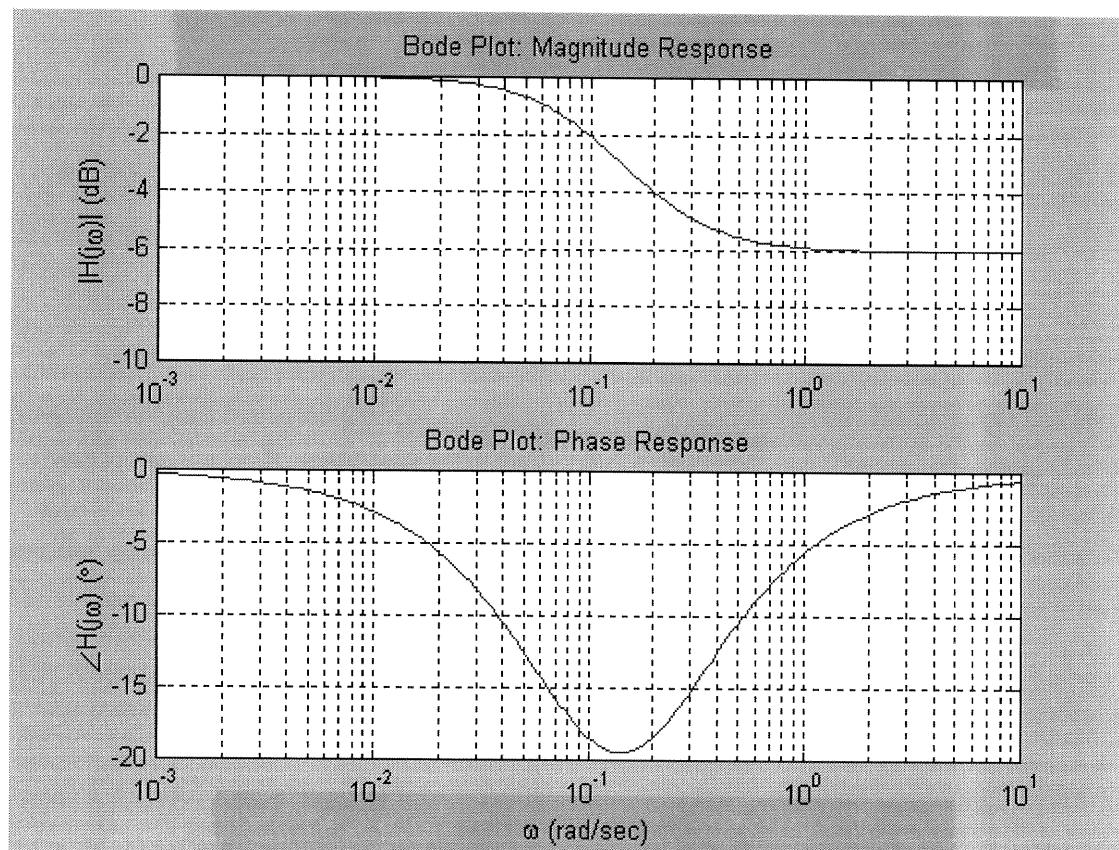
$$H(j\omega) \approx \frac{1}{2} \left[ \frac{j\omega + 1/5}{j\omega + 1/10} \right]$$




## 12.8 Draw the Bode plot for the network function

$$H(j\omega) = \frac{10(10j\omega + 1)}{(100j\omega + 1)(0.01j\omega + 1)}$$

SOLUTION:
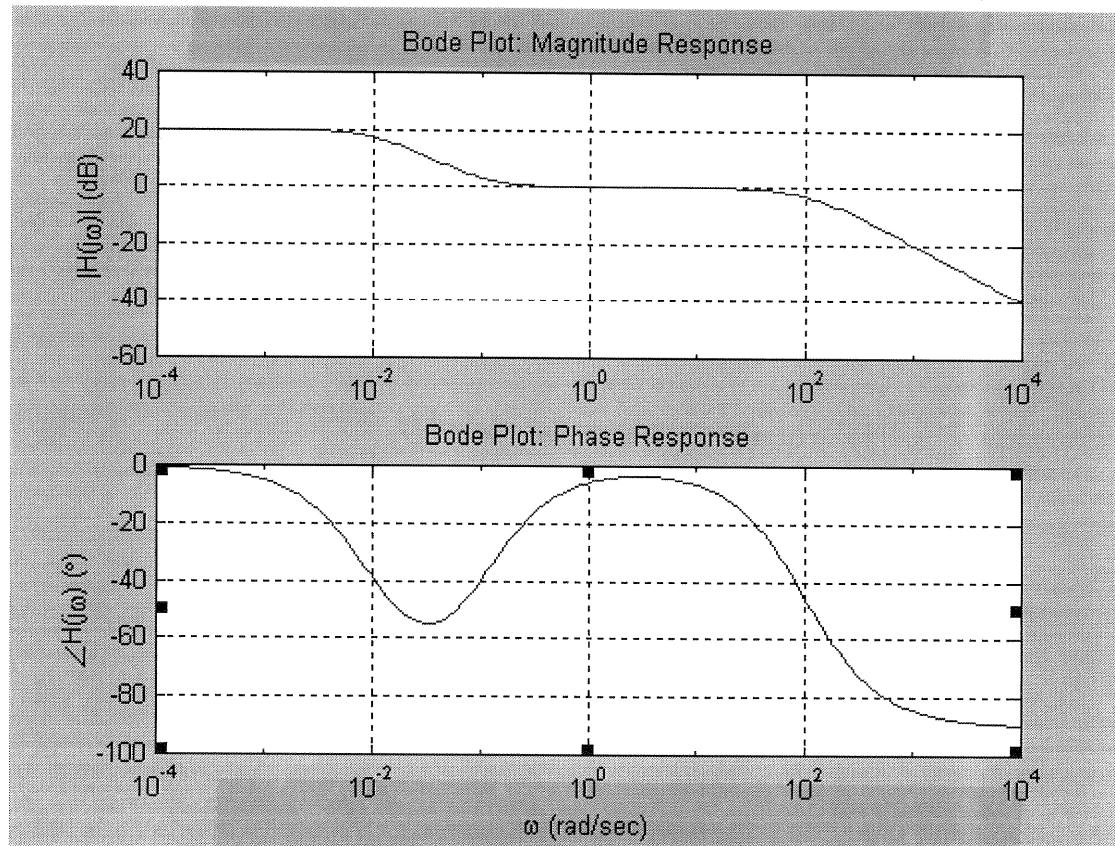
$$H(j\omega) = \frac{100 (j\omega + 1/10)}{(j\omega + 1/100) (j\omega + 100)}$$




**12.9** Draw the Bode plot for the network function

$$H(j\omega) = \frac{j\omega}{(j\omega + 1)(0.1j\omega + 1)}$$

cs

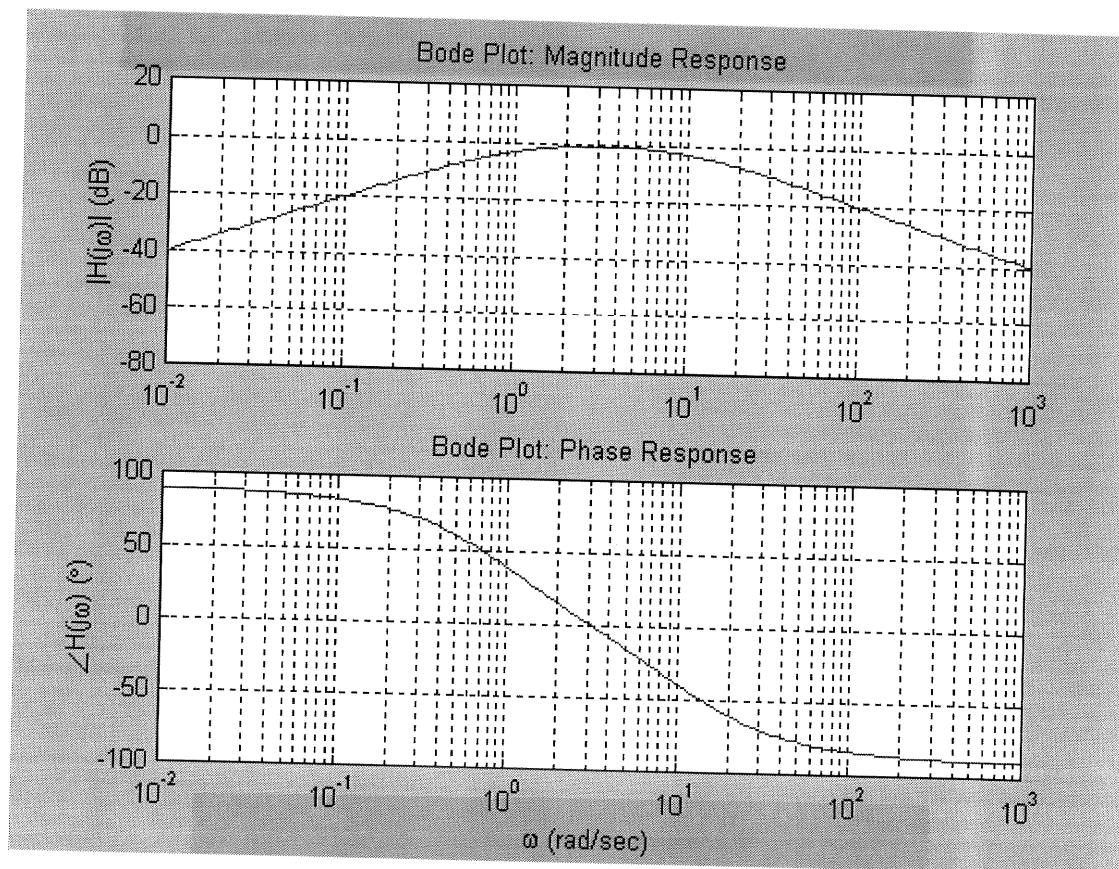**SOLUTION:**

$$H(j\omega) = \frac{10(j\omega)}{(j\omega+1)(j\omega+10)}$$




**12.10** Draw the Bode plot for the network function

$$H(j\omega) = \frac{10j\omega + 1}{j\omega(0.01j\omega + 1)}$$

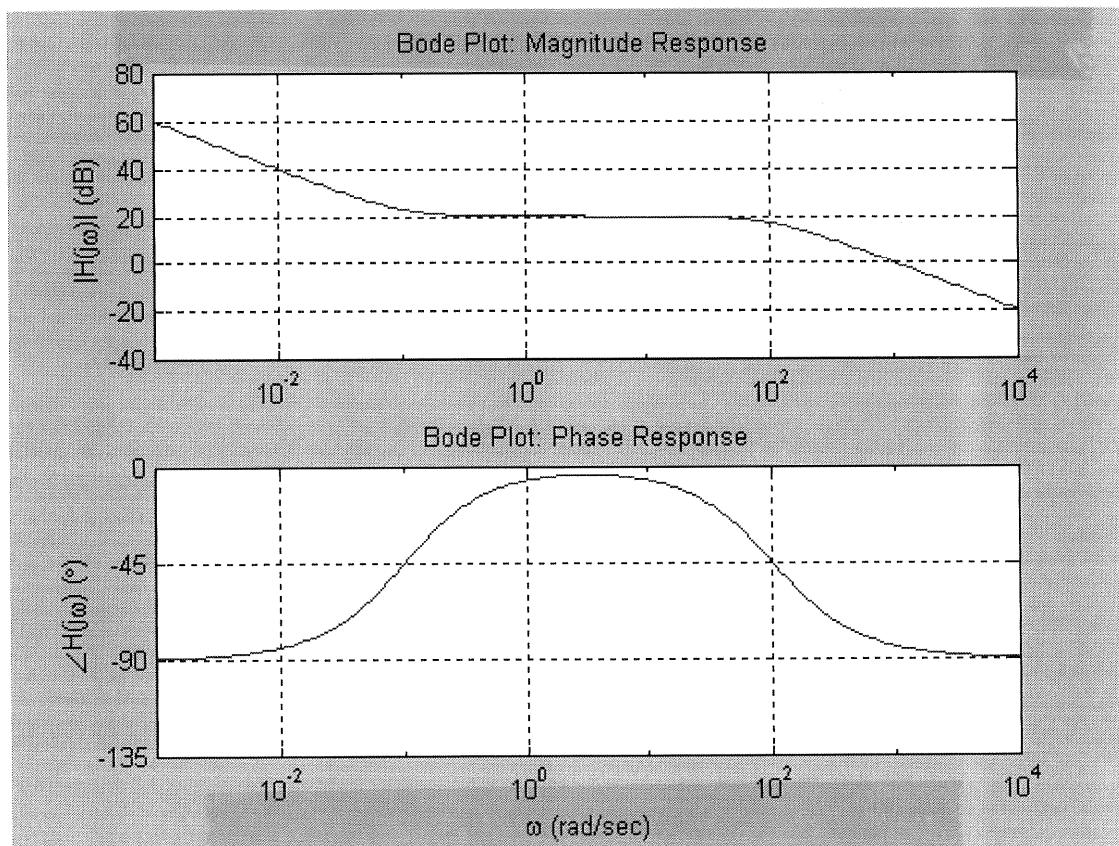**SOLUTION:**

$$H(j\omega) = \frac{10(j\omega + 0.1)}{j\omega(j\omega + 100)} = \frac{1000(j\omega + 0.1)}{j\omega(j\omega + 100)}$$



- 12.11 Sketch the magnitude characteristic of the Bode plot for the transfer function


$$H(j\omega) = \frac{100}{j\omega(0.1j\omega + 1)}$$

**PSV**

SOLUTION:

$$H(j\omega) = \frac{100}{j\omega(j\omega + 10)} = \frac{1000}{j\omega(j\omega + 10)}$$

$$|H| \Big|_{\omega=1} \approx \frac{1000}{(1)(10)} = 100 = 40 \text{ dB}$$

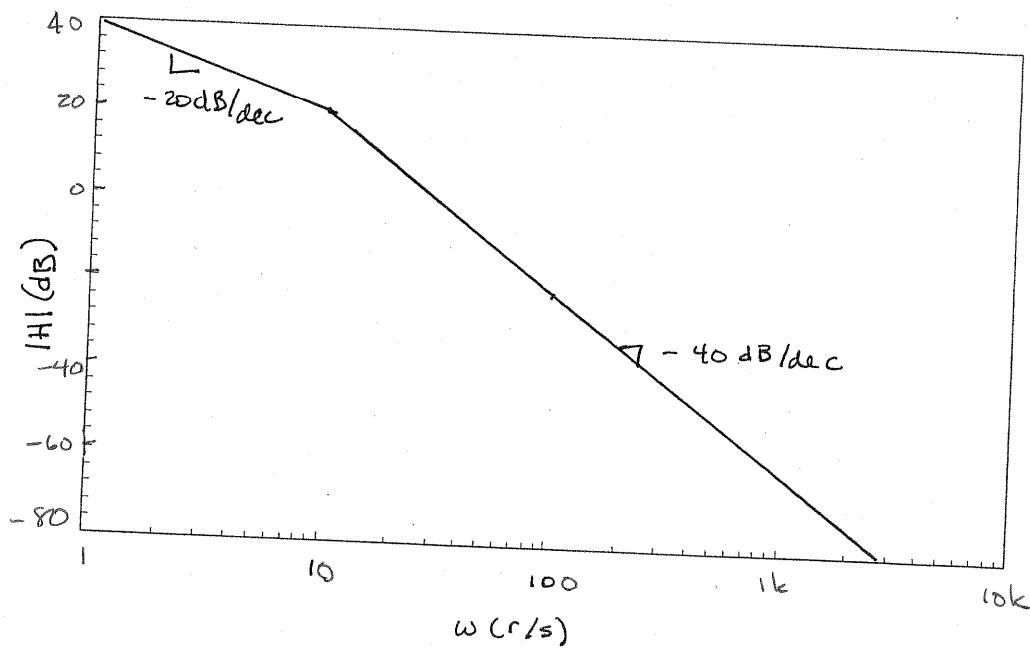

**12.12** Sketch the magnitude characteristic of the Bode plot for the transfer function


$$H(j\omega) = \frac{20(0.1j\omega + 1)}{j\omega(j\omega + 1)(0.01j\omega + 1)}$$

**SOLUTION:**

$$H(j\omega) = \frac{20(0.1)(j\omega + 10)}{j\omega(j\omega + 1)(0.01)(j\omega + 100)} = \frac{200(j\omega + 10)}{j\omega(j\omega + 1)(j\omega + 100)}$$

$$\text{As } \omega \rightarrow 0, |H| \rightarrow 20/\omega$$

$$|H| \Big|_{\omega=0.1} \approx \frac{200(10)}{(0.1)(1)(100)} = 200 = 46 \text{ dB}$$

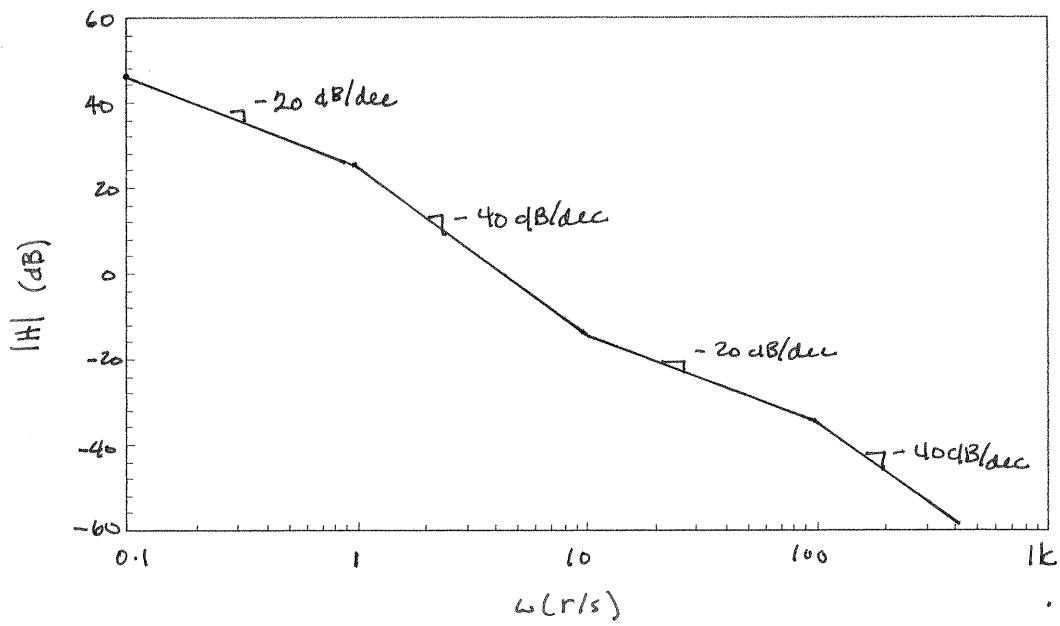


**12.13** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$H(j\omega) = \frac{100(j\omega)}{(j\omega + 1)(j\omega + 10)(j\omega + 50)}$$

CS

**SOLUTION:**

$$H(j\omega) = \frac{100(j\omega)}{(j\omega+1)(j\omega+10)(j\omega+50)} \quad |H| \Big|_{\omega = \frac{1}{150}} \approx 2 \times 10^{-3} = -54 \text{ dB}$$

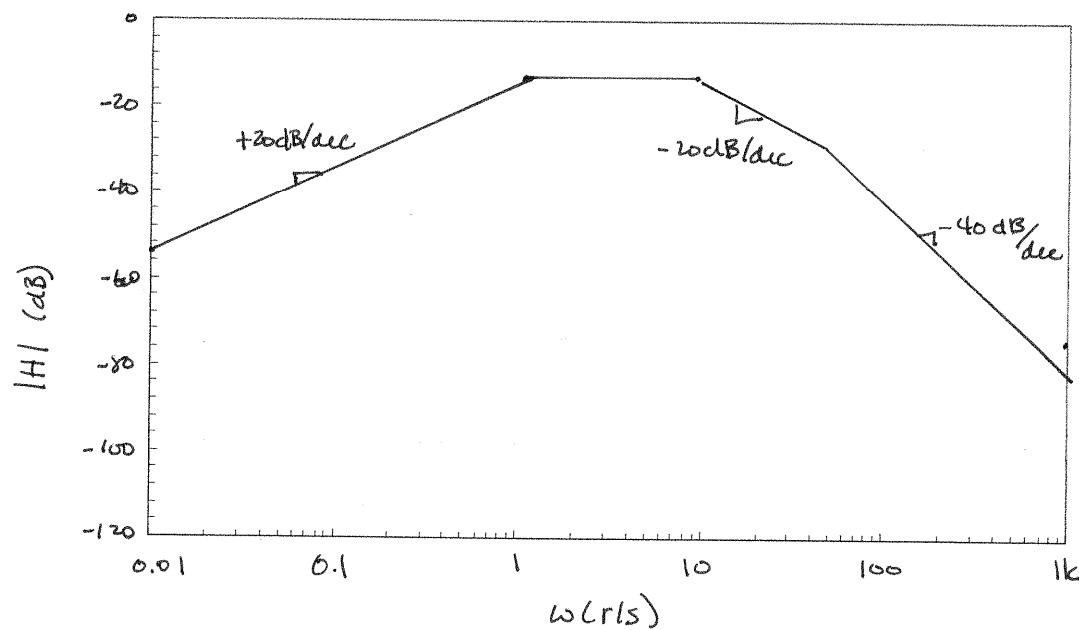


**12.14** Draw the Bode plot for the network function

$$H(j\omega) = \frac{100}{(j\omega)^2(j\omega^2 + 1)}$$

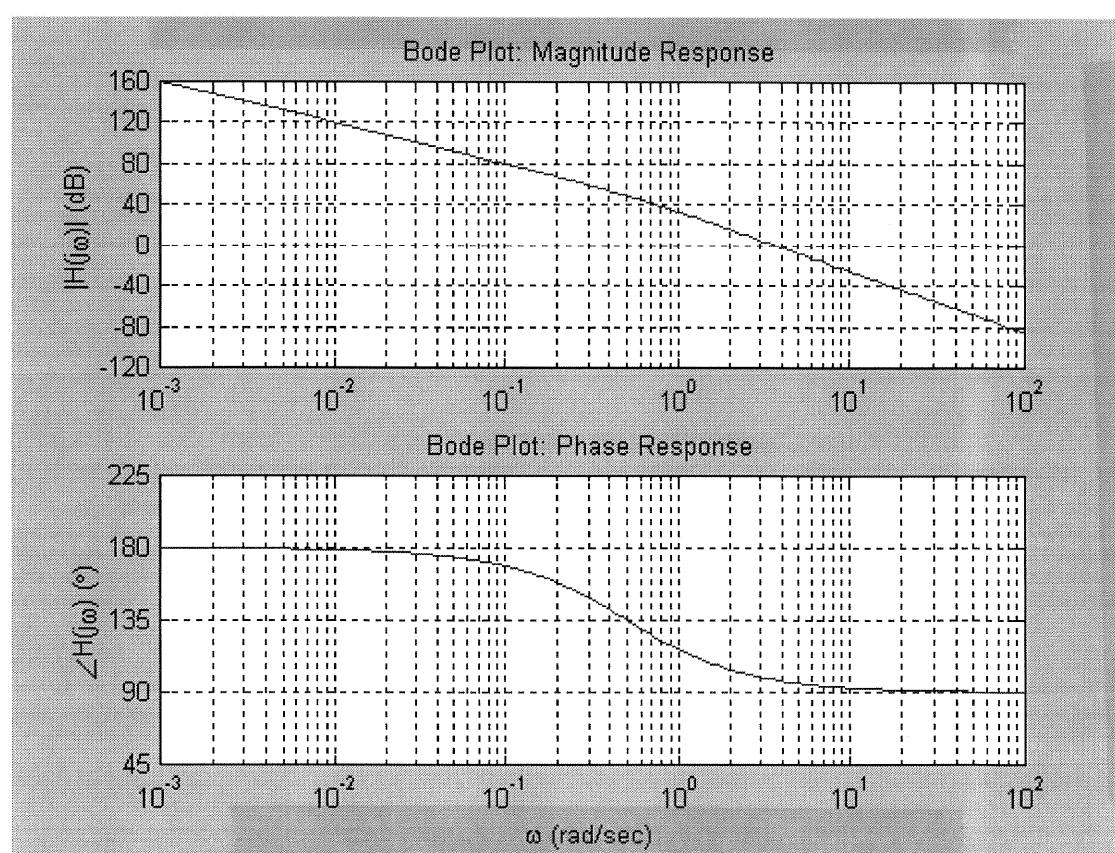**SOLUTION:**

$$H(j\omega) = \frac{100}{(j\omega)^2(j\omega^2 + 1)} = \frac{50}{(j\omega)^2(j\omega + 0.5)}$$




12.15 Sketch the magnitude characteristic of the Bode plot for the transfer function

$$H(j\omega) = \frac{36 \times 10^5 (5j\omega + 1)^2}{(j\omega)^2 (j\omega + 10)(j\omega + 100)^2}$$

SOLUTION:

$$H(j\omega) = \frac{36 \times 10^5 (25) (j\omega + 0.2)^2}{(j\omega)^2 (j\omega + 10)(j\omega + 100)^2} = \frac{9 \times 10^7 (j\omega + 0.2)^2}{(j\omega)^2 (j\omega + 10)(j\omega + 100)^2}$$

$$|H| \Big|_{\omega=0.01} \approx \frac{9 \times 10^7 (0.2)^2}{(0.01)^2 (10)(100)^2} = 3.60 \times 10^5 = 111 \text{ dB}$$

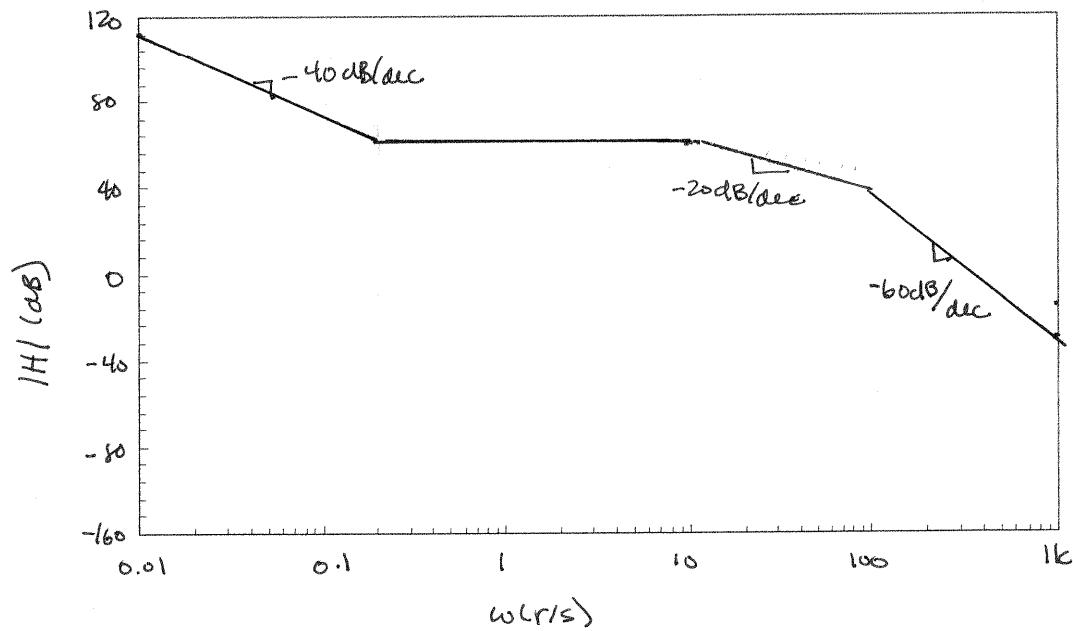


- 12.16 Sketch the magnitude characteristic of the Bode plot for the transfer function

$$G(j\omega) = \frac{400(j\omega + 2)(j\omega + 50)}{-\omega^2(j\omega + 100)^2}$$

SOLUTION:

$$G(j\omega) = \frac{400 (j\omega + 2)(j\omega + 50)}{-\omega^2 (j\omega + 100)^2} \quad |G| \Big|_{\omega=0.1} \approx \frac{400 (2)(50)}{(0.1)^2 (100)^2} = 400 \\ = 52.0 \text{dB}$$

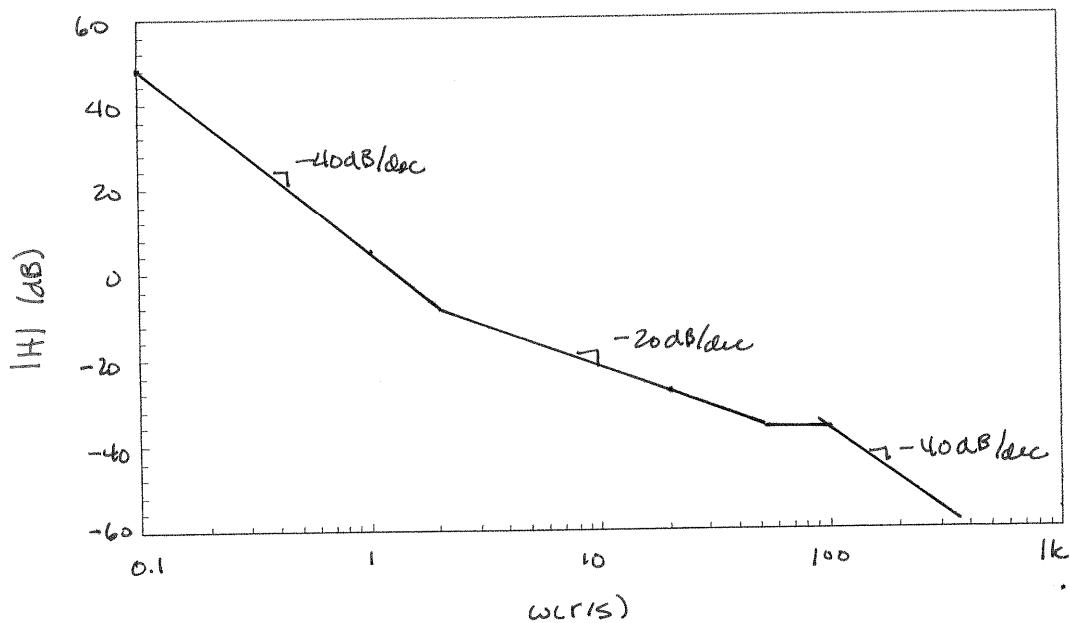

12.17 Sketch the magnitude characteristic of the Bode plot for the transfer function


$$G(j\omega) = \frac{10j\omega}{(j\omega + 1)(j\omega + 10)^2}$$

cs

---

SOLUTION:

$$|G| \Big|_{\omega=0.1} \approx \frac{10(0.1)}{1(10)^2} = \frac{1}{100} = -40 \text{ dB}$$

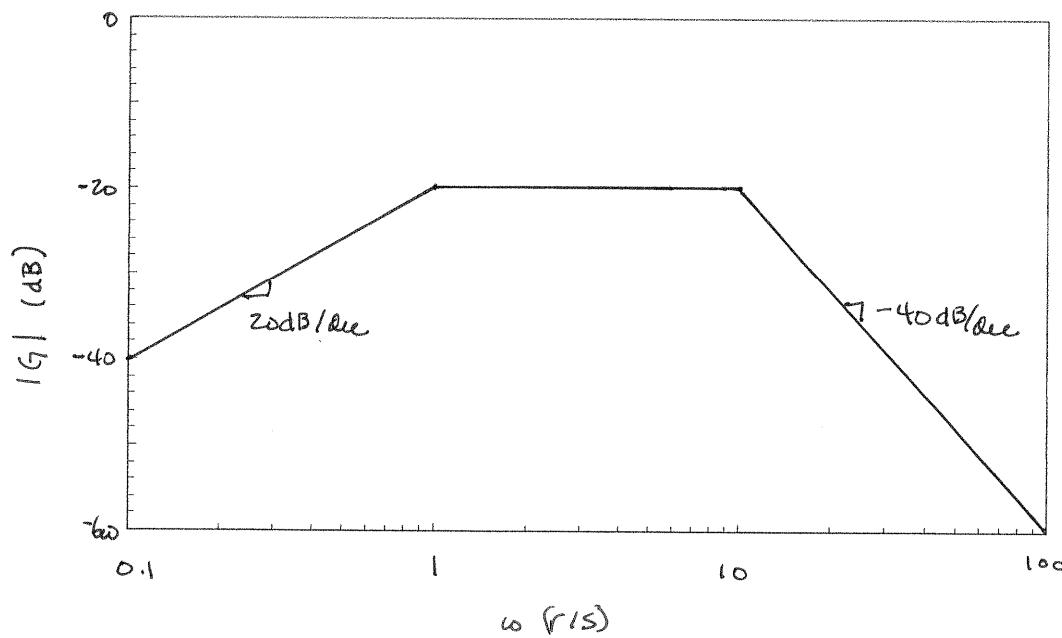


**12.18** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$G(j\omega) = \frac{-\omega^2 10^4}{(j\omega + 1)^2 (j\omega + 10)(j\omega + 100)^2}$$

**SOLUTION:**

$$|G| \Big|_{\omega=0.1} \approx \frac{(0.1)^2 (10^4)}{(1)^2 (10) (100)^2} = 10^{-3} = -60 \text{ dB}$$

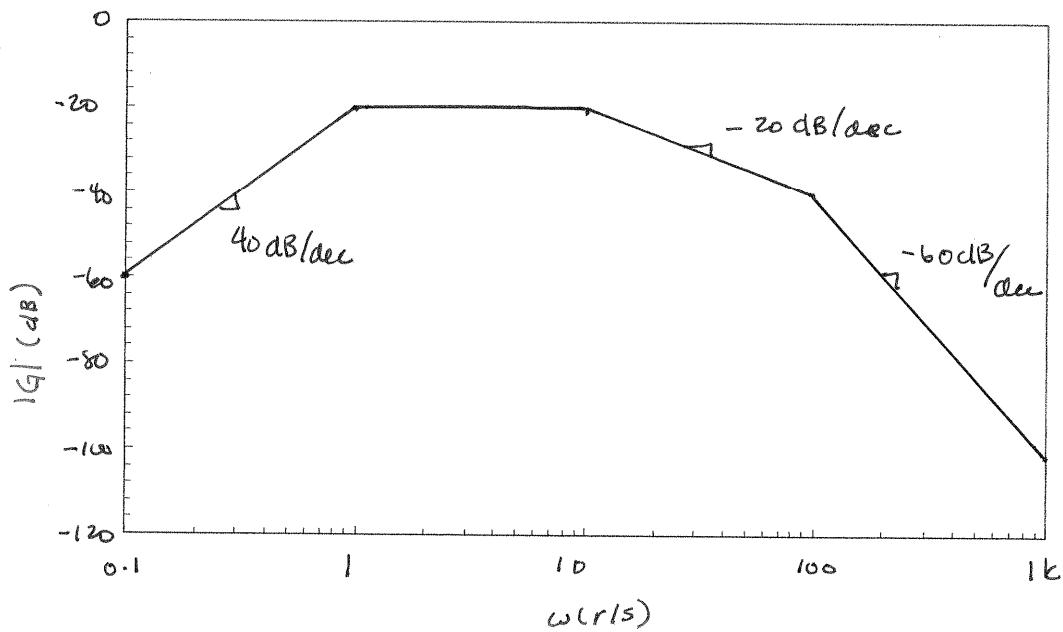


**12.19** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$G(j\omega) = \frac{8(j\omega + 1)^2}{-j\omega^3(0.1j\omega + 1)}$$

**SOLUTION:**

$$\left| G(j\omega) \right| \Big|_{\omega=0.1} \approx \frac{8(1)^2}{(0.1)^3(1)} = 8000 = 78 \text{ dB}$$
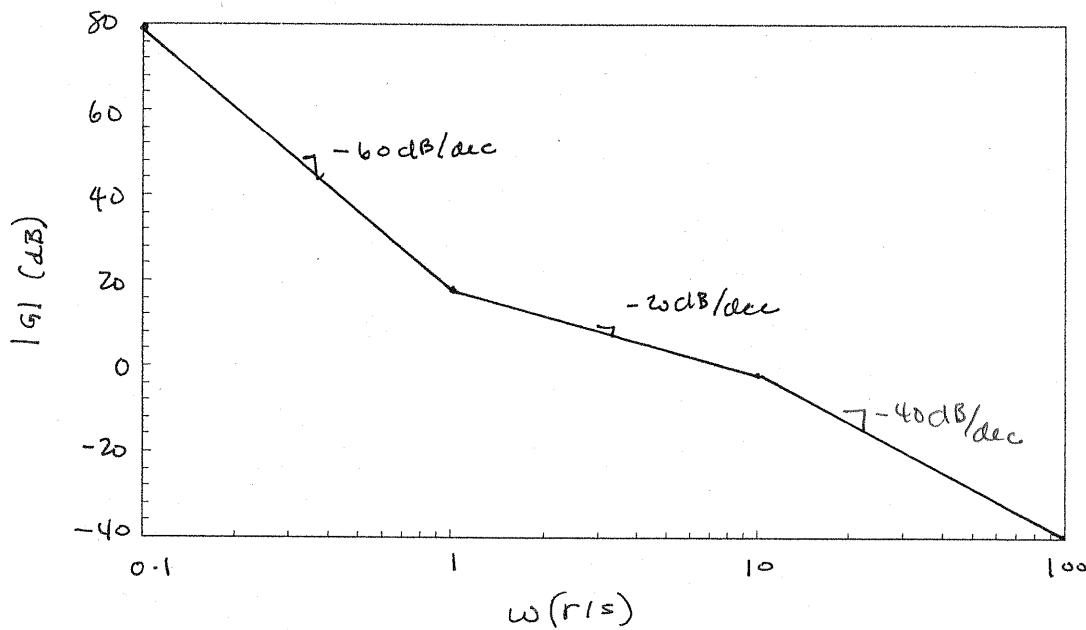
$$G(j\omega) = \frac{80(j\omega+1)^2}{-j\omega^3(\omega+10)}$$




- 12.20 Sketch the magnitude characteristic of the Bode plot for the transfer function

$$G(j\omega) = \frac{-\omega^2}{(j\omega + 1)^3} \quad \text{cs}$$

SOLUTION:

$$|G| \Big|_{\omega=0.1} \approx \frac{(0.1)^2}{(1)^3} = 10^{-2} = -40 \text{ dB}$$

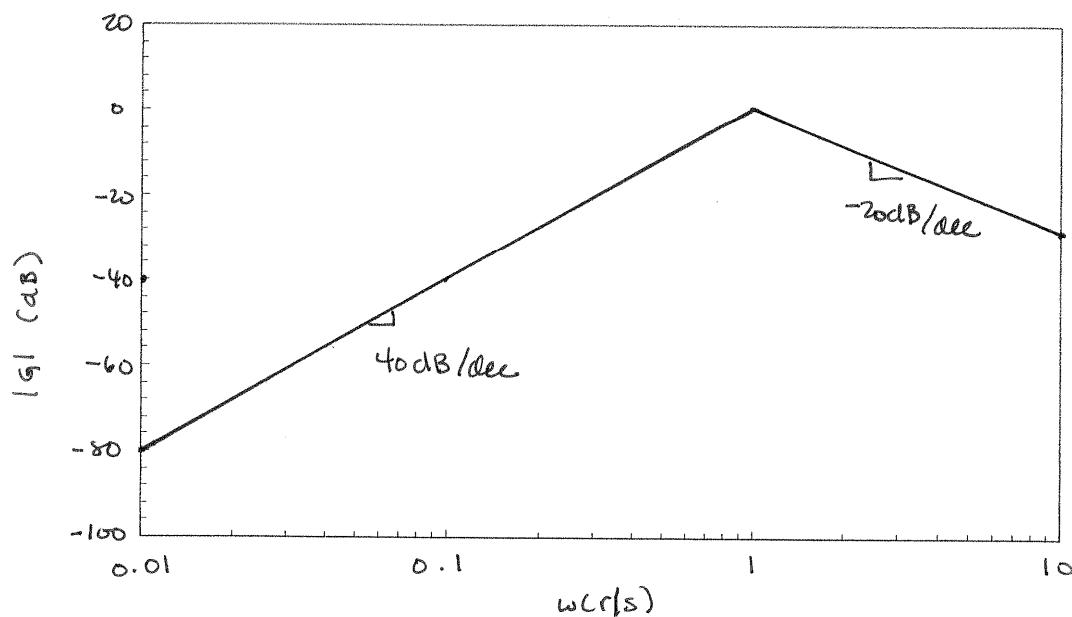

**12.21** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$G(j\omega) = \frac{10^4(j\omega + 1)(-\omega^2 + 6j\omega + 225)}{j\omega(j\omega + 50)^2(j\omega + 450)}$$


**SOLUTION:**

$$|G| \Big|_{\omega=0.1} \approx \frac{10^4(1)(225)}{(0.1)(50)^2(450)} = 20 = 26 \text{ dB}$$

$$-\omega^2 + 6j\omega + 225 = (j\omega)^2 + 6j\omega + 225 = (j\omega + 3 + j14.7)(j\omega + 3 - j14.7)$$

$$\text{or, } \frac{1}{225} \left[ 1 - \frac{\omega^2}{225} + \frac{6j\omega}{225} \right] = \frac{1}{225} \left[ 1 - (\omega\tau)^2 + 2j\xi(\omega\tau) \right]$$
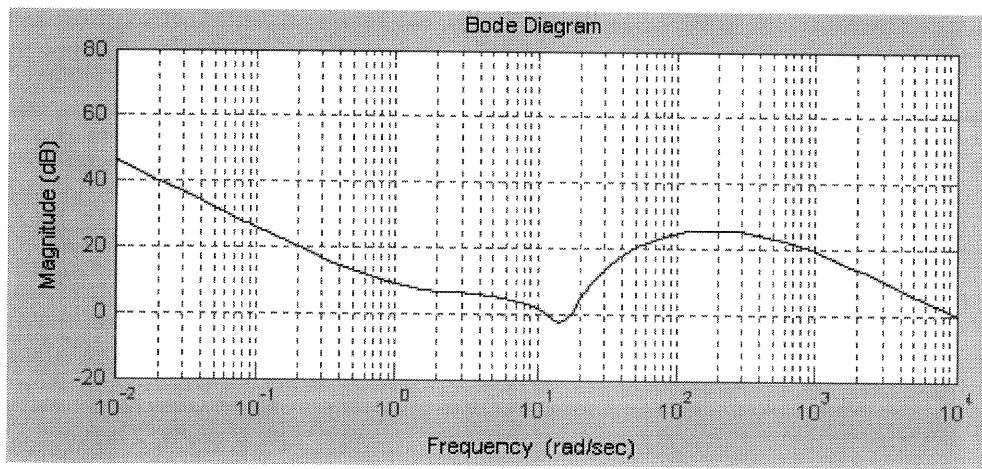
$$\text{So, } \tau = 1/\sqrt{225} = 1/15 \quad \xi = \frac{6}{225(2)\tau} = 0.2$$



12.22 Sketch the magnitude characteristic of the Bode plot for the transfer function


$$H(j\omega) = \frac{+6.4}{(j\omega + 1)(-\omega^2 + 8j\omega + 16)}$$

SOLUTION:

$$-\omega^2 + 8j\omega + 16 = 16 \left\{ \left( 1 - \left(\frac{\omega}{4}\right)^2 \right) + j\omega \frac{1}{2} \right\} = 16 \left\{ 1 - (\omega/4)^2 + j\omega/2 \right\}$$

$$\zeta = 1/4 \quad \xi = \frac{1}{2(2)\zeta} = 1$$

$$H(j\omega) = \frac{6.4}{(j\omega+1)(j\omega+4)^2} \quad |H| \Big|_{\omega=0.1} \stackrel{\omega=0.1}{\approx} \frac{6.4}{(1)(16)} = 0.4 = -8 \text{dB}$$

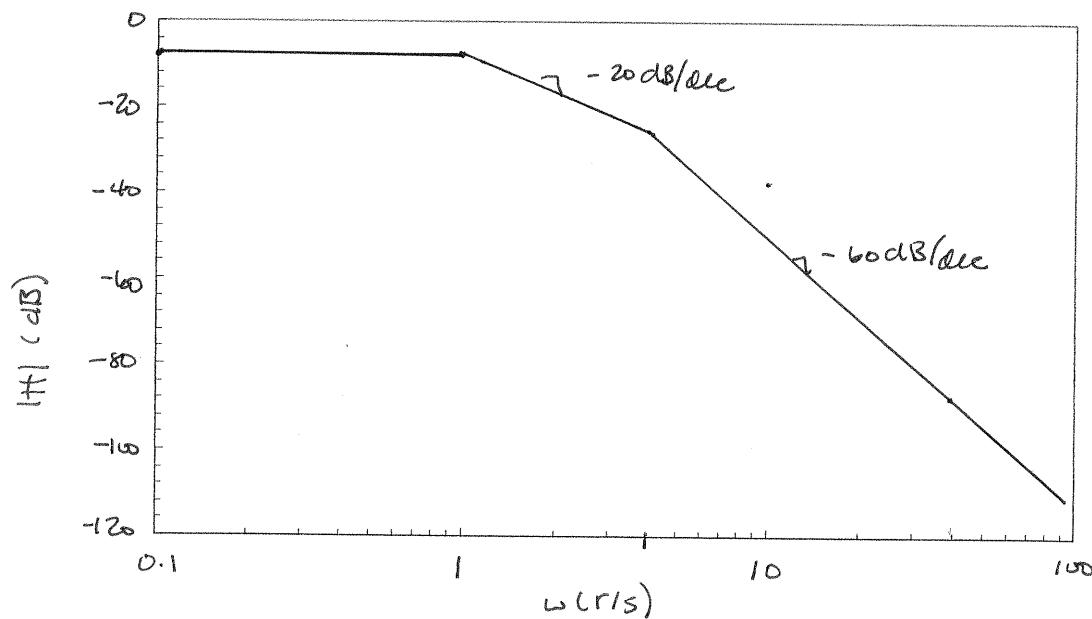

**12.23** Sketch the magnitude characteristic of the Bode plot for the transfer function


$$G(j\omega) = \frac{10(j\omega + 2)(j\omega + 100)}{j\omega(-\omega^2 + 4j\omega + 100)}$$

**SOLUTION:**

$$100 - \omega^2 + 4j\omega = 100 \left[ 1 - \left(\frac{\omega}{10}\right)^2 + \frac{4}{100} j\omega \right] = 100 \left[ 1 - (\omega T)^2 + j2\zeta(\omega T) \right]$$

$$T = \frac{1}{10} \text{ s} \quad \zeta = \frac{4}{100} \cdot \frac{1}{2} \cdot \frac{1}{T} = 0.2$$

$$|G| \Big|_{\omega=0.1} \approx \frac{10(2)(100)}{(0.1)(100)} = 200 = 46 \text{ dB}$$

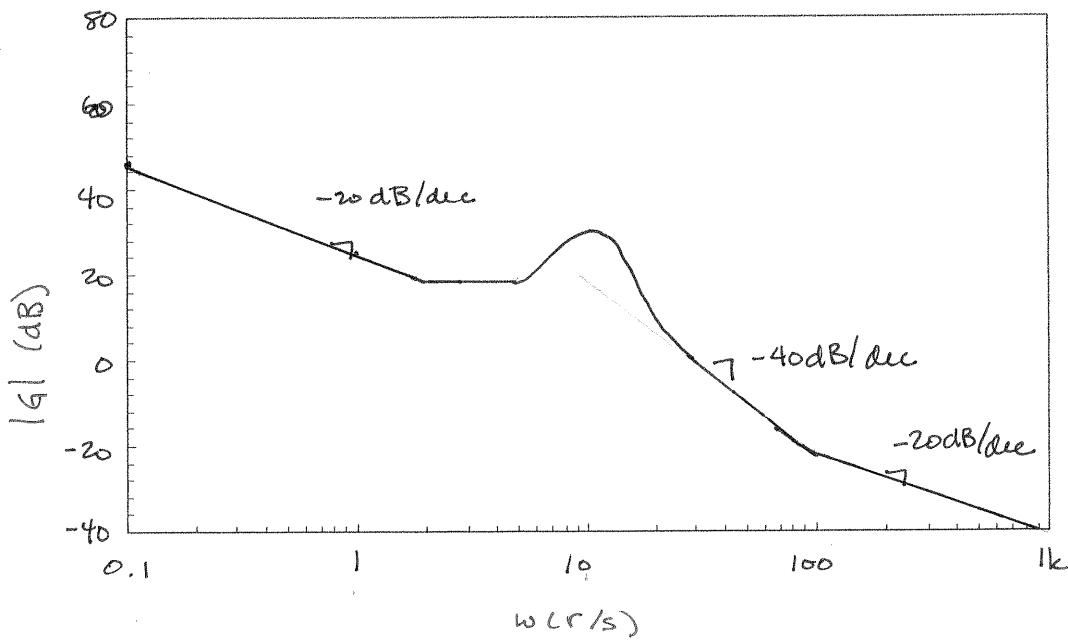

**12.24** Sketch the magnitude characteristic of the Bode plot for the transfer function


$$G(j\omega) = \frac{j\omega(j\omega + 100)}{(j\omega + 1)(-\omega^2 + 6j\omega + 400)}$$

**SOLUTION:**

$$400 - \omega^2 + 6j\omega = 400 \left[ 1 - \left(\frac{\omega}{20}\right)^2 + \frac{6}{400} (j\omega) \right] = 400 \left[ 1 - (\omega/20)^2 + 2j\cdot 5\omega/20 \right]$$

$$\zeta = \frac{1}{20} \quad \xi = \frac{6}{400} \cdot \frac{1}{2} \cdot \frac{1}{20} = 0.15$$

$$|G| \Big|_{\omega=0.1} \approx \frac{(0.1)(100)}{(1)(400)} = \frac{1}{40} = -32 \text{ dB}$$

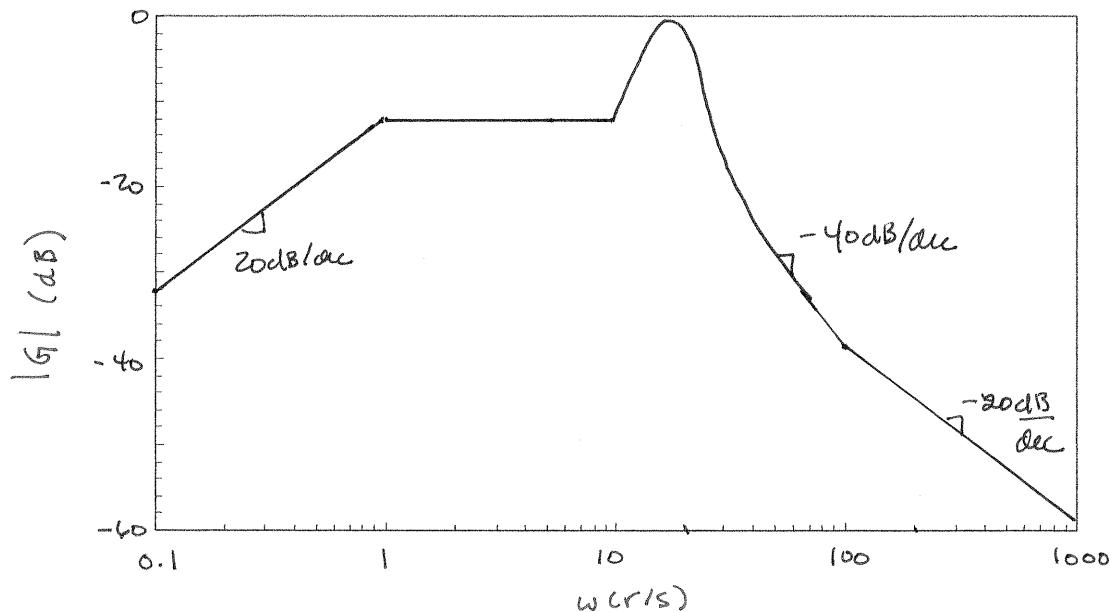

**12.25** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$H(j\omega) = \frac{+6.4(j\omega)}{(j\omega + 1)(-\omega^2 + 8j\omega + 64)}$$


CS

**SOLUTION:**

$$64 - \omega^2 + 8j\omega = 64 \left[ 1 - \left(\frac{\omega}{8}\right)^2 + \left(\frac{1}{8}\right) j\omega \right] = 64 \left[ 1 - (\omega\tau)^2 + 2j\zeta\omega\tau \right]$$

$$\tau = 1/8 \text{ s} \quad \zeta = \frac{1}{2\tau} = 0.5$$

$$|G| \Big|_{\omega=0.1} \approx \frac{6.4(0.1)}{(1)(64)} = 10^{-2} = -40 \text{ dB}$$

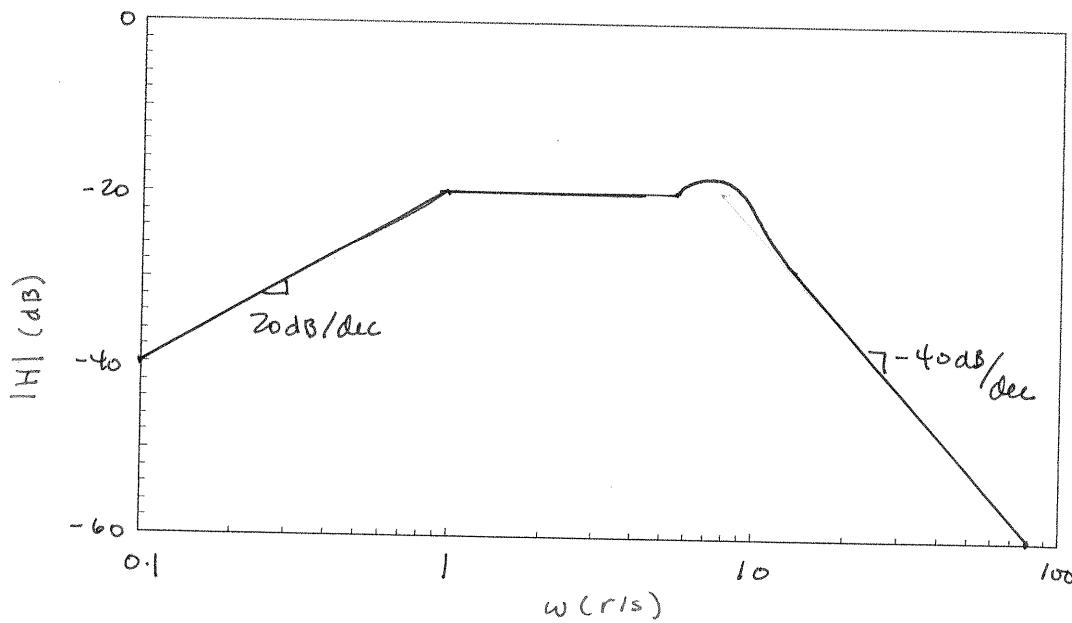

- 12.26** Use MATLAB to generate the Bode plot for the following transfer function over the frequency range from  $\omega = 0.01$  to  $1000$  rad/s.

$$G(j\omega) = \frac{10(j\omega + 1)}{(j\omega)(j\omega + 10)}$$


---

SOLUTION:

12.26

This sequence of commands works in both the commercial and student versions of MATLAB.

```
>> figure(1);
>> w = logspace(-2,3,200);
>> H = 10*(j*w+1)./((10+j*w).*(j*w));
>> subplot(2,1,1);
>> semilogx(w,20*log10(abs(H)));
>> grid; ylabel('|H(j\omega)| (dB)');
>> title('Bode Plot: Magnitude Response');
>> subplot(2,1,2);
>> semilogx(w,unwrap(angle(H))*180/pi);
>> grid; xlabel('\omega (rad/sec)'); ylabel('\angleH(j\omega) (\circ)');
>> title('Bode Plot: Phase Response');
```

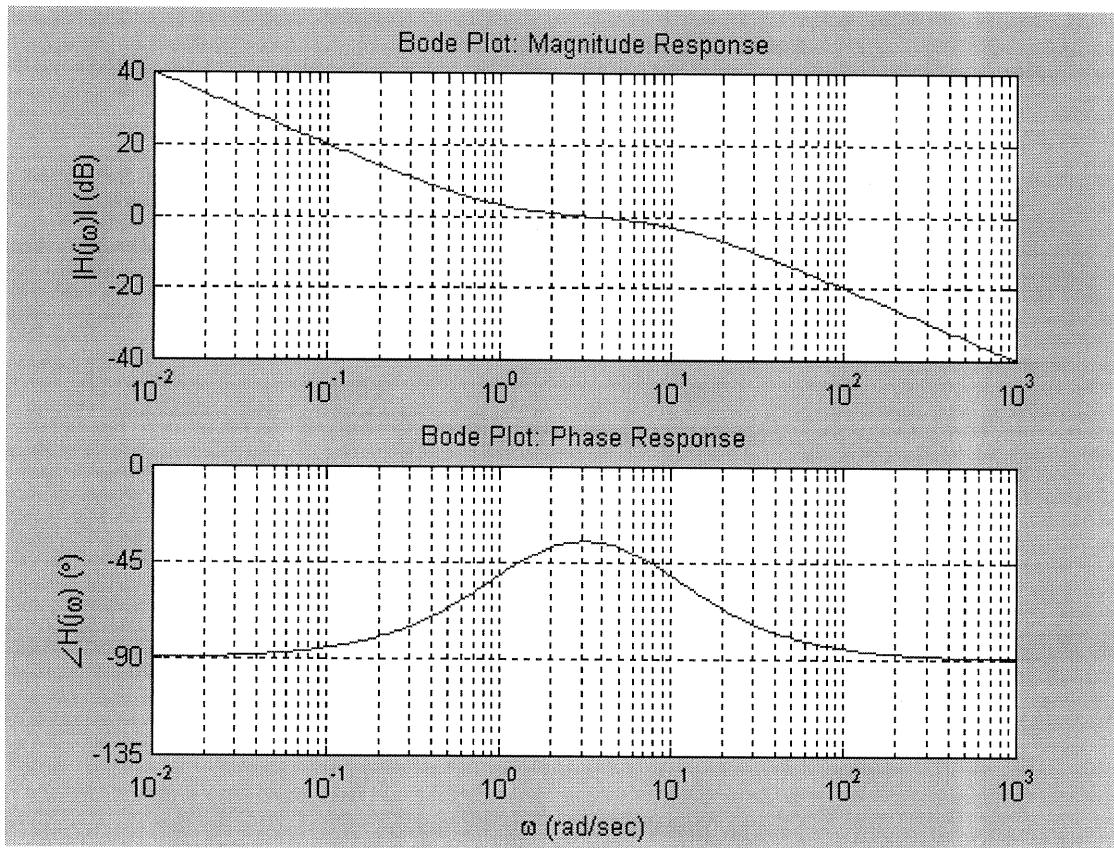

**12.27** Use MATLAB to generate the Bode plot for the following transfer function over the frequency range from  $\omega = 0.1$  to 10,000 rad/s.

$$G(j\omega) = \frac{20(j\omega + 10)}{(j\omega)(j\omega + 1)(j\omega + 100)}$$


---

SOLUTION:


12.27

This sequence of commands works in both the commercial and student versions of MATLAB.

```
EDU> figure(1);
EDU> w = logspace(-2,3,200);
EDU> H = 20*(j*w+10)./((1+j*w).* (j*w).* (100+j*w));
EDU> figure(1);
EDU> w = logspace(-1,4,200);
EDU> H = 20*(j*w+10)./((1+j*w).* (j*w).* (100+j*w));
EDU> subplot(2,1,1);
EDU> semilogx(w,20*log10(abs(H)));
EDU> grid; ylabel('|H(j\omega)| (dB)');
EDU> title('Bode Plot: Magnitude Response');
EDU> subplot(2,1,2);
EDU> semilogx(w,unwrap(angle(H))*180/pi);
EDU> grid; xlabel('\omega (rad/sec)'); ylabel('\angle H(j\omega) (\circ)');
EDU> title('Bode Plot: Phase Response');
```

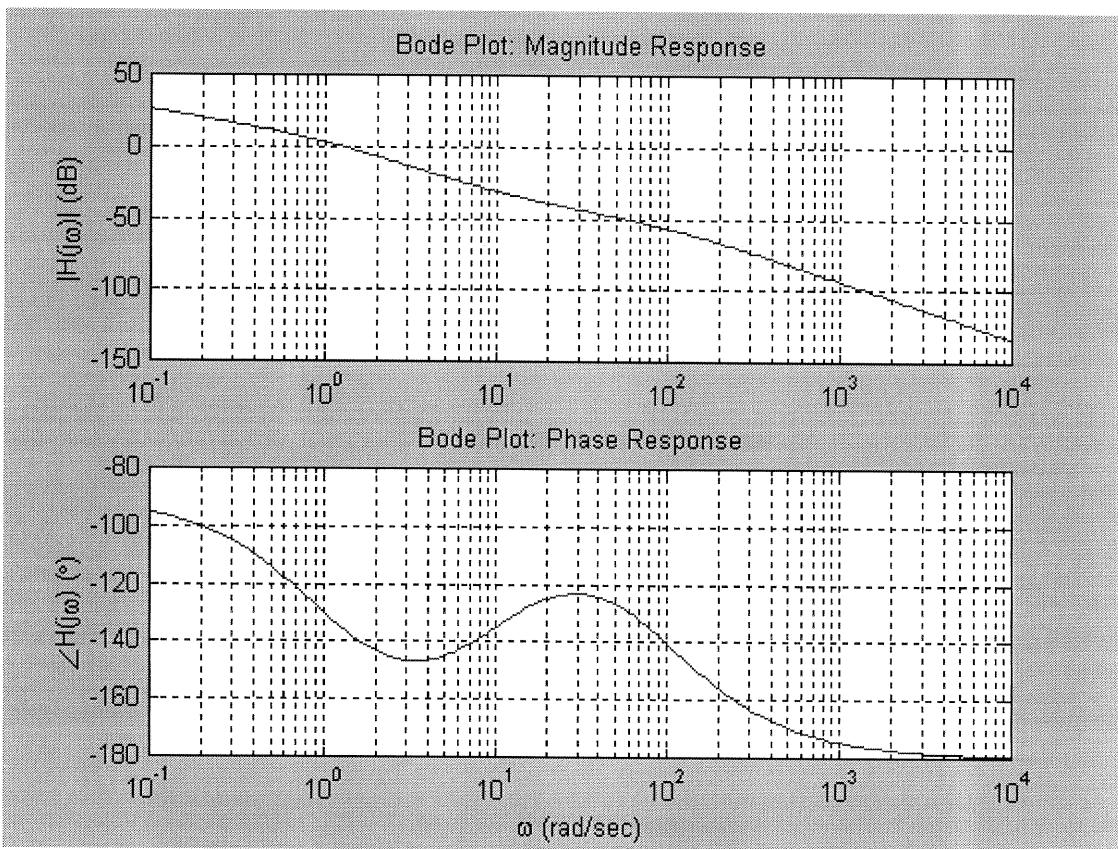

- 12.28 The magnitude characteristic of a band-elimination filter is shown in Fig. P12.28. Determine  $H(j\omega)$ .

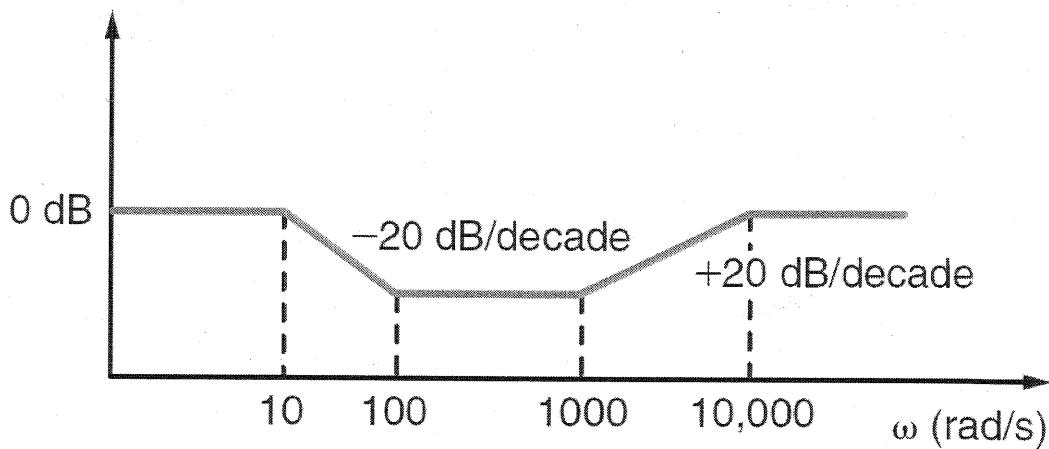

**Figure P12.28**

---

SOLUTION:

poles at 10 and 10,000 r/s      zeros at 100 and 1000 r/s

$$H(j\omega) = \frac{K(j\omega + 100)(j\omega + 1000)}{(j\omega + 10)(j\omega + 10000)} \quad 0 \text{ dB} = 1$$

$$|H| \Big|_{\omega \ll 10} = \frac{K(100)(1000)}{10(10^4)} = 1 \Rightarrow K = 1$$

$$H(j\omega) = \frac{(j\omega + 100)(j\omega + 10^3)}{(j\omega + 10)(j\omega + 10^4)}$$

- 12.29 Find  $H(j\omega)$  if its magnitude characteristic is shown in Fig. P12.29. **PSV**

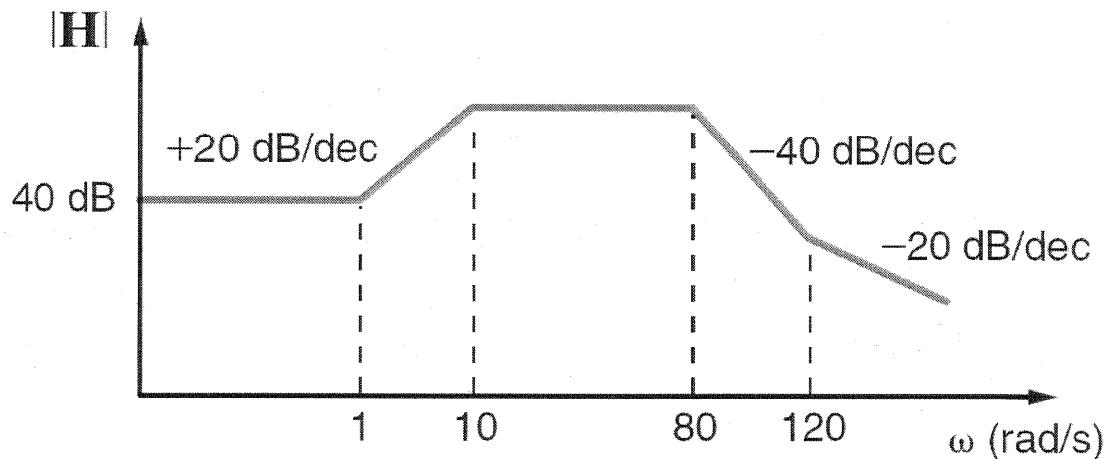


Figure P12.29

SOLUTION:


poles at  $\left\{ \begin{array}{l} 10 \text{ r/s} \\ 80 \text{ r/s (double)} \end{array} \right\}$  zeros at  $\left\{ \begin{array}{l} 1 \text{ r/s} \\ 120 \text{ r/s} \end{array} \right\}$

$$H(j\omega) = \frac{K(j\omega+1)(j\omega+120)}{(j\omega+10)(j\omega+80)^2}$$

$$\text{for } \omega \ll 1, |H| = 40 \text{ dB} = 100 = \frac{K(1)(120)}{10(80)^2} \Rightarrow K = 5.33 \times 10^4$$

$$H(j\omega) = \frac{5.33 \times 10^4 (j\omega+1)(j\omega+120)}{(j\omega+10)(j\omega+80)^2}$$

**12.30** Find  $H(j\omega)$  if its magnitude characteristic is shown in Fig. P12.30. **cs**

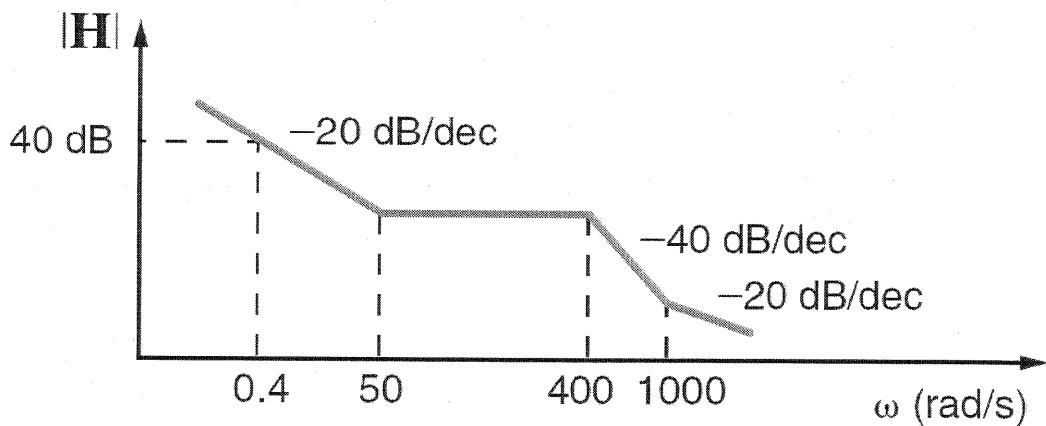

**Figure P12.30**

**SOLUTION:**

$$\text{poles at: } \left\{ \begin{array}{l} \text{origin } (\omega=0) \\ 400 \text{ r/s (double)} \end{array} \right\} \quad \text{zeros at: } \left\{ \begin{array}{l} 50 \text{ r/s} \\ 1000 \text{ r/s} \end{array} \right\}$$

$$H(j\omega) = \frac{K(j\omega+50)(j\omega+1000)}{j\omega(j\omega+400)^2}$$

$$\text{At } \omega = 0.4 \text{ r/s, } |H| = 40 \text{ dB} = 100 \Rightarrow \frac{K(50)(1000)}{0.4(400)^2} \Rightarrow K = 128$$

$$H(j\omega) = \frac{128(j\omega+50)(j\omega+1000)}{j\omega(j\omega+400)^2}$$

- 12.31 Find  $H(j\omega)$  if its amplitude characteristic is shown in Fig. P12.31.

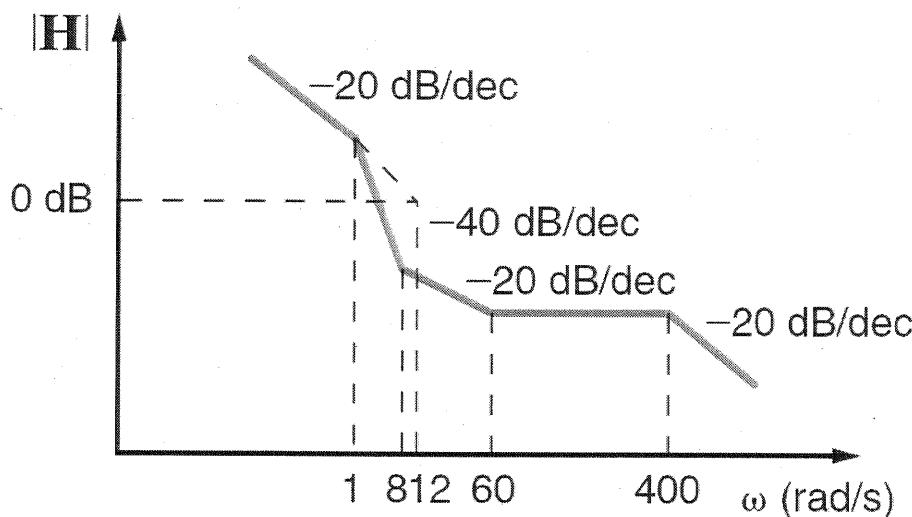


Figure P12.31

SOLUTION:

$$\text{Poles at } \left\{ \begin{array}{l} \omega = 0 \\ \omega = 1 \text{ rad/s} \\ \omega = 400 \text{ rad/s} \end{array} \right\} \quad \text{Zeros at : } \left\{ \begin{array}{l} \omega = 8 \text{ rad/s} \\ \omega = 60 \text{ rad/s} \end{array} \right\}$$

$$H(j\omega) = \frac{K(j\omega + 8)(j\omega + 60)}{j\omega(j\omega + 1)(j\omega + 400)}$$

$$\text{At } \omega = 2 \text{ rad/s}, |H| = 0 \text{ dB} = 1 \approx \frac{K(8)(60)}{2\sqrt{2^2+1^2}(400)} \Rightarrow K = 3.73$$

$$H(j\omega) = \frac{3.73(j\omega + 8)(j\omega + 60)}{j\omega(j\omega + 1)(j\omega + 400)}$$

- 12.32 Given the magnitude characteristic in Fig. P12.32, find  $H(j\omega)$ .

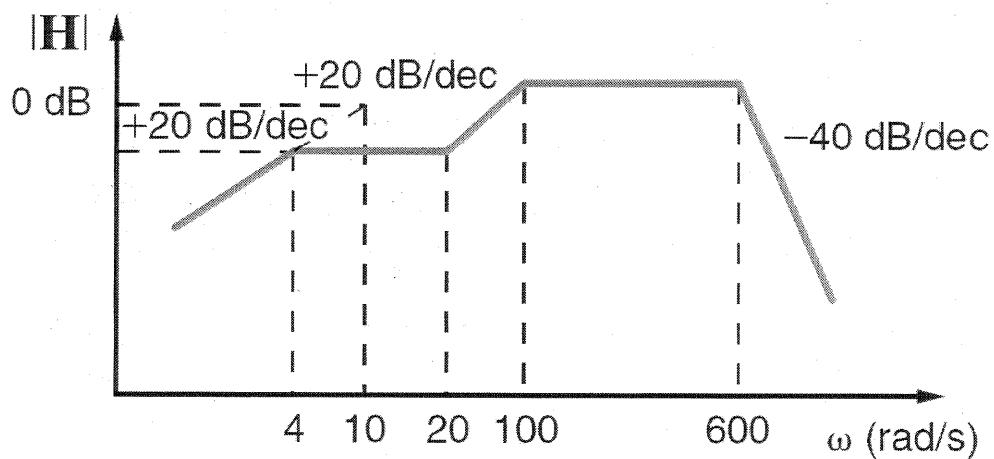


Figure P12.32

SOLUTION:

$$\text{poles at: } \left\{ \begin{array}{l} \omega = 4 \text{ rad/s} \\ 100 \text{ rad/s} \\ 600 \text{ rad/s (double)} \end{array} \right\}$$

$$\text{zeros at: } \left\{ \begin{array}{l} \omega = 0 \text{ rad/s} \\ 20 \text{ rad/s} \end{array} \right\}$$

$$H(j\omega) = \frac{K(j\omega)(j\omega+20)}{(j\omega+4)(j\omega+100)(j\omega+600)^2}$$

$$\text{At } \omega = 1 \text{ rad/s, } |H| = -20 \text{ dB} = 0.1 = \frac{K(1)(20)}{4(100)(600)^2} \Rightarrow K = 7.2 \times 10^5$$

$$H(j\omega) = \frac{7.2 \times 10^5 (j\omega)(j\omega+20)}{(j\omega+4)(j\omega+100)(j\omega+600)^2}$$

12.33 Determine  $H(j\omega)$  if its magnitude characteristic is shown in Fig. P12.33.

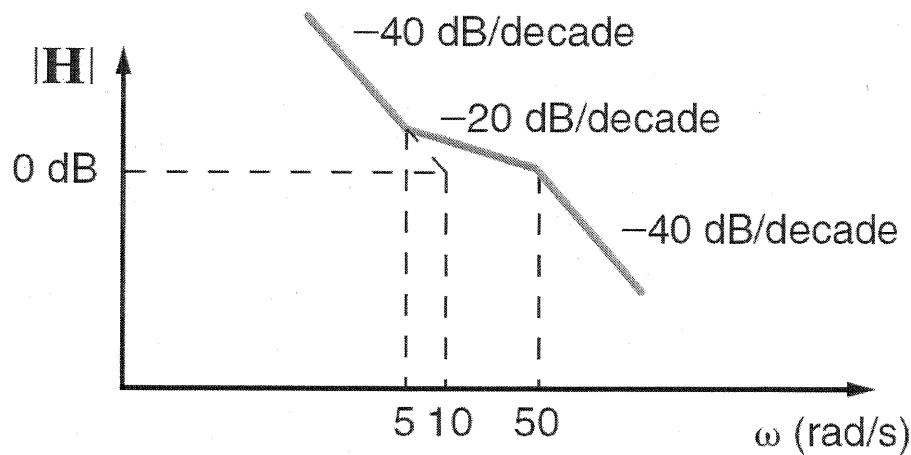


Figure P12.33

SOLUTION:

poles at:  $\left\{ \begin{array}{l} \omega = 0 \text{ rad/s (double)} \\ \omega = 50 \text{ rad/s} \end{array} \right\}$  zero at:  $\left\{ s = 5 \text{ rad/s} \right\}$

$$H(j\omega) = \frac{K(j\omega + s)}{(j\omega)^2 (j\omega + 50)}$$

$$\text{at } \omega = 1 \text{ rad/s}, |H| = 40 \text{ dB} = 100 = \frac{K(5)}{(1)^2 (50)} \Rightarrow K = 1000$$

$$H(j\omega) = \frac{1000(j\omega + 5)}{(j\omega)^2 (j\omega + 50)}$$

- 12.34 Find  $\mathbf{G}(j\omega)$  for the magnitude characteristic shown in Fig. P12.34. **CS**

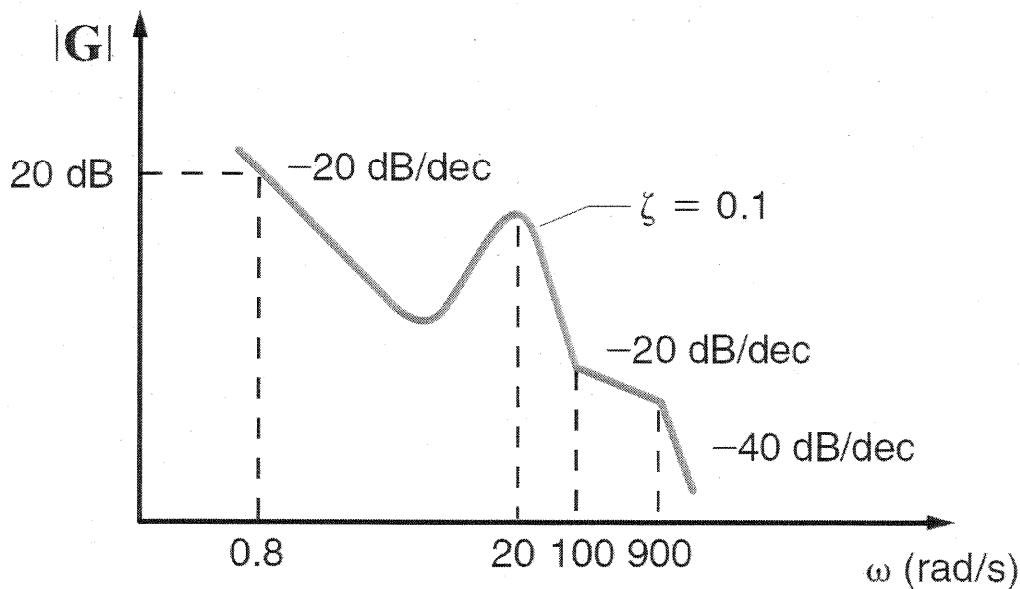


Figure P12.34

SOLUTION:

Simple poles:  $\left\{\begin{array}{l} \omega = 0 \text{ r/s} \\ \omega = 900 \text{ r/s} \end{array}\right\}$  zeros at 100 r/s (double)

Complex conjugate poles at  $\omega = 20 \text{ r/s}$  with  $\zeta = 0.1$

$$\text{or } -1 - \left(\frac{\omega}{20}\right)^2 + 2j(0.1)/20 \Rightarrow ((j\omega)^2 + j4\omega + 400)/400$$

$$G(j\omega) = \frac{K(j\omega + 100)^2}{j\omega(j\omega + 900)[(j\omega)^2 + j4\omega + 400]}$$

$$\text{at } \omega = 0.8 \text{ r/s}, |G| = 20 \text{ dB} = 10 = K(100)^2 / \{(0.8)(900)(400)\}$$

$$K = 288$$

$$G(j\omega) = \boxed{\frac{288(j\omega + 100)^2}{j\omega(j\omega + 900)[(j\omega)^2 + j4\omega + 400]}}$$

- 12.35 A series  $RLC$  circuit resonates at 1000 rad/s. If  $C = 20 \mu\text{F}$ , and it is known that the impedance at resonance is  $2.4 \Omega$ , compute the value of  $L$ , the  $Q$  of the circuit, and the bandwidth.

SOLUTION:

$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

at resonance,  $\omega_0 = \frac{1}{\sqrt{LC}} = 1000 \Rightarrow \boxed{L = 50 \text{ mH}}$

also  $Z(j\omega_0) = R = 2.4 \Omega$

$$Q = \frac{\omega_0 L}{R} = \frac{1000(50 \times 10^{-3})}{2.4} \quad \boxed{Q = 20.8}$$

$$\text{BW} = \frac{\omega_0}{Q} \quad \boxed{\text{BW} = 48 \text{ rad/s}}$$

- 12.36 A series resonant circuit has a  $Q$  of 120 and a resonant frequency of 10,000 rad/s. Determine the half-power frequencies and the bandwidth of the circuit.

---

SOLUTION:  $\omega_0 = 10 \text{ k r/s}$

$$\text{BW} = \omega_0/Q$$

$$\boxed{\text{BW} = 83.3 \text{ r/s}}$$


$$\omega_{L0} = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$\boxed{\omega_{L0} = 9958 \text{ r/s}}$$

$$\omega_{HI} = \omega_0^2/\omega_{L0} \quad \Rightarrow$$

$$\boxed{\omega_{HI} = 10.04 \text{ kr/s}}$$


- 12.37** The series RLC circuit in Fig. P12.37 is driven by a variable-frequency source. If the resonant frequency of the network is selected as  $\omega_0 = 1600 \text{ rad/s}$ , find the value of  $C$ . In addition, compute the current at resonance and at  $\omega_0/4$  and  $4\omega_0$ . **PSV**

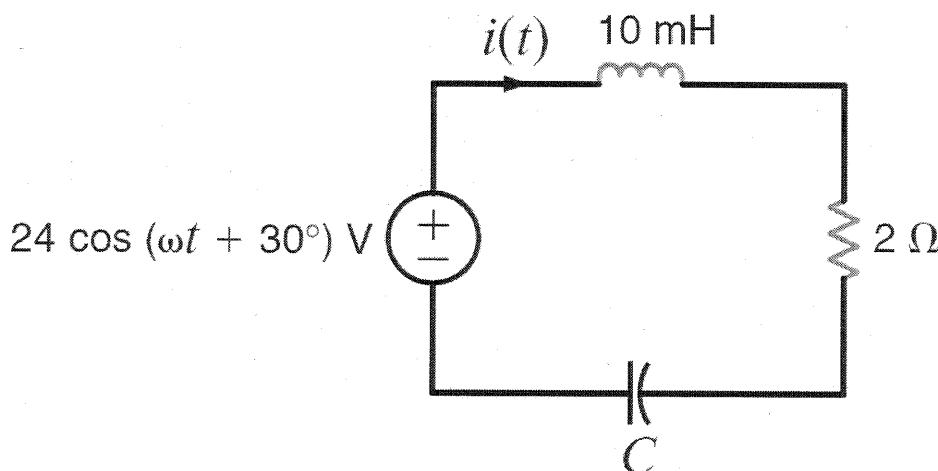

**Figure P12.37**

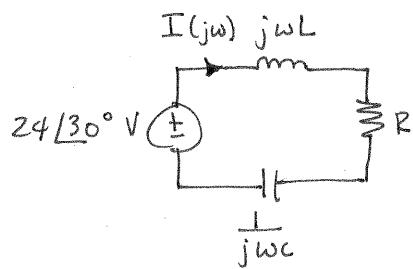**SOLUTION:**

$$\omega_0 = 1600 = \frac{1}{\sqrt{LC}} \Rightarrow C = 39 \mu\text{F}$$



$$I(j\omega) = \frac{24 \angle 30^\circ}{j(\omega L - \frac{1}{\omega C}) + R}$$

$\omega/\omega_0$	$I(j\omega)$
1	$12 \angle 30^\circ \text{ A}$
$1/4$	$0.400 \angle 118^\circ \text{ A}$
4	$0.400 \angle -58^\circ \text{ A}$

- 12.38** Given the series RLC circuit in Fig. P12.38, (a) derive the expression for the half-power frequencies, the resonant frequency, the bandwidth, and the quality factor for the transfer characteristic  $\mathbf{I}/\mathbf{V}_{in}$  in  $R$ ,  $L$ ,  $C$ , (b) Compute the quantities in part (a) if  $R = 10 \Omega$ ,  $L = 50 \text{ mH}$ , and  $C = 10 \mu\text{F}$ .

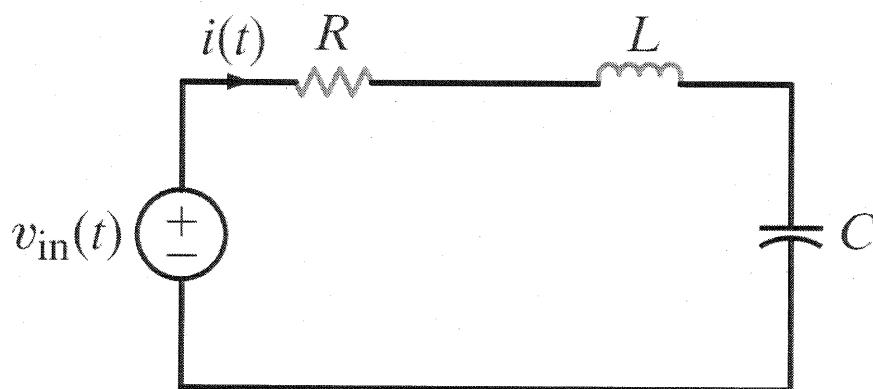


Figure P12.38

SOLUTION: a. Let  $Z = R + j\omega L + \frac{1}{j\omega C}$

At resonance,  $Z = R$ . So  $\omega_0 L + \frac{1}{\omega_0 C} = 0 \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$

$Q$  is defined as  $\frac{\omega_0 L}{R} \Rightarrow \boxed{Q = \frac{1}{R} \sqrt{\frac{L}{C}}}$

$\frac{I}{V_{in}} = \frac{1}{Z(j\omega)}$  At half power,  $\left| \frac{I}{V_{in}} \right| = \frac{1}{\sqrt{2}R} = \frac{1}{|Z(j\omega)|}$

so,  $|R + j(\omega L - 1/\omega C)| = \sqrt{2}R = R |1 + j(\omega L/R - 1/\omega_0 C)|$

$\sqrt{2} = |1 + jQ(\omega/\omega_0 - \omega_0/\omega)| \quad \text{or} \quad Q(\omega/\omega_0 - \omega_0/\omega) = \pm 1$

Quadratic equation yields  $\omega_{L0} = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$

$\omega_{H1} = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$

In terms of  $R, L, C \rightarrow \frac{\omega_0}{Q} = R/L$

$$\omega_{LO} = \left[ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$\omega_{HI} = \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$BW = \omega_{HI} - \omega_{LO} = \omega_0/Q$$

$$BW = R/L$$

b.  $R = 10\Omega$     $L = 50mH$     $C = 10\mu F$

$$\omega_0 = 1414 \text{ r/s}$$

$$Q = 7.07$$

$$BW = 200 \text{ r/s}$$

$$\omega_{HI} = 1518 \text{ r/s}$$

$$\omega_{LO} = 1318 \text{ r/s}$$

- 12.39 Given the network in Fig. P12.39, find  $\omega_0$ ,  $Q$ ,  $\omega_{\max}$ , and  $|V_o|_{\max}$ . cs

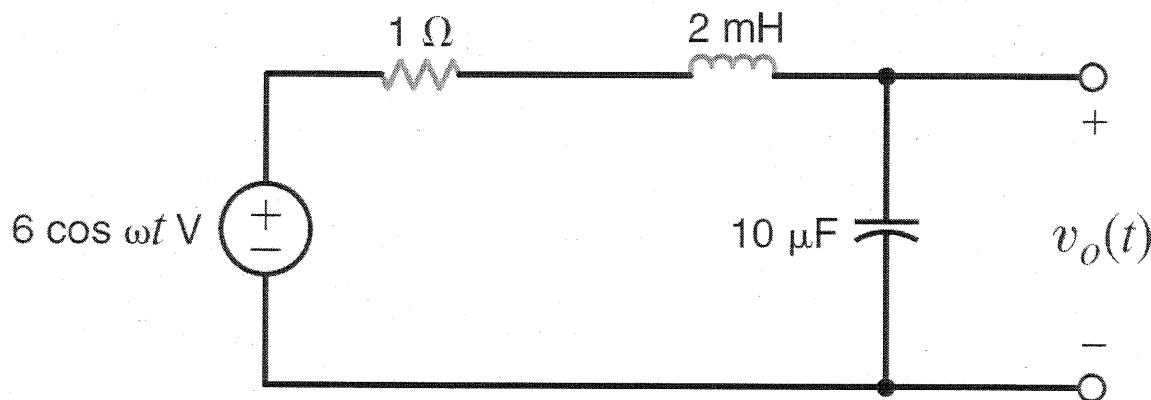


Figure P12.39

SOLUTION:

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{\omega_0 = 7.07 \text{ kr/s}}$$

$$Q = \omega_0 L / R \Rightarrow \boxed{Q = 14.14}$$

$$\omega_{\max} = \omega_0 \sqrt{1 - \frac{1}{2Q^2}} \Rightarrow \boxed{\omega_{\max} = 7.06 \text{ kr/s}}$$

$$|V_{o\max}| = \frac{Q |V_s|}{\sqrt{1 - \frac{1}{4Q^2}}} \quad |V_s| = 6 \text{ V}$$

$$\boxed{|V_{o\max}| = 84.9 \text{ V}}$$

**12.40** A series  $RLC$  circuit is driven by a signal generator.

The resonant frequency of the network is known to be 1600 rad/s, and at that frequency the impedance seen by the signal generator is  $5 \Omega$ . If  $C = 20 \mu\text{F}$ , find  $L$ ,  $Q$ , and the bandwidth.

**SOLUTION:**


$$Z = R + j(\omega L - 1/\omega C) \quad \text{at } \omega = 1600 \text{ rad/s}, \quad Z = 5 = R$$

$$\text{So, } 1600 \text{ rad/s} = \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} \quad \boxed{L = 19.5 \text{ mH}}$$

$$Q = \frac{\omega_0 L}{R} \Rightarrow \boxed{Q = 6.24}$$

$$BW = \frac{\omega_0}{Q} \Rightarrow \boxed{BW = 256 \text{ rad/s}}$$

- 12.41** A variable-frequency voltage source drives the network in Fig. P12.41. Determine the resonant frequency,  $Q$ , BW, and the average power dissipated by the network at resonance.

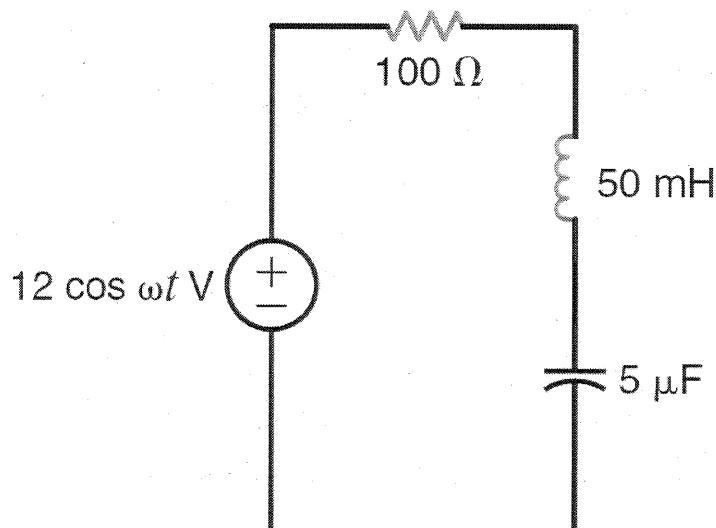


**Figure P12.41**

**SOLUTION:**

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{\omega_0 = 2 \text{ kr/s}}$$

$$Q = \omega_0 L / R \Rightarrow \boxed{Q = 1}$$
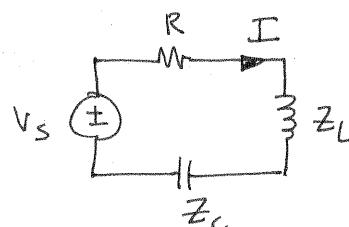
$$\text{BW} = \omega_0 / Q \Rightarrow \boxed{\text{BW} = 2 \text{ kr/s}}$$



$$\text{At resonance, } Z = R = 100 \Omega \quad I = \frac{V_s}{R} = \frac{12 \angle 0^\circ}{100} = 0.12 \angle 0^\circ \text{ A}$$

$$P = \frac{|I|^2 R}{2} \quad \boxed{P = 720 \text{ mW}}$$

- 12.42 A parallel RLC resonant circuit with a resonant frequency of 20,000 rad/s has an admittance at resonance of 1 mS. If the capacitance of the network is 2  $\mu\text{F}$ , find the values of  $R$  and  $L$ . **PSV**

SOLUTION:  $\omega_0 = 20 \text{ kr/s}$        $Y(j\omega_0) = 10^{-3} \text{ S} = 1/R \Rightarrow R = 1 \text{ k}\Omega$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow L = 1.25 \text{ mH}$$

- 12.43 A parallel  $RLC$  resonant circuit has a resistance of  $200 \Omega$ . If it is known that the bandwidth is  $80 \text{ rad/s}$  and the lower half-power frequency is  $800 \text{ rad/s}$ , find the values of the parameters  $L$  and  $C$ .

---


SOLUTION:  $R = 200 \Omega$      $B\omega = 80 \text{ rad/s}$      $\omega_{L_0} = 800 \text{ rad/s}$

$$B\omega = \frac{1}{2C} \Rightarrow C = 62.5 \mu\text{F}$$

$$\omega_{H\pm} = \omega_{L_0} + B\omega = 880 \text{ rad/s} \quad \omega_0 = \sqrt{\omega_{H\pm}\omega_{L_0}} = 839 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow L = 22.7 \text{ mH}$$

- 12.44** In the network in Fig. P12.44, the inductor value is 10 mH, and the circuit is driven by a variable-frequency source. If the magnitude of the current at resonance is 12 A,  $\omega_0 = 1000$  rad/s, and  $L = 10$  mH, find  $C$ ,  $Q$ , and the bandwidth of the circuit. **cs**

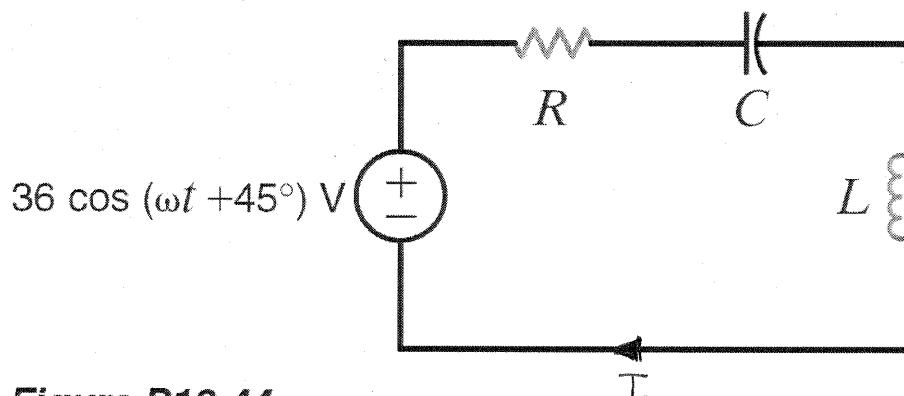

**Figure P12.44**

SOLUTION:  $Z = R + j(\omega L - 1/\omega C)$

at  $\omega = \omega_0$ ,  $Z = R$  and  $|I| = 36/R = 12 \Rightarrow R = 3 \Omega$

$$Q = \omega_0 L / R \Rightarrow Q = 3.33$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega_0^2 L} \Rightarrow C = 100 \mu F$$

$$BW = \frac{\omega_0}{Q} \Rightarrow BW = 300 \text{ rad/s}$$


**12.45** A parallel  $RLC$  circuit, which is driven by a variable-frequency 2-A current source, has the following values:  $R = 1 \text{ k}\Omega$ ,  $L = 400 \text{ mH}$ , and  $C = 10 \mu\text{F}$ . Find the bandwidth of the network, the half-power frequencies, and the voltage across the network at the half-power frequencies. **CS**

**SOLUTION:**

$$\text{BW} = \frac{1}{RC} \Rightarrow \boxed{\text{BW} = 100 \text{ r/s}} \quad \omega_0 = \frac{1}{\sqrt{LC}} = 500 \text{ r/s}$$

$$\Phi = \omega_0 / \text{BW} = 5 \quad \omega_{HP} = \omega_0 \left[ \frac{1}{2\Phi} + \sqrt{\left( \frac{1}{2\Phi} \right)^2 + 1} \right] = 552 \text{ r/s}$$
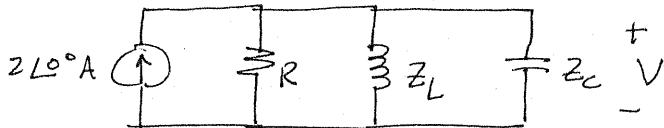
$$\boxed{\omega_{HP} = 552 \text{ r/s}} \quad \omega_{LO} = \omega_0^2 / \omega_{HP} \Rightarrow \boxed{\omega_{LO} = 452 \text{ r/s}}$$



$$Y = \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \quad V = I/Y = 2∠0° / Y$$

$$Y(j\omega_{HP}) = 1 + j1 \text{ mS}$$

$$\boxed{V(j\omega_{HP}) = 1414 \angle -45^\circ \text{ V}}$$

$$Y(j\omega_{LO}) = 1 - j1 \text{ mS}$$

$$\boxed{V(j\omega_{LO}) = 1414 \angle +45^\circ \text{ V}}$$

- 12.46** A parallel  $RLC$  circuit, which is driven by a variable-frequency 2-A current source, has the following values:  $R = 1 \text{ k}\Omega$ ,  $L = 100 \text{ mH}$ , and  $C = 10 \mu\text{F}$ . Find the bandwidth of the network, the half-power frequencies, and the voltage across the network at the half-power frequencies. **CS**

SOLUTION:

$$BW = \frac{1}{RC} \Rightarrow BW = 100 \text{ r/s} \quad \omega_0 = \frac{1}{\sqrt{LC}} = 1000 \text{ r/s}$$

$$Q = \omega_0 / BW = 10$$

$$\omega_{HF} = \omega_0 \left[ \frac{1}{Z_Q} + \sqrt{\left(\frac{1}{Z_Q}\right)^2 + 1} \right] \Rightarrow \omega_{HF} = 1051 \text{ r/s}$$

$$\omega_{LO} = \omega_0^2 / \omega_{HF} \Rightarrow \omega_{LO} = 951 \text{ r/s}$$

$$Y = \frac{1}{R} + \frac{1}{Z_L} + Z_C \quad V = I/Y \quad E = 2L^0 \text{ A}$$

$$Y(j\omega_{HF}) = 1 + j1 \text{ ms} \quad V = \sqrt{2} \angle -45^\circ \text{ kV @ } \omega_{HF}$$

$$Y(j\omega_{LO}) = 1 - j1 \text{ ms} \quad V = \sqrt{2} \angle +45^\circ \text{ kV @ } \omega_{LO}$$

- 12.47** Consider the network in Fig. P12.47. If  $R = 1 \text{ k}\Omega$ ,  $L = 20 \text{ mH}$ ,  $C = 50 \mu\text{F}$ , and  $R_S = \infty$ , determine the resonant frequency  $\omega_0$ , the  $Q$  of the network, and the bandwidth of the network. What impact does an  $R_S$  of  $10 \text{ k}\Omega$  have on the quantities determined?

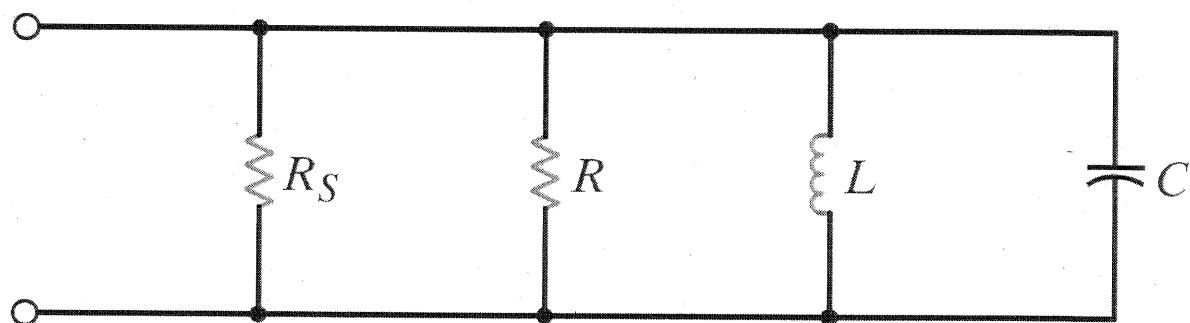


Figure P12.47

SOLUTION:  $\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{\omega_0 = 1000 \text{ r/s}}$   $R_{eq} = R_S // R = 1 \text{ k}\Omega$

$$Q = \omega_0 R_{eq} C = 50 \Rightarrow \boxed{Q = 50} \quad Bw = \omega_0 / Q \Rightarrow \boxed{Bw = 20 \text{ r/s}}$$

If  $R_S = 10 \text{ k}\Omega$ ,  $R_{eq} = 909 \Omega$ .

$\omega_0$  is unchanged.  $\boxed{\omega_0 = 1000 \text{ r/s}}$

$Q$  changes  $\boxed{Q = 45.5}$

$Bw$  changes  $\boxed{Bw = 22.0 \text{ r/s}}$

12.48 The source in the network in Fig. P12.48 is

$i_s(t) = \cos 1000t + \cos 1500t$  A.  $R = 200 \Omega$  and  $C = 500 \mu\text{F}$ . If  $\omega_0 = 1000 \text{ rad/s}$ , find  $L$ ,  $Q$ , and the BW. Compute the output voltage  $v_o(t)$  and discuss the magnitude of the output voltage at the two input frequencies.

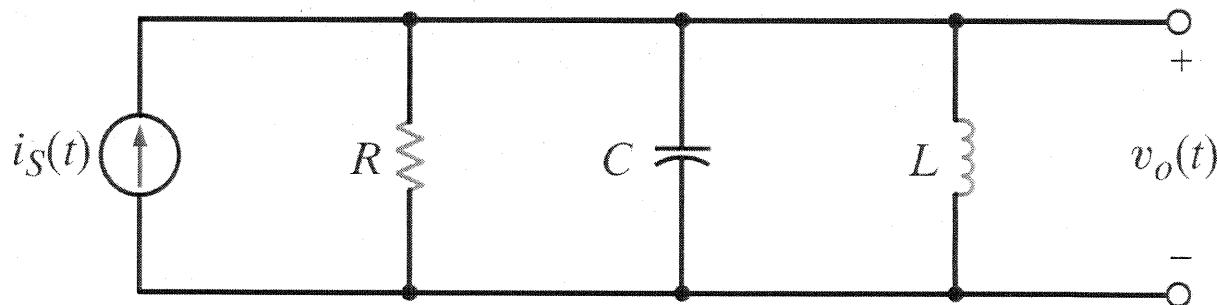


Figure P12.48

SOLUTION:

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow L = 2 \text{ mH}$$

$$\text{BW} = \frac{1}{RC} \Rightarrow \text{BW} = 10 \text{ r/s} \quad Q = \omega_0 / \text{BW} \Rightarrow Q = 100$$

Use superposition. Let  $I_{s1} = 1 \angle 0^\circ$  at 1000 r/s and  $I_{s2} = 1 \angle 0^\circ$  A @ 1500 r/s.

$$Y = \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \quad Y(j1000) = 1/R = 5 \text{ mS} = Y_1$$

$$V_{o1} = I_{s1} / Y_1 = 1 \angle 0^\circ / 5 \times 10^{-3} = 200 \angle 0^\circ \text{ V}$$

$$Y(j1500) = Y_2 = 5 + j417 \text{ mS} \quad V_{o2} = 1 \angle 0^\circ / Y_2 = 2.4 \angle -89.3^\circ \text{ V}$$

$$v_{o1}(t) = 200 \cos 1000t \text{ V} \quad v_{o2}(t) = 2.4 \cos(1500t - 89.3^\circ) \text{ V}$$

$$v_o(t) = v_{o1} + v_{o2} \Rightarrow v_o(t) = 200 \cos 1000t + 2.4 \cos(1500t - 89.3^\circ) \text{ V}$$

Magnitude difference (200 V versus 2.4 V) is due to  $|Y|$  at the two frequencies!

- 12.49 Determine the parameters of a parallel resonant circuit that has the following properties:  $\omega_0 = 2 \text{ Mrad/s}$ ,  $\text{BW} = 20 \text{ rad/s}$ , and an impedance at resonance of  $2000 \Omega$ . **CS**

---

SOLUTION:

$$\text{At Resonance, } Z = R = 2000 \Omega \quad R = 2000 \Omega$$

$$\text{BW} = \frac{1}{RC} \Rightarrow C = \frac{1}{(\text{BW})R} \Rightarrow C = 25 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow L = 10 \text{nH}$$

- 12.50 Determine the value of  $C$  in the network shown in Fig. P12.50 for the circuit to be in resonance.

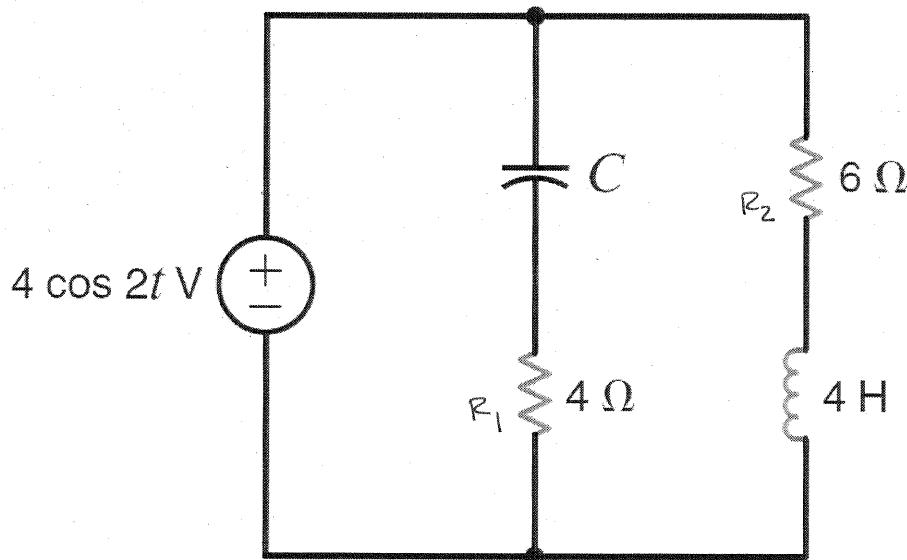


Figure P12.50

SOLUTION:  $\omega = 2 \text{ rad/s}$        $Z_L = j8\Omega$        $Z_C = -j1/2C \Omega$

Let  $Z_1 = Z_C + R_1$  &  $Z_2 = R_2 + Z_L = 6 + j8\Omega$

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{R_1 R_2 + L/C + j(\omega L R_1 - R_2/\omega C)}{R_1 + R_2 + j(\omega L - 1/\omega C)}$$


At resonance,  $Z$  is real. So, phase angle of numerator and denominator are equal.

$$\frac{\omega L R_1 - R_2/\omega C}{R_1 R_2 + L/C} = \frac{\omega L - 1/\omega C}{R_1 + R_2} \Rightarrow \frac{32 - 3/C}{24 + 4/C} = \frac{8 - 1/2C}{10}$$

$$\frac{32C - 3}{24C + 4} = \frac{16C - 1}{20C} \Rightarrow \frac{32C - 3}{6C + 1} = \frac{16C - 1}{5C} \Rightarrow 64C^2 - 25C + 1 = 0$$

$C = \left\{ \begin{array}{l} 345 \text{ mF} \\ 46 \text{ mF} \end{array} \right.$
--

- 12.51 Determine the equation for the nonzero resonant frequency of the impedance shown in Fig. P12.51.

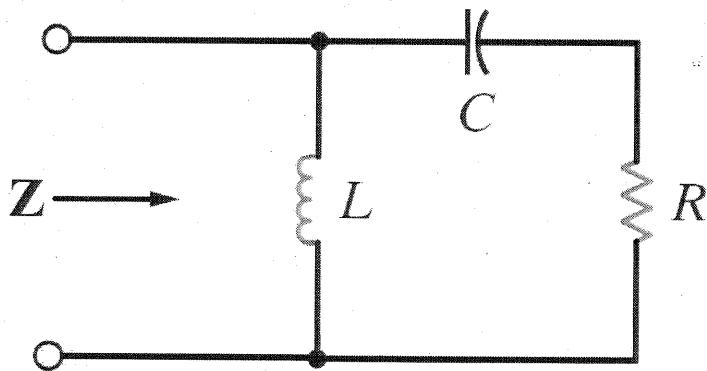

**Figure P12.51**

SOLUTION:


$$Z = \frac{j\omega L (R - j/\omega C)}{R + j(\omega L - 1/\omega C)} = \frac{\frac{L}{C} + j\omega LR}{R + j(\omega L - 1/\omega C)} = \frac{L \left[ \frac{1}{C} + j\omega R \right]}{R + j(\omega L - 1/\omega C)}$$

At resonance,  $\Im Z = 0$ . So,

$$\frac{\omega_0 R}{1/C} = \frac{\omega_0 L - 1/\omega_0 C}{R} \Rightarrow \omega_0 R^2 C = \omega_0 L - \frac{1}{\omega_0 C} \Rightarrow \omega_0^2 (R^2 C^2 - L^2) = -1$$

$$\boxed{\omega_0 = \sqrt{\frac{1}{LC - (RC)^2}}}$$

**12.52** Determine the new parameters of the network shown in Fig. P12.52 if  $Z_{\text{new}} = 10^4 Z_{\text{old}}$ .

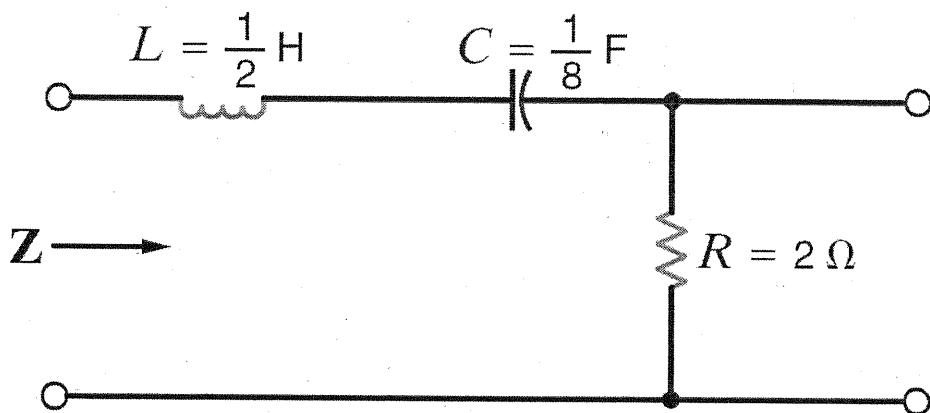

**Figure P12.52**

**SOLUTION:**

$$\text{scale factor} = K_M = Z_{\text{new}} / Z_{\text{old}} = 10^4$$

$$R_{\text{new}} = K_M R_{\text{old}}$$

$$L_{\text{new}} = K_M L_{\text{old}}$$

$$C_{\text{new}} = C_{\text{old}} / K_M$$

$R_{\text{new}} = 20 \text{ k}\Omega$
$L_{\text{new}} = 5 \text{ kH}$
$C_{\text{new}} = 12.5 \mu\text{F}$

- 12.53 Determine the new parameters of the network in Problem 12.52 if  $\omega_{\text{new}} = 10^4 \omega_{\text{old}}$ . **CS**

---

SOLUTION:

$$L_{\text{old}} = 0.5 \text{ H} \quad C_{\text{old}} = 0.125 \text{ F} \quad R_{\text{old}} = 2 \Omega$$

$$\text{Let } K_F = \omega_{\text{new}} / \omega_{\text{old}} = 10^4$$

$$L_{\text{new}} = L_{\text{old}} / K_F$$

$$C_{\text{new}} = C_{\text{old}} / K_F$$

$$R_{\text{new}} = R_{\text{old}}$$

$$L_{\text{new}} = 50 \mu\text{H}$$

$$C_{\text{new}} = 12.5 \mu\text{F}$$

$$R = 2 \Omega$$

- 12.54 Given the network in Fig. P12.54, sketch the magnitude characteristic of the transfer function

$$\mathbf{G}_v(j\omega) = \frac{\mathbf{V}_o(j\omega)}{\mathbf{V}_i(j\omega)}$$

Identify the type of filter.

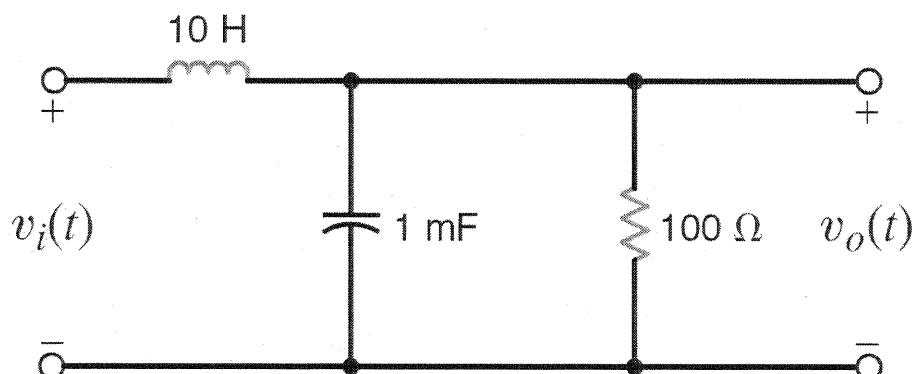


Figure P12.54


SOLUTION:

$\frac{V_o}{V_s} = \frac{\frac{1}{j\omega C}}{1 + \frac{j\omega C}{R} + \frac{1}{j\omega L}} = \frac{\frac{1}{j\omega C}}{1 + \frac{j\omega C}{100} + \frac{1}{j\omega \cdot 10}} = \frac{\frac{1}{j\omega C}}{1 + \frac{100}{\omega^2} + \frac{j\omega}{10}}$

Let  $Z = \frac{100}{100 - j\frac{1000}{\omega}} = \frac{10^3}{10 + j\omega}$

Complex conjugate poles:  $\zeta = \frac{1}{10} \quad \frac{10}{100} = 2\zeta \Rightarrow \zeta = 0.5$

Filter is low-pass

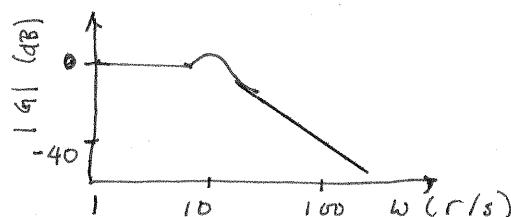

12.55 Given the network in Fig. P12.55, sketch the magnitude characteristic of the transfer function

$$G_v(j\omega) = \frac{V_o}{V_i}(j\omega)$$

Identify the type of filter.


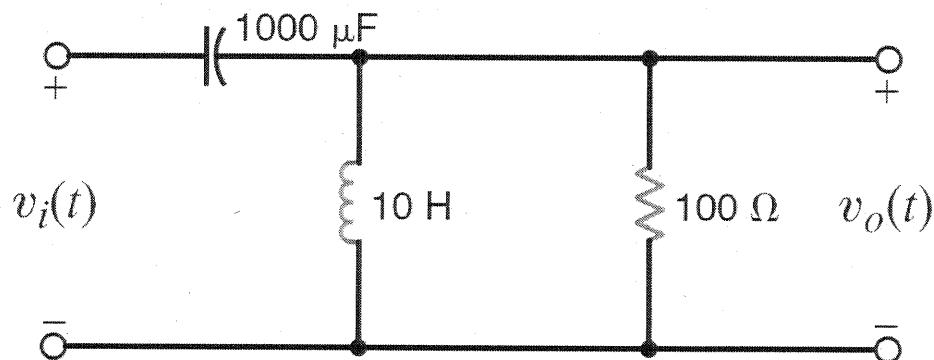



Figure P12.55

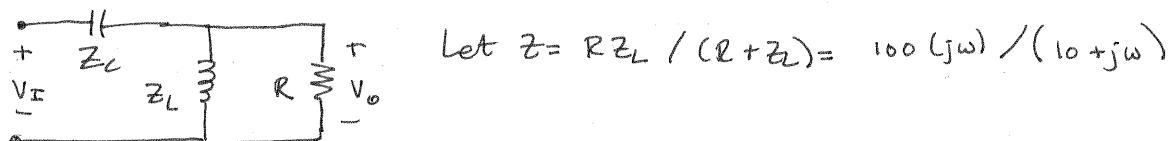SOLUTION:  $Z_L = j\omega(10) \Omega$      $Z_C = 1000 / (j\omega) \Omega$      $R = 100 \Omega$




$$V_o/I_I = G_v(j\omega) = \frac{Z}{(Z+Z_C)} = \frac{(j\omega)^2}{(j\omega)^2 + 10(j\omega) + 100}$$

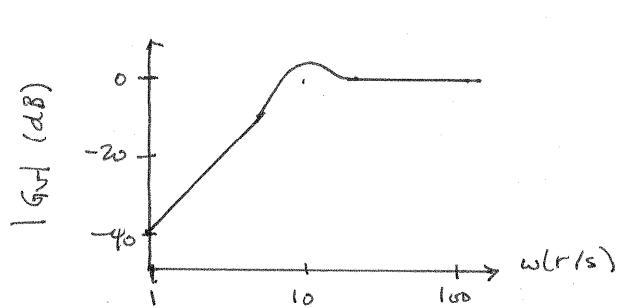Complex conjugate poles at:  $\tau = 1/10$      $2\zeta\tau = 0.1 \Rightarrow \zeta = 0.5$




filter is high pass

**12.56** Determine what type of filter the network shown in Fig. P12.56 represents by determining the voltage transfer function. **CS**

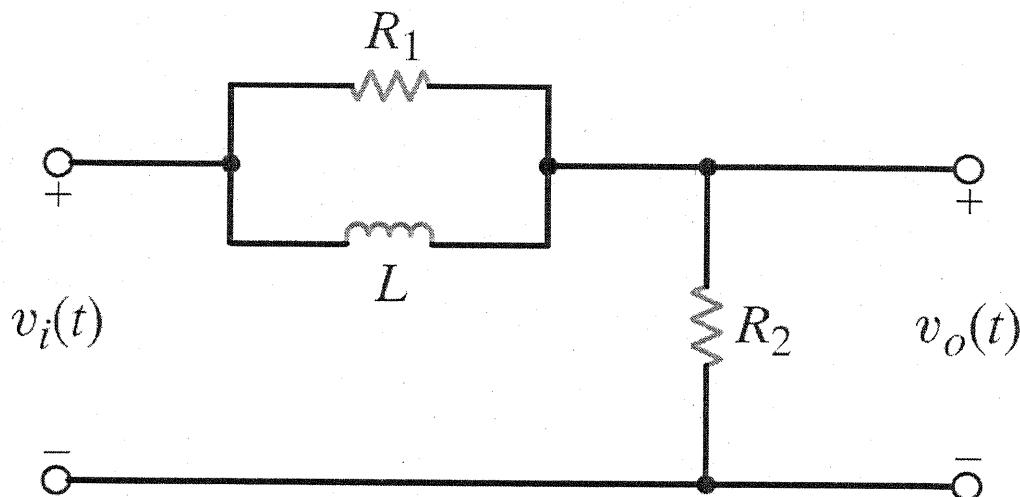

**Figure P12.56**

**SOLUTION:**

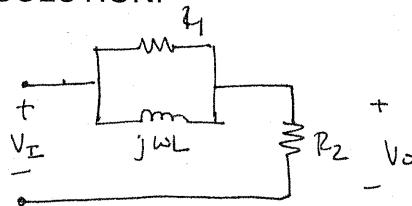


$$\text{Let } z = R_1(j\omega L) / (R_1 + j\omega L)$$

$$\frac{V_o}{V_I} = G_{tr}(j\omega) = \frac{R_2}{R_2 + z}$$


$$G_{tr}(j\omega) = \frac{j\omega LR_1 + R_1 R_2}{j\omega LR_1 + R_1 R_2 + j\omega LR_2} = \frac{(j\omega L + R_1) R_2}{R_1 R_2 + j\omega L (R_1 + R_2)} = \frac{R_2}{R_1 + R_2} \left[ \frac{j\omega + R_1/L}{j\omega + (R_1 R_2)/(R_1 + R_2) / L} \right]$$

Rough sketch

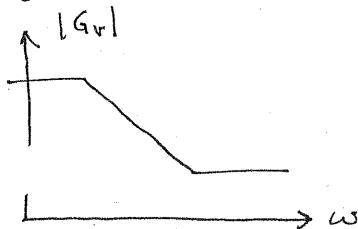

filter is lowpass

- 12.57** Determine what type of filter the network shown in Fig. P12.57 represents by determining the voltage transfer function. **PSV**

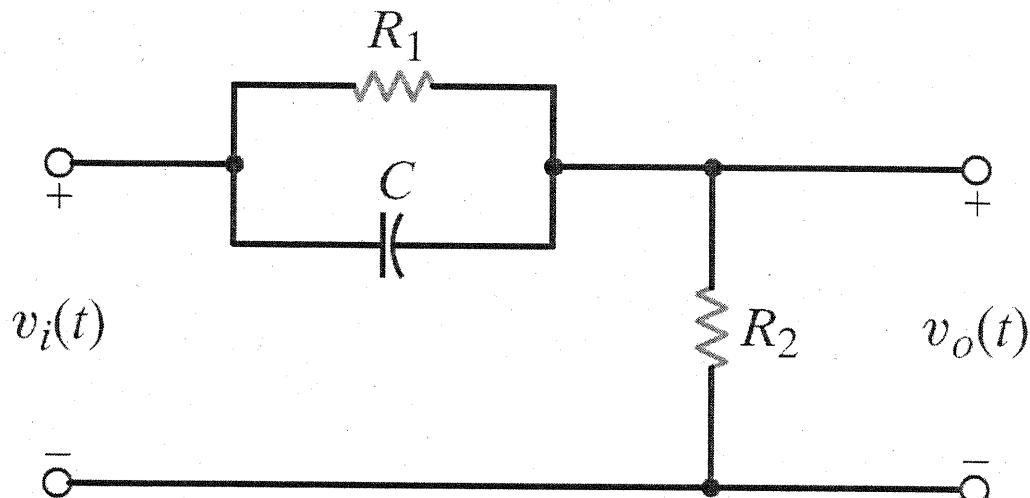


**Figure P12.57**

**SOLUTION:**

Diagram showing the circuit for the solution. The input voltage  $V_I$  is applied across  $R_1$ . The total impedance seen by the input is  $Z_C = \frac{1}{j\omega C}$ . The total output voltage  $V_O$  is across  $R_2$ . The voltage across  $R_2$  is  $V_O$ . The voltage across the parallel combination of  $R_1$  and  $Z_C$  is  $V_I - V_O$ . The current through  $R_2$  is  $\frac{V_O}{R_2}$ . The current through  $R_1$  and  $Z_C$  is  $\frac{V_I - V_O}{R_1 + Z_C}$ . Therefore, the voltage transfer function is  $G_{rl}(j\omega) = \frac{V_O}{V_I} = \frac{R_2}{R_2 + R_1 + Z_C} = \frac{R_2}{R_2 + \frac{R_1}{j\omega C + 1}}$ .

$$G_{rl}(j\omega) = \frac{R_2}{R_2 + \frac{R_1}{j\omega R_1 C + 1}} = \frac{R_2(j\omega R_1 C + 1)}{j\omega R_1 R_2 C + R_1 + R_2} = \frac{j\omega + \frac{1}{R_1 C}}{j\omega + \frac{1}{R_2 C}} \quad R_P = R_1 // R_2$$

Rough sketch

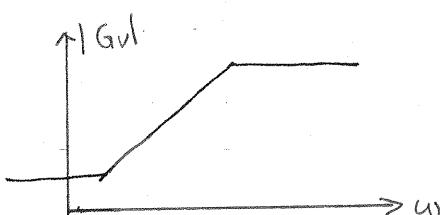

filter is highpass

- 12.58 Given the lattice network shown in Fig. P12.58, determine what type of filter this network represents by determining the voltage transfer function.


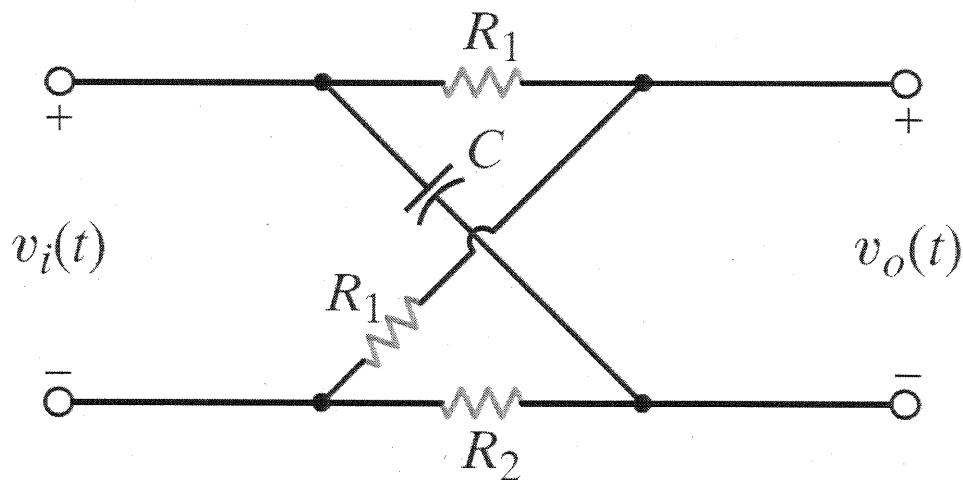


Figure P12.58

SOLUTION:  $z_C = 1/j\omega C$

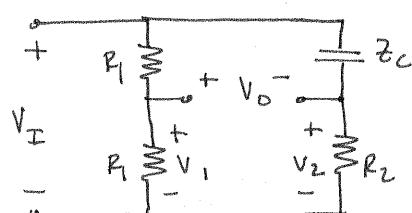

$$V_1 = \frac{V_I R_1}{R_1 + R_1} = V_I / 2$$

$$V_2 = \frac{V_I R_2}{R_2 + z_C} = \frac{V_I (j\omega R_2 C)}{j\omega R_2 C + 1}$$

$$V_o = V_1 - V_2 = V_I \left[ \frac{1}{2} - \frac{j\omega R_2 C}{j\omega R_2 C + 1} \right] = V_I \left\{ \frac{1}{2} \left[ \frac{1 - j\omega C R_2}{1 + j\omega C R_2} \right] \right\}$$

$$G_V = V_o / V_I = \frac{1}{2} \left[ \frac{1 - j\omega C R_2}{1 + j\omega C R_2} \right]$$

$|G_V|$  is independent of  $\omega$ !

All pass filter

- 12.59** Given the network in Fig. P12.59, and employing the voltage follower analyzed in Chapter 4, determine the voltage transfer function and its magnitude characteristic. What type of filter does the network represent?

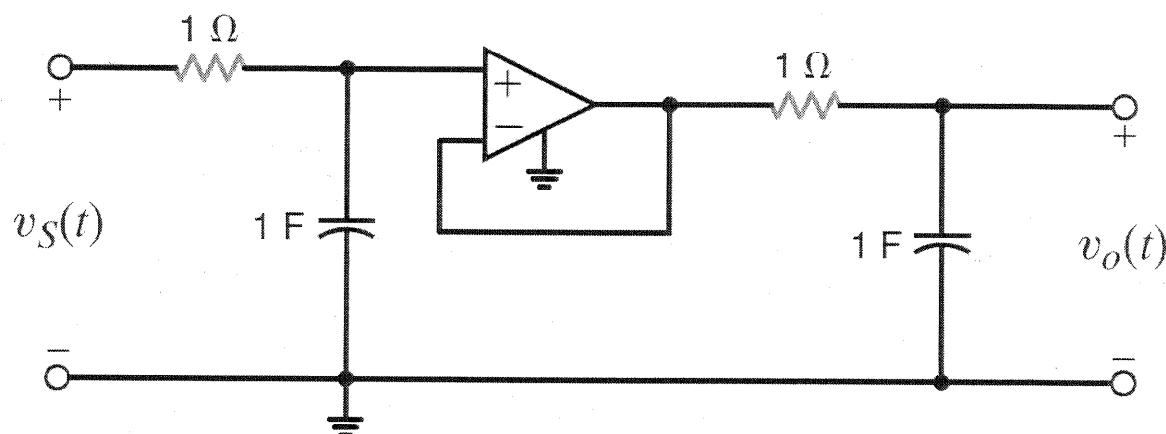


Figure P12.59


**SOLUTION:**

$$\frac{V_1}{V_s} = \frac{1/j\omega}{1 + 1/j\omega} = \frac{1}{j\omega + 1}$$

$$\frac{V_o}{V_1} = \frac{1/j\omega}{1 + 1/j\omega} = \frac{1}{j\omega + 1}$$

$$\frac{V_o}{V_s} = \frac{1}{(j\omega + 1)^2} = G_{v_s}$$

low pass filter

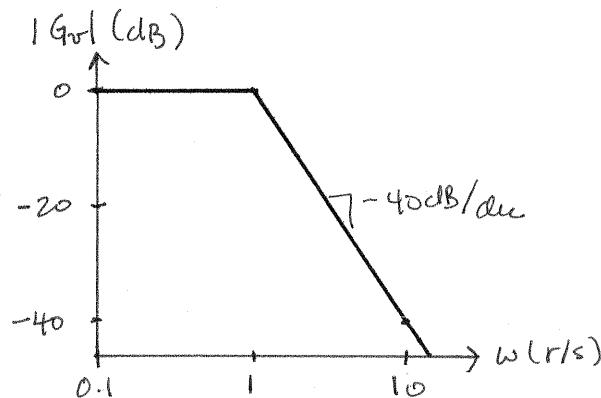

12.60 Given the network in Fig. P12.60, find the transfer function

$$\frac{V_o}{V_i} (j\omega)$$

and determine what type of filter the network represents.

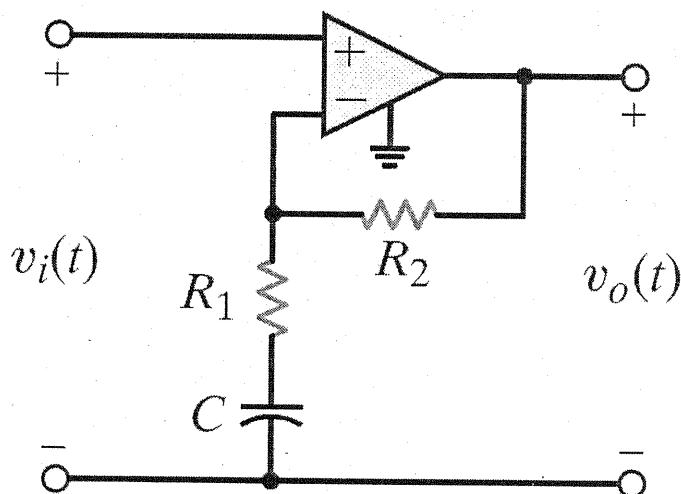


Figure P12.60


SOLUTION: Let  $Z_1 = R_1 + \frac{1}{j\omega C}$

$$\frac{V_o}{V_i} = G_{vV} (j\omega) = 1 + \frac{R_2}{Z_1} = 1 + \frac{j\omega C R_2}{j\omega C R_1 + 1} = \frac{j\omega C (R_1 + R_2) + 1}{j\omega C R_1 + 1} = G_V(j\omega)$$

$$G_{vV} = \left(1 + \frac{R_2}{R_1}\right) \frac{\frac{j\omega + \frac{1}{C(R_1 + R_2)}}{j\omega + \frac{1}{CR_1}}}{j\omega + \frac{1}{CR_1}}$$

High pass filter

Rough sketch

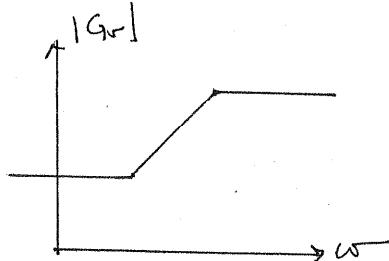

- 12.61 Repeat Problem 12.55 for the network shown in Fig. P12.61.

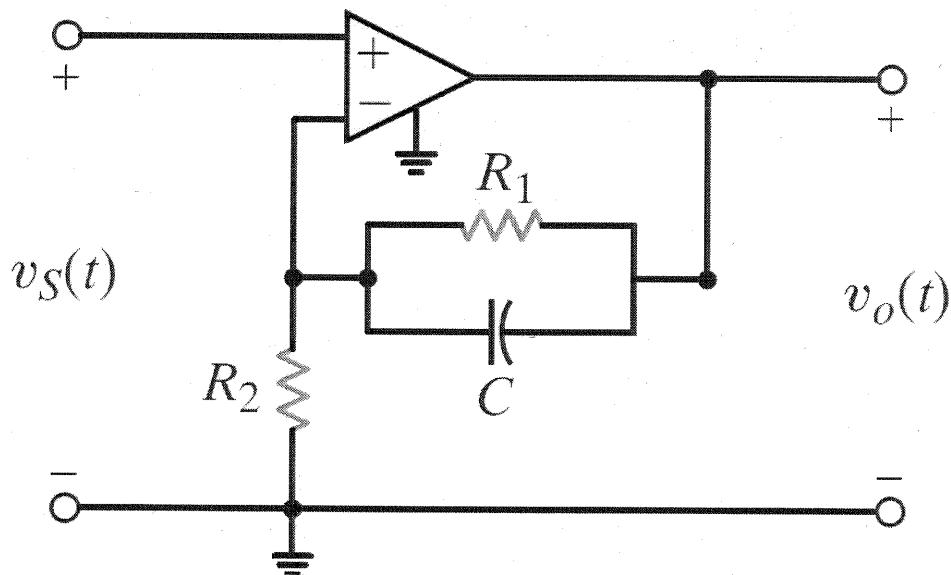


Figure P12.61

SOLUTION:


$$\text{Let } z_2 = R_1 (1/j\omega C) / (R_1 + 1/j\omega C) = R_1 / (j\omega C R_1 + 1)$$

$$\frac{V_o}{V_I} = G_v(j\omega) = 1 + \frac{z_2}{R_2} = 1 + \frac{R_1/R_2}{j\omega C R_1 + 1} = \frac{j\omega C R_1 + 1 + R_1/R_2}{j\omega C R_1 + 1}$$

$$G_v(j\omega) = \frac{j\omega + \frac{1}{R_2 C}}{j\omega + \frac{1}{R_1 C}}$$

$$R_p = R_1 // R_2$$

Lowpass Filter

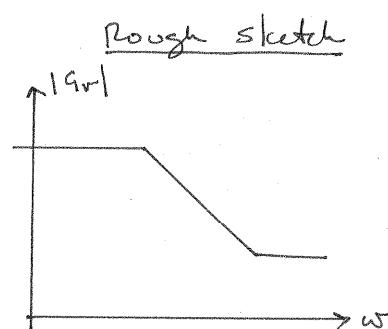

**12.62** Determine the voltage transfer function and its magnitude characteristic for the network shown in Fig. P12.62 and identify the filter properties.

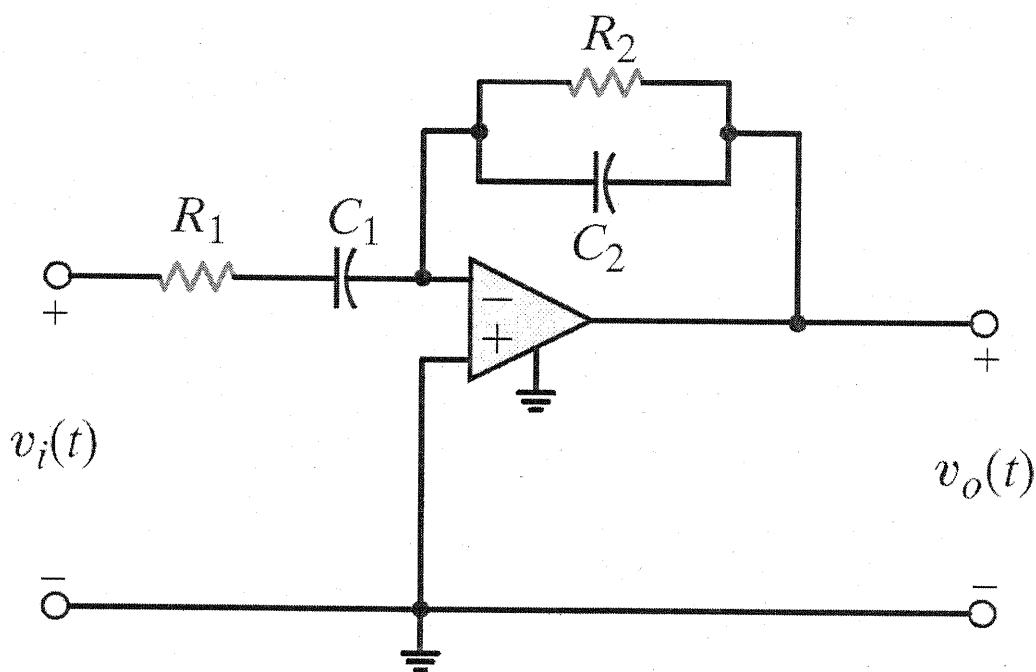



Figure P12.62

SOLUTION: Let  $Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{j\omega C_1 R_1 + 1}{j\omega C_1}$

$$\text{Let } Z_2 = \frac{R_2 \left( \frac{1}{j\omega C_2} \right)}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{j\omega C_2 R_2 + 1}$$

$$G_{vI}(j\omega) = \frac{V_o}{V_I} = -\frac{Z_2}{Z_1} = \boxed{-\frac{j\omega C_1 R_2}{(j\omega C_2 R_2 + 1)(j\omega C_1 R_1 + 1)} = G_{vI}(j\omega)}$$

Bandpass filter

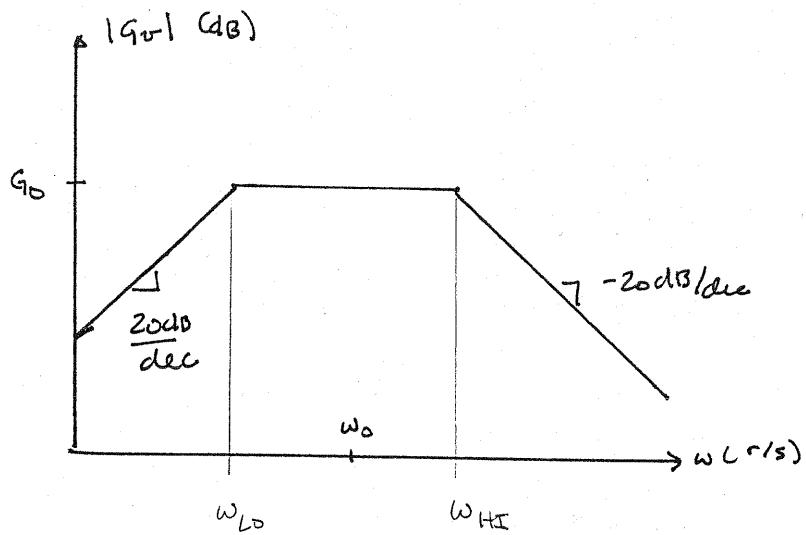

$$G_v(j\omega) = \frac{j\omega C_1 R_2 / C_1 C_2 R_1 R_2}{(j\omega)^2 + j\omega \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2}\right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

Center freq =  $\boxed{\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}}$

$$\frac{\omega_0}{Q} = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} \Rightarrow \boxed{Q = \sqrt{\frac{R_1 R_2 C_1 C_2}{R_1 C_1 + R_2 C_2}}}$$


$$BW = \frac{\omega_0}{Q} \Rightarrow \boxed{BW = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2}}$$

**12.63** An OTA with a transconductance of 1 mS is required.

A 5-V supply is available, and the sensitivity of  $g_m$  to  $I_{ABC}$  is 20.

- (a) What values of  $I_{ABC}$  and  $R_G$  do you recommend?
- (b) If  $R_G$  has a tolerance of +5%, what is the possible range of  $g_m$  in the final circuit?

**SOLUTION:**

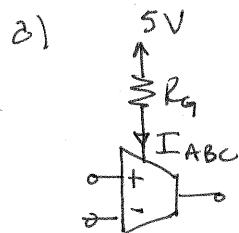

$$I_{ABC} = 5 / R_G \quad g_m = 20 I_{ABC} = 1 \text{ mS}$$

$$I_{ABC} = \frac{10^{-3}}{20} \Rightarrow I_{ABC} = 50 \mu\text{A}$$

$$R_G = 5 / I_{ABC} \Rightarrow R_G = 100 \text{ k}\Omega$$

b)  $g_m = 20 \left( \frac{5}{R_G} \right) = \frac{100}{R_G}$

$$95 \text{ k}\Omega \leq R_G \leq 105 \text{ k}\Omega$$

$$0.952 \text{ mS} \leq g_m \leq 1.053 \text{ mS}$$

**12.64** A particular OTA has a maximum transconductance of 5 mS with a range of 6 decades.

- (a) What is the minimum possible transconductance?
- (b) What is the range of  $I_{ABC}$ ?
- (c) Using a 5-V power supply and resistor to set  $I_{ABC}$ , what is the range of values for the resistor and the power it consumes?

**SOLUTION:**

$$a) \frac{G_{\max}}{G_{\min}} = 10^6 \Rightarrow G_{\min} = \frac{G_{\max}}{10^6} = 5 \text{nS} \quad G_{\min} = 5 \text{nS}$$

$$b) G_m = 20 I_{ABC} \Rightarrow 250 \text{pA} \leq I_{ABC} < 250 \mu\text{A}$$

$$c) S = R I_{ABC} \Rightarrow R = \frac{S}{I_{ABC}} \quad 20 \text{k}\Omega \leq R \leq 20 \text{G}\Omega$$

$$P_R = I_{ABC}^2 R \quad 1.25 \text{nW} \leq P \leq 1.25 \text{mW}$$

12.65 The OTA and 5-V source described in Problem 12.64 are used to create a transconductance of 2.5 mS.

(a) What resistor value is required?

(b) If the input voltage to the amplifier is  $v_{in}(t) = 1.5\cos(\omega t)V$ , what is the output current function?

---

SOLUTION:

$$G_{max} = 5 \text{ mS} \quad G_m = 20I_{ABC} \quad I_{ABC} = 5/R_G$$

a)  $G_m = \frac{100}{R_G} = 2.5 \text{ mS} \Rightarrow R_G = 40 \text{ k}\Omega$

b)  $\frac{i_o(t)}{v_{in}(t)} = G_m = 2.5 \text{ mS}$        $i_o(t) = 3.75 \cos(\omega t) \text{ mA}$

**12.66** A fluid level sensor, used to measure water level in a reservoir, outputs a voltage directly proportional to fluid level. Unfortunately, the sensitivity of the sensor drifts about 10% over time. Some means for tuning the sensitivity is required. Your engineering team produces the simple OTA circuit in Fig. P12.66.

- (a) Show that either  $V_G$  or  $R_G$  can be used to vary the sensitivity.
- (b) List all pros and cons you can think of for these two options.
- (c) What's your recommendation?

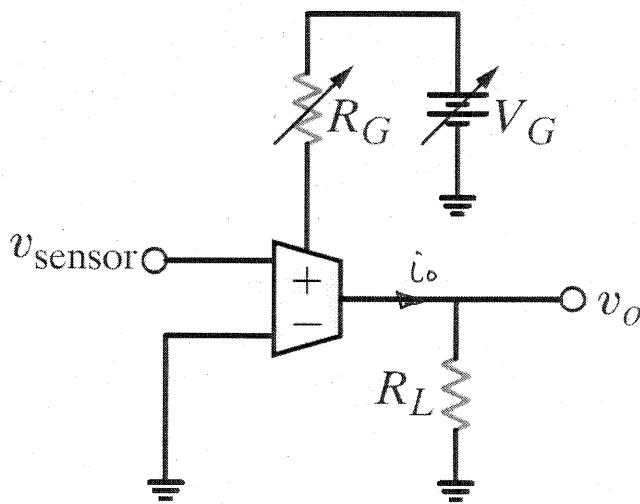


Figure P12.66

---

### SOLUTION:

$$a) v_o = i_o R_L \quad i_o = G_m v_{\text{sensor}} \quad G_m = 20 I_{ABC} \quad I_{ABC} = \frac{V_G}{R_G}$$

$$\text{So, } v_o = \frac{20 V_G R_L}{R_G} v_{\text{sensor}} \quad \text{changing } V_G \text{ or } R_G \text{ will change } v_o(t) !$$

- b) Tuning with  $V_G$  requires a variable voltage source. These are much more costly than a fixed source. On the plus side,  $V_G$  and  $v_o$  are directly related - double  $V_G$  and double  $v_o$ . Tuning with  $R_G$  requires only an inexpensive potentiometer, but the  $R_G - v_o$  relation is indirect.

- c) Based primarily on cost considerations, recommend tuning with  $R_G$ !

**12.67** A circuit is required that can double the frequency of a sinusoidal voltage.

- (a) If  $v_{in}(t) = 1 \sin(\omega t)$ , show that the multiplier circuit in Fig. P12.67 can produce an output that contains a sinusoid at frequency  $2\omega$ .
- (b) We want the magnitude of the double-frequency sinusoid to be 1 V. Determine values for  $R_G$  and  $R_L$  if the transconductance range is limited between  $10 \mu S$  and  $10 mS$ .

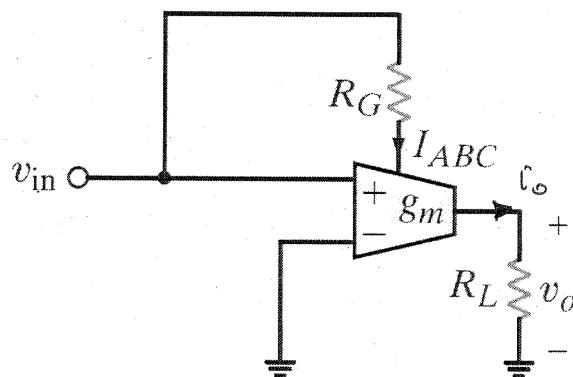


Figure P12.67

---

**SOLUTION:**

a)  $v_o = i_o R_L$      $i_o = g_m v_{in}$      $g_m = 20 I_{ABC}$      $I_{ABC} = v_{in} / R_G$

$$\text{So, } v_o = R_L \frac{20}{R_G} v_{in}^2 = R_L \frac{20}{R_G} \sin^2(\omega t) = \boxed{\frac{10 R_L}{R_G} [1 - \cos(2\omega t)] = v_o}$$

b)  $|v_{in}| = 1V$      $g_{max} = 10 mS = 20 |v_{in}| / R_G = 20 (1) / R_G$

$$R_G = 20 / 10^{-2} \Rightarrow \boxed{R_G = 2 k\Omega}$$

$$|v_o| = 1 = \frac{10 R_L}{R_G} \Rightarrow \boxed{R_L = 200 \Omega} \quad (\text{applies to } \sin(2\omega t) \text{ signal only})$$

**12.68** The frequency doubler in Problem 12.67 uses a two-quadrant multiplier.

- (a) What effect does this have on the output signal?
- (b) The circuit in Fig. P12.68 is one solution. Show that  $v_o$  has a double-frequency term.
- (c) How would you propose to eliminate the other terms?

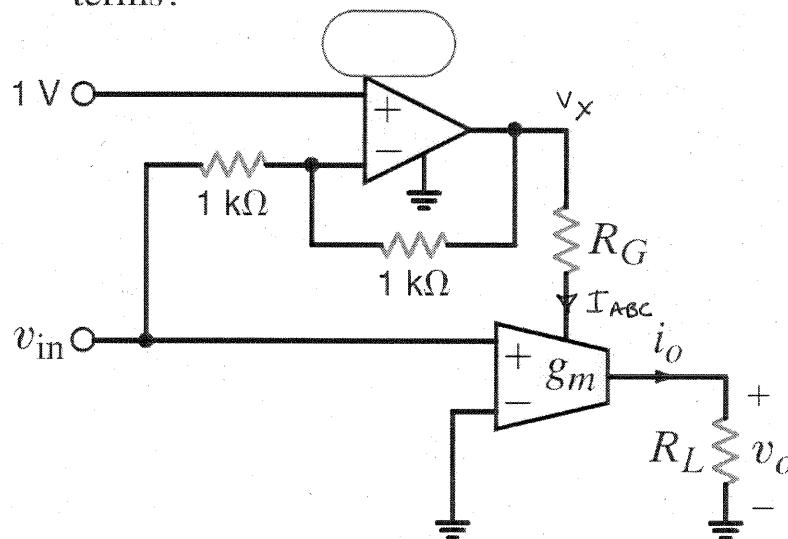


Figure P12.68

---

### SOLUTION:

a) In problem 12.67, the negative half-cycles of  $v_{in}(t)$  "try" to create a  $I_{ABC} < 0$ . This is not possible. The multiplier works only when  $v_{in}(t) > 0$ .

$$b) v_x = 1 \left( 1 + \frac{1000}{1000} \right) - v_{in} \left( \frac{1000}{1000} \right) = 2 - v_{in}$$

If as in 12.67,  $v_{in}(t) = 1 \sin(\omega t) V$ ,  $v_x$  is always  $> 0$  and so is  $I_{ABC}$ .

$$v_o = i_o R_L = g_m v_{in} R_L = 20 I_{ABC} v_{in} R_L = 20 v_x R_L v_{in} / R_G$$

$$v_o = 20 (R_L / R_G) [2 \sin(\omega t) - \frac{1}{2} + \frac{1}{2} \cos(\omega t)]$$

c) use a highpass filter to reject the dc &  $\sin(\omega t)$  terms!

**12.69** In Fig. P12.69,  $V_x$  is a dc voltage. The circuit is intended to be a dc wattmeter where the output voltage value equals the power consumed by  $R_L$  in watts.

- (a) The  $g_m - I_{ABC}$  sensitivity is 20 S/A. Find  $R_G$  such that  $I_x/I_1 = 10^4$ .
- (b) Choose  $R$  such that 1 V at  $V_o$  corresponds to 1 W dissipated in  $R_L$ .

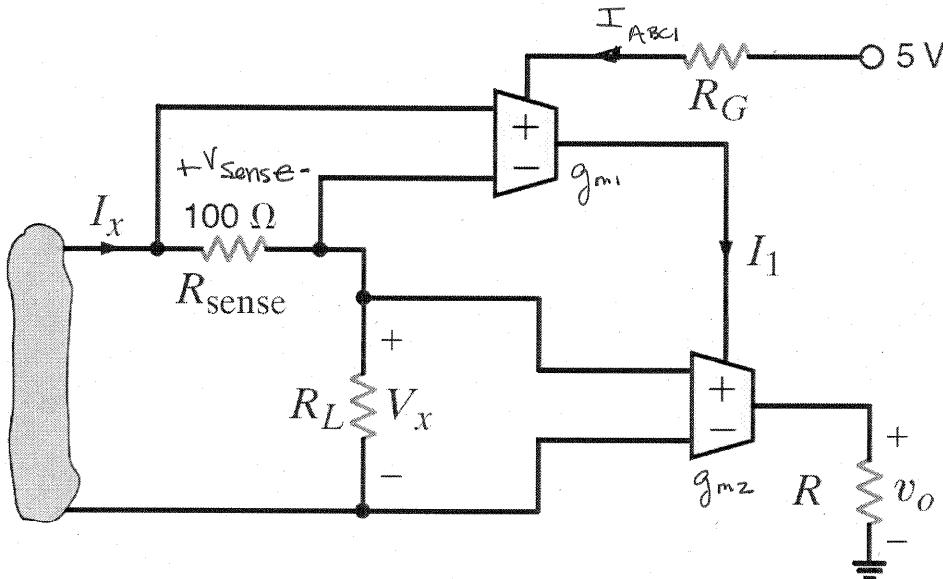


Figure P12.69

SOLUTION:

$$a) V_{sense} = 100 I_x \quad I_1 = g_{m1} V_{sense} = \frac{20(5)}{R_g} V_{sense} = \frac{10^4 I_x}{R_g}$$

$$\frac{I_x}{I_1} = 10^4 = \frac{R_g}{10^4} \Rightarrow R_g = 100 M\Omega$$

$$b) V_o = V_x g_{m2} R = V_x (20 I_1) R = V_x \frac{I_x}{10^4} (20 R) = P_L \left( \frac{20 R}{10^4} \right)$$

$$1V = (1W) \left( \frac{20R}{10^4} \right) \Rightarrow R = 500 \Omega$$

- 12.70** The automatic gain control circuit in Fig. P12.70 is used to limit the transconductance,  $i_o/v_{in}$ .

- Find an expression for  $v_o$  in terms of  $v_{in}$ ,  $R_G$ , and  $R_L$ .
- Express the asymptotic transconductance,  $i_o/v_{in}$ , in terms of  $R_G$  and  $R_L$  at  $v_{in} = 0$  and as  $v_{in}$  approaches infinity. Given  $R_L$  and  $R_G$  values in the circuit diagram, what are the values of the asymptotic transconductance?
- What are the consequences of your results in (b)?
- If  $v_{in}$  must be no more than  $V_{CC}$  for proper operation, what is the minimum transconductance for the functional circuit?

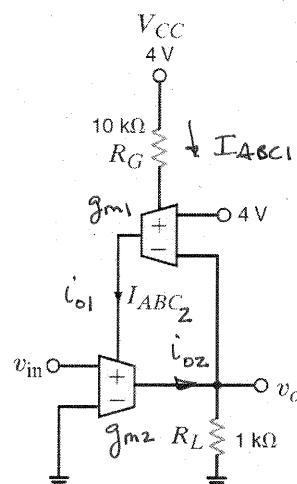


Figure P12.70

**SOLUTION:** a)  $v_o = i_{o2} R_L = v_{in} g_{m2} R_L = 20 I_{ABC2} v_{in} R_L = 20 i_{o1} v_{in} R_L$

$$i_{o1} = g_{m1} (4 - v_o) = 20 I_{ABC1} (4 - v_o) = 20 \left(\frac{4}{R_G}\right) (4 - v_o)$$

$$\text{So, } v_o = 20 v_{in} R_L \left[ \frac{80}{R_G} (4 - v_o) \right] \Rightarrow 6400 v_{in} \frac{R_L}{R_G} - 1600 v_{in} v_o \frac{R_L}{R_G}$$

yields  $v_o (1 + 160 v_{in}) = 640 v_{in} \Rightarrow$

$$v_o = \frac{640 v_{in}}{1 + 160 v_{in}}$$

b)  $G_m = i_o/v_{in} = \frac{v_o}{v_{in}} \left( \frac{1}{R_L} \right) = \frac{0.64}{1 + 160 v_{in}}$

As  $v_{in} \rightarrow 0$ ,  $G_m \rightarrow 0.64$

As  $v_{in} \rightarrow \infty$ ,  $G_m \rightarrow \frac{1}{250 v_{in}}$

$G_m \rightarrow \frac{6400}{R_G}$

$G_m \rightarrow \frac{4}{R_L v_{in}}$

c) When  $V_{in}$  is small,  $G_m$  is high at  $0.64 S$ .


But as  $V_{in}$  increases,  $G_m$  decreases. Eventually,  $i_o$  is limited to  $4/R_L$ .

d)  $G_m \rightarrow \frac{0.64}{1+160(4)} = \boxed{\text{minimum } G_m = 998 \mu S}$

- 12.71** Design a low-pass filter using one resistor and one capacitor that will produce a 4.24-volt output at 159 Hz when 6 volts at 159 Hz is applied at the input.

---

**SOLUTION:**

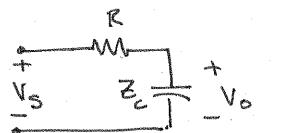

$$V_s = 6 \text{ V} \quad f = 159 \text{ Hz} \quad \omega = 2\pi f = 1 \text{ kr/s}$$


$$V_o = \frac{V_s Z_c}{Z_c + R} = \frac{6 \text{ V}}{j\omega C R + 1}$$

$$|V_o| = \frac{6}{\sqrt{(\omega C)^2 + 1}} = 4.24 \Rightarrow \omega C = 10^{-3} \text{ s}$$

Arbitrarily select  $C = 1 \mu\text{F} \Rightarrow R = 1 \text{k}\Omega$

**12.72** Design a low-pass filter with a cutoff frequency between 15 and 16 kHz.

**SOLUTION:**

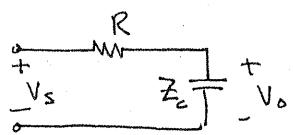


$$\frac{V_o}{V_s} = \frac{Z_c}{R+Z_c} = \frac{1}{j\omega RC + 1} = \frac{V_c}{j\omega + 1/RC}$$

$$\omega_{\text{cutoff}} = \frac{1}{RC}$$

Arbitrarily select  $\omega_{\text{cutoff}} = 2\pi(15.5)\text{krad/s}$  &  $C = 10\text{nF}$   
 yields,  $R = 1.03\text{k}\Omega$

**12.73** Design a high-pass filter with a half-power frequency between 159 and 161 Hz.

**SOLUTION:**

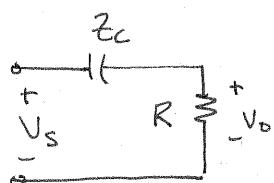


$$\frac{V_o}{V_s} = \frac{R}{R + Z_C} = \frac{j\omega}{j\omega + \frac{1}{RC}} \quad \omega_{cutoff} = \frac{1}{RC}$$

Arbitrarily select  $\omega_{cutoff} = 160 \text{ rad/s}$   
and  $C = 1 \mu\text{F}$

yields,  $R = 6.25 \text{ k}\Omega$

**12.74** Design a band-pass filter with a low cutoff frequency of approximately 4535 Hz and a high cutoff frequency of approximately 5535 Hz.

**SOLUTION:**

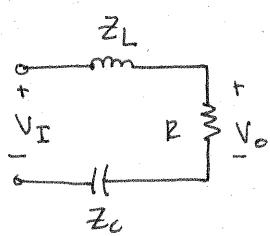

$$\frac{V_o}{V_I} = \frac{R}{j\omega L + R + \frac{1}{j\omega C}} = \frac{j\omega (\frac{R}{L})}{(j\omega)^2 + j\omega (\frac{R}{L}) + \frac{1}{LC}}$$

Series RLC circuit,  $BW = \frac{R}{L} = 2\pi(1000)$


$$\omega_0 = \sqrt{\omega_{HI} \omega_{LO}} = 2\pi \sqrt{f_{HI} f_{LO}} = 31.5 \text{ kHz} = \frac{1}{\sqrt{LC}}$$

Arbitrarily select  $C = 100 \text{ nF}$

yields  $L = 10 \text{ mH}$

and  $R = 62.8 \Omega$

- 12.75** An engineer has proposed the circuit shown in Fig. P12.75 to filter out high-frequency noise. Determine the values of the capacitor and resistor to achieve a 3-dB voltage drop at 23.16 kHz.

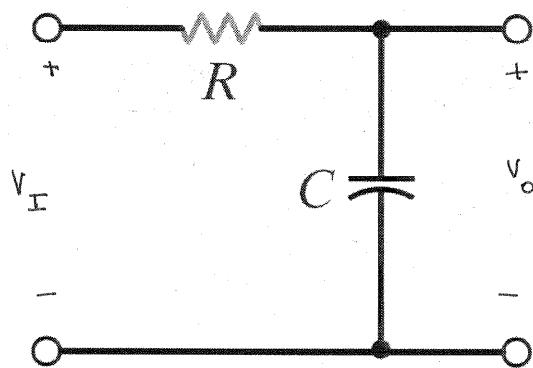

**Figure P12.75**

SOLUTION:  $Z_C = \frac{1}{j\omega C}$

$$\frac{V_O}{V_I} = \frac{Z_C}{Z_C + R} = \frac{1/RC}{j\omega + 1/RC}$$

3 dB down at  $\omega = \frac{1}{RC} = 2\pi(23.16 \times 10^3)$

Arbitrarily select  $C = 1 \text{ nF}$ , yields  $R = 6.87 \text{ k}\Omega$

- 12.76 For the low-pass active filter in Fig. P12.76, choose  $R_2$  and  $C$  such that  $H_o = -7$  and  $f_c = 10 \text{ kHz}$ .

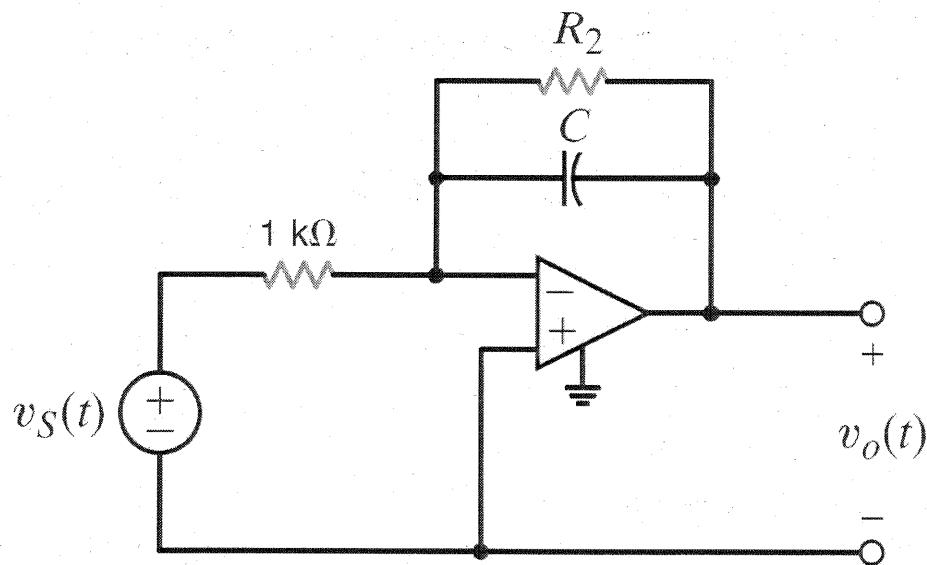


Figure P12.76

SOLUTION: Let  $Z_2 = \frac{R_2 / j\omega C}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1} \quad \# \quad Z_1 = 1 \text{ k}\Omega$

$$H(j\omega) = \frac{V_o}{V_S} = -\frac{Z_2}{Z_1} = -\frac{-R_2 (10^{-3})}{j\omega C R_2 + 1} = -\left(\frac{1}{10^3 C}\right)\left(\frac{1}{j\omega + \frac{1}{CR_2}}\right)$$

$$H_o = -7 = -\frac{1(CR_2)}{CR_1} = -\frac{R_2}{R_1} \Rightarrow \boxed{R_2 = 7 \text{ k}\Omega}$$

$$\omega_c = \frac{1}{CR_2} = 2\pi f_c \Rightarrow \boxed{C = 2.27 \text{ nF}}$$

- 12.77 For the high-pass active filter in Fig. P12.77, choose  $C$ ,  $R_1$ , and  $R_2$  such that  $H_o = 5$  and  $f_c = 3 \text{ kHz}$ .

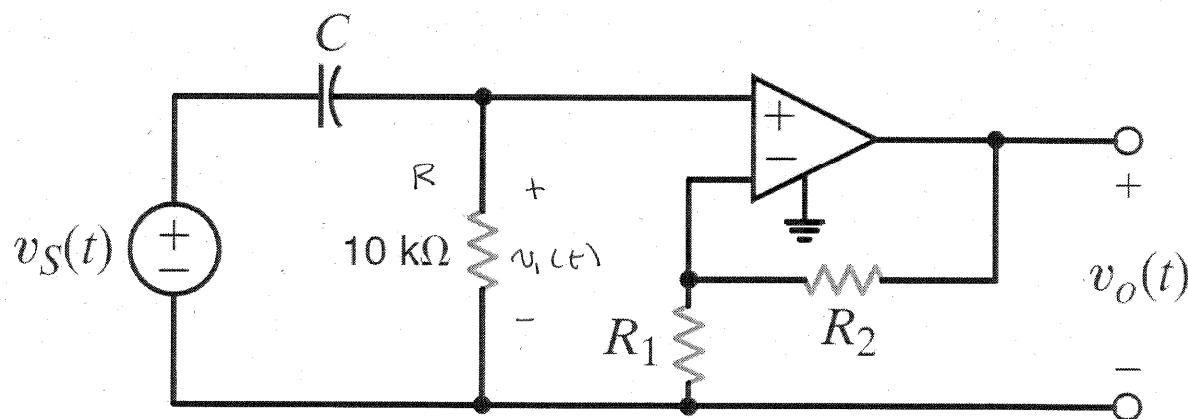


Figure P12.77

SOLUTION:

$$\frac{V_1}{V_s} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega}{j\omega + \frac{1}{RC}}$$

$$\frac{V_o}{V_1} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1}\right) \frac{j\omega}{j\omega + \frac{1}{RC}} \quad H_o = 1 + \frac{R_2}{R_1} = 5 \quad \omega_c = 2\pi f_c = \frac{1}{RC}$$

$$C = \frac{1}{2\pi f_c R} \Rightarrow C = 5.31 \text{ nF}$$

Arbitrarily select  $R_1 = 10 \text{ k}\Omega$ , yields  $R_2 = 40 \text{ k}\Omega$

- 12.78** Given the second-order low-pass filter in Fig. P12.78, design a filter that has  $H_o = 100$  and  $f_c = 5 \text{ kHz}$ . Set  $R_1 = R_3 = 1 \text{ k}\Omega$ , and let  $R_2 = R_4$  and  $C_1 = C_2$ . Use an op-amp model with  $R_i = \infty$ ,  $R_o = 0$ , and  $A = (2)10^5$ .

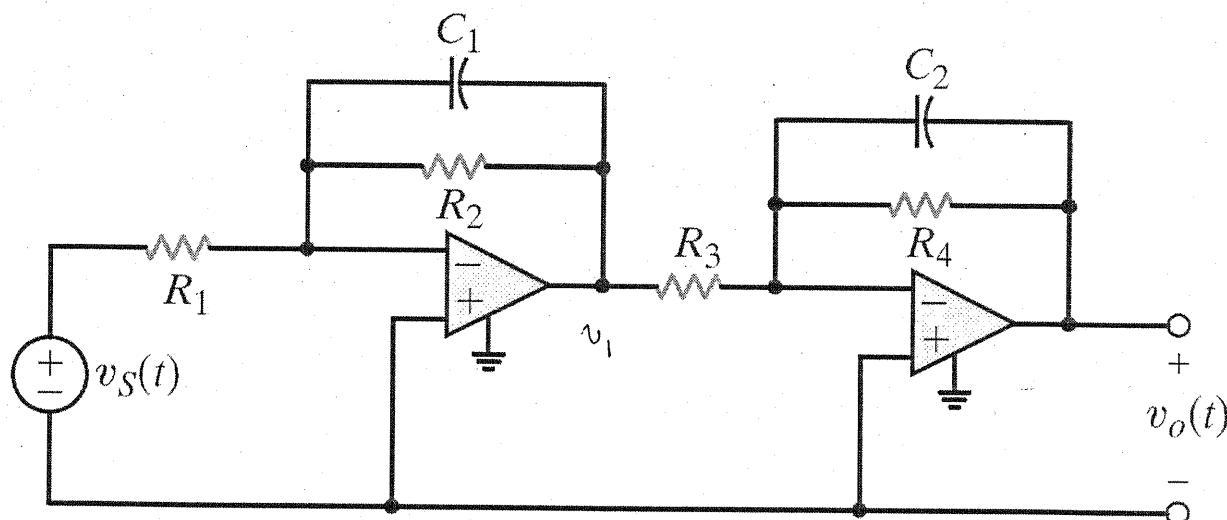


Figure P12.78

**SOLUTION:** Constraints yield

$$\frac{V_1}{V_S} = G_1(j\omega) = \frac{V_o}{V_1} = G_2(j\omega)$$

$$\text{Let } Z = \frac{R_2 / j\omega C}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1} = \frac{1/C}{j\omega + 1/R_2 C}$$

$$* G_1(j\omega) = -Z/R_1 = -\frac{1/R_1 C}{j\omega + 1/R_2 C}$$

$$G(j\omega) = G_1 G_2 = \frac{(1/R_1 C)^2}{(j\omega + 1/R_2 C)^2} \quad \left\{ \begin{array}{l} H_o = (R_2/R_1)^2 = 100 \Rightarrow R_2/R_1 = 10 \\ \omega_c = 2\pi f_c = \frac{1}{R_2 C} = \frac{1}{10^4 C} \end{array} \right.$$

$$C = 3.18 \text{nF}, \text{ yields } R_2 = 10 \text{k}\Omega \text{ and } R_4 = 10 \text{k}\Omega$$

\* For each op amp,  $R_2/R_1 = 10$  which is  $\ll A$  for op amp ( $2 \times 10^5$ ). Including  $A$  in the analysis would only affect beyond 4 digits!

- 12.79 The second-order low-pass filter shown in Fig. P12.79 has the transfer function

$$\frac{V_o}{V_i}(s) = \frac{\frac{-R_3}{R_1} \left( \frac{1}{R_2 R_3 C_1 C_2} \right)}{s^2 + \frac{s}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{R_2 R_3 C_1 C_2}}$$

Design a filter with  $H_o = -10$  and  $f_c = 5 \text{ kHz}$ , assuming that  $C_1 = C_2 = 10 \text{ nF}$  and  $R_1 = 1 \text{ k}\Omega$ .

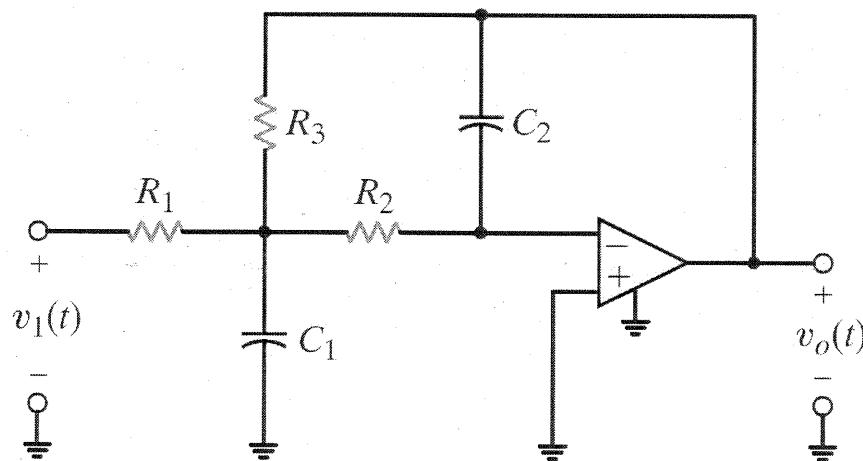


Figure P12.79

SOLUTION:

$$H_o = -\frac{R_3}{R_1} \left( \frac{1}{R_2 R_3 C_1 C_2} \right) / \frac{1}{R_2 R_3 C_1 C_2} = -\frac{R_3}{R_1} = -10 \Rightarrow R_3 = 10 \text{ k}\Omega$$

$R_2$  affects  $f_c$ . Look at characteristic equation

$$s^2 + Bs + C = 0 \quad B = \frac{1}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad C = \frac{1}{R_2 R_3 C_1 C_2}$$

Roots at

$$(s + \frac{B}{2} - \sqrt{\frac{B^2}{4} - C})(s + \frac{B}{2} + \sqrt{\frac{B^2}{4} - C}) = 0 = (s + \omega_{p1})(s + \omega_{p2})$$

where  $\omega_{p1}$  &  $\omega_{p2}$  are the poles. Since  $\omega_{p1} < \omega_{p2}$ ,

$$\omega_{p1} = 2\pi f_c = \omega_c$$

$$\frac{B}{2} - \sqrt{\frac{B^2}{4} - C} = \omega_c \Rightarrow \left( \frac{B}{2} - \omega_c \right)^2 = \frac{B^2}{4} - C$$

$$\frac{B^2}{4} - B\omega_c + \omega_c^2 = \frac{B^2}{4} - C \Rightarrow B\omega_c - C = \omega_c^2$$

Using  $R$  &  $C$  values and  $f_c = 500 \text{ Hz}$ ,  $B = 1.1 \times 10^5 + 10^8/R_2$

$$\text{and } C = 10^{12}/R_2 \text{ & } \omega_c = 1000\pi$$

$$\left(1.1 \times 10^5 + \frac{10^8}{R_2}\right) 1000\pi - \frac{10^{12}}{R_2} = 10^6\pi^2$$

$$1.1 \times 10^8\pi + \frac{10^8\pi}{R_2} - \frac{10^{12}}{R_2} = 10^6\pi^2$$

$$110\pi - \pi^2 = \frac{10^6 - 10^5\pi}{R_2} \Rightarrow R_2 = \frac{10^5(10-\pi)}{\pi(110-\pi)}$$

$R_2 = 2043 \Omega$

As on aside :  $\omega_{p1} = 500(2\pi) \text{ r/s}$

$$\omega_{p2} = 2\pi (24.8) \text{ kr/s}$$

**12.80** Given the circuit in Figure 12.57, design a second-order bandpass filter with a center frequency gain of  $-5$ ,  $\omega_0 = 50 \text{ krad/s}$ , and a  $\text{BW} = 10 \text{ krad/s}$ . Let  $C_1 = C_2 = C$  and  $R_1 = 1 \text{ k}\Omega$ . What is the  $Q$  of this filter? Sketch the Bode plot for the filter. Use the ideal op-amp model.

---

SOLUTION:

From the text,

$$\omega_0 = \left( \frac{1 + R_1/R_3}{R_1 R_2 C^2} \right)^{1/2} = 50 \text{ krad/s}$$

$$\frac{\omega_0}{Q} = \beta\omega = \frac{ZC}{R_2 C^2} = \frac{Z}{R_2 C} = \text{BW} = 10 \text{ krad/s}$$

$$\text{center freq gain} = \frac{-\frac{1}{R_1 C}}{\frac{1}{R_2 C} + \frac{1}{R_C C}} = -\frac{R_2}{Z R_1} = -5 = H_0$$

$$R_2 = 10 R_1$$

$R_2 = 10 \text{ k}\Omega$

$$C = \frac{Z}{R_2 (\text{BW})}$$

$C = 20 \text{nF}$

$$R_3 = \frac{R_1}{\omega_0^2 R_1 R_2 C^2 - 1}$$



$R_3 = 111 \text{k}\Omega$

$$Q = \omega_0 / \text{BW}$$

$Q = 5$

$$H(s) = \frac{H_0 (2\text{BW}) s}{s^2 + 2\text{BW}s + \omega_0^2} = \frac{-10^5 s}{s^2 + 2 \times 10^4 s + 2.5 \times 10^9}$$

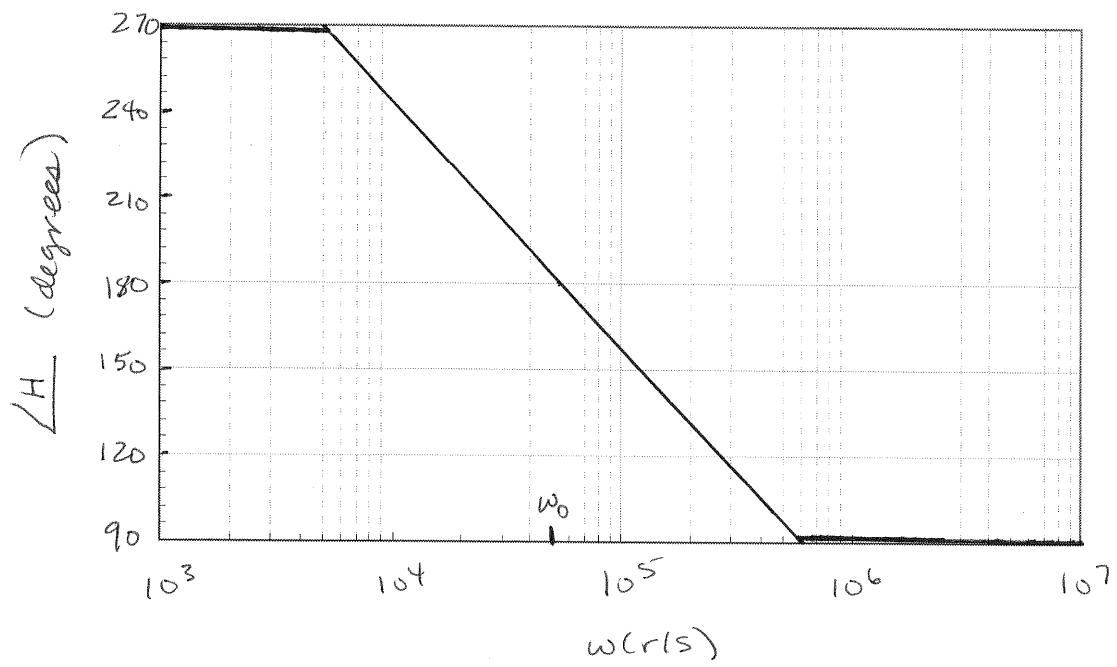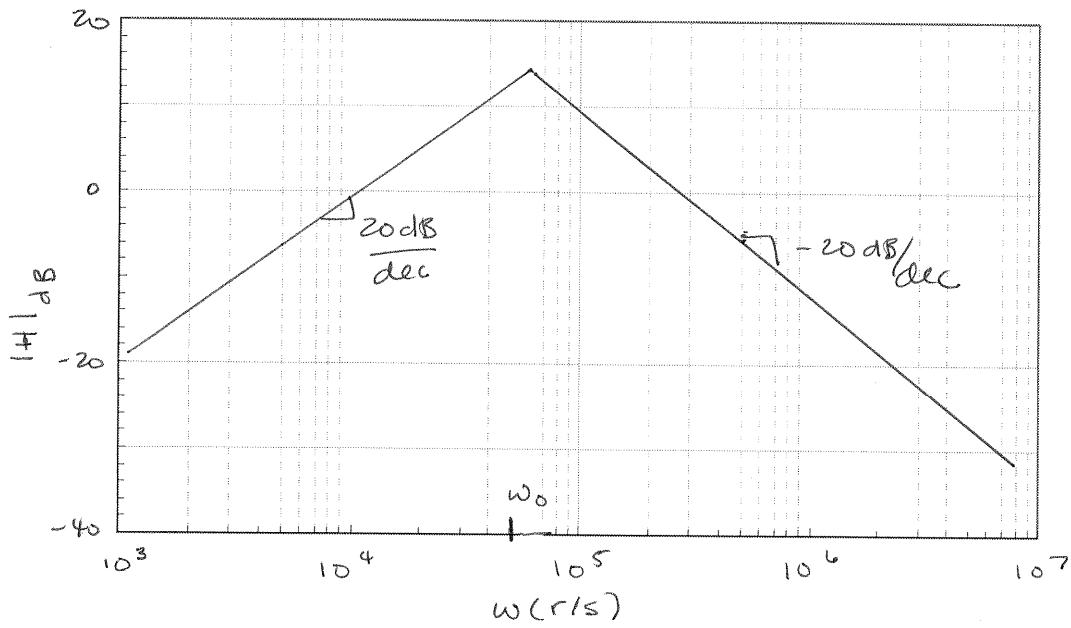poles at  $s = -10^4 \pm j4.90 \times 10^4 \text{ rad/s}$



- 12.81 Referring to Example 12.38, design a notch filter for the tape deck for use in Europe, where power utilities generate at 50 Hz.

---

SOLUTION:

From Ex. 12.38,  $\omega_z = \frac{1}{\sqrt{LC}}$

We need  $\omega_z = 2\pi(50) = 100\pi \text{ r/s}$

Arbitrarily, we select  $C = 1000 \mu\text{F}$   
yielding  $L = 10 \text{ mH}$

**12FE-1** Determine the resonant frequency of the circuit in Fig. 12PFE-1, and find the voltage  $V_o$  at resonance.

CS

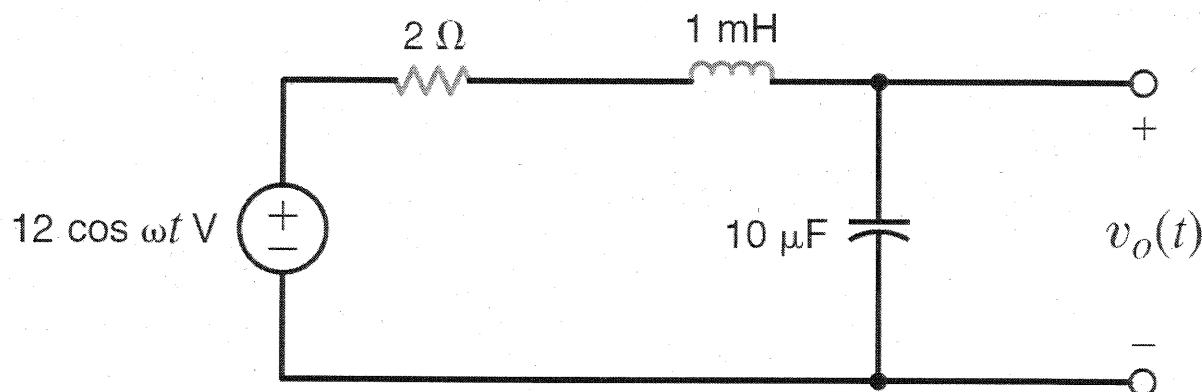


Figure 12PFE-1

**SOLUTION:**

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{\omega_0 = 10 \text{ rad/s}}$$

$$V_o(j\omega_0) = 12 \angle 0^\circ \left[ \frac{Z_C(j\omega_0)}{2} \right] = 6 \angle 0^\circ \left( \frac{1}{\omega_0 C \angle -90^\circ} \right)$$

$$\boxed{V_o(j\omega_0) = 6 \angle -90^\circ \text{ V}}$$

**12FE-2** Given the series circuit in Fig. 12PFE-2, determine the resonant frequency, and find the value of  $R$  so that the BW of the network about the resonant frequency is 200 rad/s.

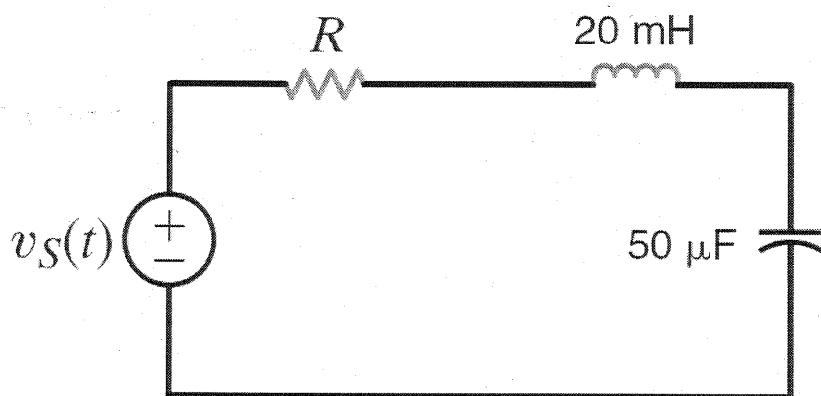


Figure 12PFE-2

---

SOLUTION:

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{\omega_0 = 1000 \text{ rad/s}}$$

$$\text{BW} = R/L = 200 \text{ rad/s} \Rightarrow \boxed{R = 4 \Omega}$$

**12FE-3** Given the low-pass filter circuit shown in Fig. 12PFE-3, find the frequency in Hz at which the output is down 3 dB from the dc, or very low frequency, output. **CS**

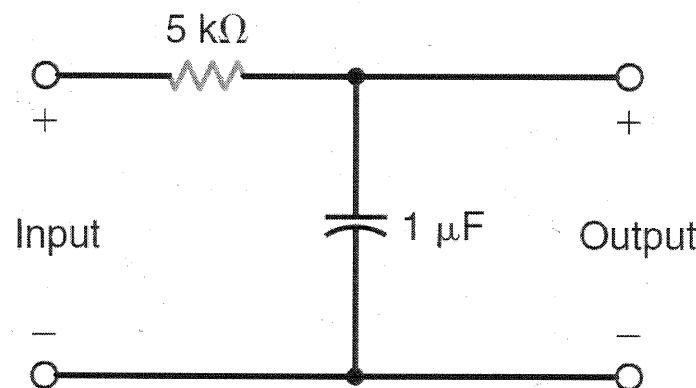


Figure 12PFE-3

SOLUTION:

$$\frac{V_o}{V_i} = \frac{Z_c}{Z_c + R} = \frac{1/j\omega C}{j\omega C + R} = \frac{1/RC}{j\omega + 1/RC} = G_v(j\omega)$$

$$\text{at dc, } G_v = 1 = 0 \text{ dB}$$

$$\text{at } 3 \text{ dB down, } \omega = \frac{1}{RC} \Rightarrow \boxed{\omega = 200 \text{ r/s}}$$

- 12FE-4** Given the band-pass filter shown in Fig. 12PFE-4, find the components  $L$  and  $R$  necessary to provide a resonant frequency of 1000 rad/s and a BW of 100 rad/s.

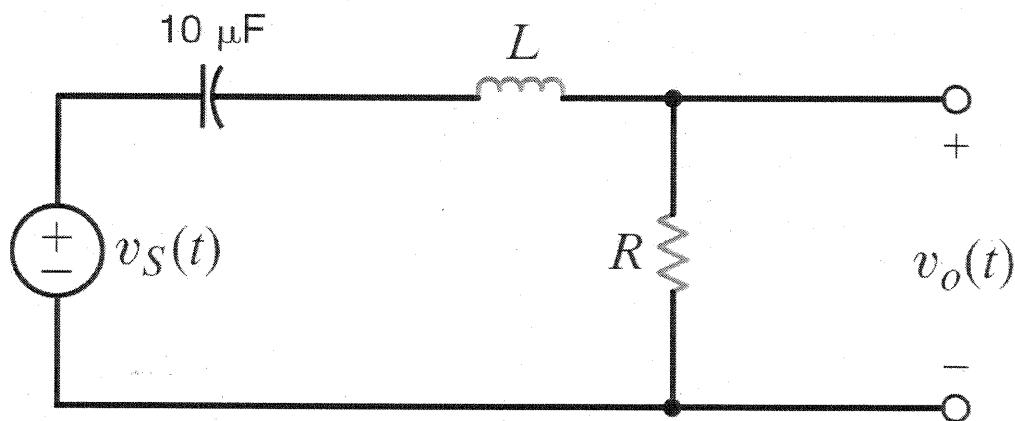


Figure 12PFE-4


---

SOLUTION:

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1000 \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow \boxed{L = 100 \text{ mH}}$$

$$\text{BW} = R/L = 100 \text{ rad/s} \Rightarrow \boxed{R = 10 \Omega}$$

- 12FE-5** Given the low-pass filter shown in Fig. 12PFE-5, find the half-power frequency and the gain of this circuit, if the source frequency is 8 Hz. **CS**

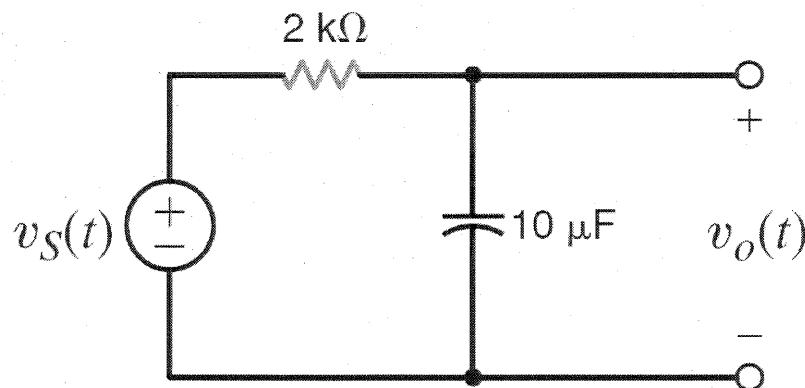

**Figure 12PFE-5**

**SOLUTION:**

$$f = 8 \text{ Hz} \quad \omega_1 = 16\pi \text{ rad/s} \quad Z_C = \frac{1}{j\omega C} = -j2.0 \text{ k}\Omega$$

$$\frac{V_o}{V_s} = G_V(j\omega) = \frac{Z_C}{Z_C + R} = \frac{-j2000}{2000 - j2000} \Rightarrow G_V(j\omega_1) = 0.707 \angle -45^\circ$$

$$\text{In general, } G_V(j\omega) = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1/RC}{j\omega + 1/RC}$$

$$\text{Half power freq} = f_c = \frac{1}{2\pi RC} \Rightarrow f_c = 8.0 \text{ Hz}$$