 


# **Chapter Fourteen:**

# **Application of the LaPlace**

# **Transform to Circuit Analysis**



14.1 Find the input impedance  $Z(s)$  of the network in Fig. P14.1.


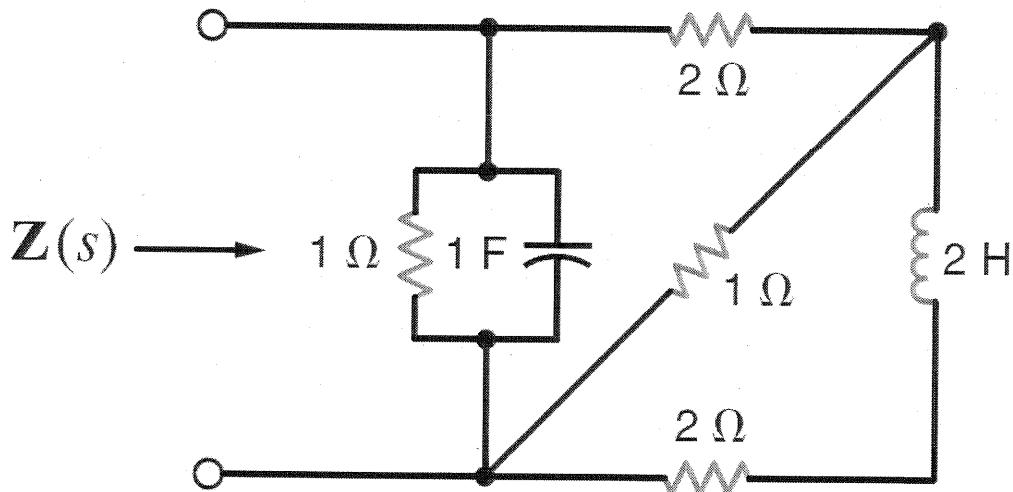


Figure P14.1

SOLUTION:

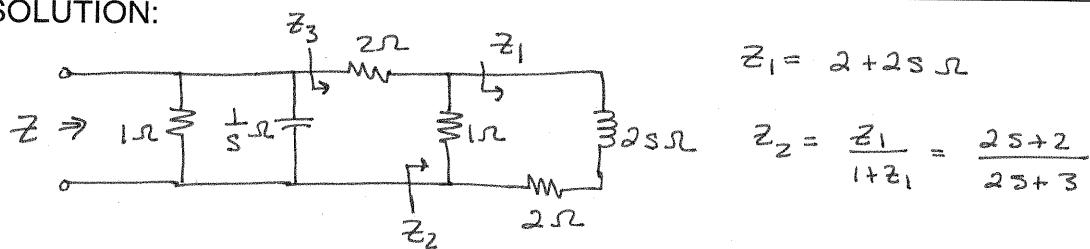

$$z_3 = Z - z_2 = 2 + \frac{2s+2}{2s+3} = \frac{4s+6+2s+2}{2s+3} = \frac{6s+8}{2s+3}$$

$$Z = \frac{1}{\frac{1}{s+2} + \frac{1}{z_3}} = s+2 + \frac{1}{z_3} = s+2 + \frac{2s+3}{6s+8} = \frac{6s^2+16s+11}{6s+8}$$

$$Z = \frac{6s+8}{6s^2+16s+11}$$

14.2 Given the network in Fig. P14.2, determine the value of the output voltage as  $t \rightarrow \infty$ .

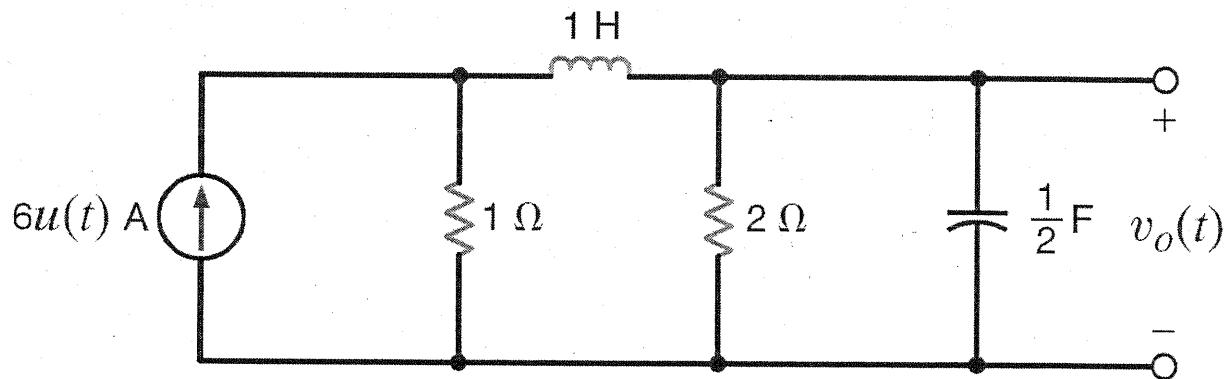


Figure P14.2

---

SOLUTION:

Since input is dc for  $t > 0$ , all voltages & currents will eventually become dc as well, thus  $V_L \rightarrow 0$  &  $i_c \rightarrow 0$  as  $t \rightarrow \infty$ .

$$V_o(\infty) = \frac{6((1)(2))}{1+2} = \frac{6(2)}{3} = 4 \quad V_o(\infty) = 4V$$

14.3 For the network shown in Fig. P14.3, determine the value of the output voltage as  $t \rightarrow \infty$ .


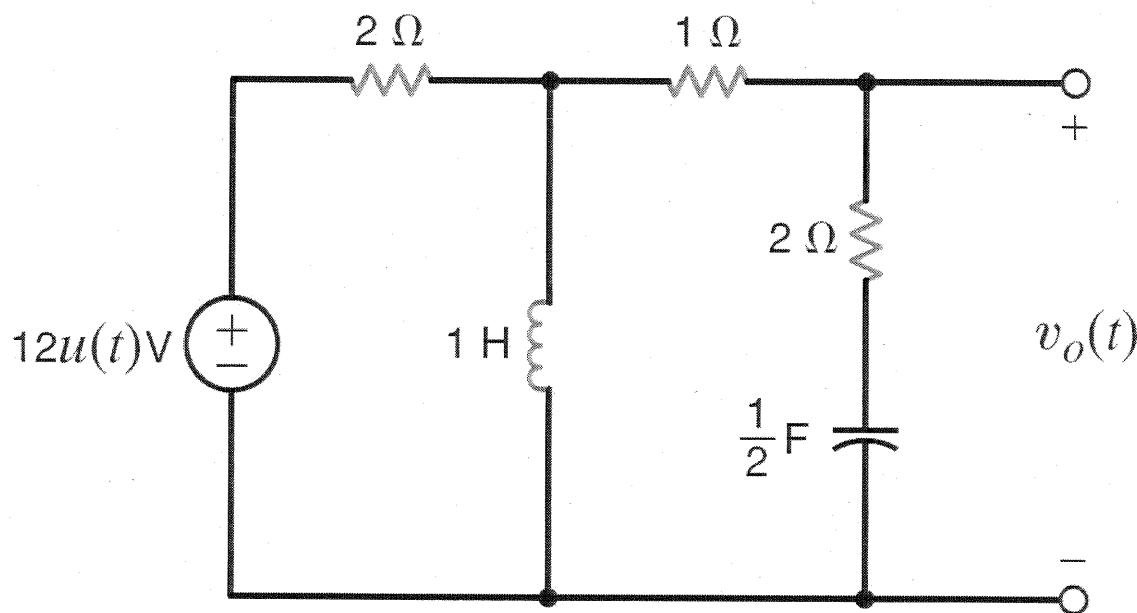


Figure P14.3

---

SOLUTION:

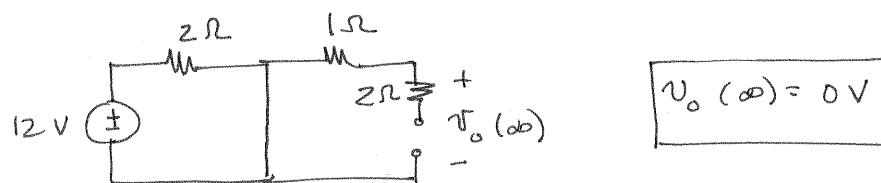Since input is dc for  $t > 0$ , all voltages & currents will eventually go to dc as well. Thus  $V_L \rightarrow 0$  &  $i_c \rightarrow 0$  as  $t \rightarrow \infty$ .



14.4 Use Laplace transforms to find  $v(t)$  for  $t > 0$  in the network shown in Fig. P14.4. Assume zero initial conditions.

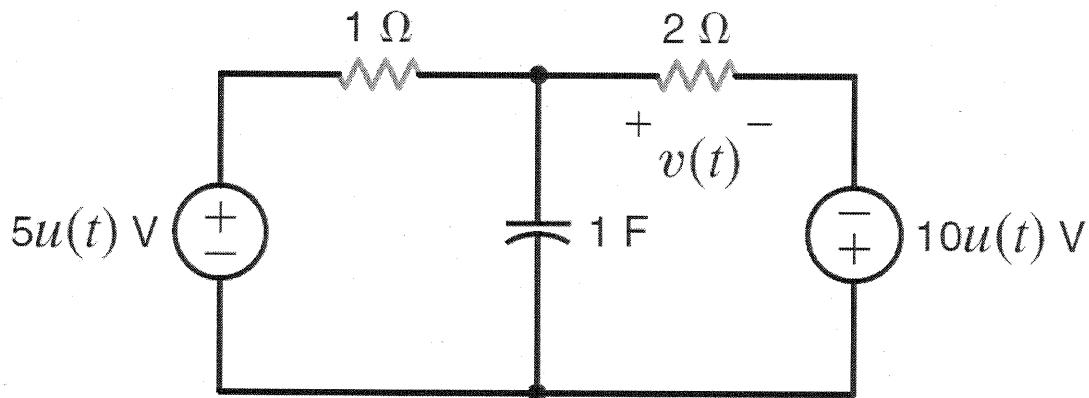


Figure P14.4

SOLUTION:

$$\frac{5}{s} = I_1(s) \left[ 1 + \frac{1}{s} \right] - I_2(s) \left( \frac{1}{s} \right)$$

$$\frac{10}{s} = -I_1(s) \left( \frac{1}{s} \right) + I_2(s) \left[ 2 + \frac{1}{s} \right]$$

$$\text{or, } \begin{cases} s = I_1(s+1) - I_2 \\ 10 = -I_1 + I_2(2s+1) \end{cases} \quad \begin{cases} I_1 = s/s \\ I_2 = s/s \end{cases}$$

$$V(s) = 2 I_2(s) = \frac{10}{s}$$

$$v(t) = 10 u(t)$$

- 14.5 Use Laplace transforms and nodal analysis to find  $i_1(t)$  for  $t > 0$  in the network shown in Fig. P14.5. Assume zero initial conditions.


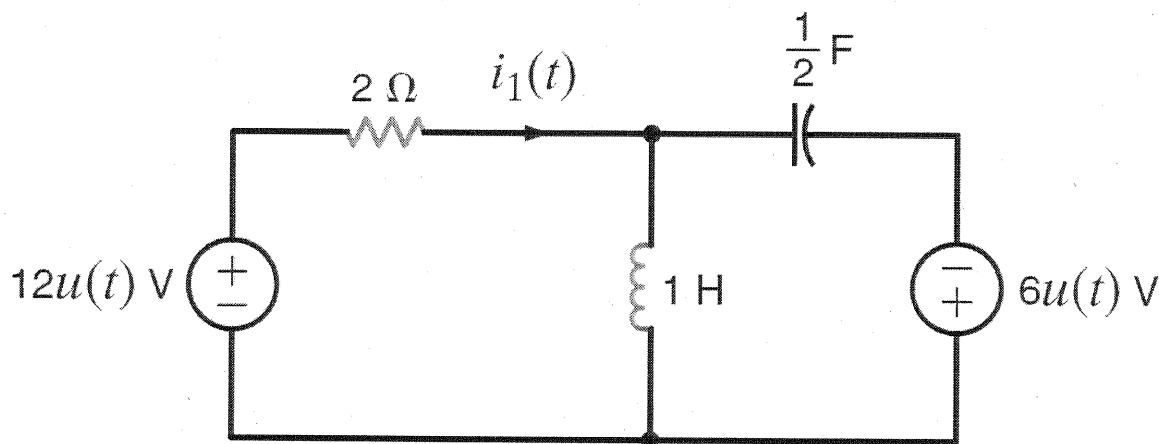


Figure P14.5

SOLUTION:

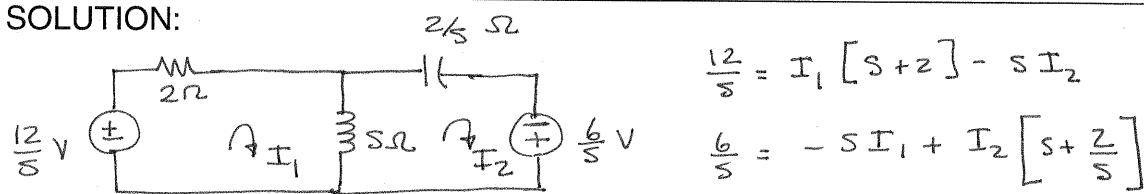

$$\frac{12}{s} = I_1 [s + z] - s I_2$$

$$\frac{6}{s} = -s I_1 + I_2 \left[ s + \frac{z}{s} \right]$$

$$\text{or, } \frac{12}{s} = I_1 [s + z] - s I_2 \quad \& \quad \frac{6}{s} = -s I_1 + I_2 \left[ \frac{s^2 + z}{s} \right]$$

$$\text{Solve for } I_1 \text{ yields } I_1(s) = \frac{3(3s^2 + 4)}{s(s^2 + s + 2)}$$

$$F_1(s) = \frac{K_1}{s} + \frac{K_2}{s + \frac{1}{2} - j\sqrt{7}/2} + \frac{K_2^*}{s + \frac{1}{2} + j\sqrt{7}/2} \quad K_1 = 6$$

$$K_2 = \frac{3(3s^2 + 4)}{s(s + \frac{1}{2} + j\sqrt{7}/2)} \Big|_{s = -\frac{1}{2} + j\sqrt{7}/2} = 3.21 \angle 62.1^\circ$$

$$i_1(t) = [6 + 6.42 e^{-t/2} \cos(\sqrt{7}t/2 + 62.1^\circ)] u(t) \text{ V}$$

- 14.6 For the network shown in Fig. P14.6, find  $v_o(t)$ ,  $t > 0$ , using node equations. **PSV**

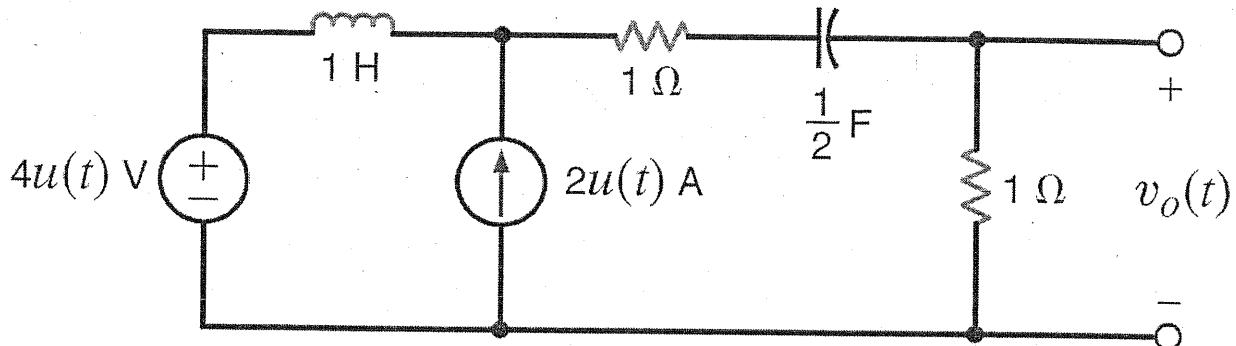


Figure P14.6

SOLUTION: at  $t = 0^-$ , no excitation. So initial conditions = 0.

$$\begin{aligned}
 &\text{Circuit diagram in the s-domain: } \\
 &\text{Voltage source: } \frac{4}{s}V, \text{ Current source: } \frac{2}{s}A, \text{ Inductor: } \frac{s}{2} \Omega, \text{ Capacitor: } \frac{1}{2s} \Omega, \text{ Load: } 1 \Omega, \text{ Output: } V_o(s) \\
 &\frac{V}{s} - \frac{4}{s} + \frac{V}{\frac{2}{s} + \frac{1}{2s}} = \frac{2}{s} \\
 &\frac{V}{s} + \frac{\frac{Vs}{2}}{\frac{2}{s} + \frac{1}{2s}} = \frac{2}{s} + \frac{4}{s^2} \\
 &V \left[ s(s+1) + \frac{s^3}{2} \right] = 2s(s+1) + 4(s+1) = 2s^2 + 6s + 4 \\
 &\frac{V}{2} \left[ s^3 + 2s^2 + 2s \right] = 2(s^2 + 3s + 2) \Rightarrow V = \frac{4(s+1)(s+2)}{s(s^2 + 2s + 2)} \\
 &V_o = V \left[ \frac{1}{s^2 + 2s + 2} \right] = V \left[ \frac{s}{2(s+1)} \right] = \frac{2(s+2)}{(s+1-j1)(s+1+j1)}
 \end{aligned}$$

$$V_o = \frac{K_1}{s+1-j1} + \frac{K_1^*}{s+1+j1} \quad K_1 = \frac{2(1+j1)}{j2} = \sqrt{2} \angle -45^\circ$$

$$v_o(t) = [\sqrt{2} e^{-t} \cos(t - 45^\circ)] u(t) \quad \checkmark$$

**14.7** For the network shown in Fig. P14.7, find  $i_o(t)$ ,  $t > 0$ .

CS


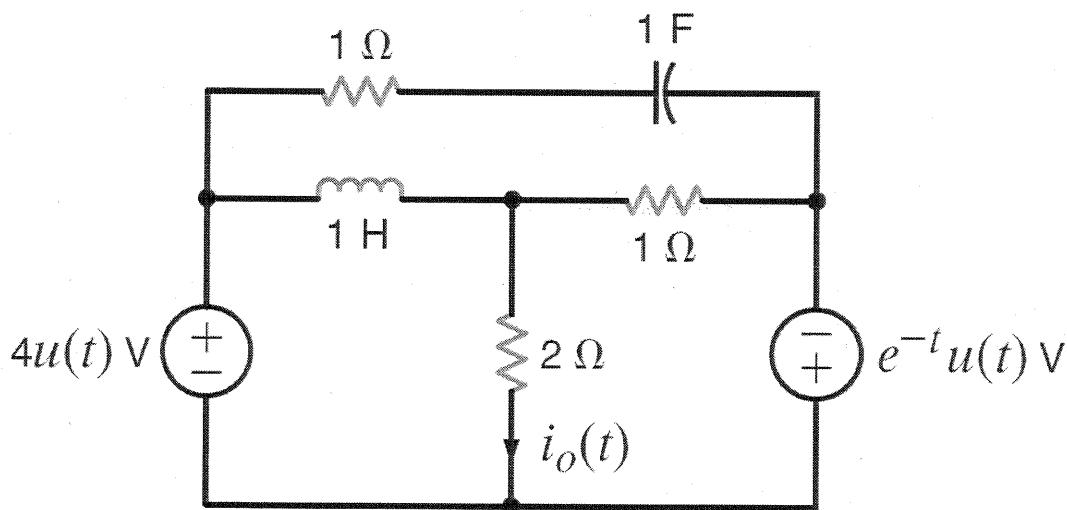


Figure P14.7

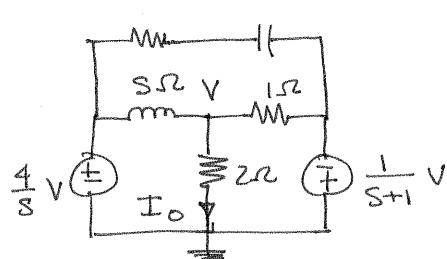**SOLUTION:**  $t=0^-$ : No excitation. So, all initial conditions = 0.



$$\frac{V - 4/s}{s} + \frac{V + \frac{1}{s+1}}{1} + \frac{V}{2} = 0$$

$$V \left( \frac{1}{s} + \frac{3}{2} \right) = \frac{4}{s^2} - \frac{1}{s+1}$$

$$V = \frac{2(-s^2 + 4s + 4)}{s(s+1)(3s+2)}$$

$$I_0 = \frac{V}{2} = \frac{\frac{1}{3}(-s^2 + 4s + 4)}{s(s+1)(s+2/3)} = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+2/3}$$

$$K_1 = 2 \quad K_2 = -1 \quad K_3 = -4/3$$

$$i_o(t) = [2 - e^{-t} - \frac{4}{3}e^{-(2/3)t}] u(t) \quad \checkmark$$

**14.8** Find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.8 using node equations.

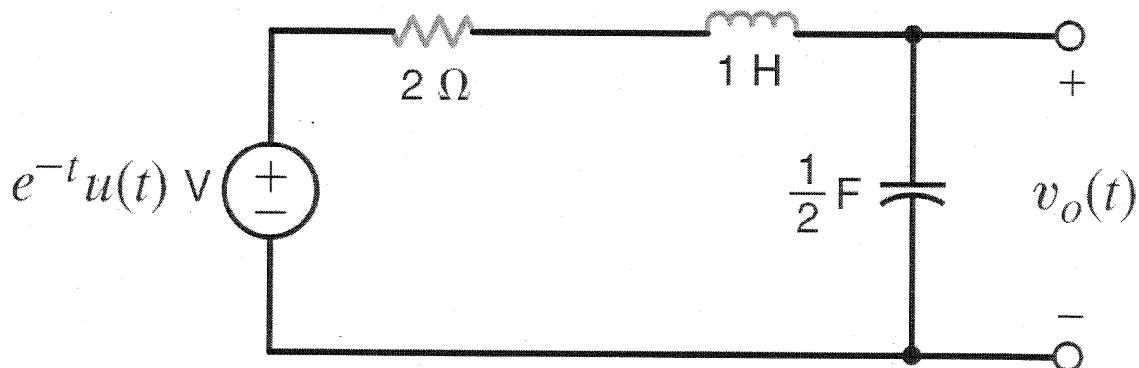


Figure P14.8

SOLUTION:  $V_c(0^-) = 0V$

$$\frac{1}{s+1} V \begin{array}{c} 2\Omega \\ \text{---} \\ \text{---} \end{array} \begin{array}{c} s\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} V_o(s) \\ + \\ - \end{array}$$

$$\frac{V_o(s)}{2/s} + \frac{V_o(s) - \frac{1}{s+1}}{s+2} = 0$$

$$\frac{s V_o}{2} + \frac{V_o}{s+2} - \frac{1}{(s+2)(s+1)} = 0$$

$$s(s+2)V_o + 2V_o = \frac{2}{s+1} = V_o [s^2 + 2s + 2]$$

$$V_o = \frac{2}{(s+1)(s^2 + 2s + 2)} = \frac{K_1}{s+1} + \frac{K_2}{s+1-j1} + \frac{K_2^*}{s+1+j1}$$

$$K_1 = 2 \quad K_2 = \frac{2}{(j1)(j2)} = -1 \quad K_2^* = -1$$

$$V_o = \frac{2}{s+1} - \frac{1}{s+1-j1} - \frac{1}{s+1+j1}$$

$$v_o(t) = [2e^{-t} - 2e^{-t} \cos(t)] u(t)$$

**14.9** Find  $v_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.9 using nodal analysis. **CS**


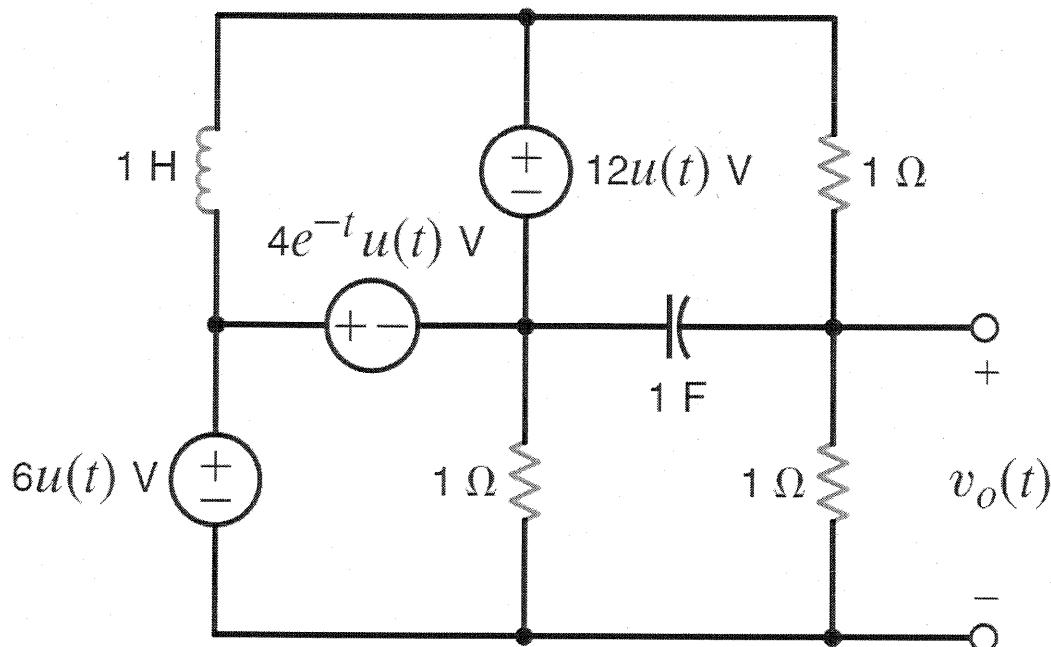


Figure P14.9

**SOLUTION:**

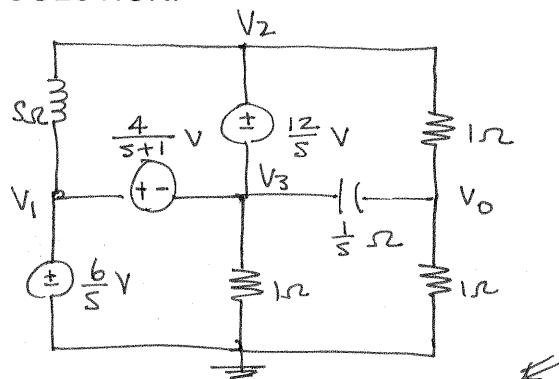

$$V_1 = \frac{6}{s} \quad V_1 - V_3 = \frac{4}{s+1} \Rightarrow V_3 = \frac{6}{s} - \frac{4}{s+1}$$

$$V_2 - V_3 = \frac{12}{s} \Rightarrow V_2 = \frac{12}{s} + V_3 = \frac{18}{s} - \frac{4}{s+1}$$

$$\frac{V_0 - V_2}{1} + s(V_0 - V_3) + \frac{V_0}{1} = 0$$

$$V_0(s+2) = V_2 + sV_3$$

$$V_0(s+2) = \frac{2(s+9)}{s} \Rightarrow V_0(s) = \frac{2(s+9)}{s(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+2}$$

$$k_1 = 9 \quad k_2 = -7$$

$$v_o(t) = [9 - 7e^{-2t}]u(t)$$

- 14.10 Use nodal analysis to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.10. **PSV**

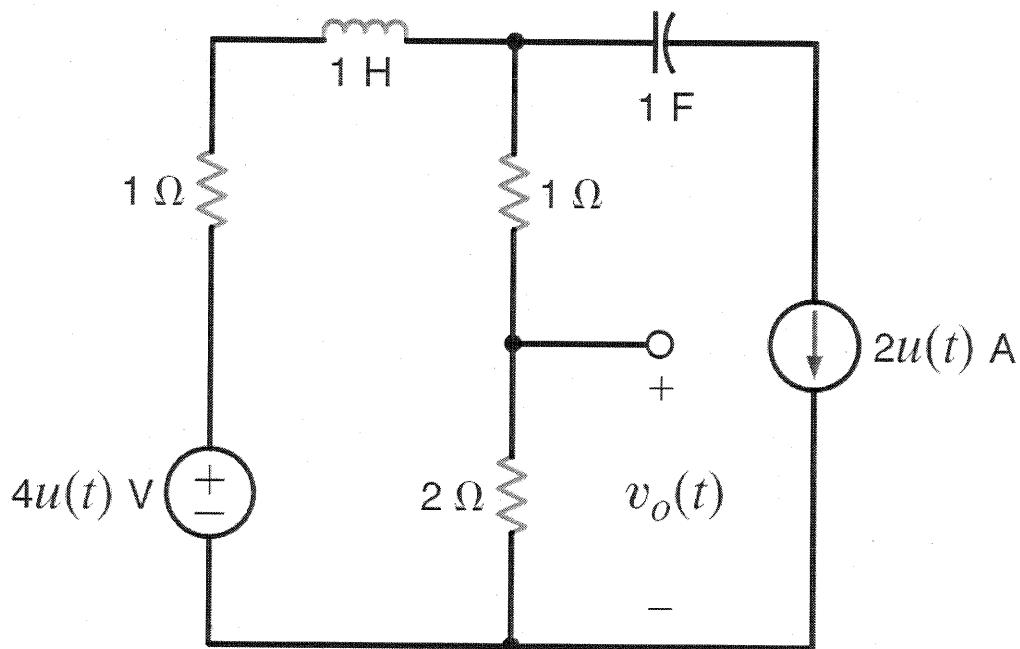


Figure P14.10

**SOLUTION:**

$$\begin{array}{c}
 \text{Circuit diagram: } \frac{4}{s}V \text{ source, } 1\Omega \text{ resistor, } 1H \text{ inductor, } 2\Omega \text{ resistor, } 1F \text{ capacitor, } 2u(t) \text{ current source.} \\
 \text{Nodal analysis: Node 1 (top), Node 2 (bottom).} \\
 \frac{V}{s+1} + \frac{V}{3} + \frac{2}{s} = 0 \\
 V \left[ \frac{1}{s+1} + \frac{1}{3} \right] = \frac{4}{s(s+4)} - \frac{2}{s}
 \end{array}$$

$$V \left[ \frac{3+s+1}{3(s+1)} \right] = -\frac{2s+2}{s(s+1)} \Rightarrow V(s) = \frac{6(-s+1)}{s(s+4)} \quad v_o = \frac{2}{3}V$$

$$v_o(s) = \frac{4(-s+1)}{s(s+4)} = \frac{1}{s} - \frac{5}{s+4}$$

$$v_o(t) = [1 - 5e^{-4t}]u(t)$$

- 14.11 For the network shown in Fig. P14.11, find  $v_o(t)$ ,  $t > 0$ , using loop equations.

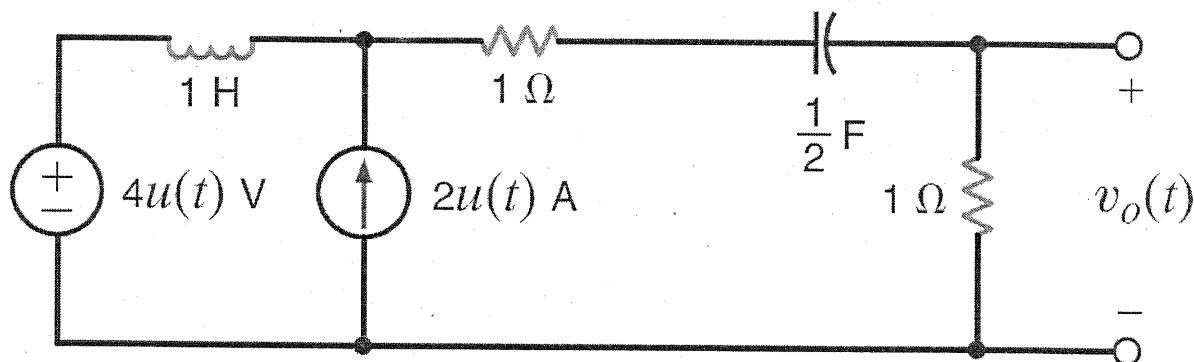


Figure P14.11

SOLUTION:

$$\begin{aligned}
 &\text{Circuit diagram in the s-domain:} \\
 &\text{Left side: } \frac{4}{s} \text{ V, } s\Omega, \text{ current } I_1 \text{ (clockwise)} \\
 &\text{Middle: } 1\Omega, \text{ current } I_2 \text{ (right)} \\
 &\text{Top: } \frac{2}{s}\Omega, \text{ current } I_2 \text{ (right)} \\
 &\text{Bottom: } 1\Omega, \text{ current } I_2 - I_1 \text{ (right)} \\
 &\text{Output: } V_o(s) \text{ (positive terminal up)}
 \end{aligned}$$

$$\begin{aligned}
 \frac{4}{s} &= sI_1 + \left(z + \frac{2}{s}\right) I_2 \\
 \text{or, } 4 &= s^2 I_1 + (zs + z) I_2 \\
 \text{and, } I_2 - I_1 &= \frac{2}{s} \Rightarrow I_1 = I_2 - \frac{2}{s}
 \end{aligned}$$

$$4 = s^2 I_2 - 2s + (zs + z) I_2 = I_2 (s^2 + zs + z) - zs$$

$$I_2 = \frac{2s + 4}{s^2 + zs + z} \quad V_o = (1) I_2 = \frac{z(s+z)}{(s+1-j)(s+1+j)} = \frac{K_1}{s+1-j} + \frac{K_1^*}{s+1+j}$$

$$K_1 = \frac{2(-1+j1+2)}{j^2} = \sqrt{2} \angle -45^\circ$$

$$V_o(t) = [2\sqrt{2} e^{-t} \cos(t - 45^\circ)] u(t) \text{ V}$$

- 14.12 For the network shown in Fig. P14.12, find  $v_o(t)$ ,  $t > 0$ , using mesh equations.

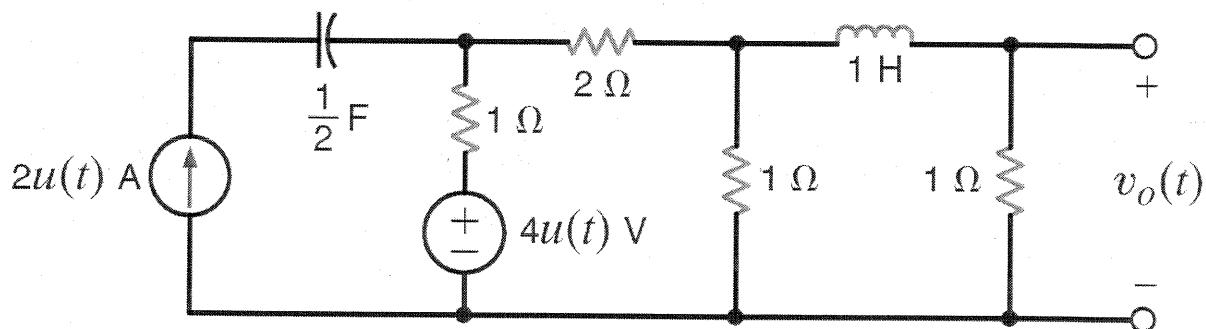


Figure P14.12

SOLUTION:

Mesh currents  $I_1, I_2, I_3$  are defined in the circuit diagram. The circuit has three meshes. Mesh 1 (leftmost) has a current  $\frac{2}{s} A$  entering the top node. Mesh 2 (middle) has a dependent voltage source  $\frac{4}{s} V$  and a current  $I_2$ . Mesh 3 (rightmost) has a voltage  $V_o(s)$  and a current  $I_3$ .

Equations from mesh analysis:

$$\frac{2}{s} = -\frac{2}{s} + 4I_2 - I_3 \Rightarrow \frac{6}{s} = 4I_2 - I_3$$

$$0 = -I_2 + I_3(s+2)$$

$$\frac{4}{s} = -\frac{2}{s} + I_1(4) - I_3 \Rightarrow \frac{6}{s} = -I_1 + 4I_3$$

$$0 = -I_1 + I_3(s+2)$$

$$I_3(s)[4(s+2)-1] = 6/s$$

$$I_3(s) = \frac{6}{s(4s+7)} \quad V_o = (1) I_3 = \frac{3/2}{s(s+7/4)}$$

$$V_o(s) = \frac{k_1}{s} + \frac{k_2}{s+7/4} \quad k_1 = \left(\frac{3}{2}\right)\left(\frac{4}{7}\right) = \frac{6}{7} \quad k_2 = \frac{3}{2}\left(-\frac{4}{7}\right) = -\frac{6}{7}$$

$$V_o(s) = \frac{6}{7} \left[ \frac{1}{s} - \frac{1}{s+7/4} \right] \quad \boxed{v_o(t) = \left[ \frac{6}{7} (1 - e^{-1.75t}) \right] u(t)}$$

- 14.13** Use mesh equations to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.13. **CS**


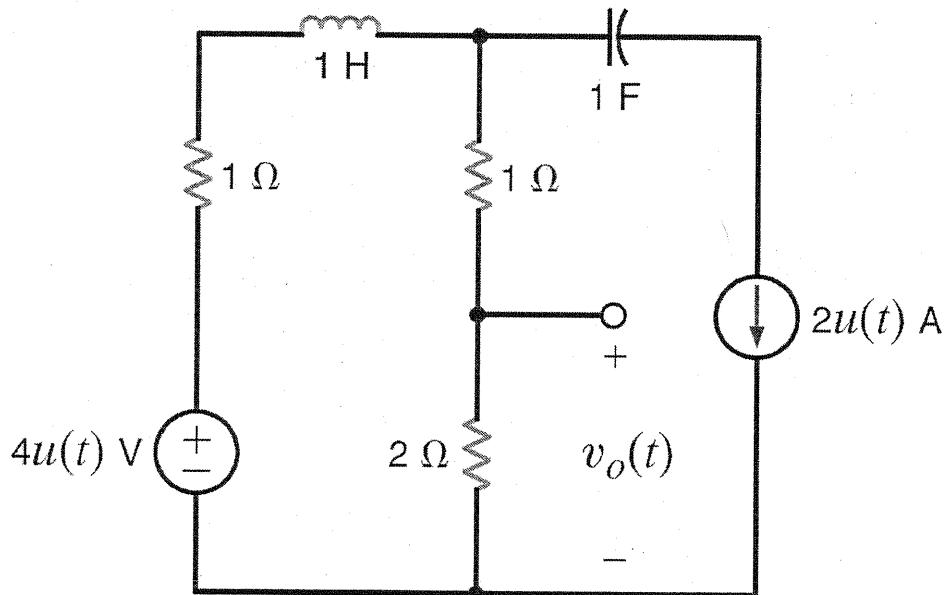


Figure P14.13

**SOLUTION:**

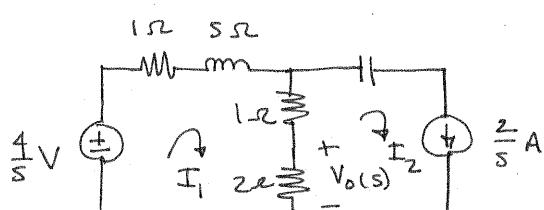

$$\frac{4}{s} = I_1 (s+4) - 3I_2 \quad I_2 = 2/s$$

$$\frac{4}{s} = I_1 (s+4) - \frac{6}{s}$$

$$\frac{10}{s} = I_1 (s+4)$$

↔

$$I_1 = \frac{10}{s(s+4)}$$

$$V_o = 2(I_1 - I_2) = 2\left[\frac{10}{s(s+4)} - \frac{2}{s}\right] = \frac{4(-s+1)}{s(s+4)} = \frac{1}{s} - \frac{s}{s+4}$$

$$v_o(t) = [1 - 5e^{-4t}]u(t) \text{ V}$$

- 14.14 Use loop equations to find  $i_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.14.


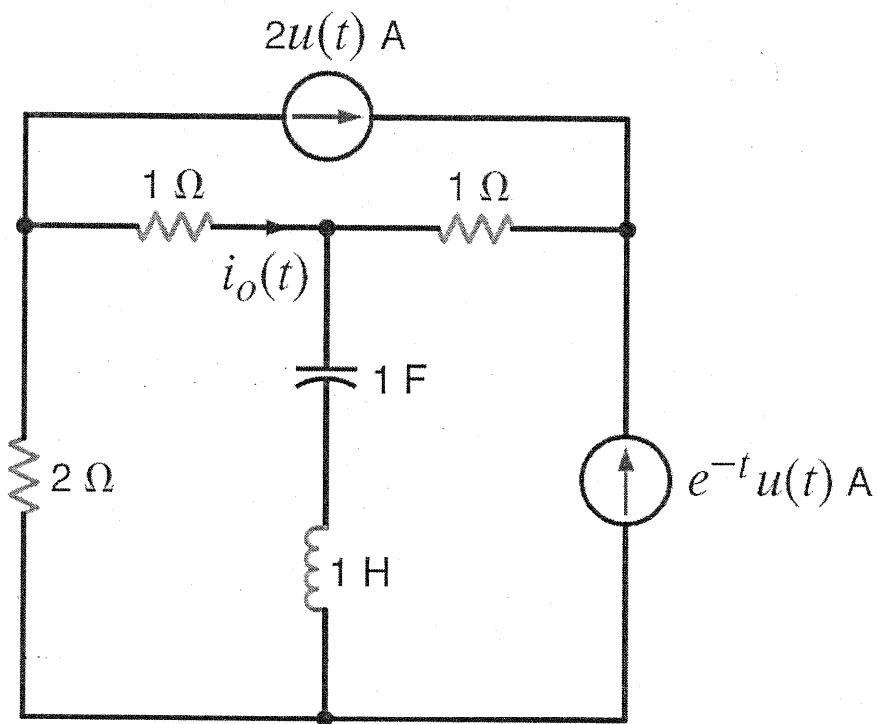


Figure P14.14

SOLUTION:

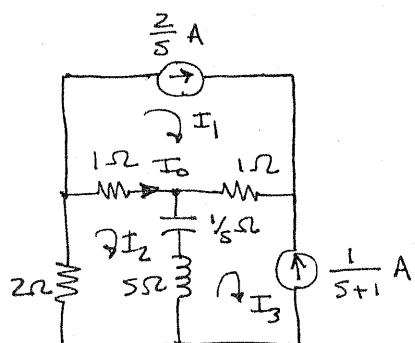

$$I_1 = \frac{2}{s} A \quad \# \quad I_3 = -\frac{1}{s+1} A$$

$$I_2 (s + 3 + 1/s) - I_1 (1) - I_3 (s + \frac{1}{s}) = 0$$

$$\text{or, } I_2 (s^2 + 3s + 1) = sI_1 + (s^2 + 1)I_3$$

$$I_2 (s^2 + 3s + 1) = 2 - \frac{s^2 + 1}{s+1} = \frac{-s^2 + 2s + 1}{s+1}$$

$$I_2 = \frac{-s^2 + 2s + 1}{(s^2 + 3s + 1)(s+1)}$$

$$I_0 = I_2 - I_1 = -\frac{s^2 + 2s + 1}{s^2 + 3s + 1} - \frac{2}{s} = -\frac{(3s^3 + 6s^2 + 7s + 2)}{s(s+1)(s^2 + 3s + 1)}$$

$$I_0(s) = \frac{-(3s^3 + 6s^2 + 7s + 2)}{s(s+1)(s+0.382)(s+2.62)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+0.382} + \frac{k_4}{s+2.62}$$

$$K_1 = \frac{-2}{(1)(1)} = -2$$

$$K_2 = \frac{(-3+6-7+2)}{(-1)(1-3+1)} = 2$$

$$K_3 = \frac{-(3s^3 + 6s^2 + 7s + 2)}{s(s+1)(s+2.62)} \Big|_{s=-0.382} = 0.065$$

$$K_4 = \frac{-(3s^2 + 6s^2 + 7s + 2)}{s(s+1)(s+2.62)} \Big|_{s=2.62} = -3.065$$

$$i_o(t) = \left[ 2 + 2e^{-t} + 0.065e^{-0.382t} - 3.065e^{-2.62t} \right] u(t) \quad \checkmark$$

- 14.15 Use loop analysis to find  $v_o(t)$  for  $t > 0$  in the network in Fig. P14.15.

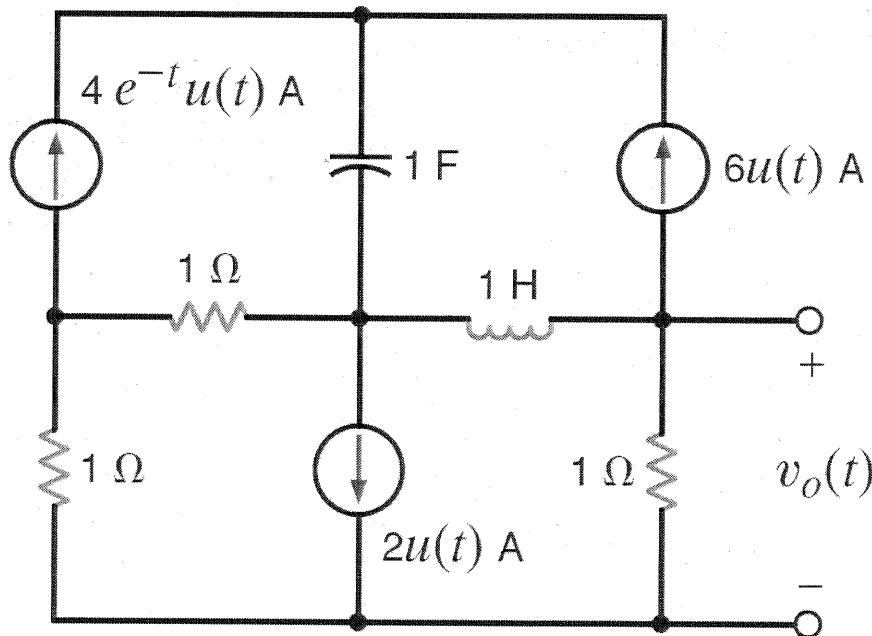


Figure P14.15

SOLUTION:

$$\begin{aligned}
 I_1 &= \frac{4}{s+1} & I_2 &= -\frac{6}{s} & I_3 - I_4 &= \frac{2}{s} \\
 I_3(s) - I_1 + I_4(s+1) - sI_2 &= 0 & V_o &= (1) I_4 & I_3 &= \frac{2}{s} + I_4 \\
 Z \left[ \frac{2}{s} + I_4 \right] - \frac{4}{s+1} + I_4(s+1) + 6 &= 0 \Rightarrow I_4(s+3) = \frac{4}{s+1} - \frac{4}{s} - 6
 \end{aligned}$$

$$I_4(s+3) = \frac{4s^2 - 4s - 4 - 6s^2 - 6s}{s(s+1)} = -\frac{(6s^2 + 6s + 4)}{s(s+1)}$$

$$V_o = \frac{-(6s^2 + 6s + 4)}{s(s+1)(s+3)} = \frac{-4/3}{s} + \frac{2}{s+1} - \frac{20/3}{s+3}$$

$$v_o(t) = [2e^{-t} - \frac{4}{3} - \frac{20}{3}e^{-3t}]u(t)$$

- 14.16 Use mesh analysis to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.16. [CS]

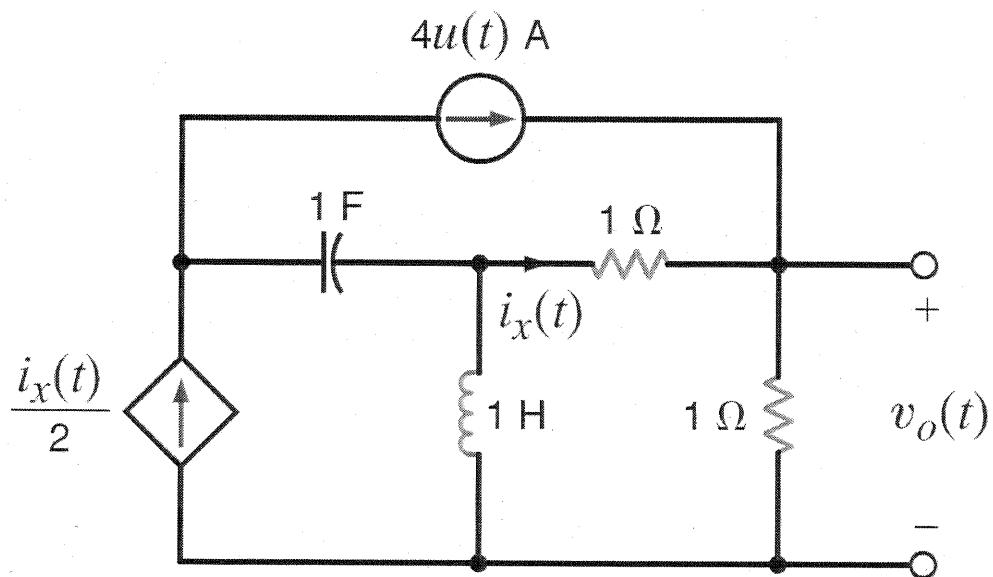


Figure P14.16

SOLUTION:

Mesh currents are defined as follows:

- Top mesh:  $I_1 = \frac{I_x}{2} = \frac{I_1 - I_3}{2} \Rightarrow I_1 = -I_3$
- Middle mesh:  $I_2 = \frac{4}{s}$
- Bottom mesh:  $I_3(s+2) - sI_1 - I_2 = 0$
- Output voltage:  $V_o = (1)I_3$

Equations for mesh currents:

$$I_3(s+2) + sI_3 = \frac{4}{s} \Rightarrow I_3 = \frac{4}{s(2s+2)} = \frac{2}{s(s+1)}$$

$$V_o = \frac{2}{s(s+1)} = \frac{2}{s} - \frac{2}{s+1}$$

$$\boxed{v_o(t) = [2(1 - e^{-t})]u(t)}$$

- 14.17 Use superposition to find  $v_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.17.


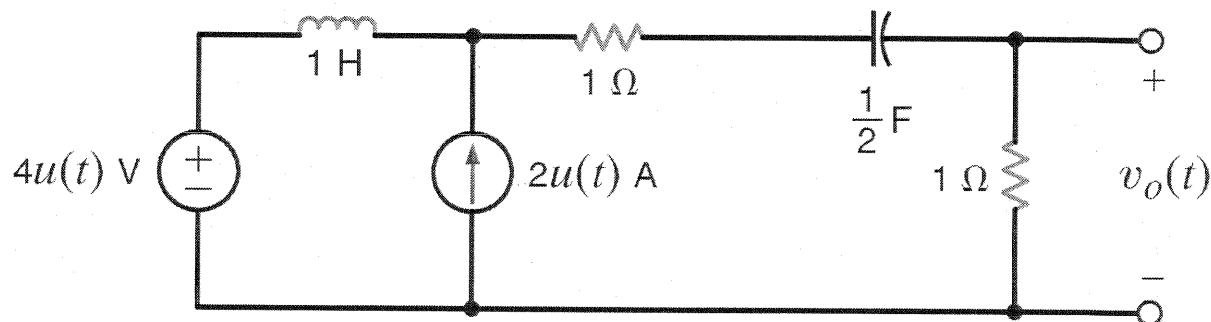


Figure P14.17

SOLUTION:

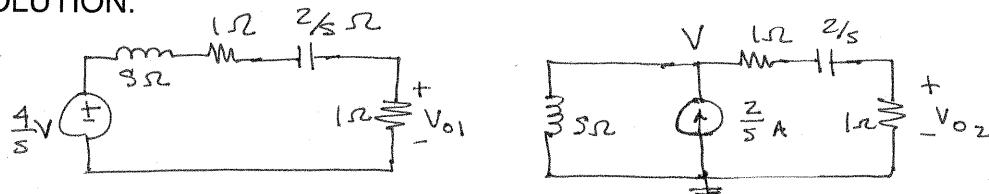

$$V_{o1} = \frac{4}{s} \left[ \frac{1}{s+1 + \frac{2}{s}} \right] \quad V + \frac{V}{2+s} = \frac{2}{s} \Rightarrow V \left[ 1 + \frac{s^2}{2(s+1)} \right] = 2$$

$$V_{o1} = \frac{4}{s^2 + 2s + 2}$$

$$V = \frac{4(s+1)}{s^2 + 2s + 2} \quad \frac{V_{o2}}{V} = \frac{1}{2 + \frac{2}{s}} = \frac{s}{2(s+1)}$$


$$V_{o2} = \frac{2s}{s^2 + 2s + 2}$$

$$V_o = V_{o1} + V_{o2} = \frac{2(s+2)}{s^2 + 2s + 2} = \frac{K_1}{s+1+j} + \frac{K_1}{s+1-j} \quad K_1 = \sqrt{2} \angle -45^\circ$$

$$v_o(t) = [2\sqrt{2} e^{-t} \cos(t - 45^\circ)] u(t)$$

14.18 Use source transformation to solve Problem 14.17.

SOLUTION:

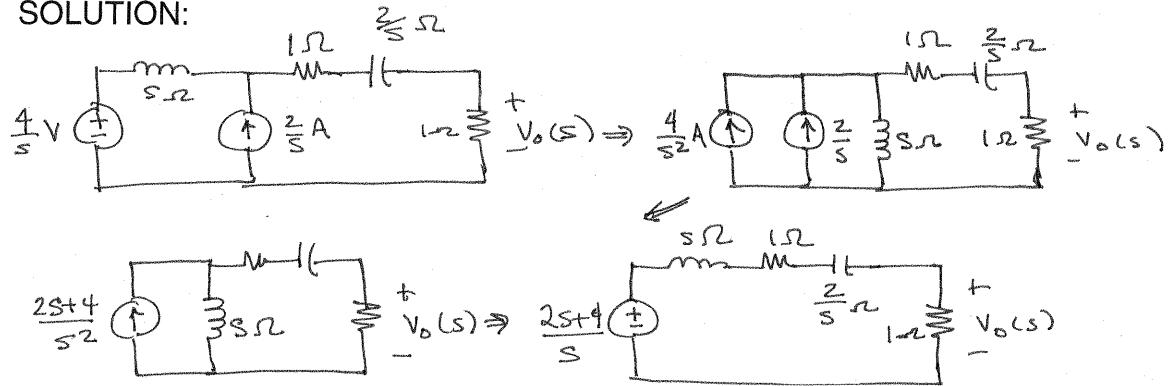

$$V_o(s) = \frac{2s+4}{s} \left[ \frac{1}{s + 1 + \frac{2}{s} + 1} \right] = \frac{2s+4}{s} \left( \frac{s}{s^2 + 2s + 2} \right) = \frac{2(s+2)}{s^2 + 2s + 2}$$


$$V_o = \frac{K_1}{s+1-j1} + \frac{K_1^*}{s+1+j1} \quad K_1 = \sqrt{2} / -45^\circ$$

$$V_o(t) = [2\sqrt{2} e^{-t} \cos(t - 45^\circ)] u(t) \text{ V}$$

**14.19** Use Thévenin's theorem to solve Problem 14.17.

CS

**SOLUTION:**

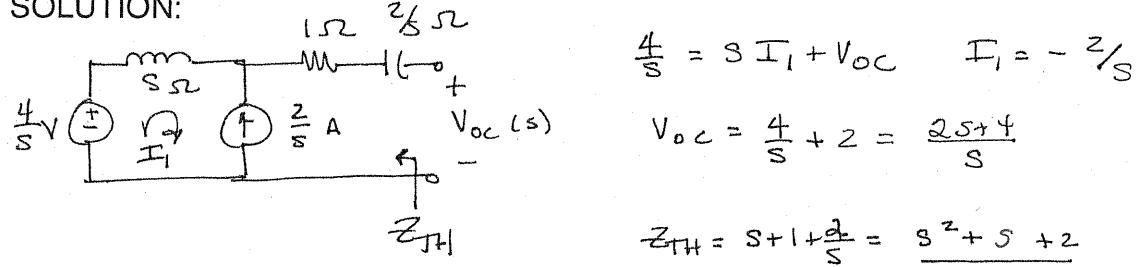


$$V_o = V_{oc} \left[ \frac{1}{1 + Z_{TH}} \right] = \frac{2(s+2)}{s^2 + 2s + 2}$$

$$V_o = \frac{k_1}{s + 1 - j_1} + \frac{k_1^*}{s + 1 + j_1} \quad k_1 = \sqrt{2} \angle -45^\circ$$

$$V_o(t) = [2\sqrt{2} e^{-t} \cos(t - 45^\circ)] u(t) \quad V$$

14.20 Use Thévenin's theorem to solve Problem 14.13.

SOLUTION:

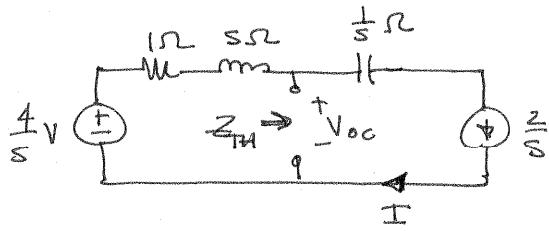


$$I = \frac{2}{s}$$

$$\frac{4}{s} = (1)I + sI + V_{oc}$$

$$V_{oc} = \frac{4}{s} - \frac{2}{s} - 2 = \frac{2}{s} - 2 = \frac{(-s+1)2}{s}$$

$$Z_{TH} = s + 1 \text{ ohm}$$

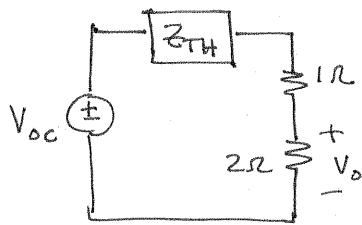

$$V_o = \frac{V_{oc}(s)}{s + 1 + Z_{TH}} = \frac{4(-s+1)}{s[3+s+1]} = \frac{4(-s+1)}{s(s+4)}$$

$$\leftarrow V_o = \frac{1}{s} - \frac{5}{s+4}$$

$$v_o(t) = [1 - 5e^{-4t}]u(t) \text{ V}$$

- 14.21 Use Thévenin's theorem to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.21. CS


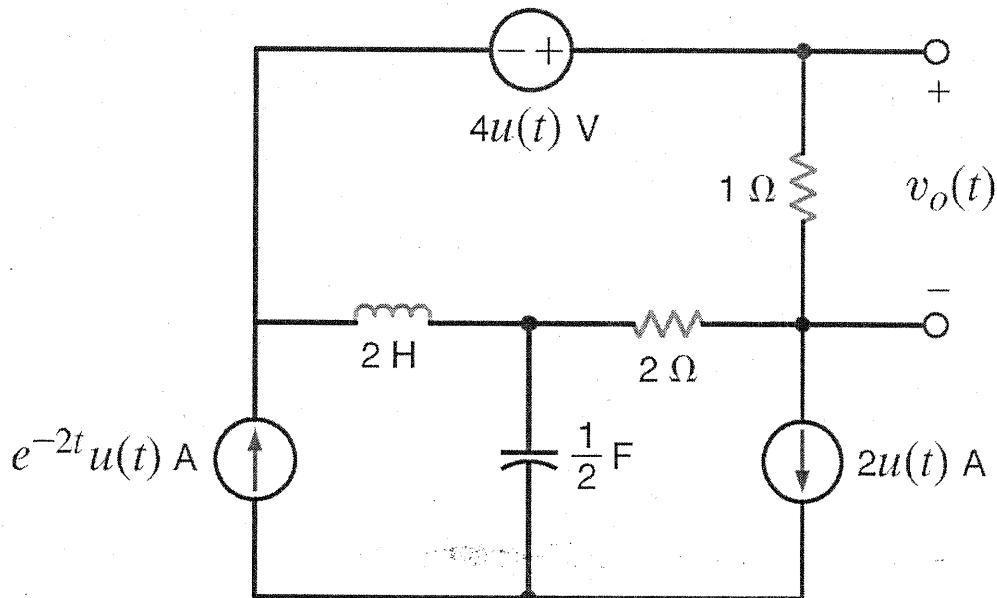


Figure P14.21

SOLUTION:

Find  $\frac{V_{oc}}{Z_{Th}}$ :
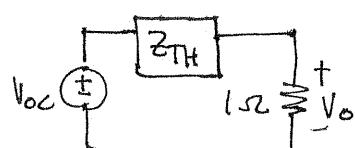
$$\begin{aligned} I_1 &= \frac{1}{s+2} & I_2 &= \frac{1}{s} \\ \frac{4}{s} &= V_{oc} - 2I_2 - 2sI_1 \\ V_{oc} &= \frac{4}{s} + \frac{4}{s} + \frac{2s}{s+2} = \frac{8}{s} + \frac{2s}{s+2} \\ V_{oc} &= \frac{2s^2 + 8s + 16}{s(s+2)} \\ Z_{Th} &= 2s + 2 \end{aligned}$$



$$V_o = \frac{V_{oc}(1)}{1 + Z_{Th}} = \frac{2(s^2 + 4s + 8)}{s(s+2)(s+1.5)^2} = \frac{s^2 + 4s + 8}{s(s+1.5)(s+2)} = \frac{8/3}{s} - \frac{17/3}{s+1.5} + \frac{4}{s+2}$$

$$V_o(t) = \left[ \frac{8}{3} - \frac{17}{3} e^{-1.5t} + 4e^{-2t} \right] u(t) \text{ V}$$

- 14.22** Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.22 using Thévenin's theorem.


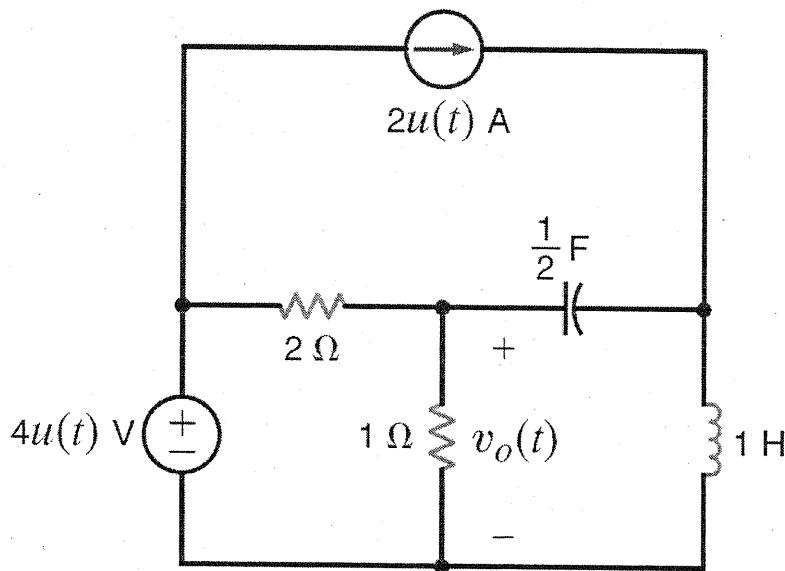


Figure P14.22

**SOLUTION:**

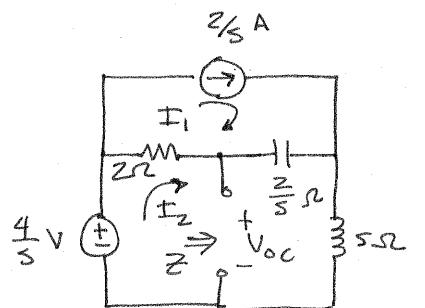

$$Z = Z \left( s + \frac{2}{s} \right) = \frac{2s^2 + 4}{s^2 + 2s + 2}$$


$$I_1 = \frac{2}{s} + \frac{4}{s} = I_2 \left[ 2 + \frac{2}{s} + s \right] - I_1 \left[ 2 + \frac{2}{s} \right]$$

$$\text{or}, \quad \frac{4}{s} = I_2 \left( \frac{s^2 + 2s + 2}{s} \right) - \frac{2}{s} \left( \frac{2s + 2}{s} \right)$$

$$I_2 = \frac{8s + 4}{s(s^2 + 2s + 2)}$$

$$v_{oc} = \frac{4}{s} - Z(I_2 - I_1) = \frac{8s^2 + 8}{s(s^2 + 2s + 2)}$$
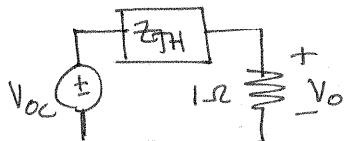
$$V_o = \frac{v_{oc}(1)}{1 + Z_{TH}} = \frac{(8/3)(s^2 + 1)}{s(s^2 + \frac{2}{3}s + 2)}$$



$$V_o = \frac{4/3}{s} + \frac{K_1}{s + \frac{1}{3} - j\sqrt{\frac{17}{3}}} + \frac{K_1 *}{s + \frac{1}{3} + j\sqrt{\frac{17}{3}}}$$

$$K_1 = 0.825 / 36.0^\circ$$

$$V_o(t) = \left[ \frac{4}{3} + 1.65 e^{-t/3} \cos \left( \frac{\sqrt{17}}{3} t + 36^\circ \right) \right] u(t) \text{ V}$$

- 14.23 Use Thévenin's theorem to determine  $i_o(t)$ ,  $t > 0$ , in the circuit shown in Fig. P14.23. **PSV**


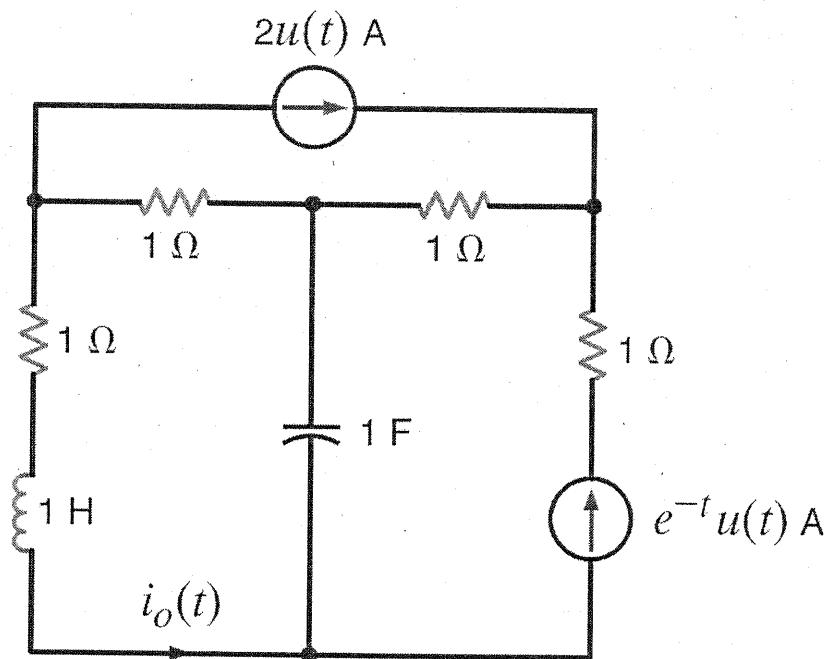


Figure P14.23

SOLUTION:

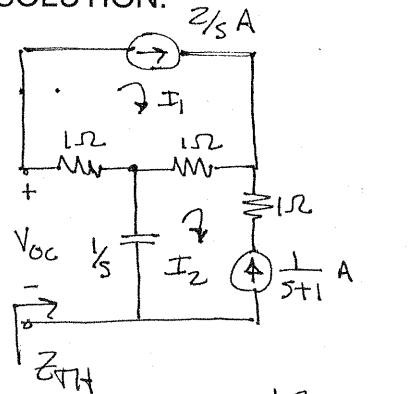


$$I_1 = \frac{2}{s} \quad I_2 = -\frac{1}{s+1}$$

$$V_{OC} = (1)(-\mathcal{I}_1) - \frac{1}{s} \mathcal{I}_2 = -\frac{2}{s} + \frac{1}{s(s+1)} = -\frac{(2s+1)}{s(s+1)}$$

$$Z = 1 + 1/s = (s+1)/s$$


$$I_0 = -\frac{V_{OC}}{Z + 1/s} = \frac{(2s+1)}{(s+1)^2}$$
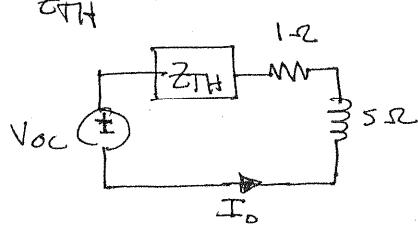
$$I_0 = \frac{k_1}{(s+1)^3} + \frac{k_2}{(s+1)^2} + \frac{k_3}{s+1} = \frac{-1}{(s+1)^3} + \frac{2}{(s+1)^2}$$




$$i_o(t) = [2te^{-t} - \frac{1}{2}t^2e^{-t}]u(t) \text{ A}$$

- 14.24** Use Thévenin's theorem to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.24.

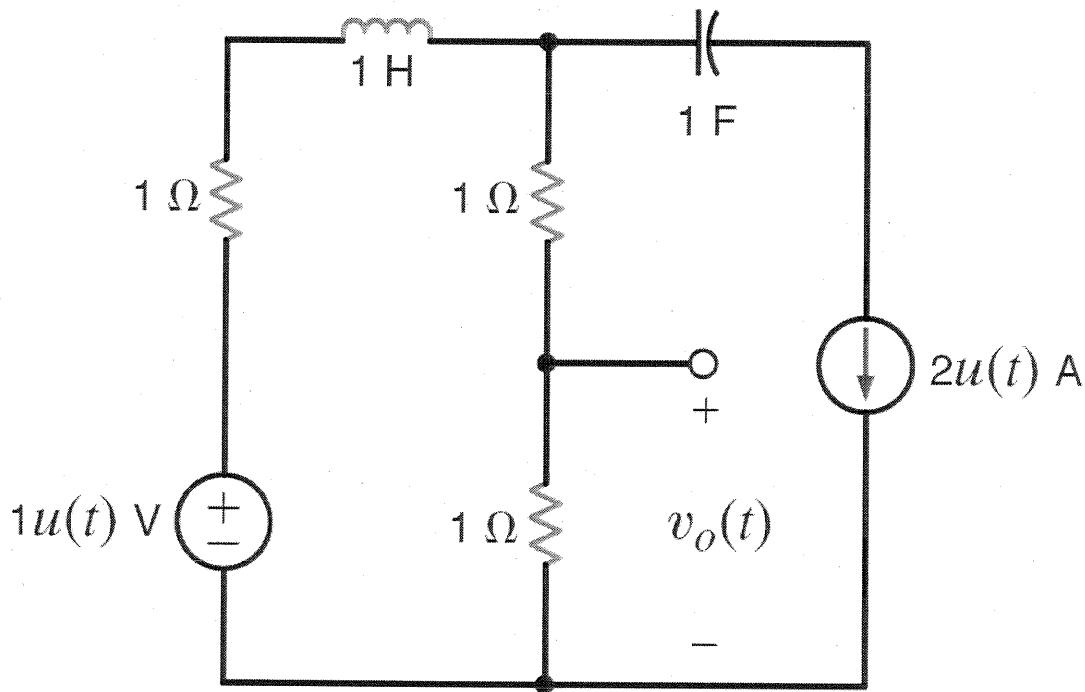

**Figure P14.24**


**SOLUTION:**

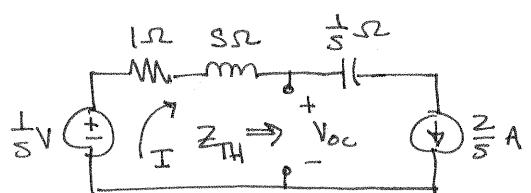

$$I = \frac{2}{s} A \quad \frac{1}{s} = (s+1) I + V_{oc}$$

$$\text{So, } V_{oc} = -\frac{(2s+1)}{s}$$

$$Z_{TH} = s + 1\Omega$$

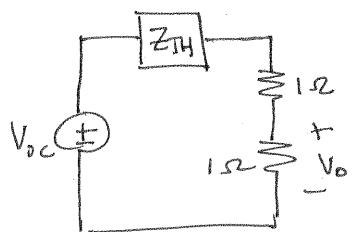

$$V_o = \frac{V_{oc}}{Z_{TH} + 1} = \frac{-(2s+1)}{s + s + 1} = -\frac{(2s+1)}{2s+2}$$

$$V_o = \frac{-1/3}{s} - \frac{5/3}{s+3}$$

$$V_o(t) = \left[ -\frac{1}{3} - \frac{5}{3} e^{-3t} \right] u(t) V$$

- 14.25** Use Thévenin's theorem to find  $v_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.25. **PSV**


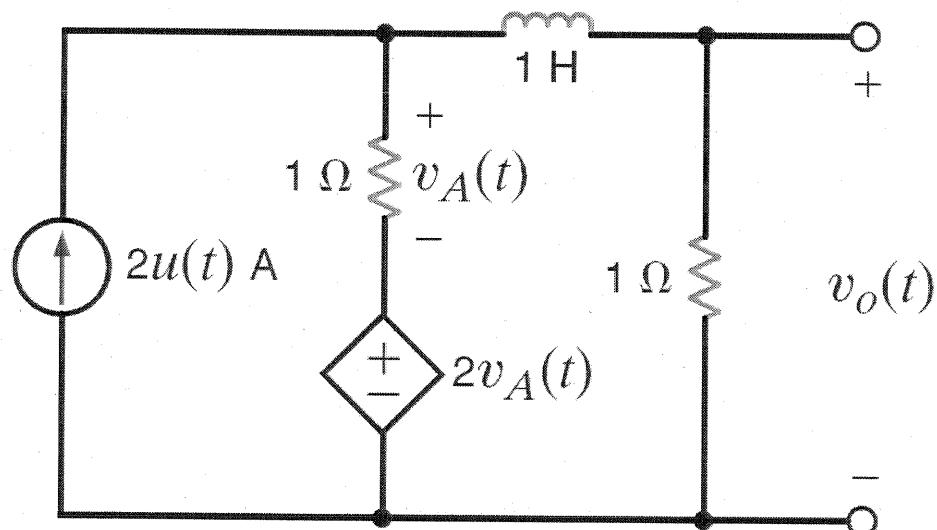



Figure P14.25

SOLUTION:

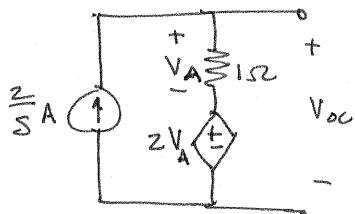

$$V_{oc} = 3V_A \neq V_A = (1)(2/s)$$


$$V_{oc} = 6/s$$

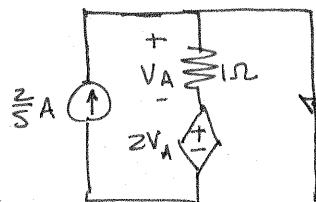

$$I_{sc} = \frac{2}{s}$$

$$Z_{TH} = V_{oc} / I_{sc}$$

$$Z_{TH} = 3\Omega$$

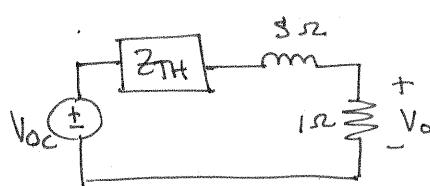

$$v_o = \frac{V_{oc}(1)}{s + 1 + Z_{TH}} = \frac{6}{s(s+4)} = \frac{3/s}{s} - \frac{3/s}{s+4}$$

$$v_o(t) = [1.5(1 - e^{-4t})] u(t) V$$

- 14.26** Find  $v_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.26 using Laplace transforms. Assume that the circuit has reached steady state at  $t = 0-$ .

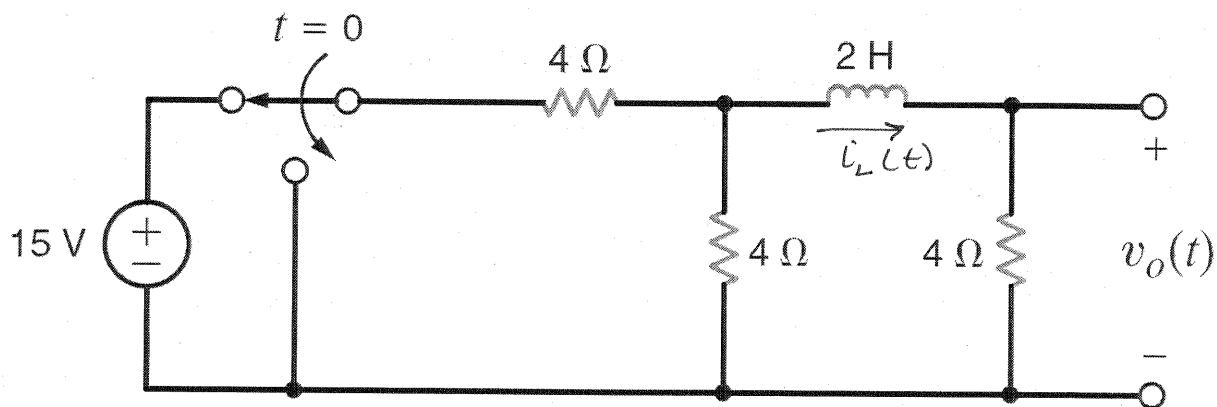


Figure P14.26

**SOLUTION:**

$$\begin{aligned} \text{At } t=0^- & \quad i_L(0^-) \\ \text{Circuit:} & \quad \text{15V source, } 4\Omega, 4\Omega, 4\Omega, i_L(0^-) \\ \text{Currents:} & \quad \frac{15}{4} \text{ A} \uparrow, \quad 4\Omega, 4\Omega, 4\Omega, 4\Omega \\ i_L(0^-) & = \left(\frac{15}{4}\right) \frac{1}{3} = 1.25 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{At } t=0^+ & \quad 2s\Omega, 2i_L(s), 4\Omega, 4\Omega, +v_o \\ \text{Circuit:} & \quad 4\Omega, 4\Omega, 2\Omega, 2\Omega \\ V_o & = Z i_L(0^-) \left[ \frac{4}{4+2+2s} \right] = \frac{5}{s+3} \\ V_o(t) & = 5 e^{-3t} \text{ V} \end{aligned}$$

14.27 Find  $i_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.27.



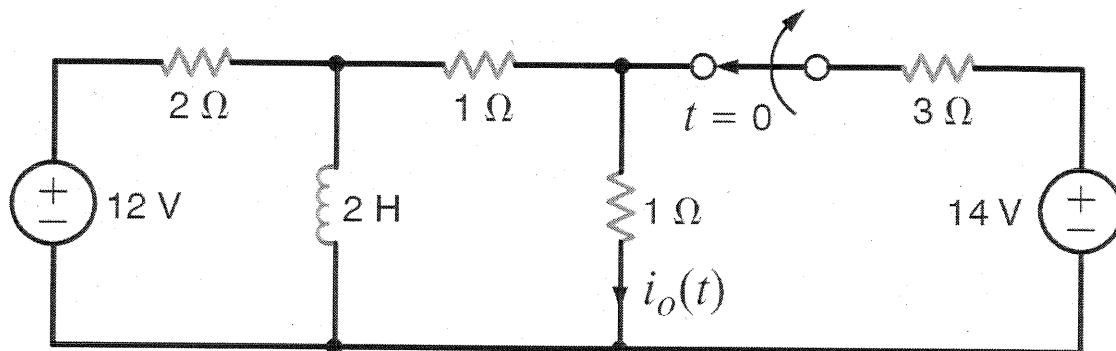


Figure P14.27

SOLUTION:



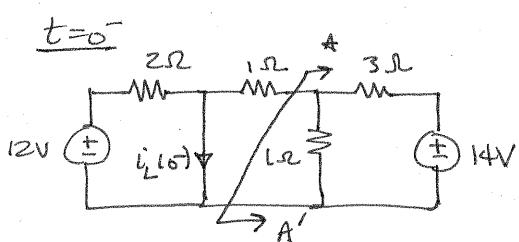


Use source transform & Norton's

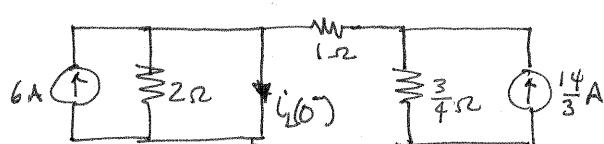

By superposition:
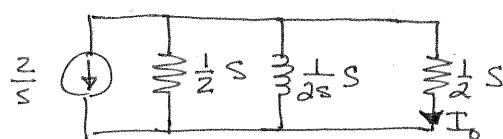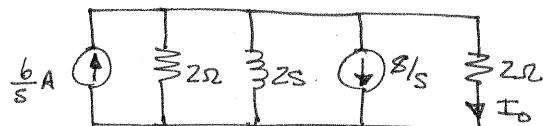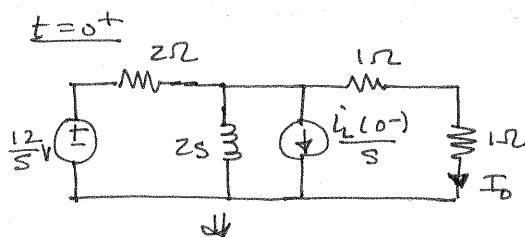
$$(i_L(0^-)) = 6 + \frac{14}{3} \left[ \frac{\frac{3}{4}}{1 + \frac{3}{4}} \right] = 8A$$



$$I_o = -\frac{2}{5} \left[ \frac{1/2}{1/2 + 1/2 + 1/2S} \right] = \frac{-1}{5 + 1/2}$$

$$i_o(t) = -e^{-t/2} u(t) A$$

14.28 Find  $i_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.28.

cs


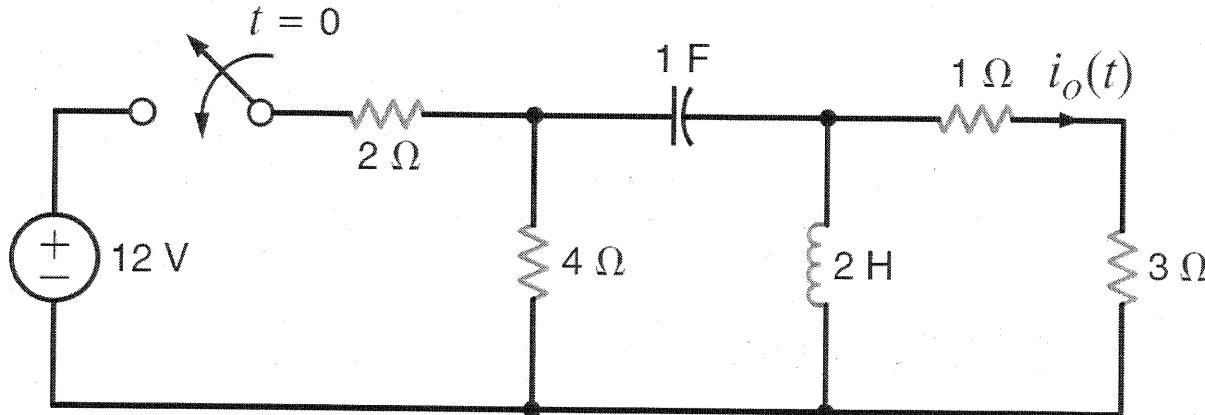



Figure P14.28

SOLUTION:
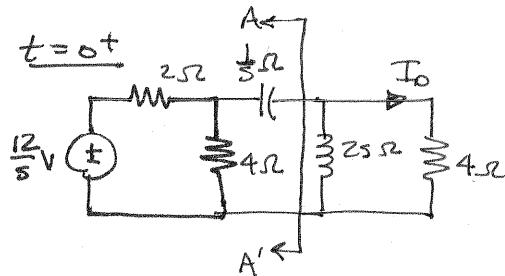
$$\begin{aligned} t=0^-, \quad i_L(0^-) &= 0 \\ V_C(0^-) &= 0 \end{aligned}$$




Thevenin at A-A'

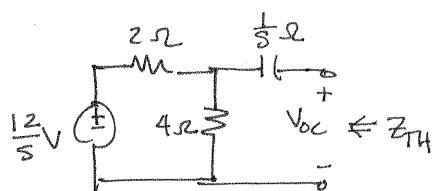

$$V_{oC} = \frac{12}{5} \left( \frac{4}{6} \right) = \frac{8}{5} V$$
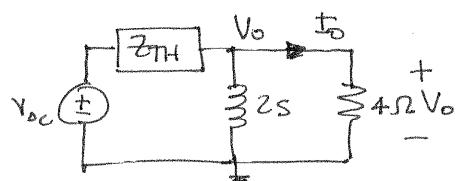
$$Z_{TH} = \frac{1}{s} + \frac{2(4)}{6} = \frac{1}{s} + \frac{4}{3} = \frac{4s+3}{3s}$$



$$\frac{V_0 - V_{oC}}{Z_{TH}} + \frac{V_0}{4} + \frac{V_0}{2s} = 0 \quad I_o = \frac{V_0}{4}$$

$$\text{Let } Z_1 = 2s(4)/(2s+4) = 4s/(s+2)$$

$$V_0 = V_{oC} Z_1 / (Z_1 + Z_{TH}) \Rightarrow I_o = V_0 / 4 = \frac{1.5s}{s^2 + (\frac{11}{16})s + \frac{6}{16}}$$

$$I_o = \frac{K}{s + \frac{11}{32} - j \sqrt{\frac{263}{32}}} + \frac{K^*}{s + \frac{11}{32} + j \sqrt{\frac{263}{32}}} \quad K = 0.906 \angle 34.2^\circ$$

$$i_o(t) = 6.81 e^{-0.344t} \cos(0.507t + 34.2^\circ) u(t) \text{ A}$$

14.29 Find  $v_o(t)$ ,  $t > 0$ , in the circuit shown in Fig. P14.29.

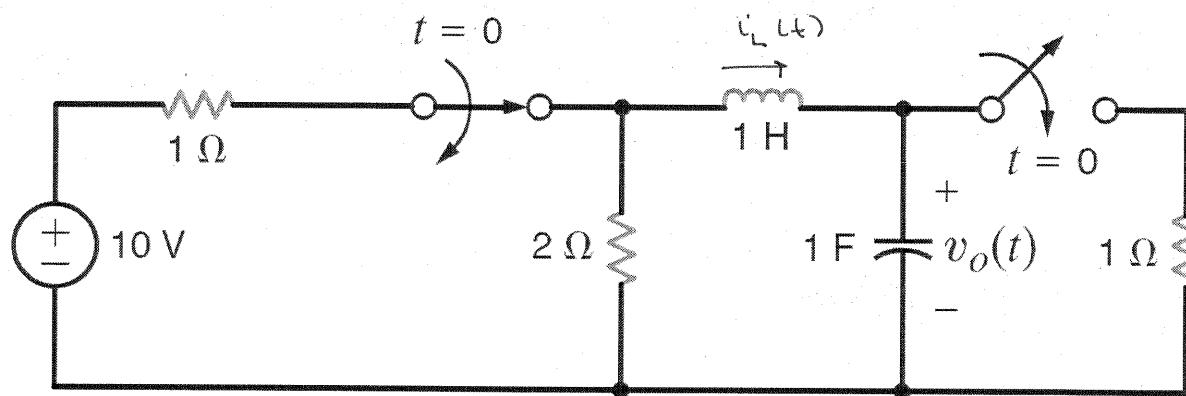



Figure P14.29

SOLUTION:

$$\begin{aligned} \underline{t=0^-} \quad & i_L(0^-) \\ \text{Circuit:} \quad & \begin{array}{c} \text{10V} \\ \text{+} \end{array} \text{---} \begin{array}{c} \text{1}\Omega \\ \text{---} \end{array} \text{---} \begin{array}{c} \text{2}\Omega \\ \text{---} \end{array} \text{---} \begin{array}{c} \text{?} \\ \text{+} \end{array} \text{---} \begin{array}{c} \text{?} \\ \text{-} \end{array} \end{aligned}$$

$$i_L(0^-) = 0$$
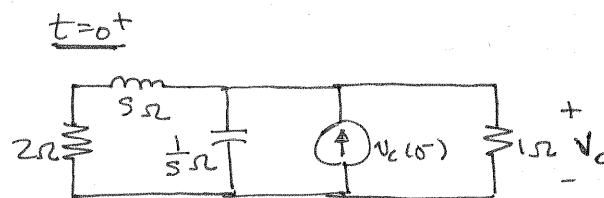
$$v_C(0^-) = \frac{10(2)}{3} = \frac{20}{3} \text{ V}$$



$$\frac{V_o}{s+2} + V_o(s) + \frac{V_o}{1} = \frac{20}{3} = V_o \left[ s+1 + \frac{1}{s+2} \right]$$

$$V_o \left[ \frac{s^2 + 3s + 3}{s+2} \right] = 20/3$$

$$V_o = \frac{20/3(s+2)}{s^2 + 3s + 3} = \frac{K}{s + \frac{3}{2} - j\frac{\sqrt{3}}{2}} + \frac{K^*}{s + \frac{3}{2} + j\frac{\sqrt{3}}{2}} ; \quad K = 3.85 \angle -30^\circ$$

$$V_o(t) = 7.7 e^{-(3/2)t} \cos[(\sqrt{3}/2)t - 30^\circ] u(t) \text{ V}$$

**14.30** Find  $v_o(t)$ ,  $t > 0$ , in the circuit in Fig. P14.30. **cs**


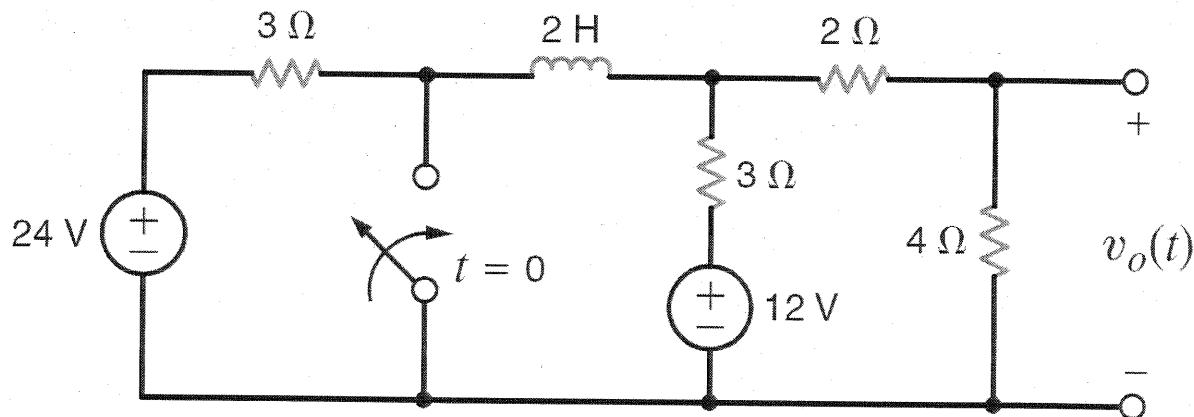


Figure P14.30

**SOLUTION:**

$t=0^-$

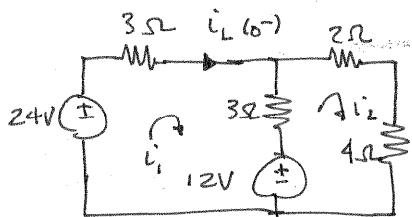


$$12 = 6i_1 - 3i_2$$

$$12 = -3i_1 + 9i_2$$

$$\text{yields } i_L(0^-) = i_1 = 3.2 \text{ A}$$

$t=0^+$

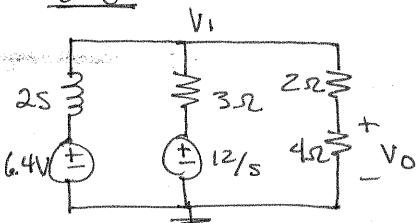

$$\frac{V_1 - 6.4}{2s} + \frac{V_1 - 12/s}{3} + \frac{V_1}{6} = 0$$

$$V_1 (3 + 3s) = 6(3.2) + 24 = 43.2$$

$$V_1 = 14.4 / (s+1)$$

$$V_o = V_1 (4/6) = 9.6 / (s+1)$$

$$v_o(t) = 9.6 e^{-t} u(t) \text{ V}$$

14.31 Find  $i_o(t)$ ,  $t > 0$ , in the network in Fig. P14.31.

**PSV**

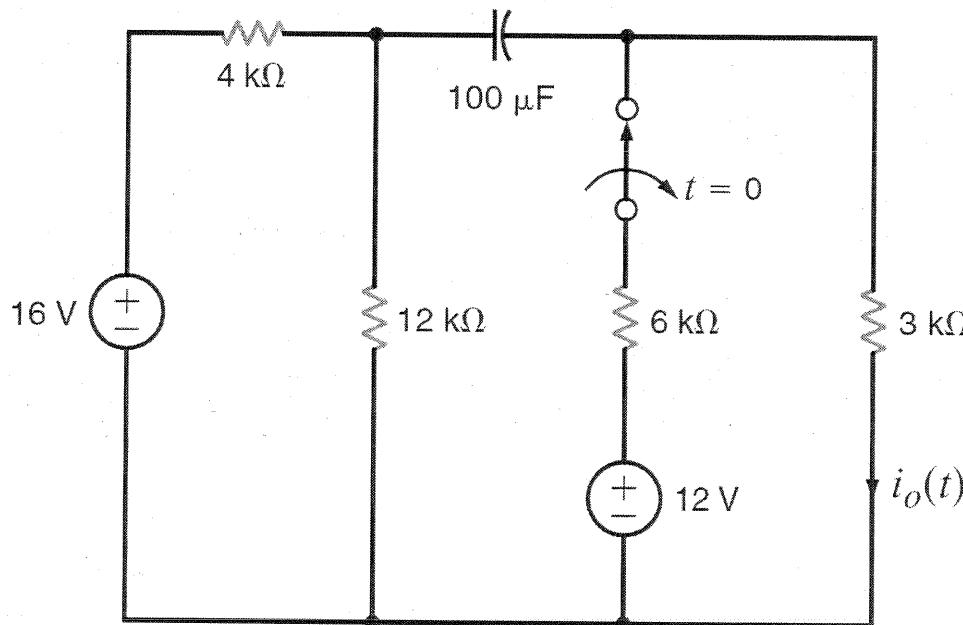


Figure P14.31


SOLUTION:

$$\underline{t=0^-}$$

$$v_c(0^-) = 16 \left(\frac{12}{16}\right) - 12 \left(\frac{3}{9}\right) = 8V$$

$$\underline{t=0^+} \quad (\text{w/ a source transformation})$$
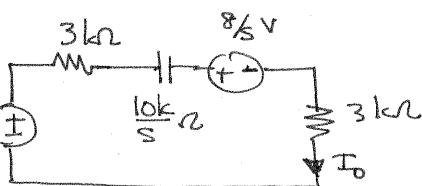
$$\frac{12}{s} = \left(3000 + 3000 + \frac{10^4}{s}\right) I_o + \frac{8}{s} \quad \Leftrightarrow \frac{12}{s}V$$



$$I_o = \frac{\frac{4}{6s+10}}{mA} = \frac{2/3}{s + 5/3}$$

$$i_o(t) = \frac{2}{3} e^{-\frac{(5/3)t}{}} u(t) \text{ mA}$$

14.32 Find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.32.

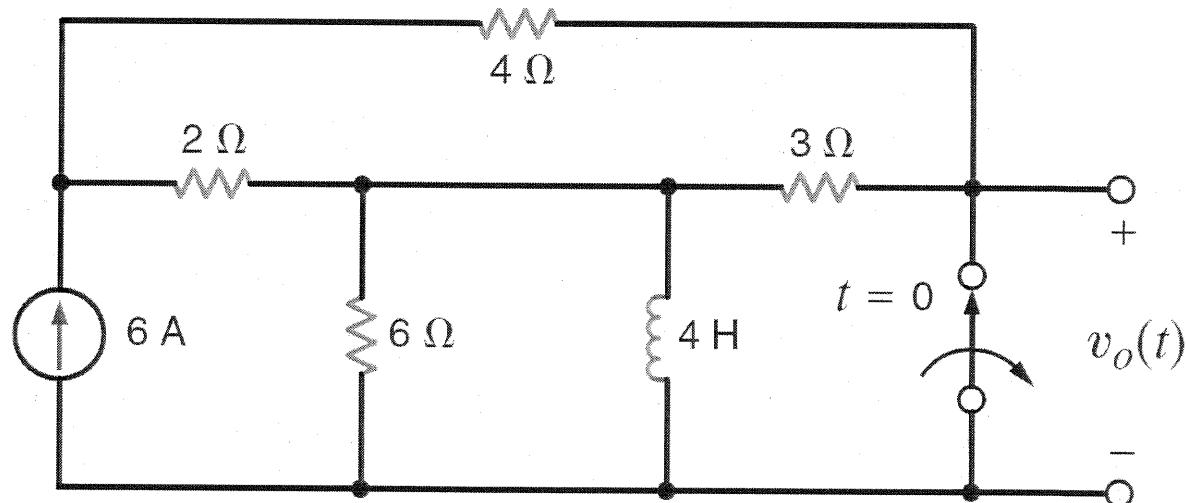


Figure P14.32

SOLUTION:

$$\begin{aligned} t=0^- & \quad 2\Omega \\ & \quad 4\Omega \quad 6A \uparrow \quad 6\Omega \quad i_L(0) \downarrow \quad 3\Omega \\ & \quad 4\Omega \end{aligned}$$

$$i_L(0) = 6 \left[ \frac{4}{4+2} \right] = 4A$$

$$\begin{aligned} t=0^+ & \quad 4\Omega \\ & \quad I_2 \quad 3\Omega \\ & \quad \frac{6}{s} \uparrow \quad I_1 \quad 2\Omega \quad 6\Omega \quad I_3 \quad 4s \quad 16V \\ & \quad + \quad V_o \quad - \end{aligned}$$

$$I_1 = 6/s \quad I_2(0) - 2I_1 = 0$$

$$V_o = 3I_2 + 4sI_3 - 16$$

$$16 = I_3(4s+6) - 6I_1$$

$$V_o = \frac{4}{s} + \frac{32s+72}{2s+3} - 16$$

$$\Leftrightarrow \text{yields } I_2 = \frac{4/3}{s} \quad I_3 = \frac{8s+18}{s(2s+3)}$$

$$V_o = \frac{16s+6}{s(s+1.5)} = \frac{4}{s} + \frac{12}{s+1.5} \Rightarrow$$

$$V_o(t) = \left[ 4 + 12e^{-1.5t} \right] u(t) V$$

14.33 Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.33.


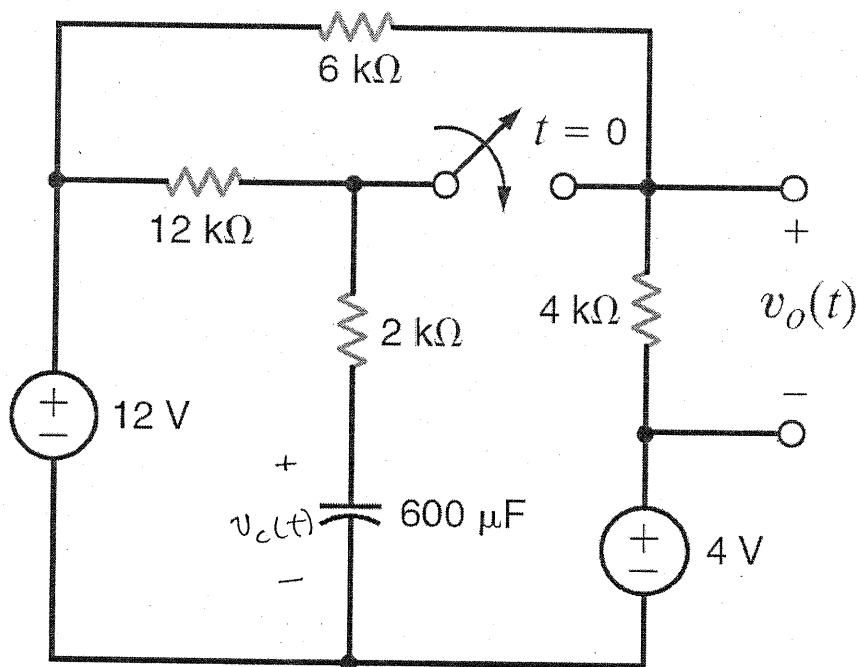


Figure P14.33

SOLUTION:  $V_c(0^-) = 12V$

$t=0^+$  ( $12k \neq 6k$  in parallel!)

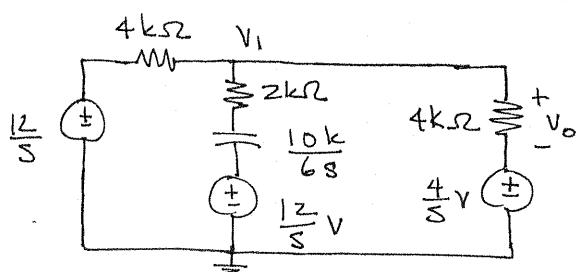

$$\frac{V_1 - 12/s}{4 \times 10^3} + \frac{V_1 - 12/s}{(2 + \frac{10}{6s}) \times 10^3} + \frac{V_1 - 4/s}{4 \times 10^3} = 0$$

$$\text{or}, \frac{V_1}{4} + \frac{V_1}{2 + \frac{10}{6s}} + \frac{V_1}{4} = \frac{3}{s} + \frac{1}{s} + \frac{12}{s(2 + \frac{10}{6s})}$$

$$V_1 \left[ \frac{12s + 5}{12s + 10} \right] = \frac{120s + 40}{s(12s + 10)}$$

$$V_1 = \frac{120s + 40}{s(12s + 5)}$$

$$V_B = V_1 - \frac{4}{s} = \frac{72s + 20}{s(12s + 5)}$$

$$V_o = \frac{(72s + 20)/12}{s(s + 5/12)} = \frac{4}{s} + \frac{2}{s + 5/12}$$

$$v_o(t) = [4 + 2e^{-(5/12)t}] u(t) V$$

14.34 Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.34.


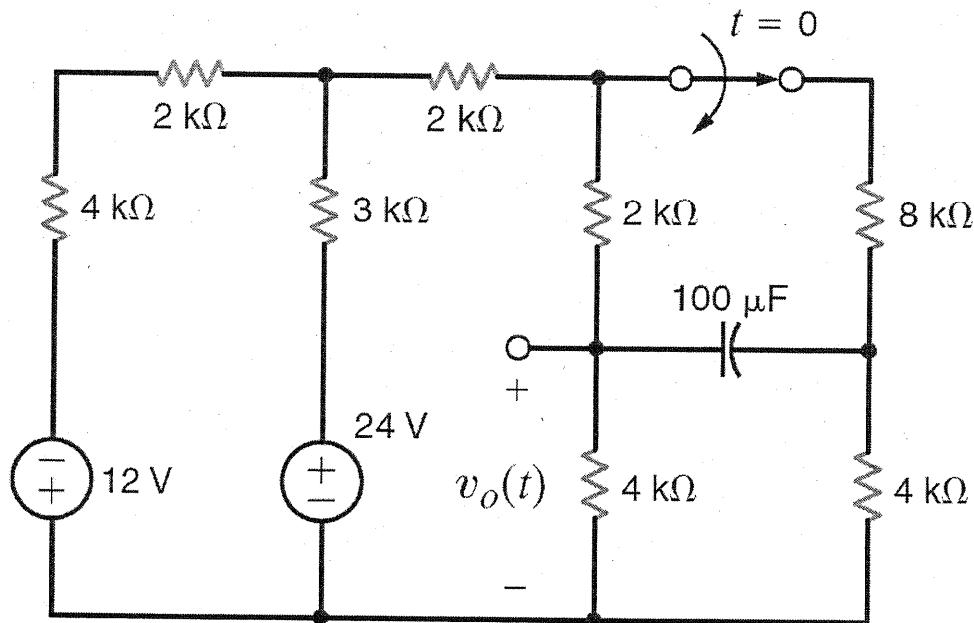
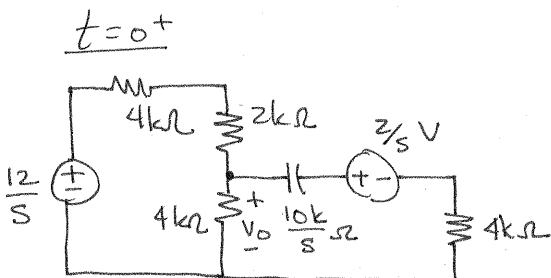
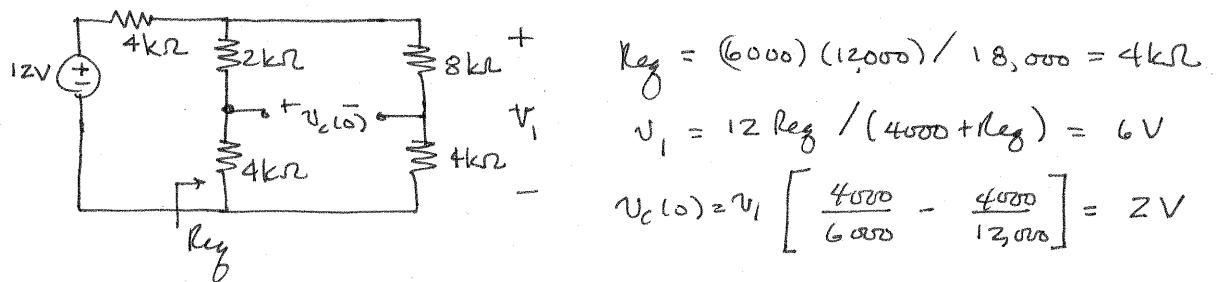


Figure P14.34

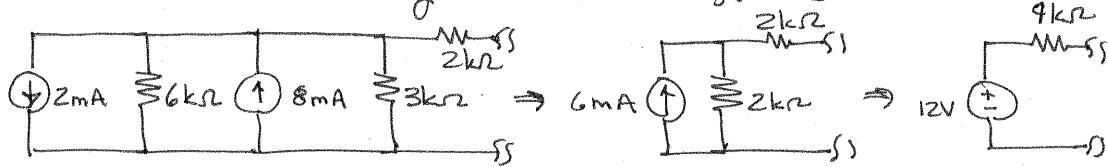SOLUTION:  $t=0^-$  (using source transforms!!)



$$\frac{v_o - 12/s}{6000} + \frac{v_o}{4000} + \frac{v_o - 2/s}{4000 + 10000/s} = 0$$

$$\frac{v_o}{6} + \frac{v_o}{4} + \frac{v_o s}{4s + 10} = \frac{2}{5} + \frac{2}{4s + 10}$$

$$V_o \left[ \frac{5}{12} + \frac{s}{4s+10} \right] = \frac{10s+20}{s(4s+10)} = V_o \left[ \frac{32s+50}{12(4s+10)} \right]$$

$$V_o = \frac{\frac{15}{4}(s+2)}{s(s+\frac{25}{16})} = \frac{24/5}{s} - \frac{21/20}{s + 25/16}$$

$$\boxed{V_o(t) = \left[ \frac{24}{5} - \frac{21}{20} e^{-\frac{(25/16)t}{}} \right] u(t) \text{ V}}$$

**14.35** Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.35.

CS

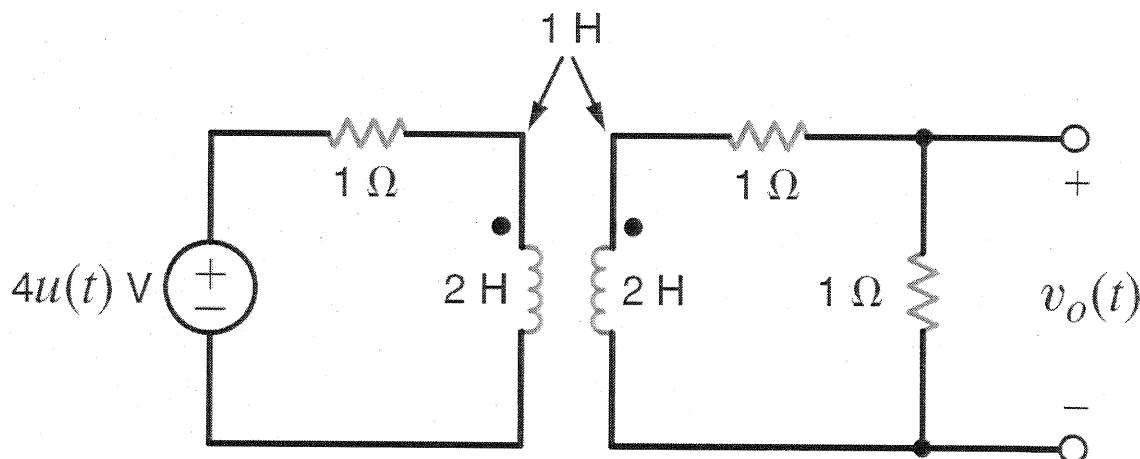


Figure P14.35

SOLUTION:  $t = 0^-$ : no excitation  $\rightarrow$  no initial conditions

$$\begin{aligned} t > 0 & \quad \text{Circuit diagram showing two parallel branches. Left branch has } 1\Omega \text{ and } \frac{4}{s}V \text{ source. Right branch has } 2H \text{ and } 1\Omega \text{ in series. Currents } I_1 \text{ and } I_2 \text{ are indicated.} \\ \frac{4}{s}V & \quad \text{Yields, } I_2 = \frac{4/3}{s^2 + 2s + 2/3} \\ I_1 & \quad \text{or, } I_1 = I_2(2s+2)/s \\ & \quad \text{or, } I_1 = \frac{4/3}{s^2 + 2s + 2/3} \end{aligned}$$

$$V_o = (1)I_2 = \frac{4/3}{(s+0.42)(s+1.58)}$$

$$V_o = \frac{1.15}{s+0.42} - \frac{1.15}{s+1.58}$$

$$v_o(t) = 1.15 [e^{-0.42t} - e^{-1.58t}] u(t) V$$

**14.36** Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.36.

**PSV**

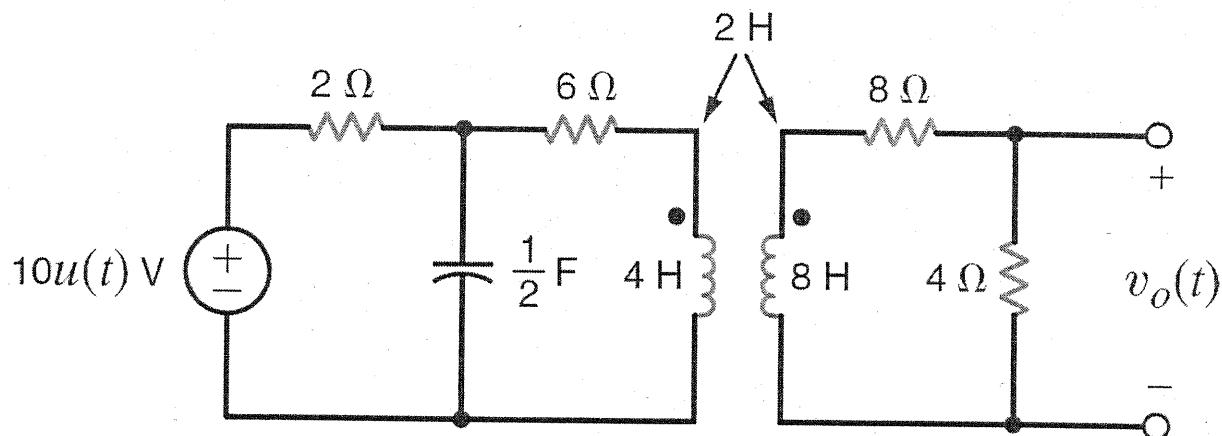


Figure P14.36

**SOLUTION:**  $t = 0^-$ : no excitation  $\Rightarrow \emptyset$  initial conditions

$t = 0^+$  (use Thevenin 1st)

$$\frac{10}{s} \text{ V} \quad \begin{array}{l} 2\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} Z_{TH} \\ + \\ - \end{array} \quad V_{OC}$$

$$V_{OC} = \frac{10}{s} \left[ \frac{2/s}{2/s + 2} \right] = \frac{10}{s(s+1)} \text{ V}$$

$$Z_{TH} = 2(2/s) / \left[ 2 + \frac{2}{s} \right] = \frac{2}{s+1} \Omega$$

$$\begin{array}{l} \frac{10}{s} \text{ V} \quad \begin{array}{l} 2\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} Z_{TH} \\ + \\ - \end{array} \quad I_1 \\ V_{OC} \quad \begin{array}{l} 6\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} 2s \\ + \\ - \end{array} \quad I_1 \\ \begin{array}{l} 4s \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} 8\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} 8s \\ + \\ - \end{array} \quad I_2 \\ \begin{array}{l} 8s \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} 4\Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{l} V_o \\ + \\ - \end{array} \quad I_2 \end{array}$$

$$V_{OC} = I_1(4s+6+Z_{TH}) - 2sI_2$$

$$0 = -2sI_1 + I_2(8s+12)$$

$$\text{yields, } I_1 = I_2 (4s+6)/s \Rightarrow V_{OC} = I_2 \left[ (4s+6+Z_{TH})(4s+6) - 2s \right]$$

solve for  $I_2$  and use  $V_o = 4I_2$

$$V_o = \frac{20/s}{s^3 + \left(\frac{31}{7}\right)s^2 + \left(\frac{46}{7}\right)s + \frac{24}{7}}$$

Using the ROOTS function in MATLAB yields

$$V_0 = \frac{20j}{(s+2)(s+1.21-j0.5)(s+1.21+j0.5)} = \frac{A}{s+2} + \frac{K}{s+1.21-j/2} + \frac{K^*}{s+1.21+j/2}$$

$$A = 3.33 \quad K = 3.15 \underline{-122}$$

$$v_o(t) = [3.33 e^{-2t} + 6.30 e^{-1.21t} \cos(t/2 - 122^\circ)] u(t) V \quad \checkmark$$

14.37 Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.37.

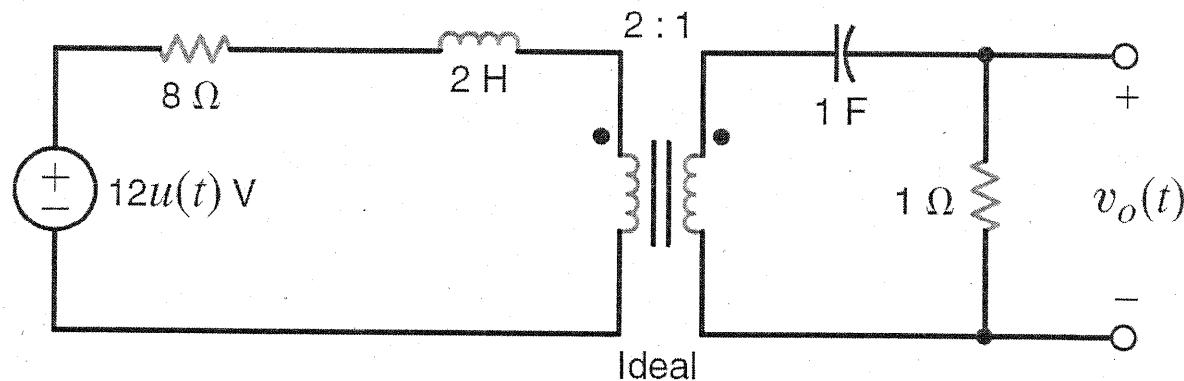


Figure P14.37

SOLUTION:

$$\begin{aligned}
 &\text{Circuit diagram: } \frac{12}{s} \text{ V source, } 8 \Omega \text{ resistor, } 2 \text{ H inductor, } 2:1 \text{ ideal transformer, } 1 \text{ F capacitor, } 1 \Omega \text{ resistor, } v_o(t) \\
 &\text{Transformed circuit: } \frac{12}{s} \text{ V source, } \frac{2s}{8} = \frac{s}{4} \Omega \text{ resistor, } 2:1 \text{ ideal transformer, } \frac{1}{s} \Omega \text{ capacitor, } 1 \Omega \text{ resistor, } v_o \\
 &n = \frac{1}{2} \\
 &\text{Circuit diagram: } \frac{6}{s} \text{ V source, } \frac{s}{2} \Omega \text{ resistor, } \frac{1}{2} \Omega \text{ resistor, } \frac{1}{s} \Omega \text{ capacitor, } 1 \Omega \text{ resistor, } v_o \\
 &V_o = \frac{6}{s} \left[ \frac{1}{2 + \frac{s}{2} + \frac{1}{s} + 1} \right] = \frac{12}{s^2 + 6s + 2} \\
 &V_o = \frac{A}{s+0.35} + \frac{B}{s+5.65}
 \end{aligned}$$

$$A = 2.28 \quad * \quad B = -2.28$$

$$v_o(t) = 2.28 [e^{-0.35t} - e^{-5.65t}] u(t) \text{ V}$$

14.38 Find  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.38.

(CS)


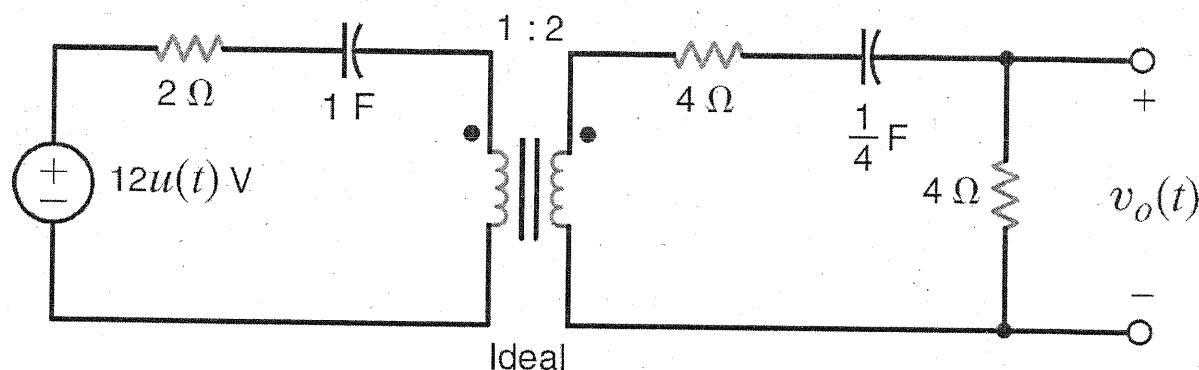
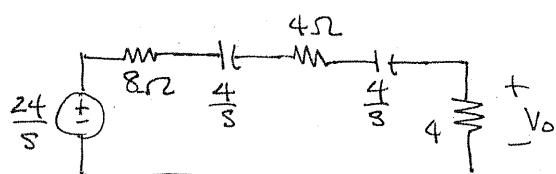


Figure P14.38

SOLUTION:

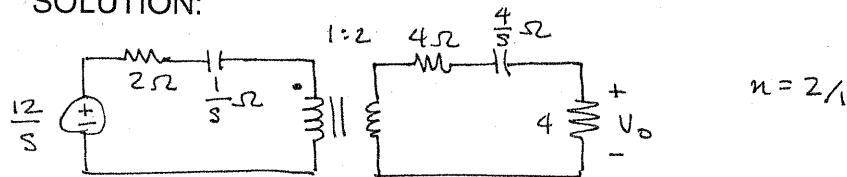

$$V_o = \frac{24}{s} \left[ \frac{4}{(8/s) + 16} \right] \Rightarrow V_o = \frac{6}{s + 16}$$

$$v_o(t) = 6e^{-t/16} u(t) V$$

- 14.39 Determine the initial and final values of the voltage  $v_o(t)$  in the network in Fig. P14.39.

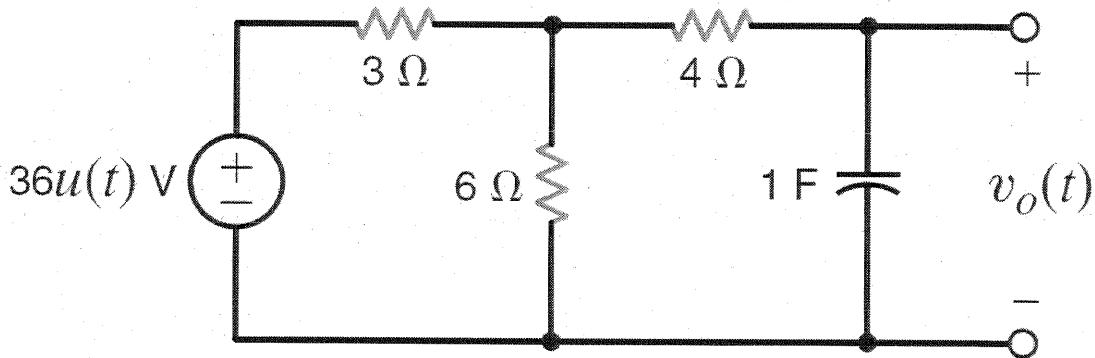


Figure P14.39

SOLUTION: Use Thévenin's

$$\frac{36}{s} \text{ V} \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \quad \leftarrow Z_{TH} \quad V_{OC} = \frac{6}{9} (36/s) = 24/s \text{ V}$$

$$Z_{TH} = 3(6)/9 = 2\Omega$$

$$\frac{24}{s} \text{ V} \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \quad \frac{1}{s} \quad \frac{1}{s} \quad V_o$$

$$V_o = \frac{24}{s} \left[ \frac{1/s}{6 + 1/s} \right] = \frac{24}{s(6s+1)}$$

$$\lim_{t \rightarrow 0} V_o(t) = \lim_{s \rightarrow \infty} s V_o(s) = \frac{24}{6(0)} = 0 \quad \boxed{V_o(0) \rightarrow 0 \text{ V}}$$

$$\lim_{t \rightarrow \infty} V_o(t) = \lim_{s \rightarrow 0} s V_o(s) = \frac{24}{1} = 24 \text{ V} \quad \boxed{V_o(\infty) \rightarrow 24 \text{ V}}$$

- 14.40** Determine the initial and final values of the voltage  $v_o(t)$  in the network in Fig. P14.40.

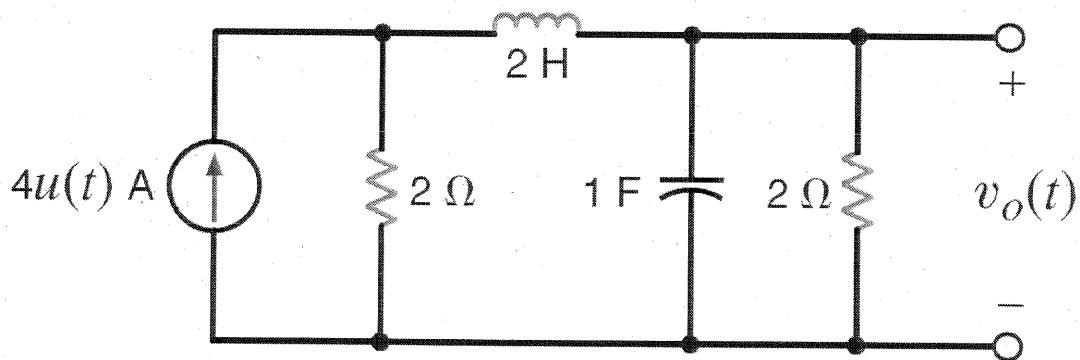
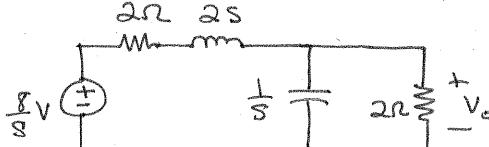


Figure P14.40

**SOLUTION:** Use source transformation,

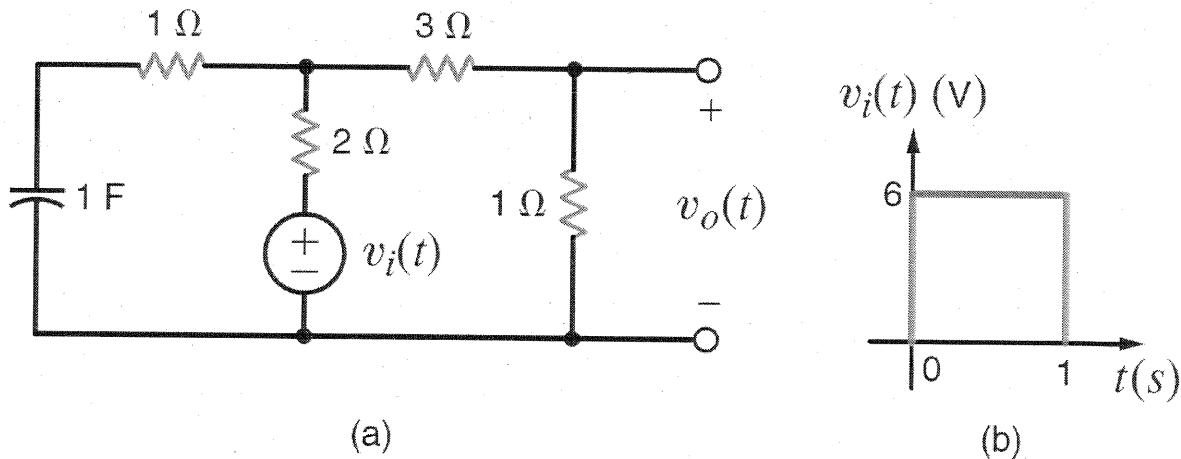

 Let  $Z_1 = 2 + 2s$  and  
 $Z_2 = 2(1/s) / (2 + 1/s) = \frac{2}{2s+1} \Omega$

$$V_o = \frac{8}{s} \left[ \frac{Z_2}{Z_1 + Z_2} \right] = \frac{8}{s} \left[ \frac{2}{2 + (2s+2)(2s+1)} \right] = \frac{16}{s(4s^2 + 6s + 4)}$$

$$\lim_{t \rightarrow 0} v_o(t) = \lim_{s \rightarrow \infty} sV_o(s) = \frac{16}{4\infty^2} = 0 \quad \boxed{v_o(0) \rightarrow 0}$$

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} sV_o(s) = \frac{16}{4} = 4 \quad \boxed{v_o(\infty) \rightarrow 4V}$$

- 14.41** Determine the output voltage  $v_o(t)$  in the network in Fig. P14.41a if the input is given by the source in Fig. P14.41b. **PSV**


**Figure P14.41**

SOLUTION:  $v_i(t) = 6u(t) - 6u(t-1)$        $V_I(s) = \frac{6}{s} (1 - e^{-s})$


Use Thevenin eq.

$$\begin{aligned}
 & \text{Circuit diagram showing the Thevenin equivalent circuit: } V_I \text{ is applied to a } 2\Omega \text{ resistor in series with a } 1\Omega \text{ resistor. The output } V_{oc} \text{ is measured across the } 1\Omega \text{ resistor. The Thevenin resistance } Z_{TH} \text{ is shown.} \\
 & V_{oc} = V_I \left[ \frac{1 + 1/s}{3 + 1/s} \right] = V_I \left( \frac{s+1}{3s+1} \right) \\
 & Z_{TH} = \frac{(1 + 1/s)(2)}{3 + 1/s} = \frac{2(s+1)}{3s+1} \\
 & \text{Circuit diagram showing the final circuit with the Thevenin source: } V_{oc} \text{ is applied to a } Z_{TH} \text{ resistor in series with a } 3\Omega \text{ resistor. The output } V_o \text{ is measured across the } 3\Omega \text{ resistor.} \\
 & V_o = V_{oc} \left[ \frac{1}{4 + Z_{TH}} \right] = V_I \left( \frac{s+1}{3s+1} \right) \left( \frac{3s+1}{4(3s+1) + 2s+2} \right) \\
 & V_o = \frac{(6/14)(s+1)(1-e^{-s})}{s(s+6/14)} = \left[ 1 - \frac{4/7}{s+6/14} \right] (1-e^{-s}) \\
 & V_o(t) = \left[ 1 - \frac{4}{7} e^{-\frac{(6/14)t}{}} \right] u(t) - \left[ 1 - \frac{4}{7} e^{-\frac{(6/14)(t-1)}{}} \right] u(t-1) \quad V \quad \checkmark
 \end{aligned}$$

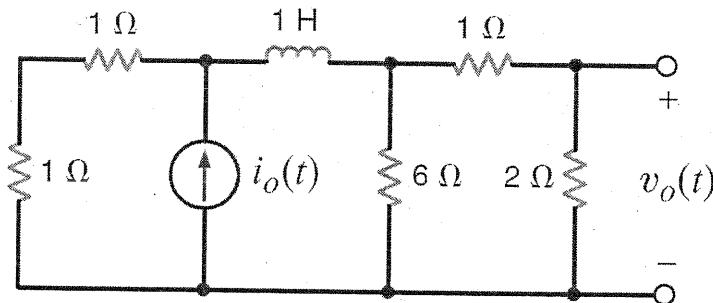- 14.42** Find the output voltage,  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.42a if the input is represented by the waveform shown in Fig. P14.42b.



(a)

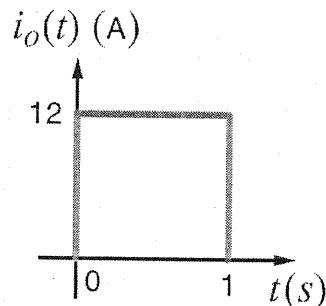


(b)

**Figure P14.42**

**SOLUTION:**  $i_o(t) = 12u(t) - 12u(t-1)$  A  $\Rightarrow I_o(s) = \frac{12}{s}(1 - e^{-s})$  A


Use Thevenin Eq.
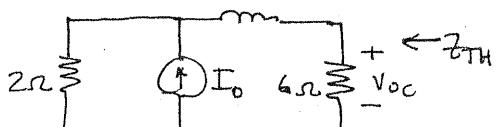
$$V_{oc} = I_o \left[ \frac{2(6)}{s+8} \right] = I_o \left( \frac{12}{s+8} \right)$$



$$Z_{TH} = \frac{6(s+2)}{s+8}$$
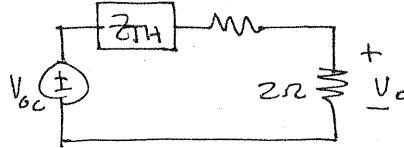
$$V_o = V_{oc} \left( \frac{2}{3 + Z_{TH}} \right) = I_o \left[ \frac{24}{3(s+8) + 6(s+2)} \right]$$




$$V_o = I_o \left[ \frac{24}{9s + 36} \right] = \frac{(8/3)(12)}{s(s+4)} (1 - e^{-s})$$


$$V_o = \left( \frac{8}{s} - \frac{8}{s+4} \right) (1 - e^{-s})$$

$$v_o(t) = [8 - 8e^{-4t}]u(t) - [8 - 8e^{-4(t-1)}]u(t-1) \quad V \quad \leftarrow$$

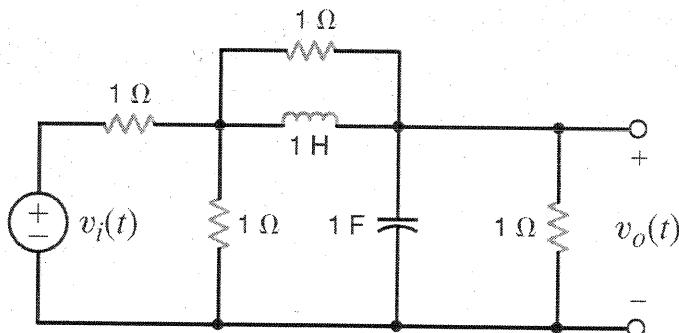- 14.43 Determine the output voltage,  $v_o(t)$ , in the circuit in Fig. P14.43a if the input is given by the source described in Fig. P14.43b.



(a)

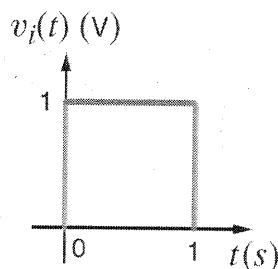


(b)

Figure P14.43


$$\text{SOLUTION: } v_i(t) = u(t) - u(t-1) \Rightarrow V_I(s) = \frac{1}{s} (1 - e^{-s}) \text{ V}$$

Use Thevenins twice!

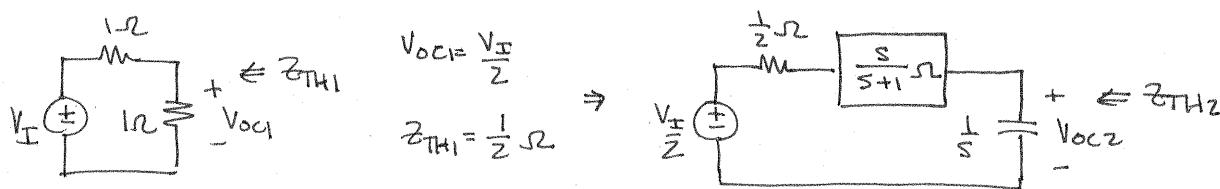


$$V_{OC1} = \frac{V_I}{2}$$

$$Z_{TH1} = \frac{1}{2}\ \Omega$$

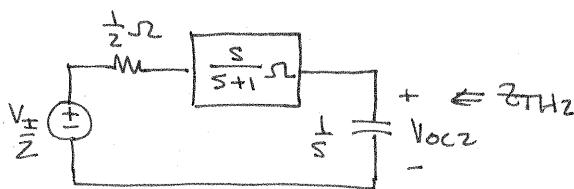

$$V_{OC2} = \frac{V_I}{2} \left[ \frac{\frac{1}{s}}{\frac{1}{2} + \frac{s}{s+1} + \frac{1}{s}} \right] = \frac{V_I (s+1)}{3s^2 + 3s + 2}$$
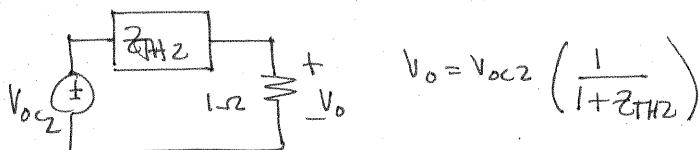
$$Z_{TH2} = \frac{\frac{1}{s} \left( \frac{1}{2} + \frac{s}{s+1} \right)}{\frac{1}{2} + \frac{1}{s} + \frac{s}{s+1}}$$



$$V_o = V_{OC2} \left( \frac{1}{1 + Z_{TH2}} \right)$$

$$Z_{TH2} = \frac{3s+1}{3s^2 + 3s + 2}$$

$$V_0 = \frac{\left(\frac{1}{3}\right)}{s(s+1)} (1 - e^{-s}) = \left(\frac{1}{s} - \frac{1}{s+1}\right) (1 - e^{-s})$$

$$v_0(t) = \frac{1}{3} [1 - e^{-t}] u(t) - \frac{1}{3} [1 - e^{-(t-1)}] u(t-1) \quad \checkmark$$

**14.44** Determine the transfer function  $\mathbf{I}_o(s)/\mathbf{I}_i(s)$  for the network shown in Fig. P14.44.


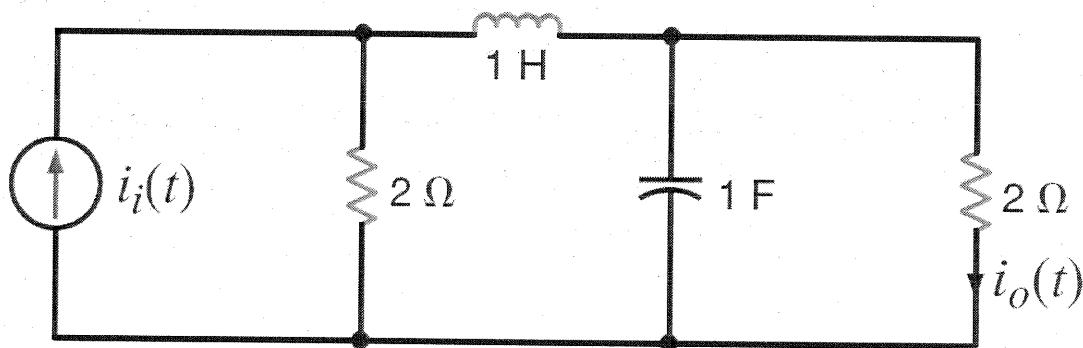


Figure P14.44

**SOLUTION:** Use source transformations

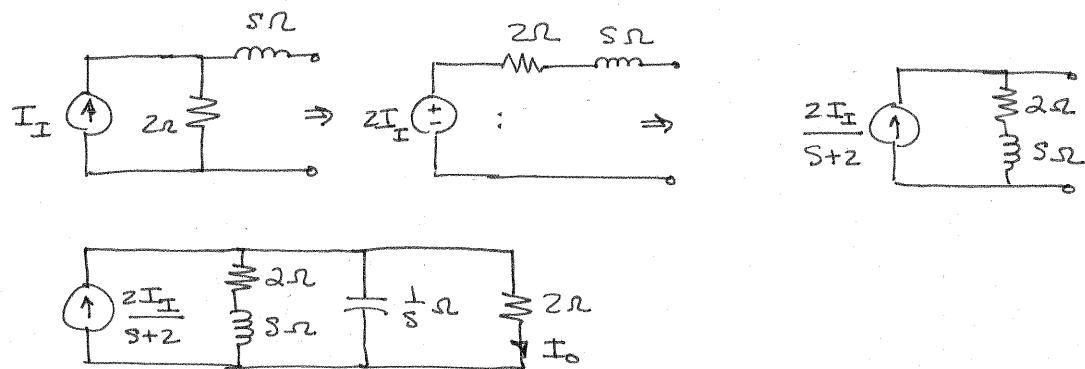

$$\text{Current Division: } \mathbf{I}_o = \frac{2\mathbf{I}_I}{s+2} \left[ \frac{\frac{1}{2}}{\frac{1}{2} + s + \frac{1}{s+2}} \right] = \frac{\mathbf{I}_I}{(s+2)(s+\frac{1}{2})+1}$$

$$\boxed{\frac{\mathbf{I}_o}{\mathbf{I}_I} = \frac{1}{s^2 + 2.5s + 2}}$$

- 14.45 Find the transfer function  $V_o(s)/V_i(s)$  for the network shown in Fig. P14.45. [cs]


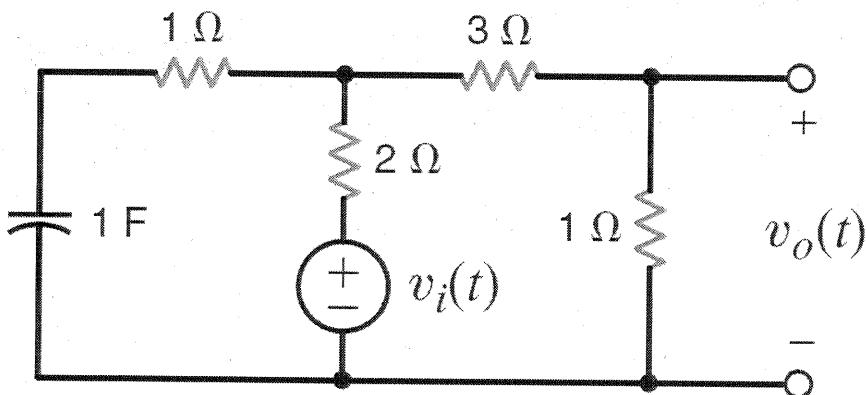



Figure P14.45

SOLUTION: Use Thévenin eq

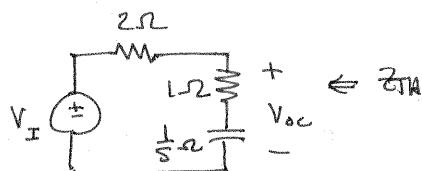

$$V_{oc} = V_I \frac{(1 + 1/s)}{3 + 1/s} = \frac{V_I (s+1)}{3s+1}$$
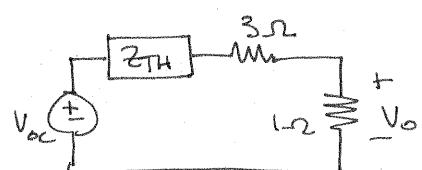
$$Z_{TH} = \frac{2(1 + 1/s)}{3 + 1/s} = \frac{2(s+1)}{3s+1}$$




$$V_o = V_{oc} \left[ \frac{1}{4 + Z_{TH}} \right] = \frac{V_I (s+1)}{3s+1} \left( \frac{3s+1}{4(3s+1) + 2(s+1)} \right)$$

$$V_o = V_I \left[ \frac{s+1}{14s+6} \right]$$

$$\boxed{\frac{V_o}{V_I} = \frac{s+1}{14s+6}}$$

**14.46** Find the transfer function for the network shown in Fig. P14.46.

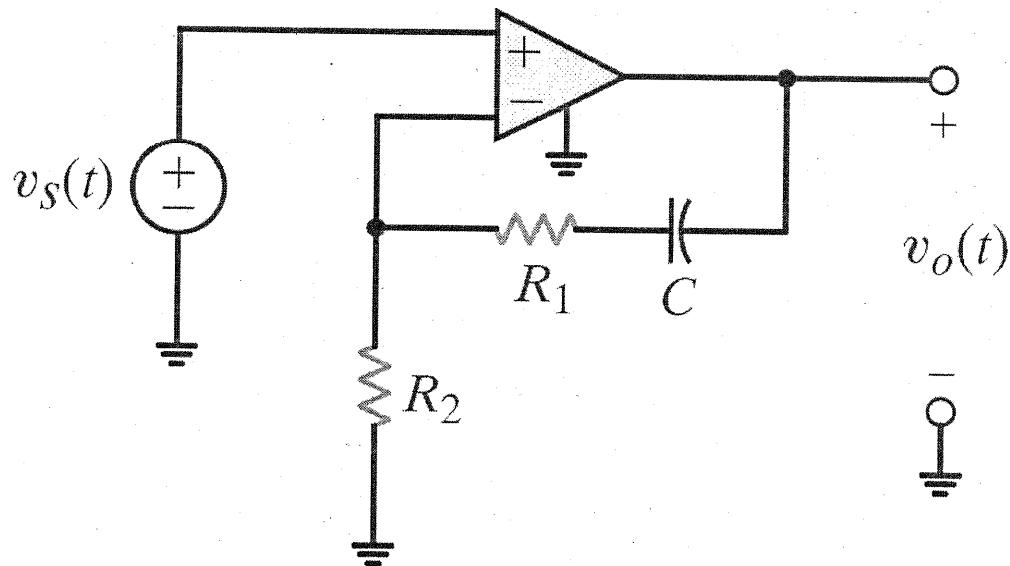

**Figure P14.46**


**SOLUTION:**

$$\text{Let } Z_2 = R_1 + \frac{1}{sC} \quad \text{and} \quad Z_1 = R_2 \quad \frac{V_o}{V_s} = 1 + \frac{Z_2}{Z_1}$$

$$\frac{V_o}{V_s} = 1 + \frac{R_1 + \frac{1}{sC}}{R_2} = 1 + \frac{R_1 s C + 1}{R_2 s C} = \frac{(R_1 + R_2) s C + 1}{R_2 s C}$$

$$\boxed{\frac{V_o}{V_s} = \left(1 + \frac{R_1}{R_2}\right) \left[ \frac{s + \frac{1}{C(R_1 + R_2)}}{s} \right]}$$

**14.47** Find the transfer function for the network shown in Fig. P14.47.

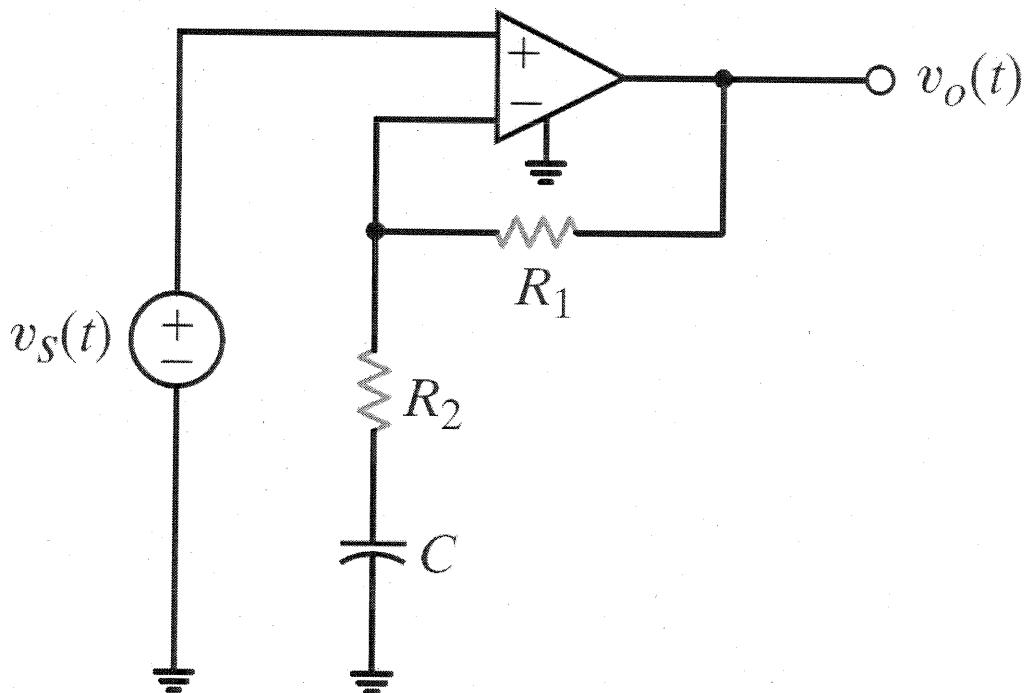

**Figure P14.47**


SOLUTION: Let  $Z_2 = R_1$  &  $Z_1 = R_2 + \frac{1}{sC} = \frac{R_2 Cs + 1}{sC}$

$$\frac{V_o}{V_s} = 1 + \frac{Z_2}{Z_1} = 1 + \frac{R_1 Cs}{R_2 Cs + 1} = \frac{(R_1 + R_2)Cs + 1}{R_2 Cs + 1}$$

$$\frac{V_o}{V_s} = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{s + \frac{1}{CR_2}}{s + \frac{1}{CR_1}}\right)$$

$$R = R_1 + R_2$$

**14.48** Find the transfer function for the network in Fig. P14.48. **PSV**

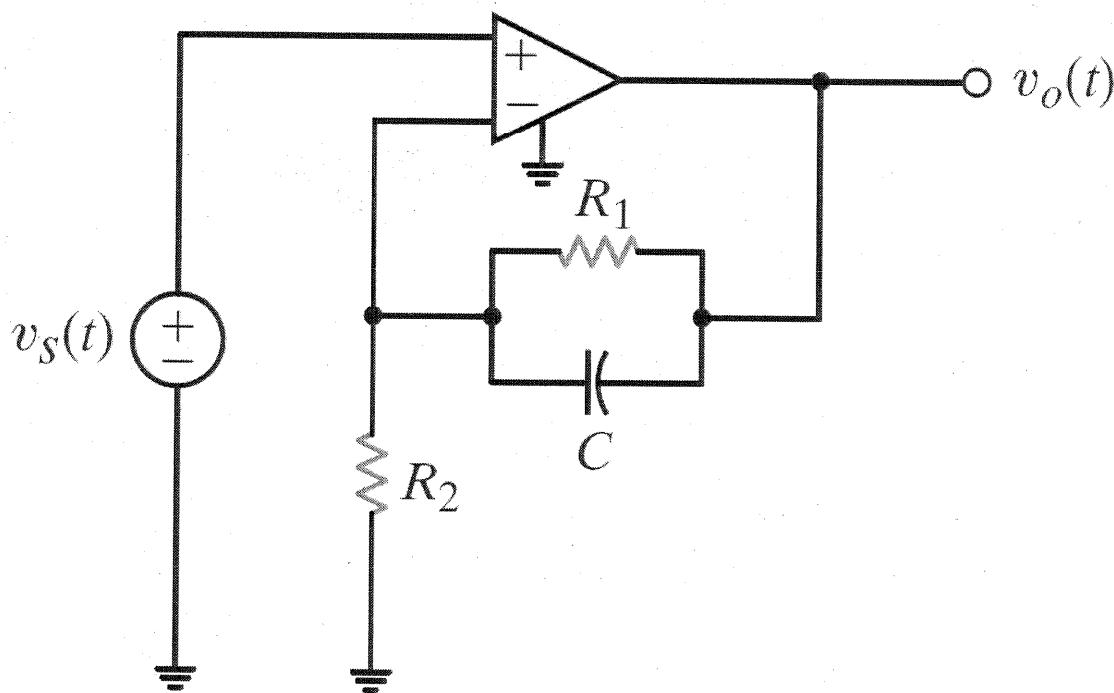

**Figure P14.48**

SOLUTION: Let  $Z_1 = R_2$  &  $Z_2 = \frac{R_1/sC}{R_1 + 1/sC} = \frac{R_1}{sCR_1 + 1}$

$$\frac{V_o}{V_s} = 1 + \frac{Z_2}{Z_1} = 1 + \frac{R_1/R_2}{sCR_1 + 1} = \frac{sCR_1 + 1 + R_1/R_2}{sCR_1 + 1} = \frac{1}{R_2} \left[ \frac{sCR_1R_2 + R_1 + R_2}{sCR_1 + 1} \right]$$

$$\boxed{\frac{V_o}{V_s} = \left(1 + \frac{R_1}{R_2}\right) \left( \frac{sCR_P + 1}{sCR_1 + 1} \right) \quad R_P = \frac{R_1R_2}{R_1 + R_2}}$$

- 14.49** Find the transfer function for the network in Fig. P14.49. If a step function is applied to the network, will the response be overdamped, underdamped, or critically damped?

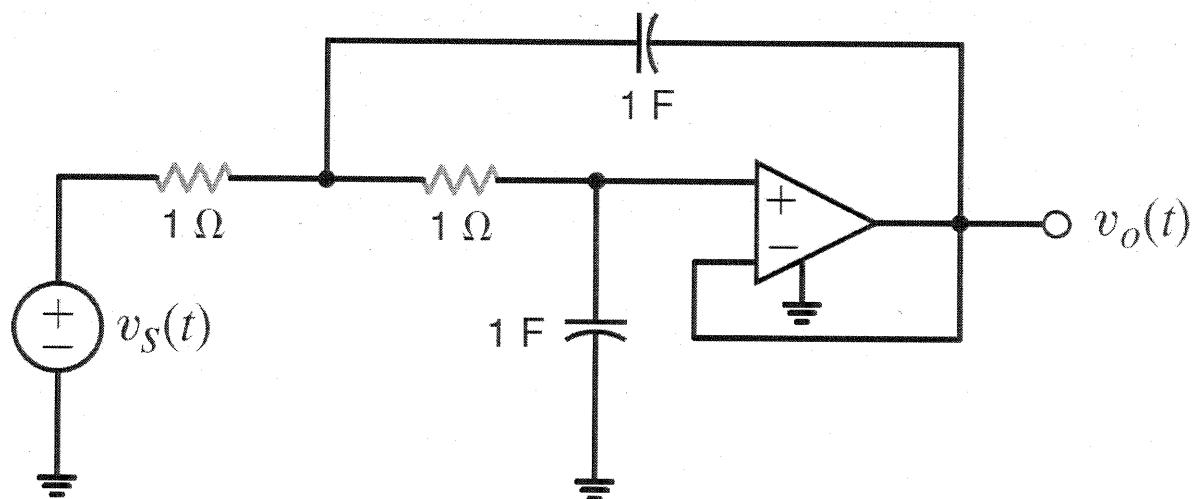


Figure P14.49

**SOLUTION:** Op amp is in unity gain configuration.

$$\frac{V_x - V_o}{1} = \frac{V_o}{1/s} \Rightarrow V_x = V_o(s+1)$$

$$\frac{V_s - V_x}{1} = \frac{V_x - V_o}{1} + \frac{V_x - V_o}{1/s}$$

yields  $V_s = V_o (s+1)^2$

$$\frac{V_o}{V_s} = \frac{1}{(s+1)^2}$$

Poles are real & identical,  
so,

CRITICALLY DAMPED!

- 14.50 Find the transfer function for the network in Fig. P14.50.


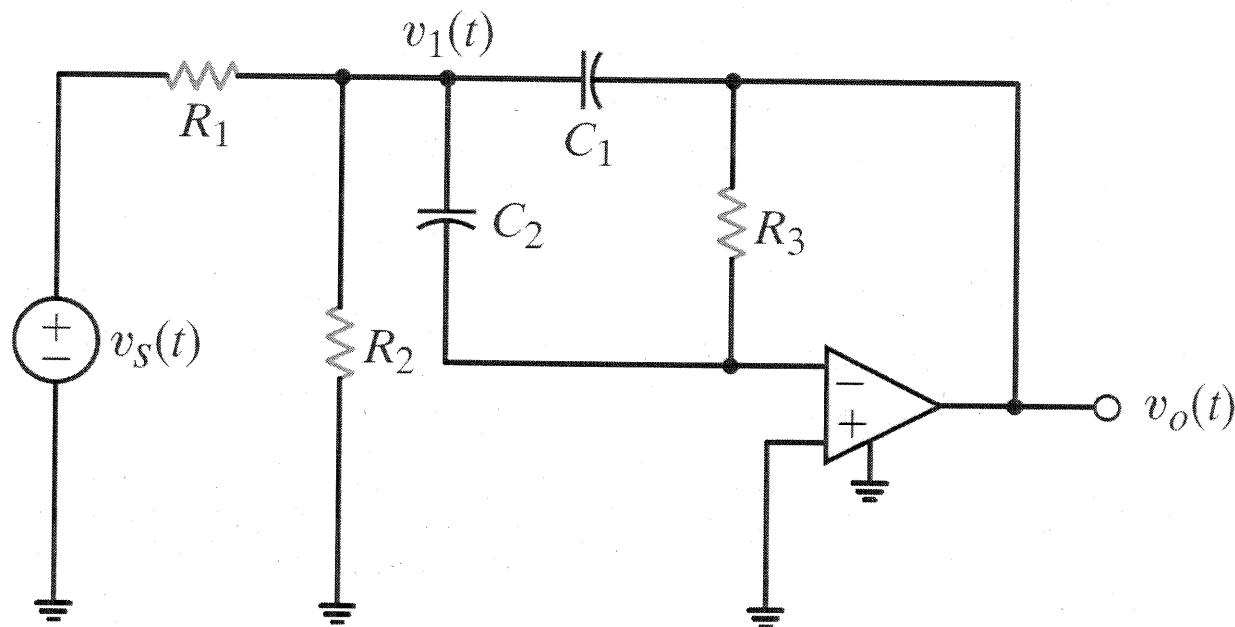


Figure P14.50

SOLUTION: Red raw

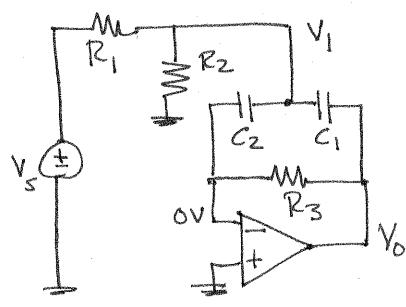

Nodal analysis

$$V_1 s C_2 + V_o / R_3 = 0 \Rightarrow V_1 = -V_o / s C_2 R_3$$

$$\frac{V_s - V_1}{R_1} = \frac{V_1}{R_2} + V_1 s C_2 + (V_1 - V_o) s C_1$$

$$\leftarrow \frac{V_s}{R_1} = -V_o \left[ s C_1 + \frac{1}{s C_2 R_3} \left( \frac{1}{R_1} + \frac{1}{R_2} + s(C_2 + C_1) \right) \right]$$

$$\frac{V_o}{V_s} = \frac{-1/R_1}{sC_1 + \frac{C_1 + C_2}{C_2 R_3} + \frac{R_1 + R_2}{s R_1 R_2 R_3 C_2}}$$

$$\boxed{\frac{V_o}{V_s} = \frac{-(1/C_1 R_1)s}{s^2 + s \left( \frac{C_1 + C_2}{C_1 C_2 R_3} \right) + \frac{R_1 + R_2}{C_1 C_2 R_1 R_2 R_3}}}$$

- 14.51 Determine the transfer function for the network shown in Fig. P14.51. If a step function is applied to the network, what type of damping will the network exhibit?


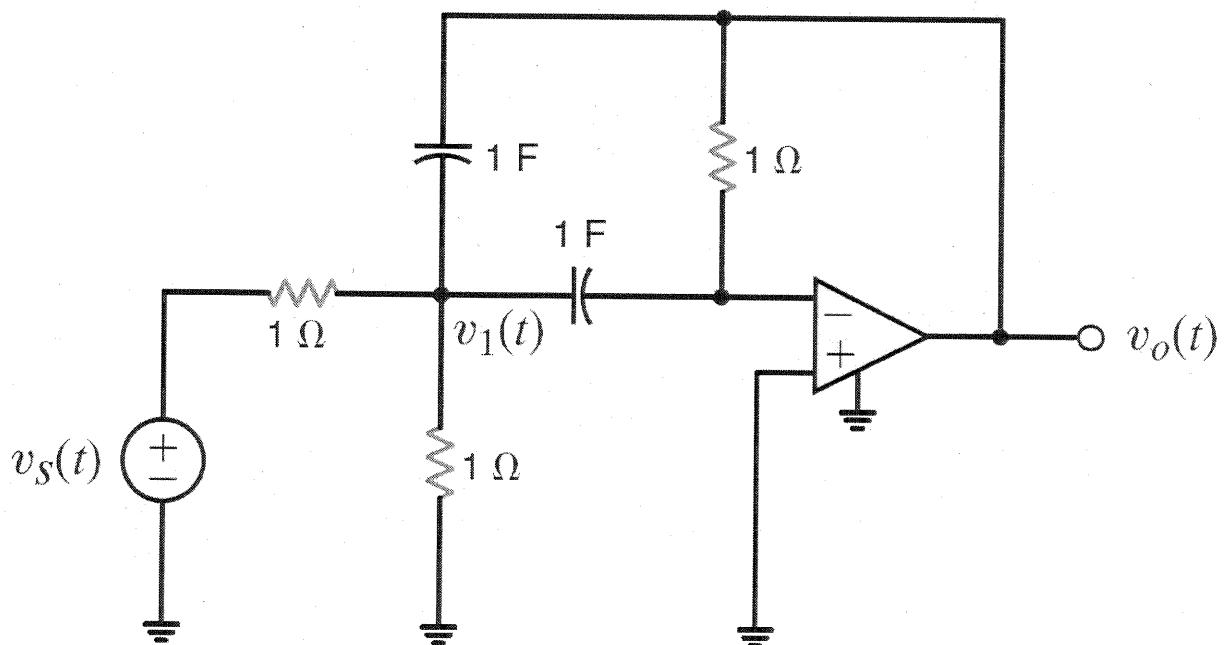


Figure P14.51

SOLUTION:

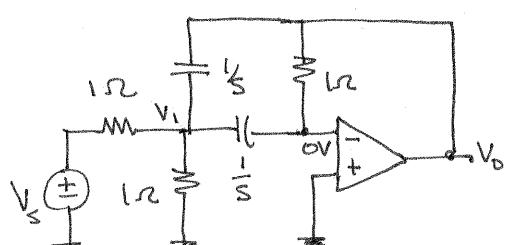

$$\frac{V_s - V_1}{1} = \frac{V_1}{\frac{1}{2s}} + V_1 s + (V_1 - V_o) s$$

$$\frac{V_o}{1} + V_1 s = 0 \Rightarrow V_1 = -V_o / s$$

$$V_s = V_1 (2s + 1) - s V_o = -V_o \left( \frac{s^2 + 2s + 2}{s} \right)$$

$$\boxed{\frac{V_o}{V_s} = \frac{-s}{s^2 + 2s + 2}}$$

$$\text{Roots at } s = -\frac{2 \pm \sqrt{4 - 8}}{2} = -1 \pm j1$$

complex conjugate poles.  
 Network is  
 UNDERDAMPED!

**14.52** The voltage response of the network to a unit step input is

$$V_o(s) = \frac{2(s + 1)}{s(s^2 + 10s + 25)}$$

Is the response overdamped?

**SOLUTION:**

3 poles at  $s = \begin{cases} 0 \\ -\frac{10}{2} \pm \sqrt{\frac{100-100}{4}} = -5 \end{cases}$   $\leftarrow$  [These poles are real & equal]

System is critically damped, not overdamped

- 14.53 The transfer function of the network is given by the expression

$$G(s) = \frac{100s}{s^2 + 13s + 40}$$

Determine the damping ratio, the undamped natural frequency, and the type of response that will be exhibited by the network.

---

SOLUTION:

Char. eq. is  $s^2 + 13s + 40 = s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$

$$\omega_n = \sqrt{40} \text{ rad/s}$$

$$2\zeta\omega_n = 13 \Rightarrow \zeta = \frac{13}{2\sqrt{40}} \Rightarrow \zeta = 1.03$$

$\zeta > 1$  (barely), so system is over damped

**14.54** The transfer function of the network is given by the expression

$$G(s) = \frac{100s}{s^2 + 22s + 40}$$

Determine the damping ratio, the undamped natural frequency, and the type of response that will be exhibited by the network. **CS**

**SOLUTION:**

char. eq. is:  $s^2 + 22s + 40 = s^2 + 2\zeta\omega_0 s + \omega_0^2$

$$\omega_0 = \sqrt{40} \text{ r/s}$$

$$2\zeta\omega_0 = 22 \Rightarrow \zeta = 1.74$$

overdamped

14.55 The voltage response of a network to a unit step input is

$$V_o(s) = \frac{10}{s(s^2 + 8s + 18)}$$

Is the response critically damped?

SOLUTION:

$$V_I(s) = \frac{1}{s} \quad H(s) = \frac{V_o(s)}{V_I(s)} = \frac{10}{s^2 + 8s + 18}$$

Char. eq. is:  $s^2 + 8s + 18 = s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$

$$\omega_n = \sqrt{18} \text{ r/s}$$

$$\zeta = \frac{8}{2\sqrt{18}} = 0.94$$

Under damped!  
Not critically damped!

- 14.56 For the network in Fig. P14.56, choose the value of  $C$  for critical damping.


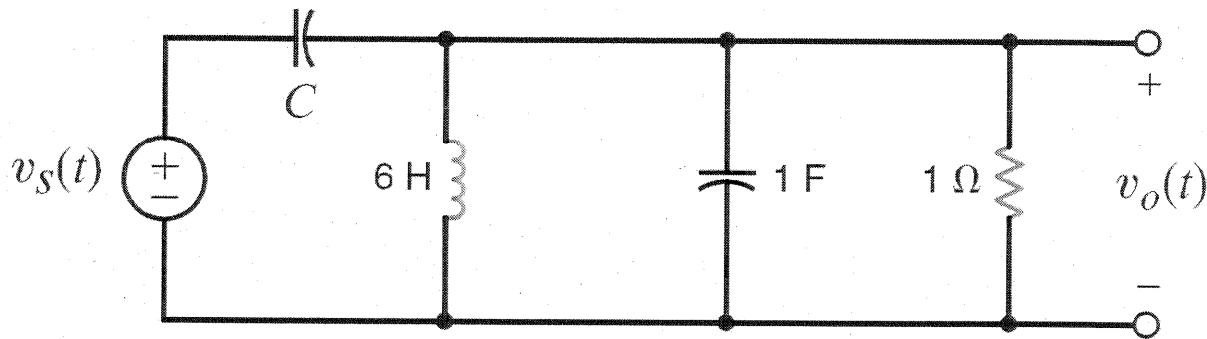


Figure P14.56

SOLUTION:

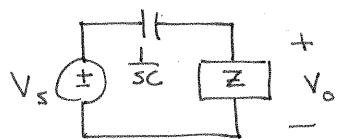

$$H(s) = \frac{V_o}{V_s} = \frac{Z}{Z + \frac{1}{sc}} \quad \frac{1}{Z} = \frac{1}{6s} + s + 1 = \frac{6s^2 + 6s + 1}{6s}$$

$$H(s) = \frac{C6s^2}{6Cs^2 + 6s^2 + 6s + 1} = \frac{6Cs^2}{6(C+1)s^2 + 6s + 1}$$

$$H(s) = \frac{\left(\frac{C}{C+1}\right)s}{s^2 + \frac{s}{C+1} + \frac{1}{6(C+1)}}$$

$$\omega_0 = \frac{1}{\sqrt{6(C+1)}} \quad \zeta = 1$$

$$2\zeta\omega_0 = \frac{1}{C+1} = \frac{Z}{\sqrt{6(C+1)}}$$

$$\sqrt{C+1} = \sqrt{6}/2 \Rightarrow \boxed{C=0.5F}$$

- 14.57 For the filter in Fig. P14.57, choose the values of  $C_1$  and  $C_2$  to place poles at  $s = -2$  and  $s = -5$  rad/s.


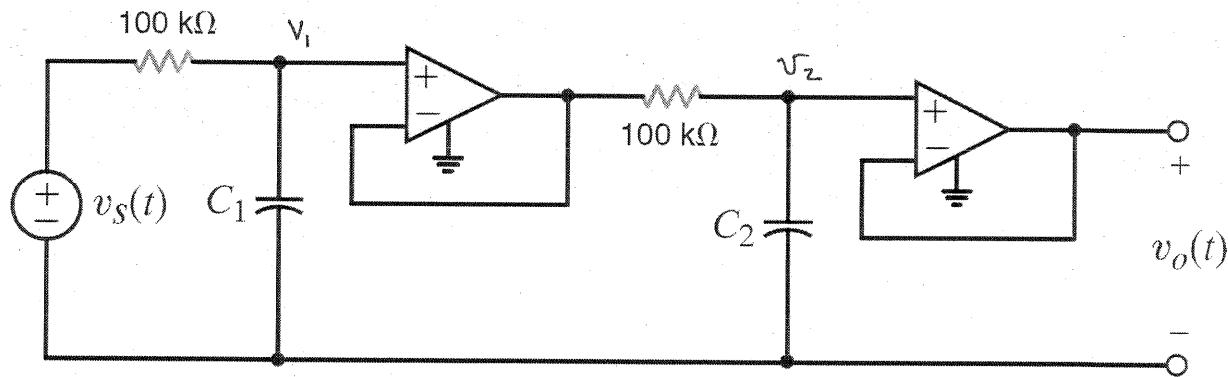


Figure P14.57

SOLUTION:

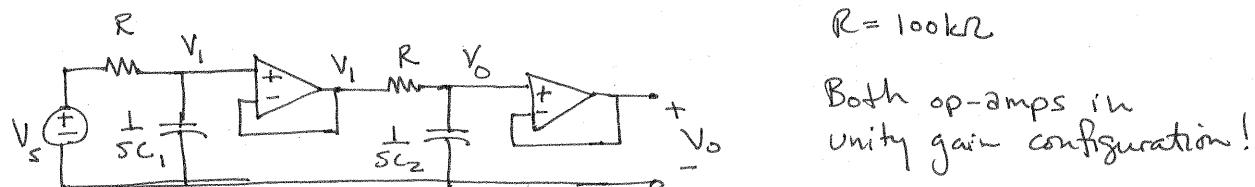

$$\frac{V_1}{V_s} = \frac{\frac{1}{SC_1}}{R + \frac{1}{SC_1}} = \frac{1}{SC_1 R + 1} = \frac{1/RC_1}{s + 1/RC_1}$$

$$\frac{V_0}{V_1} = \frac{1/RC_2}{s + 1/RC_2}$$

$$\frac{V_0}{V_s} = \frac{\frac{1}{RC_2}}{(s + \frac{1}{RC_1})(s + \frac{1}{RC_2})}$$

$$\frac{1}{RC_1} = 2 \quad \text{and} \quad \frac{1}{RC_2} = 5$$

$$\boxed{C_1 = 5 \mu F}$$

$$C_2 = 2 \mu F$$

**14.58** Find the steady-state response  $v_o(t)$  for the network in Fig. P14.58.



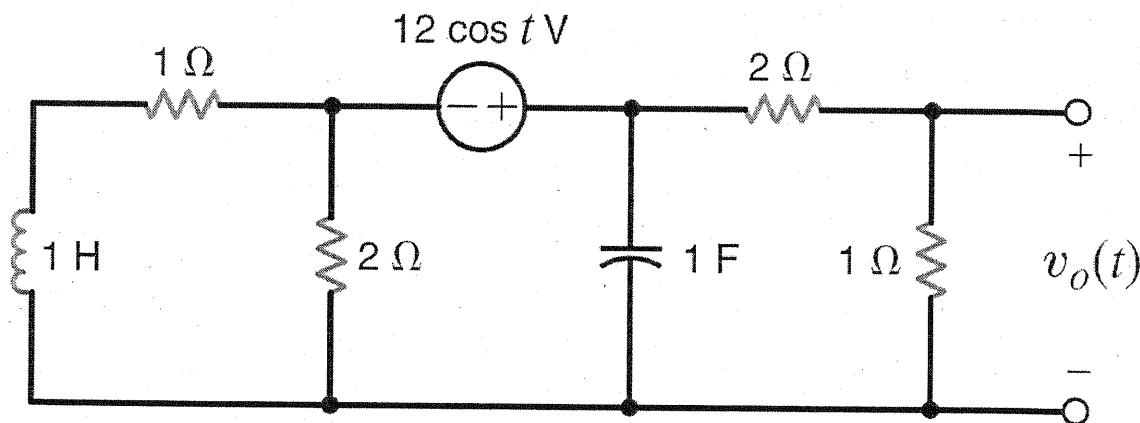


Figure P14.58

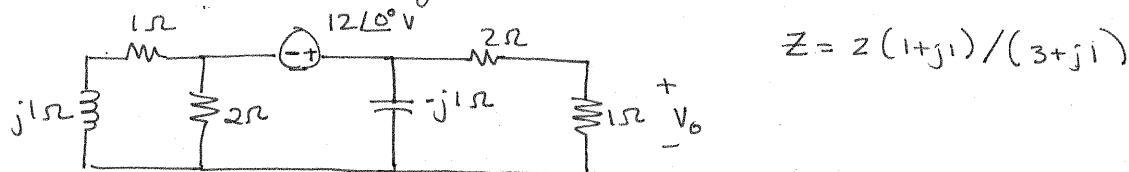
**SOLUTION:** In steady state  $s \rightarrow j\omega$  and  $\cos \omega t \Rightarrow$  phasor.


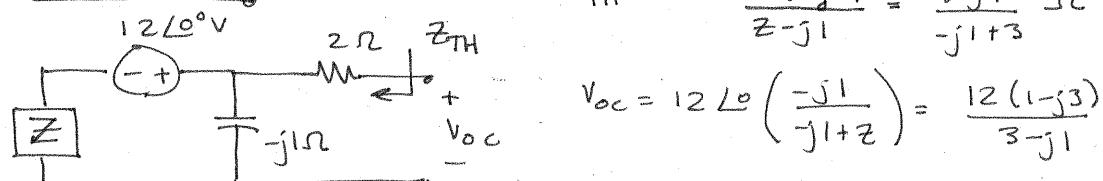
$$\text{Thevenin } \xrightarrow{\text{eg}} Z_{TH} = Z + \frac{Z(-j1)}{Z-j1} = \frac{8-j4}{-j1+3} \Omega$$


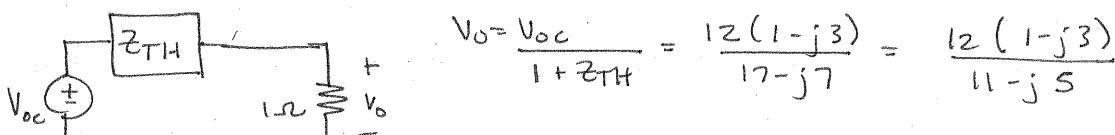
$$V_{oc} = 12 L^0 \left( \frac{-j1}{-j1+Z} \right) = \frac{12(1-j3)}{3-j1}$$




$$V_o = \frac{V_{oc}}{1 + Z_{TH}} = \frac{12(1-j3)}{17-j7} = \frac{12(1-j3)}{11-j5}$$

$$V_o = 3.13 \angle -47.2^\circ V$$


$$V_o(t) = 3.13 \cos(t - 47.2^\circ) V$$

- 14.59 Find the steady-state response  $v_o(t)$  for the circuit shown in Fig. P14.59. **PSV**

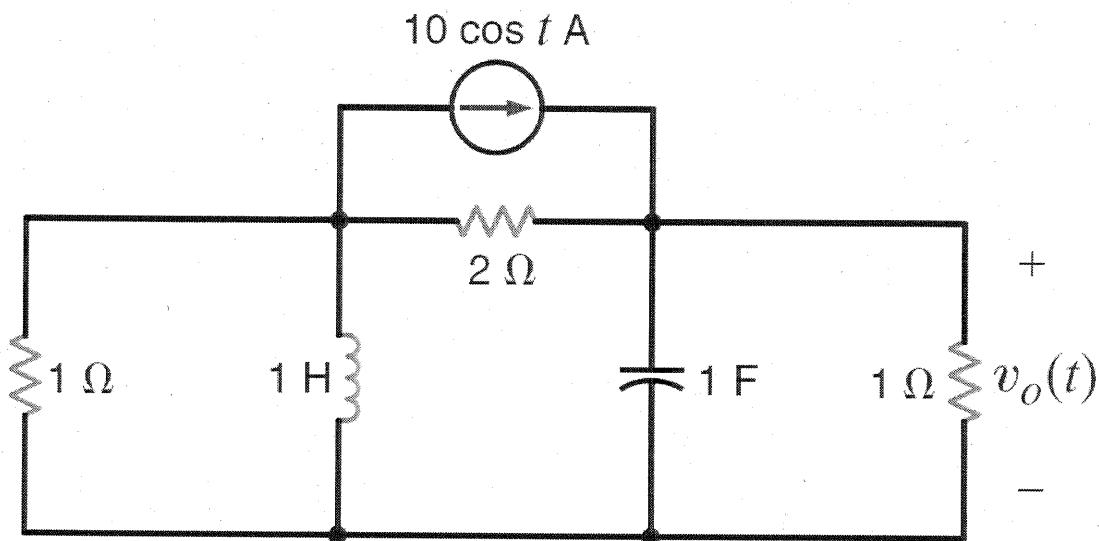

**Figure P14.59**

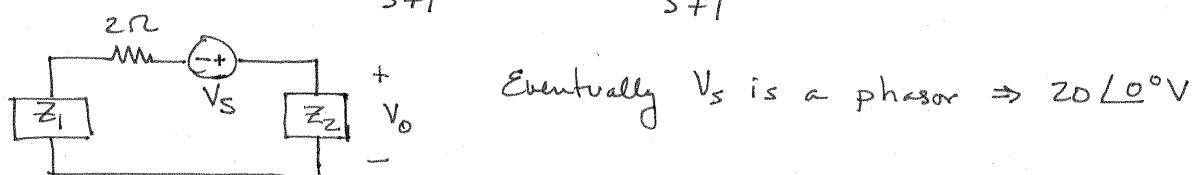SOLUTION: Let  $Z_1 = \frac{s}{s+1}$  &  $Z_2 = \frac{1}{s+1}$



Eventually  $V_s$  is a phasor  $\Rightarrow 20 \angle 0^\circ V$

$$V_o = V_s \left( \frac{Z_2}{Z_1 + Z_2 + Z} \right) = V_s \left( \frac{1}{s+1 + 2s+2} \right) = V_s \left( \frac{1/3}{s+1} \right)$$

In steady state,  $s \rightarrow j\omega$

$$V_o = 20 \angle 0^\circ \left[ \frac{1/3}{1+j\omega} \right] \quad V_o = 4.17 \angle -45^\circ V$$

$$v_o(t) = 4.71 \cos(t - 45^\circ) V$$

**14.60** Determine the steady-state response  $i_o(t)$  for the network in Fig. P14.60.


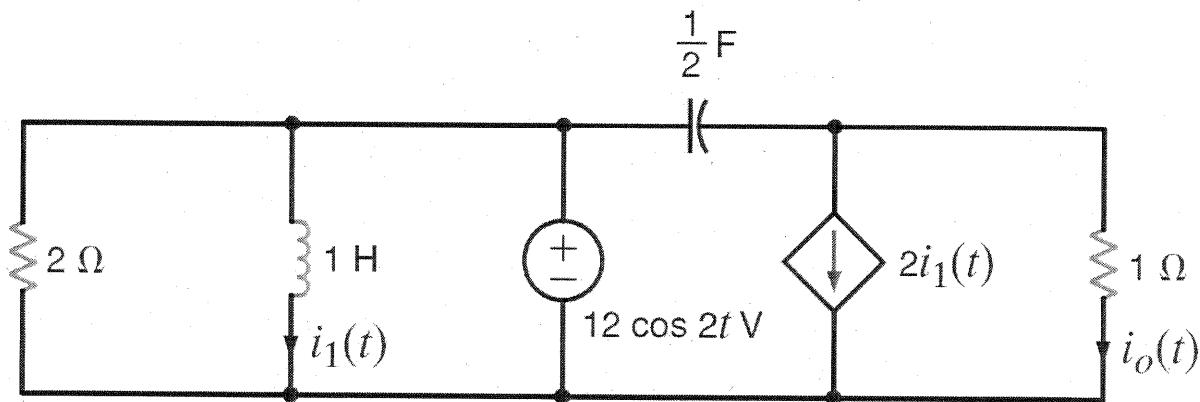


Figure P14.60

**SOLUTION:** Use KCL,

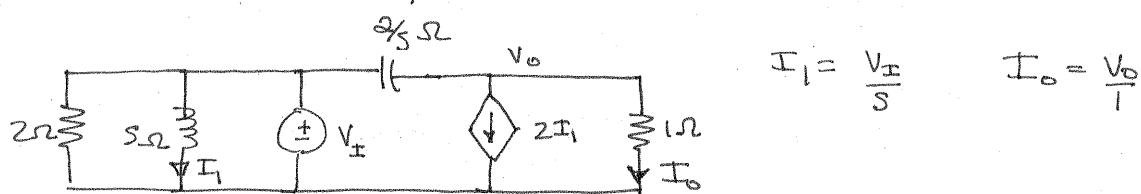

$$\frac{V_o - V_I}{2/s} + 2I_1 + \frac{V_o}{1} = 0 \Rightarrow V_o \left( \frac{s}{2} + 1 \right) = V_I \left( \frac{s}{2} - \frac{2}{s} \right)$$

$$\frac{V_o}{V_I} = \frac{s-2}{s} \Rightarrow I_o = \frac{V_I (s-2)}{s}$$

At steady-state,  $V_I = 12 \angle 0^\circ V$  &  $s = j\omega$

$$I_o = 12\sqrt{2} \angle 45^\circ A$$

$$i_o(t) = 12\sqrt{2} \cos(2t + 45^\circ) A$$

- 14.61 Find the steady-state response  $i_o(t)$  for the network shown in Fig. P14.61. **CS**


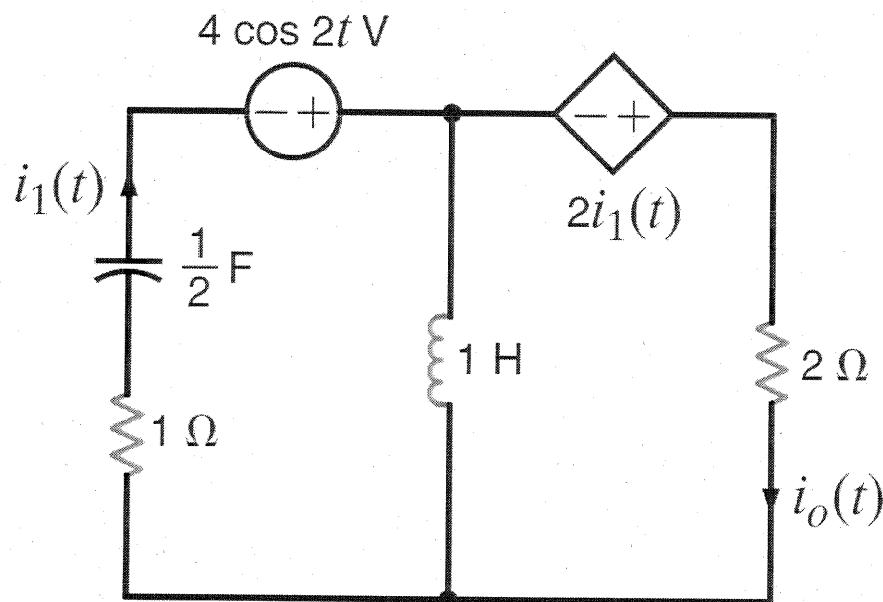


Figure P14.61

SOLUTION:

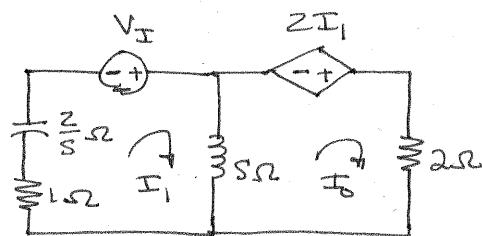

$$\begin{aligned} V_I &= I_1 (s+1+\frac{2}{s}) - sI_o \\ &= I_1 \left( \frac{s^2+s+2}{s} \right) - sI_o \end{aligned}$$

and,

$$2I_1 = -sI_1 + (s+2)I_o$$

or,

$$0 = -I_1(s+2) + I_o(s+2)$$

$$V_I = I_o \left[ \frac{s^2+s+2 - s^2}{s} \right] \quad \Leftarrow \text{yields } I_1 = I_o$$

$$I_o = \frac{V_I(s)}{s+2}$$

In steady state,  $V_I = 4 \angle 0^\circ V \quad s \rightarrow j2$

$$I_o = \frac{4 \angle 0^\circ (j2)}{2+j2} = 2\sqrt{2} \angle 45^\circ A$$

$$i_o(t) = 2\sqrt{2} \cos(2t + 45^\circ) A$$

14.62 Find the steady-state response  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.62.


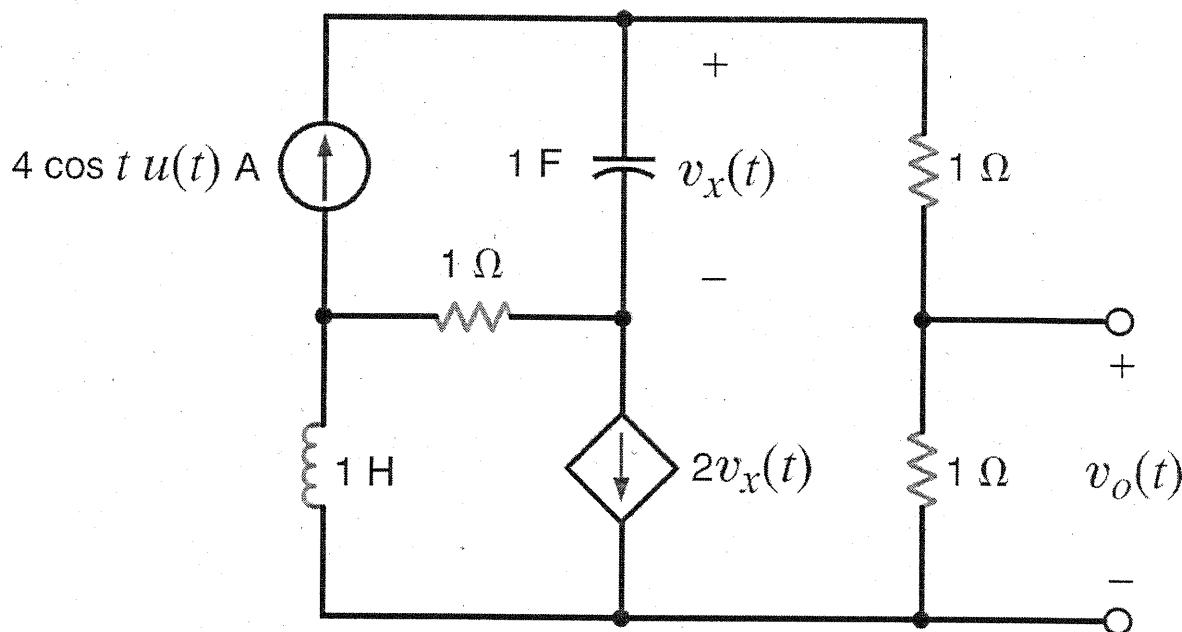


Figure P14.62

SOLUTION:

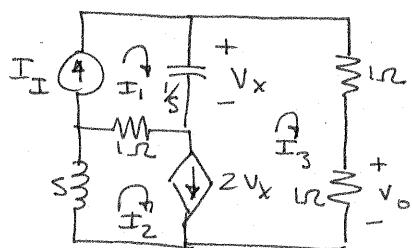

$$I_1 = I_2 \quad I_2 - I_3 = 2V_x = Z (I_1 - I_3) / s$$

$$\text{yields} \quad I_2 = \frac{2I_1}{s} + I_3 \left(1 - \frac{Z}{s}\right)$$

and

$$I_2(s+1) + I_3(z + 1/s) - I_1(1 + 1/s) = 0$$

$$I_1 \left[ \frac{2}{s}(s+1) - \frac{s+1}{s} \right] + I_3 \left[ \frac{s-2}{s}(s+1) + \frac{2s+1}{s} \right] = 0 \quad V_o = (1) I_3$$

$$I_1 [2s+2 - s-1] + V_o [s^2 - s - 2 + 2s+1] = 0$$

$$V_o = -I_1 (s+1) / (s^2 + s - 1)$$

In steady state,  $I_1 = 4 \angle 0^\circ A$  &  $s=j1 \Rightarrow V_o = 2.53 \angle 71.6^\circ V$

$$V_o(t) = 2.53 \cos(t + 71.6^\circ) V$$

- 14.63 Find the steady-state response  $v_o(t)$ , for  $t > 0$ , in the network in Fig. P14.63.


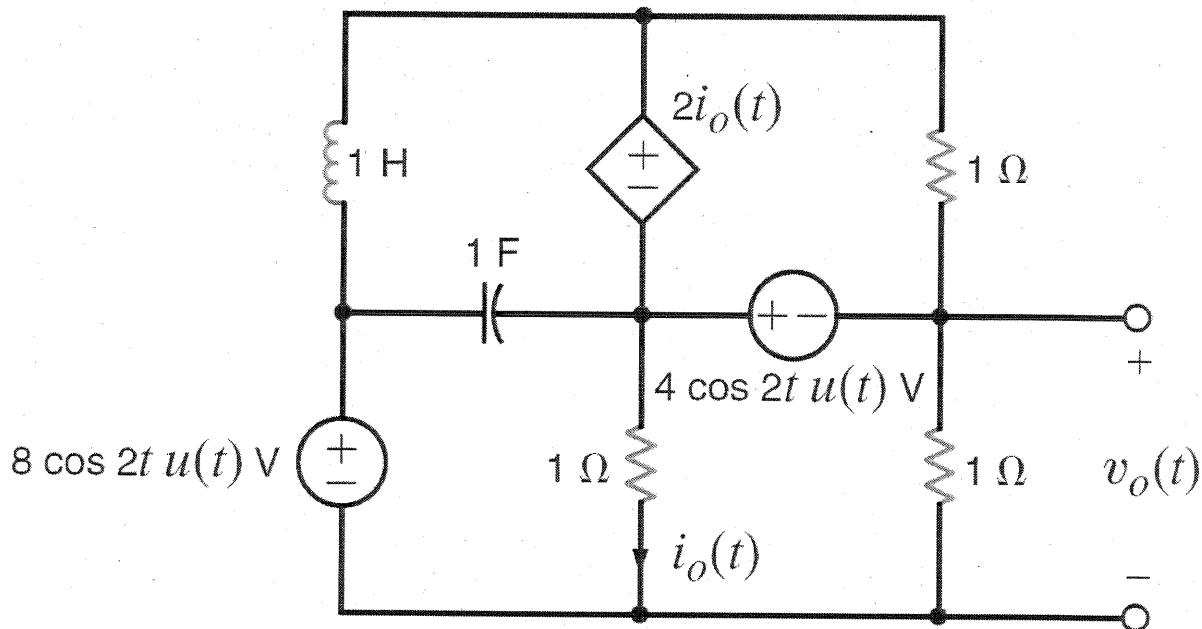


Figure P14.63

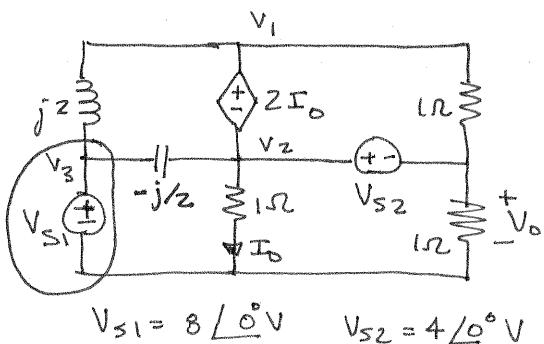SOLUTION: Go straight to freq domain.  $s \rightarrow j^2$  & sources  $\Rightarrow$  phasors.



$$V_3 = 8 \angle 0^\circ V \quad V_2 - V_o = 4 \angle 0^\circ V$$

$$V_1 - V_2 = 2V_2 = Z(V_2/V_1) \Rightarrow V_1 = 3V_2$$

At super node:

$$\frac{V_1 - V_3}{j^2} + \frac{V_2 - V_3}{-j/2} + \frac{V_2 + V_o}{1} = 0$$

$$\text{yields } V_o = 5.22 \angle 97.8^\circ V$$

$v_o(t) = 5.22 \cos(2t + 97.8^\circ) V$

**14FE-1** A single loop, second-order circuit is described by the following differential equation.

$$2\frac{dv^2(t)}{dt^2} + 4\frac{dv(t)}{dt} + 4v(t) = 12u(t) \quad t > 0$$

Which is the correct form of the total (natural plus forced) response? **CS**

- (a)  $v(t) = K_1 + K_2 e^{-t}$
- (b)  $v(t) = K_1 \cos t + K_2 \sin t$
- (c)  $v(t) = K_1 + K_2 t e^{-t}$
- (d)  $v(t) = K_1 + K_2 e^{-t} \cos t + K_3 e^{-t} \sin t$

**SOLUTION:**

Natural response has char eq:  $s^2 + 2s + 2 = 0$

roots are at  $s = -1 \pm j1 \Rightarrow$  natural response is sinusoidal!

Forced response is constant =  $K_1$

Answer is (d)

**14FE-2** If all initial conditions are zero in the network in Fig. 14PFE-2, find the transfer function  $V_o(s)/V_s(s)$ , and determine the type of damping exhibited by the network.

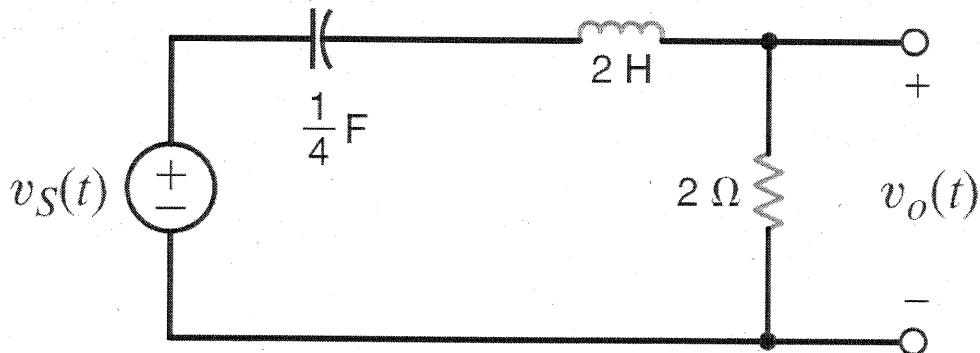


Figure 14PFE-2

SOLUTION:

$$\frac{V_o(s)}{V_s(s)} = \frac{2}{2 + 2s + 4/s} = \frac{2s}{2s^2 + 2s + 4} = \frac{s}{s^2 + s + 2}$$

$$\boxed{\frac{V_o}{V_s} = \frac{s}{s^2 + s + 2}}$$

Poles at  $s = -\frac{1}{2} \pm j \frac{\sqrt{7}}{2}$

since poles are complex,  
the circuit is underdamped

**14FE-3** The initial conditions in the circuit in Fig. 14PFE-3 are zero. Find the transfer function  $\mathbf{I}_o(s)/\mathbf{I}_s(s)$ , and determine the type of damping exhibited by the circuit.


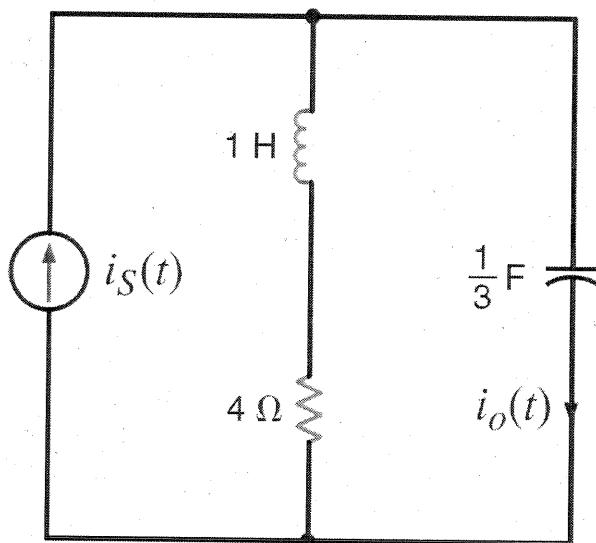


Figure 14PFE-3

**SOLUTION:**

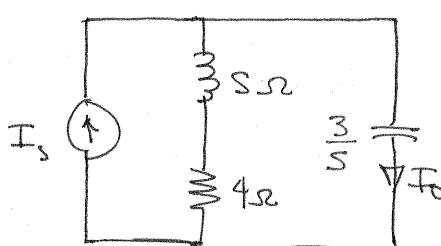

$$\frac{\mathbf{I}_o}{\mathbf{I}_s} = \frac{\frac{3}{s}}{\frac{3}{s} + 4 + s} = \frac{3}{s^2 + 4s + 3}$$

$$\boxed{\frac{\mathbf{I}_o}{\mathbf{I}_s} = \frac{3}{s^2 + 4s + 3}}$$

Char equation:  $s^2 + 4s + 3$

Poles at  $s = -2 \pm 1 = \left\{ \begin{matrix} -1 \\ -3 \end{matrix} \right.$

Poles are real and unequal,  
network is overdamped