
 


Chapter Sixteen


Two-Port Networks

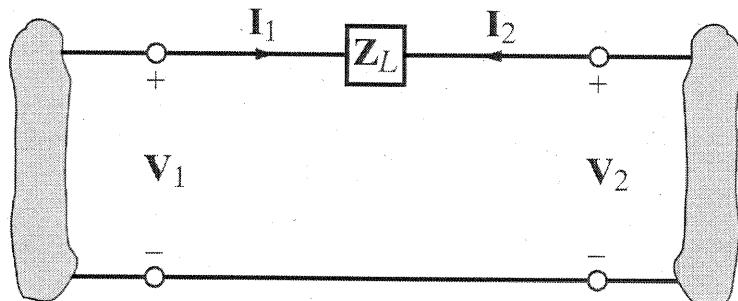

- 16.1 Given the two networks in Fig. P16.1, find the Y parameters for the circuit in (a) and the Z parameters for the circuit in (b). [CS]



(a)

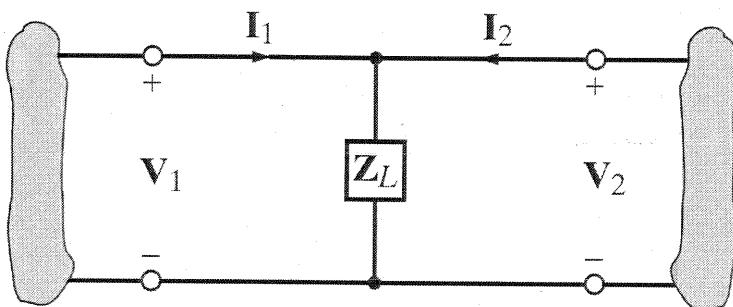

(b)

Figure P16.1

SOLUTION:

$$a) \quad Y_{11} = I_1 / V_1 \Big|_{V_2=0} = \frac{1}{Z_L} \quad Y_{21} = -\frac{1}{Z_L} \quad Y_{12} = -\frac{1}{Z_L} \quad Y_{22} = \frac{1}{Z_L}$$

$$b) \quad Z_{11} = V_1 / I_1 \Big|_{I_2=0} = Z_L \quad Z_{21} = V_2 / I_1 \Big|_{I_2=0} = Z_L$$

$$Z_{12} = Z_L \quad Z_{22} = Z_L$$

16.2 Find the Y parameters for the two-port network shown in Fig. P16.2.


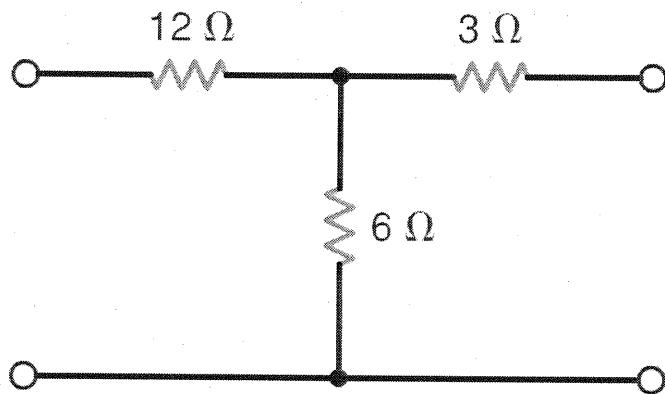


Figure P16.2

SOLUTION:

$$Y_{11} = \left. I_1 / V_1 \right|_{V_2=0} = \frac{1}{12 + (6//3)} = \frac{1}{14} \text{ S}$$

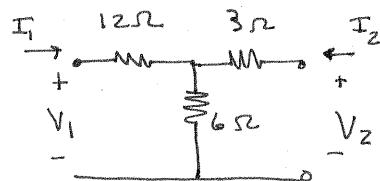

$$Y_{22} = \left. I_2 / V_2 \right|_{V_1=0} = \frac{1}{3 + (12//6)} = \frac{1}{7} \text{ S}$$

$$Y_{12} = \left. I_1 / V_2 \right|_{V_1=0} = \left[\frac{12//6}{(12//6) + 3} \right] \left(-\frac{1}{12} \right) = -\frac{1}{21} \text{ S}$$

$$Y_{21} = \left. I_2 / V_1 \right|_{V_2=0} = \left[\frac{3//6}{(3//6) + 12} \right] \left(-\frac{1}{3} \right) = -\frac{1}{21} \text{ S}$$

- 16.3 Find the Y parameters for the two-port network shown in Fig. P16.3. **PSV**

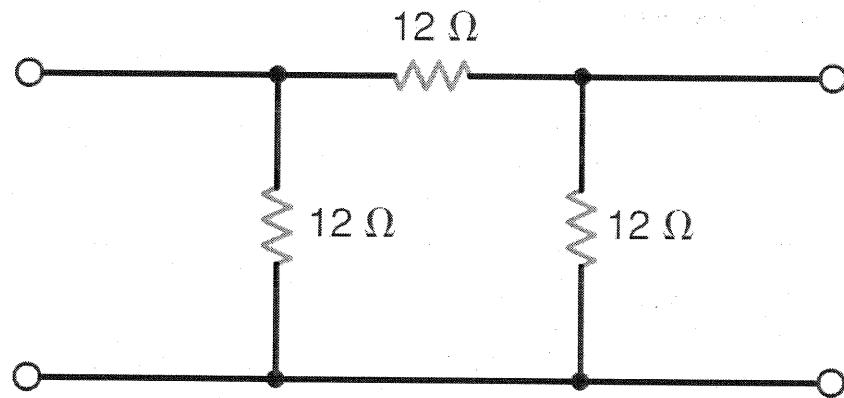


Figure P16.3


SOLUTION:

$$Y_{11} = I_1 / V_1 |_{V_2=0} = \frac{1}{R_1 // R_2} = \frac{1}{6} S$$

$$Y_{22} = \frac{1}{R_2 // R_3} = \frac{1}{6} S$$

$$Y_{21} = I_2 / V_1 |_{V_2=0} = -\frac{1}{R_2} = -\frac{1}{12} S$$

$$Y_{12} = I_1 / V_2 |_{V_1=0} = -\frac{1}{R_1} = -\frac{1}{12} S$$

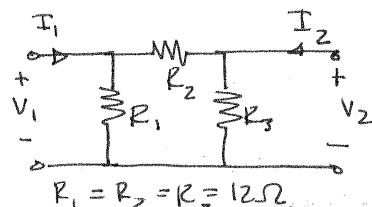

16.4 Determine the Y parameters for the network shown in Fig. P16.4.

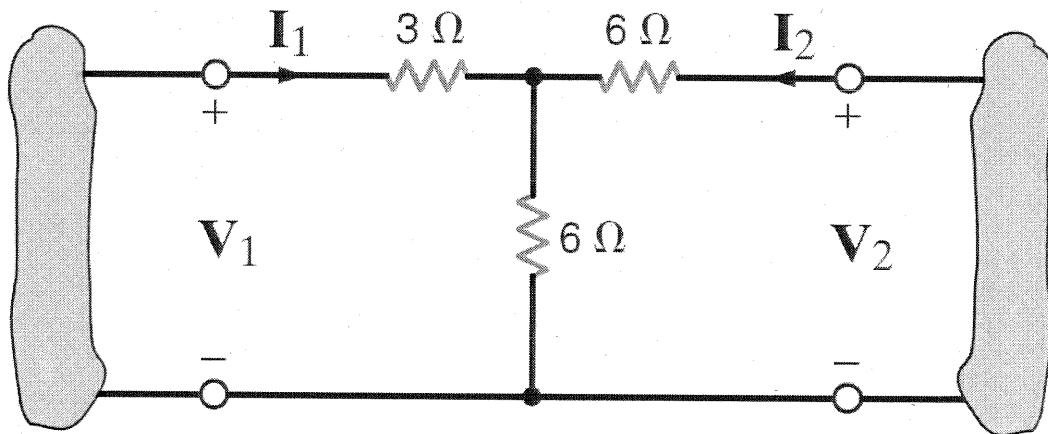


Figure P16.4

SOLUTION:

$$Y_{11} = I_1 / V_1 \mid V_2 = 0 = \frac{1}{3 + (6//6)} = \frac{1}{6} S$$

$$Y_{22} = I_2 / V_2 \mid V_1 = 0 = \frac{1}{6 + (6//3)} = \frac{1}{8} S$$

$$Y_{21} = I_2 / V_1 \mid V_2 = 0 = \frac{6//6}{(6//6) + 3} \left(-\frac{1}{6} \right) = -\frac{1}{12} S$$

$$Y_{12} = I_1 / V_2 \mid V_1 = 0 = \frac{3//6}{(3//6) + 6} \left(-\frac{1}{3} \right) = -\frac{1}{12} S$$

16.5 Find the Z parameters for the two-port network in Fig. P16.5.

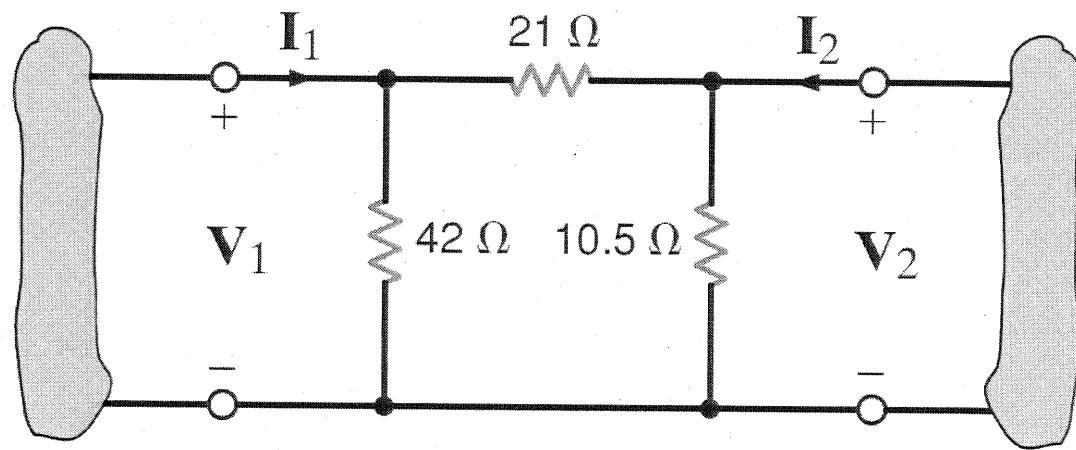


Figure P16.5

SOLUTION:

$$Z_{11} = \left. V_1 / I_1 \right|_{I_2=0} = 42 \parallel (21 + 10.5) = 18 \Omega$$

$$Z_{22} = \left. V_2 / I_2 \right|_{I_1=0} = 10.5 \parallel (21 + 42) = 9 \Omega$$

$$Z_{21} = \left. V_2 / I_1 \right|_{I_2=0} = \frac{42}{42 + 21 + 10.5} (10.5) = 6 \Omega$$

$$Z_{12} = \left. V_1 / I_2 \right|_{I_1=0} = \frac{10.5}{10.5 + 21 + 42} (42) = 6 \Omega$$

16.6 Determine the admittance parameters for the network shown in Fig. P16.6.

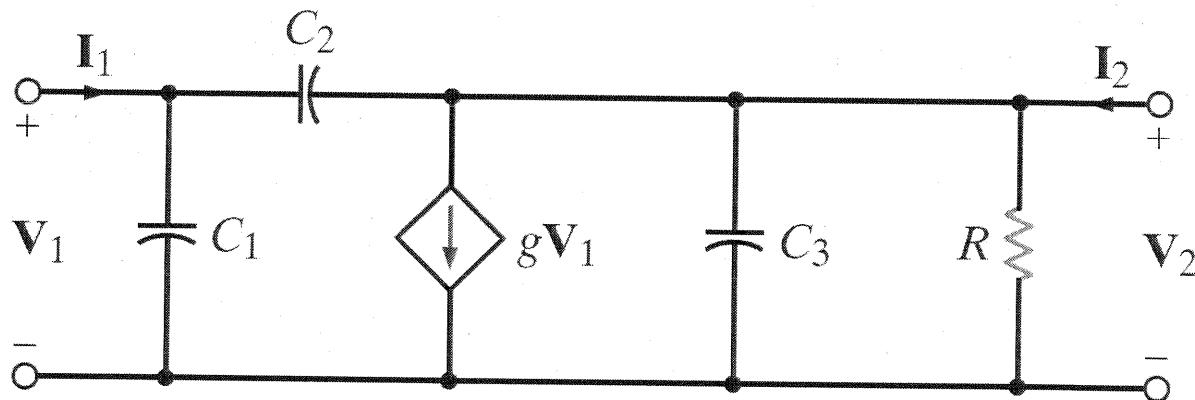


Figure P16.6

SOLUTION:


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = j\omega(C_1 + C_2)$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R} + j\omega(C_2 + C_3)$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = g - j\omega C_2$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -j\omega C_2$$

For Y_{21}

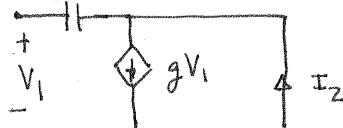

$$I_2 + V_1(j\omega C_2) = gV_1$$

$$I_2/V_1 = g - j\omega C_2$$

16.7 Find the Y parameters for the two-port network in Fig. P16.7. **cs**

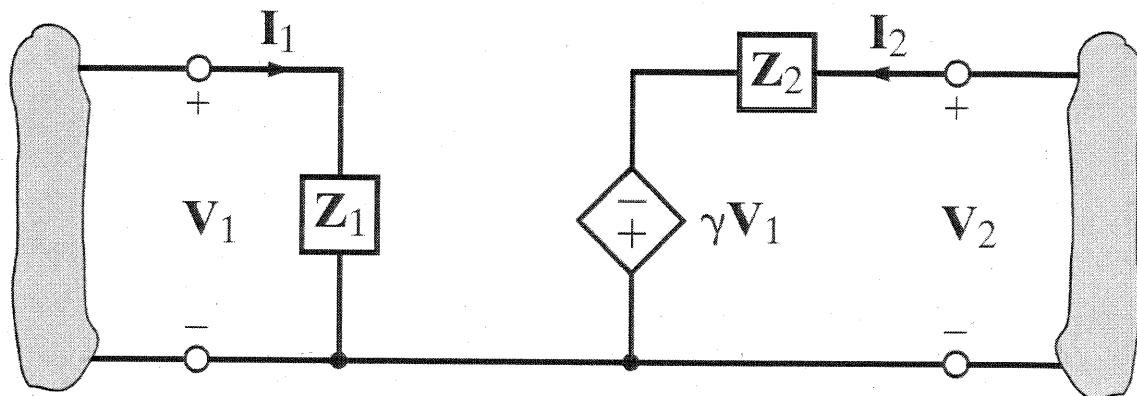



Figure P16.7

SOLUTION:

$$Y_{11} = \left. I_1 / V_1 \right|_{V_2=0} = \frac{1}{Z_1}$$

For Y_{21}

$$Y_{22} = \left. I_2 / V_2 \right|_{V_1=0} = \frac{1}{Z_2}$$

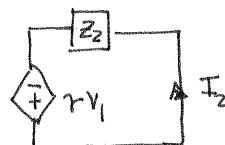

$$I_2 = \frac{\gamma V_1}{Z_2}$$

$$\frac{I_2}{V_1} = \frac{\gamma}{Z_2}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \gamma / Z_2$$



$$Y_{12} = \left. I_1 / V_2 \right|_{V_1=0} = 0$$

16.8 Find the Z parameters for the network in Fig. P16.7.

CS

SOLUTION:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = z_1$$

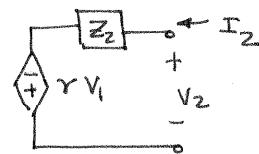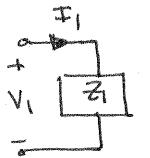

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = z_2$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = -\frac{\gamma V_1}{V_1/z_1} = -\gamma z_1$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 0$$

- 16.9 Find the Z parameters for the two-port network shown in Fig. P16.9 and determine the voltage gain of the entire circuit with a 4-k Ω load attached to the output.

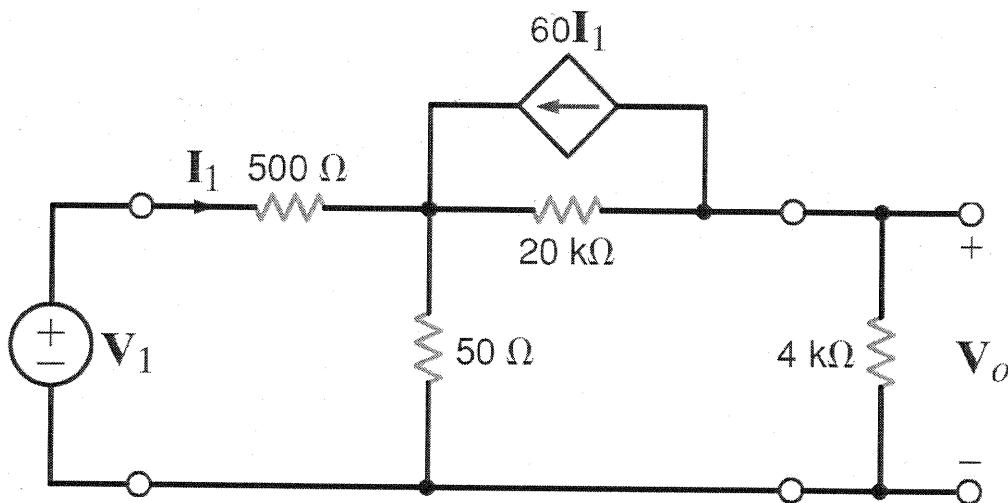
P S V

Figure P16.9

SOLUTION:

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 550 \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 20.05 \text{ k}\Omega$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = 50 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{50I_1 - 60I_1(20 \times 10^3)}{I_1} = -1.2 \text{ M}\Omega$$

w/ load


$$\left. \begin{array}{l} V_1 = 550I_1 + 50I_2 \\ V_2 = -1.2 \times 10^6 I_1 + 20.05 \times 10^3 I_2 \end{array} \right\}$$

$$V_2 = -4000I_2$$

Solving for I_2/V_1 yields

$$I_2/V_1 = 16.39 \times 10^{-3}$$

$V_o/V_1 = 65.5$

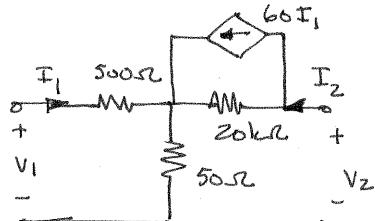

- 16.10 Find the Z parameters for the two-port network shown in Fig. P16.10.

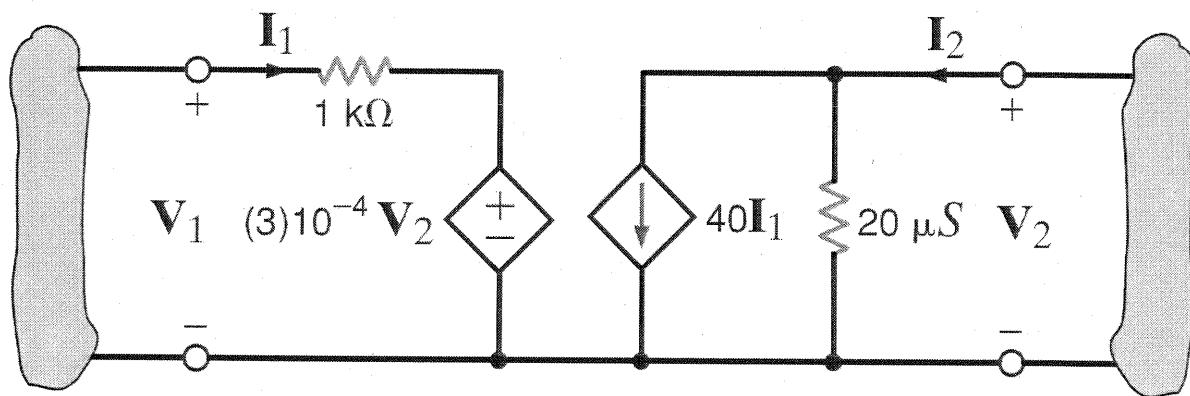


Figure P16.10

SOLUTION: Using h parameters,

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = 1 \text{ k}\Omega \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = 20 \mu\text{S}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = 3 \times 10^{-4} \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = 40$$

$$\Delta h = h_{11}h_{22} - h_{12}h_{21} = 8 \times 10^{-3}$$

$$Z_{11} = \frac{\Delta h}{h_{22}} = 400 \Omega \quad Z_{12} = \frac{h_{12}}{h_{22}} = 15 \Omega$$

$$Z_{21} = \frac{-h_{21}}{h_{22}} = -2 \times 10^6 = -2 \text{ M}\Omega \quad Z_{22} = \frac{1}{h_{22}} = 50 \text{ k}\Omega$$


- 16.11 Find the voltage gain of the two-port network in Fig. P16.10 if a $12\text{-k}\Omega$ load is connected to the output port. **CS**

SOLUTION:

$$\text{From P16.10, } z_{11} = 400\ \Omega \quad z_{12} = 15\ \Omega \quad z_{21} = -2\text{M}\ \Omega \quad z_{22} = 50\text{k}\Omega$$

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

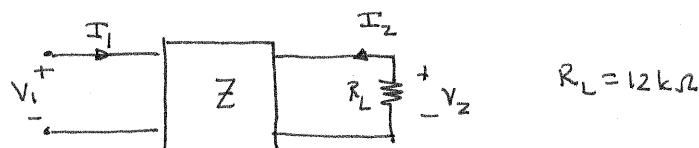

$$V_2 = -I_2 R_L$$

3 equations + unknowns. Eliminate I_1 & find V_2/V_1 .

$$\frac{V_2}{V_1} = -438$$

16.12 Find the input impedance of the network in Fig. P16.10.

SOLUTION:

$$Z_{IN} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_{II}$$

from P16.10, $Z_{II} = 400\Omega$

$$\boxed{Z_{IN} = 400\Omega}$$

16.13 Find the Z parameters of the two-port network in Fig. P16.13.

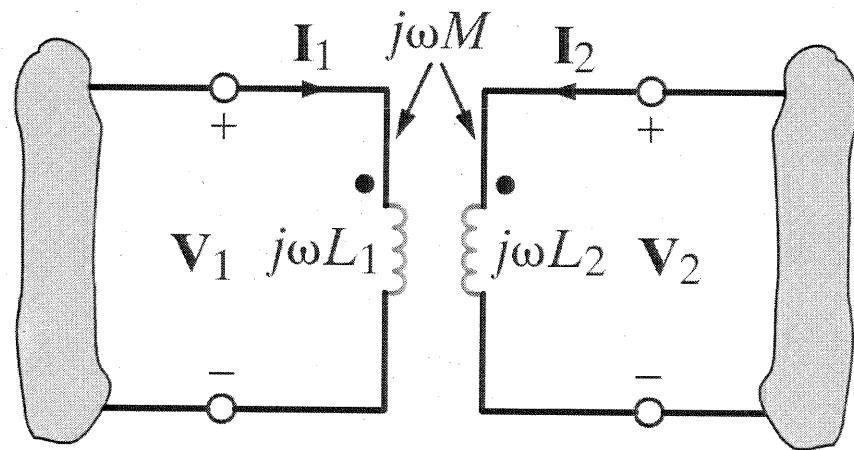


Figure P16.13

SOLUTION:

$$V_1 = I_1(j\omega L_1) + I_2(j\omega M) \quad V_2 = I_1(j\omega M) + I_2(j\omega L_2)$$

$$Z_{11} = j\omega L_1 \quad Z_{12} = j\omega M \quad Z_{21} = j\omega M \quad Z_{22} = j\omega L_2$$

16.14 Determine the Z parameters for the two-port network in Fig. P16.14.

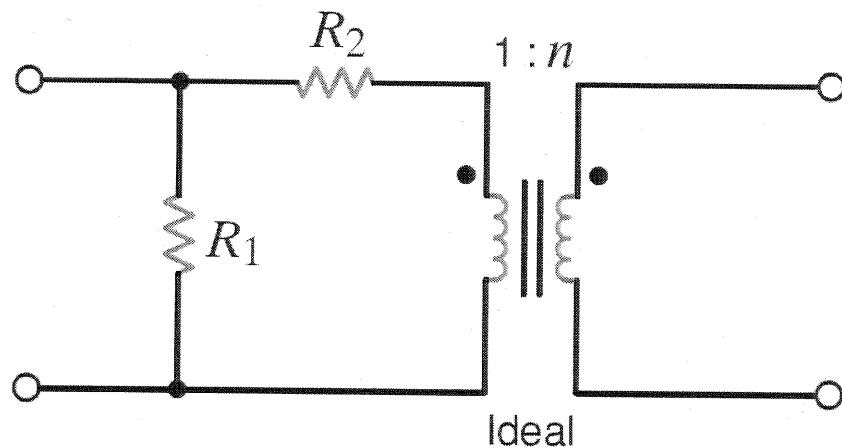



Figure P16.14

SOLUTION:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = R_1$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$
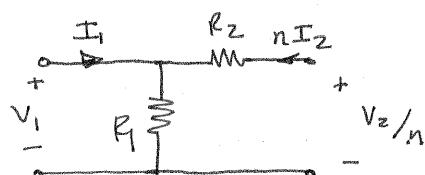
$$V_1 = n I_2 R_1 \Rightarrow Z_{12} = n R_1$$



$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Rightarrow \frac{V_2}{n} = I_1 R_1 \Rightarrow Z_{21} = n R_1$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \Rightarrow \frac{V_2}{n} = I_2 n (R_1 + R_2) \Rightarrow Z_{22} = n^2 (R_1 + R_2)$$


- 16.15 Draw the circuit diagram (with all passive elements in ohms) for a network that has the following Y parameters:

$$[Y] = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{6} \end{bmatrix}$$

SOLUTION:

$$I_1 = V_1 Y_{11} + V_2 Y_{12}$$

$$I_2 = V_1 Y_{21} + V_2 Y_{22}$$

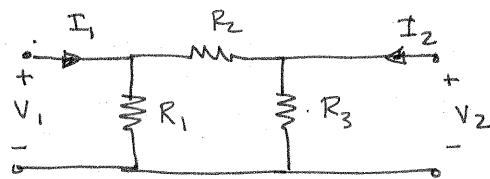

$$I_1 = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{R_2} \right)$$


$$I_2 = -\frac{1}{R_2} V_1 + V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$R_2 = 2\Omega$	$R_1 = 1\Omega$	$R_3 = 3\Omega$
-----------------	-----------------	-----------------

16.16 Draw the circuit diagram for a network that has the following Z parameters:

$$[Z] = \begin{bmatrix} 6 - j2 & 4 - j6 \\ 4 - j6 & 7 + j2 \end{bmatrix}$$

SOLUTION:

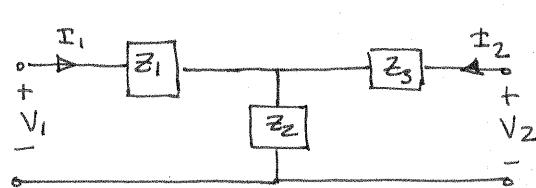

$$V_1 = I_1 (z_1 + z_2) + z_2 I_2$$

$$V_2 = +z_2 I_1 + I_2 (z_2 + z_3)$$

$$z_2 = 4 - j6 \Omega \quad z_1 = z + j4 \Omega$$

$$z_3 = 3 + j8 \Omega$$

- 16.17 Show that the network in Fig. P16.17 does not have a set of Y parameters unless the source has an internal impedance.


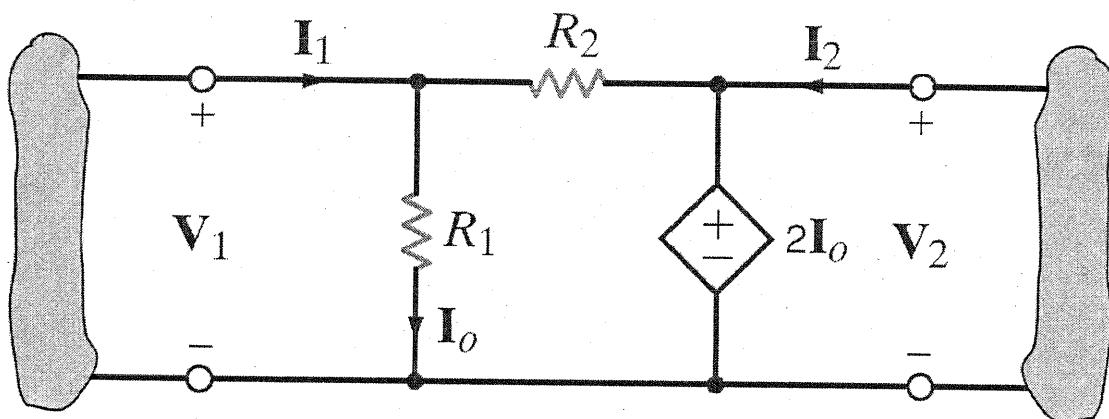


Figure P16.17

SOLUTION:

with $V_2 = 0$

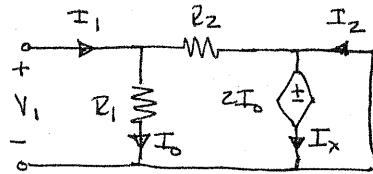

$$2I_0 = V_2 = 0 \Rightarrow I_0 = 0$$

$$V_1 = I_0 R_1 = 0 \Rightarrow V_1 = 0$$

$$I_1 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

No power supplied by input port or consumed by R_1 & R_2

thus, $I_x = 0$ & $I_2 = 0$.

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{0}{0} \text{ undefined!} \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{0}{0} \text{ undefined!}$$

with $V_1 = 0$: $I_0 = V_1 / R_1 = 0$ $V_2 = 2I_0 = 0$

$$I_1 = \frac{V_1}{R_1} + \frac{(V_1 - V_2)}{R_2} = 0$$

No power at input port or consumed by R_1 & $R_2 \Rightarrow I_2 = 0$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{0}{0} \text{ undefined!} \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{0}{0} \text{ undefined!}$$

16.18 Compute the hybrid parameters for the network in Fig. E16.1.


SOLUTION:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 // R_2 = 14\Omega$$

$$h_{21} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = -\frac{R_1}{R_1+R_2} = -\frac{2}{3}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_1}{R_1+R_2} = \frac{2}{3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_3 // (R_1+R_2)} = \frac{1}{9} S$$

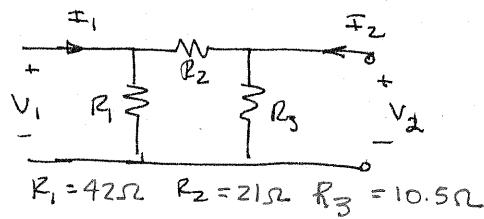

16.19 Find the hybrid parameters for the network in Fig. 16.3. **PSV**


SOLUTION:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$h_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{R_1}{R_1 + R_2} = -\frac{1}{3}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = +\frac{R_1}{R_1 + R_2} = \frac{1}{3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_3 // (R_1 + R_2)} = \frac{2}{3} \text{ S}$$

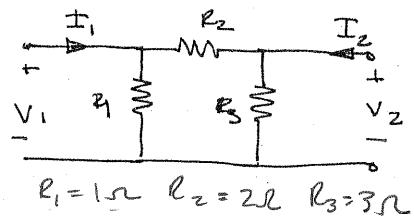

$$R_1 = 1 \Omega \quad R_2 = 2 \Omega \quad R_3 = 3 \Omega$$

- 16.20** Consider the network in Fig. P16.20. The two-port network is a hybrid model for a basic transistor. Determine the voltage gain of the entire network, V_2/V_S , if a source V_S with internal resistance R_1 is applied at the input to the two-port network and a load R_L is connected at the output port.

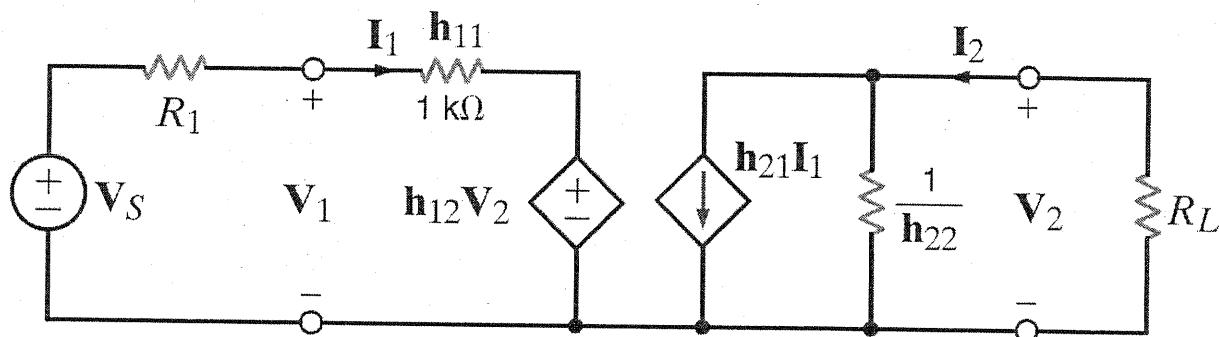


Figure P16.20

SOLUTION:

$$\left. \begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \right\} \quad \text{and,} \quad \left. \begin{aligned} V_2 &= -R_L I_2 \Rightarrow I_2 = -V_2/R_L \\ V_S &= I_1 R_1 + V_1 \Rightarrow V_1 = V_S - I_1 R_1 \end{aligned} \right\}$$

Now,

$$V_S = I_1 (h_{11} + R_1) + h_{12} V_2$$

$$0 = h_{21} I_1 + V_2 (h_{22} + \frac{1}{R_L})$$

$$V_2 = \frac{\begin{vmatrix} h_{11} + R_1 & V_S \\ h_{21} & 0 \end{vmatrix}}{\begin{vmatrix} h_{11} + R_1 & h_{12} \\ h_{21} & h_{22} + \frac{1}{R_L} \end{vmatrix}} \Rightarrow V_2 = \frac{-V_S h_{21}}{(h_{11} + R_1)(h_{22} + \frac{1}{R_L}) - h_{12} h_{21}}$$

$$\boxed{\frac{V_2}{V_S} = \frac{h_{21} R_L}{h_{12} h_{21} R_L - (1 + h_{22} R_L)(h_{11} + R_1)}}$$

16.21 Determine the hybrid parameters for the network shown in Fig. P16.21.


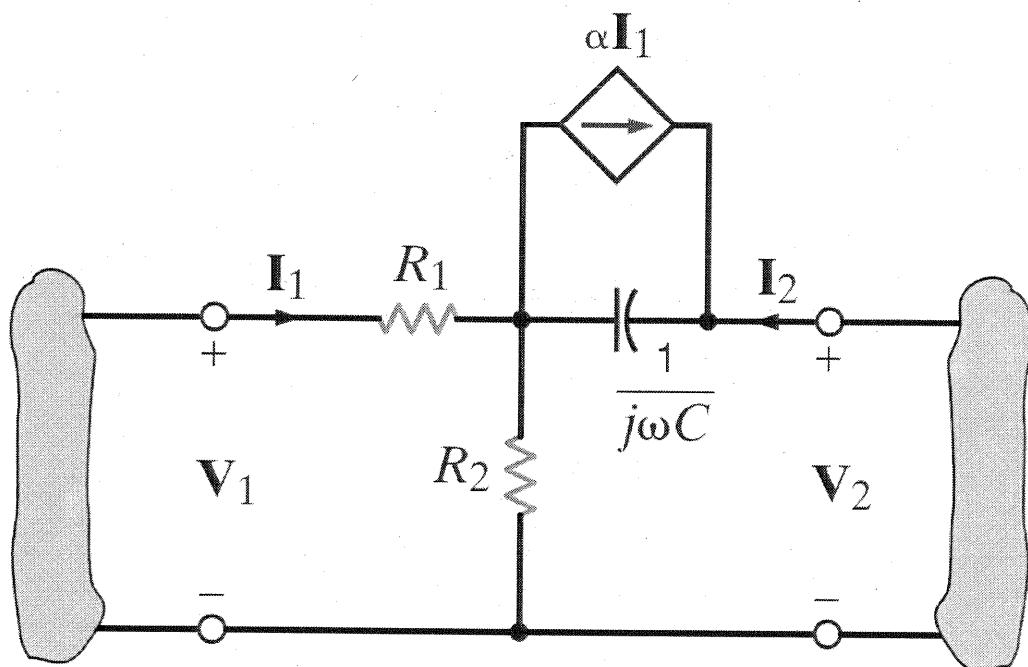


Figure P16.21

SOLUTION:

For $I_1 = 0$

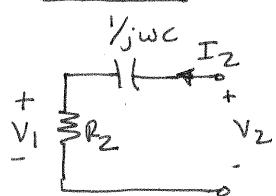

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{j\omega CR_2}{1 + j\omega CR_2}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{j\omega C}{1 + j\omega CR_2}$$

For $V_2 = 0$ Use loop analysis!

$$(I_2 + \alpha I_1) / j\omega C + (I_1 + I_2) R_2 = 0$$

$$\text{yields } I_1 (\alpha + j\omega CR_2) + I_2 (1 + j\omega CR_2) = 0$$

$$h_{21} = \frac{I_2}{I_1} = - \frac{\alpha + j\omega CR_2}{1 + j\omega CR_2} \quad \times$$

and,

$$V_1 = I_1 (R_1 + R_2) + I_2 R_2 = \pm_1 \left\{ R_1 + R_2 - R_2 \left(\frac{\alpha + j\omega CR_2}{1 + j\omega CR_2} \right) \right\}$$

$$V_1 = I_1 \left\{ \frac{R_1 + R_2 (1 - \alpha) + j\omega R_1 R_2 C}{1 + j\omega R_2 C} \right\}$$


$$h_{11} = \frac{V_1}{I_1} = \frac{R_1 + R_2 (1 - \alpha) + j\omega R_1 R_2 C}{1 + j\omega R_2 C} \quad \times$$

16.22 Find the ABCD parameters for the networks in Fig. P16.1. **cs**

SOLUTION:

$$a) A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = Z_L$$

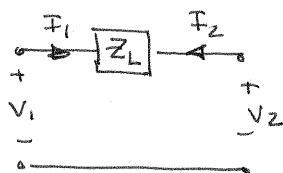


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0$$

$$D = \left. \frac{-I_1}{-I_2} \right|_{V_2=0} = 1$$

$$b) A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = 0$$

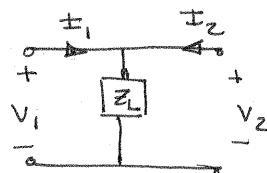

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{Z_L}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = 1$$

16.23 Find the transmission parameters for the network in Fig. P16.23.

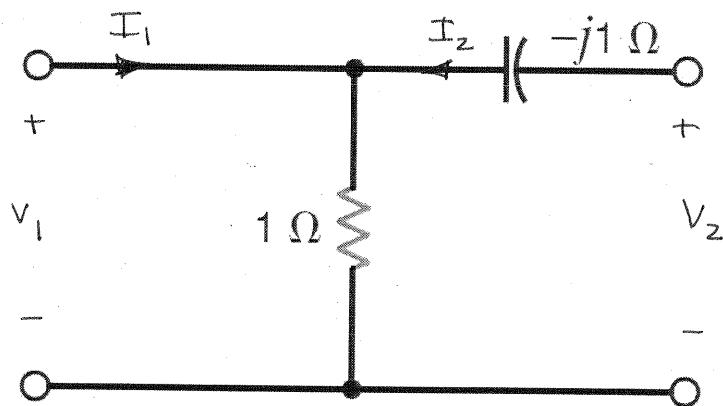


Figure P16.23

SOLUTION:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = -j1\Omega$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 1 \text{ s}$$


$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \Rightarrow -I_2 = I_1 \left(\frac{1}{1-j1} \right) \Rightarrow D = 1-j1$$

16.24 Find the transmission parameters for the network shown in Fig. P16.2.

PSV

SOLUTION:

$$A = \left. \frac{V_2}{V_1} \right|_{I_2=0} \Rightarrow V_2 = \frac{6}{12} V_1 \Rightarrow A = 3$$

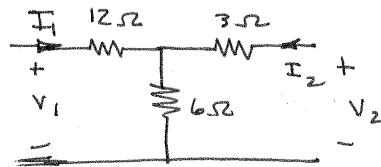

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \Rightarrow -I_2 = \frac{(3//6)V_1}{12+(3//6)} \left(\frac{1}{3} \right) \Rightarrow B = 21 \Omega$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{6} S$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \Rightarrow -I_2 = I_1 \left(\frac{6}{6+3} \right) \Rightarrow D = \frac{3}{2}$$

16.25 Find the ABCD parameters for the circuit in Fig. P16.7.

SOLUTION:

$$A = \left. \frac{V_2}{V_1} \right|_{I_2=0} \Rightarrow V_2 = -\gamma V_1 \Rightarrow A = -\frac{1}{\gamma}$$

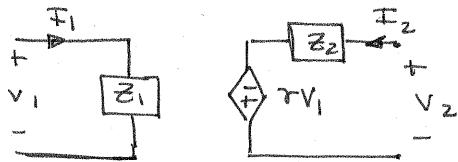

$$B = \left. \frac{I_2}{V_1} \right|_{V_2=0} \Rightarrow I_2 = \frac{\gamma V_1}{Z_2} \Rightarrow B = -\frac{Z_2}{\gamma}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \Rightarrow V_2 = -\gamma V_1 \text{ & } V_1 = I_1 Z_1 \Rightarrow C = -\frac{1}{\gamma Z_1}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} \Rightarrow I_2 = \frac{\gamma V_1}{Z_2} \text{ & } I_1 = \frac{V_1}{Z_1} \Rightarrow D = -\frac{Z_2}{\gamma Z_1}$$

16.26 Determine the transmission parameters for the network in Fig. P16.26. **CS**

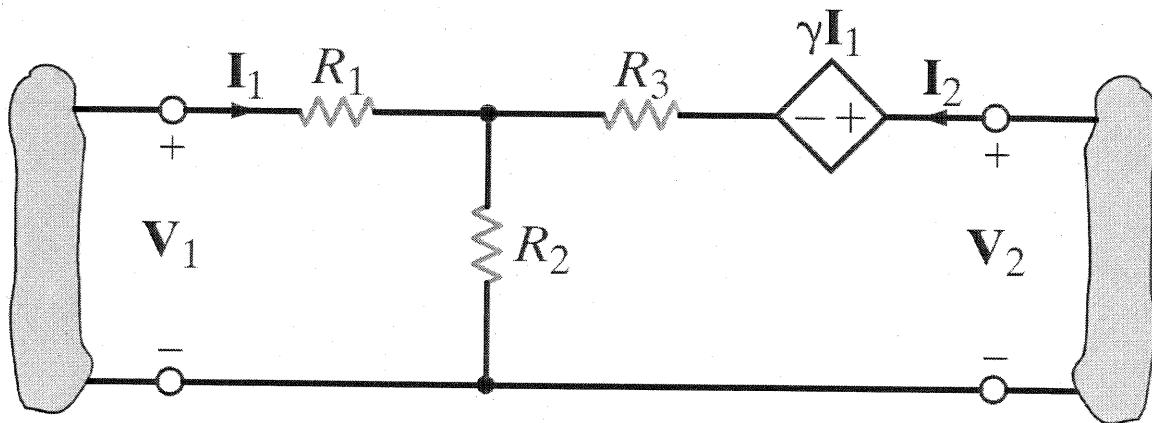


Figure P16.26

SOLUTION: Loop analysis!

$$V_1 = I_1(R_1 + R_2) + R_2 I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{R_1 + R_2}{r + R_1} \quad *$$

$$V_2 = (r + R_2)I_1 + (R_2 + R_3)I_2$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{r + R_2} \quad *$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$D = \left. \frac{\pm I_1}{I_2} \right|_{V_2=0} = \frac{R_2 + R_3}{r + R_2} \quad *$$

$$\text{So, } I_1 = -I_2(r_2 + R_3)/(r + R_2)$$

$$\text{and, } V_1 = I_2 \left[R_2 - (R_1 + R_2) \frac{R_2 + R_3}{r + R_2} \right] = -I_2 \left[\frac{R_1 R_2 + R_1 R_3 + R_2 R_3 - r R_2}{r + R_2} \right]$$

$$* B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3 - r R_2}{r + R_2}$$

16.27 Find the transmission parameters for the circuit in Fig. P16.27.

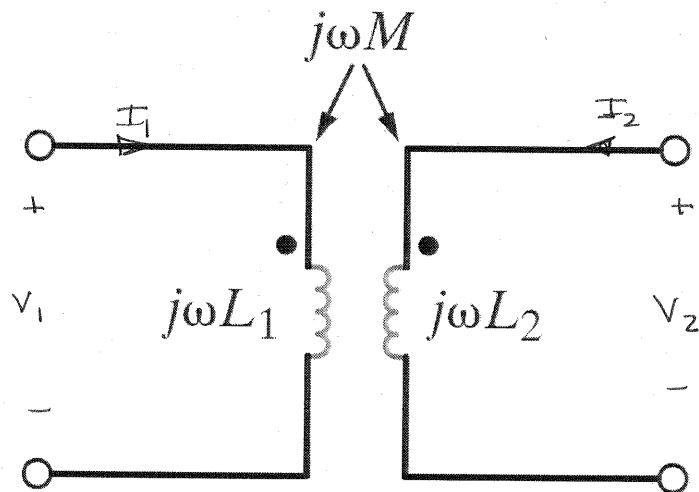


Figure P16.27

SOLUTION:

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{L_1}{M} \quad *$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{j\omega M} \quad *$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{L_2}{M} \quad *$$

$$\text{or, } I_1 = -I_2 \left(\frac{L_2}{M} \right)$$

$$* \quad V_1 = -I_2 \left(\frac{j\omega L_1 L_2}{M} - j\omega M \right) = -I_2 \left(\frac{j\omega L_1 L_2 - j\omega M^2}{M} \right)$$

$$* \quad B = j\omega \left(\frac{L_1 L_2 - M^2}{M} \right)$$

- 16.28 Given the network in Fig. P16.28, find the transmission parameters for the two-port network and then find I_o using the terminal conditions.

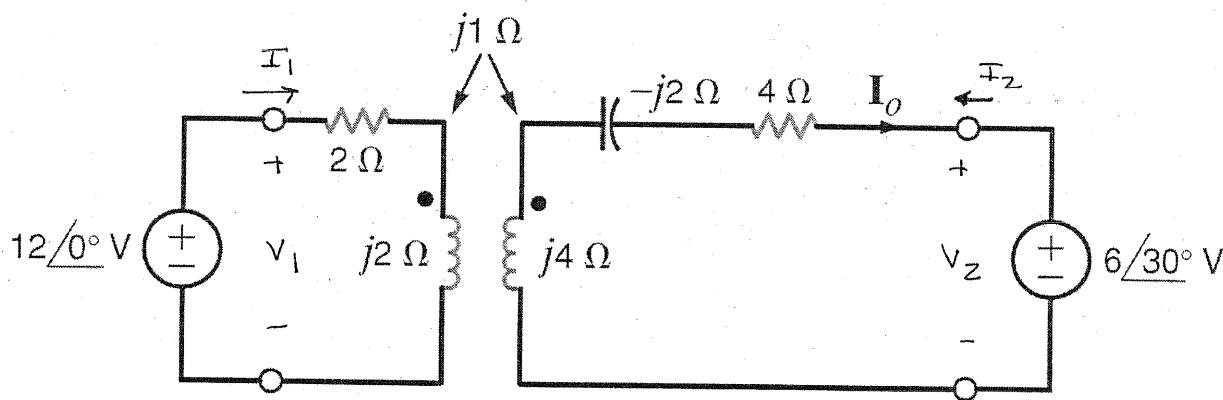


Figure P16.28

SOLUTION:

$$V_1 = I_1 (2 + j2) + j1 I_2 \quad A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{2 + j2}{j1} = 2 - j2 \quad *$$

$$V_2 = j1 I_1 + I_2 (4 + j2) \quad D = \frac{I_1}{-I_2} \Big|_{V_2=0} = \frac{4 + j2}{j1} = 2 - j4 \quad *$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \quad C = \frac{I_1}{V_2} \Big|_{I_2=0} = -j1 \quad S$$

$$\text{now, } I_1 = -I_2 (2 - j4)$$

$$\text{and } V_1 = -I_2 [(2 - j4)(2 + j2) - j1] = -I_2 (12 - j5)$$

$$* B = 12 - j5 \quad \Omega$$

Terminal conditions, $V_1 = 12 \angle 0^\circ V \quad V_2 = 6 \angle 30^\circ V \quad I_o = -I_2$

$$\begin{bmatrix} 2 + j2 & -j1 \\ j1 & -4 - j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \angle 0^\circ \\ 6 \angle 30^\circ \end{bmatrix} \Rightarrow I_2 = 0.48 \angle 157.6^\circ A \quad *$$

- 16.29** Find the input admittance of the two-port in Fig. P16.29 in terms of the Y parameters and the load \mathbf{Y}_L .

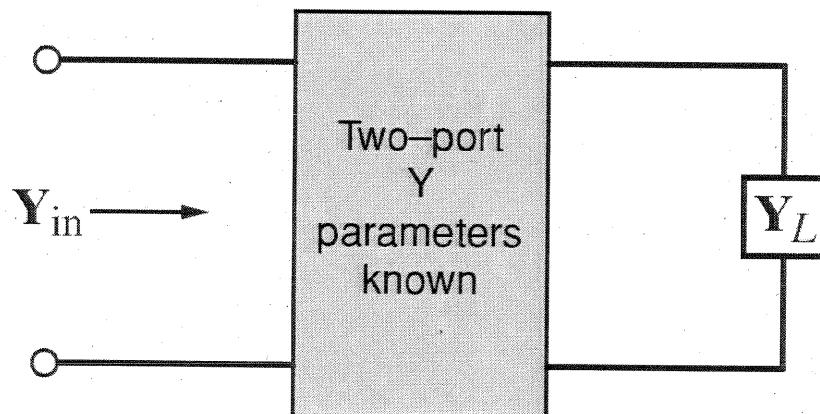


Figure P16.29

SOLUTION:

$$\left. \begin{array}{l} I_1 = V_1 Y_{11} + V_2 Y_{12} \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{array} \right\} \quad \begin{aligned} F_2 &= -V_2 Y_L \\ Y_{in} &= \frac{I_1}{V_1} = Y_{11} + Y_{12} \left(\frac{V_2}{V_1} \right) \end{aligned}$$

$$-V_2 Y_L = Y_{21} V_1 + Y_{22} V_2$$

$$0 = Y_{21} V_1 + V_2 (Y_{22} + Y_L) \Rightarrow \frac{V_2}{V_1} = -\frac{Y_{21}}{Y_{22} + Y_L}$$

$$Y_{in} = Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22} + Y_L}$$

16.30 Find the voltage gain V_2/V_1 for the network in Fig. P16.30 using the Z parameters.

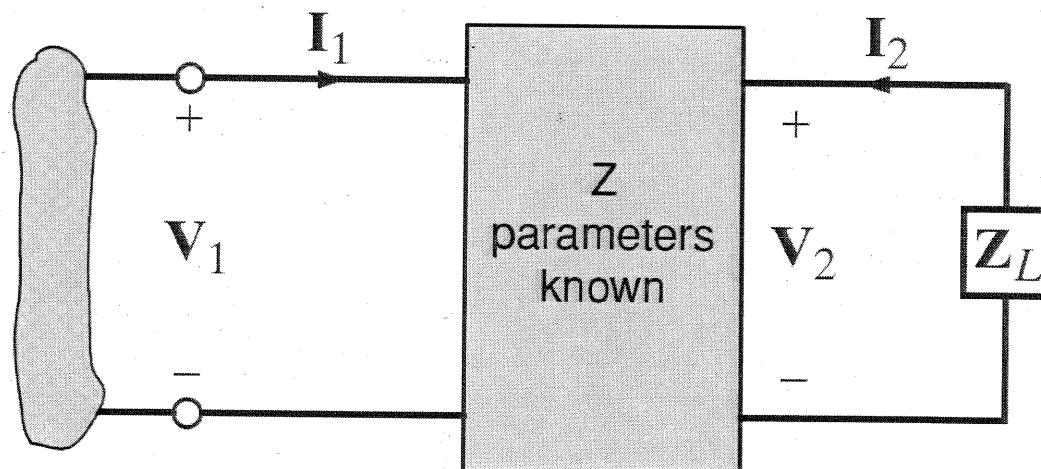


Figure P16.30

SOLUTION:

$$V_1 = I_1 Z_{11} + I_2 Z_{12} \quad V_2 = I_1 Z_{21} + I_2 Z_{22} \quad V_2 = -I_2 Z_L \Rightarrow I_2 = -\frac{V_2}{Z_L}$$

$$\text{now, } V_1 = I_1 Z_{11} - V_2 \left(\frac{Z_{12}}{Z_L} \right)$$

$$V_2 = I_1 Z_{21} - V_2 \left(\frac{Z_{22}}{Z_L} \right) \Rightarrow I_1 = V_2 \left(\frac{Z_L + Z_{22}}{Z_L Z_{21}} \right)$$

$$\text{and, } V_1 = V_2 \left[\frac{Z_{11} (Z_L + Z_{22})}{Z_L Z_{21}} - \frac{Z_{12}}{Z_L} \right] = V_2 \left[\frac{Z_{11} Z_L + Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_L Z_{21}} \right]$$

$$\frac{V_2}{V_1} = \frac{Z_{11} Z_L + Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_L Z_{21}}$$

16.31 Following are the hybrid parameters for a network.

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{11}{5} & \frac{2}{5} \\ -\frac{2}{5} & \frac{1}{5} \end{bmatrix}$$

Determine the Y parameters for the network.

SOLUTION:

$$* y_{11} = \frac{1}{h_{11}} = \frac{5}{11} \text{ S} \quad y_{21} = \frac{h_{21}}{h_{11}} = -\frac{2}{11} \text{ S} \quad *$$

$$* y_{12} = -\frac{h_{12}}{h_{11}} = -\frac{2}{11} \text{ S}$$

$$y_{22} = \frac{\Delta_H}{h_{11}} \quad \Delta_H = \frac{11}{5} \left(\frac{1}{5}\right) - \left(-\frac{2}{5}\right)\left(\frac{2}{5}\right) = \frac{11}{25} + \frac{4}{25} = \frac{15}{25} = \frac{3}{5}$$

$$* y_{22} = \frac{3}{11} \text{ S}$$

16.32 If the Y parameters for a network are known to be

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{11} & -\frac{2}{11} \\ -\frac{2}{11} & \frac{3}{11} \end{bmatrix}$$

find the Z parameters. **CS**

SOLUTION:

$$\Delta_Y = \frac{5}{11} \left(\frac{3}{11} \right) - \left(-\frac{2}{11} \right)^2 = \frac{15}{121} - \frac{4}{121} = \frac{1}{11}$$

$$Z_{11} = y_{22}/\Delta_Y = 3\Omega$$

$$Z_{21} = -y_{21}/\Delta_Y = 2\Omega$$

$$Z_{12} = -y_{12}/\Delta_Y = 2\Omega$$

$$Z_{22} = y_{11}/\Delta_Y = 5\Omega$$

16.33 Find the Z parameters in terms of the ABCD parameters.

SOLUTION:

ABCD Parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$V_2 = I_1/C + (D/C) I_2$$

$$V_1 = \frac{A}{C} I_1 + \frac{AD}{C} I_2 - BI_2 = \frac{A}{C} I_1 + \left(\frac{AD - BC}{C} \right) I_2$$

Z Parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

By comparison,

$$Z_{21} = \frac{1}{C} \quad Z_{22} = \frac{D}{C} \quad Z_{11} = \frac{A}{C}$$

$$Z_{12} = \frac{AD - BC}{C} = \frac{D}{C}$$

16.34 Find the hybrid parameters in terms of the impedance parameters.

SOLUTION:

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2) \Rightarrow I_2 = -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \quad (3)$$

Put (3) into (1)

$$V_1 = I_1 \left(Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right) + \frac{Z_{12}}{Z_{22}} V_2 \quad (4)$$

from (3) & (4):

$h_{11} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}}$ $h_{12} = \frac{Z_{12}}{Z_{22}}$ $h_{21} = -\frac{Z_{21}}{Z_{22}}$ $h_{22} = \frac{1}{Z_{22}}$
--

16.35 Find the Y parameters for the network in Fig. P16.35.

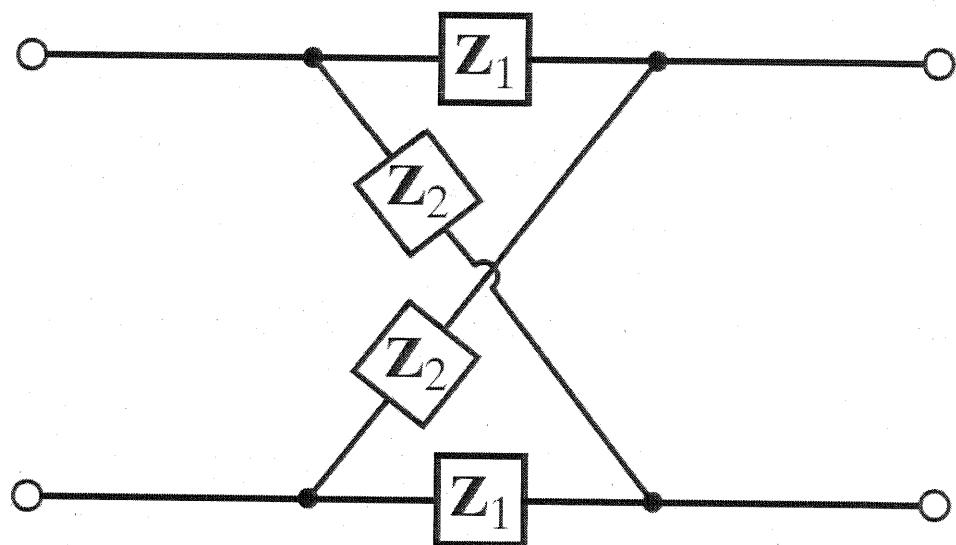


Figure P16.35

SOLUTION: Use parallel connections.

Case A

$$y_{11a} = \frac{1}{2Z_1}, \quad y_{12a} = -\frac{1}{2Z_1}$$

$$y_{21a} = -\frac{1}{2Z_1}, \quad y_{22a} = \frac{1}{2Z_1}$$

Case B

$$y_{11b} = \frac{1}{2Z_1}, \quad y_{12b} = \frac{1}{2Z_2}$$

$$y_{21b} = \frac{1}{2Z_2}, \quad y_{22b} = \frac{1}{2Z_2}$$

Total network: $y_{ij} = y_{ija} + y_{ijb}$

$$y_{11} = \frac{1}{2Z_1} + \frac{1}{2Z_2} \quad y_{12} = \frac{1}{2Z_2} - \frac{1}{2Z_1}$$

$$y_{21} = \frac{1}{2Z_2} - \frac{1}{2Z_1} \quad y_{22} = \frac{1}{2Z_1} + \frac{1}{2Z_2}$$

16.36 Determine the Y parameters for the network shown in Fig. P16.36.


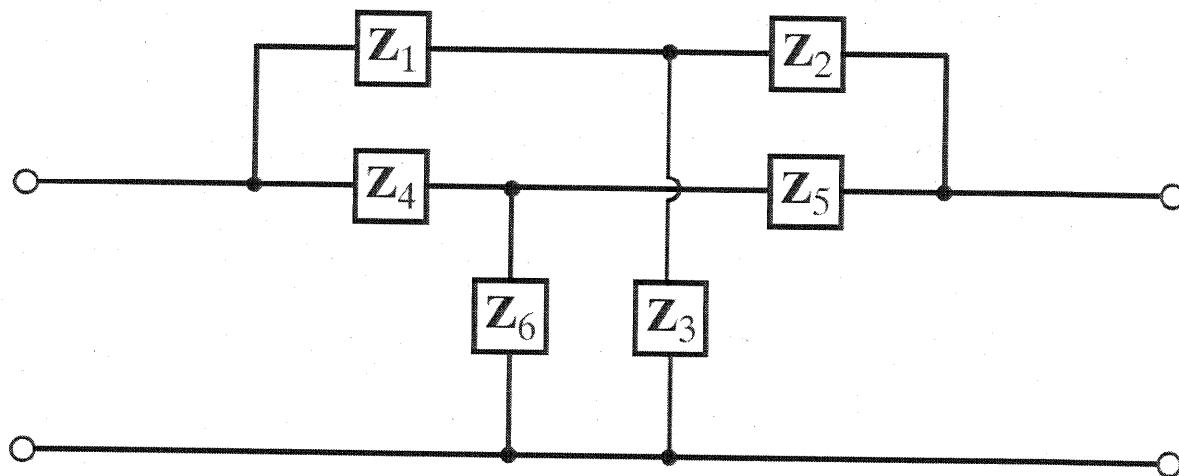


Figure P16.36

SOLUTION: 2 parallel T networks.

Case A

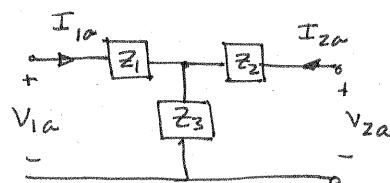

$$y_{11a} = \frac{1}{Z_1 + (Z_2//Z_3)} = \frac{Z_2 + Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3} = \frac{Z_2 + Z_3}{Z_A}$$

$$y_{22a} = \frac{1}{Z_2 + (Z_1//Z_3)} = \frac{Z_1 + Z_3}{Z_A}$$

$$y_{12a} = \frac{Z_1//Z_3}{Z_2 + (Z_1//Z_3)} \left(-\frac{1}{Z_1} \right) = -\frac{Z_3}{Z_A} \quad y_{21a} = -\frac{Z_3}{Z_A}$$

Similarly for the $Z_4-Z_5-Z_6$ T network,

$$y_{11b} = \frac{Z_5 + Z_6}{Z_B} \quad y_{22b} = \frac{Z_4 + Z_6}{Z_B} \quad y_{21b} = y_{12b} = -\frac{Z_6}{Z_B} \quad Z_B = Z_4 Z_5 + Z_5 Z_6 + Z_4 Z_6$$

Total y parameters : $y_{ij} = y_{ija} + y_{ijb}$

$$y_{11} = \frac{Z_2 + Z_3}{Z_A} + \frac{Z_5 + Z_6}{Z_B} \quad y_{12} = -\frac{Z_3}{Z_A} - \frac{Z_6}{Z_B}$$

$$y_{21} = -\frac{Z_3}{Z_A} - \frac{Z_6}{Z_B} \quad y_{22} = \frac{Z_1 + Z_3}{Z_A} + \frac{Z_4 + Z_6}{Z_B}$$

- 16.37 Find the Y parameters of the two-port network in Fig. P16.37. Find the input admittance of the network when the capacitor is connected to the output port. **CS**


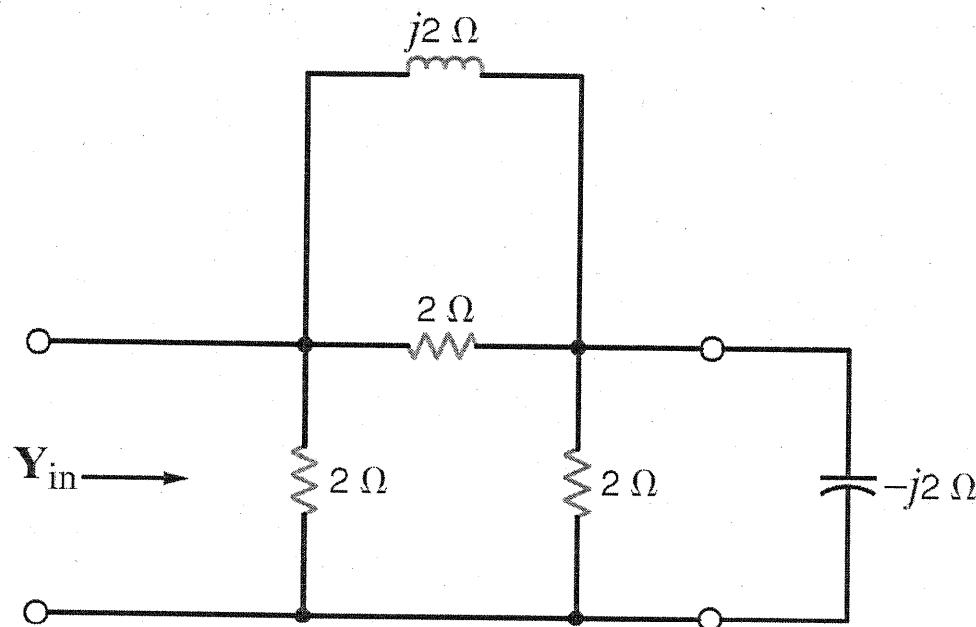
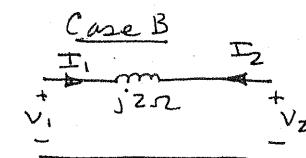


Figure P16.37

SOLUTION: Use 2 parallel networks

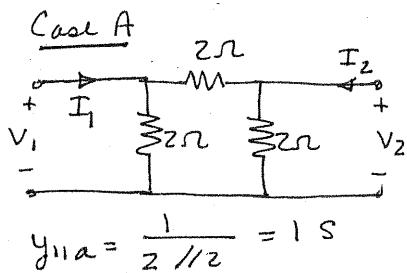

$$Y_{11} = Y_{11a} - \frac{Y_{12}Y_{21}}{Y_{22} + Y_L}$$

$$Y_{11} = 1 - \frac{1}{2} - \frac{\frac{1}{4}(1-j1)^2}{(1-j0.5)+j0.5}$$

$$Y_{11} = 1 - \frac{j}{2} - \frac{(1-j1)^2}{4}$$

$$Y_{in} = 1 \text{ S}$$

$$Y_{11} = 1 + \frac{1}{j2} = Y_{22} \quad Y_{12} = Y_{21} = -\frac{1}{2} - \frac{1}{j2} = -\frac{1}{2}(1-j1)$$

- 16.38 Find the Z parameters of the network in Fig. E16.3 by considering the circuit to be a series interconnection of two two-port networks as shown in Fig. P16.38.


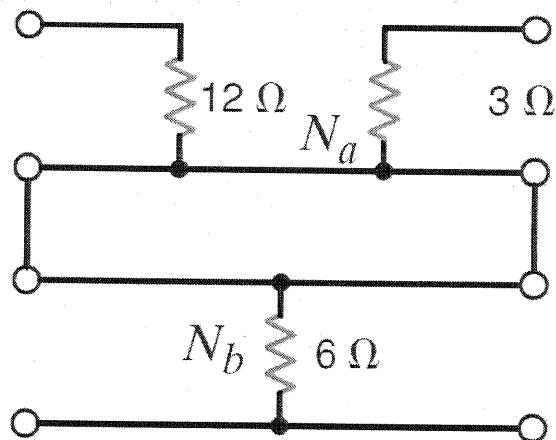


Figure P16.38

SOLUTION: Network consists of 2 series connected subcircuits

Circuit A

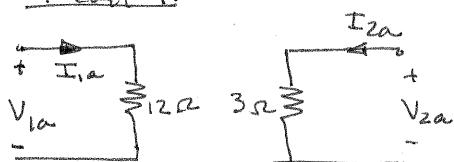


$$Z_{11a} = 12 \Omega \quad Z_{22a} = 3 \Omega$$

$$Z_{12a} = 0 \Omega \quad Z_{21a} = 0 \Omega$$

$$Z_{ij} = Z_{ija} + Z_{ijb}$$

Circuit B

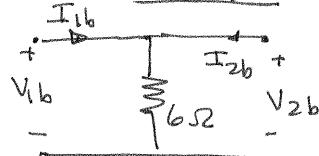

$$Z_{11b} = 6 \Omega \quad Z_{22b} = 6 \Omega$$

$$Z_{12b} = 6 \Omega \quad Z_{21b} = 6 \Omega$$

$Z_{11} = 18 \Omega$	$Z_{12} = 6 \Omega$	$Z_{21} = 6 \Omega$	$Z_{22} = 9 \Omega$
----------------------	---------------------	---------------------	---------------------

- 16.39 Find the transmission parameters of the network in Fig. E16.3 by considering the circuit to be a cascade interconnection of three two-port networks as shown in Fig. P16.39.

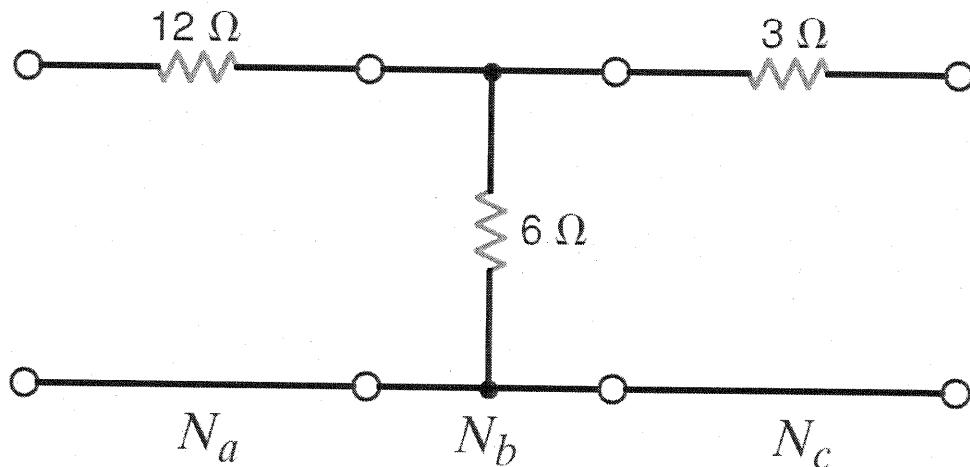


Figure P16.39

SOLUTION: Network consists of 3 two-ports!

<u>Circuit A</u>	<u>Circuit B</u>	<u>Circuit C</u>
 $A_a = \frac{V_1}{V_2} \Big _{I_2=0} = 1$	 $A_b = 1$	 $A_c = 1$
$B_a = \frac{V_1}{I_2} \Big _{V_2=0} = 12 \Omega$	$B_b = 0 \quad (I_{2b} = \infty)$	$B_c = 3 \Omega$
$C_a = \frac{I_1}{V_2} \Big _{I_2=0} = 0$	$C_b = \frac{1}{6} S$	$C_c = 0$
$D_a = \frac{I_1}{I_2} \Big _{V_2=0} = 1$	$D_b = 1$	$D_c = 1$
	$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 12 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{6} & 1 \end{bmatrix} \begin{bmatrix} 1 & 3 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 & 21 \\ \frac{1}{6} & \frac{3}{2} \end{bmatrix}$	✓

16.40 Find the ABCD parameters for the circuit in Fig. P16.40.


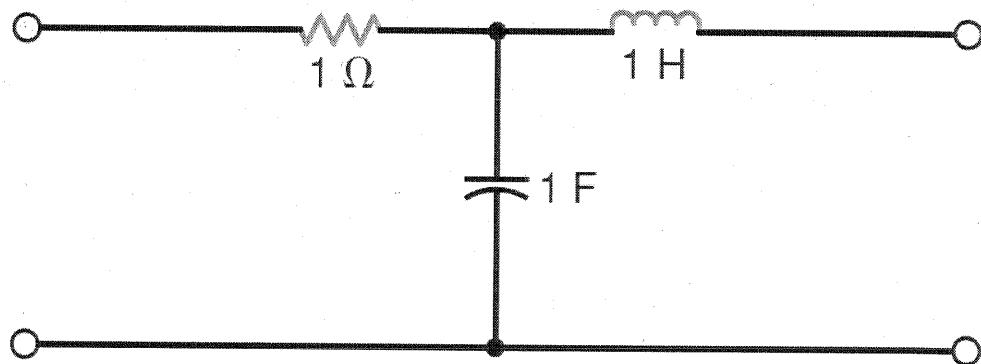


Figure P16.40

SOLUTION:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \Rightarrow \frac{V_2}{V_1} = \frac{\frac{1}{j\omega}}{1 + \frac{1}{j\omega}} = \frac{1}{j\omega + 1}$$

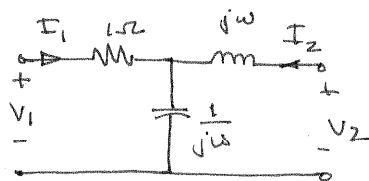

$$* \quad A = j\omega + l$$

$$B = -V_1/I_{Z_2} \Big|_{V_2=0} \Rightarrow -\frac{I_Z}{V_1} = \frac{j\omega // Y_{j\omega}}{(j\omega // Y_{j\omega}) + 1} \left(\frac{1}{j\omega} \right) = \frac{1}{1 + j\omega - \omega^2}$$

$$B = 1 + j\omega - \omega^2 \Omega$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \Rightarrow V_2/I_1 = \frac{1}{j\omega} \Rightarrow C = j\omega *$$

$$D = -I_1 / I_2 \Big|_{V_2=0} \Rightarrow -I_2 / I_1 = \frac{1/j\omega}{j\omega + 1/j\omega} = \frac{1}{1 - \omega^2}$$

$$\forall D = 1 - \omega^2$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} j\omega + 1 & 1+j\omega - \omega^2 \\ j\omega & 1-\omega^2 \end{bmatrix}$$

- 16.41 Find the Z parameters for the two-port network in Fig. P16.41 and then determine I_o for the specified terminal conditions.

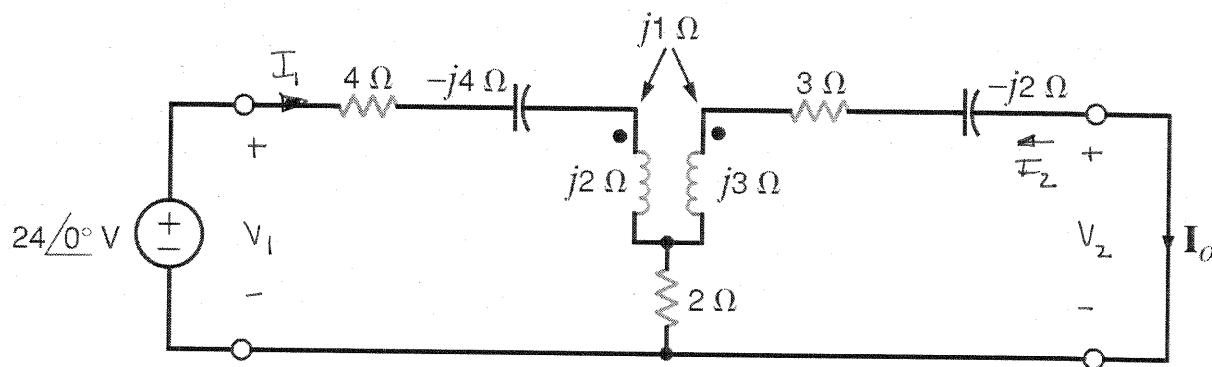


Figure P16.41

SOLUTION:

$$V_1 = I_1 (6 - j2) + I_2 (2 + j1)$$

$$V_2 = I_1 (2 + j1) + I_2 (5 + j1)$$

$$Z_{11} = 6 - j2 \Omega$$

$$Z_{12} = 2 + j1 \Omega$$

$$Z_{21} = 2 + j1 \Omega$$

$$Z_{22} = 5 + j1 \Omega$$

$$V_1 = 24 \angle 0^\circ V$$

$$I_2 = -I_o$$

$$V_2 = 0$$

$$\begin{bmatrix} 6 - j2 & 2 + j1 \\ 2 + j1 & 5 + j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 24 \angle 0^\circ \\ 0 \end{bmatrix} \Rightarrow I_2 = 1.78 \angle -138^\circ A$$

$$I_o = 1.78 \angle 42^\circ A$$

16.42 Determine the output voltage V_o in the network in Fig.

P16.42 if the Z parameters for the two-port are

$$Z = \begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix} \quad \text{PSV}$$


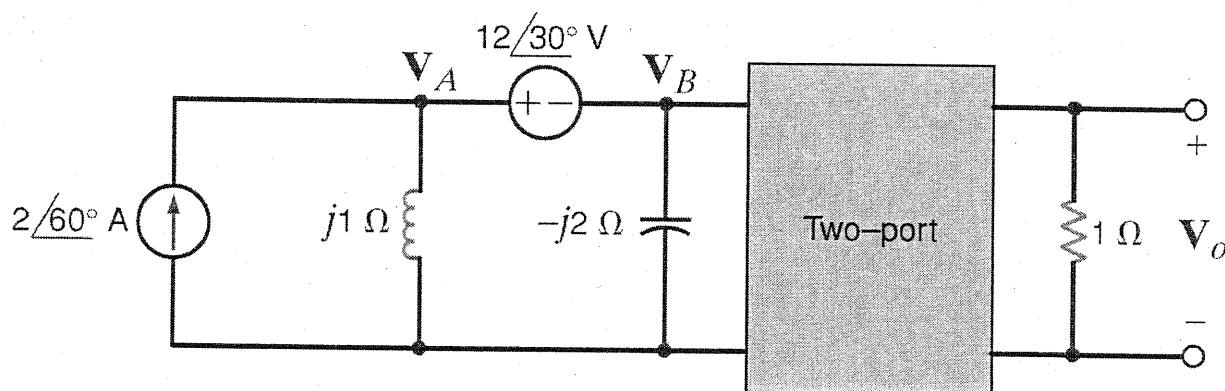


Figure P16.42

SOLUTION: Thevenin eq. at V_B . Use source exchange first.

$$\begin{aligned} & \text{Thevenin circuit at } V_B: \\ & \text{Source exchange: } 12 \angle 30^\circ \text{ V source and } j1 \Omega \text{ resistor} \\ & \text{Equivalent circuit: } -j2 \angle 0^\circ \text{ source and } j2 \Omega \text{ resistor} \\ & Z_{TH} = -j2 \parallel j1 = j2 \Omega \\ & V_{OC} = (2 \angle 150^\circ - 12 \angle 30^\circ) \left(\frac{-j2}{-j2 + j1} \right) = 26.2 \angle -158^\circ \end{aligned}$$

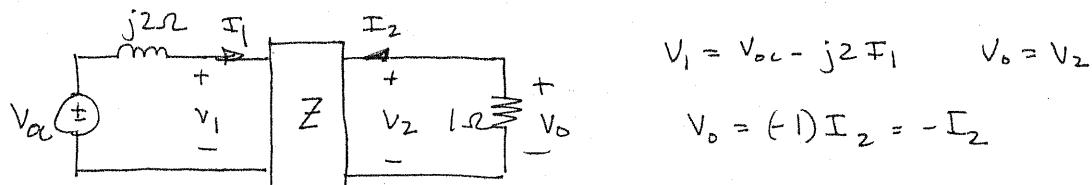

$$V_1 = 3I_1 + 2I_2 = V_{OC} - j2I_1 \Rightarrow I_1(3 + j2) + 2I_2 = V_{OC}$$

$$V_2 = 2I_1 + 3I_2 = -I_2 \Rightarrow I_1 + 2I_2 = 0 \Rightarrow I_1 = -2I_2$$

$$\text{now, } [(3 - j2)(-2) + 2]I_2 = V_{OC} \Rightarrow I_2 = -V_{OC}/(4 + j4)$$

$$V_o = \frac{V_{OC}}{4 + j4}$$

$$V_o = 4.64 \angle 157^\circ \text{ V}$$

16FE-1 A two-port network is known to have the following parameters:

$$y_{11} = \frac{1}{14} S \quad y_{12} = y_{21} = -\frac{1}{21} S \quad y_{22} = \frac{1}{7} S$$

If a 2-A current source is connected to the input terminals as shown in Fig. 16PFE-1, find the voltage across this current source. **CS**

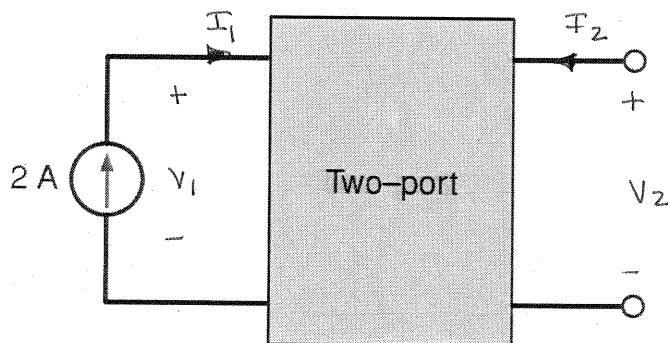


Figure 16PFE-1


SOLUTION: $I_1 = 2A$ $I_2 = 0$

$$\left. \begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 = 2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 = 0 \end{aligned} \right\} \quad \left. \begin{aligned} (1/14)V_1 - (1/21)V_2 &= 2 \Rightarrow 3V_1 - 2V_2 = 84 \\ -(1/21)V_1 + (1/7)V_2 &= 0 \Rightarrow -V_1 + 3V_2 = 0 \end{aligned} \right\}$$

Find V_1 . $V_1 = 36 V$

16FE-2 Find the Thévenin equivalent circuit at the output terminals of the network in Fig. 16PFE-1.

SOLUTION:

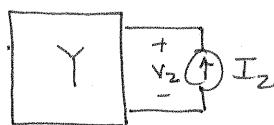

$$Y = \begin{bmatrix} Y_{11} & -Y_{12} \\ -Y_{21} & Y_{22} \end{bmatrix}$$

$$I_1 = 0 = Y_{11}V_1 + Y_{12}V_2 \Rightarrow V_1 = -V_2 \left(\frac{Y_{12}}{Y_{11}} \right)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \Rightarrow I_2 = V_2 \left(\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} \right)$$

$$Z_{TH} = \frac{V_2}{I_2} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{12}Y_{21}} = \frac{Y_{11}}{\Delta_Y}$$

$$\boxed{Z_{TH} = 1.575 \Omega}$$