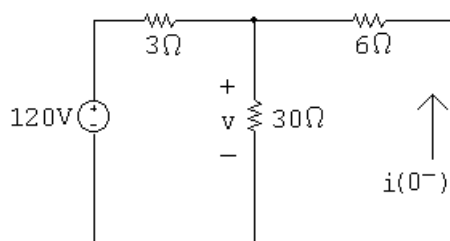


# Response of First-Order $RL$ and $RC$ Circuits

## Assessment Problems

AP 7.1 [a] The circuit for  $t < 0$  is shown below. Note that the inductor behaves like a short circuit, effectively eliminating the  $2\ \Omega$  resistor from the circuit.



First combine the  $30\ \Omega$  and  $6\ \Omega$  resistors in parallel:

$$30 \parallel 6 = 5\ \Omega$$

Use voltage division to find the voltage drop across the parallel resistors:

$$v = \frac{5}{5+3}(120) = 75\ \text{V}$$

Now find the current using Ohm's law:

$$i(0^-) = -\frac{v}{6} = -\frac{75}{6} = -12.5\ \text{A}$$

[b]  $w(0) = \frac{1}{2}Li^2(0) = \frac{1}{2}(8 \times 10^{-3})(12.5)^2 = 625\ \text{mJ}$

[c] To find the time constant, we need to find the equivalent resistance seen by the inductor for  $t > 0$ . When the switch opens, only the  $2\ \Omega$  resistor remains connected to the inductor. Thus,


$$\tau = \frac{L}{R} = \frac{8 \times 10^{-3}}{2} = 4\ \text{ms}$$

[d]  $i(t) = i(0^-)e^{t/\tau} = -12.5e^{-t/0.004} = -12.5e^{-250t}\ \text{A}, \quad t \geq 0$

[e]  $i(5\ \text{ms}) = -12.5e^{-250(0.005)} = -12.5e^{-1.25} = -3.58\ \text{A}$

$$\begin{aligned} \text{So } w(5 \text{ ms}) &= \frac{1}{2} Li^2(5 \text{ ms}) = \frac{1}{2}(8) \times 10^{-3}(3.58)^2 = 51.3 \text{ mJ} \\ w(\text{dis}) &= 625 - 51.3 = 573.7 \text{ mJ} \\ \% \text{ dissipated} &= \left( \frac{573.7}{625} \right) 100 = 91.8\% \end{aligned}$$

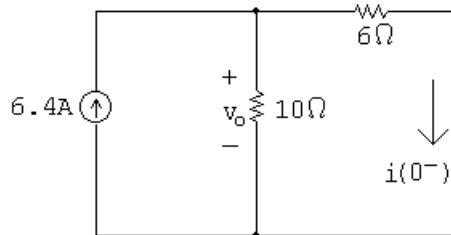
AP 7.2 [a] First, use the circuit for  $t < 0$  to find the initial current in the inductor:



Using current division,

$$i(0^-) = \frac{10}{10 + 6}(6.4) = 4 \text{ A}$$

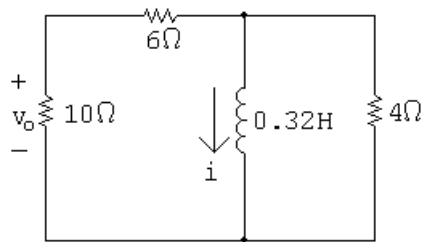Now use the circuit for  $t > 0$  to find the equivalent resistance seen by the inductor, and use this value to find the time constant:



$$R_{\text{eq}} = 4 \parallel (6 + 10) = 3.2 \Omega, \quad \therefore \quad \tau = \frac{L}{R_{\text{eq}}} = \frac{0.32}{3.2} = 0.1 \text{ s}$$

Use the initial inductor current and the time constant to find the current in the inductor:

$$i(t) = i(0^-)e^{-t/\tau} = 4e^{-t/0.1} = 4e^{-10t} \text{ A}, \quad t \geq 0$$

Use current division to find the current in the  $10 \Omega$  resistor:

$$i_o(t) = \frac{4}{4 + 10 + 6}(-i) = \frac{4}{20}(-4e^{-10t}) = -0.8e^{-10t} \text{ A}, \quad t \geq 0^+$$

Finally, use Ohm's law to find the voltage drop across the  $10 \Omega$  resistor:

$$v_o(t) = 10i_o = 10(-0.8e^{-10t}) = -8e^{-10t} \text{ V}, \quad t \geq 0^+$$

[b] The initial energy stored in the inductor is

$$w(0) = \frac{1}{2} Li^2(0^-) = \frac{1}{2}(0.32)(4)^2 = 2.56 \text{ J}$$

Find the energy dissipated in the  $4 \Omega$  resistor by integrating the power over all time:

$$v_{4\Omega}(t) = L \frac{di}{dt} = 0.32(-10)(4e^{-10t}) = -12.8e^{-10t} \text{ V}, \quad t \geq 0^+$$


$$p_{4\Omega}(t) = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0^+$$

$$w_{4\Omega}(t) = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

Find the percentage of the initial energy in the inductor dissipated in the  $4\Omega$  resistor:

$$\% \text{ dissipated} = \left( \frac{2.048}{2.56} \right) 100 = 80\%$$

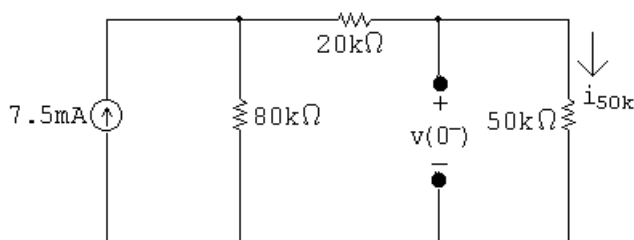AP 7.3 [a] The circuit for  $t < 0$  is shown below. Note that the capacitor behaves like an open circuit.



Find the voltage drop across the open circuit by finding the voltage drop across the  $50\text{ k}\Omega$  resistor. First use current division to find the current through the  $50\text{ k}\Omega$  resistor:

$$i_{50k} = \frac{80 \times 10^3}{80 \times 10^3 + 20 \times 10^3 + 50 \times 10^3} (7.5 \times 10^{-3}) = 4 \text{ mA}$$

Use Ohm's law to find the voltage drop:

$$v(0^-) = (50 \times 10^3) i_{50k} = (50 \times 10^3)(0.004) = 200 \text{ V}$$

[b] To find the time constant, we need to find the equivalent resistance seen by the capacitor for  $t > 0$ . When the switch opens, only the  $50\text{ k}\Omega$  resistor remains connected to the capacitor. Thus,

$$\tau = RC = (50 \times 10^3)(0.4 \times 10^{-6}) = 20 \text{ ms}$$

$$[c] \quad v(t) = v(0^-)e^{-t/\tau} = 200e^{-t/0.02} = 200e^{-50t} \text{ V}, \quad t \geq 0$$


$$[d] \quad w(0) = \frac{1}{2}Cv^2 = \frac{1}{2}(0.4 \times 10^{-6})(200)^2 = 8 \text{ mJ}$$

$$[e] \quad w(t) = \frac{1}{2}Cv^2(t) = \frac{1}{2}(0.4 \times 10^{-6})(200e^{-50t})^2 = 8e^{-100t} \text{ mJ}$$

The initial energy is 8 mJ, so when 75% is dissipated, 2 mJ remains:

$$8 \times 10^{-3}e^{-100t} = 2 \times 10^{-3}, \quad e^{100t} = 4, \quad t = (\ln 4)/100 = 13.86 \text{ ms}$$

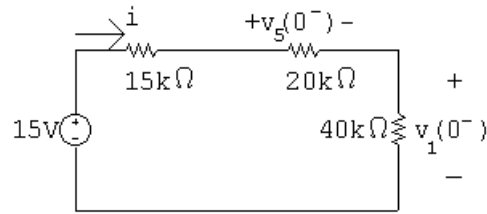AP 7.4 [a] This circuit is actually two  $RC$  circuits in series, and the requested voltage,  $v_o$ , is the sum of the voltage drops for the two  $RC$  circuits. The circuit for  $t < 0$  is shown below:



Find the current in the loop and use it to find the initial voltage drops across the two  $RC$  circuits:

$$i = \frac{15}{75,000} = 0.2 \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

There are two time constants in the circuit, one for each  $RC$  subcircuit.  $\tau_5$  is the time constant for the  $5 \mu\text{F} - 20 \text{ k}\Omega$  subcircuit, and  $\tau_1$  is the time constant for the  $1 \mu\text{F} - 40 \text{ k}\Omega$  subcircuit:

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}; \quad \tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}$$

Therefore,

$$v_5(t) = v_5(0^-)e^{-t/\tau_5} = 4e^{-t/0.1} = 4e^{-10t} \text{ V}, \quad t \geq 0$$

$$v_1(t) = v_1(0^-)e^{-t/\tau_1} = 8e^{-t/0.04} = 8e^{-25t} \text{ V}, \quad t \geq 0$$

Finally,

$$v_o(t) = v_1(t) + v_5(t) = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

**[b]** Find the value of the voltage at 60 ms for each subcircuit and use the voltage to find the energy at 60 ms:

$$v_1(60 \text{ ms}) = 8e^{-25(0.06)} \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) = 4e^{-10(0.06)} \cong 2.20 \text{ V}$$

$$w_1(60 \text{ ms}) = \frac{1}{2}Cv_1^2(60 \text{ ms}) = \frac{1}{2}(1 \times 10^{-6})(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = \frac{1}{2}Cv_5^2(60 \text{ ms}) = \frac{1}{2}(5 \times 10^{-6})(2.20)^2 \cong 12.05 \mu\text{J}$$

$$w(60 \text{ ms}) = 1.59 + 12.05 = 13.64 \mu\text{J}$$

Find the initial energy from the initial voltage:


$$w(0) = w_1(0) + w_2(0) = \frac{1}{2}(1 \times 10^{-6})(8)^2 + \frac{1}{2}(5 \times 10^{-6})(4)^2 = 72 \mu\text{J}$$

Now calculate the energy dissipated at 60 ms and compare it to the initial energy:

$$w_{\text{diss}} = w(0) - w(60 \text{ ms}) = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36 \times 10^{-6} / 72 \times 10^{-6})(100) = 81.05 \%$$

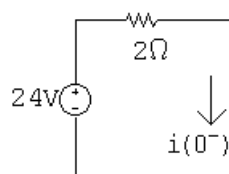
AP 7.5 **[a]** Use the circuit at  $t < 0$ , shown below, to calculate the initial current in the inductor:



$$i(0^-) = 24/2 = 12 \text{ A} = i(0^+)$$

Note that  $i(0^-) = i(0^+)$  because the current in an inductor is continuous.

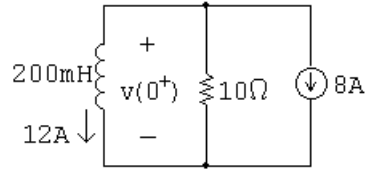- [b]** Use the circuit at  $t = 0^+$ , shown below, to calculate the voltage drop across the inductor at  $0^+$ . Note that this is the same as the voltage drop across the  $10 \Omega$  resistor, which has current from two sources — 8 A from the current source and 12 A from the initial current through the inductor.




$$v(0^+) = -10(8 + 12) = -200 \text{ V}$$

- [c]** To calculate the time constant we need the equivalent resistance seen by the inductor for  $t > 0$ . Only the  $10 \Omega$  resistor is connected to the inductor for  $t > 0$ . Thus,

$$\tau = L/R = (200 \times 10^{-3}/10) = 20 \text{ ms}$$

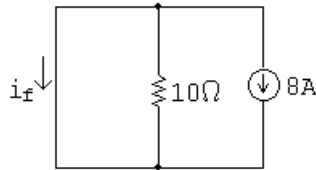- [d]** To find  $i(t)$ , we need to find the final value of the current in the inductor. When the switch has been in position a for a long time, the circuit reduces to the one below:



Note that the inductor behaves as a short circuit and all of the current from the 8 A source flows through the short circuit. Thus,

$$i_f = -8 \text{ A}$$


Now,

$$\begin{aligned} i(t) &= i_f + [i(0^+) - i_f]e^{-t/\tau} = -8 + [12 - (-8)]e^{-t/0.02} \\ &= -8 + 20e^{-50t} \text{ A}, \quad t \geq 0 \end{aligned}$$

- [e]** To find  $v(t)$ , use the relationship between voltage and current for an inductor:

$$v(t) = L \frac{di(t)}{dt} = (200 \times 10^{-3})(-50)(20e^{-50t}) = -200e^{-50t} \text{ V}, \quad t \geq 0^+$$

AP 7.6 [a]

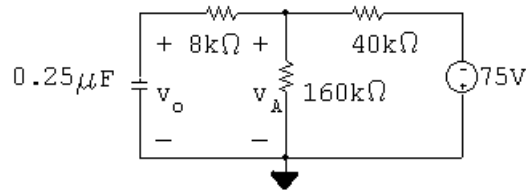

From Example 7.6,

$$v_o(t) = -60 + 90e^{-100t} \text{ V}$$

Write a KVL equation at the top node and use it to find the relationship between  $v_o$  and  $v_A$ :

$$\frac{v_A - v_o}{8000} + \frac{v_A}{160,000} + \frac{v_A + 75}{40,000} = 0$$

$$20v_A - 20v_o + v_A + 4v_A + 300 = 0$$

$$25v_A = 20v_o - 300$$


$$v_A = 0.8v_o - 12$$

Use the above equation for  $v_A$  in terms of  $v_o$  to find the expression for  $v_A$ :

$$v_A(t) = 0.8(-60 + 90e^{-100t}) - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+$$

[b]  $t \geq 0^+$ , since there is no requirement that the voltage be continuous in a resistor.

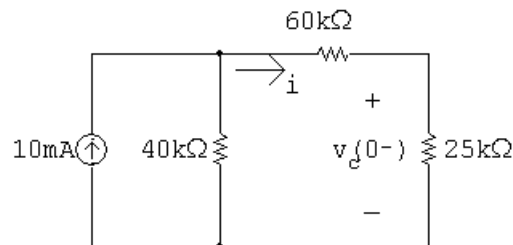
AP 7.7 [a] Use the circuit shown below, for  $t < 0$ , to calculate the initial voltage drop across the capacitor:



$$i = \left( \frac{40 \times 10^3}{125 \times 10^3} \right) (10 \times 10^{-3}) = 3.2 \text{ mA}$$

$$v_c(0^-) = (3.2 \times 10^{-3})(25 \times 10^3) = 80 \text{ V} \quad \text{so} \quad v_c(0^+) = 80 \text{ V}$$

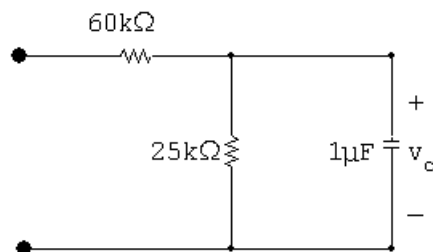Now use the next circuit, valid for  $0 \leq t \leq 10 \text{ ms}$ , to calculate  $v_c(t)$  for that interval:



For  $0 \leq t \leq 100 \text{ ms}$ :


$$\tau = RC = (25 \times 10^3)(1 \times 10^{-6}) = 25 \text{ ms}$$

$$v_c(t) = v_c(0^-)e^{t/\tau} = 80e^{-40t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

**[b]** Calculate the starting capacitor voltage in the interval  $t \geq 10 \text{ ms}$ , using the capacitor voltage from the previous interval:

$$v_c(0.01) = 80e^{-40(0.01)} = 53.63 \text{ V}$$

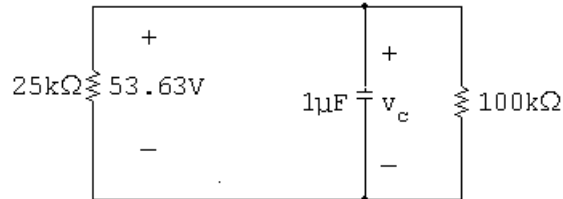Now use the next circuit, valid for  $t \geq 10 \text{ ms}$ , to calculate  $v_c(t)$  for that interval:



For  $t \geq 10 \text{ ms}$ :

$$R_{\text{eq}} = 25 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$\tau = R_{\text{eq}}C = (20 \times 10^3)(1 \times 10^{-6}) = 0.02 \text{ s}$$

$$\text{Therefore } v_c(t) = v_c(0.01^+)e^{-(t-0.01)/\tau} = 53.63e^{-50(t-0.01)} \text{ V}, \quad t \geq 0.01 \text{ s}$$

**[c]** To calculate the energy dissipated in the  $25 \text{ k}\Omega$  resistor, integrate the power absorbed by the resistor over all time. Use the expression  $p = v^2/R$  to calculate the power absorbed by the resistor.

$$w_{25 \text{ k}} = \int_0^{0.01} \frac{[80e^{-40t}]^2}{25,000} dt + \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{25,000} dt = 2.91 \text{ mJ}$$

**[d]** Repeat the process in part (c), but recognize that the voltage across this resistor is non-zero only for the second interval:

$$w_{100 \text{ k}\Omega} = \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{100,000} dt = 0.29 \text{ mJ}$$

We can check our answers by calculating the initial energy stored in the capacitor. All of this energy must eventually be dissipated by the  $25 \text{ k}\Omega$  resistor and the  $100 \text{ k}\Omega$  resistor.

$$\text{Check: } w_{\text{stored}} = (1/2)(1 \times 10^{-6})(80)^2 = 3.2 \text{ mJ}$$


$$w_{\text{diss}} = 2.91 + 0.29 = 3.2 \text{ mJ}$$

**AP 7.8 [a]** Note – the  $30 \Omega$  resistor should be a  $3 \Omega$  resistor; the resistor in parallel with the  $8 \text{ A}$  current source should be  $9 \Omega$ .

Prior to switch a closing at  $t = 0$ , there are no sources connected to the inductor; thus,  $i(0^-) = 0$ .

At the instant A is closed,  $i(0^+) = 0$ .

For  $0 \leq t \leq 1$  s,

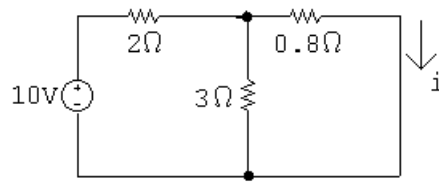

The equivalent resistance seen by the 10 V source is  $2 + (3 \parallel 0.8)$ . The current leaving the 10 V source is

$$\frac{10}{2 + (3 \parallel 0.8)} = 3.8 \text{ A}$$

The final current in the inductor, which is equal to the current in the  $0.8 \Omega$  resistor is

$$i(\infty) = \frac{3}{3 + 0.8}(3.8) = 3 \text{ A}$$

The resistance seen by the inductor is calculated to find the time constant:

$$0.8 + (2 \parallel 3) = 2 \Omega \quad \tau = \frac{L}{R} = \frac{2}{2} = 1 \text{ s}$$


Therefore,

$$i = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau} = 3 - 3e^{-t} \text{ A}, \quad 0 \leq t \leq 1 \text{ s}$$

For part (b) we need the value of  $i(t)$  at  $t = 1$  s:

$$i(1) = 3 - 3e^{-1} = 1.896 \text{ A}$$

**[b]** For  $t > 1$  s

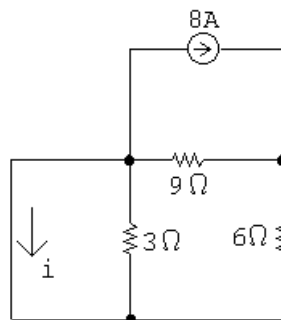

Use current division to find the final value of the current:

$$i = \frac{9}{9 + 6}(-8) = -4.8 \text{ A}$$

The equivalent resistance seen by the inductor is used to calculate the time constant:


$$3 \parallel (9 + 6) = 2.5 \Omega \quad \tau = \frac{L}{R} = \frac{2}{2.5} = 0.8 \text{ s}$$



Therefore,

$$\begin{aligned}
 i &= i(\infty) + [i(1^+) - i(\infty)]e^{-(t-1)/\tau} \\
 &= -4.8 + 6.696e^{-1.25(t-1)} \text{ A}, \quad t \geq 1 \text{ s}
 \end{aligned}$$

AP 7.9  $0 \leq t \leq 32 \text{ ms}$ :

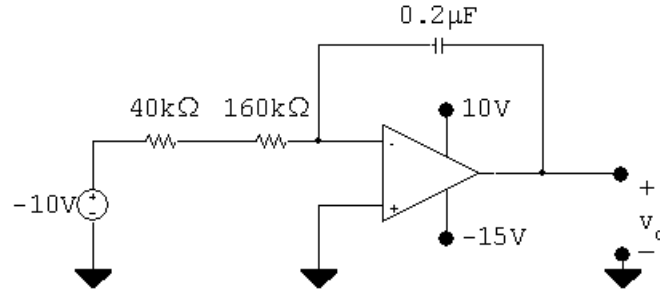


$$v_o = -\frac{1}{RC_f} \int_0^{32 \times 10^{-3}} -10 \, dt + 0 = -\frac{1}{RC_f} (-10t) \Big|_0^{32 \times 10^{-3}} = -\frac{1}{RC_f} (-320 \times 10^{-3})$$

$$RC_f = (200 \times 10^3)(0.2 \times 10^{-6}) = 40 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 25$$

$$v_o = -25(-320 \times 10^{-3}) = 8 \text{ V}$$

$t \geq 32 \text{ ms}$ :

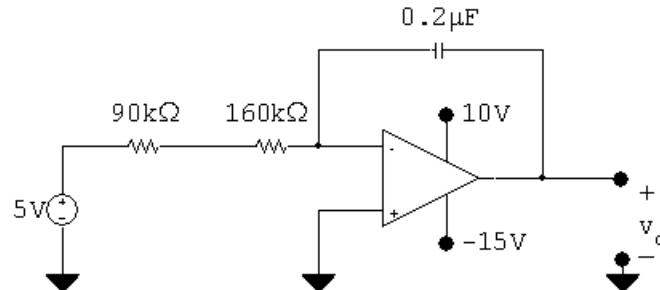

$$v_o = -\frac{1}{RC_f} \int_{32 \times 10^{-3}}^t 5 \, dy + 8 = -\frac{1}{RC_f} (5y) \Big|_{32 \times 10^{-3}}^t + 8 = -\frac{1}{RC_f} 5(t - 32 \times 10^{-3}) + 8$$

$$RC_f = (250 \times 10^3)(0.2 \times 10^{-6}) = 50 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 20$$

$$v_o = -20(5)(t - 32 \times 10^{-3}) + 8 = -100t + 11.2$$

The output will saturate at the negative power supply value:

$$-15 = -100t + 11.2 \quad \therefore \quad t = 262 \text{ ms}$$

AP 7.10 [a] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (0 + 2)e^{-t/\tau}$$

$$\tau = (160 \times 10^3)(10 \times 10^{-9}) = 10^{-3}; \quad 1/\tau = 625$$

$$v_p = -2 + 2e^{-625t} \text{ V}; \quad v_n = v_p$$

Write a KVL equation at the inverting input, and use it to determine  $v_o$ :

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{40,000} = 0$$

$$\therefore v_o = 5v_n = 5v_p = -10 + 10e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 10e^{-625t} = -5; \quad e^{-625t} = 1/2; \quad t = \ln 2/625 = 1.11 \text{ ms}$$

[b] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (1 + 2)e^{-625t} = -2 + 3e^{-625t} \text{ V}$$


The analysis for  $v_o$  is the same as in part (a):

$$v_o = 5v_p = -10 + 15e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 15e^{-625t} = -5; \quad e^{-625t} = 1/3; \quad t = \ln 3/625 = 1.76 \text{ ms}$$

## Problems

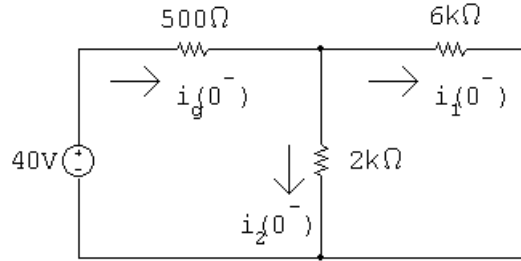P 7.1 [a]  $t < 0$ 

$$2\text{ k}\Omega \parallel 6\text{ k}\Omega = 1.5\text{ k}\Omega$$

Find the current from the voltage source by combining the resistors in series and parallel and using Ohm's law:

$$i_g(0^-) = \frac{40}{(1500 + 500)} = 20\text{ mA}$$

Find the branch currents using current division:

$$i_1(0^-) = \frac{2000}{8000}(0.02) = 5\text{ mA}$$

$$i_2(0^-) = \frac{6000}{8000}(0.02) = 15\text{ mA}$$

[b] The current in an inductor is continuous. Therefore,

$$i_1(0^+) = i_1(0^-) = 5\text{ mA}$$

$$i_2(0^+) = -i_1(0^+) = -5\text{ mA} \quad (\text{when switch is open})$$

$$\text{[c]} \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3}}{8 \times 10^3} = 5 \times 10^{-5}\text{ s}; \quad \frac{1}{\tau} = 20,000$$

$$i_1(t) = i_1(0^+)e^{-t/\tau} = 5e^{-20,000t}\text{ mA}, \quad t \geq 0$$

$$\text{[d]} \quad i_2(t) = -i_1(t) \quad \text{when } t \geq 0^+$$

$$\therefore i_2(t) = -5e^{-20,000t}\text{ mA}, \quad t \geq 0^+$$

[e] The current in a resistor can change instantaneously. The switching operation forces  $i_2(0^-)$  to equal 15 mA and  $i_2(0^+) = -5\text{ mA}$ .

P 7.2 [a]  $i(0) = 60\text{ V}/(10\text{ }\Omega + 5\text{ }\Omega) = 4\text{ A}$ 

$$\text{[b]} \quad \tau = \frac{L}{R} = \frac{4}{45 + 5} = 80\text{ ms}$$

$$[\mathbf{c}] \quad i = 4e^{-t/0.08} = 4e^{-12.5t} \text{ A}, \quad t \geq 0$$

$$v_1 = -45i = -180e^{-12.5t} \text{ V} \quad t \geq 0^+$$

$$v_2 = L \frac{di}{dt} = (4)(-12.5)(4e^{-12.5t}) = -200e^{-12.5t} \text{ V} \quad t \geq 0^+$$

$$[\mathbf{d}] \quad p_{\text{diss}} = i^2(45) = 720e^{-25t} \text{ W}$$

$$w_{\text{diss}} = \int_0^t 720e^{-25x} dx = 720 \frac{e^{-25x}}{-25} \Big|_0^t = 28.8 - 28.8e^{-25t} \text{ J}$$


$$w_{\text{diss}}(40 \text{ ms}) = 28.8 - 28.8e^{-1} = 18.205 \text{ J}$$

$$w(0) = \frac{1}{2}(4)(4)^2 = 32 \text{ J}$$

$$\% \text{ dissipated} = \frac{18.205}{32}(100) = 56.89\%$$

P 7.3 **[a]**  $i_o(0^-) = 0$  since the switch is open for  $t < 0$ .

**[b]** For  $t = 0^-$  the circuit is:

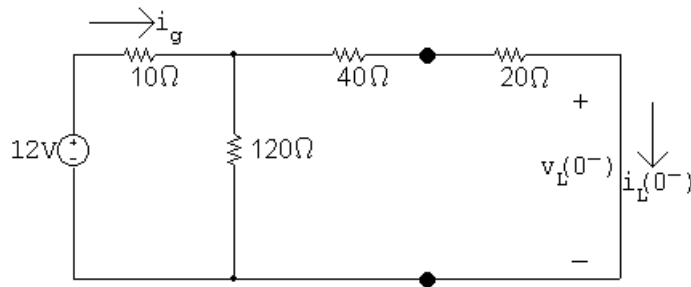


$$120 \Omega \parallel 60 \Omega = 40 \Omega$$

$$\therefore i_g = \frac{12}{10 + 40} = 0.24 \text{ A} = 240 \text{ mA}$$

$$i_L(0^-) = \left(\frac{120}{180}\right) i_g = 160 \text{ mA}$$

**[c]** For  $t = 0^+$  the circuit is:

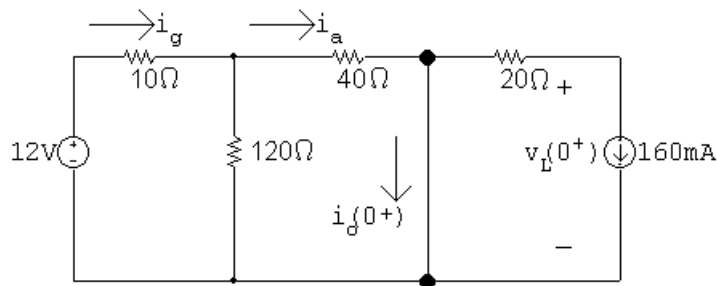

$$120 \Omega \parallel 40 \Omega = 30 \Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30 \text{ A} = 300 \text{ mA}$$

$$i_a = \left(\frac{120}{160}\right) 300 = 225 \text{ mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65 \text{ mA}$$

$$\textbf{[d]} \quad i_L(0^+) = i_L(0^-) = 160 \text{ mA}$$

$$\textbf{[e]} \quad i_o(\infty) = i_a = 225 \text{ mA}$$

$$\textbf{[f]} \quad i_L(\infty) = 0, \quad \text{since the switch short circuits the branch containing the } 20 \, \Omega \text{ resistor and the } 100 \text{ mH inductor.}$$

$$\textbf{[g]} \quad \tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$$

$$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t} \text{ mA}, \quad t \geq 0$$

$$\textbf{[h]} \quad v_L(0^-) = 0 \quad \text{since for } t < 0 \text{ the current in the inductor is constant}$$

$$\textbf{[i]} \quad \text{Refer to the circuit at } t = 0^+ \text{ and note:}$$

$$20(0.16) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -3.2 \text{ V}$$

$$\textbf{[j]} \quad v_L(\infty) = 0, \quad \text{since the current in the inductor is a constant at } t = \infty.$$

$$\textbf{[k]} \quad v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t} \text{ V}, \quad t \geq 0^+$$

$$\textbf{[l]} \quad i_o = i_a - i_L = 225 - 160e^{-200t} \text{ mA}, \quad t \geq 0^+$$

$$\textbf{P 7.4 [a]} \quad \frac{v}{i} = R = \frac{400e^{-5t}}{10e^{-5t}} = 40 \, \Omega$$

$$\textbf{[b]} \quad \tau = \frac{1}{5} = 200 \text{ ms}$$

$$\textbf{[c]} \quad \tau = \frac{L}{R} = 200 \times 10^{-3}$$

$$L = (200 \times 10^{-3})(40) = 8 \text{ H}$$

$$\textbf{[d]} \quad w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(8)(10)^2 = 400 \text{ J}$$

$$\textbf{[e]} \quad w_{\text{diss}} = \int_0^t 4000e^{-10x} dx = 400 - 400e^{-10t}$$

$$0.8w(0) = (0.8)(400) = 320 \text{ J}$$

$$400 - 400e^{-10t} = 320 \quad \therefore e^{10t} = 5$$

$$\text{Solving, } t = 160.9 \text{ ms.}$$

P 7.5 [a]  $i_L(0) = \frac{12}{6} = 2 \text{ A}$

$$i_o(0^+) = \frac{12}{2} - 2 = 6 - 2 = 4 \text{ A}$$

$$i_o(\infty) = \frac{12}{2} = 6 \text{ A}$$

[b]  $i_L = 2e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{1}{4} \text{ s}$

$$i_L = 2e^{-4t} \text{ A}$$

$$i_o = 6 - i_L = 6 - 2e^{-4t} \text{ A}, \quad t \geq 0^+$$

[c]  $6 - 2e^{-4t} = 5$

$$1 = 2e^{-4t}$$

$$e^{6t} = 2 \quad \therefore t = 173.3 \text{ ms}$$

P 7.6  $w(0) = \frac{1}{2}(30 \times 10^{-3})(3^2) = 135 \text{ mJ}$

$$\frac{1}{5}w(0) = 27 \text{ mJ}$$

$$i_R = 3e^{-t/\tau}$$

$$p_{\text{diss}} = i_R^2 R = 9Re^{-2t/\tau}$$

$$w_{\text{diss}} = \int_0^t R(9)e^{-2x/\tau} dx$$

$$w_{\text{diss}} = 9R \frac{e^{-2x/\tau}}{-2/\tau} \Big|_0^{t_o} = -4.5\tau R(e^{-2t_o/\tau} - 1) = 4.5L(1 - e^{-2t_o/\tau})$$

$$4.5L = (4.5)(30) \times 10^{-3} = 0.135; \quad t_o = 15 \mu\text{s}$$

$$1 - e^{-2t_o/\tau} = \frac{1}{5}$$

$$e^{2t_o/\tau} = 1.25; \quad \frac{2t_o}{\tau} = \frac{2t_o R}{L} = \ln 1.25$$

$$R = \frac{L \ln 1.25}{2t_o} = \frac{30 \times 10^{-3} \ln 1.25}{30 \times 10^{-6}} = 223.14 \Omega$$

P 7.7 [a]  $w(0) = \frac{1}{2}LI_g^2$

$$w_{\text{diss}} = \int_0^{t_o} I_g^2 R e^{-2t/\tau} dt = I_g^2 R \left. \frac{e^{-2t/\tau}}{(-2/\tau)} \right|_0^{t_o}$$

$$= \frac{1}{2} I_g^2 R \tau (1 - e^{-2t_o/\tau}) = \frac{1}{2} I_g^2 L (1 - e^{-2t_o/\tau})$$

$$w_{\text{diss}} = \sigma w(0)$$

$$\therefore \frac{1}{2} L I_g^2 (1 - e^{-2t_o/\tau}) = \tau \left( \frac{1}{2} L I_g^2 \right)$$

$$1 - e^{-2t_o/\tau} = \sigma; \quad e^{2t_o/\tau} = \frac{1}{1 - \sigma}$$


$$\frac{2t_o}{\tau} = \ln \left[ \frac{1}{1 - \sigma} \right]; \quad \frac{R(2t_o)}{L} = \ln[1/(1 - \sigma)]$$

$$R = \frac{L \ln[1/(1 - \sigma)]}{2t_o}$$

[b]  $R = \frac{(30 \times 10^{-3}) \ln[1/0.8]}{30 \times 10^{-6}}$


$$R = 223.14 \Omega$$

P 7.8 [a]  $t < 0$

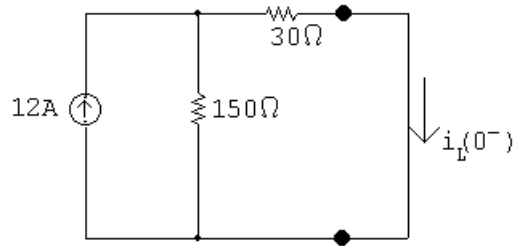

$$i_L(0^-) = \frac{150}{180}(12) = 10 \text{ A}$$

$$t \geq 0$$

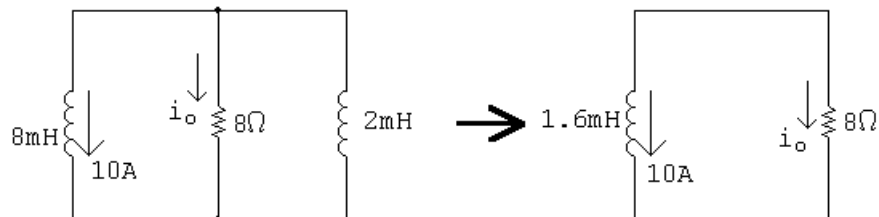

$$\tau = \frac{1.6 \times 10^{-3}}{8} = 200 \times 10^{-6}; \quad 1/\tau = 5000$$

$$i_o = -10e^{-5000t} \text{ A} \quad t \geq 0$$

$$\textbf{[b]} \quad w_{\text{del}} = \frac{1}{2}(1.6 \times 10^{-3})(10)^2 = 80 \text{ mJ}$$

$$\textbf{[c]} \quad 0.95w_{\text{del}} = 76 \text{ mJ}$$


$$\therefore 76 \times 10^{-3} = \int_0^{t_o} 8(100e^{-10,000t}) dt$$

$$\therefore 76 \times 10^{-3} = -80 \times 10^{-3} e^{-10,000t} \Big|_0^{t_o} = 80 \times 10^{-3}(1 - e^{-10,000t_o})$$

$$\therefore e^{-10,000t_o} = 4 \times 10^{-3} \quad \text{so} \quad t_o = 552.1 \mu\text{s}$$

$$\therefore \frac{t_o}{\tau} = \frac{552.1 \times 10^{-6}}{200 \times 10^{-6}} = 2.76 \quad \text{so} \quad t_o \approx 2.76\tau$$


P 7.9 For  $t < 0^+$

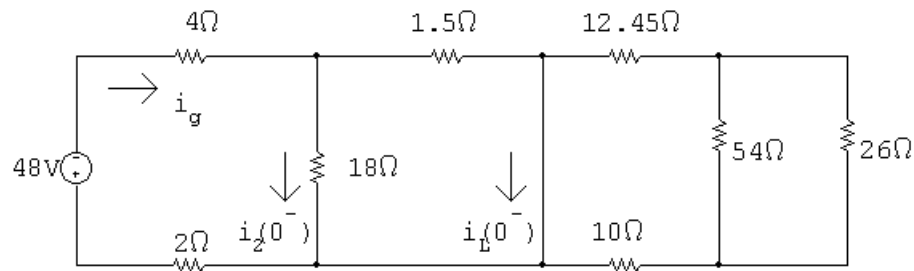

$$i_g = \frac{-48}{6 + (18 \parallel 1.5)} = -6.5 \text{ A}$$

$$i_L(0^-) = \frac{18}{18 + 1.5}(-6.5) = -6 \text{ A} = i_L(0^+)$$

For  $t > 0$

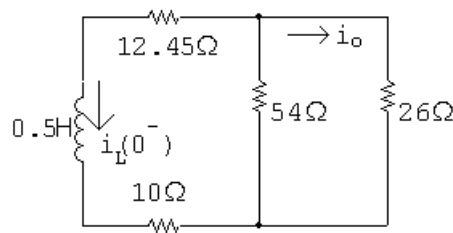

$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.5}{10 + 12.45 + (54 \parallel 26)} = 0.0125 \text{ s}; \quad \frac{1}{\tau} = 80$$

$$i_L(t) = -6e^{-80t} \text{ A}, \quad t \geq 0$$

$$i_o(t) = \frac{54}{80}(-i_L(t)) = \frac{54}{80}(6e^{-80t}) = 4.05e^{-80t} \text{ V}, \quad t \geq 0^+$$



P 7.10 From the solution to Problem 7.9,

$$i_{54\Omega} = \frac{26}{80}(-i_L) = -1.95e^{-80t} \text{ A}$$


$$P_{54\Omega} = 54(i_{54\Omega})^2 = 205.335e^{-160t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{0.0125} 205.335e^{-160t} dt \\ &= \frac{205.335}{-160} e^{-160t} \bigg|_0^{0.0125} \\ &= 1.28(1 - e^{-2}) = 1.11 \text{ J} \end{aligned}$$


$$w_{\text{stored}} = \frac{1}{2}(0.5)(-6)^2 = 9 \text{ mJ}.$$

$$\% \text{ diss} = \frac{1.11}{9} \times 100 = 12.3\%$$

P 7.11 [a]  $t < 0$  :

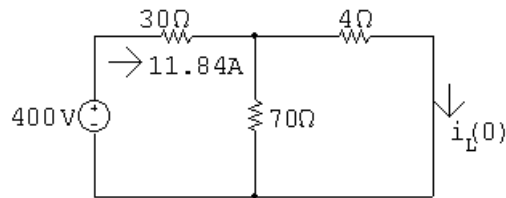

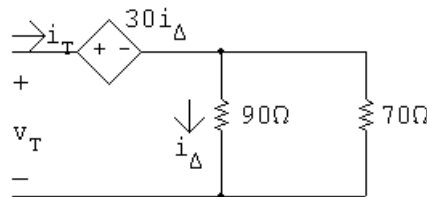
$$i_L(0^-) = i_L(0^+) = \frac{70}{70 + 4}(11.84) = 11.2 \text{ A}$$



$$i_{\Delta} = \frac{70}{160}i_T = 0.4375i_T$$

$$v_T = 30i_{\Delta} + i_T \frac{(90)(70)}{160} = 30(0.4375)i_T + \frac{(90)(70)}{160}i_T = 52.5i_T$$
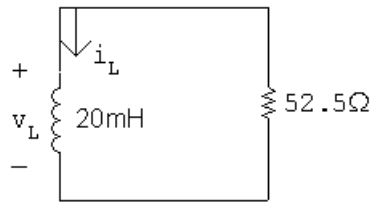
$$\frac{v_T}{i_T} = R_{\text{Th}} = 52.5 \Omega$$




$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{52.5} = \therefore \frac{1}{\tau} = 2625$$

$$i_L = 11.2e^{-2625t} \text{ A}, \quad t \geq 0$$

**[b]**  $v_L = L \frac{di_L}{dt} = 20 \times 10^{-3}(-2625)(11.2e^{-2625t}) = -588e^{-2625t} \text{ V}, \quad t \geq 0^+$

**[c]**

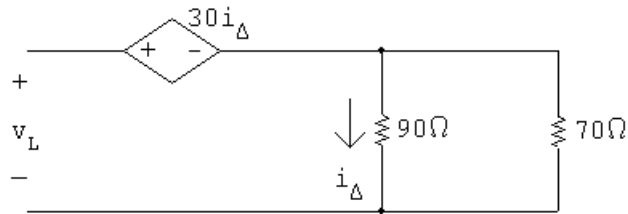

$$v_L = 30i_{\Delta} + 90i_{\Delta} = 120i_{\Delta}$$

$$i_{\Delta} = \frac{v_L}{120} = -4.9e^{-2625t} \text{ A} \quad t \geq 0^+$$


**P 7.12**  $w(0) = \frac{1}{2}(20 \times 10^{-3})(11.2)^2 = 1254.4 \text{ mJ}$

$$p_{30i_{\Delta}} = -30i_{\Delta}i_L = -30(-4.9e^{-2625t})(11.2e^{-2625t}) = 1646.4e^{-5250t} \text{ W}$$


$$w_{30i_{\Delta}} = \int_0^{\infty} 1646.4e^{-5250t} dt = 1646.4 \frac{e^{-5250t}}{-5250} \Big|_0^{\infty} = 313.6 \text{ mJ}$$

$$\% \text{ dissipated} = \frac{313.6}{1254.4}(100) = 25\%$$


**P 7.13**  $t < 0$

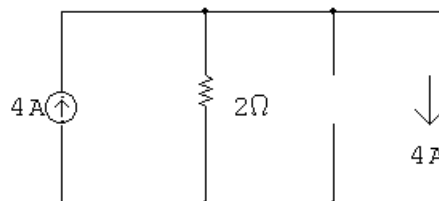

$$i_L(0^-) = i_L(0^+) = 4 \text{ A}$$

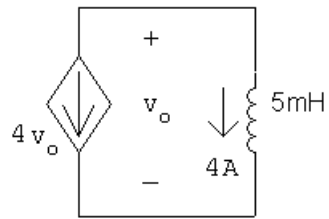
$t > 0$ 

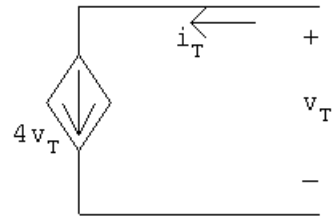Find Thévenin resistance seen by inductor




$$i_T = 4v_T; \quad \frac{v_T}{i_T} = R_{Th} = \frac{1}{4} = 0.25 \, \Omega$$
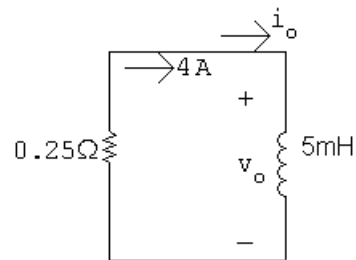
$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{0.25} = 20 \, \text{ms}; \quad 1/\tau = 50$$




$$i_o = 4e^{-50t} \, \text{A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (5 \times 10^{-3})(-200e^{-50t}) = -e^{-50t} \, \text{V}, \quad t \geq 0^+$$

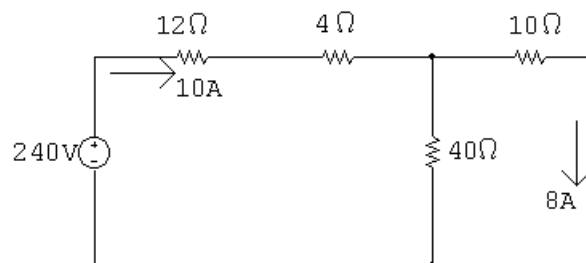P 7.14  $t < 0$ :

$$i_L(0^+) = 8 \, \text{A}$$

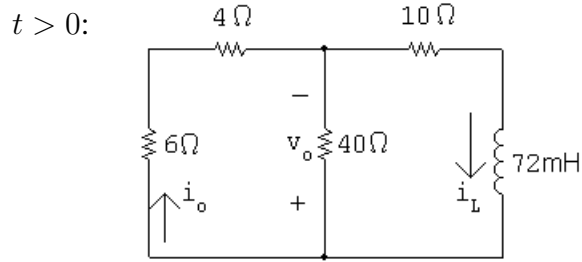

$$R_e = \frac{(10)(40)}{50} + 10 = 18 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{0.072}{18} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 8e^{-250t} \text{ A}$$

$$\begin{aligned} \therefore v_o &= -10i_L - 0.072 \frac{di_L}{dt} = -80e^{-250t} + 144e^{-250t} \\ &= 64e^{-250t} \text{ A} \quad t \geq 0^+ \end{aligned}$$

P 7.15  $w(0) = \frac{1}{2}(72 \times 10^{-3})(8)^2 = 2304 \text{ mJ}$

$$p_{40\Omega} = \frac{v_o^2}{40} = \frac{64^2}{40}e^{-500t} = 102.4e^{-500t} \text{ W}$$

$$w_{40\Omega} = \int_0^\infty 102.4e^{-500t} dt = 204.8 \text{ mJ}$$

$$\% \text{diss} = \frac{204.8}{2304}(100) = 8.89\%$$

P 7.16 [a]  $v_o(t) = v_o(0^+)e^{-t/\tau}$

$$\therefore v_o(0^+)e^{-1 \times 10^{-3}/\tau} = 0.5v_o(0^+)$$

$$\therefore e^{1 \times 10^{-3}/\tau} = 2$$

$$\therefore \tau = \frac{L}{R} = \frac{1 \times 10^{-3}}{\ln 2}$$

$$\therefore L = \frac{10 \times 10^{-3}}{\ln 2} = 14.43 \text{ mH}$$

**[b]**  $v_o(0^+) = -10i_L(0^+) = -10(1/10)30 \times 10^{-3} = -30 \text{ mV}$

$$\therefore v_o = -0.03e^{-t/\tau} \text{ V}, \quad t \geq 0^+$$

$$p_{10\Omega} = \frac{v_o^2}{10} = 9 \times 10^{-5} e^{-2t/\tau}$$

$$\begin{aligned} w_{10\Omega}(1 \text{ ms}) &= \int_{0^+}^{10^{-3}} 9 \times 10^{-5} e^{-2t/\tau} dt \\ &= 4.5\tau \times 10^{-5} (1 - e^{-2(0.001)/\tau}) \end{aligned}$$


$$\tau = \frac{1}{1000 \ln 2}$$

$$\therefore w_{10\Omega}(1 \text{ ms}) = 48.69 \text{ nJ}$$


$$w_L(0) = \frac{1}{2} L i_L^2(0) = \frac{1}{2} (14.43 \times 10^{-3}) (3 \times 10^{-3})^2 = 64.92 \text{ nJ}$$

$$\% \text{dissipated in } 1 \text{ ms} = \frac{48.69}{64.92} (100) = 75\%$$

**P 7.17 [a]**  $t < 0$ :

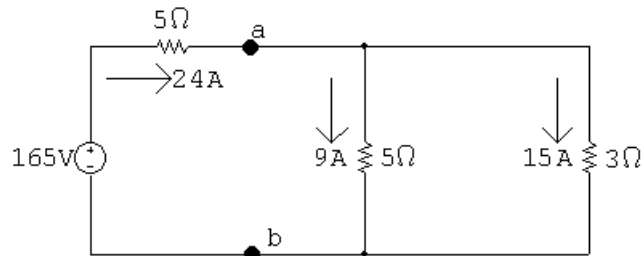


$t = 0^+$ :

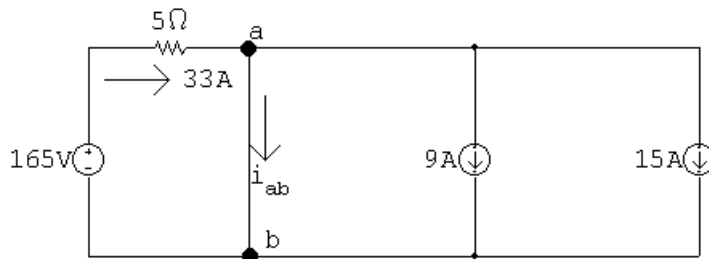


$$33 = i_{ab} + 9 + 15, \quad i_{ab} = 9 \text{ A}, \quad t = 0^+$$

**[b]** At  $t = \infty$ :

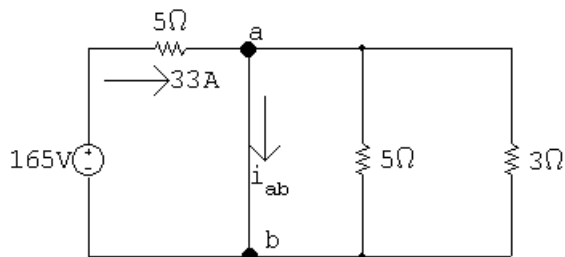
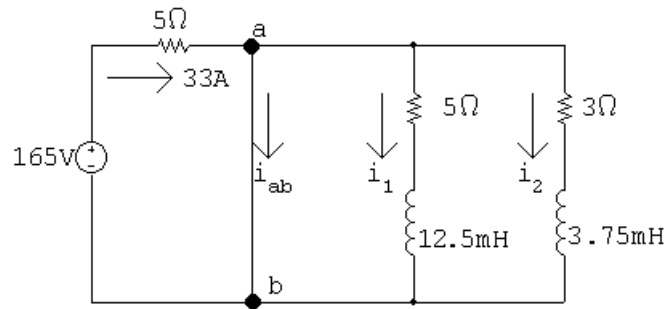
$$i_{ab} = 165/5 = 33 \text{ A}, \quad t = \infty$$



$$\text{[c]} \quad i_1(0) = 9, \quad \tau_1 = \frac{12.5 \times 10^{-3}}{5} = 2.5 \text{ ms}$$

$$i_2(0) = 15, \quad \tau_2 = \frac{3.75 \times 10^{-3}}{3} = 1.25 \text{ ms}$$

$$i_1(t) = 9e^{-400t} \text{ A}, \quad t \geq 0$$

$$i_2(t) = 15e^{-800t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 33 - 9e^{-400t} - 15e^{-800t} \text{ A}, \quad t \geq 0^+$$

$$33 - 9e^{-400t} - 15e^{-800t} = 19$$

$$14 = 9e^{-400t} + 15e^{-800t}$$


$$\text{Let } x = e^{-400t} \quad \therefore \quad x^2 = e^{-800t}$$

Substituting,

$$15x^2 + 9x - 14 = 0 \quad \text{so} \quad x = 0.7116 = e^{-400t}$$

$$\therefore \quad t = \frac{[\ln(1/0.7116)]}{400} = 850.6 \mu\text{s}$$


P 7.18 [a]  $t < 0$

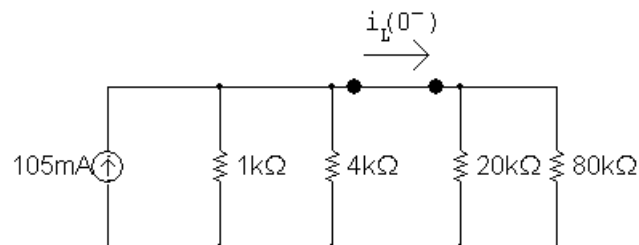

$$1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$$


$$20 \text{ k}\Omega \parallel 80 \text{ k}\Omega = 16 \text{ k}\Omega$$
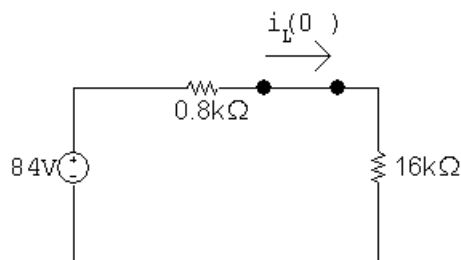
$$(105 \times 10^{-3})(0.8 \times 10^3) = 84 \text{ V}$$



$$i_L(0^-) = \frac{84}{16,800} = 5 \text{ mA}$$

$$t > 0$$

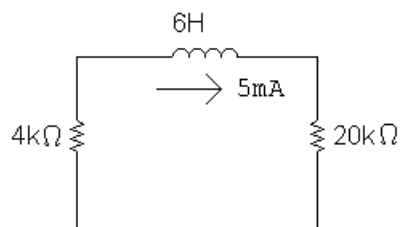

$$\tau = \frac{L}{R} = \frac{6}{24} \times 10^{-3} = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L(t) = 5e^{-4000t} \text{ mA}, \quad t \geq 0$$

$$p_{4k} = 25 \times 10^{-6} e^{-8000t} (4000) = 0.10e^{-8000t} \text{ W}$$

$$w_{\text{diss}} = \int_0^t 0.10e^{-8000x} dx = 12.5 \times 10^{-6} [1 - e^{-8000t}] \text{ J}$$

$$w(0) = \frac{1}{2}(6)(25 \times 10^{-6}) = 75 \mu\text{J}$$

$$0.10w(0) = 7.5 \mu\text{J}$$

$$12.5(1 - e^{-8000t}) = 7.5; \quad \therefore e^{8000t} = 2.5$$


$$t = \frac{\ln 2.5}{8000} = 114.54 \mu\text{s}$$

$$\textbf{[b]} \quad w_{\text{diss}}(\text{total}) = 75(1 - e^{-8000t}) \mu\text{J}$$


$$w_{\text{diss}}(114.54 \mu\text{s}) = 45 \mu\text{J}$$

$$\% = (45/75)(100) = 60\%$$


P 7.19 [a]  $t < 0$ :

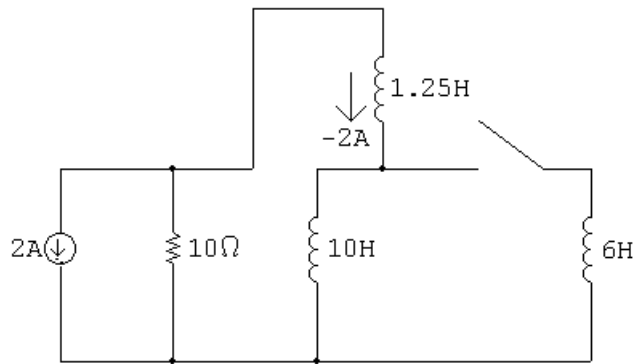

$t = 0^+$ :

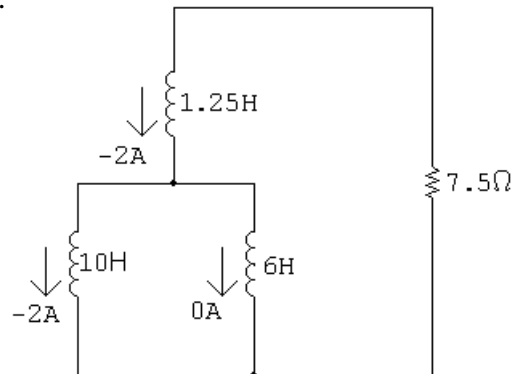


$t > 0$ :

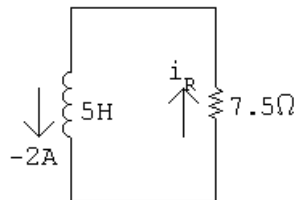

$$i_R = -2e^{-t/\tau} \text{ A}; \quad \tau = \frac{L}{R} = \frac{5}{7.5} = 666.67 \text{ ms} \quad \therefore \frac{1}{\tau} = 1.5$$

$$i_R = -2e^{-1.5t} \text{ A}$$

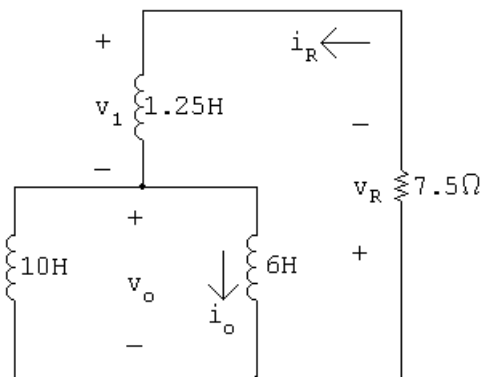

$$v_R = (7.5)(-2e^{-1.5t}) = -15e^{-1.5t} \text{ V}$$



$$v_1 = 1.25[(-1.5)(-2e^{-1.5t})] = 3.75e^{-1.5t} \text{ V},$$

$$v_o = -v_1 - v_R = 11.25e^{-1.5t} \text{ V} \quad t \geq 0^+$$

$$\text{[b]} \quad i_o = \frac{1}{6} \int_0^t 11.25e^{-1.5x} dx + 0 = 1.25 - 1.25e^{-1.5t} \text{ A} \quad t \geq 0$$

P 7.20 [a] From the solution to Problem 7.19,

$$i_R = -2e^{-1.5t} \text{ A}$$

$$p_R = (-2e^{-1.5t})^2(7.5) = 30e^{-3t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^\infty 30e^{-3t} dt \\ &= 30 \left. \frac{e^{-3t}}{-3} \right|_0^\infty = 10 \text{ J} \end{aligned}$$


$$\text{[b]} \quad w_{\text{trapped}} = \frac{1}{2}(10)(-1.25)^2 + \frac{1}{2}(6)(1.25)^2 = 12.5 \text{ J}$$

$$\text{CHECK: } w(0) = \frac{1}{2}(1.25)(2)^2 + \frac{1}{2}(10)(2)^2 = 22.5 \text{ J}$$

$$\therefore w(0) = w_{\text{diss}} + w_{\text{trapped}}$$


P 7.21 [a]  $v_1(0^-) = v_1(0^+) = 40 \text{ V}$   $v_2(0^+) = 0$
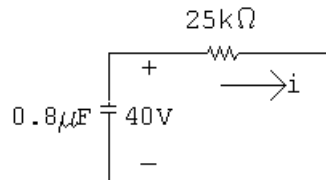
$$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$$



$$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$
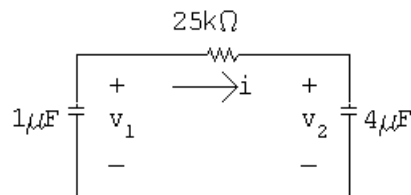
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$\textbf{[b]} \quad w(0) = \frac{1}{2}(10^{-6})(40)^2 = 800 \mu\text{J}$$

$$\textbf{[c]} \quad w_{\text{trapped}} = \frac{1}{2}(10^{-6})(8)^2 + \frac{1}{2}(4 \times 10^{-6})(8)^2 = 160 \mu\text{J}.$$

The energy dissipated by the 25 k $\Omega$  resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors (final voltage on the equivalent capacitor is zero):

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(40)^2 = 640 \mu\text{J}.$$

$$\text{Check:} \quad w_{\text{trapped}} + w_{\text{diss}} = 160 + 640 = 800 \mu\text{J}; \quad w(0) = 800 \mu\text{J}.$$

P 7.22 **[a]** Calculate the initial voltage drop across the capacitor:

$$v(0) = (2.7 \text{ k} \parallel 3.3 \text{ k})(40 \text{ mA}) = (1485)(40 \times 10^{-3}) = 59.4 \text{ V}$$

The equivalent resistance seen by the capacitor is

$$R_e = 3 \text{ k} \parallel (2.4 \text{ k} + 3.6 \text{ k}) = 3 \text{ k} \parallel 6 \text{ k} = 2 \text{ k}\Omega$$

$$\tau = R_e C = (2000)(0.5) \times 10^{-6} = 1000 \mu\text{s}; \quad \frac{1}{\tau} = 1000$$

$$v = v(0)e^{-t/\tau} = 59.4e^{-1000t} \text{ V} \quad t \geq 0$$

$$i_o = \frac{v}{2.4 \text{ k} + 3.6 \text{ k}} = 9.9e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$\textbf{[b]} \quad w(0) = \frac{1}{2}(0.5 \times 10^{-6})(59.4)^2 = 882.09 \mu\text{J}$$

$$i_{3k} = \frac{59.4e^{-1000t}}{3000} = 19.8e^{-1000t} \text{ mA}$$

$$p_{3k} = [(19.8 \times 10^{-3})e^{-1000t}]^2(3000) = 1.176e^{-2000t}$$

$$w_{3k}(500 \mu\text{s}) = 1.176 \frac{e^{-2000x}}{-2000} \bigg|_0^{500 \times 10^{-6}} = \frac{1.176}{-2000}(e^{-1} - 1) = 371.72 \mu\text{J}$$

$$\% = \frac{371.72}{882.09} \times 100 = 42.14\%$$

P 7.23 **[a]**  $R = \frac{v}{i} = 4 \text{ k}\Omega$


$$\textbf{[b]} \quad \frac{1}{\tau} = \frac{1}{RC} = 25; \quad C = \frac{1}{(25)(4 \times 10^3)} = 10 \mu\text{F}$$

$$\textbf{[c]} \quad \tau = \frac{1}{25} = 40 \text{ ms}$$

$$\textbf{[d]} \quad w(0) = \frac{1}{2}(10 \times 10^{-6})(48)^2 = 11.52 \text{ mJ}$$


$$\begin{aligned}
 \text{[e]} \quad w_{\text{diss}}(60 \text{ ms}) &= \int_0^{0.06} \frac{v^2}{R} dt = \int_0^{0.06} \frac{(48e^{-25t})^2}{(4 \times 10^3)} dt \\
 &= 0.576 \frac{e^{-50t}}{-50} \bigg|_0^{0.06} = -5.74 \times 10^{-4} + 0.01152 = 10.95 \text{ mJ}
 \end{aligned}$$

P 7.24 [a]  $t < 0$ :

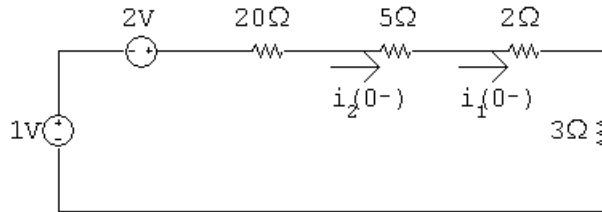

$$i_1(0^-) = i_2(0^-) = \frac{3 \text{ V}}{30 \Omega} = 100 \text{ mA}$$

[b]  $t > 0$ :

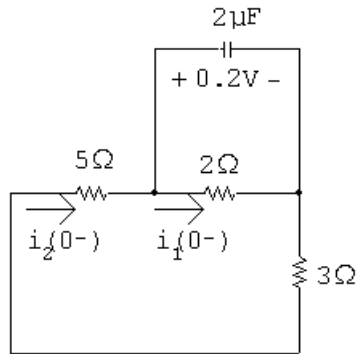

$$i_1(0^+) = \frac{0.2}{2} = 100 \text{ mA}$$

$$i_2(0^+) = \frac{-0.2}{8} = -25 \text{ mA}$$

[c] Capacitor voltage cannot change instantaneously, therefore,

$$i_1(0^-) = i_1(0^+) = 100 \text{ mA}$$

[d] Switching can cause an instantaneous change in the current in a resistive branch. In this circuit

$$i_2(0^-) = 100 \text{ mA} \quad \text{and} \quad i_2(0^+) = -25 \text{ mA}$$


[e]  $v_c = 0.2e^{-t/\tau} \text{ V}, \quad t \geq 0 \quad R_e = 2 \parallel (5 + 3) = 1.6 \Omega$

$$\tau = 1.6(2 \times 10^{-6}) = 3.2 \times 10^{-6} \text{ s}$$

$$v_c = 0.2e^{-312,500t} \text{ V}, \quad t \geq 0$$


$$i_1 = \frac{v_c}{2} = 0.1e^{-312,500t} \text{ A}, \quad t \geq 0$$

[f]  $i_2 = \frac{-v_c}{8} = -25e^{-312,500t} \text{ mA}, \quad t \geq 0^+$

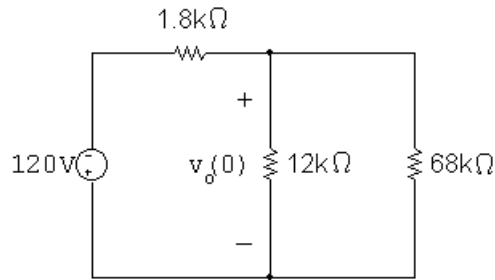P 7.25 [a]  $t < 0$ :

$$R_e = 12 \text{ k} \parallel 68 \text{ k} = 10.2 \text{ k}\Omega$$

$$v_o(0) = \frac{10,200}{10,200 + 1800}(-120) = -102 \text{ V}$$

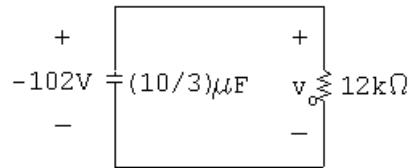 $t > 0$ :

$$\tau = [(10/3) \times 10^{-6}](12,000) = 40 \text{ ms}; \quad \frac{1}{\tau} = 25$$

$$v_o = -102e^{-25t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12,000} = 867 \times 10^{-3} e^{-50t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{12 \times 10^{-3}} 867 \times 10^{-3} e^{-50t} dt \\ &= 17.34 \times 10^{-3} (1 - e^{-50(12 \times 10^{-3})}) = 7.82 \text{ mJ} \end{aligned}$$


$$\text{[b]} \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{10}{3}\right) (102)^2 \times 10^{-6} = 17.34 \text{ mJ}$$

$$0.75w(0) = 13 \text{ mJ}$$

$$\int_0^{t_o} 867 \times 10^{-3} e^{-50x} dx = 13 \times 10^{-3}$$

$$\therefore 1 - e^{-50t_o} = 0.75; \quad e^{50t_o} = 4; \quad \text{so } t_o = 27.73 \text{ ms}$$

P 7.26 [a]

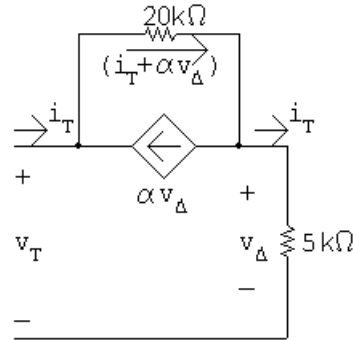

$$v_T = 20 \times 10^3(i_T + \alpha v_\Delta) + 5 \times 10^3 i_T$$

$$v_\Delta = 5 \times 10^3 i_T$$

$$v_T = 25 \times 10^3 i_T + 20 \times 10^3 \alpha (5 \times 10^3 i_T)$$


$$R_{Th} = 25,000 + 100 \times 10^6 \alpha$$

$$\tau = R_{Th} C = 40 \times 10^{-3} = R_{Th} (0.8 \times 10^{-6})$$


$$R_{Th} = 50 \text{ k}\Omega = 25,000 + 100 \times 10^6 \alpha$$

$$\alpha = \frac{25,000}{100 \times 10^6} = 2.5 \times 10^{-4} \text{ A/V}$$

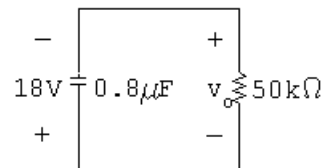**[b]**  $v_o(0) = (-5 \times 10^{-3})(3600) = -18 \text{ V} \quad t < 0$   
 $t > 0$ :


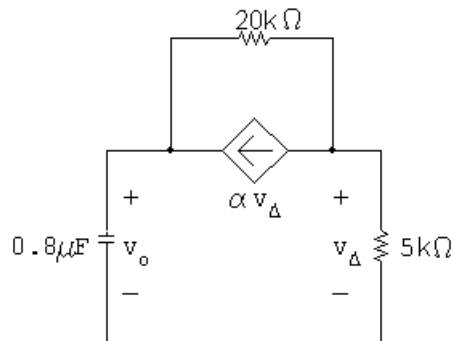
$$v_o = -18e^{-25t} \text{ V}, \quad t \geq 0$$




$$\frac{v_\Delta}{5000} + \frac{v_\Delta - v_o}{20,000} + 2.5 \times 10^{-4} v_\Delta = 0$$

$$4v_{\Delta} + v_{\Delta} - v_o + 5v_{\Delta} = 0$$

$$\therefore v_{\Delta} = \frac{v_o}{10} = -1.8e^{-25t} \text{ V}, \quad t \geq 0^+$$

P 7.27 [a]

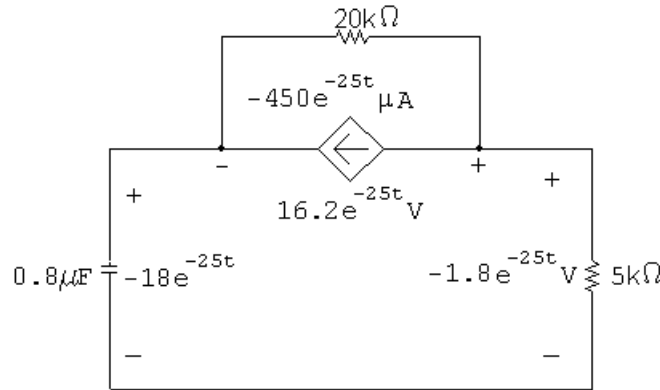

$$p_{ds} = (16.2e^{-25t})(-450 \times 10^{-6}e^{-25t}) = -7290 \times 10^{-6}e^{-50t} \text{ W}$$

$$w_{ds} = \int_0^{\infty} p_{ds} dt = -145.8 \mu\text{J}.$$

$\therefore$  dependent source is delivering  $145.8 \mu\text{J}$

$$\text{[b]} \quad w_{5k} = \int_0^{\infty} (5000)(0.36 \times 10^{-3}e^{-25t})^2 dt = 648 \times 10^{-6} \int_0^{\infty} e^{-50t} dt = 12.96 \mu\text{J}$$


$$w_{20k} = \int_0^{\infty} \frac{(16.2e^{-25t})^2}{20,000} dt = 13,122 \times 10^{-6} \int_0^{\infty} e^{-50t} dt = 262.44 \mu\text{J}$$


$$w_c(0) = \frac{1}{2}(0.8 \times 10^{-6})(18)^2 = 129.6 \mu\text{J}$$

$$\sum w_{\text{diss}} = 12.96 + 262.44 = 275.4 \mu\text{J}$$


$$\sum w_{\text{dev}} = 145.8 + 129.6 = 275.4 \mu\text{J}.$$

P 7.28  $t < 0$

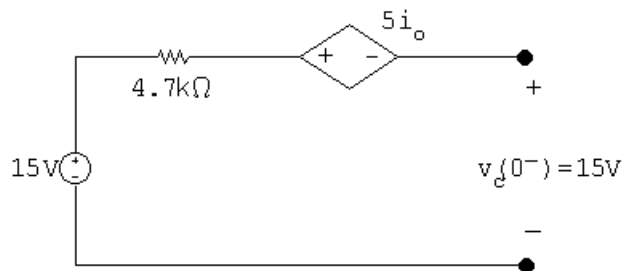

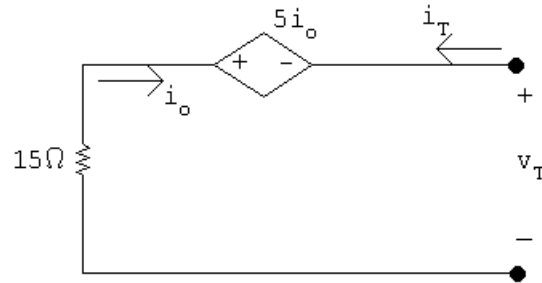$t > 0$ 
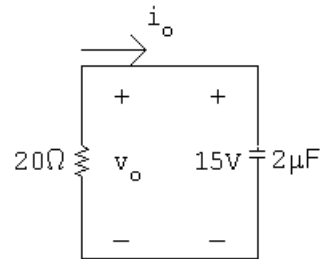
$$v_T = -5i_o - 15i_o = -20i_o = 20i_T \quad \therefore \quad R_{Th} = \frac{v_T}{i_T} = 20 \, \Omega$$




$$\tau = RC = 40 \, \mu s; \quad \frac{1}{\tau} = 25,000$$

$$v_o = 15e^{-25,000t} \, \text{V}, \quad t \geq 0$$

$$i_o = -\frac{v_o}{20} = -0.75e^{-25,000t} \, \text{A}, \quad t \geq 0^+$$

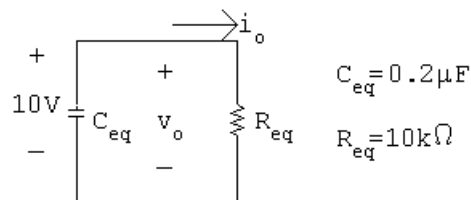P 7.29 [a] The equivalent circuit for  $t > 0$ :



$$\tau = 2 \, \text{ms}; \quad 1/\tau = 500$$

$$v_o = 10e^{-500t} \, \text{V}, \quad t \geq 0$$

$$i_o = e^{-500t} \, \text{mA}, \quad t \geq 0^+$$

$$i_{24k\Omega} = e^{-500t} \left( \frac{16}{40} \right) = 0.4e^{-500t} \, \text{mA}, \quad t \geq 0^+$$

$$p_{24k\Omega} = (0.16 \times 10^{-6} e^{-1000t})(24,000) = 3.84e^{-1000t} \, \text{mW}$$

$$w_{24k\Omega} = \int_0^\infty 3.84 \times 10^{-3} e^{-1000t} dt = -3.84 \times 10^{-6} (0 - 1) = 3.84 \, \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.25 \times 10^{-6})(40)^2 + \frac{1}{2}(1 \times 10^{-6})(50)^2 = 1.45 \text{ mJ}$$

$$\% \text{ diss } (24 \text{ k}\Omega) = \frac{3.84 \times 10^{-6}}{1.45 \times 10^{-3}} \times 100 = 0.26\%$$

$$\textbf{[b]} \quad p_{400\Omega} = 400(1 \times 10^{-3}e^{-500t})^2 = 0.4 \times 10^{-3}e^{-1000t}$$

$$w_{400\Omega} = \int_0^\infty p_{400} dt = 0.40 \mu\text{J}$$

$$\% \text{ diss } (400\Omega) = \frac{0.4 \times 10^{-6}}{1.45 \times 10^{-3}} \times 100 = 0.03\%$$

$$i_{16k\Omega} = e^{-500t} \left( \frac{24}{40} \right) = 0.6e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{16k\Omega} = (0.6 \times 10^{-3}e^{-500t})^2(16,000) = 5.76 \times 10^{-3}e^{-1000t} \text{ W}$$

$$w_{16k\Omega} = \int_0^\infty 5.76 \times 10^{-3}e^{-1000t} dt = 5.76 \mu\text{J}$$

$$\% \text{ diss } (16\text{k}\Omega) = 0.4\%$$

$$\textbf{[c]} \quad \sum w_{\text{diss}} = 3.84 + 5.76 + 0.4 = 10 \mu\text{J}$$

$$w_{\text{trapped}} = w(0) - \sum w_{\text{diss}} = 1.45 \times 10^{-3} - 10 \times 10^{-6} = 1.44 \text{ mJ}$$


$$\% \text{ trapped} = \frac{1.44}{1.45} \times 100 = 99.31\%$$

$$\text{Check: } 0.26 + 0.03 + 0.4 + 99.31 = 100\%$$

$$\text{P 7.30} \quad \textbf{[a]} \quad C_e = \frac{(2+1)6}{2+1+6} = 2 \mu\text{F}$$

$$v_o(0) = -5 + 30 = 25 \text{ V}$$
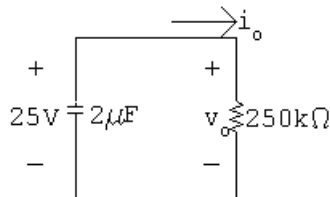
$$\tau = (2 \times 10^{-6})(250 \times 10^3) = 0.5 \text{ s}; \quad \frac{1}{\tau} = 2$$



$$v_o = 25e^{-2t} \text{ V}, \quad t > 0^+$$



$$\text{[b]} \quad w_o = \frac{1}{2}(3 \times 10^{-6})(30)^2 + \frac{1}{2}(6 \times 10^{-6})(5)^2 = 1425 \mu\text{J}$$

$$w_{\text{diss}} = \frac{1}{2}(2 \times 10^{-6})(25)^2 = 625 \mu\text{J}$$

$$\% \text{ diss} = \frac{1425 - 625}{1425} \times 100 = 56.14\%$$

$$\text{[c]} \quad i_o = \frac{v_o}{250 \times 10^{-3}} = 100e^{-2t} \mu\text{A}$$

$$\begin{aligned} v_1 &= -\frac{1}{6 \times 10^{-6}} \int_0^t 100 \times 10^{-6} e^{-2x} dx - 5 = -16.67 \int_0^t e^{-2x} dx - 5 \\ &= -16.67 \left. \frac{e^{-2x}}{-2} \right|_0^t - 5 = 8.33e^{-2t} - 13.33 \text{ V} \quad t \geq 0 \end{aligned}$$


$$\text{[d]} \quad v_1 + v_2 = v_o$$

$$v_2 = v_o - v_1 = 25e^{-2t} - 8.33e^{-2t} + 13.33 = 16.67e^{-2t} + 13.33 \text{ V} \quad t \geq 0$$

$$\text{[e]} \quad w_{\text{trapped}} = \frac{1}{2}(6 \times 10^{-6})(13.33)^2 + \frac{1}{2}(3 \times 10^{-6})(13.33)^2 = 800 \mu\text{J}$$

$$w_{\text{diss}} + w_{\text{trapped}} = 625 + 800 = 1425 \mu\text{J} \quad (\text{check})$$

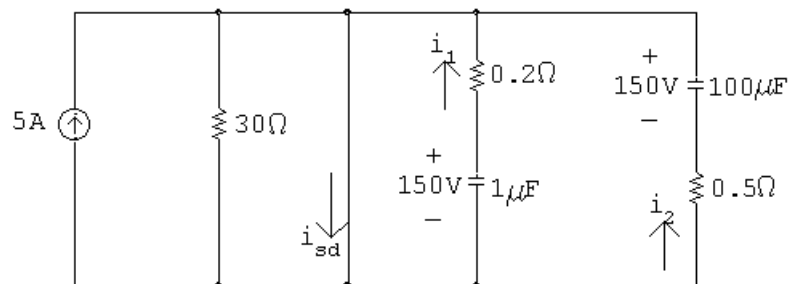P 7.31 [a] At  $t = 0^-$  the voltage on each capacitor will be  $150 \text{ V}$  ( $5 \times 30$ ), positive at the upper terminal. Hence at  $t \geq 0^+$  we have



$$\therefore i_{sd}(0^+) = 5 + \frac{150}{0.2} + \frac{150}{0.5} = 1055 \text{ A}$$

At  $t = \infty$ , both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 5 \text{ A}$$

$$\text{[b]} \quad i_{sd}(t) = 5 + i_1(t) + i_2(t)$$

$$\tau_1 = 0.2(10^{-6}) = 0.2 \mu\text{s}$$


$$\tau_2 = 0.5(100 \times 10^{-6}) = 50 \mu\text{s}$$

$$\therefore i_1(t) = 750e^{-5 \times 10^6 t} \text{ A}, \quad t \geq 0^+$$

$$i_2(t) = 300e^{-20,000t} \text{ A}, \quad t \geq 0$$

$$\therefore i_{sd} = 5 + 750e^{-5 \times 10^6 t} + 300e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

P 7.32 [a]  $t < 0$ :

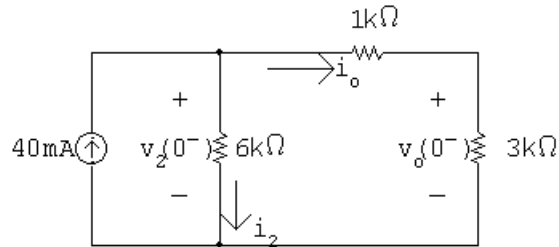


$$i_o(0^-) = \frac{6000}{6000 + 4000}(40 \text{ m}) = 24 \text{ mA}$$

$$v_o(0^-) = (3000)(24 \text{ m}) = 72 \text{ V}$$


$$i_2(0^-) = 40 - 24 = 16 \text{ mA}$$

$$v_2(0^-) = (6000)(16 \text{ m}) = 96 \text{ V}$$

$t > 0$

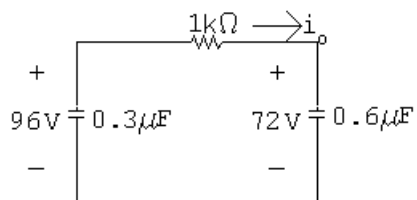

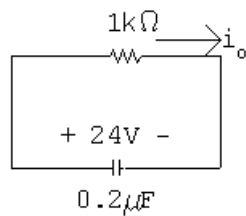
$$\tau = RC = (1000)(0.2 \times 10^{-6}) = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{24}{1 \times 10^3} e^{-t/\tau} = 24e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

[b]

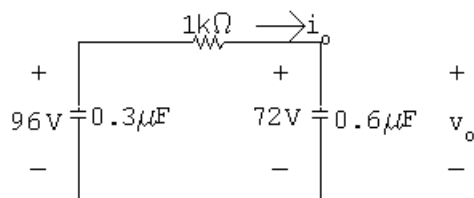

$$\begin{aligned}
 v_o &= \frac{1}{0.6 \times 10^{-6}} \int_0^t 24 \times 10^{-3} e^{-5000x} dx + 72 \\
 &= (40,000) \frac{e^{-5000x}}{-5000} \bigg|_0^t + 72 \\
 &= -8e^{-5000t} + 8 + 72 \\
 v_o &= [-8e^{-5000t} + 80] \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\text{[c]} \quad w_{\text{trapped}} = (1/2)(0.3 \times 10^{-6})(80)^2 + (1/2)(0.6 \times 10^{-6})(80)^2$$

$$w_{\text{trapped}} = 2880 \mu\text{J}.$$

Check:


$$w_{\text{diss}} = \frac{1}{2}(0.2 \times 10^{-6})(24)^2 = 57.6 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.3 \times 10^{-6})(96)^2 + \frac{1}{2}(0.6 \times 10^{-6})(72)^2 = 2937.6 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$


$$2880 + 57.6 = 2937.6 \quad \text{OK.}$$

P 7.33 [a]  $t < 0$

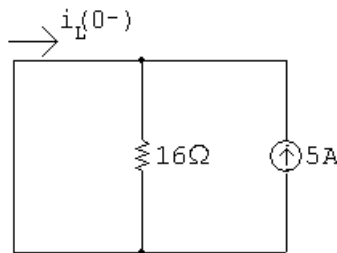

$$i_L(0^-) = -5 \text{ A}$$

$t > 0$

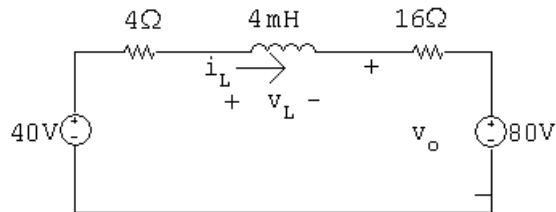

$$i_L(\infty) = \frac{40 - 80}{4 + 16} = -2 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{4 \times 10^{-3}}{4 + 16} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$

$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -2 + (-5 + 2)e^{-5000t} = -2 - 3e^{-5000t} \text{ A}, \quad t \geq 0$$


$$v_o = 16i_L + 80 = 16(-2 - 3e^{-5000t}) + 80 = 48 - 48e^{-5000t} \text{ V}, \quad t \geq 0^+$$

**[b]**  $v_L = L \frac{di_L}{dt} = 4 \times 10^{-3}(-5000)[-3e^{-5000t}] = 60e^{-5000t} \text{ V}, \quad t \geq 0^+$

$$v_L(0^+) = 60 \text{ V}$$


From part (a)  $v_o(0^+) = 0 \text{ V}$

Check: at  $t = 0^+$  the circuit is:

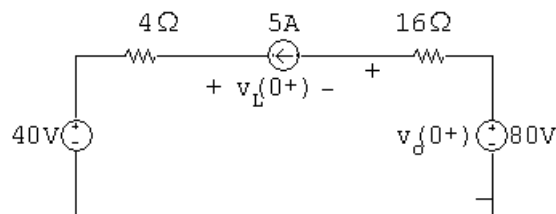

$$v_o(0^+) = 40 + (5 \text{ A})(4 \Omega) = 60 \text{ V}, \quad v_o(0^+) = 80 - (16 \Omega)(5 \text{ A}) = 0 \text{ V}$$

P 7.34 **[a]**  $t < 0$

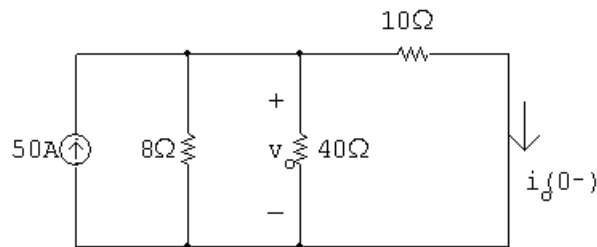

KVL equation at the top node:


$$50 = \frac{v_o}{8} + \frac{v_o}{40} + \frac{v_o}{10}$$

Multiply by 40 and solve:

$$2000 = (5 + 1 + 4)v_o; \quad v_o = 200 \text{ V}$$

$$\therefore i_o(0^-) = \frac{v_o}{10} = 200/10 = 20 \text{ A}$$

$t > 0$

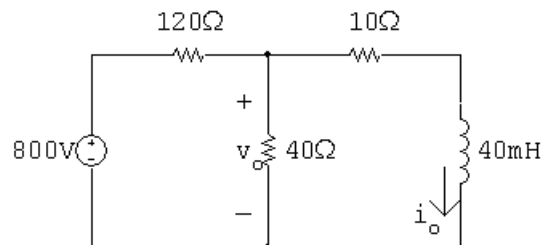


Use voltage division to find the Thévenin voltage:

$$V_{Th} = v_o = \frac{40}{40 + 120}(800) = 200 \text{ V}$$

Remove the voltage source and make series and parallel combinations of resistors to find the equivalent resistance:

$$R_{Th} = 10 + 120 \parallel 40 = 10 + 30 = 40 \Omega$$

The simplified circuit is:

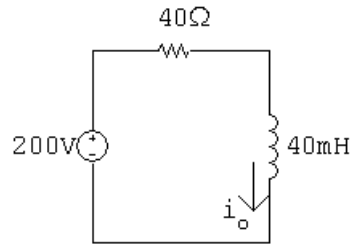


$$\tau = \frac{L}{R} = \frac{40 \times 10^{-3}}{40} = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$i_o(\infty) = \frac{200}{40} = 5 \text{ A}$$

$$\begin{aligned} \therefore i_o &= i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} \\ &= 5 + (20 - 5)e^{-1000t} = 5 + 15e^{-1000t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_o &= 10i_o + L \frac{di_o}{dt} \\ &= 10(5 + 15e^{-1000t}) + 0.04(-1000)(15e^{-1000t}) \\ &= 50 + 150e^{-1000t} - 600e^{-1000t} \\ v_o &= 50 - 450e^{-1000t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

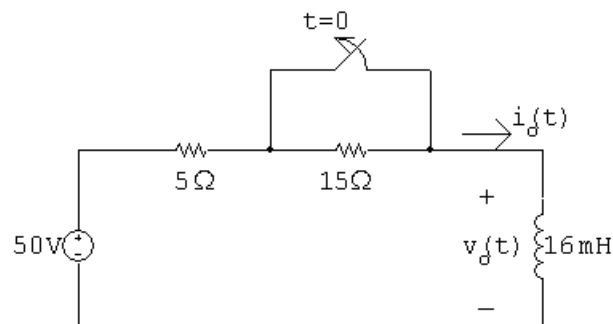P 7.35 After making a Thévenin equivalent we have



For  $t < 0$ , the  $15 \Omega$  resistor is bypassed:

$$i_o(0^-) = i_o(0^+) = 50/5 = 10 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{16 \times 10^{-3}}{5 + 15} = 8 \times 10^{-4}; \quad \frac{1}{\tau} = 1250$$

$$i(\infty) = \frac{V}{R_{\text{eq}}} = \frac{50}{5 + 15} = 2.5 \text{ A}$$

$$i_o = i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} = 2.5 + (10 - 2.5)e^{-1250t} = 2.5 + 7.5e^{-1250t} \text{ A}, t \geq 0$$

$$v_o = L \frac{di_o}{dt} = 16 \times 10^{-3}(-1250)(7.5e^{-1250t}) = -150e^{-1250t} \text{ V}, \quad t \geq 0^+$$

P 7.36 [a]  $v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-(R_1 + R_2)/L t} \text{ V}, \quad t \geq 0^+$$

[b]  $v_o = -(10)(15)e^{-\frac{(5+15)}{0.016}t} = -150e^{-1250t} \text{ V}, \quad t \geq 0^+$

[c]  $v_o(0^+) \rightarrow \infty$ , and the duration of  $v_o(t) \rightarrow \text{zero}$

[d]  $v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$

Therefore  $i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[ I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-(R_1 + R_2)/L t}$

$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-(R_1 + R_2)/L t}$$

Therefore  $v_{sw} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-(R_1 + R_2)/L t}, \quad t \geq 0^+$

[e]  $|v_{sw}(0^+)| \rightarrow \infty; \quad \text{duration} \rightarrow 0$

P 7.37 Opening the inductive circuit causes a very large voltage to be induced across the inductor  $L$ . This voltage also appears across the switch (part [e] of Problem 7.36) causing the switch to arc over. At the same time, the large voltage across  $L$  damages the meter movement.

P 7.38 [a] From Eqs. (7.35) and (7.42)

$$i = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-(R/L)t}$$

$$v = (V_s - I_o R) e^{-(R/L)t}$$

$$\therefore \frac{V_s}{R} = 4; \quad I_o - \frac{V_s}{R} = 4$$

$$V_s - I_o R = -80; \quad \frac{R}{L} = 40$$

$$\therefore I_o = 4 + \frac{V_s}{R} = 8 \text{ A}$$

Now since  $V_s = 4R$  we have

$$4R - 8R = -80; \quad R = 20 \Omega$$

$$V_s = 80 \text{ V}; \quad L = \frac{R}{40} = 0.5 \text{ H}$$

$$\text{[b]} \quad i = 4 + 4e^{-40t}; \quad i^2 = 16 + 32e^{-40t} + 16e^{-80t}$$

$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.5) [16 + 32e^{-40t} + 16e^{-80t}] = 4 + 8e^{-40t} + 4e^{-80t}$$

$$\therefore 4 + 8e^{-40t} + 4e^{-80t} = 9 \quad \text{or} \quad e^{-80t} + 2e^{-40t} - 1.25 = 0$$


Let  $x = e^{-40t}$ :

$$x^2 + 2x - 1.25 = 0; \quad \text{Solving, } x = 0.5; \quad x = -2.5$$

But  $x \geq 0$  for all  $t$ . Thus,

$$e^{-40t} = 0.5; \quad e^{40t} = 2; \quad t = 25 \ln 2 = 17.33 \text{ ms}$$

P 7.39 For  $t < 0$

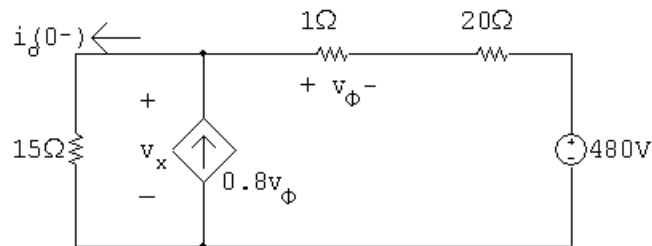

$$\frac{v_x}{15} - 0.8v_\phi + \frac{v_x - 480}{21} = 0$$


$$v_\phi = \frac{v_x - 480}{21}$$

$$\frac{v_x}{15} - 0.8 \left( \frac{v_x - 480}{21} \right) + \left( \frac{v_x - 480}{21} \right)$$


$$= \frac{v_x}{15} + 0.2 \left( \frac{v_x - 480}{21} \right) = 21v_x + 3(v_x - 480) = 0$$

$$\therefore 24v_x = 1440 \quad \text{so} \quad v_x = 60 \text{ V} \quad i_o(0^-) = \frac{v_x}{15} = 4 \text{ A}$$


$t > 0$

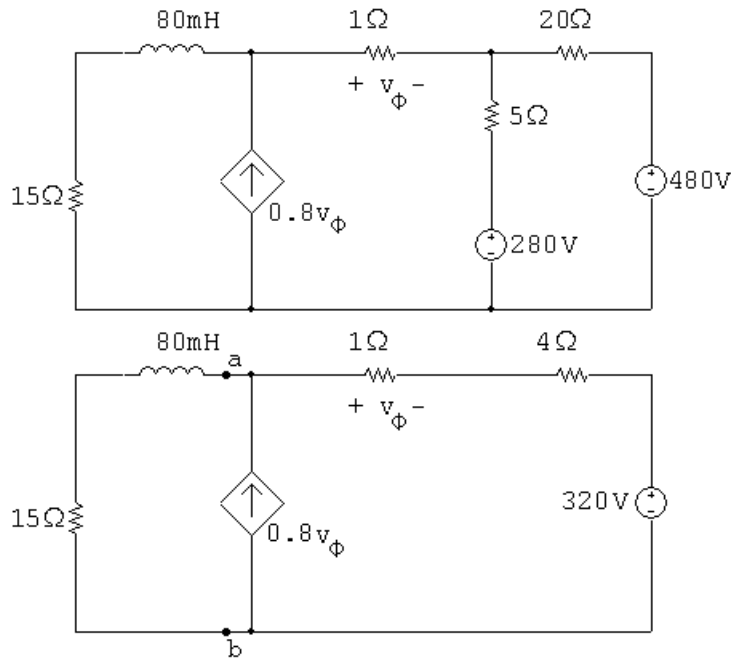

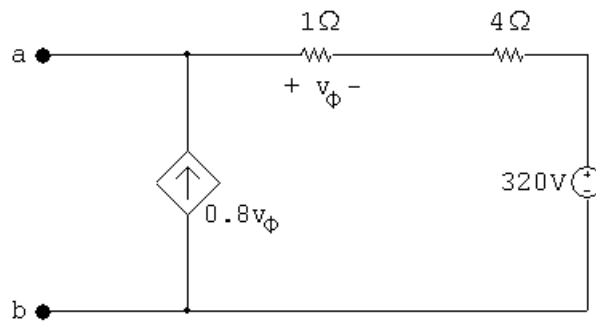Find Thévenin equivalent with respect to a, b


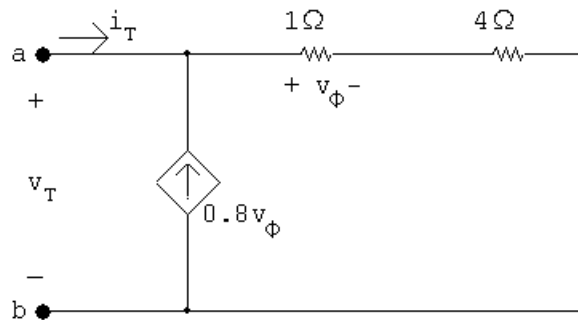
$$\frac{V_{Th} - 320}{5} - 0.8 \left( \frac{V_{Th} - 320}{5} \right) = 0 \quad V_{Th} = 320 \text{ V}$$




$$v_T = (i_T + 0.8v_\phi)(5) = \left( i_T + 0.8 \frac{v_T}{5} \right) (5)$$



$$v_T = 5i_T + 0.8v_T \quad \therefore \quad 0.2v_T = 5i_T$$

$$\frac{v_T}{i_T} = R_{Th} = 25\Omega$$

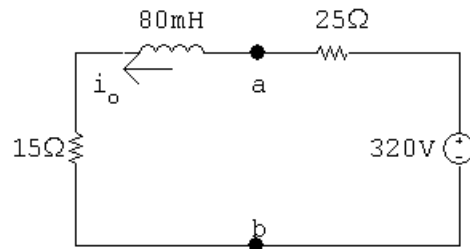


$$i_o(\infty) = 320/40 = 8\text{ A}$$

$$\tau = \frac{80 \times 10^{-3}}{40} = 2\text{ ms}; \quad 1/\tau = 500$$

$$i_o = 8 + (4 - 8)e^{-500t} = 8 - 4e^{-500t} \text{ A}, \quad t \geq 0$$

P 7.40  $t > 0$ ;

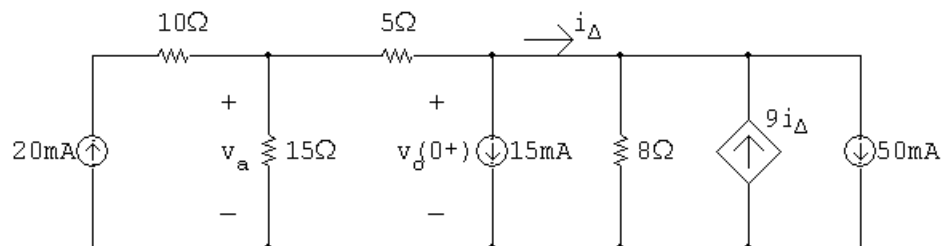

$$\frac{v_a}{15} + \frac{v_a - v_o(0^+)}{5} = 20 \times 10^{-3}$$

$$\therefore v_a = 0.75v_o(0^+) + 75 \times 10^{-3}$$

$$15 \times 10^{-3} + \frac{v_o(0^+) - v_a}{5} + \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3} = 0$$

$$13v_o(0^+) - 8v_a - 360i_\Delta = -2600 \times 10^{-3}$$

$$i_\Delta = \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3}$$

$$\therefore i_\Delta = \frac{v_o(0^+)}{80} + 5 \times 10^{-3}$$

$$\therefore 360i_\Delta = 4.5v_o(0^+) + 1800 \times 10^{-3}$$

$$8v_a = 6v_o(0^+) + 600 \times 10^{-3}$$


$$\therefore 13v_o(0^+) - 6v_o(0^+) - 600 \times 10^{-3} - 4.5v_o(0^+) -$$

$$1800 \times 10^{-3} = -2600 \times 10^{-3}$$

$$2.5v_o(0^+) = -200 \times 10^{-3}; \quad v_o(0^+) = -80 \text{ mV}$$

$$v_o(\infty) = 0$$

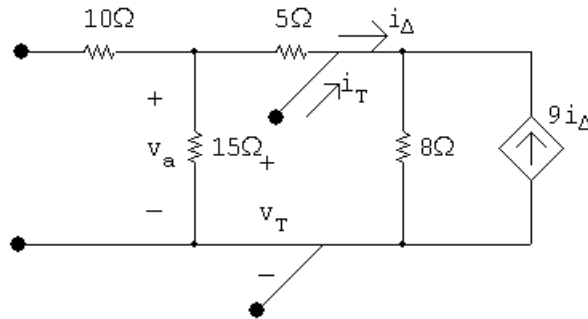Find the Thévenin resistance seen by the 4 mH inductor:



$$i_T = \frac{v_T}{20} + \frac{v_T}{8} - 9i_\Delta$$

$$i_\Delta = \frac{v_T}{8} - 9i_\Delta \quad \therefore 10i_\Delta = \frac{v_T}{8}; \quad i_\Delta = \frac{v_T}{80}$$

$$i_T = \frac{v_T}{20} + \frac{10v_T}{80} - \frac{9v_T}{80}$$


$$\frac{i_T}{v_T} = \frac{1}{20} + \frac{1}{80} = \frac{5}{80} = \frac{1}{16} \text{ S}$$

$$\therefore R_{Th} = 16\Omega$$

$$\tau = \frac{4 \times 10^{-3}}{16} = 0.25 \text{ ms}; \quad 1/\tau = 4000$$

$$\therefore v_o = 0 + (-80 - 0)e^{-4000t} = -80e^{-4000t} \text{ mV}, \quad t \geq 0^+$$

P 7.41 [a]

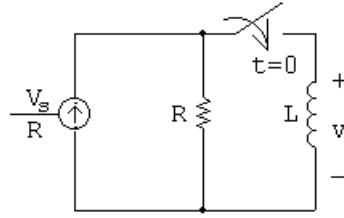

$$\frac{v}{R} + \frac{1}{L} \int_0^t v \, dx = \frac{V_s}{R}$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0$$

$$\frac{dv}{dt} + \frac{R}{L} v = 0$$

[b]  $\frac{dv}{dt} = -\frac{R}{L} v$

$$\frac{dv}{dt} dt = -\frac{R}{L} v \, dt$$

$$\therefore \frac{dv}{v} = -\frac{R}{L} dt$$


$$\int_{v(0^+)}^{v(t)} \frac{dy}{y} = -\frac{R}{L} \int_{0^+}^t dx$$

$$\ln y \Big|_{v(0^+)}^{v(t)} = -\left(\frac{R}{L}\right) t$$

$$\ln \left[ \frac{v(t)}{v(0^+)} \right] = -\left(\frac{R}{L}\right) t$$

$$v(t) = v(0^+) e^{-(R/L)t}; \quad v(0^+) = \left( \frac{V_s}{R} - I_o \right) R = V_s - I_o R$$

$$\therefore v(t) = (V_s - I_o R) e^{-(R/L)t}$$

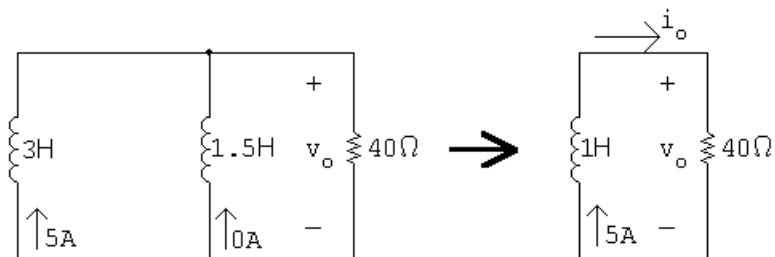P 7.42  $t > 0$ 

$$\tau = \frac{1}{40}$$

$$i_o = 5e^{-40t} \text{ A}, \quad t \geq 0$$

$$v_o = 40i_o = 200e^{-40t} \text{ V}, \quad t > 0^+$$

$$200e^{-40t} = 100; \quad e^{40t} = 2$$

$$\therefore t = \frac{1}{40} \ln 2 = 17.33 \text{ ms}$$

P 7.43 [a]  $w_{\text{diss}} = \frac{1}{2} L_e i^2(0) = \frac{1}{2} (1)(5)^2 = 12.5 \text{ J}$

[b]  $i_{3H} = \frac{1}{3} \int_0^t (200)e^{-40x} dx - 5$   
 $= 1.67(1 - e^{-40t}) - 5 = -1.67e^{-40t} - 3.33 \text{ A}$


$$i_{1.5H} = \frac{1}{1.5} \int_0^t (200)e^{-40x} dx + 0$$

$$= -3.33e^{-40t} + 3.33 \text{ A}$$


$$w_{\text{trapped}} = \frac{1}{2} (4.5)(3.33)^2 = 25 \text{ J}$$

[c]  $w(0) = \frac{1}{2} (3)(5)^2 = 37.5 \text{ J}$

P 7.44 [a]  $t < 0$

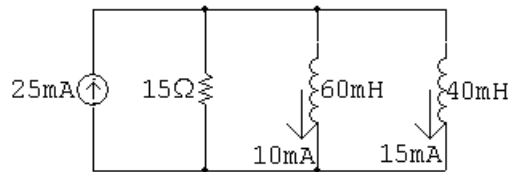

$$t > 0$$

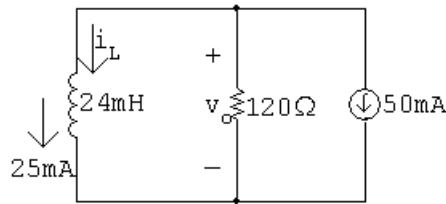

$$i_L(0^-) = i_L(0^+) = 25 \text{ mA}; \quad \tau = \frac{24 \times 10^{-3}}{120} = 0.2 \text{ ms}; \quad \frac{1}{\tau} = 5000$$

$$i_L(\infty) = -50 \text{ mA}$$

$$i_L = -50 + (25 + 50)e^{-5000t} = -50 + 75e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$v_o = -120[75 \times 10^{-3}e^{-5000t}] = -9e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$\text{[b]} \quad i_1 = \frac{1}{60 \times 10^{-3}} \int_0^t -9e^{-5000x} dx + 10 \times 10^{-3} = (30e^{-5000t} - 20) \text{ mA}, \quad t \geq 0$$

$$\text{[c]} \quad i_2 = \frac{1}{40 \times 10^{-3}} \int_0^t -9e^{-5000x} dx + 15 \times 10^{-3} = (45e^{-5000t} - 30) \text{ mA}, \quad t \geq 0$$

P 7.45 [a] Let  $v$  be the voltage drop across the parallel branches, positive at the top node, then

$$-I_g + \frac{v}{R_g} + \frac{1}{L_1} \int_0^t v dx + \frac{1}{L_2} \int_0^t v dx = 0$$

$$\frac{v}{R_g} + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t v dx = I_g$$

$$\frac{v}{R_g} + \frac{1}{L_e} \int_0^t v dx = I_g$$

$$\frac{1}{R_g} \frac{dv}{dt} + \frac{v}{L_e} = 0$$

$$\frac{dv}{dt} + \frac{R_g}{L_e} v = 0$$

Therefore  $v = I_g R_g e^{-t/\tau}; \quad \tau = L_e / R_g$

Thus


$$i_1 = \frac{1}{L_1} \int_0^t I_g R_g e^{-x/\tau} dx = \frac{I_g R_g}{L_1} \frac{e^{-x/\tau}}{(-1/\tau)} \Big|_0^t = \frac{I_g L_e}{L_1} (1 - e^{-t/\tau})$$

$$i_1 = \frac{I_g L_2}{L_1 + L_2} (1 - e^{-t/\tau}) \quad \text{and} \quad i_2 = \frac{I_g L_1}{L_1 + L_2} (1 - e^{-t/\tau})$$

$$\text{[b]} \quad i_1(\infty) = \frac{L_2}{L_1 + L_2} I_g; \quad i_2(\infty) = \frac{L_1}{L_1 + L_2} I_g$$

P 7.46 For  $t < 0$ ,  $i_{80\text{mH}}(0) = 50 \text{ V} / 10 \Omega = 5 \text{ A}$

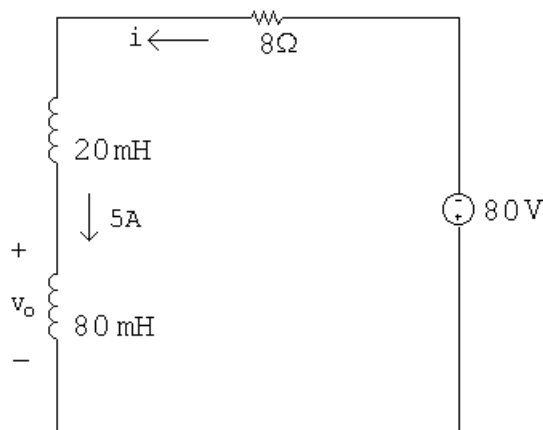For  $t > 0$ , after making a Thévenin equivalent we have



$$i = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-t/\tau}$$


$$\frac{1}{\tau} = \frac{R}{L} = \frac{8}{100 \times 10^{-3}} = 80$$

$$I_o = 5 \text{ A}; \quad I_f = \frac{V_s}{R} = \frac{-80}{8} = -10 \text{ A}$$

$$i = -10 + (5 + 10)e^{-80t} = -10 + 15e^{-80t} \text{ A}, \quad t \geq 0$$

$$v_o = 0.08 \frac{di}{dt} = 0.08(-1200e^{-80t}) = -96e^{-80t} \text{ V}, \quad t > 0^+$$

P 7.47 For  $t < 0$

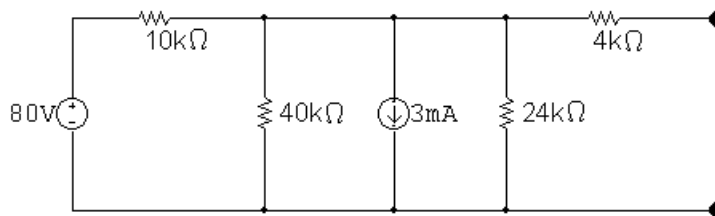


Simplify the circuit:

$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$


$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

Thus, for  $t < 0$

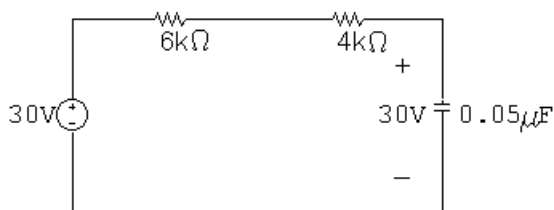

$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

$t > 0$

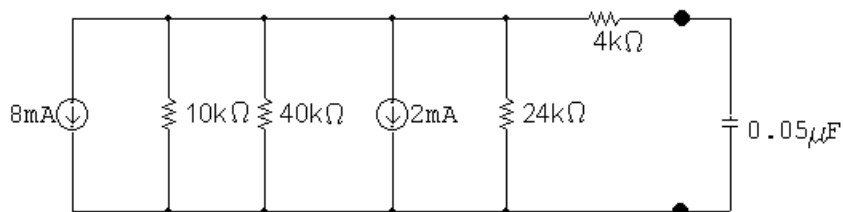


Simplify the circuit:

$$8\text{ mA} + 2\text{ mA} = 10\text{ mA}$$

$$10\text{ k}\parallel 40\text{ k}\parallel 24\text{ k} = 6\text{ k}\Omega$$

$$(10\text{ mA})(6\text{ k}\Omega) = 60\text{ V}$$

Thus, for  $t > 0$

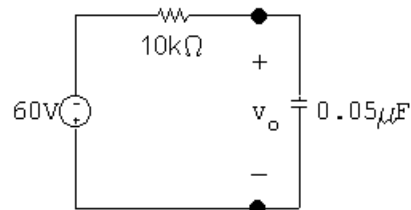


$$v_o(\infty) = -60\text{ V}$$

$$\tau = RC = (10\text{ k})(0.05\text{ }\mu) = 0.5\text{ ms}; \quad \frac{1}{\tau} = 2000$$

$$\begin{aligned} v_o &= v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = -60 + [30 - (-60)]e^{-2000t} \\ &= -60 + 90e^{-2000t}\text{ V} \quad t \geq 0 \end{aligned}$$

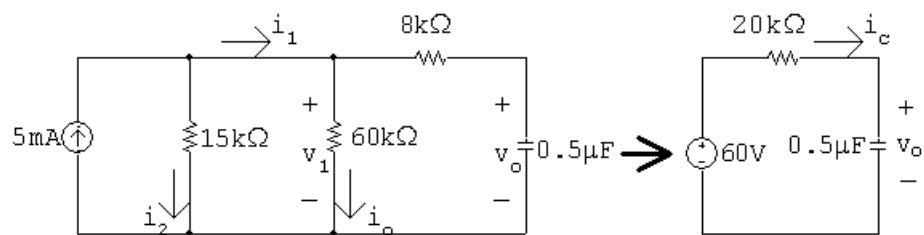P 7.48 [a] Simplify the circuit for  $t > 0$  using source transformation:



Since there is no source connected to the capacitor for  $t < 0$

$$v_o(0^-) = v_o(0^+) = 0\text{ V}$$

From the simplified circuit,

$$v_o(\infty) = 60\text{ V}$$

$$\tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 10\text{ ms} \quad 1/\tau = 100$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = (60 - 60e^{-100t})\text{ V}, \quad t \geq 0$$

$$\textbf{[b]} \quad i_c = C \frac{dv_o}{dt}$$

$$i_c = 0.5 \times 10^{-6}(-100)(-60e^{-100t}) = 3e^{-100t} \text{ mA}$$

$$v_1 = 8000i_c + v_o = (8000)(3 \times 10^{-3})e^{-100t} + (60 - 60e^{-100t}) = 60 - 36e^{-100t} \text{ V}$$

$$i_o = \frac{v_1}{60 \times 10^3} = 1 - 0.6e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$\textbf{[c]} \quad i_1(t) = i_o + i_c = 1 + 2.4e^{-100t} \text{ mA} \quad t \geq 0^+$$

$$\textbf{[d]} \quad i_2(t) = \frac{v_1}{15 \times 10^3} = 4 - 2.4e^{-100t} \text{ mA} \quad t \geq 0^+$$

$$\textbf{[e]} \quad i_1(0^+) = 1 + 2.4 = 3.4 \text{ mA}$$

At  $t = 0^+$ :

$$R_e = 15 \text{ k} \parallel 60 \text{ k} \parallel 8 \text{ k} = 4800 \Omega$$

$$v_1(0^+) = (5 \times 10^{-3})(4800) = 24 \text{ V}$$

$$i_1(0^+) = \frac{v_1(0^+)}{60,000} + \frac{v_1(0^+)}{8000} = 0.4 \text{ m} + 3 \text{ m} = 3.4 \text{ mA} \quad (\text{checks})$$

$$\textbf{P 7.49} \quad \textbf{[a]} \quad v = I_s R + (V_o - I_s R)e^{-t/RC} \quad i = \left(I_s - \frac{V_o}{R}\right)e^{-t/RC}$$

$$\therefore I_s R = 40, \quad V_o - I_s R = -24$$

$$\therefore V_o = 16 \text{ V}$$

$$I_s - \frac{V_o}{R} = 3 \times 10^{-3}; \quad I_s - \frac{16}{R} = 3 \times 10^{-3}; \quad R = \frac{40}{I_s}$$

$$\therefore I_s - 0.4I_s = 3 \times 10^{-3}; \quad I_s = 5 \text{ mA}$$

$$R = \frac{40}{5} \times 10^3 = 8 \text{ k}\Omega$$

$$\frac{1}{RC} = 2500; \quad C = \frac{1}{2500R} = \frac{10^{-3}}{20 \times 10^3} = 50 \text{ nF}; \quad \tau = RC = \frac{1}{2500} = 400 \mu\text{s}$$

$$\textbf{[b]} \quad v(\infty) = 40 \text{ V}$$

$$w(\infty) = \frac{1}{2}(50 \times 10^{-9})(1600) = 40 \mu\text{J}$$


$$0.81w(\infty) = 32.4 \mu\text{J}$$

$$v^2(t_o) = \frac{32.4 \times 10^{-6}}{25 \times 10^{-9}} = 1296; \quad v(t_o) = 36 \text{ V}$$

$$40 - 24e^{-2500t_o} = 36; \quad e^{2500t_o} = 6; \quad \therefore t_o = 716.70 \mu\text{s}$$



P 7.50 [a] For  $t > 0$ :

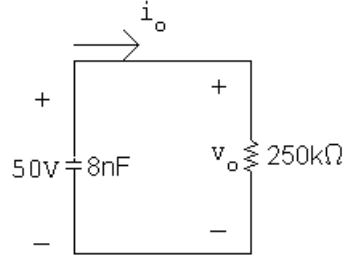

$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 50e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$\text{[b]} \quad i_o = \frac{v_o}{250,000} = \frac{50e^{-500t}}{250,000} = 200e^{-500t} \mu\text{A}$$

$$v_1 = \frac{-1}{40 \times 10^{-9}} \times 200 \times 10^{-6} \int_0^t e^{-500x} dx + 50 = 10e^{-500t} + 40 \text{ V}, \quad t \geq 0$$

P 7.51 [a]  $w = \frac{1}{2} C_{\text{eq}} v_o^2 = \frac{1}{2} (8 \times 10^{-9}) (50^2) = 10 \mu\text{J}$

[b]  $w_{\text{trapped}} = \frac{1}{2} (40)^2 (50 \times 10^{-9}) = 40 \mu\text{J}$

[c]  $w(0) = \frac{1}{2} (40 \times 10^{-9}) (50^2) = 50 \mu\text{J}$


P 7.52 For  $t > 0$

$$V_{\text{Th}} = (-25)(16,000)i_b = -400 \times 10^3 i_b$$

$$i_b = \frac{33,000}{80,000} (120 \times 10^{-6}) = 49.5 \mu\text{A}$$

$$V_{\text{Th}} = -400 \times 10^3 (49.5 \times 10^{-6}) = -19.8 \text{ V}$$

$$R_{\text{Th}} = 16 \text{ k}\Omega$$

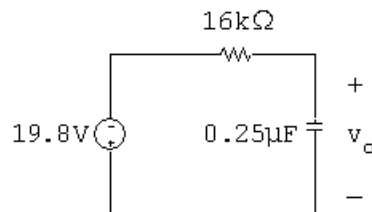

$$v_o(\infty) = -19.8 \text{ V}; \quad v_o(0^+) = 0$$

$$\tau = (16,000)(0.25 \times 10^{-6}) = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_o = -19.8 + 19.8e^{-250t} \text{ V}, \quad t \geq 0$$


$$w(t) = \frac{1}{2}(0.25 \times 10^{-6})v_o^2 = w(\infty)(1 - e^{-250t})^2 \text{ J}$$

$$(1 - e^{-250t})^2 = \frac{0.36w(\infty)}{w(\infty)} = 0.36$$

$$1 - e^{-250t} = 0.6$$

$$e^{-250t} = 0.4 \quad \therefore \quad t = 3.67 \text{ ms}$$

P 7.53 [a]

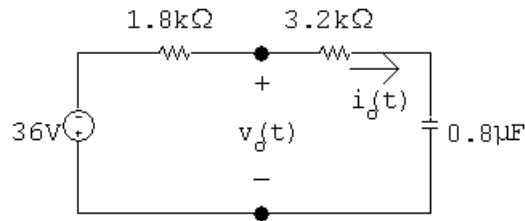

$$i_o(0^+) = \frac{-36}{5000} = -7.2 \text{ mA}$$


[b]  $i_o(\infty) = 0$

[c]  $\tau = RC = (5000)(0.8 \times 10^{-6}) = 4 \text{ ms}$

[d]  $i_o = 0 + (-7.2)e^{-250t} = -7.2e^{-250t} \text{ mA}, \quad t \geq 0^+$

[e]  $v_o = -[36 + 1800(-7.2 \times 10^{-3}e^{-250t})] = -36 + 12.96e^{-250t} \text{ V}, \quad t \geq 0^+$

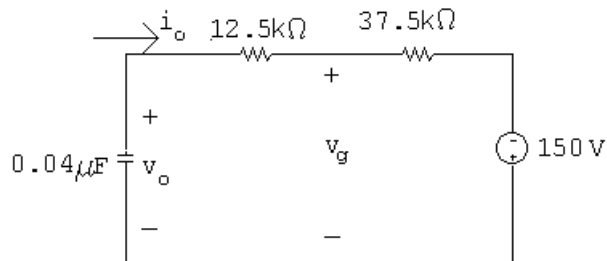P 7.54 [a]  $v_o(0^-) = v_o(0^+) = 120 \text{ V}$



$$v_o(\infty) = -150 \text{ V}; \quad \tau = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = -150 + (120 - (-150))e^{-500t}$$

$$v_o = -150 + 270e^{-500t} \text{ V}, \quad t \geq 0$$

[b]  $i_o = -0.04 \times 10^{-6}(-500)[270e^{-500t}] = 5.4e^{-500t} \text{ mA}, \quad t \geq 0^+$

**[c]**  $v_g = v_o - 12.5 \times 10^3 i_o = -150 + 202.5e^{-500t} \text{ V}$

**[d]**  $v_g(0^+) = -150 + 202.5 = 52.5 \text{ V}$

Checks:

$$v_g(0^+) = i_o(0^+)[37.5 \times 10^3] - 150 = 202.5 - 150 = 52.5 \text{ V}$$


$$i_{50k} = \frac{v_g}{50k} = -3 + 4.05e^{-500t} \text{ mA}$$

$$i_{150k} = \frac{v_g}{150k} = -1 + 1.35e^{-500t} \text{ mA}$$


$$-i_o + i_{50k} + i_{150k} + 4 = 0 \quad (\text{ok})$$

P 7.55 For  $t < 0$ ,  $v_o(0) = (-3 \text{ m})(15 \text{ k}) = -45 \text{ V}$

$t > 0$ :

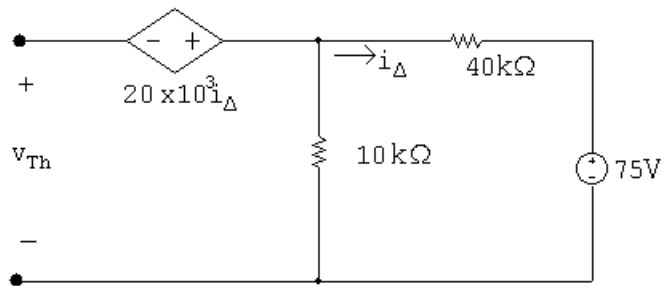

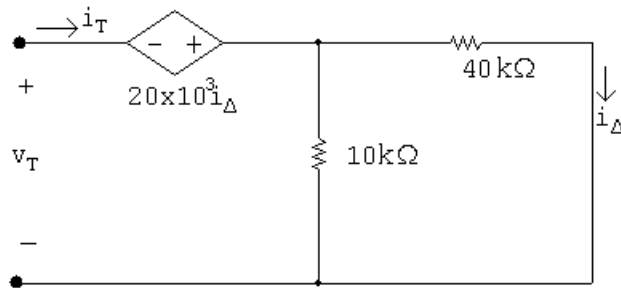
$$V_{Th} = -20 \times 10^3 i_{\Delta} + \frac{10}{50}(75) = -20 \times 10^3 \left( \frac{-75}{50 \times 10^3} \right) + 15 = 45 \text{ V}$$



$$v_T = -20 \times 10^3 i_{\Delta} + 8 \times 10^3 i_T = -20 \times 10^3 (0.2) i_T + 8 \times 10^3 i_T = 4 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = 4 \text{ k}\Omega$$

$t > 0$

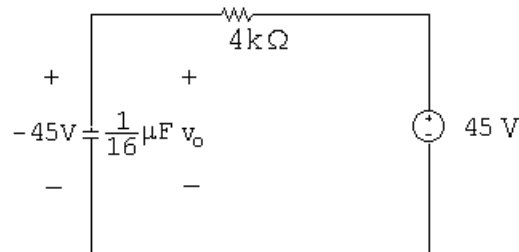

$$v_o = 45 + (-45 - 45)e^{-t/\tau}$$

$$\tau = RC = (4000) \left( \frac{1}{16} \times 10^{-6} \right) = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$v_o = 45 - 90e^{-4000t} \text{ V}, \quad t \geq 0$$

P 7.56  $v_o(0) = 45 \text{ V}; \quad v_o(\infty) = -45 \text{ V}$

$$R_{\text{Th}} = 20 \text{ k}\Omega$$


$$\tau = (20 \times 10^3) \left( \frac{1}{16} \times 10^{-6} \right) = 1.25 \times 10^{-3}; \quad \frac{1}{\tau} = 800$$

$$v = -45 + (45 + 45)e^{-800t} = -45 + 90e^{-800t} \text{ V}, \quad t \geq 0$$

P 7.57  $t < 0;$

$$i_o(0^-) = \frac{20}{100}(10 \times 10^{-3}) = 2 \text{ mA}; \quad v_o(0^-) = (2 \times 10^{-3})(50,000) = 100 \text{ V}$$

$$t = \infty:$$

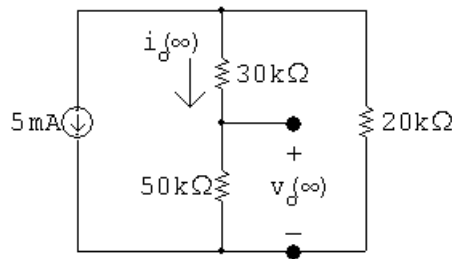


$$i_o(\infty) = -5 \times 10^{-3} \left( \frac{20}{100} \right) = -1 \text{ mA}; \quad v_o(\infty) = i_o(\infty)(50,000) = -50 \text{ V}$$

$$R_{\text{Th}} = 50 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 25 \text{ k}\Omega; \quad C = 16 \text{ nF}$$

$$\tau = (25,000)(16 \times 10^{-9}) = 0.4 \text{ ms}; \quad \frac{1}{\tau} = 2500$$
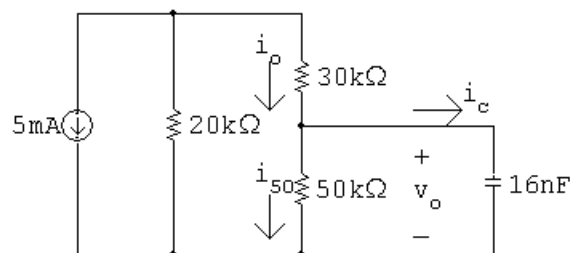
$$\therefore v_o(t) = -50 + 150e^{-2500t} \text{ V}, \quad t \geq 0$$



$$i_c = C \frac{dv_o}{dt} = -6e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{50k} = \frac{v_o}{50,000} = -1 + 3e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_o = i_c + i_{50k} = -(1 + 3e^{-2500t}) \text{ mA}, \quad t \geq 0^+$$

P 7.58 [a] Let  $i$  be the current in the clockwise direction around the circuit. Then

$$\begin{aligned} V_g &= iR_g + \frac{1}{C_1} \int_0^t i \, dx + \frac{1}{C_2} \int_0^t i \, dx \\ &= iR_g + \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t i \, dx = iR_g + \frac{1}{C_e} \int_0^t i \, dx \end{aligned}$$

Now differentiate the equation

$$0 = R_g \frac{di}{dt} + \frac{i}{C_e} \quad \text{or} \quad \frac{di}{dt} + \frac{1}{R_g C_e} i = 0$$

$$\text{Therefore} \quad i = \frac{V_g}{R_g} e^{-t/R_g C_e} = \frac{V_g}{R_g} e^{-t/\tau}; \quad \tau = R_g C_e$$


$$v_1(t) = \frac{1}{C_1} \int_0^t \frac{V_g}{R_g} e^{-x/\tau} \, dx = \frac{V_g}{R_g C_1} \left. \frac{e^{-x/\tau}}{-1/\tau} \right|_0^t = -\frac{V_g C_e}{C_1} (e^{-t/\tau} - 1)$$

$$v_1(t) = \frac{V_g C_2}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

$$v_2(t) = \frac{V_g C_1}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

$$\text{[b]} \quad v_1(\infty) = \frac{C_2}{C_1 + C_2} V_g; \quad v_2(\infty) = \frac{C_1}{C_1 + C_2} V_g$$

P 7.59 [a]

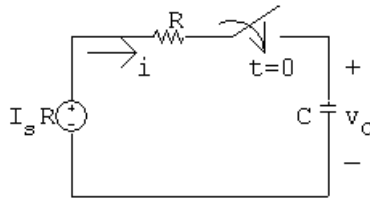

$$I_s R = Ri + \frac{1}{C} \int_{0^+}^t i \, dx + V_o$$

$$0 = R \frac{di}{dt} + \frac{i}{C} + 0$$

$$\therefore \frac{di}{dt} + \frac{i}{RC} = 0$$

$$\text{[b]} \quad \frac{di}{dt} = -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC}$$


$$\int_{i(0^+)}^{i(t)} \frac{dy}{y} = -\frac{1}{RC} \int_{0^+}^t dx$$

$$\ln \frac{i(t)}{i(0^+)} = \frac{-t}{RC}$$


$$i(t) = i(0^+)e^{-t/RC}; \quad i(0^+) = \frac{I_s R - V_o}{R} = \left(I_s - \frac{V_o}{R}\right)$$

$$\therefore i(t) = \left(I_s - \frac{V_o}{R}\right)e^{-t/RC}$$

P 7.60 [a]  $t < 0$

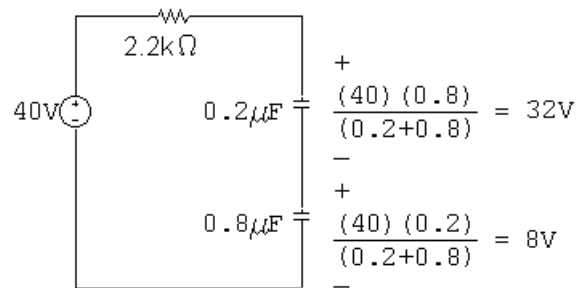

$t > 0$

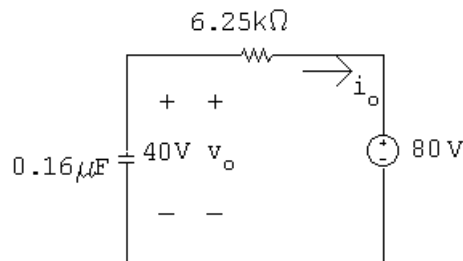

$$v_o(0^-) = v_o(0^+) = 40\text{V}$$

$$v_o(\infty) = 80\text{V}$$

$$\tau = (0.16 \times 10^{-6})(6.25 \times 10^3) = 1\text{ms}; \quad 1/\tau = 1000$$

$$v_o = 80 - 40e^{-1000t}\text{V}, \quad t \geq 0$$

$$\text{[b]} \quad i_o = -C \frac{dv_o}{dt} = -0.16 \times 10^{-6} [40,000e^{-1000t}]$$

$$= -6.4e^{-1000t}\text{mA}; \quad t \geq 0^+$$

$$\begin{aligned} \text{[c]} \quad v_1 &= \frac{-1}{0.2 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 32 \\ &= 64 - 32e^{-1000t} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad v_2 &= \frac{-1}{0.8 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 8 \\ &= 16 - 8e^{-1000t} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\text{[e]} \quad w_{\text{trapped}} = \frac{1}{2}(0.2 \times 10^{-6})(64)^2 + \frac{1}{2}(0.8 \times 10^{-6})(16)^2 = 512 \mu\text{J}.$$

P 7.61 [a]  $v_c(0^+) = 50 \text{ V}$

[b] Use voltage division to find the final value of voltage:


$$v_c(\infty) = \frac{20}{20+5}(-30) = -24 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{\text{Th}} = -24 \text{ V}, \quad R_{\text{Th}} = 20 \parallel 5 = 4 \Omega,$$

$$\text{Therefore } \tau = R_{\text{eq}}C = 4(25 \times 10^{-9}) = 0.1 \mu\text{s}$$

The simplified circuit for  $t > 0$  is:

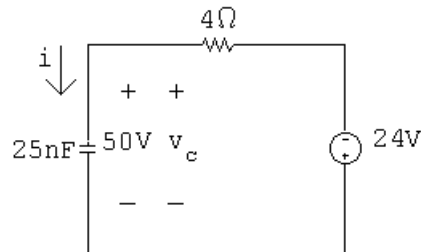

$$\text{[d]} \quad i(0^+) = \frac{-24 - 50}{4} = -18.5 \text{ A}$$

$$\text{[e]} \quad v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau}$$

$$= -24 + [50 - (-24)]e^{-t/\tau} = -24 + 74e^{-10^7 t} \text{ V}, \quad t \geq 0$$

$$\text{[f]} \quad i = C \frac{dv_c}{dt} = (25 \times 10^{-9})(-10^7)(74e^{-10^7 t}) = -18.5e^{-10^7 t} \text{ A}, \quad t \geq 0^+$$

P 7.62 [a] Use voltage division to find the initial value of the voltage:

$$v_c(0^+) = v_{9k} = \frac{9k}{9k+3k}(120) = 90 \text{ V}$$

[b] Use Ohm's law to find the final value of voltage:

$$v_c(\infty) = v_{40k} = -(1.5 \times 10^{-3})(40 \times 10^3) = -60 \text{ V}$$

**[c]** Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{Th} = -60 \text{ V}, \quad R_{Th} = 10 \text{ k} + 40 \text{ k} = 50 \text{ k}\Omega$$


$$\tau = R_{Th}C = 1 \text{ ms} = 1000 \mu\text{s}$$

$$\begin{aligned} \text{[d]} \quad v_c &= v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau} \\ &= -60 + (90 + 60)e^{-1000t} = -60 + 150e^{-1000t} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\text{We want } v_c = -60 + 150e^{-1000t} = 0:$$

$$\text{Therefore } t = \frac{\ln(150/60)}{1000} = 916.3 \mu\text{s}$$

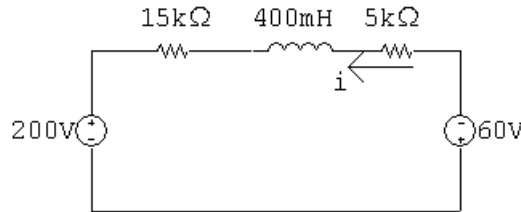
P 7.63 **[a]** For  $t < 0$ , calculate the Thévenin equivalent for the circuit to the left and right of the 400-mH inductor. We get



$$i(0^-) = \frac{-60 - 200}{15 \text{ k} + 5 \text{ k}} = -13 \text{ mA}$$

$$i(0^-) = i(0^+) = -13 \text{ mA}$$

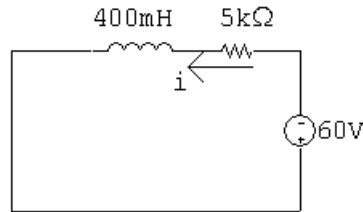**[b]** For  $t > 0$ , the circuit reduces to



$$\text{Therefore } i(\infty) = -60/5,000 = -12 \text{ mA}$$

$$\text{[c]} \quad \tau = \frac{L}{R} = \frac{400 \times 10^{-3}}{5000} = 80 \mu\text{s}$$

$$\begin{aligned} \text{[d]} \quad i(t) &= i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau} \\ &= -12 + [-13 + 12]e^{-12,500t} = -12 - e^{-12,500t} \text{ mA}, \quad t \geq 0 \end{aligned}$$

P 7.64 **[a]** From Example 7.10,

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{36 - 16}{20 - 8} = \frac{5}{3} \text{ H}$$

$$\tau = \frac{L_{eq}}{R} = \frac{(5/3)}{(50/3)} = \frac{1}{10}$$



$$i_o = \frac{100}{(50/3)} - \frac{100}{(50/3)}e^{-10t} = 6 - 6e^{-10t} \text{ A} \quad t \geq 0$$

$$\textbf{[b]} \quad v_o = 100 - \frac{50}{3}i_o = 100 - \frac{50}{3}(6 - 6e^{-10t}) = 100e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$\textbf{[c]} \quad v_o = 2\frac{di_1}{dt} + 4\frac{di_2}{dt}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = \frac{di_o}{dt} - \frac{di_1}{dt} = 60e^{-10t} - \frac{di_1}{dt}$$

$$\therefore 100e^{-10t} = 2\frac{di_1}{dt} + 4\left(60e^{-10t} - \frac{di_1}{dt}\right)$$

$$\therefore \frac{di_1}{dt} = 70e^{-10t}$$

$$di_1 = 70e^{-10t} dt$$

$$\int_0^{i_1} dx = 70 \int_0^t e^{-10y} dy$$

$$\therefore i_1 = 70 \frac{e^{-10y}}{-10} \Big|_0^t = 7 - 7e^{-10t} \text{ A}, \quad t \geq 0$$

$$\begin{aligned} \textbf{[d]} \quad i_2 &= i_o - i_1 \\ &= 6 - 6e^{-10t} - 7 + 7e^{-10t} \\ &= -1 + e^{-10t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \textbf{[e]} \quad v_o &= L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \\ &= 18(-10e^{-10t}) + 4(70e^{-10t}) \\ &= 100e^{-10t} \text{ V}, \quad t \geq 0^+ \quad (\text{checks}) \end{aligned}$$

Also,

$$\begin{aligned} v_o &= L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ &= 2(70e^{-10t}) + 4(-10e^{-10t}) \\ &= 100e^{-10t} \text{ V}, \quad t \geq 0^+ \quad \text{CHECKS} \end{aligned}$$

$$i_1(0) = 7 - 7 = 0; \text{ agrees with initial conditions;}$$

$$i_2(0) = -1 + 1 = 0; \text{ agrees with initial conditions;}$$

The final values of  $i_o$ ,  $i_1$ , and  $i_2$  can be checked via the conservation of Wb-turns:

$$i_o(\infty)L_{\text{eq}} = 6 \times (5/3) = 10 \text{ Wb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = 7(2) - 1(4) = 10 \text{ Wb-turns}$$

$$i_2(\infty)L_2 + i_1(\infty)M = -1(18) + 7(4) = 10 \text{ Wb-turns}$$

Thus our solutions make sense in terms of known circuit behavior.

P 7.65 [a]  $L_{\text{eq}} = \frac{(3)(15)}{3 + 15} = 2.5 \text{ H}$

$$\tau = \frac{L_{\text{eq}}}{R} = \frac{2.5}{7.5} = \frac{1}{3} \text{ s}$$

$$i_o(0) = 0; \quad i_o(\infty) = \frac{120}{7.5} = 16 \text{ A}$$

$$\therefore i_o = 16 - 16e^{-3t} \text{ A}, \quad t \geq 0$$

$$v_o = 120 - 7.5i_o = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

$$i_1 = \frac{1}{3} \int_0^t 120e^{-3x} dx = \frac{40}{3} - \frac{40}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

$$i_2 = i_o - i_1 = \frac{8}{3} - \frac{8}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

[b]  $i_o(0) = i_1(0) = i_2(0) = 0$ , consistent with initial conditions.  
 $v_o(0^+) = 120 \text{ V}$ , consistent with  $i_o(0) = 0$ .

$$v_o = 3 \frac{di_1}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

or

$$v_o = 15 \frac{di_2}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

The voltage solution is consistent with the current solutions.

$$\lambda_1 = 3i_1 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$$\lambda_2 = 15i_2 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$$\therefore \lambda_1 = \lambda_2 \text{ as it must, since}$$

$$v_o = \frac{d\lambda_1}{dt} = \frac{d\lambda_2}{dt}$$

$$\lambda_1(\infty) = \lambda_2(\infty) = 40 \text{ Wb-turns}$$

$$\lambda_1(\infty) = 3i_1(\infty) = 3(40/3) = 40 \text{ Wb-turns}$$

$$\lambda_2(\infty) = 15i_2(\infty) = 15(8/3) = 40 \text{ Wb-turns}$$

$\therefore i_1(\infty)$  and  $i_2(\infty)$  are consistent with  $\lambda_1(\infty)$  and  $\lambda_2(\infty)$ .

P 7.66 [a] From Example 7.10,

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{50 - 25}{15 + 10} = 1 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{1}{20}; \quad \frac{1}{\tau} = 20$$

$$\therefore i_o(t) = 4 - 4e^{-20t} \text{ A}, \quad t \geq 0$$

$$\text{[b]} v_o = 80 - 20i_o = 80 - 80 + 80e^{-20t} = 80e^{-20t} \text{ V}, \quad t \geq 0^+$$

$$\text{[c]} v_o = 5\frac{di_1}{dt} - 5\frac{di_2}{dt} = 80e^{-20t} \text{ V}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = 80e^{-20t} \text{ A/s}$$

$$\therefore \frac{di_2}{dt} = 80e^{-20t} - \frac{di_1}{dt}$$

$$\therefore 80e^{-20t} = 5\frac{di_1}{dt} - 400e^{-20t} + 5\frac{di_1}{dt}$$

$$\therefore 10\frac{di_1}{dt} = 480e^{-20t}; \quad di_1 = 48e^{-20t} dt$$

$$\int_0^{t_1} dx = \int_0^t 48e^{-20y} dy$$

$$i_1 = \frac{48}{-20}e^{-20y} \Big|_0^t = 2.4 - 2.4e^{-20t} \text{ A}, \quad t \geq 0$$

$$\text{[d]} i_2 = i_o - i_1 = 4 - 4e^{-20t} - 2.4 + 2.4e^{-20t}$$

$$= 1.6 - 1.6e^{-20t} \text{ A}, \quad t \geq 0$$

[e]  $i_o(0) = i_1(0) = i_2(0) = 0$ , consistent with zero initial stored energy.

$$v_o = L_{\text{eq}} \frac{di_o}{dt} = 1(80)e^{-20t} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

Also,

$$v_o = 5\frac{di_1}{dt} - 5\frac{di_2}{dt} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o = 10 \frac{di_2}{dt} - 5 \frac{di_1}{dt} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o(0^+) = 80 \text{ V}, \text{ which agrees with } i_o(0^+) = 0 \text{ A}$$

$$i_o(\infty) = 4 \text{ A}; \quad i_o(\infty)L_{\text{eq}} = (4)(1) = 4 \text{ Wb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = (2.4)(5) + (1.6)(-5) = 4 \text{ Wb-turns (ok)}$$

$$i_2(\infty)L_2 + i_1(\infty)M = (1.6)(10) + (2.4)(-5) = 4 \text{ Wb-turns (ok)}$$

Therefore, the final values of  $i_o$ ,  $i_1$ , and  $i_2$  are consistent with conservation of flux linkage. Hence, the answers make sense in terms of known circuit behavior.

P 7.67 [a]  $L_{\text{eq}} = 5 + 10 - 2.5(2) = 10 \text{ H}$

$$\tau = \frac{L}{R} = \frac{10}{40} = \frac{1}{4}; \quad \frac{1}{\tau} = 4$$

$$i = 2 - 2e^{-4t} \text{ A}, \quad t \geq 0$$

[b]  $v_1(t) = 5 \frac{di_1}{dt} - 2.5 \frac{di}{dt} = 2.5 \frac{di}{dt} = 2.5(8e^{-4t}) = 20e^{-4t} \text{ V}, \quad t \geq 0^+$

[c]  $v_2(t) = 10 \frac{di_1}{dt} - 2.5 \frac{di}{dt} = 7.5 \frac{di}{dt} = 7.5(8e^{-4t}) = 60e^{-4t} \text{ V}, \quad t \geq 0^+$

[d]  $i(0) = 2 - 2 = 0$ , which agrees with initial conditions.

$$80 = 40i_1 + v_1 + v_2 = 40(2 - 2e^{-4t}) + 20e^{-4t} + 60e^{-4t} = 80 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of  $t \geq 0$ . Thus, the answers make sense in terms of known circuit behavior.

P 7.68 [a]  $L_{\text{eq}} = 5 + 10 + 2.5(2) = 20 \text{ H}$

$$\tau = \frac{L}{R} = \frac{20}{40} = \frac{1}{2}; \quad \frac{1}{\tau} = 2$$

$$i = 2 - 2e^{-2t} \text{ A}, \quad t \geq 0$$

[b]  $v_1(t) = 5 \frac{di_1}{dt} + 2.5 \frac{di}{dt} = 7.5 \frac{di}{dt} = 7.5(4e^{-2t}) = 30e^{-2t} \text{ V}, \quad t \geq 0^+$

[c]  $v_2(t) = 10 \frac{di_1}{dt} + 2.5 \frac{di}{dt} = 12.5 \frac{di}{dt} = 12.5(4e^{-2t}) = 50e^{-2t} \text{ V}, \quad t \geq 0^+$

[d]  $i(0) = 0$ , which agrees with initial conditions.

$$80 = 40i_1 + v_1 + v_2 = 40(2 - 2e^{-2t}) + 30e^{-2t} + 50e^{-2t} = 80 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of  $t \geq 0$ . Thus, the answers make sense in terms of known circuit behavior.

P 7.69 Use voltage division to find the initial voltage:

$$v_o(0) = \frac{60}{40 + 60}(50) = 30 \text{ V}$$


Use Ohm's law to find the final value of voltage:

$$v_o(\infty) = (-5 \text{ mA})(20 \text{ k}\Omega) = -100 \text{ V}$$

$$\tau = RC = (20 \times 10^3)(250 \times 10^{-9}) = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$$

$$\begin{aligned} v_o &= v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} \\ &= -100 + (30 + 100)e^{-200t} = -100 + 130e^{-200t} \text{ V}, \quad t \geq 0 \end{aligned}$$

P 7.70 [a]  $t < 0$ :

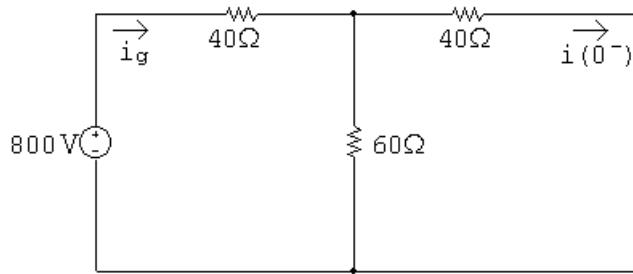

Using Ohm's law,

$$i_g = \frac{800}{40 + 60 \parallel 40} = 12.5 \text{ A}$$

Using current division,

$$i(0^-) = \frac{60}{60 + 40}(12.5) = 7.5 \text{ A} = i(0^+)$$

[b]  $0 \leq t \leq 1 \text{ ms}$ :

$$i = i(0^+)e^{-t/\tau} = 7.5e^{-t/\tau}$$


$$\frac{1}{\tau} = \frac{R}{L} = \frac{40 + 120 \parallel 60}{80 \times 10^{-3}} = 1000$$

$$i = 7.5e^{-1000t}$$

$$i(200 \mu\text{s}) = 7.5e^{-10^3(200 \times 10^{-6})} = 7.5e^{-0.2} = 6.14 \text{ A}$$

**[c]**  $i(1\text{ms}) = 7.5e^{-1} = 2.7591\text{ A}$

$$1\text{ ms} \leq t < \infty$$

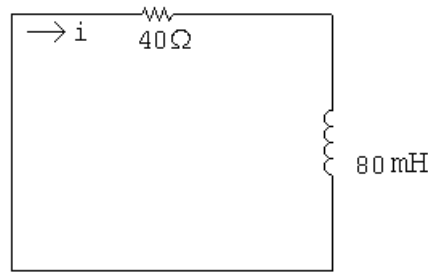

$$\frac{1}{\tau} = \frac{R}{L} = \frac{40}{80 \times 10^{-3}} = 500$$

$$i = i(1\text{ ms})e^{-(t-1\text{ ms})/\tau} = 2.7591e^{-500(t-0.001)}\text{ A}$$

$$i(6\text{ms}) = 2.7591e^{-500(0.005)} = 2.7591e^{-2.5} = 226.48\text{ mA}$$

**[d]**  $0 \leq t \leq 1\text{ ms}$ :

$$i = 7.5e^{-1000t}$$

$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-1000)(7.5e^{-1000t}) = -600e^{-1000t}\text{ V}$$

$$v(1^{-}\text{ms}) = -600e^{-1} = -220.73\text{ V}$$

**[e]**  $1\text{ ms} \leq t \leq \infty$ :

$$i = 2.7591e^{-500(t-0.001)}$$


$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-500)(2.591e^{-500(t-0.001)})$$

$$= -110.4e^{-500(t-0.001)}\text{ V}$$

$$v(1^{+}\text{ms}) = -110.4\text{ V}$$


**P 7.71** Note that for  $t > 0$ ,  $v_o = (4/6)v_c$ , where  $v_c$  is the voltage across the  $0.5\text{ }\mu\text{F}$  capacitor. Thus we will find  $v_c$  first.

$t < 0$

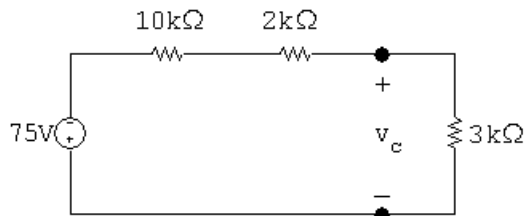

$$v_c(0) = \frac{3}{15}(-75) = -15\text{ V}$$

$$0 \leq t \leq 800 \mu\text{s}:$$

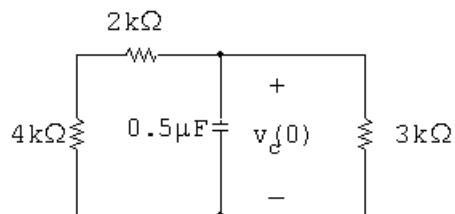


$$\tau = R_e C, \quad R_e = \frac{(6000)(3000)}{9000} = 2 \text{ k}\Omega$$

$$\tau = (2 \times 10^3)(0.5 \times 10^{-6}) = 1 \text{ ms}, \quad \frac{1}{\tau} = 1000$$

$$v_c = -15e^{-1000t} \text{ V}, \quad t \geq 0$$

$$v_c(800 \mu\text{s}) = -15e^{-0.8} = -6.74 \text{ V}$$

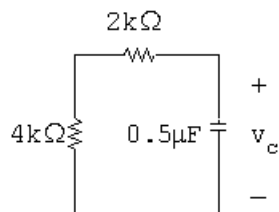
$$800 \mu\text{s} \leq t \leq 1.1 \text{ ms}:$$



$$\tau = (6 \times 10^3)(0.5 \times 10^{-6}) = 3 \text{ ms}, \quad \frac{1}{\tau} = 333.33$$

$$v_c = -6.74e^{-333.33(t-800 \times 10^{-6})} \text{ V}$$

$$1.1 \text{ ms} \leq t < \infty:$$

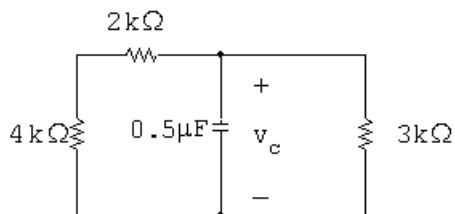

$$\tau = 1 \text{ ms}, \quad \frac{1}{\tau} = 1000$$

$$v_c(1.1 \text{ ms}) = -6.74e^{-333.33(1100-800)10^{-6}} = -6.74e^{-0.1} = -6.1 \text{ V}$$

$$v_c = -6.1e^{-1000(t-1.1 \times 10^{-3})} \text{ V}$$

$$v_c(1.5\text{ms}) = -6.1e^{-1000(1.5-1.1)10^{-3}} = -6.1e^{-0.4} = -4.09 \text{ V}$$

$$v_o = (4/6)(-4.09) = -2.73 \text{ V}$$

P 7.72  $w(0) = \frac{1}{2}(0.5 \times 10^{-6})(-15)^2 = 56.25 \mu\text{J}$

$$0 \leq t \leq 800 \mu\text{s}:$$

$$v_c = -15e^{-1000t}; \quad v_c^2 = 225e^{-2000t}$$

$$p_{3k} = 75e^{-2000t} \text{ mW}$$

$$\begin{aligned} w_{3k} &= \int_0^{800 \times 10^{-6}} 75 \times 10^{-3} e^{-2000t} dt \\ &= 75 \times 10^{-3} \left. \frac{e^{-2000t}}{-2000} \right|_0^{800 \times 10^{-6}} \\ &= -37.5 \times 10^{-6} (e^{-1.6} - 1) = 29.93 \mu\text{J} \end{aligned}$$

$$1.1 \text{ ms} \leq t \leq \infty:$$

$$v_c = -6.1e^{-1000(t-1.1 \times 10^{-3})} \text{ V}; \quad v_c^2 = 37.19e^{-2000(t-1.1 \times 10^{-3})}$$

$$p_{3k} = 12.4e^{-2000(t-1.1 \times 10^{-3})} \text{ mW}$$


$$\begin{aligned} w_{3k} &= \int_{1.1 \times 10^{-3}}^{\infty} 12.4 \times 10^{-3} e^{-2000(t-1.1 \times 10^{-3})} dt \\ &= 12.4 \times 10^{-3} \left. \frac{e^{-2000(t-1.1 \times 10^{-3})}}{-2000} \right|_{1.1 \times 10^{-3}}^{\infty} \\ &= -6.2 \times 10^{-6} (0 - 1) = 6.2 \mu\text{J} \end{aligned}$$

$$w_{3k} = 29.93 + 6.2 = 36.13 \mu\text{J}$$

$$\% = \frac{36.13}{56.25}(100) = 64.23\%$$




P 7.73 For  $t < 0$ :

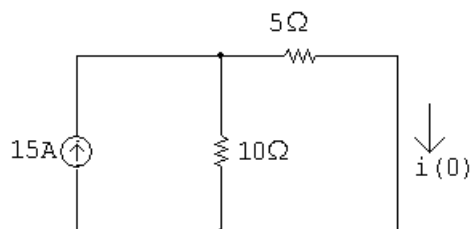

$$i(0) = \frac{10}{15}(15) = 10 \text{ A}$$


$0 \leq t \leq 10 \text{ ms}$ :

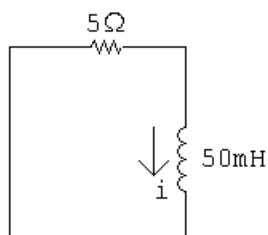

$$i = 10e^{-100t} \text{ A}$$

$$i(10\text{ms}) = 10e^{-1} = 3.68 \text{ A}$$

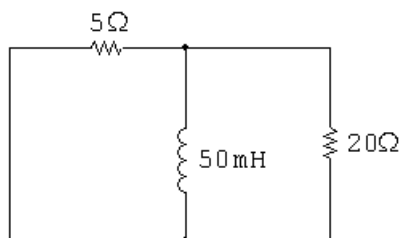$10 \text{ ms} \leq t \leq 20 \text{ ms}$ :



$$R_{\text{eq}} = \frac{(5)(20)}{25} = 4 \Omega$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{4}{50 \times 10^{-3}} = 80$$

$$i = 3.68e^{-80(t-0.01)} \text{ A}$$

$20 \text{ ms} \leq t \leq \infty$ :

$$i(20\text{ms}) = 3.68e^{-80(0.02-0.01)} = 1.65 \text{ A}$$

$$i = 1.65e^{-100(t-0.02)} \text{ A}$$

$$v_o = L \frac{di}{dt}; \quad L = 50 \text{ mH}$$

$$\frac{di}{dt} = 1.65(-100)e^{-100(t-0.02)} = -165e^{-100(t-0.02)}$$

$$\begin{aligned} v_o &= (50 \times 10^{-3})(-165)e^{-100(t-0.02)} \\ &= -8.26e^{-100(t-0.02)} \text{ V}, \quad t > 20^+ \text{ ms} \end{aligned}$$

$$v_o(25\text{ms}) = -8.26e^{-100(0.025-0.02)} = -5 \text{ V}$$

P 7.74 From the solution to Problem 7.73, the initial energy is

$$w(0) = \frac{1}{2}(50 \text{ mH})(10 \text{ A})^2 = 2.5 \text{ J}$$

$$0.04w(0) = 0.1 \text{ J}$$

$$\therefore \frac{1}{2}(50 \times 10^{-3})i_L^2 = 0.1 \quad \text{so} \quad i_L = 2 \text{ A}$$

Again, from the solution to Problem 7.73,  $t$  must be between 10 ms and 20 ms since


$$i(10 \text{ ms}) = 3.68 \text{ A} \quad \text{and} \quad i(20 \text{ ms}) = 1.65 \text{ A}$$

For  $10 \text{ ms} \leq t \leq 20 \text{ ms}$ :

$$i = 3.68e^{-80(t-0.01)} = 2$$

$$e^{80(t-0.01)} = \frac{3.68}{2} \quad \text{so} \quad t - 0.01 = 0.0076 \quad \therefore \quad t = 17.6 \text{ ms}$$

P 7.75  $0 \leq t \leq 10 \mu\text{s}$ :

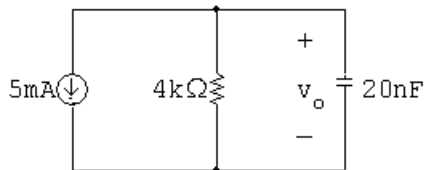


$$\tau = RC = (4 \times 10^3)(20 \times 10^{-9}) = 80 \mu\text{s}; \quad 1/\tau = 12,500$$


$$v_o(0) = 0 \text{ V}; \quad v_o(\infty) = -20 \text{ V}$$

$$v_o = -20 + 20e^{-12,500t} \text{ V} \quad 0 \leq t \leq 10 \mu\text{s}$$

$$10 \mu\text{s} \leq t \leq \infty:$$

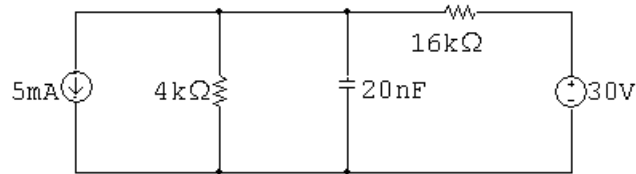

$$t = \infty:$$

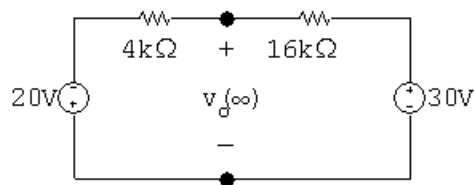

$$i = \frac{-50 \text{ V}}{20 \text{ k}\Omega} = -2.5 \text{ mA}$$

$$v_o(\infty) = (-2.5 \times 10^{-3})(16,000) + 30 = -10 \text{ V}$$

$$v_o(10 \mu\text{s}) = -20 + 20e^{-0.125} = -2.35 \text{ V}$$


$$v_o = -10 + (-2.35 + 10)e^{-(t - 10 \times 10^{-6})/\tau}$$

$$R_{\text{Th}} = 4 \text{ k}\Omega \parallel 16 \text{ k}\Omega = 3.2 \text{ k}\Omega$$

$$\tau = (3200)(20 \times 10^{-9}) = 64 \mu\text{s}; \quad 1/\tau = 15,625$$

$$v_o = -10 + 7.65e^{-15,625(t - 10 \times 10^{-6})} \quad 10 \mu\text{s} \leq t \leq \infty$$

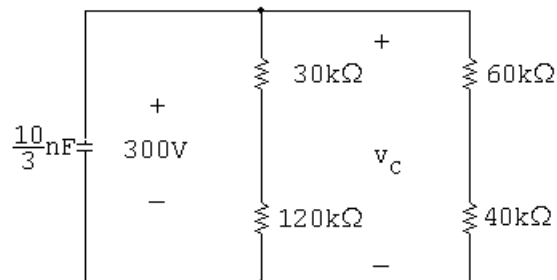**P 7.76**  $0 \leq t \leq 200 \mu\text{s};$




$$R_e = 150 \parallel 100 = 60 \text{ k}\Omega; \quad \tau = \left(\frac{10}{3} \times 10^{-9}\right)(60,000) = 200 \mu\text{s}$$

$$v_c = 300e^{-5000t} \text{ V}$$

$$v_c(200 \mu\text{s}) = 300e^{-1} = 110.36 \text{ V}$$

$$200 \mu\text{s} \leq t \leq \infty:$$

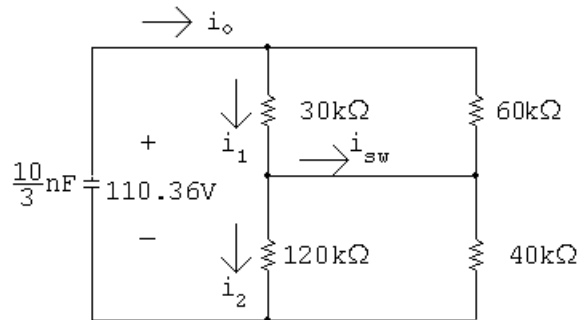

$$R_e = 30 \parallel 60 + 120 \parallel 40 = 20 + 30 = 50 \text{ k}\Omega$$

$$\tau = \left( \frac{10}{3} \times 10^{-9} \right) (50,000) = 166.67 \mu\text{s}; \quad \frac{1}{\tau} = 6000$$

$$v_c = 110.36e^{-6000(t - 200 \mu\text{s})} \text{ V}$$


$$v_c(300 \mu\text{s}) = 110.36e^{-6000(100 \mu\text{s})} = 60.57 \text{ V}$$

$$i_o(300 \mu\text{s}) = \frac{60.57}{50,000} = 1.21 \text{ mA}$$

$$i_1 = \frac{60}{90}i_o = \frac{2}{3}i_o; \quad i_2 = \frac{40}{160}i_o = \frac{1}{4}i_o$$


$$i_{sw} = i_1 - i_2 = \frac{2}{3}i_o - \frac{1}{4}i_o = \frac{5}{12}i_o = \frac{5}{12}(1.21 \times 10^{-3}) = 0.50 \text{ mA}$$

P 7.77  $t < 0$ :

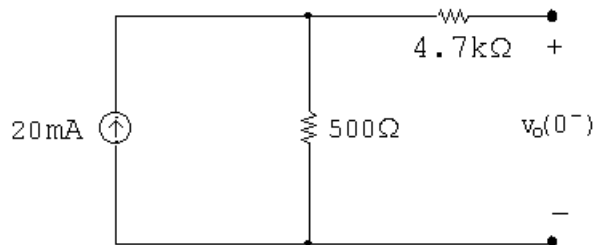


$$v_c(0^-) = (20 \times 10^{-3})(500) = 10 \text{ V} = v_c(0^+)$$

$0 \leq t \leq 50 \text{ ms}$ :

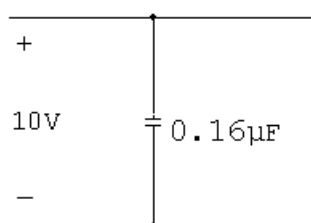

$$\tau = \infty; \quad 1/\tau = 0; \quad v_o = 10e^{-0} = 10 \text{ V}$$

$50 \text{ ms} \leq t \leq \infty$ :

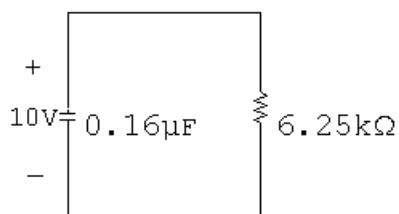


$$\tau = (6.25 \text{ k})(0.16 \mu) = 1 \text{ ms}; \quad 1/\tau = 1000; \quad v_o = 10e^{-1000(t-0.05)} \text{ V}$$

**Summary:**

$$v_o = 10 \text{ V}, \quad 0 \leq t \leq 50 \text{ ms}$$


$$v_o = 10e^{-1000(t-0.05)} \text{ V}, \quad 50 \text{ ms} \leq t \leq \infty$$

**P 7.78**  $t < 0$ :

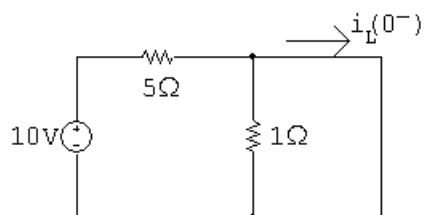

$$i_L(0^-) = 10 \text{ V}/5 \Omega = 2 \text{ A} = i_L(0^+)$$

$$0 \leq t \leq 5:$$

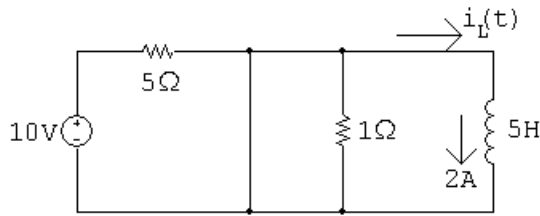


$$\tau = 5/0 = \infty$$

$$i_L(t) = 2e^{-t/\infty} = 2e^{-0} = 2$$

$$i_L(t) = 2 \text{ A}, \quad 0 \leq t \leq 5 \text{ s}$$

$$5 \leq t \leq \infty:$$

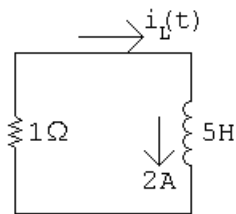

$$\tau = \frac{5}{1} = 5 \text{ s}; \quad 1/\tau = 0.2$$

$$i_L(t) = 2e^{-0.2(t-5)} \text{ A}, \quad t \geq 5 \text{ s}$$

**P 7.79 [a]**  $0 \leq t \leq 2.5 \text{ ms}$

$$v_o(0^+) = 80 \text{ V}; \quad v_o(\infty) = 0$$

$$\tau = \frac{L}{R} = 2 \text{ ms}; \quad 1/\tau = 500$$

$$v_o(t) = 80e^{-500t} \text{ V}, \quad 0^+ \leq t \leq 2.5 \text{ ms}$$


$$v_o(2.5^- \text{ ms}) = 80e^{-1.25} = 22.92 \text{ V}$$

$$i_o(2.5^- \text{ ms}) = \frac{(80 - 22.92)}{20} = 2.85 \text{ A}$$

$$v_o(2.5^+ \text{ ms}) = -20(2.85) = -57.08 \text{ V}$$

$$v_o(\infty) = 0; \quad \tau = 2 \text{ ms}; \quad 1/\tau = 500$$

$$v_o = -57.08e^{-500(t-0.0025)} \text{ V} \quad 2.5^+ \text{ ms} \leq t \leq \infty$$

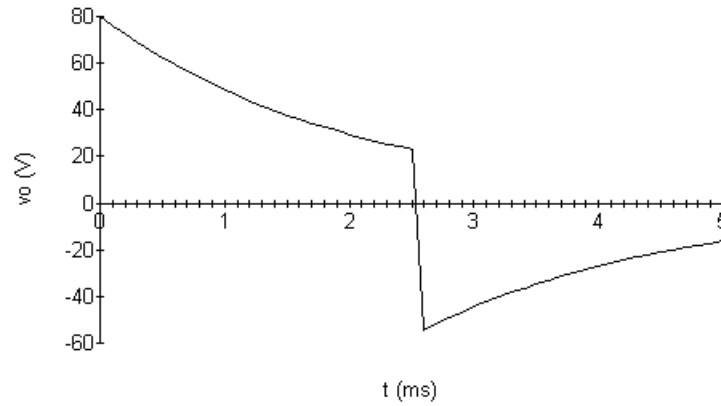**[b]**

**[c]**  $v_o(5 \text{ ms}) = -16.35 \text{ V}$

$$i_o = \frac{+16.35}{20} = 817.68 \text{ mA}$$

P 7.80 **[a]**  $i_o(0) = 0$ ;  $i_o(\infty) = 25 \text{ mA}$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{2000}{250} \times 10^3 = 8000$$

$$i_o = (25 - 25e^{-8000t}) \text{ mA}, \quad 0 \leq t \leq 75 \mu\text{s}$$

$$v_o = 0.25 \frac{di_o}{dt} = 50e^{-8000t} \text{ V}, \quad 0^+ \leq t \leq 75^- \mu\text{s}$$

$$75^+ \mu\text{s} \leq t \leq \infty:$$

$$i_o(75 \mu\text{s}) = 25 - 25e^{-0.6} = 11.28 \text{ mA}; \quad i_o(\infty) = 0$$

$$i_o = 11.28e^{-8000(t-75 \times 10^{-6})} \text{ mA}$$

$$v_o = (0.25) \frac{di_o}{dt} = -22.56e^{-8000(t-75 \mu\text{s})}$$

$$\therefore t < 0: \quad v_o = 0$$

$$0^+ \leq t \leq 75^- \mu\text{s}: \quad v_o = 50e^{-8000t} \text{ V}$$

$$75^+ \mu\text{s} \leq t \leq \infty: \quad v_o = -22.56e^{-8000(t-75 \mu\text{s})}$$

**[b]**  $v_o(75^- \mu\text{s}) = 50e^{-0.6} = 27.44 \text{ V}$

$$v_o(75^+ \mu\text{s}) = -22.56 \text{ V}$$

**[c]**  $i_o(75^- \mu\text{s}) = i_o(75^+ \mu\text{s}) = 11.28 \text{ mA}$

P 7.81 [a]  $0 \leq t < 1 \text{ ms}$ :

$$v_c(0^+) = 0; \quad v_c(\infty) = 50 \text{ V};$$

$$RC = 400 \times 10^3(0.01 \times 10^{-6}) = 4 \text{ ms}; \quad 1/RC = 250$$

$$v_c = 50 - 50e^{-250t}$$

$$v_o = 50 - 50 + 50e^{-250t} = 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$$1 \text{ ms} < t \leq \infty:$$

$$v_c(1 \text{ ms}) = 50 - 50e^{-0.25} = 11.06 \text{ V}$$


$$v_c(\infty) = 0 \text{ V}$$

$$\tau = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_c = 11.06e^{-250(t-0.001)} \text{ V}$$

$$v_o = -v_c = -11.06e^{-250(t-0.001)} \text{ V}, \quad 1 \text{ ms} < t \leq \infty$$

[b]

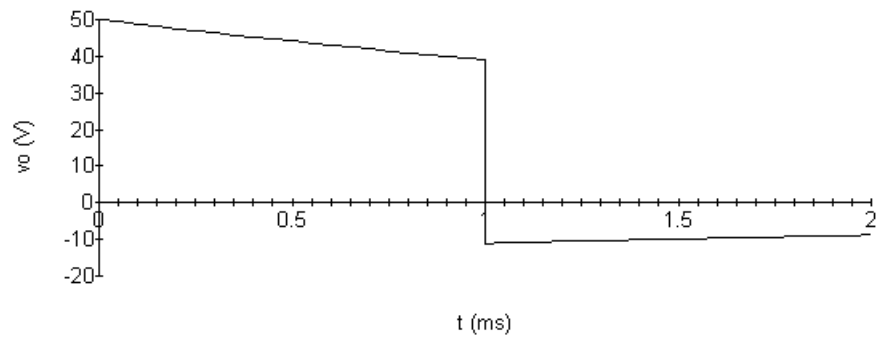P 7.82 [a]  $t < 0$ ;  $v_o = 0$ 

$$0 \leq t \leq 4 \text{ ms}:$$

$$\tau = (200 \times 10^3)(0.025 \times 10^{-6}) = 5 \text{ ms}; \quad 1/\tau = 200$$

$$v_o = 100 - 100e^{-200t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100(1 - e^{-0.8}) = 55.07 \text{ V}$$

$$4 \text{ ms} \leq t \leq 8 \text{ ms}:$$

$$v_o = -100 + 155.07e^{-200(t-0.004)} \text{ V}$$


$$v_o(8 \text{ ms}) = -100 + 155.07e^{-0.8} = -30.32 \text{ V}$$

$$8 \text{ ms} \leq t \leq \infty:$$

$$v_o = -30.32e^{-200(t-0.008)} \text{ V}$$



[b]

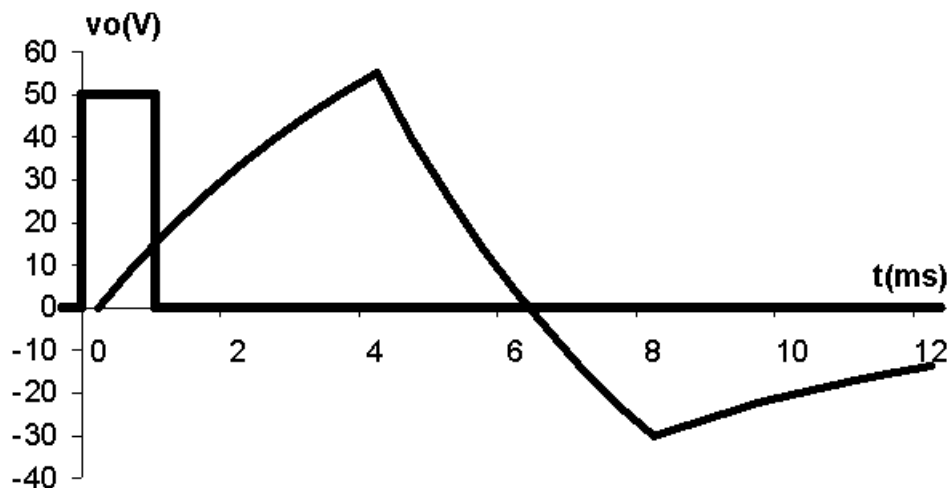[c]  $t \leq 0$ :  $v_o = 0$  $0 \leq t \leq 4 \text{ ms}$ :

$$\tau = (50 \times 10^3)(0.025 \times 10^{-6}) = 1.25 \text{ ms} \quad 1/\tau = 800$$

$$v_o = 100 - 100e^{-800t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100 - 100e^{-3.2} = 95.92 \text{ V}$$


 $4 \text{ ms} \leq t \leq 8 \text{ ms}$ :

$$v_o = -100 + 195.92e^{-800(t-0.004)} \text{ V}, \quad 4 \text{ ms} \leq t \leq 8 \text{ ms}$$

$$v_o(8 \text{ ms}) = -100 + 195.92e^{-3.2} = -92.01 \text{ V}$$

 $8 \text{ ms} \leq t \leq \infty$ :
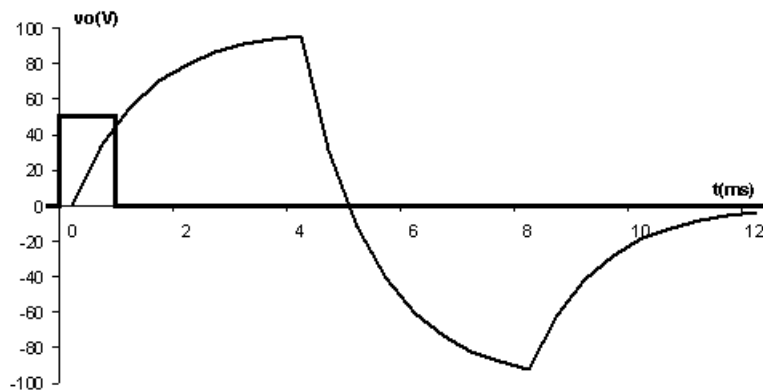
$$v_o = -92.01e^{-800(t-0.008)} \text{ V}, \quad 8 \text{ ms} \leq t \leq \infty$$



P 7.83 [a]  $\tau = RC = (20,000)(0.2 \times 10^{-6}) = 4 \text{ ms}; \quad 1/\tau = 250$

$$i_o = v_o = 0 \quad t < 0$$

$$i_o(0^+) = 20 \left( \frac{16}{20} \right) = 16 \text{ mA}, \quad i_o(\infty) = 0$$

$$\therefore i_o = 16e^{-250t} \text{ mA} \quad 0^+ \leq t \leq 2^- \text{ ms}$$

$$i_{16k\Omega} = 20 - 16e^{-250t} \text{ mA}$$

$$\therefore v_o = 320 - 256e^{-250t} \text{ V} \quad 0^+ \leq t \leq 2^- \text{ ms}$$

$$v_c = v_o - 4 \times 10^3 i_o = 320 - 320e^{-250t} \text{ V} \quad 0 \leq t \leq 2 \text{ ms}$$

$$v_c(2 \text{ ms}) = 320 - 320e^{-0.5} = 125.91 \text{ V}$$

$$\therefore i_o(2^+ \text{ ms}) = 16e^{-0.5} = 9.7 \text{ mA}$$

$$i_o(\infty) = 0$$

$$v_c = 125.91e^{-250(t-0.002)}, \quad 2^+ \text{ ms} \leq t \leq \infty$$

$$i_o = C \frac{dv_c}{dt} = (0.2 \times 10^{-6})(-250)(125.91)e^{-250(t-0.002)}$$

$$= -6.3e^{-250(t-0.002)} \text{ mA}, \quad 2^+ \text{ ms} \leq t \leq \infty$$

$$v_o = 4000i_o + v_c = 100.73e^{-250(t-0.002)} \text{ V} \quad 2^+ \text{ ms} \leq t \leq \infty$$

Summary part (a)

$$i_o = 0 \quad t < 0$$

$$i_o = 16e^{-250t} \text{ mA} \quad (0^+ \leq t \leq 2^- \text{ ms})$$

$$i_o = -6.3e^{-250(t-0.002)} \text{ mA} \quad 2^+ \text{ ms} \leq t \leq \infty$$

$$v_o = 0 \quad t < 0$$

$$v_o = 320 - 256e^{-250t} \text{ V}, \quad 0 \leq t \leq 2^- \text{ ms}$$

$$v_o = 100.73e^{-250(t-0.002)} \text{ V}, \quad 2^+ \text{ ms} \leq t \leq \infty$$

[b]  $i_o(0^-) = 0$

$$i_o(0^+) = 16 \text{ mA}$$

$$i_o(2^- \text{ ms}) = 16e^{-0.5} = 9.7 \text{ mA}$$



$$i_o(2^+ \text{ ms}) = -6.3 \text{ mA}$$

[c]  $v_o(0^-) = 0$


$v_o(0^+) = 64 \text{ V}$

$v_o(2^- \text{ ms}) = 320 - 256e^{-0.5} = 164.73 \text{ V}$

$v_o(2^+ \text{ ms}) = 100.73$

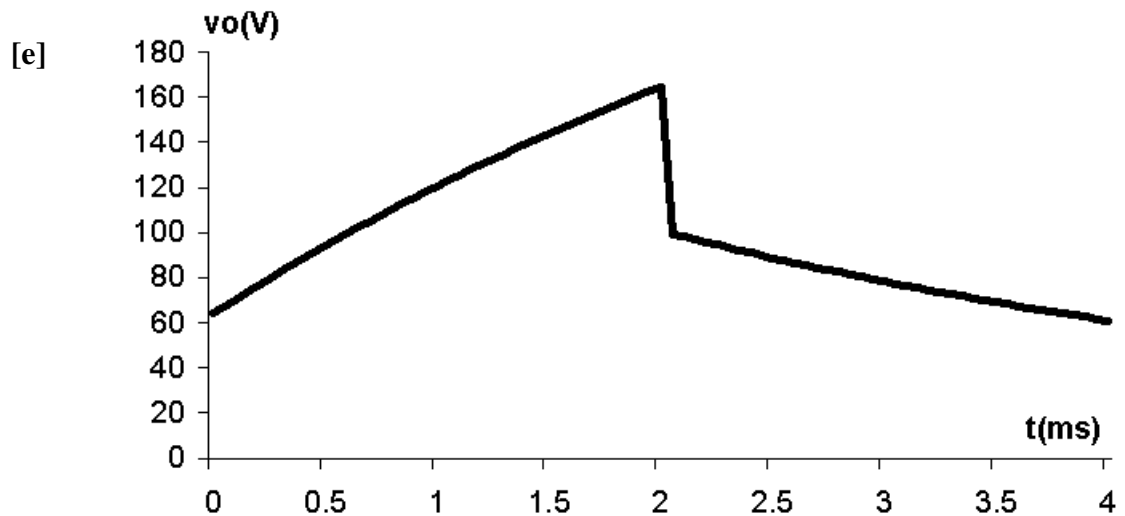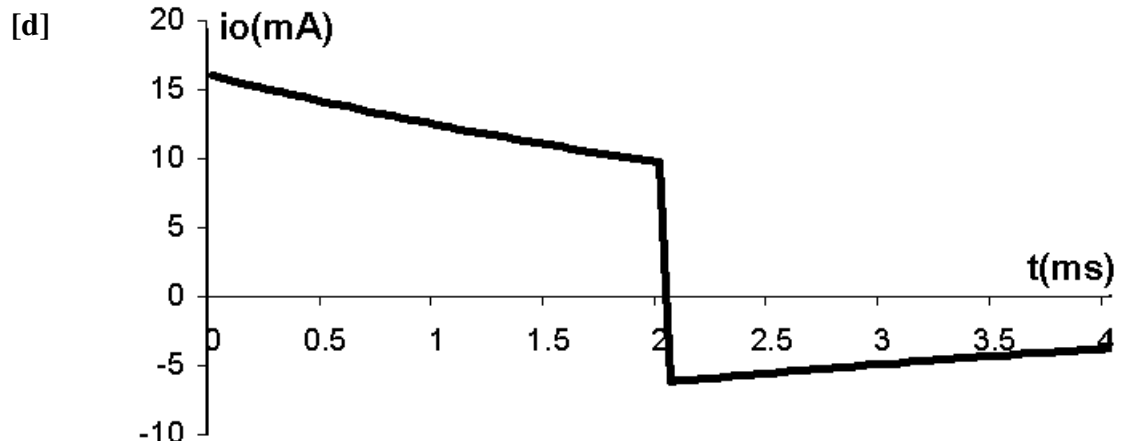

P 7.84 [a]

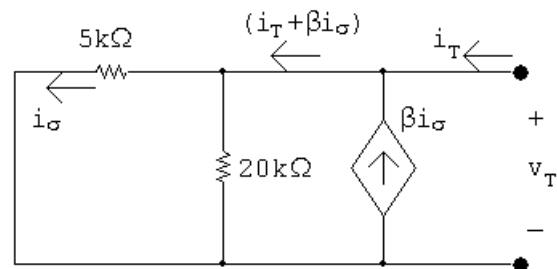

Using Ohm's law,

$$v_T = 5000i_\sigma$$

Using current division,

$$i_\sigma = \frac{20,000}{20,000 + 5000}(i_T + \beta i_\sigma) = 0.8i_T + 0.8\beta i_\sigma$$

Solve for  $i_\sigma$ :

$$i_\sigma(1 - 0.8\beta) = 0.8i_T$$


$$i_\sigma = \frac{0.8i_T}{1 - 0.8\beta}; \quad v_T = 5000i_\sigma = \frac{4000i_T}{(1 - 0.8\beta)}$$

Find  $\beta$  such that  $R_{Th} = -5 \text{ k}\Omega$ :

$$R_{Th} = \frac{v_T}{i_T} = \frac{4000}{1 - 0.8\beta} = -5000$$

$$1 - 0.8\beta = -0.8 \quad \therefore \beta = 2.25$$

**[b]** Find  $V_{Th}$ :

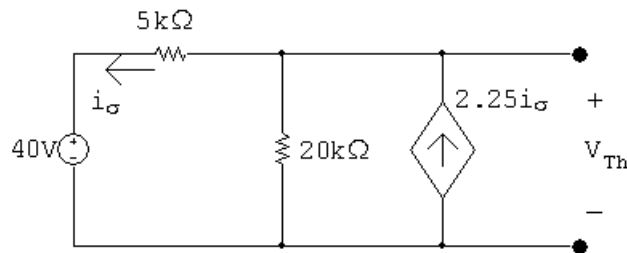

Write a KCL equation at the top node:


$$\frac{V_{Th} - 40}{5000} + \frac{V_{Th}}{20,000} - 2.25i_\sigma = 0$$

The constraint equation is:

$$i_\sigma = \frac{(V_{Th} - 40)}{5000} = 0$$

Solving,

$$V_{Th} = 50 \text{ V}$$

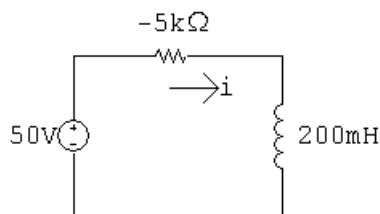

Write a KVL equation around the loop:

$$50 = -5000i + 0.2 \frac{di}{dt}$$

Rearranging:

$$\frac{di}{dt} = 250 + 25,000i = 25,000(i + 0.01)$$

Separate the variables and integrate to find  $i$ ;

$$\frac{di}{i + 0.01} = 25,000 dt$$

$$\int_0^i \frac{dx}{x + 0.01} = \int_0^t 25,000 dx$$

$$\therefore i = -10 + 10e^{25,000t} \text{ mA}$$

$$\frac{di}{dt} = (10 \times 10^{-3})(25,000)e^{25,000t} = 250e^{25,000t}$$


Solve for the arc time:

$$v = 0.2 \frac{di}{dt} = 50e^{25,000t} = 45,000; \quad e^{25,000t} = 900$$

$$\therefore t = \frac{\ln 900}{25,000} = 272.1 \mu\text{s}$$

P 7.85 Find the Thévenin equivalent with respect to the terminals of the capacitor.

$R_{Th}$  calculation:

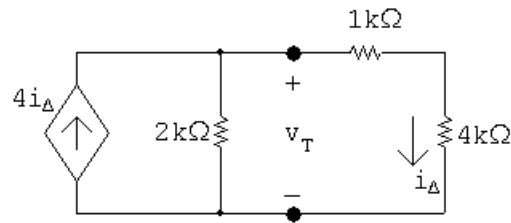


$$i_T = \frac{v_T}{2000} + \frac{v_T}{5000} - 4 \frac{v_T}{5000}$$

$$\therefore \frac{i_T}{v_T} = \frac{5 + 2 - 8}{10,000} = -\frac{1}{10,000}$$

$$\frac{v_T}{i_T} = -\frac{10,000}{1} = -10\text{ k}\Omega$$

Open circuit voltage calculation:

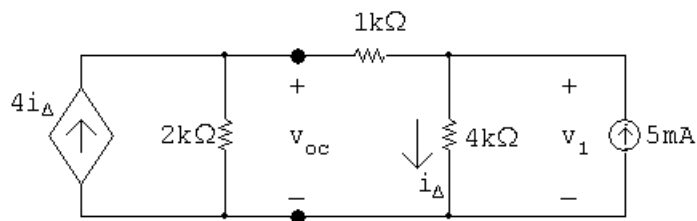

The node voltage equations:


$$\frac{v_{oc}}{2000} + \frac{v_{oc} - v_1}{1000} - 4i_{\Delta} = 0$$

$$\frac{v_1 - v_{oc}}{1000} + \frac{v_1}{4000} - 5 \times 10^{-3} = 0$$

The constraint equation:

$$i_{\Delta} = \frac{v_1}{4000}$$

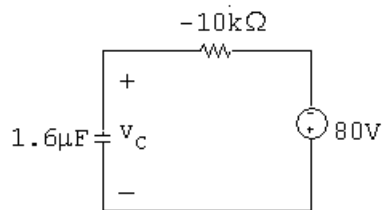Solving,  $v_{oc} = -80 \text{ V}$ ,  $v_1 = -60 \text{ V}$



$$v_c(0) = 0; \quad v_c(\infty) = -80 \text{ V}$$


$$\tau = RC = (-10,000)(1.6 \times 10^{-6}) = -16 \text{ ms}; \quad \frac{1}{\tau} = -62.5$$

$$v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau} = -80 + 80e^{62.5t} = 14,400$$

Solve for the time of the maximum voltage rating:

$$e^{62.5t} = 181; \quad 62.5t = \ln 181; \quad t = 83.18 \text{ ms}$$


P 7.86

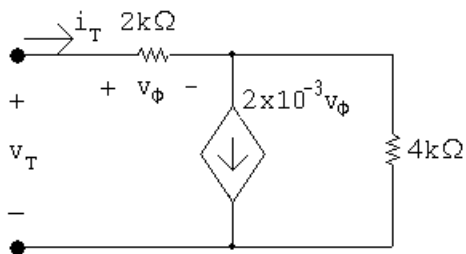

$$v_T = 2000i_T + 4000(i_T - 2 \times 10^{-3}v_{\phi}) = 6000i_T - 8v_{\phi}$$

$$= 6000i_T - 8(2000i_T)$$

$$\frac{v_T}{i_T} = -10,000$$

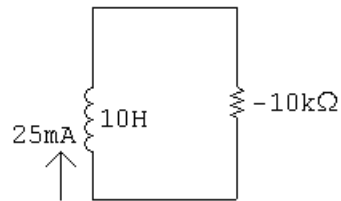


$$\tau = \frac{10}{-10,000} = -1 \text{ ms}; \quad 1/\tau = -1000$$

$$i = 25e^{1000t} \text{ mA}$$

$$\therefore 25e^{1000t} \times 10^{-3} = 5; \quad t = \frac{\ln 200}{1000} = 5.3 \text{ ms}$$

P 7.87  $t > 0$ :

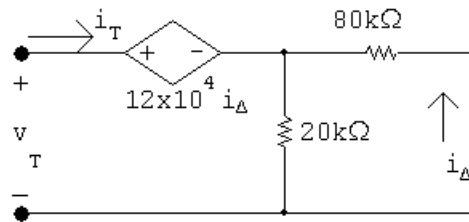

$$v_T = 12 \times 10^4 i_\Delta + 16 \times 10^3 i_T$$

$$i_\Delta = -\frac{20}{100} i_T = -0.2 i_T$$

$$\therefore v_T = -24 \times 10^3 i_T + 16 \times 10^3 i_T$$


$$R_{Th} = \frac{v_T}{i_T} = -8 \text{ k}\Omega$$

$$\tau = RC = (-8 \times 10^3)(2.5 \times 10^{-6}) = -0.02 \quad 1/\tau = -50$$

$$v_c = 20e^{50t} \text{ V}; \quad 20e^{50t} = 20,000$$

$$50t = \ln 1000 \quad \therefore \quad t = 138.16 \text{ ms}$$

P 7.88 [a]

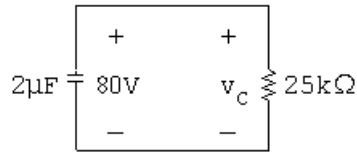

$$\tau = (25)(2) \times 10^{-3} = 50 \text{ ms}; \quad 1/\tau = 20$$


$$v_c(0^+) = 80 \text{ V}; \quad v_c(\infty) = 0$$

$$v_c = 80e^{-20t} \text{ V}$$

$$\therefore 80e^{-20t} = 5; \quad e^{20t} = 16; \quad t = \frac{\ln 16}{20} = 138.63 \text{ ms}$$

[b]  $0^+ < t < 138.63 \text{ ms}$ :

$$i = (2 \times 10^{-6})(-1600e^{-20t}) = -3.2e^{-20t} \text{ mA}$$

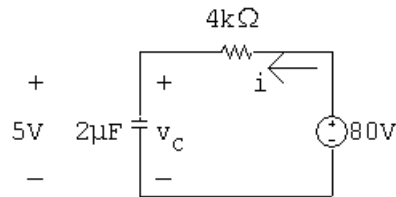 $138.63^+ \text{ ms} < t \leq \infty$ :

$$\tau = (2)(4) \times 10^{-3} = 8 \text{ ms}; \quad 1/\tau = 125$$

$$v_c(138.63^+ \text{ ms}) = 5 \text{ V}; \quad v_c(\infty) = 80 \text{ V}$$

$$v_c = 80 - 75e^{-125(t-0.13863)} \text{ V}, \quad 138.63^+ \text{ ms} \leq t \leq \infty$$

$$i = 2 \times 10^{-6}(9375)e^{-125(t-0.13863)} \\ = 18.75e^{-125(t-0.13863)} \text{ mA}, \quad 138.63^+ \text{ ms} \leq t \leq \infty$$

[c]  $80 - 75e^{-125\Delta t} = 0.85(80) = 68$ 

$$80 - 68 = 75e^{-125\Delta t} = 12$$

$$e^{125\Delta t} = 6.25; \quad \Delta t = \frac{\ln 6.25}{125} \cong 14.66 \text{ ms}$$

P 7.89 Use voltage division to find the voltage at the non-inverting terminal:

$$v_p = \frac{80}{100}(-45) = -36 \text{ V} = v_n$$



Write a KCL equation at the inverting terminal:

$$\frac{-36 - 14}{80,000} + 2.5 \times 10^{-6} \frac{d}{dt}(-36 - v_o) = 0$$

$$\therefore 2.5 \times 10^{-6} \frac{dv_o}{dt} = \frac{-50}{80,000}$$

Separate the variables and integrate:

$$\frac{dv_o}{dt} = -250 \quad \therefore dv_o = -250 dt$$

$$\int_{v_o(0)}^{v_o(t)} dx = -250 \int_0^t dy \quad \therefore v_o(t) - v_o(0) = -250t$$

$$v_o(0) = -36 + 56 = 20 \text{ V}$$

$$v_o(t) = -250t + 20$$

Find the time when the voltage reaches 0:

$$0 = -250t + 20 \quad \therefore t = \frac{20}{250} = 80 \text{ ms}$$

**P 7.90** The equation for an integrating amplifier:

$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy + v_o(0)$$

Find the values and substitute them into the equation:

$$RC = (100 \times 10^3)(0.05 \times 10^{-6}) = 5 \text{ ms}$$

$$\frac{1}{RC} = 200; \quad v_b - v_a = -15 - (-7) = -8 \text{ V}$$

$$v_o(0) = -4 + 12 = 8 \text{ V}$$

$$v_o = 200 \int_0^t -8 dx + 8 = (-1600t + 8) \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

RC circuit analysis for  $v_2$ :

$$v_2(0^+) = -4 \text{ V}; \quad v_2(\infty) = -15 \text{ V}; \quad \tau = RC = (100 \text{ k})(0.05 \mu) = 5 \text{ ms}$$

$$v_2 = v_2(\infty) + [v_2(0^+) - v_2(\infty)]e^{-t/\tau}$$

$$= -15 + (-4 + 15)e^{-200t} = -15 + 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

$$v_f + v_2 = v_o \quad \therefore \quad v_f = v_o - v_2 = 23 - 1600t - 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

Note that

$$-1600t_{\text{sat}} + 8 = -20 \quad \therefore \quad t_{\text{sat}} = \frac{-28}{-1600} = 17.5 \text{ ms}$$

so the op amp operates in its linear region until it saturates at 17.5 ms.

$$\text{P 7.91} \quad v_o = -\frac{1}{R(0.5 \times 10^{-6})} \int_0^t 4 \, dx + 0 = \frac{-4t}{R(0.5 \times 10^{-6})}$$

$$\frac{-4(15 \times 10^{-3})}{R(0.5 \times 10^{-6})} = -10$$

$$\therefore \quad R = \frac{-4(15 \times 10^{-3})}{-10(0.5 \times 10^{-6})} = 12 \text{ k}\Omega$$

$$\text{P 7.92} \quad v_o = \frac{-4t}{R(0.5 \times 10^{-6})} + 6 = \frac{-4(40 \times 10^{-3})}{R(0.5 \times 10^{-6})} + 6 = -10$$

$$\therefore \quad R = \frac{-4(40 \times 10^{-3})}{-16(0.5 \times 10^{-6})} = 20 \text{ k}\Omega$$

$$\text{P 7.93} \quad [\mathbf{a}] \quad \frac{Cdv_p}{dt} + \frac{v_p - v_b}{R} = 0; \quad \text{therefore} \quad \frac{dv_p}{dt} + \frac{1}{RC}v_p = \frac{v_b}{RC}$$

$$\frac{v_n - v_a}{R} + C \frac{d(v_n - v_o)}{dt} = 0;$$

$$\text{therefore} \quad \frac{dv_o}{dt} = \frac{dv_n}{dt} + \frac{v_n}{RC} - \frac{v_a}{RC}$$

But  $v_n = v_p$

$$\text{Therefore} \quad \frac{dv_n}{dt} + \frac{v_n}{RC} = \frac{dv_p}{dt} + \frac{v_p}{RC} = \frac{v_b}{RC}$$

$$\text{Therefore} \quad \frac{dv_o}{dt} = \frac{1}{RC}(v_b - v_a); \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) \, dy$$

**[b]** The output is the integral of the difference between  $v_b$  and  $v_a$  and then scaled by a factor of  $1/RC$ .

$$\text{[c]} \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx$$

$$RC = (50 \times 10^3)(10 \times 10^{-9}) = 0.5 \text{ ms}$$

$$v_b - v_a = -25 \text{ mV}$$

$$v_o = \frac{1}{0.0005} \int_0^t -25 \times 10^{-3} dx = -50t$$

$$-50t_{\text{sat}} = -6; \quad t_{\text{sat}} = 120 \text{ ms}$$

$$\text{P 7.94} \quad \text{[a]} \quad RC = (25 \times 10^3)(0.4 \times 10^{-6}) = 10 \text{ ms}; \quad \frac{1}{RC} = 100$$

$$v_o = 0, \quad t < 0$$

$$\text{[b]} \quad 0 \leq t \leq 250 \text{ ms} :$$

$$v_o = -100 \int_0^t -0.20 dx = 20t \text{ V}$$

$$\text{[c]} \quad 250 \text{ ms} \leq t \leq 500 \text{ ms};$$


$$v_o(0.25) = 20(0.25) = 5 \text{ V}$$

$$v_o(t) = -100 \int_{0.25}^t 0.20 dx + 5 = -20(t - 0.25) + 5 = -20t + 10 \text{ V}$$

$$\text{[d]} \quad 500 \text{ ms} \leq t \leq \infty :$$

$$v_o(0.5) = -10 + 10 = 0 \text{ V}$$

$$v_o(t) = 0 \text{ V}$$

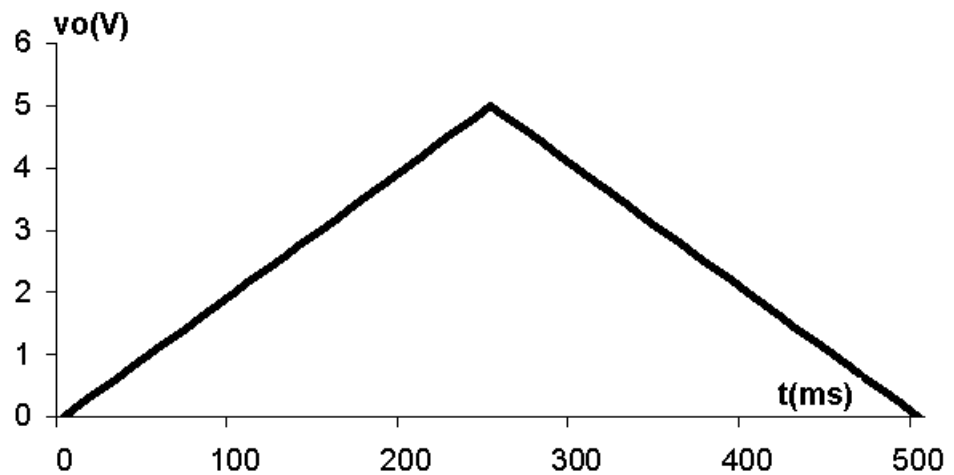

P 7.95 [a]  $v_o = 0, \quad t < 0$

$$RC = (25 \times 10^3)(0.4 \times 10^{-6}) = 10 \text{ ms} \quad \frac{1}{RC} = 100$$

[b]  $R_f C_f = (5 \times 10^6)(0.4 \times 10^{-6}) = 2; \quad \frac{1}{R_f C_f} = 0.5$


$$v_o = \frac{-5 \times 10^6}{25 \times 10^3}(-0.2)[1 - e^{-0.5t}] = 40(1 - e^{-0.5t}) \text{ V}, \quad 0 \leq t \leq 250 \text{ ms}$$

[c]  $v_o(0.25) = 40(1 - e^{-0.125}) \cong 4.70 \text{ V}$

$$\begin{aligned} v_o &= \frac{-V_m R_f}{R_s} + \frac{V_m R_f}{R_s}(2 - e^{-0.125})e^{-0.5(t-0.25)} \\ &= -40 + 40(2 - e^{-0.125})e^{-0.5(t-0.25)} \\ &= -40 + 44.70e^{-0.5(t-0.25)} \text{ V}, \quad 250 \text{ ms} \leq t \leq 500 \text{ ms} \end{aligned}$$

[d]  $v_o(0.5) = -40 + 44.70e^{-0.125} \cong -0.55 \text{ V}$
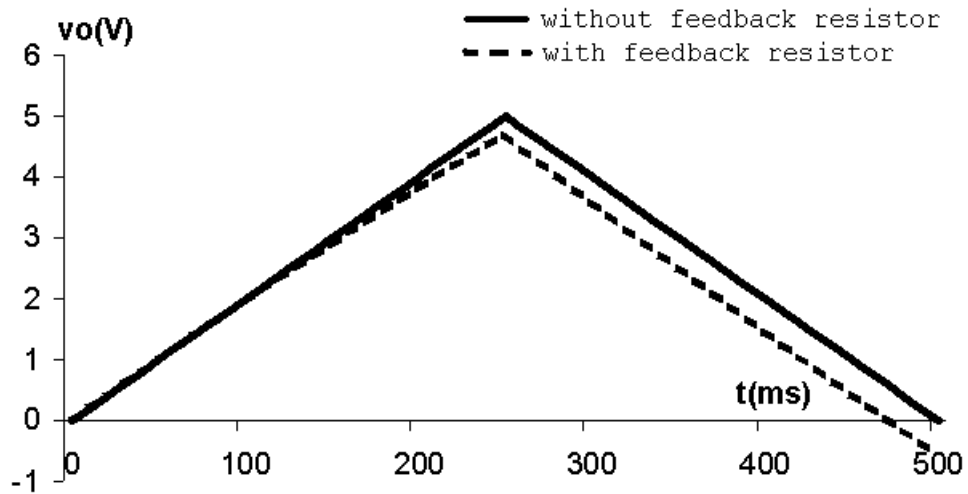
$$v_o = -0.55e^{-0.5(t-0.5)} \text{ V}, \quad 500 \text{ ms} \leq t \leq \infty$$



P 7.96 [a]  $RC = (1000)(800 \times 10^{-12}) = 800 \times 10^{-9}; \quad \frac{1}{RC} = 1,250,000$

$$0 \leq t \leq 1 \mu\text{s}:$$

$$v_g = 2 \times 10^6 t$$

$$v_o = -1.25 \times 10^6 \int_0^t 2 \times 10^6 x dx + 0$$

$$= -2.5 \times 10^{12} \frac{x^2}{2} \Big|_0^t = -125 \times 10^{10} t^2 \text{ V}, \quad 0 \leq t \leq 1 \mu\text{s}$$

$$v_o(1\mu\text{s}) = -125 \times 10^{10}(1 \times 10^{-6})^2 = -1.25\text{ V}$$

$$1\mu\text{s} \leq t \leq 3\mu\text{s}:$$

$$v_g = 4 - 2 \times 10^6 t$$


$$\begin{aligned} v_o &= -125 \times 10^4 \int_{1 \times 10^{-6}}^t (4 - 2 \times 10^6 x) dx - 1.25 \\ &= -125 \times 10^4 \left[ 4x \Big|_{1 \times 10^{-6}}^t - 2 \times 10^6 \frac{x^2}{2} \Big|_{1 \times 10^{-6}}^t \right] - 1.25 \\ &= -5 \times 10^6 t + 5 + 125 \times 10^{10} t^2 - 1.25 - 1.25 \\ &= 125 \times 10^{10} t^2 - 5 \times 10^6 t + 2.5\text{ V}, \quad 1\mu\text{s} \leq t \leq 3\mu\text{s} \\ v_o(3\mu\text{s}) &= 125 \times 10^{10}(3 \times 10^{-6})^2 - 5 \times 10^6(3 \times 10^{-6}) + 2.5 \\ &= -1.25 \end{aligned}$$

$$3\mu\text{s} \leq t \leq 4\mu\text{s}:$$

$$v_g = -8 + 2 \times 10^6 t$$


$$\begin{aligned} v_o &= -125 \times 10^4 \int_{3 \times 10^{-6}}^t (-8 + 2 \times 10^6 x) dx - 1.25 \\ &= -125 \times 10^4 \left[ -8x \Big|_{3 \times 10^{-6}}^t + 2 \times 10^6 \frac{x^2}{2} \Big|_{3 \times 10^{-6}}^t \right] - 1.25 \\ &= 10^7 t - 30 - 125 \times 10^{10} t^2 + 11.25 - 1.25 \\ &= -125 \times 10^{10} t^2 + 10^7 t - 20\text{ V}, \quad 3\mu\text{s} \leq t \leq 4\mu\text{s} \\ v_o(4\mu\text{s}) &= -125 \times 10^{10}(4 \times 10^{-6})^2 + 10^7(4 \times 10^{-6}) - 20 = 0 \end{aligned}$$

[b]

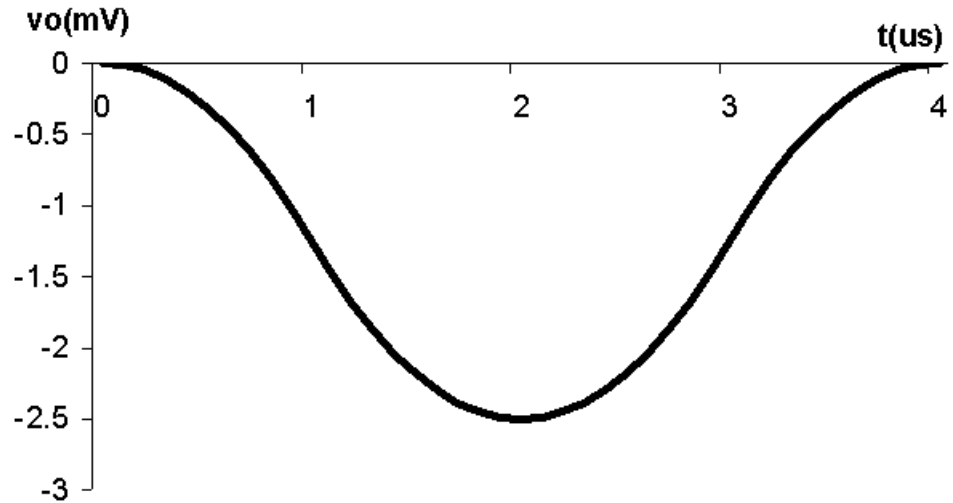


[c] The output voltage will also repeat. This follows from the observation that at  $t = 4\mu\text{s}$  the output voltage is zero, hence there is no energy stored in the capacitor. This means the circuit is in the same state at  $t = 4\mu\text{s}$  as it was at  $t = 0$ , thus as  $v_g$  repeats itself, so will  $v_o$ .

- P 7.97 [a]** While  $T_2$  has been ON,  $C_2$  is charged to  $V_{CC}$ , positive on the left terminal. At the instant  $T_1$  turns ON the capacitor  $C_2$  is connected across  $b_2 - e_2$ , thus  $v_{be2} = -V_{CC}$ . This negative voltage snaps  $T_2$  OFF. Now the polarity of the voltage on  $C_2$  starts to reverse, that is, the right-hand terminal of  $C_2$  starts to charge toward  $+V_{CC}$ . At the same time,  $C_1$  is charging toward  $V_{CC}$ , positive on the right. At the instant the charge on  $C_2$  reaches zero,  $v_{be2}$  is zero,  $T_2$  turns ON. This makes  $v_{be1} = -V_{CC}$  and  $T_1$  snaps OFF. Now the capacitors  $C_1$  and  $C_2$  start to charge with the polarities to turn  $T_1$  ON and  $T_2$  OFF. This switching action repeats itself over and over as long as the circuit is energized. At the instant  $T_1$  turns ON, the voltage controlling the state of  $T_2$  is governed by the following circuit:

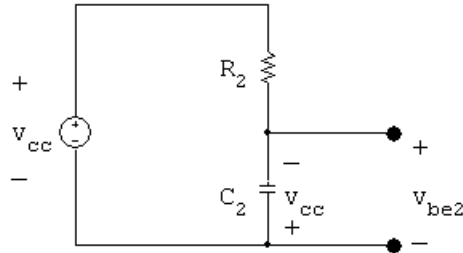

It follows that  $v_{be2} = V_{CC} - 2V_{CC}e^{-t/R_2C_2}$ .

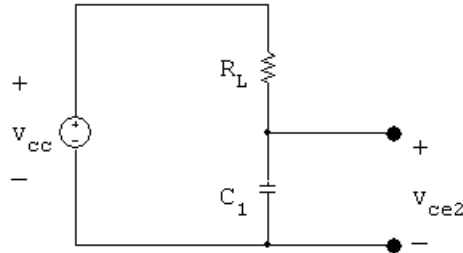- [b]** While  $T_2$  is OFF and  $T_1$  is ON, the output voltage  $v_{ce2}$  is the same as the voltage across  $C_1$ , thus




It follows that  $v_{ce2} = V_{CC} - V_{CC}e^{-t/R_LC_1}$ .

- [c]**  $T_2$  will be OFF until  $v_{be2}$  reaches zero. As soon as  $v_{be2}$  is zero,  $i_{b2}$  will become positive and turn  $T_2$  ON.  $v_{be2} = 0$  when  $V_{CC} - 2V_{CC}e^{-t/R_2C_2} = 0$ , or when  $t = R_2C_2 \ln 2$ .

- [d]** When  $t = R_2C_2 \ln 2$ , we have

$$v_{ce2} = V_{CC} - V_{CC}e^{-(R_2C_2 \ln 2)/(R_LC_1)} = V_{CC} - V_{CC}e^{-10 \ln 2} \cong V_{CC}$$

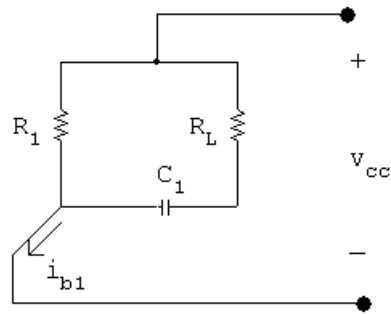- [e]** Before  $T_1$  turns ON,  $i_{b1}$  is zero. At the instant  $T_1$  turns ON, we have




$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L} e^{-t/R_L C_1}$$

**[f]** At the instant  $T_2$  turns back ON,  $t = R_2 C_2 \ln 2$ ; therefore


$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L} e^{-10 \ln 2} \cong \frac{V_{CC}}{R_1}$$

When  $T_2$  turns OFF,  $i_{b1}$  drops to zero instantaneously.

**[g]**

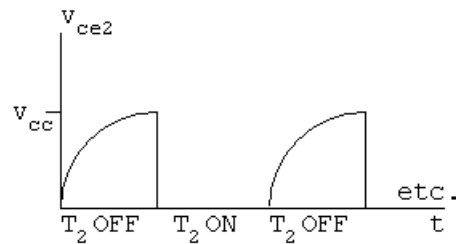

**[h]**

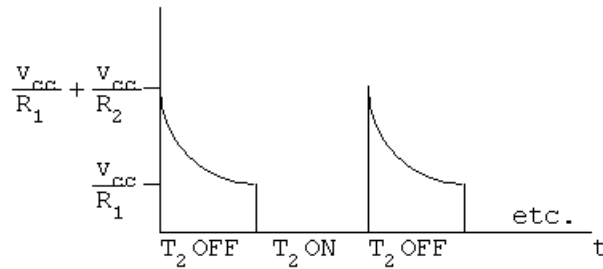

P 7.98 **[a]**  $t_{OFF2} = R_2 C_2 \ln 2 = 14.43 \times 10^3 (1 \times 10^{-9}) \ln 2 \cong 10 \mu s$

**[b]**  $t_{ON2} = R_1 C_1 \ln 2 \cong 10 \mu s$

**[c]**  $t_{OFF1} = R_1 C_1 \ln 2 \cong 10 \mu s$

**[d]**  $t_{ON1} = R_2 C_2 \ln 2 \cong 10 \mu s$

**[e]**  $i_{b1} = \frac{10}{1000} + \frac{10}{14,430} \cong 10.69 \text{ mA}$

**[f]**  $i_{b1} = \frac{10}{14,430} + \frac{10}{1000} e^{-10} \cong 0.693 \text{ mA}$

**[g]**  $v_{ce2} = 10 - 10e^{-10} \cong 10 \text{ V}$

**P 7.99 [a]**  $t_{\text{OFF}2} = R_2 C_2 \ln 2 = (14.43 \times 10^3)(0.8 \times 10^{-9}) \ln 2 \cong 8 \mu\text{s}$

**[b]**  $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

**[c]**  $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

**[d]**  $t_{\text{ON}1} = R_2 C_2 \ln 2 = 8 \mu\text{s}$

**[e]**  $i_{b1} = 10.69 \text{ mA}$

**[f]**  $i_{b1} = \frac{10}{14,430} + \frac{10}{1000}e^{-8} \cong 0.693 \text{ mA}$

**[g]**  $v_{ce2} = 10 - 10e^{-8} \cong 10 \text{ V}$

Note in this circuit  $T_2$  is OFF  $8 \mu\text{s}$  and ON  $10 \mu\text{s}$  of every cycle, whereas  $T_1$  is ON  $8 \mu\text{s}$  and OFF  $10 \mu\text{s}$  every cycle.

**P 7.100** If  $R_1 = R_2 = 50R_L = 100 \text{ k}\Omega$ , then

$$C_1 = \frac{48 \times 10^{-6}}{100 \times 10^3 \ln 2} = 692.49 \text{ pF}; \quad C_2 = \frac{36 \times 10^{-6}}{100 \times 10^3 \ln 2} = 519.37 \text{ pF}$$

If  $R_1 = R_2 = 6R_L = 12 \text{ k}\Omega$ , then

$$C_1 = \frac{48 \times 10^{-6}}{12 \times 10^3 \ln 2} = 5.77 \text{ nF}; \quad C_2 = \frac{36 \times 10^{-6}}{12 \times 10^3 \ln 2} = 4.33 \text{ nF}$$

Therefore  $692.49 \text{ pF} \leq C_1 \leq 5.77 \text{ nF}$  and  $519.37 \text{ pF} \leq C_2 \leq 4.33 \text{ nF}$


- P 7.101 [a]**  $T_2$  is normally ON since its base current  $i_{b2}$  is greater than zero, i.e.,  $i_{b2} = V_{CC}/R$  when  $T_2$  is ON. When  $T_2$  is ON,  $v_{ce2} = 0$ , therefore  $i_{b1} = 0$ . When  $i_{b1} = 0$ ,  $T_1$  is OFF. When  $T_1$  is OFF and  $T_2$  is ON, the capacitor  $C$  is charged to  $V_{CC}$ , positive at the left terminal. This is a stable state; there is nothing to disturb this condition if the circuit is left to itself.
- [b]** When  $S$  is closed momentarily,  $v_{be2}$  is changed to  $-V_{CC}$  and  $T_2$  snaps OFF. The instant  $T_2$  turns OFF,  $v_{ce2}$  jumps to  $V_{CC}R_1/(R_1 + R_L)$  and  $i_{b1}$  jumps to  $V_{CC}/(R_1 + R_L)$ , which turns  $T_1$  ON.
- [c]** As soon as  $T_1$  turns ON, the charge on  $C$  starts to reverse polarity. Since  $v_{be2}$  is the same as the voltage across  $C$ , it starts to increase from  $-V_{CC}$  toward  $+V_{CC}$ . However,  $T_2$  turns ON as soon as  $v_{be2} = 0$ . The equation for  $v_{be2}$  is  $v_{be2} = V_{CC} - 2V_{CC}e^{-t/RC}$ .  $v_{be2} = 0$  when  $t = RC \ln 2$ , therefore  $T_2$  stays OFF for  $RC \ln 2$  seconds.

**P 7.102 [a]** For  $t < 0$ ,  $v_{ce2} = 0$ . When the switch is momentarily closed,  $v_{ce2}$  jumps to

$$v_{ce2} = \left( \frac{V_{CC}}{R_1 + R_L} \right) R_1 = \frac{6(5)}{25} = 1.2 \text{ V}$$



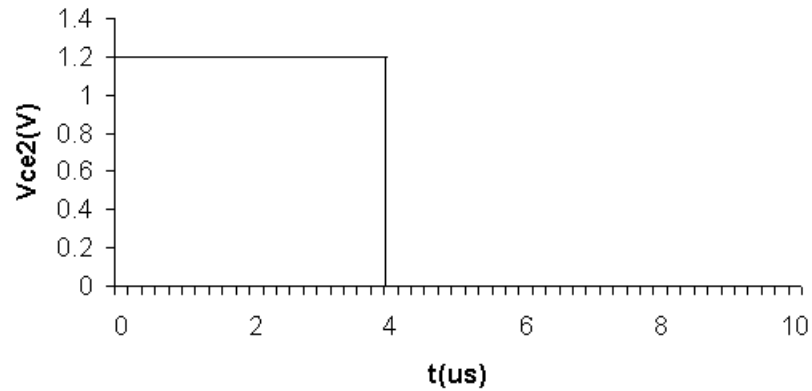$T_2$  remains open for  $(23,083)(250) \times 10^{-12} \ln 2 \cong 4 \mu\text{s}$ .




$$\text{[b]} \quad i_{b2} = \frac{V_{CC}}{R} = 259.93 \mu\text{A}, \quad -5 \leq t \leq 0 \mu\text{s}$$

$$i_{b2} = 0, \quad 0 < t < RC \ln 2$$

$$i_{b2} = \frac{V_{CC}}{R} + \frac{V_{CC}}{R_L} e^{-(t-RC \ln 2)/R_L C}$$
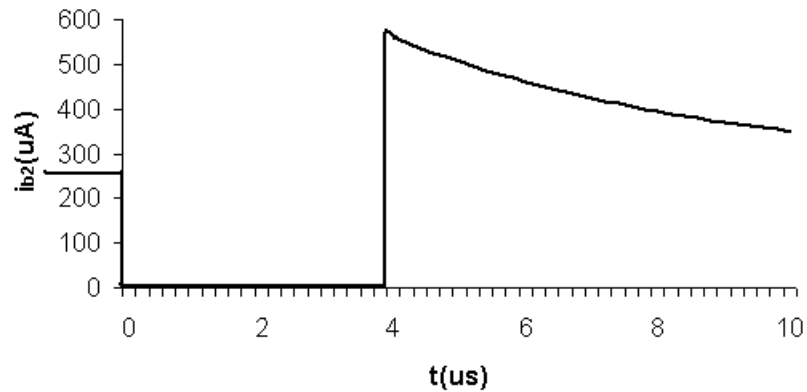
$$= 259.93 + 300 e^{-0.2 \times 10^6 (t-4 \times 10^{-6})} \mu\text{A}, \quad RC \ln 2 < t$$



P 7.103 [a] We want the lamp to be in its nonconducting state for no more than 10 s, the value of  $t_o$ :

$$10 = R(10 \times 10^{-6}) \ln \frac{1-6}{4-6} \quad \text{and} \quad R = 1.091 \text{ M}\Omega$$

[b] When the lamp is conducting

$$V_{Th} = \frac{20 \times 10^3}{20 \times 10^3 + 1.091 \times 10^6} (6) = 0.108 \text{ V}$$


$$R_{Th} = 20 \text{ k}\Omega || 1.091 \text{ M}\Omega = 19,640 \Omega$$

So,

$$(t_c - t_o) = (19,640)(10 \times 10^{-6}) \ln \frac{4 - 0.108}{1 - 0.108} = 0.289 \text{ s}$$

The flash lasts for 0.289 s.

P 7.104 [a] At  $t = 0$  we have

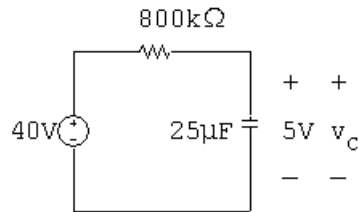

$$\tau = (800)(25) \times 10^{-3} = 20 \text{ sec}; \quad 1/\tau = 0.05$$


$$v_c(\infty) = 40 \text{ V}; \quad v_c(0) = 5 \text{ V}$$

$$v_c = 40 - 35e^{-0.05t} \text{ V}, \quad 0 \leq t \leq t_o$$


$$40 - 35e^{-0.05t_o} = 15; \quad \therefore e^{0.05t_o} = 1.4$$

$$t_o = 20 \ln 1.4 \text{ s} = 6.73 \text{ s}$$

At  $t = t_o$  we have

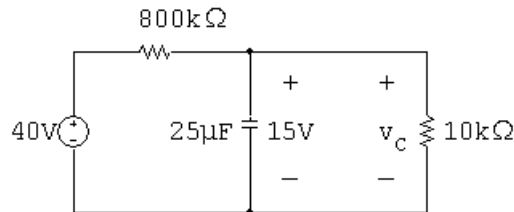

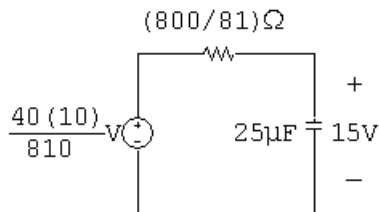The Thévenin equivalent with respect to the capacitor is



$$\tau = \left( \frac{800}{81} \right) (25) \times 10^{-3} = \frac{20}{81} \text{ s}; \quad \frac{1}{\tau} = \frac{81}{20} = 4.05$$

$$v_c(t_o) = 15 \text{ V}; \quad v_c(\infty) = \frac{40}{81} \text{ V}$$

$$v_c(t) = \frac{40}{81} + \left( 15 - \frac{40}{81} \right) e^{-4.05(t-t_o)} \text{ V} = \frac{40}{81} + \frac{1175}{81} e^{-4.05(t-t_o)}$$

$$\therefore \frac{40}{81} + \frac{1175}{81} e^{-4.05(t-t_o)} = 5$$

$$\frac{1175}{81}e^{-4.05(t-t_o)} = \frac{365}{81}$$


$$e^{4.05(t-t_o)} = \frac{1175}{365} = 3.22$$

$$t - t_o = \frac{1}{4.05} \ln 3.22 \cong 0.29 \text{ s}$$

One cycle = 7.02 seconds.

$$N = 60/7.02 = 8.55 \text{ flashes per minute}$$

**[b]** At  $t = 0$  we have

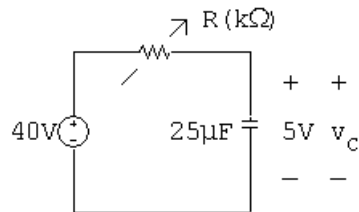


$$\tau = 25R \times 10^{-3}; \quad 1/\tau = 40/R$$

$$v_c = 40 - 35e^{-(40/R)t}$$

$$40 - 35e^{-(40/R)t_o} = 15$$

$$\therefore t_o = \frac{R}{40} \ln 1.4, \quad R \text{ in } \text{k}\Omega$$

At  $t = t_o$ :

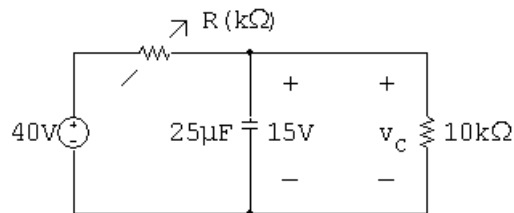

$$v_{Th} = \frac{10}{R+10}(40) = \frac{400}{R+10}; \quad R_{Th} = \frac{10R}{R+10} \text{ k}\Omega$$

$$\tau = \frac{(25)(10R) \times 10^{-3}}{R+10} = \frac{0.25R}{R+10}; \quad \frac{1}{\tau} = \frac{4(R+10)}{R}$$

$$v_c = \frac{400}{R+10} + \left(15 - \frac{400}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)}$$

$$\therefore \frac{400}{R+10} + \left[\frac{15R-250}{R+10}\right] e^{-\frac{4(R+10)}{R}(t-t_o)} = 5$$

$$\text{or } \left(\frac{15R-250}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)} = \frac{5R-350}{(R+10)}$$

$$\therefore e^{\frac{4(R+10)}{R}(t-t_o)} = \frac{3R-50}{R-70}$$

$$\therefore t - t_o = \frac{R}{4(R+10)} \ln \left( \frac{3R-50}{R-70} \right)$$

At 12 flashes per minute  $t_o + (t - t_o) = 5$  s

$$\therefore \underbrace{\frac{R}{40} \ln 1.4}_{\text{dominant term}} + \frac{R}{4(R+10)} \ln \left( \frac{3R-50}{R-70} \right) = 5$$

dominant  
term

Start the trial-and-error procedure by setting  $(R/40) \ln 1.4 = 5$ , then  $R = 200/(\ln 1.4)$  or  $594.40 \text{ k}\Omega$ . If  $R = 594.40 \text{ k}\Omega$  then  $t - t_o \cong 0.29$  s.

Second trial set  $(R/40) \ln 1.4 = 4.7$  s or  $R = 558.74 \text{ k}\Omega$ .

With  $R = 558.74 \text{ k}\Omega$ ,  $t - t_o \cong 0.30$  s

The procedure converges to  $R = 559.3 \text{ k}\Omega$

P 7.105 [a]  $t_o = RC \ln \left( \frac{V_{\min} - V_s}{V_{\max} - V_s} \right) = (3700)(250 \times 10^{-6}) \ln \left( \frac{-700}{-100} \right)$

$$= 1.80 \text{ s}$$

$$t_c - t_o = \frac{RCR_L}{R + R_L} \ln \left( \frac{V_{\max} - V_{\text{Th}}}{V_{\min} - V_{\text{Th}}} \right)$$

$$\frac{R_L}{R + R_L} = \frac{1.3}{1.3 + 3.7} = 0.26 \quad RC = (3700)(250 \times 10^{-6}) = 0.925 \text{ s}$$

$$V_{\text{Th}} = \frac{1000(1.3)}{1.3 + 3.7} = 260 \text{ V} \quad R_{\text{Th}} = 3.7 \text{ k} || 1.3 \text{ k} = 962 \Omega$$

$$\therefore t_c - t_o = (0.925)(0.26) \ln(640/40) = 0.67 \text{ s}$$

$$\therefore t_c = 1.8 + 0.67 = 2.47 \text{ s}$$

$$\text{flashes/min} = \frac{60}{2.47} = 24.32$$

[b]  $0 \leq t \leq t_o$ :

$$v_L = 1000 - 700e^{-t/\tau_1}$$

$$\tau_1 = RC = 0.925 \text{ s}$$

$t_o \leq t \leq t_c$ :


$$v_L = 260 + 640e^{-(t-t_o)/\tau_2}$$

$$\tau_2 = R_{\text{Th}}C = 962(250) \times 10^{-6} = 0.2405 \text{ s}$$

$$0 \leq t \leq t_o : \quad i = \frac{1000 - v_L}{3700} = \frac{7}{37} e^{-t/0.925} \text{ A}$$

$$t_o \leq t \leq t_c : \quad i = \frac{1000 - v_L}{3700} = \frac{74}{370} - \frac{64}{370} e^{-(t-t_o)/0.2405}$$

Graphically,  $i$  versus  $t$  is

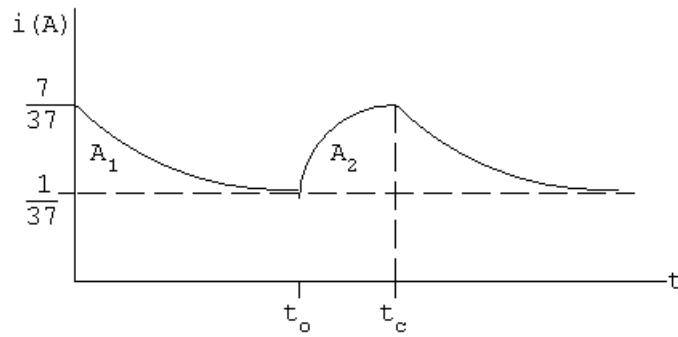

The average value of  $i$  will equal the areas  $(A_1 + A_2)$  divided by  $t_c$ .

$$\therefore i_{\text{avg}} = \frac{A_1 + A_2}{t_c}$$

$$\begin{aligned} A_1 &= \frac{7}{37} \int_0^{t_o} e^{-t/0.925} dt \\ &= \frac{6.475}{37} (1 - e^{-\ln 7}) = 0.15 \text{ A-s} \end{aligned}$$

$$\begin{aligned} A_2 &= \int_{t_o}^{t_c} \frac{74 - 64e^{-(t-t_o)/0.2405}}{370} dt \\ &= \frac{74}{370} (t_c - t_o) + \frac{15.392}{370} (e^{-\ln 16} - 1) \\ &= \frac{17.797}{370} \ln 16 - \frac{15.392}{370} (1 - e^{-\ln 16}) \\ &= 0.09436 \text{ A-s} \end{aligned}$$


$$i_{\text{avg}} = \frac{(0.15 + 0.09436)}{0.925 \ln 7 + 0.2405 \ln 16} (1000) = 99.06 \text{ mA}$$

$$\text{[c]} P_{\text{avg}} = (1000)(99.06 \times 10^{-3}) = 99.06 \text{ W}$$

$$\text{No. of kw hrs/yr} = \frac{(99.06)(24)(365)}{1000} = 867.77$$

$$\text{Cost/year} = (867.77)(0.05) = 43.39 \text{ dollars/year}$$

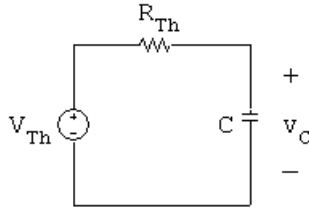P 7.106 [a] Replace the circuit attached to the capacitor with its Thévenin equivalent, where the equivalent resistance is the parallel combination of the two resistors, and the open-circuit voltage is obtained by voltage division across the lamp resistance. The resulting circuit is



$$R_{Th} = R \parallel R_L = \frac{RR_L}{R + R_L}; \quad V_{Th} = \frac{R_L}{R + R_L} V_s$$

From this circuit,

$$v_C(\infty) = V_{Th}; \quad v_C(0) = V_{\max}; \quad \tau = R_{Th}C$$

Thus,

$$v_C(t) = V_{Th} + (V_{\max} - V_{Th})e^{-(t-t_o)/\tau}$$

where

$$\tau = \frac{RR_L C}{R + R_L}$$

**[b]** Now, set  $v_C(t_c) = V_{\min}$  and solve for  $(t_c - t_o)$ :

$$V_{Th} + (V_{\max} - V_{Th})e^{-(t_c-t_o)/\tau} = V_{\min}$$

$$e^{-(t_c-t_o)/\tau} = \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$\frac{-(t_c - t_o)}{\tau} = \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$(t_c - t_o) = -\frac{RR_L C}{R + R_L} \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$(t_c - t_o) = \frac{RR_L C}{R + R_L} \ln \frac{V_{\max} - V_{Th}}{V_{\min} - V_{Th}}$$

P 7.107 **[a]**  $0 \leq t \leq 0.5$ :

$$i = \frac{21}{60} + \left( \frac{30}{60} - \frac{21}{60} \right) e^{-t/\tau} \quad \text{where } \tau = L/R.$$

$$i = 0.35 + 0.15e^{-60t/L}$$

$$i(0.5) = 0.35 + 0.15e^{-30/L} = 0.40$$

$$\therefore e^{30/L} = 3; \quad L = \frac{30}{\ln 3} = 27.31 \text{ H}$$

**[b]**  $0 \leq t \leq t_r$ , where  $t_r$  is the time the relay releases:

$$i = 0 + \left( \frac{30}{60} - 0 \right) e^{-60t/L} = 0.5e^{-60t/L}$$

$$\therefore 0.4 = 0.5e^{-60t_r/L}; \quad e^{60t_r/L} = 1.25$$

$$t_r = \frac{27.31 \ln 1.25}{60} \cong 0.10 \text{ s}$$