

# The Laplace Transform in Circuit Analysis

## Assessment Problems

AP 13.1 [a]  $Y = \frac{1}{R} + \frac{1}{sL} + sC = \frac{C[s^2 + (1/RC)s + (1/LC)]}{s}$

$$\frac{1}{RC} = \frac{10^6}{(500)(0.025)} = 80,000; \quad \frac{1}{LC} = 25 \times 10^8$$

Therefore  $Y = \frac{25 \times 10^{-9}(s^2 + 80,000s + 25 \times 10^8)}{s}$

[b]  $-z_{1,2} = -40,000 \pm \sqrt{16 \times 10^8 - 25 \times 10^8} = -40,000 \pm j30,000 \text{ rad/s}$

$$-z_1 = -40,000 - j30,000 \text{ rad/s}$$

$$-z_2 = -40,000 + j30,000 \text{ rad/s}$$

$$-p_1 = 0 \text{ rad/s}$$

AP 13.2 [a]  $Z = 2000 + \frac{1}{Y} = 2000 + \frac{4 \times 10^7 s}{s^2 + 80,000s + 25 \times 10^8}$

$$= \frac{2000(s^2 + 10^5 s + 25 \times 10^8)}{s^2 + 80,000s + 25 \times 10^8} = \frac{2000(s + 50,000)^2}{s^2 + 80,000s + 25 \times 10^8}$$


[b]  $-z_1 = -z_2 = -50,000 \text{ rad/s}$

$$-p_1 = -40,000 - j30,000 \text{ rad/s}$$

$$-p_2 = -40,000 + j30,000 \text{ rad/s}$$

AP 13.3 [a] At  $t = 0^-$ ,  $0.2v_1 = 0.8v_2$ ;  $v_1 = 4v_2$ ;  $v_1 + v_2 = 100 \text{ V}$

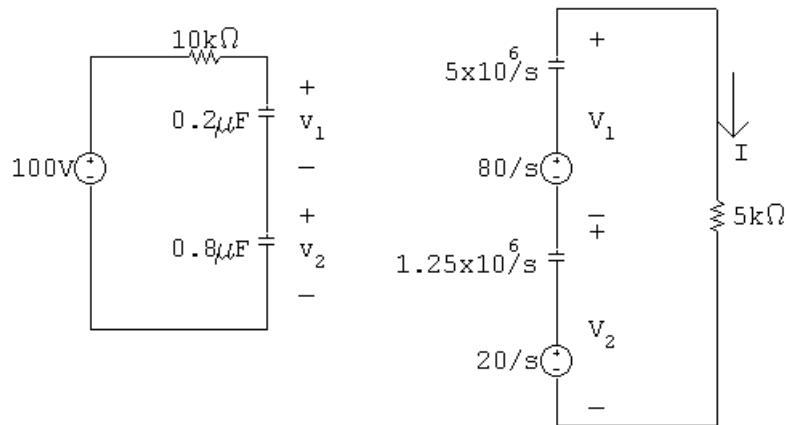Therefore  $v_1(0^-) = 80 \text{ V} = v_1(0^+)$ ;  $v_2(0^-) = 20 \text{ V} = v_2(0^+)$



$$I = \frac{(80/s) + (20/s)}{5000 + [(5 \times 10^6)/s] + (1.25 \times 10^6/s)} = \frac{20 \times 10^{-3}}{s + 1250}$$


$$V_1 = \frac{80}{s} - \frac{5 \times 10^6}{s} \left( \frac{20 \times 10^{-3}}{s + 1250} \right) = \frac{80}{s + 1250}$$

$$V_2 = \frac{20}{s} - \frac{1.25 \times 10^6}{s} \left( \frac{20 \times 10^{-3}}{s + 1250} \right) = \frac{20}{s + 1250}$$

[b]  $i = 20e^{-1250t}u(t) \text{ mA}$ ;  $v_1 = 80e^{-1250t}u(t) \text{ V}$

$v_2 = 20e^{-1250t}u(t) \text{ V}$

AP 13.4 [a]

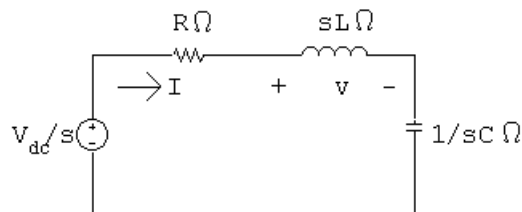

$$I = \frac{V_{dc}/s}{R + sL + (1/sC)} = \frac{V_{dc}/L}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{V_{dc}}{L} = 40; \quad \frac{R}{L} = 1.2; \quad \frac{1}{LC} = 1.0$$

$$I = \frac{40}{s^2 + 1.2s + 1}$$

$$\text{[b]} \quad I = \frac{40}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)} = \frac{K_1}{s + 0.6 - j0.8} + \frac{K_1^*}{s + 0.6 + j0.8}$$

$$K_1 = \frac{40}{j1.6} = -j25 = 25/\underline{-90^\circ}; \quad K_1^* = 25/\underline{90^\circ}$$

$$i = 50e^{-0.6t} \cos(0.8t - 90^\circ) = [50e^{-0.6t} \sin 0.8t]u(t) \text{ A}$$


$$\text{[c]} \quad V = sLI = \frac{160s}{s^2 + 1.2s + 1} = \frac{160s}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)}$$

$$= \frac{K_1}{s + 0.6 - j0.8} + \frac{K_1^*}{s + 0.6 + j0.8}$$

$$K_1 = \frac{160(-0.6 + j0.8)}{j1.6} = 100/\underline{36.87^\circ}$$

$$\text{[d]} \quad v(t) = [200e^{-0.6t} \cos(0.8t + 36.87^\circ)]u(t) \text{ V}$$

AP 13.5 [a]

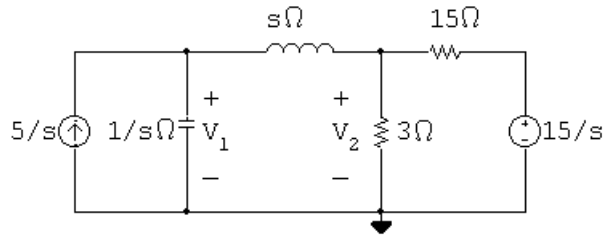

The two node voltage equations are

$$\frac{V_1 - V_2}{s} + V_1 s = \frac{5}{s} \quad \text{and} \quad \frac{V_2}{3} + \frac{V_2 - V_1}{s} + \frac{V_2 - (15/s)}{15} = 0$$

Solving for  $V_1$  and  $V_2$  yields

$$V_1 = \frac{5(s+3)}{s(s^2 + 2.5s + 1)}, \quad V_2 = \frac{2.5(s^2 + 6)}{s(s^2 + 2.5s + 1)}$$

[b] The partial fraction expansions of  $V_1$  and  $V_2$  are

$$V_1 = \frac{15}{s} - \frac{50/3}{s + 0.5} + \frac{5/3}{s + 2} \quad \text{and} \quad V_2 = \frac{15}{s} - \frac{125/6}{s + 0.5} + \frac{25/3}{s + 2}$$

It follows that

$$v_1(t) = \left[ 15 - \frac{50}{3}e^{-0.5t} + \frac{5}{3}e^{-2t} \right] u(t) \text{ V} \quad \text{and}$$


$$v_2(t) = \left[ 15 - \frac{125}{6}e^{-0.5t} + \frac{25}{3}e^{-2t} \right] u(t) \text{ V}$$

$$\text{[c]} \quad v_1(0^+) = 15 - \frac{50}{3} + \frac{5}{3} = 0$$

$$v_2(0^+) = 15 - \frac{125}{6} + \frac{25}{3} = 2.5 \text{ V}$$

**[d]**  $v_1(\infty) = 15 \text{ V}; \quad v_2(\infty) = 15 \text{ V}$


AP 13.6 **[a]**

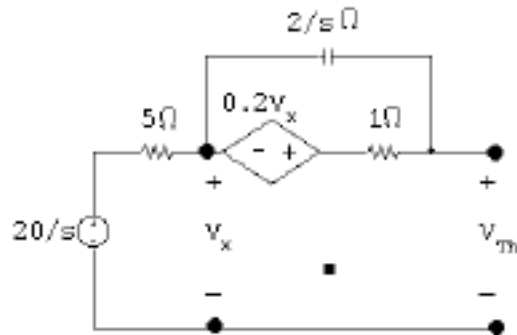

With no load across terminals  $a-b$ ,  $V_x = 20/s$ :

$$\frac{1}{2} \left[ \frac{20}{s} - V_{Th} \right] s + \left[ 1.2 \left( \frac{20}{s} \right) - V_{Th} \right] = 0$$

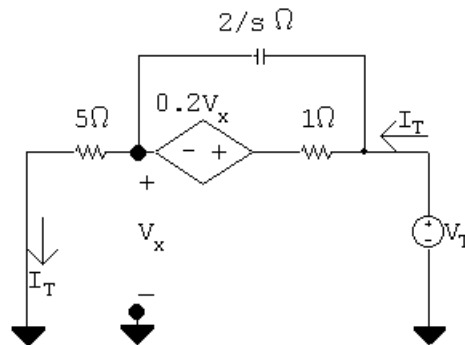therefore  $V_{Th} = \frac{20(s + 2.4)}{s(s + 2)}$



$V_x = 5I_T$  and  $Z_{Th} = \frac{V_T}{I_T}$


Solving for  $I_T$  gives

$$I_T = \frac{(V_T - 5I_T)s}{2} + V_T - 6I_T$$

Therefore

$14I_T = V_T s - 5sI_T + 2V_T$ ; therefore  $Z_{Th} = \frac{5(s + 2.8)}{s + 2}$

**[b]**

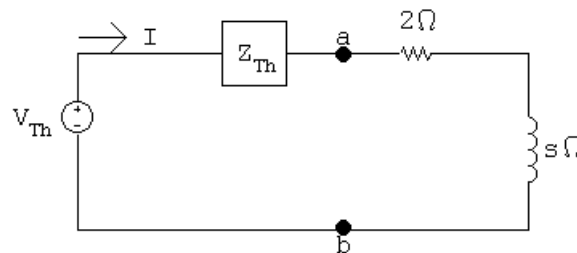

$$I = \frac{V_{Th}}{Z_{Th} + 2 + s} = \frac{20(s + 2.4)}{s(s + 3)(s + 6)}$$

AP 13.7 [a]  $i_2 = 1.25e^{-t} - 1.25e^{-3t}$ ; therefore  $\frac{di_2}{dt} = -1.25e^{-t} + 3.75e^{-3t}$

Therefore  $\frac{di_2}{dt} = 0$  when

$$1.25e^{-t} = 3.75e^{-3t} \quad \text{or} \quad e^{2t} = 3, \quad t = 0.5(\ln 3) = 549.31 \text{ ms}$$

$$i_2(\text{max}) = 1.25[e^{-0.549} - e^{-3(0.549)}] = 481.13 \text{ mA}$$

[b] From Eqs. 13.68 and 13.69, we have

$$\Delta = 12(s^2 + 4s + 3) = 12(s + 1)(s + 3) \quad \text{and} \quad N_1 = 60(s + 2)$$

Therefore  $I_1 = \frac{N_1}{\Delta} = \frac{5(s + 2)}{(s + 1)(s + 3)}$

A partial fraction expansion leads to the expression

$$I_1 = \frac{2.5}{s + 1} + \frac{2.5}{s + 3}$$

Therefore we get

$$i_1 = 2.5[e^{-t} + e^{-3t}]u(t) \text{ A}$$

[c]  $\frac{di_1}{dt} = -2.5[e^{-t} + 3e^{-3t}]$ ;  $\frac{di_1(0.54931)}{dt} = -2.89 \text{ A/s}$


[d] When  $i_2$  is at its peak value,

$$\frac{di_2}{dt} = 0$$

Therefore  $L_2 \left( \frac{di_2}{dt} \right) = 0$  and  $i_2 = - \left( \frac{M}{12} \right) \left( \frac{di_1}{dt} \right)$

[e]  $i_2(\text{max}) = \frac{-2(-2.89)}{12} = 481.13 \text{ mA}$  (Checks)

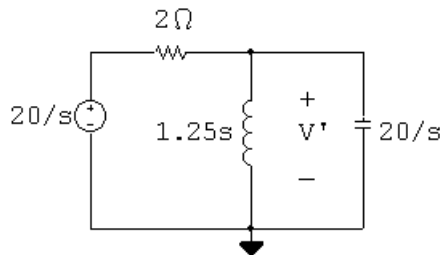AP 13.8 [a] The  $s$ -domain circuit with the voltage source acting alone is




$$\frac{V' - (20/s)}{2} + \frac{V'}{1.25s} + \frac{V's}{20} = 0$$

$$V' = \frac{200}{(s+2)(s+8)} = \frac{100/3}{s+2} - \frac{100/3}{s+8}$$

$$v' = \frac{100}{3}[e^{-2t} - e^{-8t}]u(t) \text{ V}$$

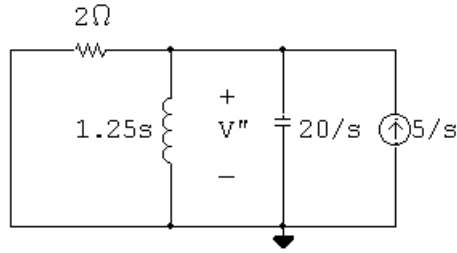**[b]** With the current source acting alone,



$$\frac{V''}{2} + \frac{V''}{1.25s} + \frac{V''s}{20} = \frac{5}{s}$$

$$V'' = \frac{100}{(s+2)(s+8)} = \frac{50/3}{s+2} - \frac{50/3}{s+8}$$

$$v'' = \frac{50}{3}[e^{-2t} - e^{-8t}]u(t) \text{ V}$$

**[c]**  $v = v' + v'' = [50e^{-2t} - 50e^{-8t}]u(t) \text{ V}$

AP 13.9 **[a]**  $\frac{V_o}{s+2} + \frac{V_o s}{10} = I_g$ ;      therefore  $\frac{V_o}{I_g} = H(s) = \frac{10(s+2)}{s^2 + 2s + 10}$

**[b]**  $-z_1 = -2 \text{ rad/s}$ ;       $-p_1 = -1 + j3 \text{ rad/s}$ ;       $-p_2 = -1 - j3 \text{ rad/s}$

AP 13.10 **[a]**  $V_o = \frac{10(s+2)}{s^2 + 2s + 10} \cdot \frac{1}{s} = \frac{K_0}{s} + \frac{K_1}{s+1-j3} + \frac{K_1^*}{s+1+j3}$

$$K_0 = 2; \quad K_1 = (5/3)/\underline{-126.87^\circ}; \quad K_1^* = (5/3)/\underline{126.87^\circ}$$

$$v_o = [2 + (10/3)e^{-t} \cos(3t - 126.87^\circ)]u(t) \text{ V}$$

**[b]**  $V_o = \frac{10(s+2)}{s^2 + 2s + 10} \cdot 1 = \frac{K_2}{s+1-j3} + \frac{K_2^*}{s+1+j3}$

$$K_2 = 5.27/\underline{-18.43^\circ}; \quad K_2^* = 5.27/\underline{18.43^\circ}$$

$$v_o = [10.54e^{-t} \cos(3t - 18.43^\circ)]u(t) \text{ V}$$

AP 13.11 **[a]**  $H(s) = \mathcal{L}\{h(t)\} = \mathcal{L}\{v_o(t)\}$

$$\begin{aligned} v_o(t) &= 10,000 \cos \theta e^{-70t} \cos 240t - 10,000 \sin \theta e^{-70t} \sin 240t \\ &= 9600e^{-70t} \cos 240t - 2800e^{-70t} \sin 240t \end{aligned}$$

$$\begin{aligned}\text{Therefore } H(s) &= \frac{9600(s+70)}{(s+70)^2 + (240)^2} - \frac{2800(240)}{(s+70)^2 + (240)^2} \\ &= \frac{9600s}{s^2 + 140s + 62,500}\end{aligned}$$

$$\begin{aligned}\text{[b] } V_o(s) &= H(s) \cdot \frac{1}{s} = \frac{9600}{s^2 + 140s + 62,500} \\ &= \frac{K_1}{s+70-j240} + \frac{K_1^*}{s+70+j240}\end{aligned}$$

$$K_1 = \frac{9600}{j480} = -j20 = 20/\underline{-90^\circ}$$

Therefore

$$v_o(t) = [40e^{-70t} \cos(240t - 90^\circ)]u(t) \text{ V} = [40e^{-70t} \sin 240t]u(t) \text{ V}$$

AP 13.12 From Assessment Problem 13.9:

$$H(s) = \frac{10(s+2)}{s^2 + 2s + 10}$$

$$\text{Therefore } H(j4) = \frac{10(2+j4)}{10-16+j8} = 4.47/\underline{-63.43^\circ}$$

Thus,

$$v_o = (10)(4.47) \cos(4t - 63.43^\circ) = 44.7 \cos(4t - 63.43^\circ) \text{ V}$$

AP 13.13 [a] Let  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 50 \text{ k}\Omega$ ,  $C = 400 \text{ pF}$ ,  $R_2C = 2 \times 10^{-5}$

$$\text{then } V_1 = V_2 = \frac{V_g R_2}{R_2 + (1/sC)}$$

$$\text{Also } \frac{V_1 - V_g}{R_1} + \frac{V_1 - V_o}{R_1} = 0$$

$$\text{therefore } V_o = 2V_1 - V_g$$

$$\text{Now solving for } V_o/V_g, \text{ we get } H(s) = \frac{R_2Cs - 1}{R_2Cs + 1}$$

$$\text{It follows that } H(j50,000) = \frac{j-1}{j+1} = j1 = 1/\underline{90^\circ}$$

$$\text{Therefore } v_o = 10 \cos(50,000t + 90^\circ) \text{ V}$$

**[b]** Replacing  $R_2$  by  $R_x$  gives us  $H(s) = \frac{R_x C s - 1}{R_x C s + 1}$

Therefore

$$H(j50,000) = \frac{j20 \times 10^{-6} R_x - 1}{j20 \times 10^{-6} R_x + 1} = \frac{R_x + j50,000}{R_x - j50,000}$$

Thus,

$$\frac{50,000}{R_x} = \tan 60^\circ = 1.7321, \quad R_x = 28,867.51 \, \Omega$$



## Problems

P 13.1  $I_{scab} = I_N = \frac{-LI_0}{sL} = \frac{-I_0}{s}; \quad Z_N = sL$

Therefore, the Norton equivalent is the same as the circuit in Fig. 13.4.

P 13.2  $i = \frac{1}{L} \int_{0^-}^t v d\tau + I_0; \quad \text{therefore} \quad I = \left(\frac{1}{L}\right) \left(\frac{V}{s}\right) + \frac{I_0}{s} = \frac{V}{sL} + \frac{I_0}{s}$

P 13.3  $V_{Th} = V_{ab} = CV_o \left(\frac{1}{sC}\right) = \frac{V_o}{s}; \quad Z_{Th} = \frac{1}{sC}$

P 13.4 [a]  $Z = R + sL + \frac{1}{sC} = \frac{L[s^2 + (R/L)s + (1/LC)]}{s}$   
 $= \frac{0.0025[s^2 + 16 \times 10^7 s + 10^{10}]}{s}$


[b] Zeros at  $-62.5 \text{ rad/s}$  and  $-1.6 \times 10^8 \text{ rad/s}$   
 Pole at 0.

P 13.5 [a]  $Y = \frac{1}{R} + \frac{1}{sL} + sC = \frac{C[s^2 + (1/RC)s + (1/LC)]}{s}$

$$Z = \frac{1}{Y} = \frac{s/C}{s^2 + (1/RC)s + (1/LC)} = \frac{4 \times 10^6 s}{s^2 + 2000s + 64 \times 10^4}$$

[b] zero at  $-z_1 = 0$   
 poles at  $-p_1 = -400 \text{ rad/s}$  and  $-p_2 = -1600 \text{ rad/s}$

P 13.6 [a]

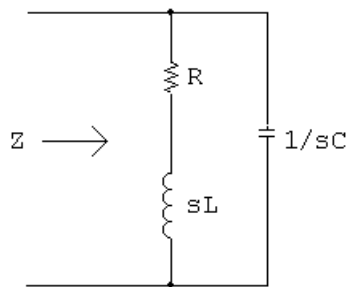

$$Z = \frac{(R + sL)(1/sC)}{R + sL + (1/sC)} = \frac{(1/C)(s + R/L)}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{R}{L} = \frac{250}{0.08} = 3125; \quad \frac{1}{LC} = \frac{1}{(0.08)(0.5 \times 10^{-6})} = 25 \times 10^6$$


$$Z = \frac{2 \times 10^6(s + 3125)}{s^2 + 3125s + 25 \times 10^6}$$

$$\text{[b]} \quad Z = \frac{2 \times 10^6(s + 3125)}{(s + 1562.5 - j4749.6)(s + 1562.5 + j4749.6)}$$

$$-z_1 = -3125 \text{ rad/s}; \quad -p_1 = -1562.5 + j4749.6 \text{ rad/s}$$

$$-p_2 = -1562.5 - j4749.6 \text{ rad/s}$$

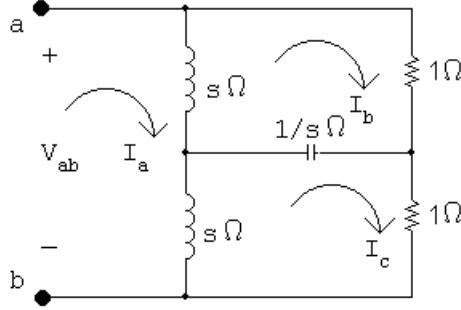P 13.7 Transform the Y-connection of the two resistors and the capacitor into the equivalent delta-connection:



where

$$Z_a = \frac{(1/s)(1) + (1)(1/s) + (1)(1)}{1/s} = s + 2$$

$$Z_b = Z_c = \frac{(1/s)(1) + (1)(1/s) + (1)(1)}{1} = \frac{s + 2}{s}$$

Then

$$Z_{ab} = Z_a \parallel [(s \parallel Z_c) + (s \parallel Z_b)] = Z_a \parallel 2(s \parallel Z_b)$$

$$s \parallel Z_b = \frac{s + 2}{s + (s + 2)/s} = \frac{s(s + 2)}{s^2 + s + 2}$$

$$\begin{aligned} Z_{ab} &= (s + 2) \parallel \frac{2s(s + 2)}{s^2 + s + 2} = \frac{2s(s + 2)^2}{(s + 2)(s^2 + s + 2) + 2s(s + 2)} \\ &= \frac{2s(s + 2)}{s^2 + 3s + 2} = \frac{2s}{s + 1} \end{aligned}$$

One zero at the origin (0 rad/s); one pole at  $-1$  rad/s.


$$\text{P 13.8} \quad Z_1 = \frac{16}{s} + s \parallel 4 = \frac{16}{s} + \frac{4s}{s + 4} = \frac{4(s^2 + 4s + 16)}{s(s + 4)}$$

$$Z_{ab} = 4 \parallel \frac{4(s^2 + 4s + 16)}{s(s + 4)} = \frac{16(s^2 + 4s + 16)}{8s^2 + 32s + 64}$$

$$= \frac{2(s^2 + 4s + 16)}{s^2 + 4s + 8} = \frac{2(s + 2 + j3.46)(s + 2 - j3.46)}{(s + 2 + j2)(s + 2 - j2)}$$

Zeros at  $-2 + j3.46$  rad/s and  $-2 - j3.46$  rad/s; poles at  $-2 + j2$  rad/s and  $-2 - j2$  rad/s.

P 13.9 [a] For  $t > 0$ :

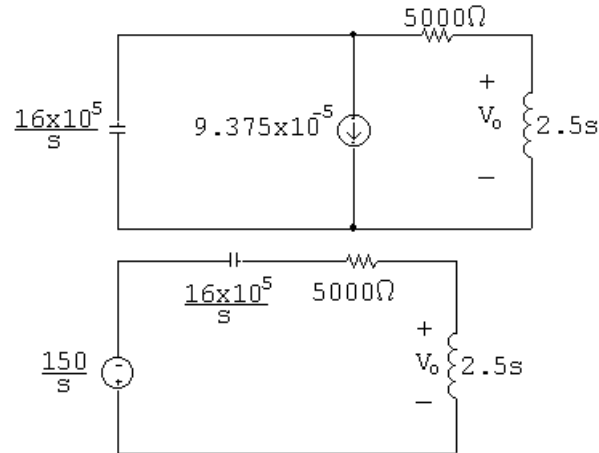

$$\text{[b]} \quad V_o = \frac{2.5s}{(16 \times 10^5)/s + 5000 + 2.5s} \left( \frac{-150}{s} \right)$$

$$= \frac{-150s}{s^2 + 2000s + 64 \times 10^4}$$

$$= \frac{-150s}{(s + 400)(s + 1600)}$$

$$\text{[c]} \quad V_o = \frac{K_1}{s + 400} + \frac{K_2}{s + 1600}$$


$$K_1 = \left. \frac{-150s}{s + 1600} \right|_{s=-400} = 50$$

$$K_2 = \left. \frac{-150s}{s + 400} \right|_{s=-1600} = -200$$

$$V_o = \frac{50}{s + 400} - \frac{200}{s + 1600}$$

$$v_o(t) = (50e^{-400t} - 200e^{-1600t})u(t) \text{ V}$$

P 13.10 [a] For  $t < 0$ :

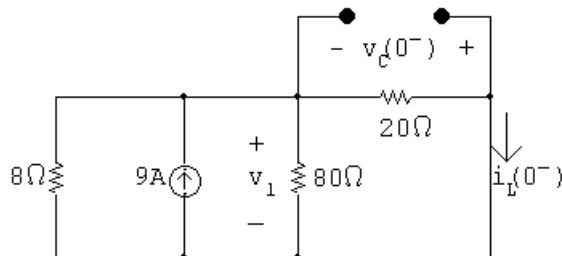


$$\frac{1}{R_e} = \frac{1}{8} + \frac{1}{80} + \frac{1}{20} = 0.1875; \quad R_e = 5.33 \Omega$$

$$v_1 = (9)(5.33) = 48 \text{ V}$$


$$i_L(0^-) = \frac{48}{20} = 2.4 \text{ A}$$

$$v_C(0^-) = -v_1 = -48 \text{ V}$$

For  $t = 0^+$ :

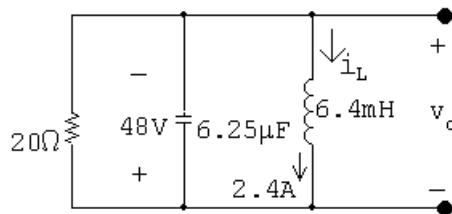

$s$ -domain circuit:

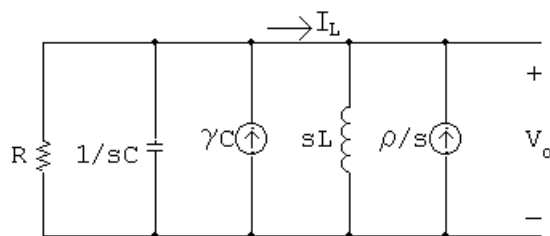

where

$$R = 20 \Omega; \quad C = 6.25 \mu\text{F}; \quad \gamma = -48 \text{ V};$$

$$L = 6.4 \text{ mH}; \quad \text{and} \quad \rho = -2.4 \text{ A}$$

[b]  $\frac{V_o}{R} + V_o sC - \gamma C + \frac{V_o}{sL} - \frac{\rho}{s} = 0$

$$\therefore V_o = \frac{\gamma[s + (\rho/\gamma C)]}{s^2 + (1/RC)s + (1/LC)}$$

$$\frac{\rho}{\gamma C} = \frac{-2.4}{(-48)(6.25 \times 10^{-6})} = 8000$$

$$\frac{1}{RC} = \frac{1}{(20)(6.25 \times 10^{-6})} = 8000$$

$$\frac{1}{LC} = \frac{1}{(6.4 \times 10^{-3})(6.25 \times 10^{-6})} = 25 \times 10^6$$

$$V_o = \frac{-48(s + 8000)}{s^2 + 8000s + 25 \times 10^6}$$


$$\begin{aligned} \text{[c]} \quad I_L &= \frac{V_o}{sL} - \frac{\rho}{s} = \frac{V_o}{0.0064s} + \frac{2.4}{s} \\ &= \frac{-7500(s + 8000)}{s(s^2 + 8000s + 25 \times 10^6)} + \frac{2.4}{s} = \frac{2.4(s + 4875)}{(s^2 + 8000s + 25 \times 10^6)} \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad V_o &= \frac{-48(s + 8000)}{s^2 + 8000s + 25 \times 10^6} \\ &= \frac{K_1}{s + 4000 - j3000} + \frac{K_1^*}{s + 4000 + j3000} \\ K_1 &= \left. \frac{-48(s + 8000)}{s + 4000 + j3000} \right|_{s=-4000+j3000} = 40 \angle 126.87^\circ \end{aligned}$$

$$v_o(t) = [80e^{-4000t} \cos(3000t + 126.87^\circ)]u(t) \text{ V}$$

$$\begin{aligned} \text{[e]} \quad I_L &= \frac{2.4(s + 4875)}{s^2 + 8000s + 25 \times 10^6} \\ &= \frac{K_1}{s + 4000 - j3000} + \frac{K_1^*}{s + 4000 + j3000} \\ K_1 &= \left. \frac{2.4(s + 4875)}{s + 4000 + j3000} \right|_{s=-4000+j3000} = 1.25 \angle -16.26^\circ \\ i_L(t) &= [2.5e^{-4000t} \cos(3000t - 16.26^\circ)]u(t) \text{ A} \end{aligned}$$

P 13.11 For  $t < 0$ :

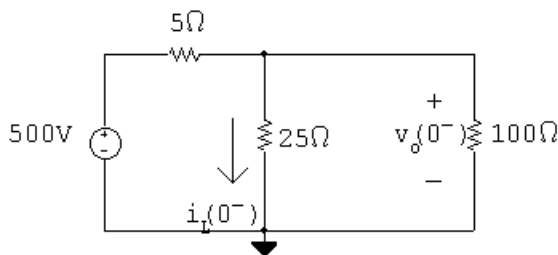


$$\frac{v_o(0^-) - 500}{5} + \frac{v_o(0^-)}{25} + \frac{v_o(0^-)}{100} = 0$$

$$25v_o(0^-) = 10,000 \quad \therefore \quad v_o(0^-) = 400 \text{ V}$$

$$i_L(0^-) = \frac{v_o(0^-)}{25} = \frac{400}{25} = 16 \text{ A}$$

For  $t > 0$  :

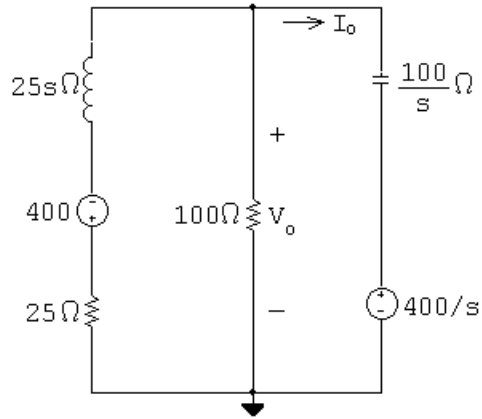

$$\frac{V_o + 400}{25 + 25s} + \frac{V_o}{100} + \frac{V_o - (400/s)}{100/s} = 0$$

$$V_o \left( \frac{1}{25 + 25s} + \frac{1}{100} + \frac{s}{100} \right) = 4 - \frac{400}{25 + 25s}$$

$$\therefore \quad V_o = \frac{400(s - 3)}{s^2 + 2s + 5}$$


$$I_o = \frac{V_o - (400/s)}{100/s} = \frac{-20s - 20}{s^2 + 2s + 5}$$

$$= \frac{K_1}{s + 1 - j2} + \frac{K_1^*}{s + 1 + j2}$$

$$K_1 = \left. \frac{-20(s + 1)}{s + 1 + j2} \right|_{s = -1 + j2} = -10$$


$$i_o(t) = [-20e^{-t} \cos 2t]u(t) \text{ A}$$

P 13.12 [a] For  $t < 0$ :

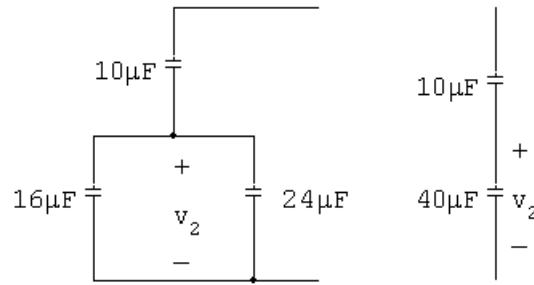

$$V_2 = \frac{10}{10 + 40}(450) = 90 \text{ V}$$

For  $t > 0$ :

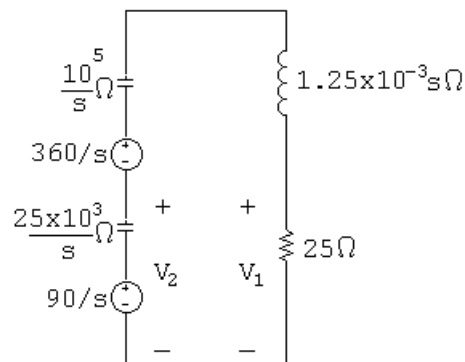


$$\begin{aligned} \text{[b]} \quad V_1 &= \frac{25(450/s)}{(125,000/s) + 25 + 1.25 \times 10^{-3}s} \\ &= \frac{9 \times 10^6}{s^2 + 20,000s + 10^8} = \frac{9 \times 10^6}{(s + 10,000)^2} \end{aligned}$$

$$v_1(t) = (9 \times 10^6 t e^{-10,000t})u(t) \text{ V}$$

$$\begin{aligned} \text{[c]} \quad V_2 &= \frac{90}{s} - \frac{(25,000/s)(450/s)}{(125,000/s) + 1.25 \times 10^{-3}s + 25} \\ &= \frac{90(s + 20,000)}{s^2 + 20,000s + 10^8} \\ &= \frac{900,000}{(s + 10,000)^2} + \frac{90}{s + 10,000} \end{aligned}$$

$$v_2(t) = [9 \times 10^5 t e^{-10,000t} + 90 e^{-10,000t}]u(t) \text{ V}$$

P 13.13 [a] For  $t < 0$ :

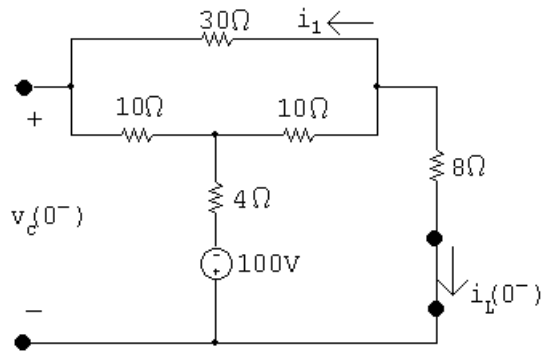


$$i_L(0^-) = \frac{-100}{4 + 10 \parallel 40 + 8} = \frac{-100}{20} = -5 \text{ A}$$

$$i_1 = \frac{10}{50}(5) = 1 \text{ A}$$

$$v_C(0^-) = 10(1) + 4(5) - 100 = -70 \text{ V}$$

For  $t > 0$ :

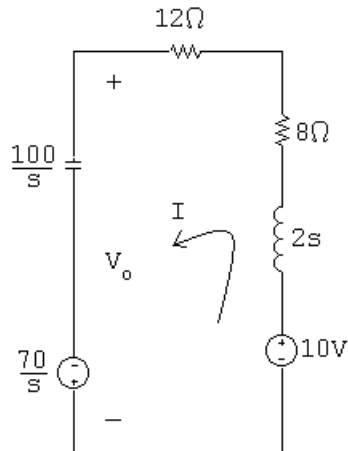

$$\text{[b]} (20 + 2s + 100/s)I = 10 + \frac{70}{s}$$

$$\therefore I = \frac{5(s+7)}{s^2 + 10s + 50}$$

$$V_o = \frac{100}{s}I - \frac{70}{s}$$

$$= \frac{-70s^2 - 200s}{s(s^2 + 10s + 50)} = \frac{-70(s + 20/7)}{s^2 + 10s + 50}$$


$$= \frac{K_1}{s + 5 - j5} + \frac{K_1^*}{s + 5 + j5}$$

$$K_1 = \frac{-70(s + 20/7)}{s + 5 + j5} \Big|_{s=-5+j5} = 38.1 \angle -156.8^\circ$$

$$\text{[c]} v_o(t) = 76.2e^{-5t} \cos(5t - 156.8^\circ)u(t) \text{ V}$$



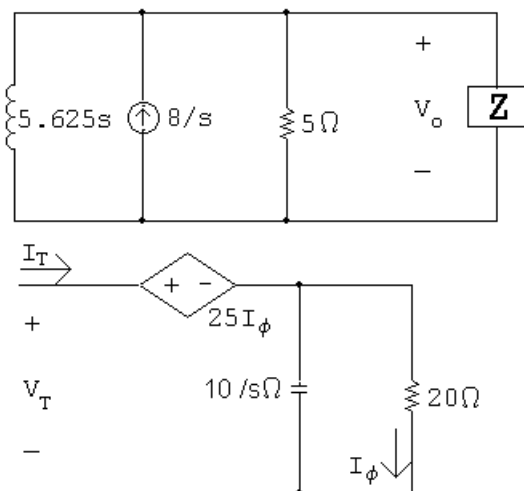P 13.14 [a]  $i_L(0^-) = i_L(0^+) = \frac{24}{3} = 8 \text{ A}$  directed upward



$$V_T = 25I_\phi + \left[ \frac{20(10/s)}{20 + (10/s)} \right] I_T = \frac{25I_T(10/s)}{20 + (10/s)} + \left( \frac{200}{10 + 20s} \right) I_T$$

$$\frac{V_T}{I_T} = Z = \frac{250 + 200}{20s + 10} = \frac{45}{2s + 1}$$

$$\frac{V_o}{5} + \frac{V_o(2s + 1)}{45} + \frac{V_o}{5.625s} = \frac{8}{s}$$

$$\frac{[9s + (2s + 1)s + 8]V_o}{45s} = \frac{8}{s}$$

$$V_o[2s^2 + 10s + 8] = 360$$

$$V_o = \frac{360}{2s^2 + 10s + 8} = \frac{180}{s^2 + 5s + 4}$$


[b]  $V_o = \frac{180}{(s + 1)(s + 4)} = \frac{K_1}{s + 1} + \frac{K_2}{s + 4}$

$$K_1 = \frac{180}{3} = 60; \quad K_2 = \frac{180}{-3} = -60$$

$$V_o = \frac{60}{s + 1} - \frac{60}{s + 4}$$

$$v_o(t) = [60e^{-t} - 60e^{-4t}]u(t) \text{ V}$$

P 13.15 [a]

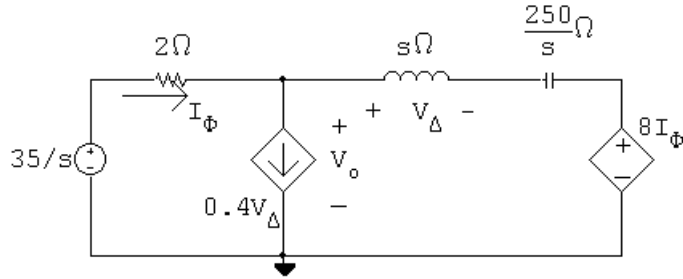

$$\frac{V_o - 35/s}{2} + 0.4V_\Delta + \frac{V_o - 8I_\phi}{s + (250/s)} = 0$$

$$V_\Delta = \left[ \frac{V_o - 8I_\phi}{s + (250/s)} \right] s; \quad I_\phi = \frac{(35/s) - V_o}{2}$$

Solving for  $V_o$  yields:

$$V_o = \frac{29.4s^2 + 56s + 1750}{s(s^2 + 2s + 50)} = \frac{29.4s^2 + 56s + 1750}{s(s + 1 - j7)(s + 1 + j7)}$$

$$V_o = \frac{K_1}{s} + \frac{K_2}{s + 1 - j7} + \frac{K_2^*}{s + 1 + j7}$$


$$K_1 = \frac{29.4s^2 + 56s + 1750}{s^2 + 2s + 50} \Big|_{s=0} = 35$$

$$K_2 = \frac{29.4s^2 + 56s + 1750}{s(s + 1 + j7)} \Big|_{s=-1-j7}$$

$$= -2.8 + j0.6 = 2.86/167.91^\circ$$

$$\therefore v_o(t) = [35 + 5.73e^{-t} \cos(7t + 167.91^\circ)]u(t) \text{ V}$$

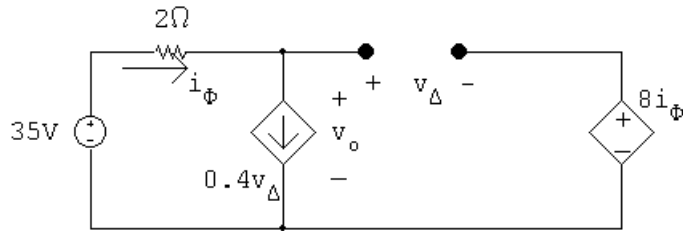**[b]** At  $t = 0^+$   $v_o = 35 + 5.73 \cos(167.91^\circ) = 29.4 \text{ V}$




$$\frac{v_o - 35}{2} + 0.4v_\Delta = 0; \quad v_o - 35 + 0.8v_\Delta = 0$$

$$v_o = v_\Delta + 8i_\phi = v_\Delta + 8(0.4v_\Delta) = 4.2v_\Delta$$


$$v_o + (0.8)\frac{v_o}{4.2} = 35; \quad \therefore v_o(0^+) = 29.4 \text{ V (Checks)}$$

At  $t = \infty$ , the circuit is

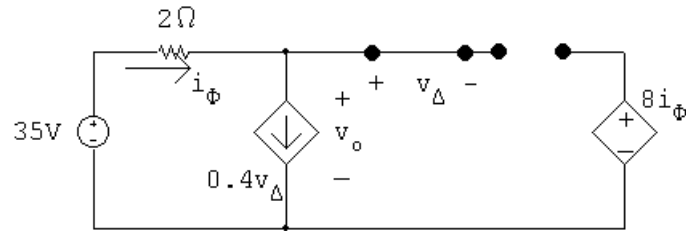

$$v_{\Delta} = 0, \quad i_{\phi} = 0 \quad \therefore v_o = 35 \text{ V (Checks)}$$

P 13.16 [a] For  $t < 0$ :

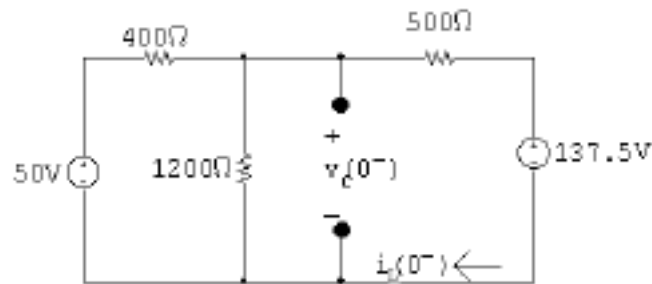


$$\frac{V_c - 50}{400} + \frac{V_c}{1200} + \frac{V_c - 137.5}{500} = 0$$

$$V_c \left( \frac{1}{400} + \frac{1}{1200} + \frac{1}{500} \right) = \frac{50}{400} + \frac{137.5}{500}$$

$$V_c = 75 \text{ V}$$

$$i_L(0^-) = \frac{75 - 137.5}{500} = -0.125 \text{ A}$$

For  $t > 0$ :

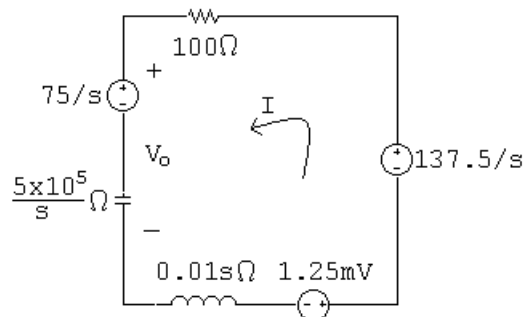

[b]  $V_o = \frac{5 \times 10^5}{s} I + \frac{75}{s}$

$$0 = -\frac{137.5}{s} + 100I + \frac{5 \times 10^5}{s} I + \frac{75}{s} - 1.25 \times 10^{-3} + 0.01sI$$

$$I \left( 100 + \frac{5 \times 10^5}{s} + 0.01s \right) = \frac{62.5}{s} + 1.25 \times 10^{-3}$$

$$\therefore I = \frac{6250 + 0.125s}{s^2 + 10^4s + 5 \times 10^7}$$

$$\begin{aligned} V_o &= \frac{5 \times 10^5}{s} \left( \frac{6250 + 0.125s}{s^2 + 10^4s + 5 \times 10^7} \right) + \frac{75}{s} \\ &= \frac{75s^2 + 812,500s + 6875 \times 10^6}{s(s^2 + 10^4s + 5 \times 10^7)} \end{aligned}$$


$$\text{[c]} \quad V_o = \frac{K_1}{s} + \frac{K_2}{s + 5000 - j5000} + \frac{K_2^*}{s + 5000 + j5000}$$

$$K_1 = \left. \frac{75s^2 + 812,500s + 6875 \times 10^6}{s^2 + 10^4s + 5 \times 10^7} \right|_{s=0} = 137.5$$

$$K_2 = \left. \frac{75s^2 + 812,500s + 6875 \times 10^6}{s(s + 5000 + j5000)} \right|_{s=-5000+j5000} = 40.02 \angle 141.34^\circ$$

$$v_o(t) = [137.5 + 80.04e^{-5000t} \cos(5000t + 141.34^\circ)]u(t) \text{ V}$$

P 13.17

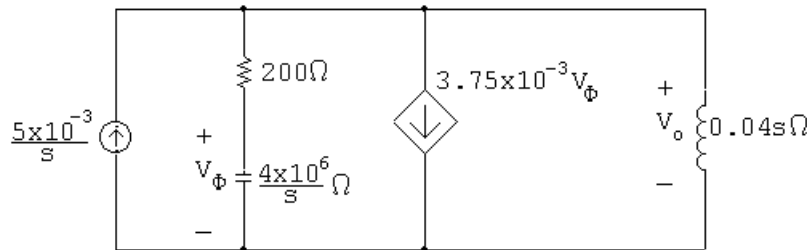

$$\frac{5 \times 10^{-3}}{s} = \frac{V_o}{200 + 4 \times 10^6/s} + 3.75 \times 10^{-3}V_\phi + \frac{V_o}{0.04s}$$

$$V_\phi = \frac{4 \times 10^6/s}{200 + 4 \times 10^6/s} V_o = \frac{4 \times 10^6 V_o}{200s + 4 \times 10^6}$$

$$\therefore \frac{5 \times 10^{-3}}{s} = \frac{V_o s}{200s + 4 \times 10^6} + \frac{15,000 V_o}{200s + 4 \times 10^6} + \frac{25 V_o}{s}$$


$$\therefore V_o = \frac{s + 20,000}{s^2 + 20,000s + 10^8} = \frac{K_1}{(s + 10,000)^2} + \frac{K_2}{s + 10,000}$$

$$K_1 = 10,000; \quad K_2 = 1$$

$$V_o = \frac{10,000}{(s + 10,000)^2} + \frac{1}{s + 10,000}$$

$$v_o(t) = [10,000te^{-10,000t} + e^{-10,000t}]u(t) \text{ V}$$

P 13.18  $v_o(0^-) = v_o(0^+) = 0$

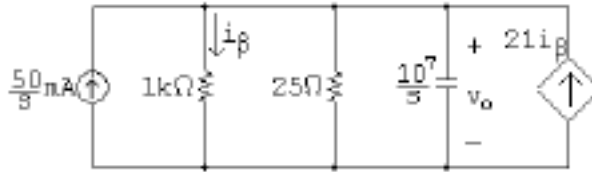


$$-\frac{0.05}{s} + \frac{V_o}{1000} + \frac{V_o}{25} - 21\frac{V_o}{1000} + \frac{V_o}{10^7/s} = 0$$

$$V_o \left( \frac{20}{1000} + \frac{s}{10^7} \right) = \frac{0.05}{s}$$

$$\therefore V_o = \frac{500,000}{s(s + 200,000)} = \frac{2.5}{s} - \frac{2.5}{s + 200,000}$$

$$v_o(t) = [2.5 - 2.5e^{-200,000t}]u(t) \text{ V}$$

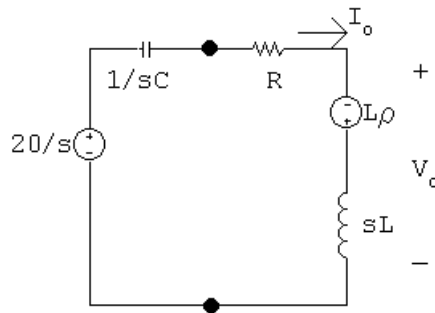P 13.19 [a]  $i_o(0^-) = \frac{20}{4000} = 5 \text{ mA}$



$$I_o = \frac{20/s + L\rho}{R + sL + 1/sC}$$

$$= \frac{20/L + s\rho}{s^2 + sR/L + 1/LC} = \frac{40 + s(0.005)}{s^2 + 8000s + 16 \times 10^6}$$


$$V_o = -L\rho + sLI_o = -0.0025 + \frac{0.0025s(s + 8000)}{s^2 + 8000s + 16 \times 10^6}$$

$$= \frac{-40,000}{(s + 4000)^2}$$

$$v_o(t) = -40,000te^{-4000t}u(t) \text{ V}$$

$$\begin{aligned}
 \text{[b]} \quad I_o &= \frac{0.005(s + 8000)}{s^2 + 8000s + 16 \times 10^6} \\
 &= \frac{K_1}{(s + 4000)^2} + \frac{K_2}{s + 4000} \\
 K_1 &= 20 \quad K_2 = 0.005 \\
 i_o(t) &= [20te^{-4000t} + 0.005e^{-4000t}]u(t) \text{ A}
 \end{aligned}$$

P 13.20

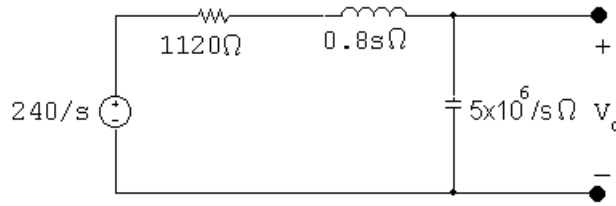


$$\begin{aligned}
 V_o &= \frac{5 \times 10^6/s}{1120 + 0.8s + 5 \times 10^6/s} \left( \frac{240}{s} \right) \\
 &= \frac{12 \times 10^8}{s(0.8s^2 + 1120s + 5 \times 10^6)} \\
 &= \frac{15 \times 10^8}{s(s^2 + 1400s + 625 \times 10^4)} \\
 &= \frac{K_1}{s} + \frac{K_2}{s + 700 - j2400} + \frac{K_2^*}{s + 700 + j2400}
 \end{aligned}$$

$$K_1 = 240; \quad K_2 = 125/\underline{163.74^\circ}$$

$$v_o(t) = [240 + 250e^{-700t} \cos(2400t + 163.74^\circ)]u(t) \text{ V}$$

P 13.21

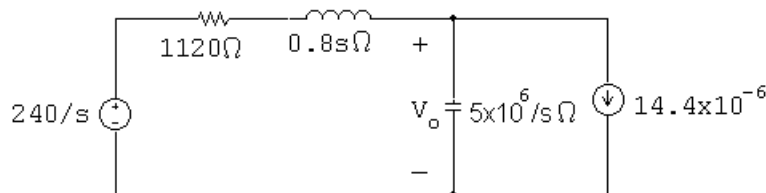

$$\frac{V_o - 240/s}{1120 + 0.8s} + \frac{V_o s}{5 \times 10^6} + 14.4 \times 10^{-6} = 0$$


$$V_o \left( \frac{1}{1120 + 0.8s} + \frac{s}{5 \times 10^6} \right) = \frac{240/s}{0.8s + 1120} - 14.4 \times 10^{-6}$$

$$V_o = \frac{-72s^2 - 100,800s + 15 \times 10^8}{s(s^2 + 1400s + 625 \times 10^4)}$$

$$= \frac{240}{s} + \frac{162.5/163.74^\circ}{s + 700 - j2400} + \frac{162.5/-163.74^\circ}{s + 700 + j2400}$$

$$\therefore v_o(t) = [240 + 325e^{-700t} \cos(2400t + 163.74^\circ)]u(t) \text{ V}$$

P 13.22 [a]

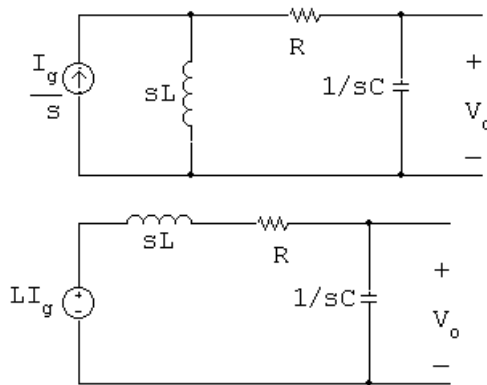

$$V_o = \frac{(1/sC)(LI_g)}{R + sL + (1/sC)} = \frac{I_g/C}{s^2 + (R/L)s + (1/LC)}$$

$$\frac{I_g}{C} = \frac{15}{0.1} = 150$$

$$\frac{R}{L} = 7; \quad \frac{1}{LC} = 10$$

$$V_o = \frac{150}{s^2 + 7s + 10}$$

**[b]**  $sV_o = \frac{150s}{s^2 + 7s + 10}$

$$\lim_{s \rightarrow 0} sV_o = 0; \quad \therefore v_o(\infty) = 0$$

$$\lim_{s \rightarrow \infty} sV_o = 0; \quad \therefore v_o(0^+) = 0$$

**[c]**  $V_o = \frac{150}{(s+2)(s+5)} = \frac{50}{s+2} + \frac{-50}{s+5}$

$$v_o = [50e^{-2t} - 50e^{-5t}]u(t) \text{ V}$$

P 13.23  $I_L = \frac{I_g}{s} - \frac{V_o}{1/sC} = \frac{I_g}{s} - sCV_o$


$$I_L = \frac{15}{s} - \frac{15s}{(s+2)(s+5)} = \frac{15}{s} - \left[ \frac{-10}{s+2} + \frac{25}{s+5} \right]$$

$$i_L(t) = [15 + 10e^{-2t} - 25e^{-5t}]u(t) \text{ A}$$

Check:

$$i_L(0^+) = 0 \quad (\text{ok}); \quad i_L(\infty) = 15 \quad (\text{ok})$$

P 13.24 [a]

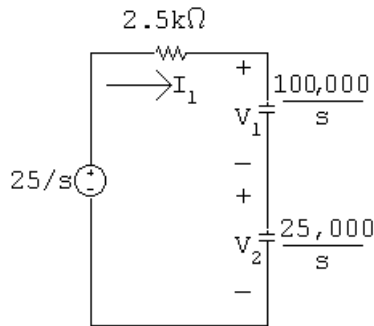

[b]  $I_1 = \frac{25/s}{2500 + (125,000/s)} = \frac{0.01}{s+50}$

$$V_1 = \frac{(100,000/s)(25/s)}{2500 + (125,000/s)} = \frac{1000}{s(s+50)}$$

$$V_2 = \frac{(25,000/s)(25/s)}{2500 + (125,000/s)} = \frac{250}{s(s+50)}$$

[c]  $i_1(t) = 10e^{-50t}u(t) \text{ mA}$

$$V_1 = \frac{20}{s} - \frac{20}{s+50} \quad \therefore \quad v_1(t) = (20 - 20e^{-50t})u(t) \text{ V}$$

$$V_2 = \frac{5}{s} - \frac{5}{s+50} \quad \therefore \quad v_2(t) = (5 - 5e^{-50t})u(t) \text{ V}$$

[d]  $i_1(0^+) = 10 \text{ mA}$

$$i_1(0^+) = \frac{25}{2.5 \times 10^{-3}} = 10 \text{ mA (Checks)}$$

$$v_1(0^+) = 0; \quad v_2(0^+) = 0 \text{ (Checks)}$$

$$v_1(\infty) = 20 \text{ V}; \quad v_2(\infty) = 5 \text{ V (Checks)}$$




$$v_1(\infty) + v_2(\infty) = 25 \text{ V (Checks)}$$

$$(10 \times 10^{-6})v_1(\infty) = 200 \mu\text{C}$$

$$(40 \times 10^{-6})v_2(\infty) = 200 \mu\text{C (Checks)}$$

P 13.25 [a]

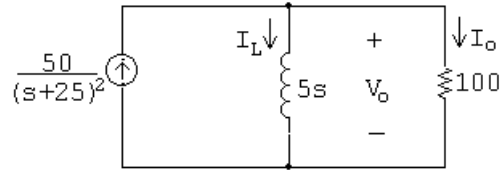

$$100 \parallel 5s = \frac{500s}{5s + 100} = \frac{100s}{s + 20}$$

$$V_o = \frac{100s}{s + 20} \left[ \frac{50}{(s + 25)^2} \right] = \frac{5000s}{(s + 20)(s + 25)^2}$$

$$I_o = \frac{V_o}{100} = \frac{50s}{(s + 20)(s + 25)^2}$$

$$I_L = \frac{V_o}{5s} = \frac{1000}{(s + 20)(s + 25)^2}$$

**[b]**  $V_o = \frac{K_1}{s + 20} + \frac{K_2}{(s + 25)^2} + \frac{K_3}{s + 25}$

$$K_1 = \left. \frac{5000s}{(s + 25)^2} \right|_{s=-20} = -4000$$

$$K_2 = \left. \frac{5000s}{(s + 20)} \right|_{s=-25} = 25,000$$

$$K_3 = \left. \frac{d}{ds} \left[ \frac{5000s}{s + 20} \right] \right|_{s=-25} = \left[ \frac{5000}{s + 20} - \frac{5000s}{(s + 20)^2} \right]_{s=-25} = 4000$$

$$v_o(t) = [-4000e^{-20t} + 25,000te^{-25t} + 4000e^{-25t}]u(t) \text{ V}$$

$$I_o = \frac{K_1}{s + 20} + \frac{K_2}{(s + 25)^2} + \frac{K_3}{s + 25}$$

$$K_1 = \left. \frac{50s}{(s + 25)^2} \right|_{s=-20} = -40$$

$$K_2 = \left. \frac{50s}{(s + 20)} \right|_{s=-25} = 250$$

$$K_3 = \left. \frac{d}{ds} \left[ \frac{50s}{s + 20} \right] \right|_{s=-25} = \left[ \frac{50}{s + 20} - \frac{50s}{(s + 20)^2} \right]_{s=-25} = 40$$

$$i_o(t) = [-40e^{-20t} + 250te^{-25t} + 40e^{-25t}]u(t) \text{ V}$$

$$I_L = \frac{K_1}{s+20} + \frac{K_2}{(s+25)^2} + \frac{K_3}{s+25}$$


$$K_1 = \frac{1000}{(s+25)^2} \Big|_{s=-20} = 40$$

$$K_2 = \frac{1000}{(s+20)} \Big|_{s=-25} = -200$$

$$K_3 = \frac{d}{ds} \left[ \frac{1000}{s+20} \right]_{s=-25} = \left[ -\frac{1000}{(s+20)^2} \right]_{s=-25} = -40$$

$$i_L(t) = [40e^{-20t} - 200te^{-25t} - 40e^{-25t}]u(t) \text{ V}$$

P 13.26

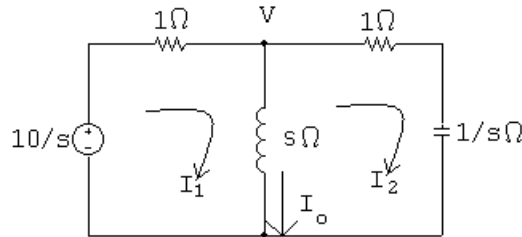

$$\frac{10}{s} = (s+1)I_1 - sI_2$$

$$0 = -sI_1 + \left(s + 1 + \frac{1}{s}\right)I_2$$

In standard form,

$$s(s+1)I_1 - s^2I_2 = 10$$

$$-s^2I_1 + (s^2 + s + 1)I_2 = 0$$

$$\Delta = \begin{vmatrix} s(s+1) & -s^2 \\ -s^2 & (s^2 + s + 1) \end{vmatrix} = 2s(s^2 + s + 0.5)$$

$$N_1 = \begin{vmatrix} 10 & -s^2 \\ 0 & (s^2 + s + 1) \end{vmatrix} = 10(s^2 + s + 1)$$

$$N_2 = \begin{vmatrix} s(s+1) & 10 \\ -s^2 & 0 \end{vmatrix} = 10s^2$$

$$I_1 = \frac{N_1}{\Delta}; \quad I_2 = \frac{N_2}{\Delta}; \quad I_0 = I_1 - I_2$$


$$\begin{aligned} \therefore I_o &= \frac{N_1 - N_2}{\Delta} = \frac{5(s+1)}{s(s^2 + s + 0.5)} \\ &= \frac{K_1}{s} + \frac{K_2}{s + 0.5 - j0.5} + \frac{K_2^*}{s + 0.5 + j0.5} \end{aligned}$$

$$K_1 = \frac{5}{0.5} = 10$$

$$K_2 = \frac{5(-0.5 + j0.5 + 1)}{(-0.5 + j0.5)(j1)} = 5 \angle -180^\circ$$

$$i_o(t) = [10 - 10e^{-t/2} \cos 0.5t]u(t) \text{ A}$$

P 13.27 [a]

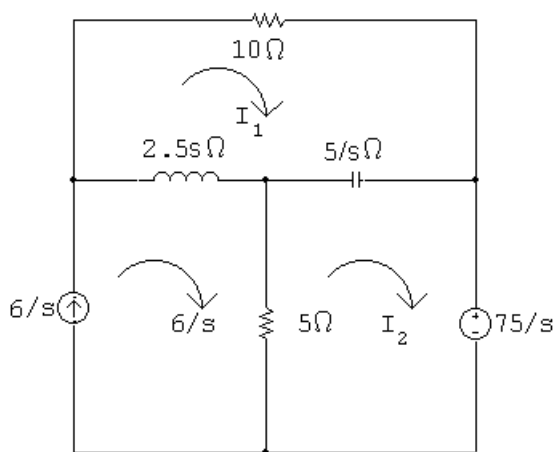

$$0 = 2.5s(I_1 - 6/s) + \frac{5}{s}(I_1 - I_2) + 10I_1$$

$$\frac{-75}{s} = \frac{5}{s}(I_2 - I_1) + 5(I_2 - 6/s)$$

or

$$(s^2 + 4s + 2)I_1 - 2I_2 = 6s$$

$$-I_1 + (s + 1)I_2 = -9$$

$$\Delta = \begin{vmatrix} (s^2 + 4s + 2) & -2 \\ -1 & (s + 1) \end{vmatrix} = s(s + 2)(s + 3)$$

$$N_1 = \begin{vmatrix} 6s & -2 \\ -9 & (s+1) \end{vmatrix} = 6(s^2 + s - 3)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{6(s^2 + s - 3)}{s(s+2)(s+3)}$$

$$N_2 = \begin{vmatrix} (s^2 + 4s + 2) & 6s \\ -1 & -9 \end{vmatrix} = -9s^2 - 30s - 18$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-9s^2 - 30s - 18}{s(s+2)(s+3)}$$

$$\textbf{[b]} \quad sI_1 = \frac{6(s^2 + s - 3)}{(s+2)(s+3)}$$

$$\lim_{s \rightarrow \infty} sI_1 = i_1(0^+) = 6 \text{ A}; \quad \lim_{s \rightarrow 0} sI_1 = i_1(\infty) = -3 \text{ A}$$

$$sI_2 = \frac{-9s^2 - 30s - 18}{(s+2)(s+3)}$$

$$\lim_{s \rightarrow \infty} sI_2 = i_2(0^+) = -9 \text{ A}; \quad \lim_{s \rightarrow 0} sI_2 = i_2(\infty) = -3 \text{ A}$$

$$\textbf{[c]} \quad I_1 = \frac{6(s^2 + s - 3)}{s(s+2)(s+3)} = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+3}$$

$$K_1 = \frac{6(-3)}{6} = -3; \quad K_2 = \frac{6(4 - 2 - 3)}{(-2)(1)} = 3$$

$$K_3 = \frac{6(9 - 3 - 3)}{(-3)(-1)} = 6$$

$$i_1(t) = [-3 + 3e^{-2t} + 6e^{-3t}]u(t) \text{ A}$$


$$I_2 = \frac{-9s^2 - 30s - 18}{s(s+2)(s+3)} = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+3}$$

$$K_1 = \frac{-18}{6} = -3; \quad K_2 = \frac{-36 + 60 - 18}{(-2)(1)} = -3$$

$$K_3 = \frac{-81 + 90 - 18}{(-3)(-1)} = -3$$

$$i_2(t) = [-3 - 3e^{-2t} - 3e^{-3t}]u(t) \text{ A}$$

P 13.28 [a]

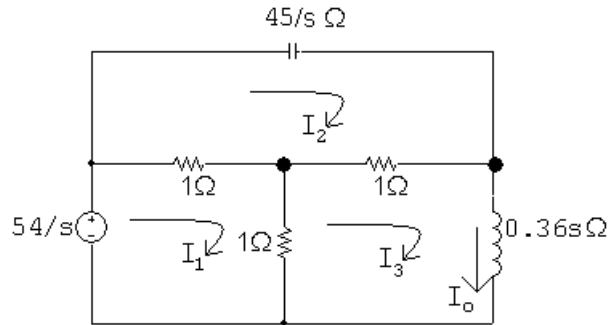

$$\frac{54}{s} = 2I_1 - I_2 - I_3$$

$$0 = -I_1 + \left(2 + \frac{45}{s}\right) I_2 - I_3$$

$$0 = -I_1 - I_2 + (2 + 0.36s)I_3$$

$$\Delta = \begin{vmatrix} 2 & -1 & -1 \\ -1 & (2s + 45)/s & -1 \\ -1 & -1 & (0.36s + 2) \end{vmatrix} = \frac{1.08(s + 5)(s + 25)}{s}$$

$$N_2 = \begin{vmatrix} 2 & (54/s) & -1 \\ -1 & 0 & -1 \\ -1 & 0 & (0.36s + 2) \end{vmatrix} = \frac{162}{s}(0.12s + 1)$$

$$N_3 = \begin{vmatrix} 2 & -1 & (54/s) \\ -1 & (2s + 45)/s & 0 \\ -1 & -1 & 0 \end{vmatrix} = \frac{162}{s^2}(s + 15)$$

$$I_2 = \frac{N_2}{\Delta} = \frac{150(0.12s + 1)}{(s + 5)(s + 25)}$$

$$V_o = \frac{45}{s} I_2 = \frac{6750(0.12s + 1)}{s(s + 5)(s + 25)}$$

$$I_3 = \frac{N_3}{\Delta} = \frac{150(s + 15)}{s(s + 5)(s + 25)} = I_o$$

**[b]**  $V_o = \frac{K_1}{s} + \frac{K_2}{s + 5} + \frac{K_3}{s + 25}$

$$K_1 = \frac{6750}{125} = 54; \quad K_2 = \frac{6750(-0.6 + 1)}{(-5)(20)} = -27$$

$$K_3 = \frac{6750(-3+1)}{(-25)(-20)} = -27$$

$$\therefore v_o(t) = [54 - 27e^{-5t} - 27e^{-25t}]u(t) \text{ V}$$


$$I_o = \frac{K_1}{s} + \frac{K_2}{s+5} + \frac{K_3}{s+25}$$

$$K_1 = \frac{150(15)}{(5)(25)} = 18; \quad K_2 = \frac{150(10)}{(-5)(20)} = -15$$

$$K_3 = \frac{150(-10)}{(-25)(-20)} = -3$$


$$\therefore i_o(t) = [18 - 15e^{-5t} - 3e^{-25t}]u(t) \text{ A}$$

[c] At  $t = 0^+$  the circuit is

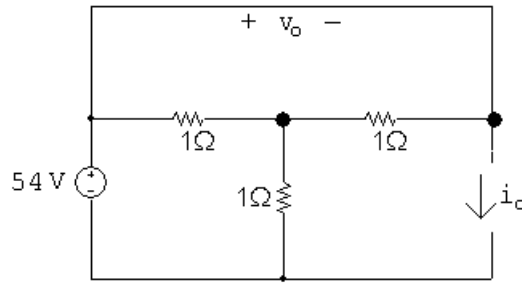

Both  $v_o$  and  $i_o$  are zero, which agrees with our solutions in part (a).

At  $t = \infty$  the circuit is

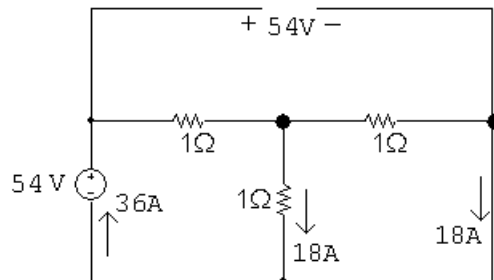

Our solutions predict  $v_o(\infty) = 54 \text{ V}$  and  $i_o(\infty) = 18 \text{ A}$ .


Also observe from the circuit at  $t = 0^+$  that the voltage across the inductor is 54 V. Our solution predicts

$$v_L(0^+) = 0.36 \frac{di_o(0^+)}{dt} = 0.36(75 + 75) = 54 \text{ V}$$

At  $t = 0^+$  the current in the capacitive branch is  $(1/2)(54/1.5) = 18 \text{ A}$ . From our solution we have

$$sI_2 = \frac{150(0.12 + 1/s)}{(1 + 5/s)(1 + 25/s)} \quad \text{and} \quad \lim_{s \rightarrow \infty} sI_2 = i_2(0^+) = 150(0.12) = 18 \text{ A}$$

P 13.29 [a]

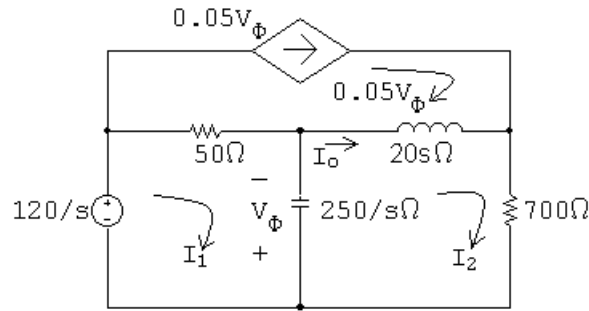

$$\frac{120}{s} = 50(I_1 - 0.05V_\phi) + \frac{250}{s}(I_1 - I_2)$$

$$\frac{120}{s} = 50I_1 - 2.5\left(\frac{250}{s}\right)(I_2 - I_1) + \frac{250}{s}I_1 - \frac{250}{s}I_2;$$

$$0 = \frac{250}{s}(I_2 - I_1) + 20s(I_2 - 0.05V_\phi) + 700I_2$$

$$0 = \frac{250}{s}(I_2 - I_1) + 20s\left[I_2 - 0.05\left(\frac{250}{s}\right)(I_2 - I_1)\right]V_\phi + 700I_2$$

Simplifying,

$$(50s + 875)I_1 - 875I_2 = 120$$

$$250(s - 1)I_1 + (20s^2 + 450s + 250)I_2 = 0$$

$$\Delta = \begin{vmatrix} (50s + 875) & -875 \\ 250(s - 1) & (20s^2 + 450s + 250) \end{vmatrix} = 1000s(s^2 + 40s + 625)$$

$$N_1 = \begin{vmatrix} 120 & -875 \\ 0 & (20s^2 + 450s + 250) \end{vmatrix} = 1200(2s^2 + 45s + 25)$$

$$N_2 = \begin{vmatrix} (50s + 875) & 120 \\ 250(s - 1) & 0 \end{vmatrix} = -30,000(s - 1)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{1.2(2s^2 + 45s + 25)}{s(s^2 + 40s + 625)}$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-30(s - 1)}{s(s^2 + 40s + 625)}$$

$$I_o = I_2 - 0.05V_\phi = I_2 - 0.05\left[\frac{250}{s}(I_2 - I_1)\right]$$

$$I_2 - I_1 = \frac{-2.4s(s + 35)}{s(s^2 + 40s + 625)}$$

$$\frac{250}{s}(I_2 - I_1) = \frac{-600(s + 35)}{s(s^2 + 40s + 625)}$$


$$\therefore I_o = \frac{-30(s - 1)}{s(s^2 + 40s + 625)} + \frac{30(s + 35)}{s(s^2 + 40s + 625)} = \frac{1080}{s(s^2 + 40s + 625)}$$

$$\text{[b]} \quad sI_o = \frac{1080}{(s^2 + 40s + 625)}$$

$$i_o(0^+) = \lim_{s \rightarrow \infty} sI_o = 0$$


$$i_o(\infty) = \lim_{s \rightarrow 0} sI_o = \frac{1080}{625} = 1728 \text{ mA}$$

**[c]** At  $t = 0^+$  the circuit is

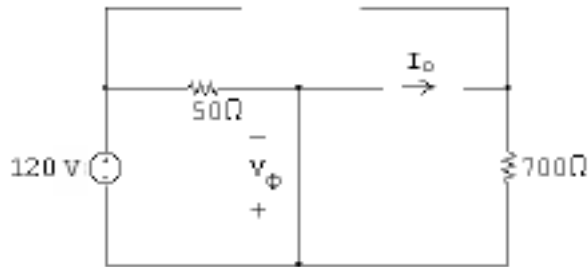

$$i_o(0^+) = 0 \text{ (Checks)}$$

At  $t = \infty$  the circuit is

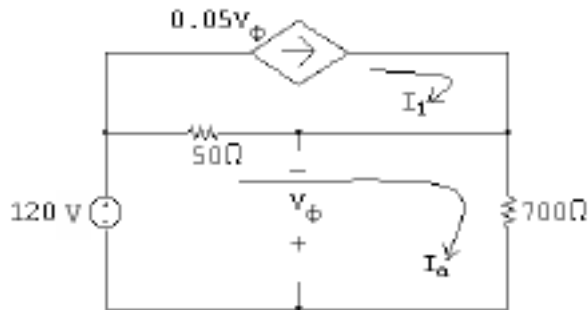

$$120 = 50(i_a - i_1) + 700i_a$$

$$= 50(i_a - 0.05v_\phi) + 700i_a = 750i_a - 2.5v_\phi$$

$$v_\phi = -700i_a \quad \therefore \quad 120 = 750i_a + 1750i_a = 2500i_a$$

$$i_a = \frac{120}{2500} = 48 \text{ mA}$$

$$v_\phi = -700i_a = -33.60 \text{ V}$$

$$i_o(\infty) = 48 \times 10^{-3} - 0.05(-33.60) = 48 \times 10^{-3} + 1.68 = 1728 \text{ mA (Checks)}$$



$$\text{[d]} \quad I_o = \frac{1080}{s(s^2 + 40s + 625)} = \frac{K_1}{s} + \frac{K_2}{s + 20 - j15} + \frac{K_2^*}{s + 20 + j15}$$


$$K_1 = \frac{1080}{625} = 1.728$$

$$K_2 = \frac{1080}{(-20 + j15)(j30)} = 1.44 \angle 126.87^\circ$$

$$i_o(t) = [1728 + 2880e^{-20t} \cos(15t + 126.87^\circ)]u(t) \text{ mA}$$

$$\text{Check:} \quad i_o(0^+) = 0 \text{ mA}; \quad i_o(\infty) = 1728 \text{ mA}$$

P 13.30 [a]

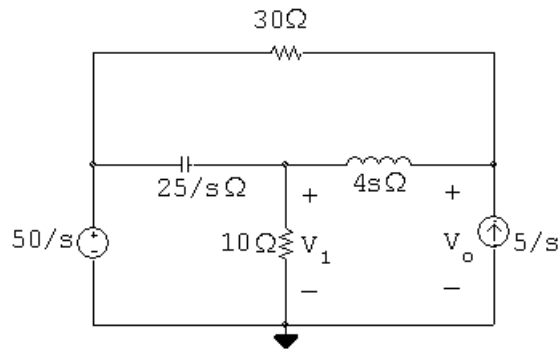

$$\frac{V_1}{10} + \frac{V_1 - 50/s}{25/s} + \frac{V_1 - V_o}{4s} = 0$$

$$\frac{-5}{s} + \frac{V_o - V_1}{4s} + \frac{V_o - 50/s}{30} = 0$$

Simplifying,

$$(4s^2 + 10s + 25)V_1 - 25V_o = 200s$$

$$-15V_1 + (2s + 15)V_o = 400$$

$$\Delta = \begin{vmatrix} (4s^2 + 10s + 25) & -25 \\ -15 & (2s + 15) \end{vmatrix} = 8s(s + 5)^2$$

$$N_o = \begin{vmatrix} (4s^2 + 10s + 25) & 200s \\ -15 & 400 \end{vmatrix} = 200(8s^2 + 35s + 50)$$

$$V_o = \frac{N_o}{\Delta} = \frac{200(8s^2 + 35s + 50)}{8s(s + 5)^2} = \frac{K_1}{s} + \frac{K_2}{(s + 5)^2} + \frac{K_3}{s + 5}$$

$$K_1 = \frac{(25)(50)}{25} = 50; \quad K_2 = \frac{25(200 - 175 + 50)}{-5} = -375$$


$$K_3 = 25 \frac{d}{ds} \left[ \frac{8s^2 + 35s + 50}{s} \right]_{s=-5} = 25 \left[ \frac{s(16s + 35) - (8s^2 + 35s + 50)}{s^2} \right]_{s=-5}$$

$$= -5(-45) - 75 = 150$$

$$\therefore V_o = \frac{50}{s} - \frac{375}{(s+5)^2} + \frac{150}{s+5}$$


**[b]**  $v_o(t) = [50 - 375te^{-5t} + 150e^{-5t}]u(t) \text{ V}$

**[c]** At  $t = 0^+$ :

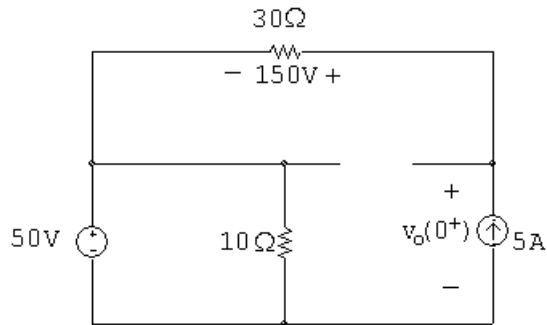

$$v_o(0^+) = 50 + 150 = 200 \text{ V (Checks)}$$

At  $t = \infty$ :

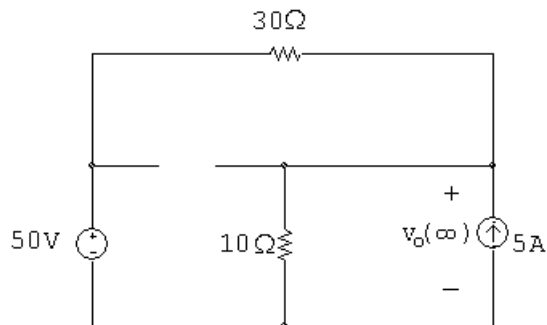


$$\frac{v_o(\infty)}{10} - 5 + \frac{v_o(\infty) - 50}{30} = 0$$

$$\therefore 3v_o(\infty) - 150 + v_o(\infty) - 50 = 0; \quad \therefore 4v_o(\infty) = 200$$

$$\therefore v_o(\infty) = 50 \text{ V (Checks)}$$

## P 13.31 [a]

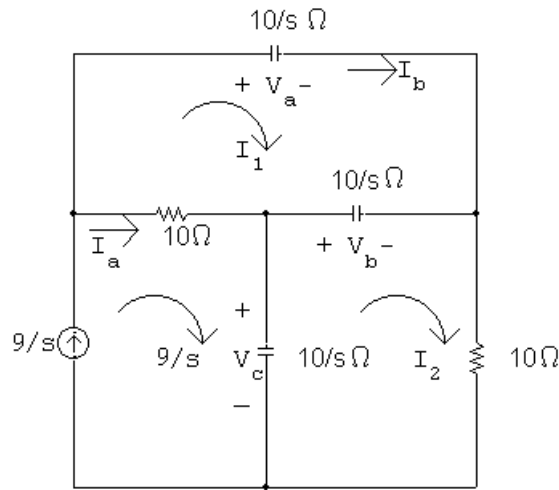

$$\frac{10}{s}I_1 + \frac{10}{s}(I_1 - I_2) + 10(I_1 - 9/s) = 0$$

$$\frac{10}{s}(I_2 - 9/s) + \frac{10}{s}(I_2 - I_1) + 10I_2 = 0$$

Simplifying,

$$(s + 2)I_1 - I_2 = 9$$

$$-I_1 + (s + 2)I_2 = \frac{9}{s}$$

$$\Delta = \begin{vmatrix} (s + 2) & -1 \\ -1 & (s + 2) \end{vmatrix} = s^2 + 4s + 3 = (s + 1)(s + 3)$$

$$N_1 = \begin{vmatrix} 9 & -1 \\ 9/s & (s + 2) \end{vmatrix} = \frac{9s^2 + 18s + 9}{s} = \frac{9}{s}(s + 1)^2$$

$$I_1 = \frac{N_1}{\Delta} = \frac{9}{s} \left[ \frac{(s + 1)^2}{(s + 1)(s + 3)} \right] = \frac{9(s + 1)}{s(s + 3)}$$

$$N_2 = \begin{vmatrix} (s + 2) & 9 \\ -1 & 9/s \end{vmatrix} = \frac{18}{s}(s + 1)$$

$$I_2 = \frac{N_2}{\Delta} = \frac{18(s + 1)}{s(s + 1)(s + 3)} = \frac{18}{s(s + 3)}$$

$$I_a = \frac{9}{s} - I_1 = \frac{9}{s} - \frac{9(s + 1)}{s(s + 3)} = \frac{6}{s} - \frac{6}{s + 3}$$

$$I_b = I_1 = \frac{9(s + 1)}{s(s + 3)} = \frac{3}{s} + \frac{6}{s + 3}$$

$$\textbf{[b]} \quad i_a(t) = 6(1 - e^{-3t})u(t) \text{ A}$$

$$i_b(t) = 3(1 + 2e^{-3t})u(t) \text{ A}$$

$$\textbf{[c]} \quad V_a = \frac{10}{s}I_b = \frac{10}{s} \left( \frac{3}{s} + \frac{6}{s+3} \right)$$

$$= \frac{30}{s^2} + \frac{60}{s(s+3)} = \frac{30}{s^2} + \frac{20}{s} - \frac{20}{s+3}$$

$$V_b = \frac{10}{s}(I_2 - I_1) = \frac{10}{s} \left[ \left( \frac{6}{s} - \frac{6}{s+3} \right) - \left( \frac{3}{s} + \frac{6}{s+3} \right) \right]$$

$$= \frac{10}{s} \left[ \frac{3}{s} - \frac{12}{s+3} \right] = \frac{30}{s^2} - \frac{40}{s} + \frac{40}{s+3}$$

$$V_c = \frac{10}{s}(9/s - I_2) = \frac{10}{s} \left( \frac{9}{s} - \frac{6}{s} + \frac{6}{s+3} \right)$$

$$= \frac{30}{s^2} + \frac{20}{s} - \frac{20}{s+3}$$

$$\textbf{[d]} \quad v_a(t) = [30t + 20 - 20e^{-3t}]u(t) \text{ V}$$

$$v_b(t) = [30t - 40 + 40e^{-3t}]u(t) \text{ V}$$

$$v_c(t) = [30t + 20 - 20e^{-3t}]u(t) \text{ V}$$

**[e]** Calculating the time when the capacitor voltage drop first reaches 1000 V:

$$30t + 20 - 20e^{-3t} = 1000 \quad \text{or} \quad 30t - 40 + 40e^{-3t} = 1000$$

Note that in either of these expressions the exponential term over time becomes negligible when compared to the other terms. Thus,


$$30t + 20 = 1000 \quad \text{or} \quad 30t - 40 = 1000$$

Thus,

$$t = \frac{980}{30} = 32.67 \text{ s} \quad \text{or} \quad t = \frac{1040}{30} = 34.67 \text{ s}$$

Therefore, the breakdown will occur at  $t = 32.67 \text{ s}$ .

P 13.32 [a]

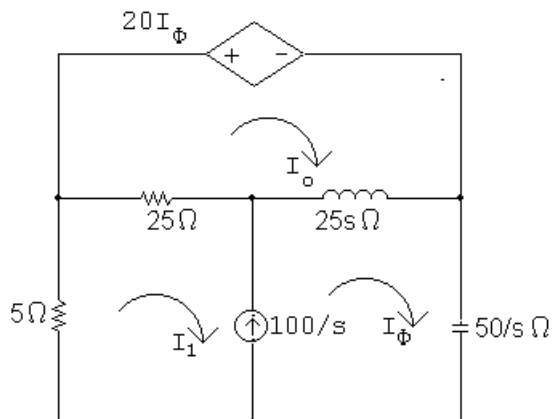

$$20I_\phi + 25s(I_o - I_\phi) + 25(I_o - I_1) = 0$$

$$\frac{50}{s}I_\phi + 5I_1 + 25(I_1 - I_o) + 25s(I_\phi - I_o) = 0$$

$$I_\phi - I_1 = \frac{100}{s} \quad \therefore \quad I_1 = I_\phi - \frac{100}{s}$$

Simplifying,

$$(-25s - 5)I_\phi + (25s + 25)I_o = -2500/s$$

$$(50/s + 25s + 30)I_\phi + (-25s - 25)I_o = 3000/s$$

$$\Delta = \begin{vmatrix} -5(5s + 1) & 25(s + 1) \\ \frac{5}{s}(5s^2 + 6s + 10) & -25(s + 1) \end{vmatrix} = -625(s + 1)(1 + 2/s)$$


$$N_2 = \begin{vmatrix} -5(5s + 1) & -2500/s \\ \frac{5}{s}(5s^2 + 6s + 10) & 3000/s \end{vmatrix} = -12,500 \frac{s^2 - 4.8s - 10}{s^2}$$

$$I_o = \frac{N_2}{\Delta} = \frac{20(s^2 - 4.8s - 10)}{s(s + 1)(s + 2)}$$

$$\textbf{[b]} \quad i_o(0^+) = \lim_{s \rightarrow \infty} sI_o = 20 \text{ A}$$

$$i_o(\infty) = \lim_{s \rightarrow 0} sI_o = \frac{-200}{2} = -100 \text{ A}$$

[c] At  $t = 0^+$  the circuit is

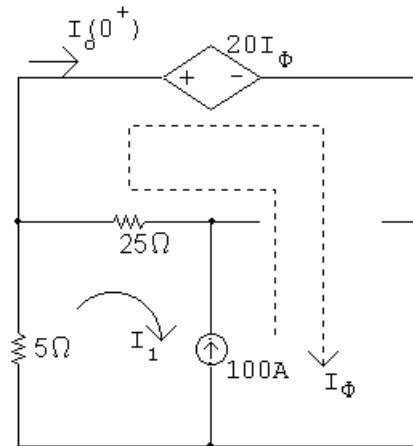


$$20I_\phi + 5I_1 = 0; \quad I_\phi - I_1 = 100$$

$$\therefore 20I_\phi + 5(I_\phi - 100) = 0; \quad 25I_\phi = 500$$

$$\therefore I_\phi = I_o(0^+) = 20 \text{ A (Checks)}$$

At  $t = \infty$  the circuit is

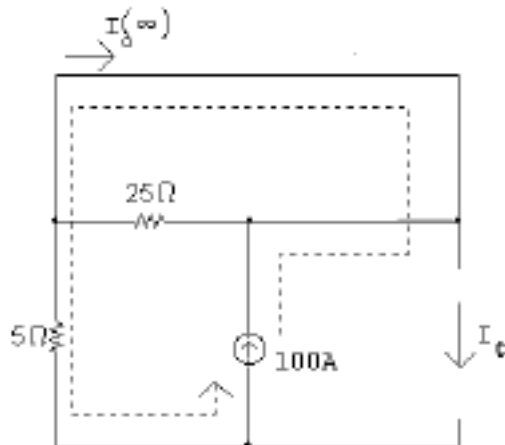

$$I_o(\infty) = -100 \text{ A (Checks)}$$

$$\text{[d]} \quad I_o = \frac{20(s^2 - 4.8s - 10)}{s(s+1)(s+2)} = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+2}$$

$$K_1 = \frac{-200}{(1)(2)} = -100; \quad K_2 = \frac{20(1 + 4.8 - 10)}{(-1)(1)} = 84$$

$$K_3 = \frac{20(4 + 9.6 - 10)}{(-2)(-1)} = 36$$

$$I_o = \frac{-100}{s} + \frac{84}{s+1} + \frac{36}{s+2}$$

$$i_o(t) = (-100 + 84e^{-t} + 36e^{-2t})u(t) \text{ A}$$

$$i_o(\infty) = -100 \text{ A (Checks)}$$

$$i_o(0^+) = -100 + 84 + 36 = 20 \text{ A (Checks)}$$

P 13.33  $v_C = 12 \times 10^5 t e^{-5000t} \text{ V}, \quad C = 5 \mu\text{F}; \quad \text{therefore}$

$$i_C = C \left( \frac{dv_C}{dt} \right) = 6e^{-5000t} (1 - 5000t) \text{ A}$$

$$i_C > 0 \quad \text{when} \quad 1 > 5000t \quad \text{or} \quad i_C < 0 \quad \text{when} \quad 0 < t < 200 \mu\text{s}$$


$$\text{and} \quad i_C < 0 \quad \text{when} \quad t > 200 \mu\text{s}$$

$$i_C = 0 \quad \text{when} \quad 1 - 5000t = 0, \quad \text{or} \quad t = 200 \mu\text{s}$$

$$\frac{dv_C}{dt} = 12 \times 10^5 e^{-5000t} [1 - 5000t]$$

$$\therefore i_C = 0 \quad \text{when} \quad \frac{dv_C}{dt} = 0$$

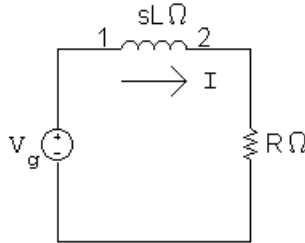P 13.34 [a] The  $s$ -domain equivalent circuit is



$$I = \frac{V_g}{R + sL} = \frac{V_g/L}{s + (R/L)}, \quad V_g = \frac{V_m(\omega \cos \phi + s \sin \phi)}{s^2 + \omega^2}$$

$$I = \frac{K_0}{s + R/L} + \frac{K_1}{s - j\omega} + \frac{K_1^*}{s + j\omega}$$

$$K_0 = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2}, \quad K_1 = \frac{V_m/\phi - 90^\circ - \theta(\omega)}{2\sqrt{R^2 + \omega^2 L^2}}$$

where  $\tan \theta(\omega) = \omega L/R$ . Therefore, we have

$$i(t) = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2} e^{-(R/L)t} + \frac{V_m \sin[\omega t + \phi - \theta(\omega)]}{\sqrt{R^2 + \omega^2 L^2}}$$

[b]  $i_{ss}(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin[\omega t + \phi - \theta(\omega)]$

$$[\mathbf{c}] \quad i_{\text{tr}} = \frac{V_m(\omega L \cos \phi - R \sin \phi)}{R^2 + \omega^2 L^2} e^{-(R/L)t}$$

$$[\mathbf{d}] \quad \mathbf{I} = \frac{\mathbf{V}_g}{R + j\omega L}, \quad \mathbf{V}_g = V_m / \phi - 90^\circ$$


$$\text{Therefore } \mathbf{I} = \frac{V_m / \phi - 90^\circ}{\sqrt{R^2 + \omega^2 L^2} / \theta(\omega)} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} / \phi - 90^\circ - \theta(\omega)$$

$$\text{Therefore } i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin[\omega t + \phi - \theta(\omega)]$$

**[e]** The transient component vanishes when


$$\omega L \cos \phi = R \sin \phi \quad \text{or} \quad \tan \phi = \frac{\omega L}{R} \quad \text{or} \quad \phi = \theta(\omega)$$

P 13.35

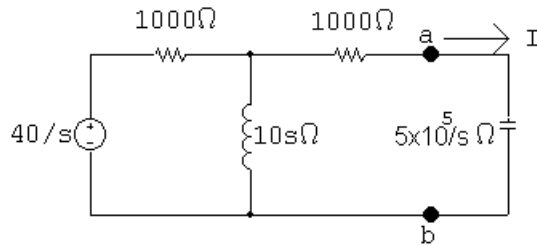

$$V_{\text{Th}} = \frac{10s}{10s + 1000} \cdot \frac{40}{s} = \frac{400}{10s + 1000} = \frac{40}{s + 100}$$
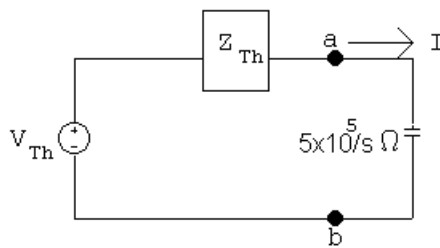
$$Z_{\text{Th}} = 1000 + 1000 \parallel 10s = 1000 + \frac{10,000s}{10s + 1000} = \frac{2000(s + 50)}{s + 100}$$




$$\begin{aligned} I &= \frac{40/(s + 100)}{(5 \times 10^5)/s + 2000(s + 50)/(s + 100)} = \frac{40s}{2000s^2 + 600,000s + 5 \times 10^7} \\ &= \frac{0.02s}{s^2 + 300s + 25,000} = \frac{K_1}{s + 150 - j50} + \frac{K_1^*}{s + 150 + j50} \end{aligned}$$

$$K_1 = \left. \frac{0.02s}{s + 150 + j50} \right|_{s=-150+j50} = 31.62 \times 10^{-3} \angle 71.57^\circ$$

$$i(t) = 63.25e^{-150t} \cos(50t + 71.57^\circ) u(t) \text{ mA}$$



P 13.36 [a]

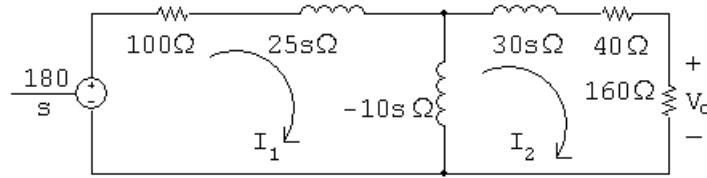

$$\frac{180}{s} = (100 + 15s)I_1 + 10sI_2$$

$$0 = 10sI_1 + (20s + 200)I_2$$

$$\Delta = \begin{vmatrix} 15s + 100 & 10s \\ 10s & 20s + 200 \end{vmatrix} = 200(s + 5)(s + 20)$$

$$N_2 = \begin{vmatrix} 15s + 100 & 180/s \\ 10s & 0 \end{vmatrix} = -1800$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-9}{(s + 5)(s + 20)}$$

$$V_o = 160I_2 = \frac{-1440}{(s + 5)(s + 20)}$$

$$\text{[b]} \quad sV_o = \frac{-1440s}{(s + 5)(s + 20)}$$


$$\lim_{s \rightarrow 0} sV_o = v_o(\infty) = 0 \text{ V}$$

$$\lim_{s \rightarrow \infty} sV_o = v_o(0^+) = 0 \text{ V}$$

$$\text{[c]} \quad V_o = \frac{-96}{s + 5} + \frac{96}{s + 20}$$

$$v_o(t) = [-96e^{-5t} + 96e^{-20t}]u(t) \text{ V}$$

P 13.37

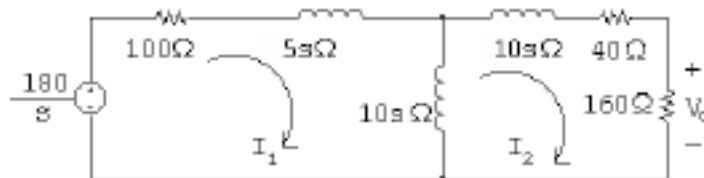

$$\frac{180}{s} = (100 + 15s)I_1 - 10sI_2$$

$$0 = -10sI_1 + (20s + 200)I_2$$

$$\Delta = \begin{vmatrix} 15s + 100 & -10s \\ -10s & 20s + 200 \end{vmatrix} = 200(s + 5)(s + 20)$$

$$N_2 = \begin{vmatrix} 15s + 100 & 180/s \\ -10s & 0 \end{vmatrix} = 1800$$

$$I_2 = \frac{N_2}{\Delta} = \frac{9}{(s + 5)(s + 20)}$$

$$V_o = 160I_2 = \frac{1440}{(s + 5)(s + 20)} = \frac{96}{s + 5} - \frac{96}{s + 20}$$

$$v_o(t) = [96e^{-5t} - 96e^{-20t}]u(t) \text{ V}$$

P 13.38 [a]  $W = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2$

$$W = 4(15)^2 + 9(100) + 150(6) = 2700 \text{ J}$$

[b]  $120i_1 + 8\frac{di_1}{dt} - 6\frac{di_2}{dt} = 0$

$$270i_2 + 18\frac{di_2}{dt} - 6\frac{di_1}{dt} = 0$$

Laplace transform the equations to get

$$120I_1 + 8(sI_1 - 15) - 6(sI_2 + 10) = 0$$

$$270I_2 + 18(sI_2 + 10) - 6(sI_1 - 15) = 0$$

In standard form,

$$(8s + 120)I_1 - 6sI_2 = 180$$

$$-6sI_1 + (18s + 270)I_2 = -270$$

$$\Delta = \begin{vmatrix} 8s + 120 & -6s \\ -6s & 18s + 270 \end{vmatrix} = 108(s + 10)(s + 30)$$

$$N_1 = \begin{vmatrix} 180 & -6s \\ -270 & 18s + 270 \end{vmatrix} = 1620(s + 30)$$

$$N_2 = \begin{vmatrix} 8s + 120 & 180 \\ -6s & -270 \end{vmatrix} = -1080(s + 30)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{1620(s+30)}{108(s+10)(s+30)} = \frac{15}{s+10}$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-1080(s+30)}{108(s+10)(s+30)} = \frac{-10}{s+10}$$

**[c]**  $i_1(t) = 15e^{-10t}u(t) \text{ A}; \quad i_2(t) = -10e^{-10t}u(t) \text{ A}$

**[d]**  $W_{120\Omega} = \int_0^\infty (225e^{-20t})(120) dt = 27,000 \left. \frac{e^{-20t}}{-20} \right|_0^\infty = 1350 \text{ J}$

$$W_{270\Omega} = \int_0^\infty (100e^{-20t})(270) dt = 27,000 \left. \frac{e^{-20t}}{-20} \right|_0^\infty = 1350 \text{ J}$$

$$W_{120\Omega} + W_{270\Omega} = 2700 \text{ J} \quad (\text{Checks})$$

**[e]**  $W = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2 = 900 + 900 - 900 = 900 \text{ J}$

With the dot reversed the  $s$ -domain equations are

$$(8s + 120)I_1 + 6sI_2 = 60$$

$$6sI_1 + (18s + 270)I_2 = -90$$

As before,  $\Delta = 108(s+10)(s+30)$ . Now,

$$N_1 = \begin{vmatrix} 60 & 6s \\ -90 & 18s + 270 \end{vmatrix} = 1620(s+10)$$

$$N_2 = \begin{vmatrix} 8s + 120 & 60 \\ 6s & -90 \end{vmatrix} = -1080(s+10)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{15}{s+30}; \quad I_2 = \frac{N_2}{\Delta} = \frac{-10}{s+30}$$


$$i_1(t) = 15e^{-30t}u(t) \text{ A}; \quad i_2(t) = -10e^{-30t}u(t) \text{ A}$$

$$W_{270\Omega} = \int_0^\infty (100e^{-60t})(270) dt = 450 \text{ J}$$

$$W_{120\Omega} = \int_0^\infty (225e^{-60t})(120) dt = 450 \text{ J}$$

$$W_{120\Omega} + W_{270\Omega} = 900 \text{ J} \quad (\text{Checks})$$

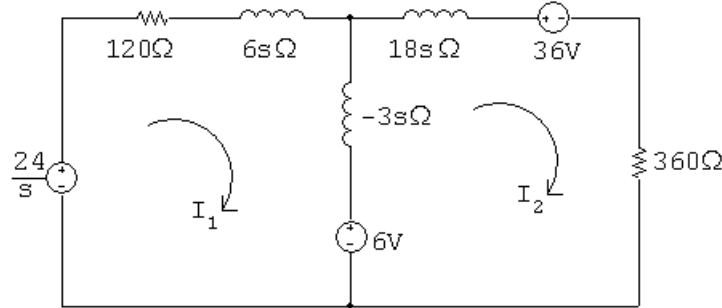P 13.39 [a]  $s$ -domain equivalent circuit is



Note:  $i_2(0^+) = -\frac{20}{10} = -2 \text{ A}$

[b]  $\frac{24}{s} = (120 + 3s)I_1 + 3sI_2 + 6$

$$0 = -6 + 3sI_1 + (360 + 15s)I_2 + 36$$

In standard form,

$$(s + 40)I_1 + sI_2 = (8/s) - 2$$

$$sI_1 + (5s + 120)I_2 = -10$$

$$\Delta = \begin{vmatrix} s + 40 & s \\ s & 5s + 120 \end{vmatrix} = 4(s + 20)(s + 60)$$

$$N_1 = \begin{vmatrix} (8/s) - 2 & s \\ -10 & 5s + 120 \end{vmatrix} = \frac{-200(s - 4.8)}{s}$$

$$I_1 = \frac{N_1}{\Delta} = \frac{-50(s - 4.8)}{s(s + 20)(s + 60)}$$

[c]  $sI_1 = \frac{-50(s - 4.8)}{(s + 20)(s + 60)}$

$$\lim_{s \rightarrow \infty} sI_1 = i_1(0^+) = 0 \text{ A}$$

$$\lim_{s \rightarrow 0} sI_1 = i_1(\infty) = \frac{(-50)(-4.8)}{(20)(60)} = 0.2 \text{ A}$$


[d]  $I_1 = \frac{K_1}{s} + \frac{K_2}{s + 20} + \frac{K_3}{s + 60}$

$$K_1 = \frac{240}{1200} = 0.2; \quad K_2 = \frac{-50(-20) + 240}{(-20)(40)} = -1.55$$


$$K_3 = \frac{-50(-60) + 240}{(-60)(-40)} = 1.35$$

$$i_1(t) = [0.2 - 1.55e^{-20t} + 1.35e^{-60t}]u(t) \text{ A}$$


P 13.40 For  $t < 0$ :

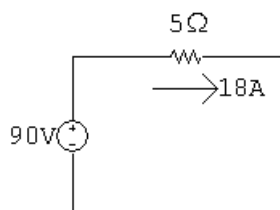

For  $t > 0^+$ :

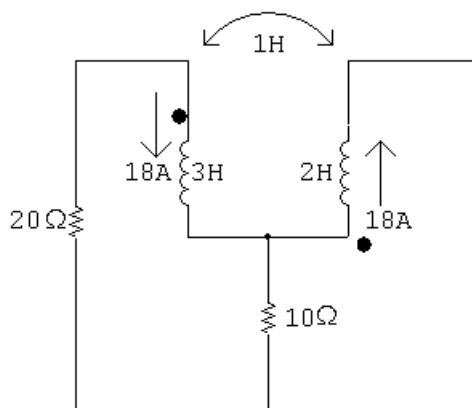
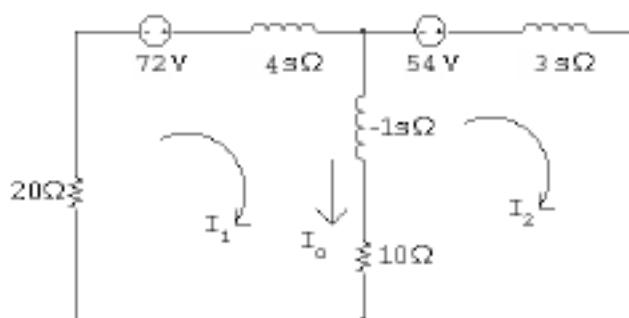
$$18 \times 4 = 72; \quad 18 \times 3 = 54$$



$$20I_1 - 72 + 4sI_1 + s(I_2 - I_1) + 10(I_1 - I_2) = 0$$

$$-54 + 3sI_2 + 10(I_2 - I_1) + s(I_1 - I_2) = 0$$

In standard form,

$$(3s + 30)I_1 + (s - 10)I_2 = 72$$

$$(s - 10)I_1 + (2s + 10)I_2 = 54$$

$$\therefore \Delta = \begin{vmatrix} (3s + 30) & (s - 10) \\ (s - 10) & (2s + 10) \end{vmatrix} = 5(s + 2)(s + 20)$$

$$N_1 = \begin{vmatrix} 72 & (s - 10) \\ 54 & (2s + 10) \end{vmatrix} = 90s + 1260$$


$$N_2 = \begin{vmatrix} (3s + 30) & 72 \\ (s - 10) & 54 \end{vmatrix} = 90s + 2340$$

$$I_o = I_1 - I_2 = \frac{N_1}{\Delta} - \frac{N_2}{\Delta} = \frac{-1080}{5(s + 2)(s + 20)}$$

$$= \frac{-216}{(s + 2)(s + 20)} - \frac{12}{s + 2} - \frac{12}{s + 20}$$

$$i_o(t) = [12e^{-2t} + 12e^{-20t}]u(t) \text{ A}$$

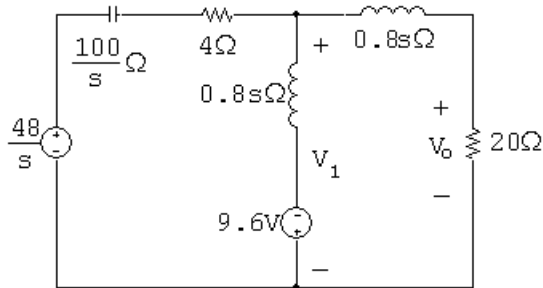P 13.41 The  $s$ -domain equivalent circuit is



$$\frac{V_1 - 48/s}{4 + (100/s)} + \frac{V_1 + 9.6}{0.8s} + \frac{V_1}{0.8s + 20} = 0$$

$$V_1 = \frac{-1200}{s^2 + 10s + 125}$$

$$V_o = \frac{20}{0.8s + 20} V_1 = \frac{-30,000}{(s + 25)(s + 5 - j10)(s + 5 + j10)}$$


$$= \frac{K_1}{s + 25} + \frac{K_2}{s + 5 - j10} + \frac{K_2^*}{s + 5 + j10}$$

$$K_1 = \frac{-30,000}{s^2 + 10s + 125} \Big|_{s=-25} = -60$$

$$K_2 = \frac{-30,000}{(s+25)(s+5+j10)} \Big|_{s=-5+j10} = 67.08 \angle 63.43^\circ$$

$$v_o(t) = [-60e^{-25t} + 134.16e^{-5t} \cos(10t + 63.43^\circ)]u(t) \text{ V}$$



P 13.42 [a] Voltage source acting alone:

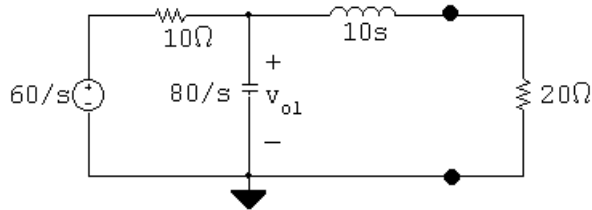

$$\frac{V_{o1} - 60/s}{10} + \frac{V_{o1}s}{80} + \frac{V_{o1}}{20 + 10s} = 0$$

$$\therefore V_{o1} = \frac{480(s+2)}{s(s+4)(s+6)}$$

Current source acting alone:

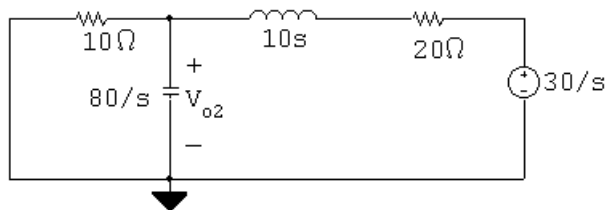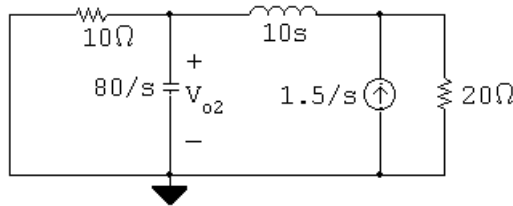

$$\frac{V_{o2}}{10} + \frac{V_{o2}s}{80} + \frac{V_{o2} - 30/s}{10(s+2)} = 0$$

$$\therefore V_{o2} = \frac{240}{s(s+4)(s+6)}$$

$$V_o = V_{o1} + V_{o2} = \frac{480(s+2) + 240}{s(s+4)(s+6)} = \frac{480(s+2.5)}{s(s+4)(s+6)}$$

$$\text{[b]} \quad V_o = \frac{K_1}{s} + \frac{K_2}{s+4} + \frac{K_3}{s+6}$$

$$K_1 = \frac{(480)(2.5)}{(4)(6)} = 50; \quad K_2 = \frac{480(-1.5)}{(-4)(2)} = 90; \quad K_3 = \frac{480(-3.5)}{(-6)(-2)} = -140$$

$$v_o(t) = [50 + 90e^{-4t} - 140e^{-6t}]u(t) \text{ V}$$


$$\text{P 13.43} \quad \Delta = \begin{vmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{vmatrix} = Y_{11}Y_{22} - Y_{12}^2$$

$$N_2 = \begin{vmatrix} Y_{11} [(V_g/R_1) + \gamma C - (\rho/s)] \\ Y_{12} & (I_g - \gamma C) \end{vmatrix}$$

$$V_2 = \frac{N_2}{\Delta}$$

Substitution and simplification lead directly to Eq. 13.90.

P 13.44

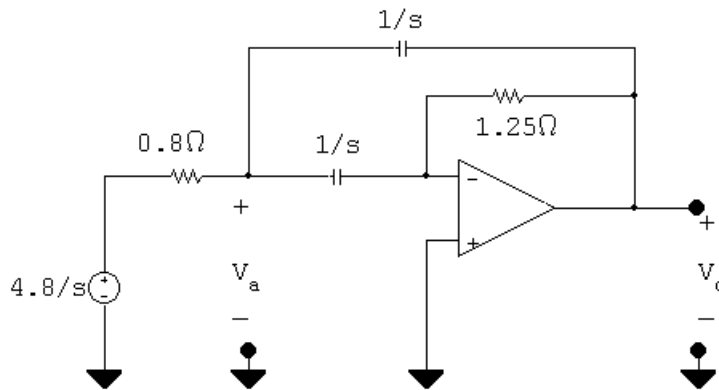

$$\frac{V_a - 4.8/s}{0.8} + \frac{V_a}{1/s} + \frac{V_a - V_o}{1/s} = 0$$

$$\frac{0 - V_a}{1/s} + \frac{0 - V_o}{1.25} = 0$$

$$V_a = \frac{-V_o}{1.25s}$$

$$V_a(2s + 1.25) - sV_o = 6/s$$



$$-V_o \left[ \frac{(2s + 1.25)}{1.25s} + s \right] = 6/s$$

$$-V_o \left[ \frac{125s^2 + 2s + 1.25}{1.25s} \right] = 6/s$$

$$V_o = \frac{-7.5}{1.25s^2 + 2s + 1.25} = \frac{-6}{s^2 + 1.6s + 1}$$

$$= \frac{K_1}{s + 0.8 - j0.6} + \frac{K_1^*}{s + 0.8 + j0.6}$$

$$K_1 = \frac{-6}{s + 0.8 + j0.6} \Big|_{s=-0.8+j0.6} = 5 \angle 90^\circ$$

$$v_o(t) = 10e^{-0.8t} \cos(0.6t + 90^\circ)u(t) \text{ V} = -10e^{-0.8t} \sin(0.6t)u(t) \text{ V}$$

**P 13.45 [a]**  $V_o = -\frac{Z_f}{Z_i} V_g$

$$Z_f = \frac{10^7}{s} \parallel 1000 = \frac{10^{10}/s}{10^7/s + 1000} = \frac{10^{10}}{1000s + 10^7} = \frac{10^7}{s + 10^4}$$

$$Z_i = \frac{2 \times 10^6}{s} + 400 = \frac{400s + 2 \times 10^6}{s} = \frac{400}{s}(s + 5000)$$

$$V_g = \frac{20,000}{s^2}$$

$$\therefore V_o = \frac{-10^7/(s + 10^4)}{(400/s)(s + 5000)} \cdot \frac{20,000}{s^2} = \frac{-5 \times 10^8}{s(s + 5000)(s + 10,000)}$$

**[b]**  $V_o = \frac{K_1}{s} + \frac{K_2}{s + 5000} + \frac{K_3}{s + 10,000}$

$$K_1 = \frac{-5 \times 10^8}{(s + 5000)(s + 10,000)} \Big|_{s=0} = -10$$

$$K_2 = \frac{-5 \times 10^8}{s(s + 10,000)} \Big|_{s=-5000} = 20$$

$$K_3 = \frac{-5 \times 10^8}{s(s + 5000)} \Big|_{s=-10,000} = -10$$

$$\therefore v_o(t) = [-10 + 20e^{-5000t} - 10e^{-10,000t}]u(t) \text{ V}$$

**[c]**  $-10 + 20e^{-5000t_s} - 10e^{-10,000t_s} = -5$

Let  $x = e^{-5000t_s}$ . Then

$$10x^2 - 20x + 5 = 0$$

Solving,

$$x = 0.292893$$

$$e^{-5000t_s} = 0.292893 \quad \therefore \quad t_s = 245.6 \mu\text{s}$$

**[d]**  $v_g = m tu(t); \quad V_g = \frac{m}{s^2}$


$$V_o = \frac{-10^7 s}{400(s + 5000)(s + 10,000)} \cdot \frac{m}{s^2}$$

$$= \frac{-25,000m}{s(s + 5000)(s + 10,000)}$$

$$K_1 = \frac{-25,000m}{(5000)(10,000)} = -5 \times 10^{-4}m$$

$$\therefore -5 = -5 \times 10^{-4}m \quad \therefore m = 10,000 \text{ V/s}$$

P 13.46 **[a]**

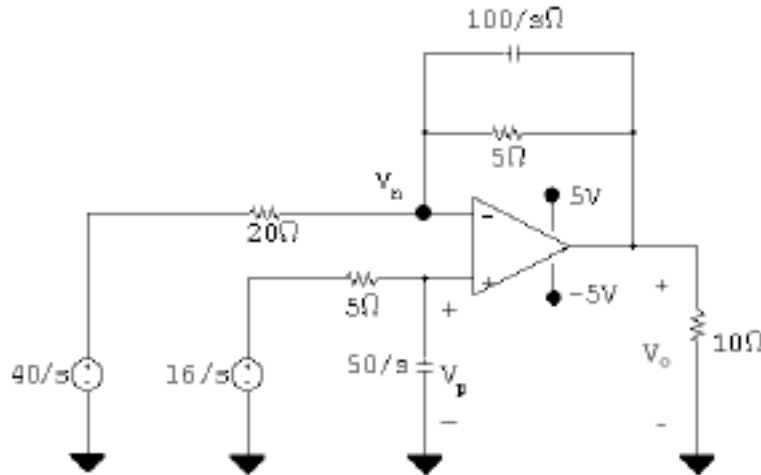

$$V_p = \frac{50/s}{5 + 50/s} V_{g2} = \frac{50}{5s + 50} V_{g2}$$

$$\frac{V_p - 40/s}{20} + \frac{V_p - V_o}{5} + \frac{V_p - V_o}{100/s} = 0$$

$$V_p \left( \frac{1}{20} + \frac{1}{5} + \frac{s}{100} \right) - V_o \left( \frac{1}{5} + \frac{s}{100} \right) = \frac{2}{s}$$

$$\frac{s + 25}{100} \left( \frac{50}{5s + 50} \right) \frac{16}{s} - \frac{2}{s} = V_o \left( \frac{1}{5} + \frac{s}{100} \right) = V_o \left( \frac{s + 20}{100} \right)$$

$$V_o = \frac{100}{s+20} \left[ \frac{16(s+25)}{10(s+10)(s)} - \frac{2}{s} \right] = \frac{-40s+2000}{s(s+10)(s+20)}$$

$$= \frac{K_1}{s} + \frac{K_2}{s+10} + \frac{K_3}{s+20}$$

$$K_1 = 10; \quad K_2 = -24; \quad K_3 = 14$$

$$\therefore v_o(t) = [10 - 24e^{-10t} + 14e^{-20t}]u(t) \text{ V}$$

**[b]**  $10 - 24e^{-10t} + 14e^{-20t} = 5$

Let  $x = e^{-10t_s}$ . Then

$$10 - 24x + 14x^2 = 5$$

$$14x^2 - 24x + 5 = 0$$

$$x = 0.242691$$

$$e^{-10t_s} = 0.242691 \quad \therefore \quad t_s = 141.60 \text{ ms}$$

**P 13.47** Let  $v_{o1}$  equal the output voltage of the first op amp. Then

$$V_{o1} = \frac{-Z_{f1}}{Z_{A1}} V_g \quad \text{where} \quad Z_{f1} = 25 \times 10^3 \Omega$$

$$Z_{A1} = 25,000 + \frac{25,000(20 \times 10^4/s)}{25,000 + (20 \times 10^4/s)}$$

$$= \frac{25,000(s+16)}{(s+8)} \Omega$$

$$\therefore V_{o1} = \frac{-(s+8)}{(s+16)} V_g$$

Also,

$$V_o = \frac{-Z_{f2}}{Z_{A2}} V_{o1} \quad \text{where} \quad Z_{f2} = \frac{2 \times 10^8}{s} \Omega \text{ and } Z_{A2} = 25,000 \Omega$$

$$\therefore V_o = \frac{-8000}{s} V_{o1} = \frac{-8000}{s} \left[ \frac{-(s+8)}{(s+16)} \right] V_g$$

$$= \frac{8000(s+8)}{s(s+16)} V_g$$

$$v_g(t) = 16u(t) \text{ mV}; \quad \therefore \quad V_g = \frac{16 \times 10^{-3}}{s}$$

$$V_o = \frac{128(s+8)}{s^2(s+16)} = \frac{K_1}{s^2} + \frac{K_2}{s} + \frac{K_3}{s+16}$$

$$K_1 = \frac{128(8)}{16} = 64$$

$$K_2 = 128 \frac{d}{ds} \left[ \frac{s+8}{s+16} \right]_{s=0} = 4$$

$$K_3 = \frac{128(-8)}{256} = -4$$

$$v_o(t) = [64t + 4 - 4e^{-16t}]u(t) \text{ V}$$

The op amp will saturate when  $v_o = \pm 6 \text{ V}$ . Hence, saturation will occur when

$$64t + 4 - 4e^{-16t} = 6 \quad \text{or} \quad 16t - 0.5 = e^{-16t}$$

This equation can be solved by trial and error. First note that  $t > 0.5/16$  or  $t > 31.25 \text{ ms}$ .

Try 40 ms:

$$0.64 - 0.5 = 0.14; \quad e^{-0.64} = 0.53$$

Try 50 ms:

$$0.80 - 0.5 = 0.30; \quad e^{-0.80} = 0.45$$

Try 60 ms:

$$0.96 - 0.5 = 0.46; \quad e^{-0.96} = 0.38$$

Further trial and error gives

$$t_{\text{sat}} \cong 56.5 \text{ ms}$$

**P 13.48 [a]** Let  $v_a$  be the voltage across the  $0.5 \mu\text{F}$  capacitor, positive at the upper terminal.

Let  $v_b$  be the voltage across the  $100 \text{ k}\Omega$  resistor, positive at the upper terminal.

Also note

$$\frac{10^6}{0.5s} = \frac{2 \times 10^6}{s} \quad \text{and} \quad \frac{10^6}{0.25s} = \frac{4 \times 10^6}{s}; \quad V_g = \frac{0.5}{s}$$

$$\frac{sV_a}{2 \times 10^6} + \frac{V_a - (0.5/s)}{200,000} + \frac{V_a}{200,000} = 0$$

$$sV_a + 10V_a - \frac{5}{s} + 10V_a = 0$$

$$V_a = \frac{5}{s(s+20)}$$

$$\frac{0 - V_a}{200,000} + \frac{(0 - V_b)s}{4 \times 10^6} = 0$$

$$\therefore V_b = -\frac{20}{s}V_a = \frac{-100}{s^2(s+20)}$$

$$\frac{V_b}{100,000} + \frac{(V_b - 0)s}{4 \times 10^6} + \frac{(V_b - V_o)s}{4 \times 10^6} = 0$$

$$40V_b + sV_b + sV_b = sV_o$$

$$\therefore V_o = \frac{2(s+20)V_b}{s}; \quad V_o = 2\left(\frac{-100}{s^3}\right) = \frac{-200}{s^3}$$

**[b]**  $v_o(t) = -100t^2u(t) \text{ V}$

**[c]**  $-100t^2 = -4; \quad t = 0.2 \text{ s} = 200 \text{ ms}$

P 13.49 **[a]**  $\frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC}$

$$H(s) = \frac{(1/RC)}{s + (1/RC)} = \frac{200}{s + 200}; \quad -p_1 = -200 \text{ rad/s}$$

**[b]**  $\frac{V_o}{V_i} = \frac{R}{R + 1/sC} = \frac{RCs}{RCs + 1} = \frac{s}{s + (1/RC)}$

$$= \frac{s}{s + 200}; \quad z_1 = 0, \quad -p_1 = -200 \text{ rad/s}$$


**[c]**  $\frac{V_o}{V_i} = \frac{sL}{R + sL} = \frac{s}{s + R/L} = \frac{s}{s + 8000}$

$$z_1 = 0; \quad -p_1 = -8000 \text{ rad/s}$$

**[d]**  $\frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R/L}{s + (R/L)} = \frac{8000}{s + 8000}$

$$-p_1 = -8000 \text{ rad/s}$$

**[e]**

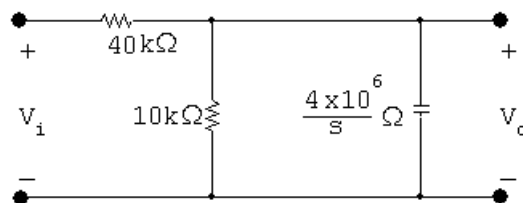

$$\frac{V_o s}{4 \times 10^6} + \frac{V_o}{10,000} + \frac{V_o - V_i}{40,000} = 0$$

$$sV_o + 400V_o + 100V_o = 100V_i$$

$$H(s) = \frac{V_o}{V_i} = \frac{100}{s + 500}$$

$$-p_1 = -500 \text{ rad/s}$$

P 13.50 [a] Let  $R_1 = 250 \text{ k}\Omega$ ;  $R_2 = 125 \text{ k}\Omega$ ;  $C_2 = 1.6 \text{ nF}$ ; and  $C_f = 0.4 \text{ nF}$ . Then

$$Z_f = \frac{(R_2 + 1/sC_2)1/sC_f}{\left(R_2 + \frac{1}{sC_2} + \frac{1}{sC_f}\right)} = \frac{(s + 1/R_2C_2)}{C_f s \left(s + \frac{C_2 + C_f}{C_2 C_f R_2}\right)}$$

$$\frac{1}{C_f} = 2.5 \times 10^9$$

$$\frac{1}{R_2 C_2} = \frac{62.5 \times 10^7}{125 \times 10^3} = 5000 \text{ rad/s}$$

$$\frac{C_2 + C_f}{C_2 C_f R_2} = \frac{2 \times 10^{-9}}{(0.64 \times 10^{-18})(125 \times 10^3)} = 25,000 \text{ rad/s}$$

$$\therefore Z_f = \frac{2.5 \times 10^9 (s + 5000)}{s(s + 25,000)} \Omega$$


$$Z_i = R_1 = 250 \times 10^3 \Omega$$

$$H(s) = \frac{V_o}{V_g} = \frac{-Z_f}{Z_i} = \frac{-10^4 (s + 5000)}{s(s + 25,000)}$$

[b]  $-z_1 = -5000 \text{ rad/s}$

$$-p_1 = 0; \quad -p_2 = -25,000 \text{ rad/s}$$

P 13.51 [a]

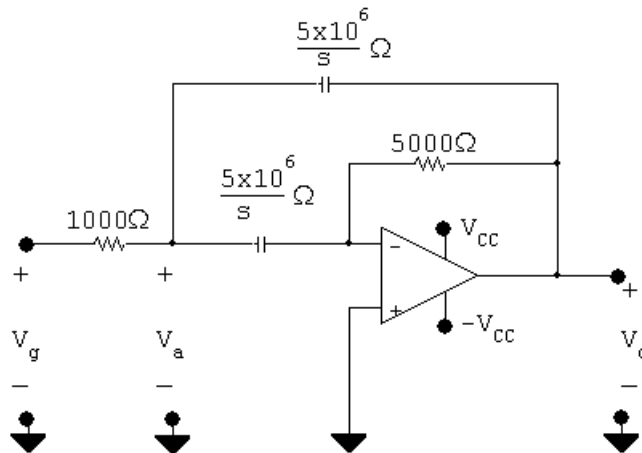

$$\frac{V_a - V_g}{1000} + \frac{sV_a}{5 \times 10^6} + \frac{(V_a - V_o)s}{5 \times 10^6} = 0$$

$$5000V_a - 5000V_g + 2sV_a - sV_o = 0$$

$$(5000 + 2s)V_a - sV_o = 5000V_g$$

$$\frac{(0 - V_a)s}{5 \times 10^6} + \frac{0 - V_o}{5000} = 0$$

$$-sV_a - 1000V_o = 0; \quad \therefore \quad V_a = \frac{-1000}{s}V_o$$

$$(2s + 5000) \left( \frac{-1000}{s} \right) V_o - sV_o = 5000V_g$$

$$1000V_o(2s + 5000) + s^2V_o = -5000sV_g$$

$$V_o(s^2 + 2000s + 5 \times 10^6) = -5000sV_g$$

$$\frac{V_o}{V_g} = \frac{-5000s}{s^2 + 2000s + 5 \times 10^6}$$

$$s_{1,2} = -1000 \pm \sqrt{10^6 - 5 \times 10^6} = -1000 \pm j2000$$

$$\frac{V_o}{V_g} = \frac{-5000s}{(s + 1000 - j2000)(s + 1000 + j2000)}$$

**[b]**  $z_1 = 0; \quad -p_1 = -1000 + j2000; \quad -p_2 = -1000 - j2000$


**P 13.52 [a]**  $Z_i = 1000 + \frac{5 \times 10^6}{s} = \frac{1000(s + 5000)}{s}$

$$Z_f = \frac{40 \times 10^6}{s} \parallel 40,000 = \frac{40 \times 10^6}{s + 1000}$$

$$H(s) = -\frac{Z_f}{Z_i} = \frac{-40 \times 10^6 / (s + 1000)}{1000(s + 5000)/s} = \frac{-40,000s}{(s + 1000)(s + 5000)}$$

**[b]** Zero at  $s = 0$ ; Poles at  $-p_1 = -1000$  rad/s and  $-p_2 = -5000$  rad/s

**P 13.53 [a]**

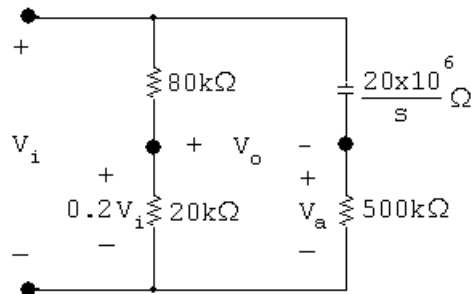

$$V_a = \frac{V_i}{500,000 + [(20 \times 10^6)/s]}(500,000) = \frac{s}{s + 40}V_i$$

$$0.2V_i = V_o + V_a$$


$$\therefore V_o = 0.2V_i - \frac{s}{s+40}V_i$$

$$\frac{V_o}{V_i} = \frac{0.2(s+40) - s}{s+40} = \frac{-0.8s+8}{s+40} = \frac{-0.8(s-10)}{s+40}$$

**[b]**  $-z_1 = 10 \text{ rad/s}$

$$-p_1 = -40 \text{ rad/s}$$

P 13.54

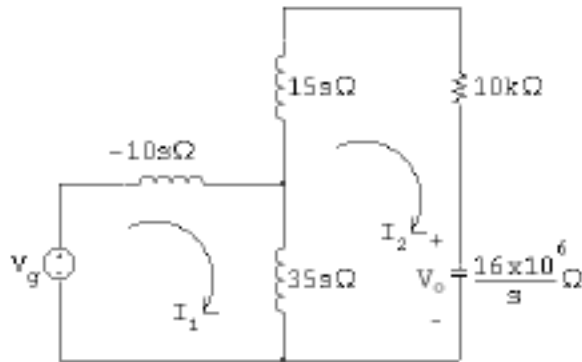

$$V_g = 25sI_1 - 35sI_2$$

$$0 = -35sI_1 + \left(50s + 10,000 + \frac{16 \times 10^6}{s}\right) I_2$$

$$\Delta = \begin{vmatrix} 25s & -35s \\ -35s & 50s + 10,000 + 16 \times 10^6/s \end{vmatrix} = 25(s+2000)(s+8000)$$

$$N_2 = \begin{vmatrix} 25s & V_g \\ -35s & 0 \end{vmatrix} = 35sV_g$$

$$I_2 = \frac{N_2}{\Delta} = \frac{35sV_g}{25(s+2000)(s+8000)}$$


$$V_o = \frac{16 \times 10^6}{s} I_2 = \frac{22.4 \times 10^6 V_g}{(s+2000)(s+8000)}$$

$$H(s) = \frac{V_o}{V_g} = \frac{22.4 \times 10^6}{(s+2000)(s+8000)}$$

$$\therefore -p_1 = -2000 \text{ rad/s}; \quad -p_2 = -8000 \text{ rad/s}$$



P 13.55 [a]

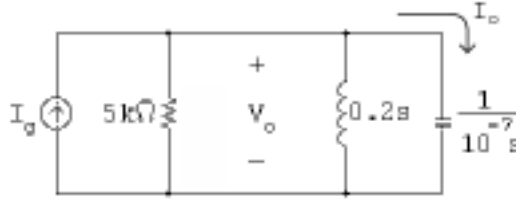

$$\frac{V_o}{5000} + \frac{V_o}{0.2s} + V_o(10^{-7})s = I_g$$

$$\therefore V_o = \frac{10 \times 10^6 s}{s^2 + 2000s + 50 \times 10^6} \cdot I_g$$

$$I_g = \frac{0.1s}{s^2 + 10^8}; \quad I_o = \frac{V_o s}{10 \times 10^6}$$

$$\therefore H(s) = \frac{s^2}{s^2 + 2000s + 50 \times 10^6}$$

$$\text{[b]} \quad I_o = \frac{(s^2)(0.1s)}{(s + 1000 - j7000)(s + 1000 + j7000)(s^2 + 10^8)}$$

$$I_o = \frac{0.1s^3}{(s + 1000 - j7000)(s + 1000 + j7000)(s + j10^4)(s - j10^4)}$$

[c] Damped sinusoid of the form

$$Me^{-1000t} \cos(7000t + \theta_1)$$

[d] Steady-state sinusoid of the form

$$N \cos(10^4 t + \theta_2)$$

$$\text{[e]} \quad I_o = \frac{K_1}{s + 1000 - j7000} + \frac{K_1^*}{s + 1000 + j7000} + \frac{K_2}{s - j10^4} + \frac{K_2^*}{s + j10^4}$$

$$K_1 = \frac{0.1(-1000 + j7000)^3}{(j14,000)(-1000 - j3000)(-1000 + j17,000)} = 46.90 \times 10^{-3} \angle -140.54^\circ$$

$$K_2 = \frac{0.1(j10^4)^3}{(j20,000)(1000 + j3000)(1000 + j17,000)} = 92.85 \times 10^{-3} \angle 21.80^\circ$$

$$i_o(t) = [93.8e^{-1000t} \cos(7000t - 140.54^\circ) + 185.7 \cos(10^4 t + 21.80^\circ)] \text{ mA}$$

Test:

$$i_o(0) = 93.8 \cos(-140.54^\circ) + 185.7 \cos(21.80^\circ) \text{ mA} = 100 \text{ mA}$$

$$Z = \frac{1}{Y}; \quad Y = \frac{1}{5000} + \frac{1}{j2000} + \frac{1}{-j1000} = \frac{2 + j5}{10,000}$$


$$\therefore Z = \frac{10,000}{2 + j5} = 1856.95 \angle -68.2^\circ \Omega$$

$$\mathbf{V}_o = \mathbf{I}_g Z = (0.1/\underline{0^\circ})(1856.95/\underline{-68.2^\circ}) = 185.695/\underline{-68.2^\circ} \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_o}{-j1000} = 185.7/\underline{21.80^\circ} \text{ mA}$$

$$i_{oss} = 185.7 \cos(10^4 t + 21.80^\circ) \text{ mA (Checks)}$$

P 13.56 [a]

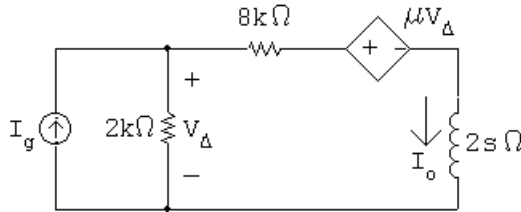

$$2000(I_o - I_g) + 8000I_o + \mu(I_g - I_o)(2000) + 2sI_o = 0$$

$$\therefore I_o = \frac{1000(1 - \mu)}{s + 1000(5 - \mu)} I_g$$

$$\therefore H(s) = \frac{1000(1 - \mu)}{s + 1000(5 - \mu)}$$

[b]  $\mu < 5$ 

[c]

$\mu$	$H(s)$	$I_o$
-3	$4000/(s + 8000)$	$20,000/s(s + 8000)$
0	$1000/(s + 5000)$	$5000/s(s + 5000)$
4	$-3000/(s + 1000)$	$-15,000/s(s + 1000)$
5	$-4000/s$	$-20,000/s^2$
6	$-5000/(s - 1000)$	$-25,000/s(s - 1000)$

 $\mu = -3$ :

$$I_o = \frac{2.5}{s} - \frac{2.5}{(s + 8000)}; \quad i_o = [2.5 - 2.5e^{-8000t}]u(t) \text{ A}$$

 $\mu = 0$ :

$$I_o = \frac{1}{s} - \frac{1}{s + 5000}; \quad i_o = [1 - e^{-5000t}]u(t) \text{ A}$$

 $\mu = 4$ :

$$I_o = \frac{-15}{s} + \frac{15}{s + 1000}; \quad i_o = [-15 + 15e^{-1000t}]u(t) \text{ A}$$

 $\mu = 5$ :


$$I_o = \frac{-20,000}{s^2}; \quad i_o = -20,000t u(t) \text{ A}$$

$$\mu = 6:$$

$$I_o = \frac{25}{s} - \frac{25}{s - 1000}; \quad i_o = 25[1 - e^{1000t}]u(t) \text{ A}$$

P 13.57  $H(s) = \frac{V_o}{V_i} = \frac{1}{s+1}; \quad h(t) = e^{-t}$

For  $0 \leq t \leq 1$ :

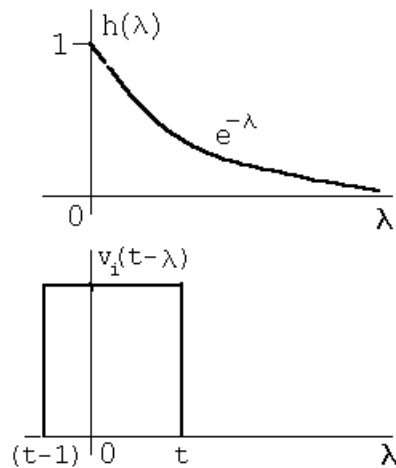

$$v_o = \int_0^t e^{-\lambda} d\lambda = (1 - e^{-t}) \text{ V}$$

For  $1 \leq t \leq \infty$ :

$$v_o = \int_{t-1}^t e^{-\lambda} d\lambda = (e - 1)e^{-t} \text{ V}$$

P 13.58  $H(s) = \frac{V_o}{V_i} = \frac{s}{s+1} = 1 - \frac{1}{s+1}; \quad h(t) = \delta(t) - e^{-t}$

$$h(\lambda) = \delta(\lambda) - e^{-\lambda}$$


For  $0 \leq t \leq 1$ :

$$v_o = \int_0^t [\delta(\lambda) - e^{-\lambda}] d\lambda = 1 + [e^{-\lambda}]_0^t = e^{-t} \text{ V}$$

For  $1 \leq t \leq \infty$ :

$$v_o = \int_{t-1}^t (-e^{-\lambda}) d\lambda = e^{-\lambda} \Big|_{t-1}^t = (1 - e)e^{-t} \text{ V}$$

P 13.59 [a]

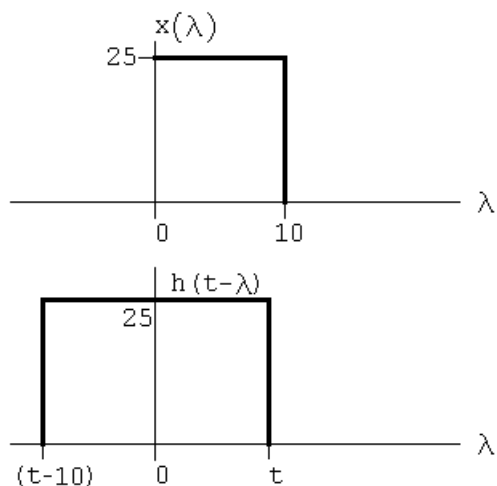


$$t < 0 : \quad y(t) = 0$$


$$0 \leq t \leq 10 : \quad y(t) = \int_0^t 625 \, d\lambda = 625t$$

$$10 \leq t \leq 20 : \quad y(t) = \int_{t-10}^{10} 625 \, d\lambda = 625(10 - t + 10) = 625(20 - t)$$

$$20 \leq t < \infty : \quad y(t) = 0$$

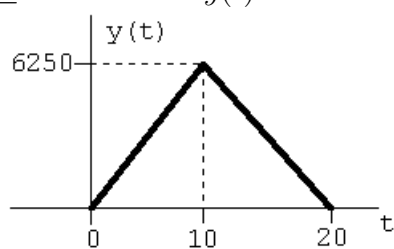

[b]

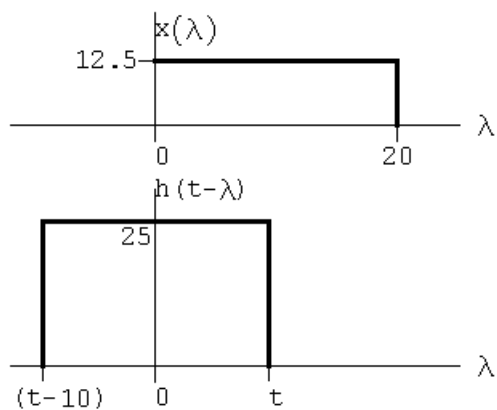



$$t < 0 : \quad y(t) = 0$$

$$0 \leq t \leq 10 : \quad y(t) = \int_0^t 312.5 \, d\lambda = 312.5t$$

$$10 \leq t \leq 20 : \quad y(t) = \int_{t-10}^t 312.5 \, d\lambda = 3125$$

$$20 \leq t \leq 30 : \quad y(t) = \int_{t-10}^{20} 312.5 \, d\lambda = 312.5(30 - t)$$

$$30 \leq t < \infty : \quad y(t) = 0$$

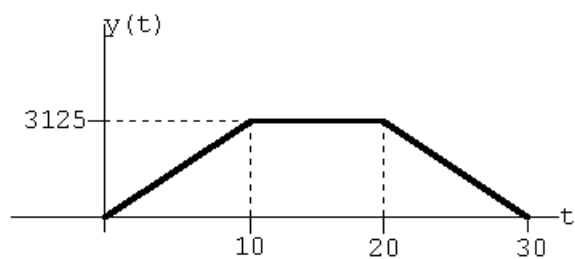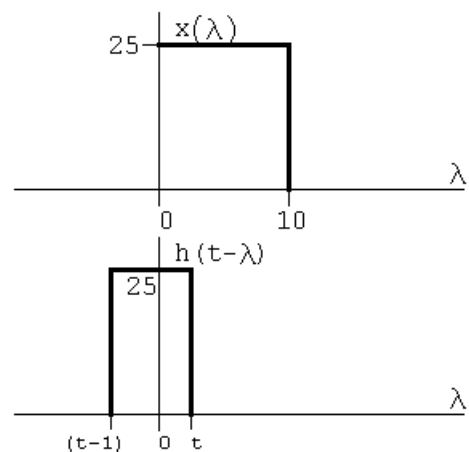**[c]**


$$t < 0 : \quad y(t) = 0$$


$$0 \leq t \leq 1 : \quad y(t) = \int_0^t 625 \, d\lambda = 625t$$

$$1 \leq t \leq 10 : \quad y(t) = \int_{t-1}^t 625 \, d\lambda = 625$$


$$10 \leq t \leq 11 : \quad y(t) = \int_{t-1}^{10} 625 \, d\lambda = 625(11 - t)$$

$$11 \leq t < \infty : \quad y(t) = 0$$

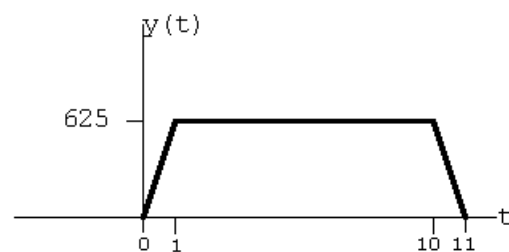

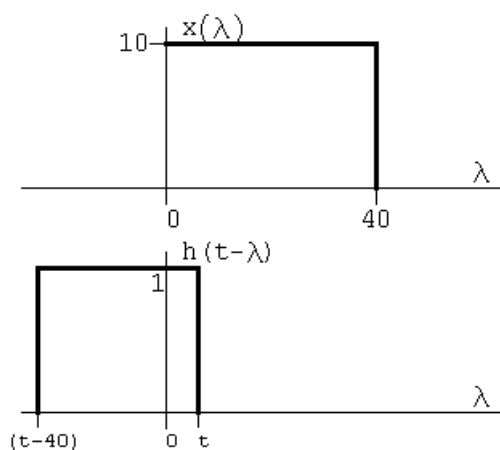P 13.60 [a]  $0 \leq t \leq 40$ :


$$y(t) = \int_0^t (10)(1)(d\lambda) = 10\lambda \Big|_0^t = 10t$$

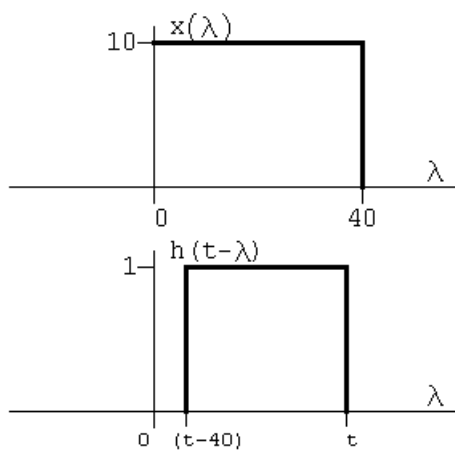 $40 \leq t \leq 80$ :

$$y(t) = \int_{t-40}^{40} (10)(1)(d\lambda) = 10\lambda \Big|_{t-40}^{40} = 10(80 - t)$$


 $t \geq 80$  :  $y(t) = 0$

**[b]**  $0 \leq t \leq 10$ :

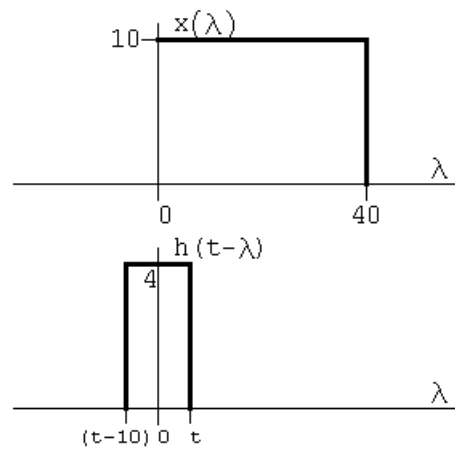


$$y(t) = \int_0^t 40 \, d\lambda = 40\lambda \Big|_0^t = 40t$$

$10 \leq t \leq 40$ :

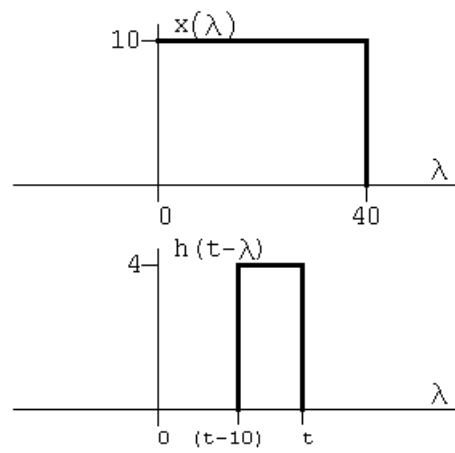

$$y(t) = \int_{t-10}^t 40 \, d\lambda = 40\lambda \Big|_{t-10}^t = 400$$

$$40 \leq t \leq 50:$$

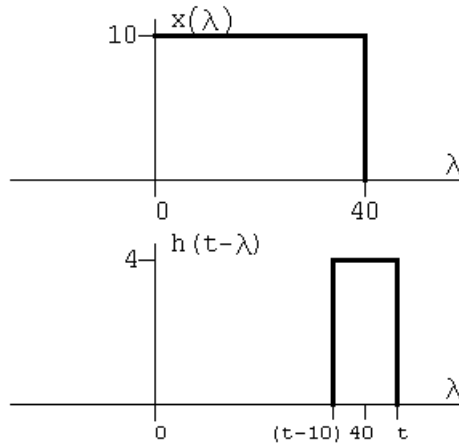

$$y(t) = \int_{t-10}^{40} 40 d\lambda = 40\lambda \Big|_{t-10}^{40} = 40(50 - t)$$

$$t \geq 50 : \quad y(t) = 0$$

**[c]** The expressions are


$$0 \leq t \leq 1 : \quad y(t) = \int_0^t 400 d\lambda = 400\lambda \Big|_0^t = 400t$$

$$1 \leq t \leq 40 : \quad y(t) = \int_{t-1}^t 400 d\lambda = 400\lambda \Big|_{t-1}^t = 400$$

$$40 \leq t \leq 41 : \quad y(t) = \int_{t-1}^{40} 400 d\lambda = 400\lambda \Big|_{t-1}^{40} = 400(41 - t)$$

$$41 \leq t < \infty : \quad y(t) = 0$$

**[d]**

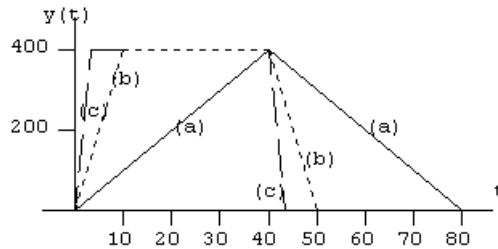

**[e]** Yes, note that  $h(t)$  is approaching  $40\delta(t)$ , therefore  $y(t)$  must approach  $40x(t)$ , i.e.

$$\begin{aligned} y(t) &= \int_0^t h(t-\lambda)x(\lambda) d\lambda \rightarrow \int_0^t 40\delta(t-\lambda)x(\lambda) d\lambda \\ &\rightarrow 40x(t) \end{aligned}$$

This can be seen in the plot, e.g., in part (c),  $y(t) \cong 40x(t)$ .



P 13.61 [a]  $-1 \leq t \leq 4$ :

$$v_o = \int_0^{t+1} 10\lambda \, d\lambda = 5\lambda^2 \Big|_0^{t+1} = 5t^2 + 10t + 5 \text{ V}$$

$4 \leq t \leq 9$ :

$$v_o = \int_{t-4}^{t+1} 10\lambda \, d\lambda = 5\lambda^2 \Big|_{t-4}^{t+1} = 50t - 75 \text{ V}$$

$9 \leq t \leq 14$ :

$$\begin{aligned} v_o &= 10 \int_{t-4}^{10} \lambda \, d\lambda + 10 \int_{10}^{t+1} 10 \, d\lambda \\ &= 5\lambda^2 \Big|_{t-4}^{10} + 100\lambda \Big|_{10}^{t+1} = -5t^2 + 140t - 480 \text{ V} \end{aligned}$$

$14 \leq t \leq 19$ :

$$v_o = 100 \int_{t-4}^{t+1} d\lambda = 500 \text{ V}$$

$19 \leq t \leq 24$ :

$$\begin{aligned} v_o &= \int_{t-4}^{20} 100 \, d\lambda + \int_{20}^{t+1} 10(30 - \lambda) \, d\lambda \\ &= 100\lambda \Big|_{t-4}^{20} + 300\lambda \Big|_{20}^{t+1} - 5\lambda^2 \Big|_{20}^{t+1} \\ &= -5t^2 + 190t - 1305 \text{ V} \end{aligned}$$

$24 \leq t \leq 29$ :

$$\begin{aligned} v_o &= 10 \int_{t-4}^{t+1} (30 - \lambda) \, d\lambda = 300\lambda \Big|_{t-4}^{t+1} - 5\lambda^2 \Big|_{t-4}^{t+1} \\ &= 1575 - 50t \text{ V} \end{aligned}$$

$29 \leq t \leq 34$ :

$$\begin{aligned} v_o &= 10 \int_{t-4}^{30} (30 - \lambda) \, d\lambda = 300\lambda \Big|_{t-4}^{30} - 5\lambda^2 \Big|_{t-4}^{30} \\ &= 5t^2 - 340t + 5780 \text{ V} \end{aligned}$$

**Summary:**

$$v_o = 0 \quad -\infty \leq t \leq -1$$

$$v_o = 5t^2 + 10t + 5 \text{ V} \quad -1 \leq t \leq 4$$

$$v_o = 50t - 75 \text{ V} \quad 4 \leq t \leq 9$$

$$v_o = -5t^2 + 140t - 480 \text{ V} \quad 9 \leq t \leq 14$$

$$v_o = 500 \text{ V} \quad 14 \leq t \leq 19$$


$$v_o = -5t^2 + 190t - 1305 \text{ V} \quad 19 \leq t \leq 24$$

$$v_o = 1575 - 50t \text{ V} \quad 24 \leq t \leq 29$$

$$v_o = 5t^2 - 340t + 5780 \text{ V} \quad 29 \leq t \leq 34$$



$$v_o = 0 \text{ V} \quad 34 \leq t \leq \infty$$

**[b]**

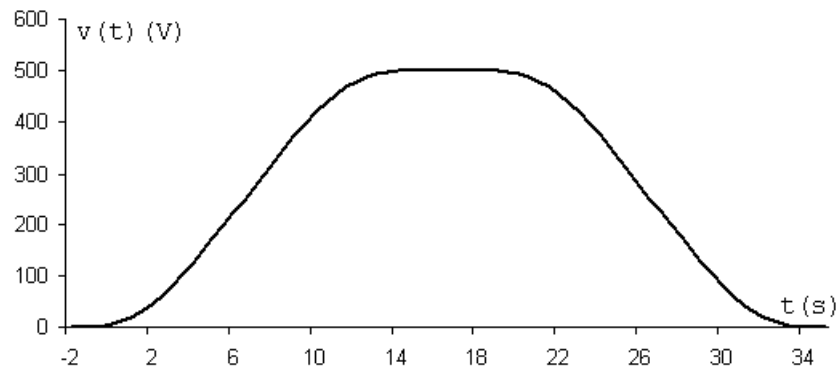

P 13.62 **[a]**  $h(\lambda) = \frac{2}{5}\lambda \quad 0 \leq \lambda \leq 5$
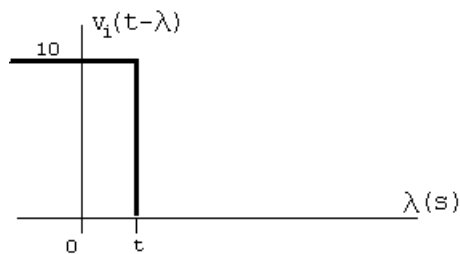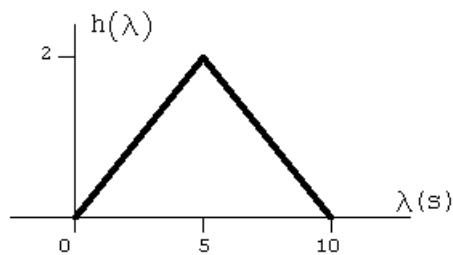
$$h(\lambda) = \left(4 - \frac{2}{5}\lambda\right) \quad 5 \leq \lambda \leq 10$$



$$0 \leq t \leq 5:$$

$$v_o = 10 \int_0^t \frac{2}{5}\lambda d\lambda = 2t^2$$

$5 \leq t \leq 10$ :

$$\begin{aligned} v_o &= 10 \int_0^5 \frac{2}{5} \lambda d\lambda + 10 \int_5^t \left(4 - \frac{2}{5} \lambda\right) d\lambda \\ &= \frac{4\lambda^2}{2} \Big|_0^5 + 40\lambda \Big|_5^t - \frac{4\lambda^2}{2} \Big|_5^t \\ &= -100 + 40t - 2t^2 \end{aligned}$$

$10 \leq t \leq \infty$ :

$$\begin{aligned} v_o &= 10 \int_0^5 \frac{2}{5} \lambda d\lambda + 10 \int_5^{10} \left(4 - \frac{2}{5} \lambda\right) d\lambda \\ &= \frac{4\lambda^2}{2} \Big|_0^5 + 40\lambda \Big|_5^{10} - \frac{4\lambda^2}{2} \Big|_5^{10} \\ &= 50 + 200 - 150 = 100 \end{aligned}$$


**Summary:**

$$v_o = 2t^2 \text{ V} \quad 0 \leq t \leq 5$$

$$v_o = 40t - 100 - 2t^2 \text{ V} \quad 5 \leq t \leq 10$$

$$v_o = 100 \text{ V} \quad 10 \leq t \leq \infty$$


**[b]**

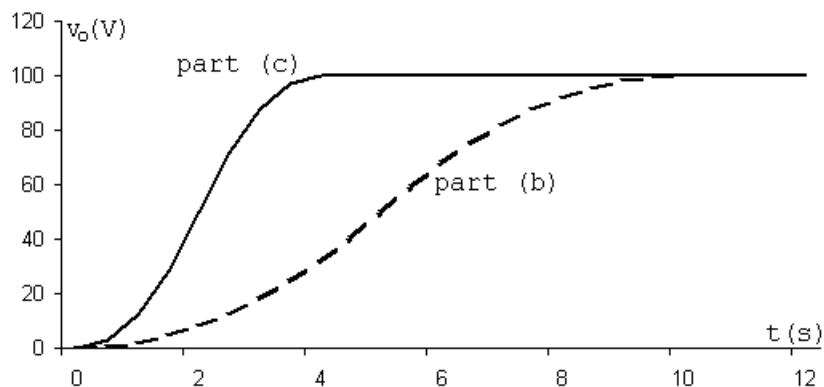

**[c]** Area =  $\frac{1}{2}(10)(2) = 10 \quad \therefore \quad \frac{1}{2}(4)h = 10 \quad \text{so} \quad h = 5$

$$h(\lambda) = \frac{5}{2}\lambda \quad 0 \leq \lambda \leq 2$$
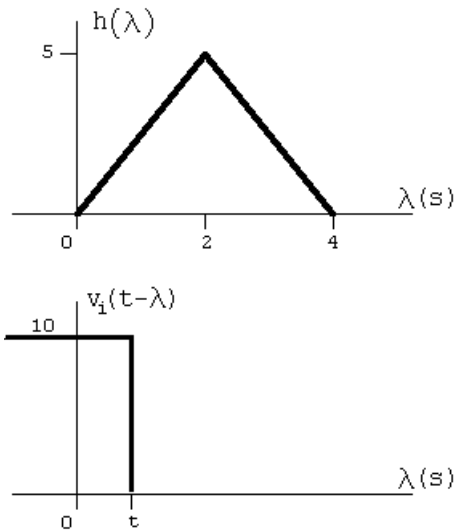
$$h(\lambda) = \left(10 - \frac{5}{2}\lambda\right) \quad 2 \leq \lambda \leq 4$$



$$0 \leq t \leq 2:$$

$$v_o = 10 \int_0^t \frac{5}{2} \lambda d\lambda = 12.5t^2$$

$$2 \leq t \leq 4:$$

$$\begin{aligned} v_o &= 10 \int_0^2 \frac{5}{2} \lambda d\lambda + 10 \int_2^t \left(10 - \frac{5}{2} \lambda\right) d\lambda \\ &= \frac{25\lambda^2}{2} \Big|_0^2 + 100\lambda \Big|_2^t - \frac{25\lambda^2}{2} \Big|_2^t \\ &= -100 + 100t - 12.5t^2 \end{aligned}$$

$$4 \leq t \leq \infty:$$

$$\begin{aligned} v_o &= 10 \int_0^2 \frac{5}{2} \lambda d\lambda + 10 \int_2^4 \left(10 - \frac{5}{2} \lambda\right) d\lambda \\ &= \frac{25\lambda^2}{2} \Big|_0^2 + 100\lambda \Big|_2^4 - \frac{25\lambda^2}{2} \Big|_2^4 \\ &= 50 + 200 - 150 = 100 \end{aligned}$$


$$v_o = 12.5t^2 \text{ V} \quad 0 \leq t \leq 2$$

$$v_o = 100t - 100 - 12.5t^2 \text{ V} \quad 2 \leq t \leq 4$$

$$v_o = 100 \text{ V} \quad 4 \leq t \leq \infty$$


**[d]** The waveform in part (c) is closer to replicating the input waveform because in part (c)  $h(\lambda)$  is closer to being an ideal impulse response. That is, the area was preserved as the base was shortened.

P 13.63 [a]

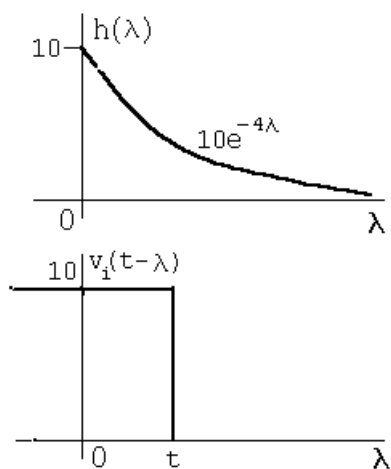

$$\begin{aligned}
 v_o &= \int_0^t 10(10e^{-4\lambda}) d\lambda \\
 &= 100 \frac{e^{-4\lambda}}{-4} \bigg|_0^t = -25[e^{-4t} - 1] \\
 &= 25(1 - e^{-4t}) \text{ V}, \quad 0 \leq t \leq \infty
 \end{aligned}$$

[b]

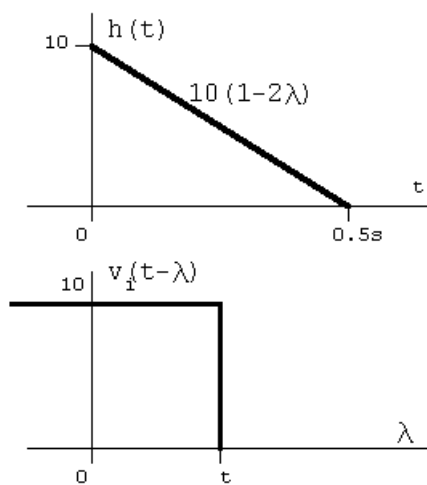


$$0 \leq t \leq 0.5:$$

$$v_o = \int_0^t 100(1 - 2\lambda) d\lambda = 100(\lambda - \lambda^2) \bigg|_0^t = 100t(1 - t)$$

$$0.5 \leq t \leq \infty:$$

$$v_o = \int_0^{0.5} 100(1 - 2\lambda) d\lambda = 100(\lambda - \lambda^2) \bigg|_0^{0.5} = 25$$

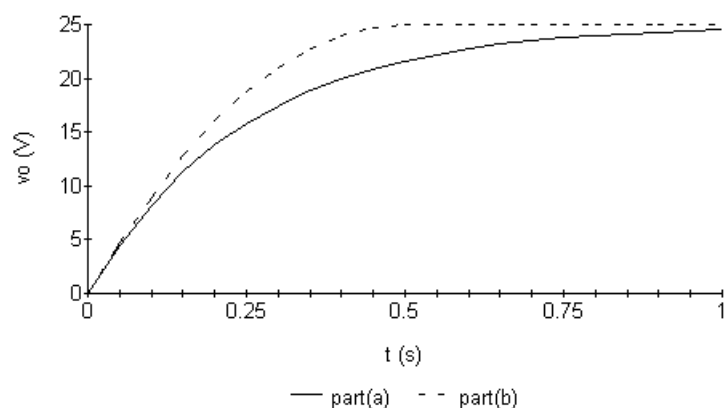**[c]**P 13.64 **[a]** From Problem 13.49(a)

$$H(s) = \frac{200}{s + 200}$$


$$h(\lambda) = 200e^{-200\lambda}$$

$$0 \leq t \leq 5 \text{ ms:}$$

$$v_o = \int_0^t 20(200)e^{-200\lambda} d\lambda = 20(1 - e^{-200t}) \text{ V}$$

$$5 \text{ ms} \leq t \leq \infty:$$

$$v_o = \int_{t-5 \times 10^{-3}}^t 20(200)e^{-200\lambda} d\lambda = 20(e^1 - 1)e^{-200t} \text{ V}$$

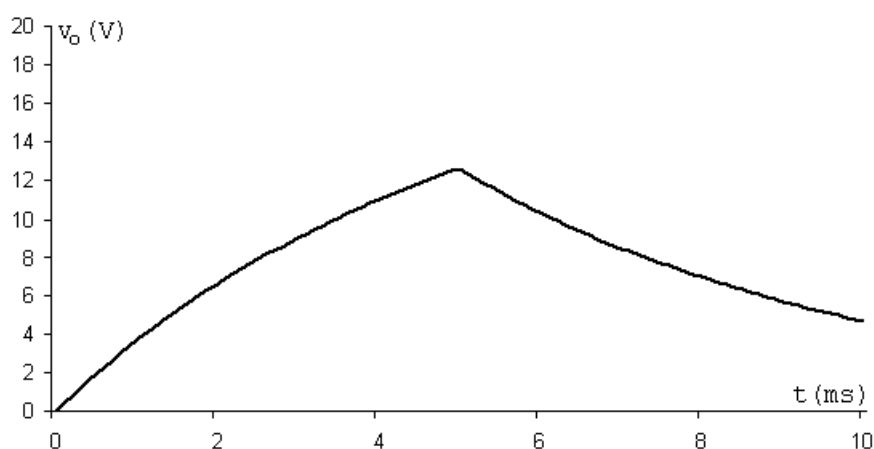**[b]**


P 13.65 **[a]**  $H(s) = \frac{2000}{s + 2000} \quad \therefore \quad h(\lambda) = 2000e^{-2000\lambda}$

$0 \leq t \leq 5 \text{ ms}$ :

$$v_o = \int_0^t 20(2000)e^{-2000\lambda} d\lambda = 20(1 - e^{-2000t}) \text{ V}$$

$5 \text{ ms} \leq t \leq \infty$ :
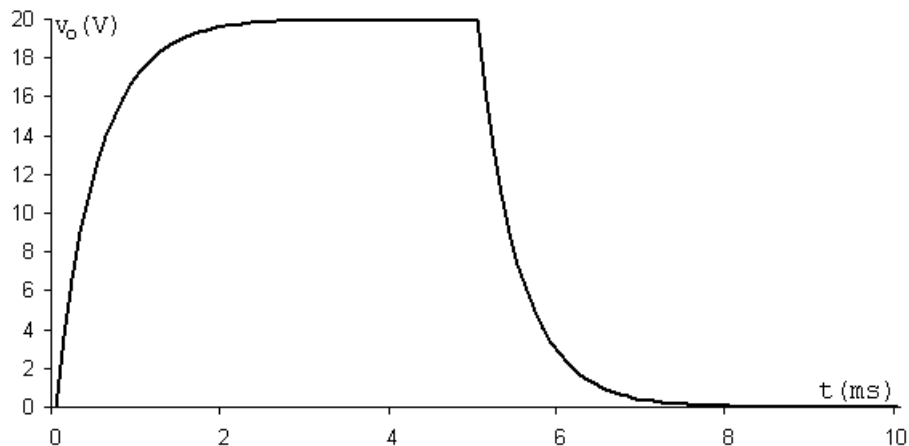
$$v_o = \int_{t-5 \times 10^{-3}}^t 20(2000)e^{-2000\lambda} d\lambda = 20(e^{10} - 1)e^{-2000t} \text{ V}$$




**[b]** decrease

**[c]** The circuit with  $R = 5 \text{ k}\Omega$ .

P 13.66 **[a]**  $I_g = \frac{V_o}{10^5} + \frac{V_o s}{5 \times 10^6} = \frac{V_o(s + 50)}{5 \times 10^6}$

$$\frac{V_o}{I_g} = H(s) = \frac{5 \times 10^6}{s + 50}$$
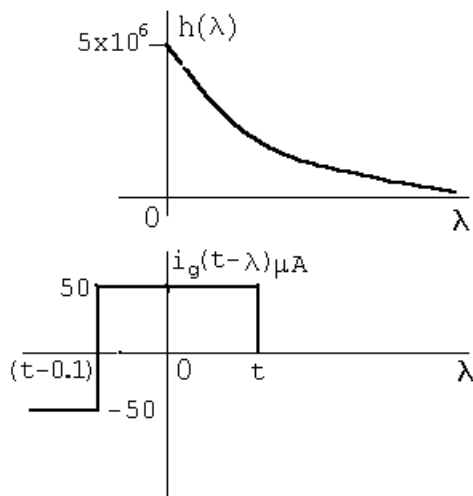
$$h(\lambda) = 5 \times 10^6 e^{-50\lambda} u(\lambda)$$




$$0 \leq t \leq 0.1 \text{ s:}$$

$$v_o = \int_0^t (50 \times 10^{-6})(5 \times 10^6) e^{-50\lambda} d\lambda = 250 \frac{e^{-50\lambda}}{-50} \Big|_0^t$$

$$= 5(1 - e^{-50t}) \text{ V}$$
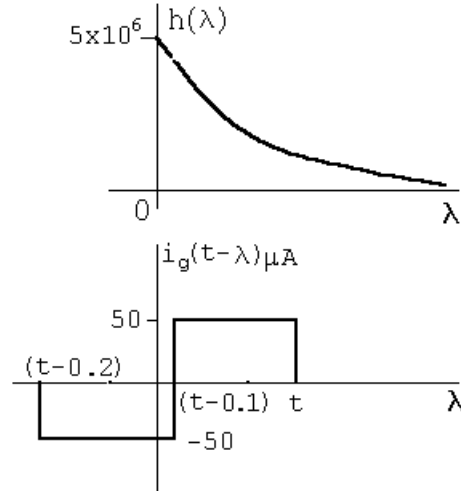
$$0.1 \text{ s} \leq t \leq 0.2 \text{ s:}$$



$$v_o = \int_0^{t-0.1} (-50 \times 10^{-6})(5 \times 10^6 e^{-50\lambda} d\lambda)$$

$$+ \int_{t-0.1}^t (50 \times 10^{-6})(5 \times 10^6 e^{-50\lambda} d\lambda)$$


$$= -250 \frac{e^{-50\lambda}}{-50} \Big|_0^{t-0.1} + 250 \frac{e^{-50\lambda}}{-50} \Big|_{t-0.1}^t$$

$$= 5 [e^{-50(t-0.1)} - 1] - 5 [e^{-50t} - e^{-50(t-0.1)}]$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50t} - 5] \text{ V}$$



$$0.2 \text{ s} \leq t \leq \infty:$$

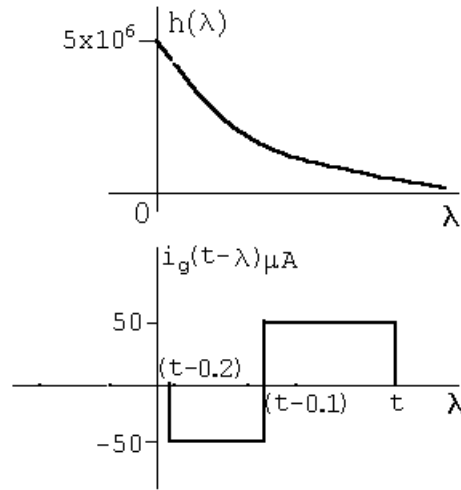

$$\begin{aligned} v_o &= \int_{t-0.2}^{t-0.1} -250e^{-50\lambda} d\lambda + \int_{t-0.1}^t 250e^{-50\lambda} d\lambda \\ &= 5e^{-50\lambda} \Big|_{t-0.2}^{t-0.1} - 5e^{-50\lambda} \Big|_{t-0.1}^t \\ v_o &= [10e^{-50(t-0.1)} - 5e^{-50(t-0.2)} - 5e^{-50t}] \text{ V} \end{aligned}$$

Summary:

$$v_o = 5(1 - e^{-50t}) \text{ V} \quad 0 \leq t \leq 0.1 \text{ s}$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50t} - 5] \text{ V} \quad 0.1 \text{ s} \leq t \leq 0.2 \text{ s}$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50(t-0.2)} - 5e^{-50t}] \text{ V} \quad 0.2 \text{ s} \leq t \leq \infty$$

$$\text{[b]} \quad I_o = \frac{V_o s}{5 \times 10^6} = \frac{s}{5 \times 10^6} \cdot \frac{5 \times 10^6 I_g}{s + 50}$$


$$\frac{I_o}{I_g} = H(s) = \frac{s}{s + 50} = 1 - \frac{50}{s + 50}$$

$$h(\lambda) = \delta(\lambda) - 50e^{-50\lambda}$$

$$0 < t < 0.1 \text{ s:}$$


$$\begin{aligned} i_o &= \int_0^t (50 \times 10^{-6}) [\delta(\lambda) - 50e^{-50\lambda}] d\lambda \\ &= 50 \times 10^{-6} - \left[ 50 \times 50 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \right] \Big|_0^t \\ &= 50 \times 10^{-6} + 50 \times 10^{-6} [e^{-50t} - 1] = 50e^{-50t} \mu\text{A} \end{aligned}$$

$0.1 \text{ s} < t < 0.2 \text{ s}$ :

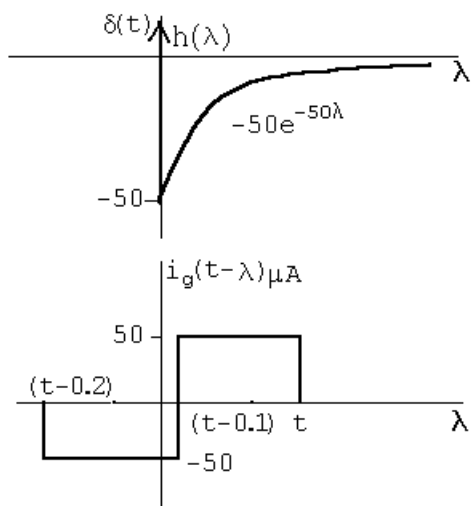

$$\begin{aligned}
 i_o &= \int_0^{t-0.1} (-50 \times 10^{-6}) [\delta(\lambda) - 50e^{-50\lambda}] d\lambda \\
 &\quad + \int_{t-0.1}^t (50 \times 10^{-6}) (-50e^{-50\lambda}) d\lambda \\
 &= -50 \times 10^{-6} + 2500 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \Big|_0^{t-0.1} - 2500 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \Big|_{t-0.1}^t \\
 &= -50 \times 10^{-6} - 50 \times 10^{-6} [e^{-50(t-0.1)} - 1] + 50 \times 10^{-6} [e^{-50t} - e^{-50(t-0.1)}] \\
 &= 50e^{-50t} - 100e^{-50(t-0.1)} \mu\text{A}
 \end{aligned}$$

$0.2 \text{ s} < t < \infty$ :

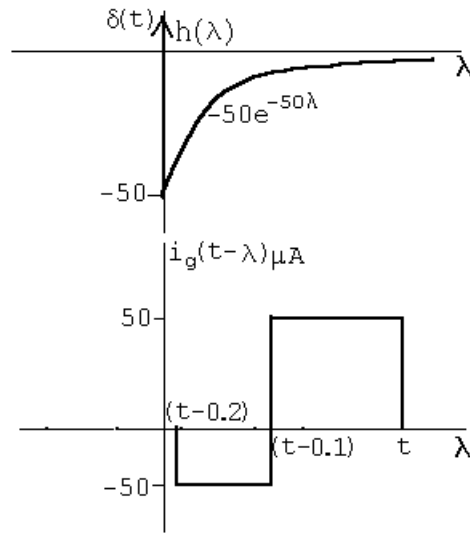

$$\begin{aligned}
 i_o &= \int_{t-0.2}^{t-0.1} (-50 \times 10^{-6})(-50e^{-50\lambda}) d\lambda \\
 &\quad + \int_{t-0.1}^t (50 \times 10^{-6})(-50e^{-50\lambda}) d\lambda \\
 &= 50e^{-50t} - 100e^{-50(t-0.1)} + 50e^{-50(t-0.2)} \mu\text{A}
 \end{aligned}$$

Summary:

$$i_o = 50e^{-50t} \mu\text{A} \quad 0 \leq t \leq 0.1 \text{ s}$$

$$i_o = 50e^{-50t} - 100e^{-50(t-0.1)} \mu\text{A} \quad 0.1 \text{ s} \leq t \leq 0.2 \text{ s}$$

$$i_o = 50e^{-50t} - 100e^{-50(t-0.1)} + 50e^{-50(t-0.2)} \mu\text{A} \quad 0.2 \text{ s} \leq t \leq \infty$$

**[c]** At  $t = 0.1^-$ :

$$v_o = 5(1 - e^{-5}) = 4.97 \text{ V}; \quad i_{100\text{k}\Omega} = \frac{4.97}{0.1} = 49.66 \mu\text{A}; \quad i_g = 50 \mu\text{A}$$

$$\therefore i_o = 50 - 49.66 = 0.34 \mu\text{A}$$

From the solution for  $i_o$  we have  $i_o(0.1^-) = 50e^{-5} = 0.34 \mu\text{A}$  (Checks)

At  $t = 0.1^+$ :

$$v_o(0.1^+) = v_o(0.1^-) = 4.97 \mu\text{V}; \quad i_{100\text{k}\Omega} = 49.66 \mu\text{A}; \quad i_g = -50 \mu\text{A}$$

$$\therefore i_o(0.1^+) = -(50 + 49.66) = -99.66 \mu\text{A}$$

From the solution for  $i_o$  we have

$$i_o(0.1^+) = 50e^{-5} - 100 = -99.66 \mu\text{A} \quad (\text{Checks})$$

At  $t = 0.2^-$ :

$$v_o = 10e^{-5} - 5e^{-10} - 5 = -4.93 \mu\text{V}$$

$$i_{100\text{k}\Omega} = -49.33 \mu\text{A} \quad i_g = -50 \mu\text{A}$$

$$i_o = i_g - i_{100\text{k}\Omega} = -50 + 49.33 = -0.67 \mu\text{A}$$

From the solution for  $i_o$ ,  $i_o(0.2^-) = 50e^{-10} - 100e^{-5} = -0.67 \mu\text{A}$  (Checks)

At  $t = 0.2^+$ :

$$v_o(0.2^+) = i_o(0.2^-) = -4.93 \text{ V}; \quad i_{100\text{k}\Omega} = -49.33 \mu\text{A}; \quad i_g = 0$$

$$i_o = i_g - i_{100\text{k}\Omega} = 49.33 \mu\text{A}$$

From the solution for  $i_o$ ,

$$i_o(0.2^+) = 50e^{-10} - 100e^{-5} + 50 = 49.33 \mu\text{A} \text{ (Checks)}$$

P 13.67  $H(s) = \frac{V_o}{V_i} = \frac{5}{5 + 2.5s} = \frac{2}{s + 2}$

$$h(\lambda) = 2e^{-2\lambda}; \quad h(t - \lambda) = 2e^{-2(t-\lambda)} = 2e^{-2t}e^{2\lambda}$$

$$\frac{T}{2} = \frac{\pi}{2}; \quad T = \pi \text{ s}; \quad f = \frac{1}{\pi} \text{ Hz}$$

$$v_i(\lambda) = (20 \sin 2\lambda)[u(\lambda) - u(\lambda - \pi/2)]$$


$$(\pi/2) \text{ s} \leq t \leq \infty:$$

$$v_o = \int_0^{\pi/2} (2e^{-2t}e^{2\lambda})(20 \sin 2\lambda) d\lambda = 40e^{-2t} \int_0^{\pi/2} e^{2\lambda} \sin 2\lambda d\lambda$$

$$= 40e^{-2t} \left[ \frac{e^{2\lambda}}{8} (2 \sin 2\lambda - 2 \cos 2\lambda) \right]_0^{\pi/2} = 10e^{-2t} [e^{\pi} (\sin \pi - \cos \pi) - 1(0 - 1)]$$

$$= 10e^{-2t} (e^{\pi} + 1) = 10(e^{\pi} + 1)e^{-2t} \text{ V}$$
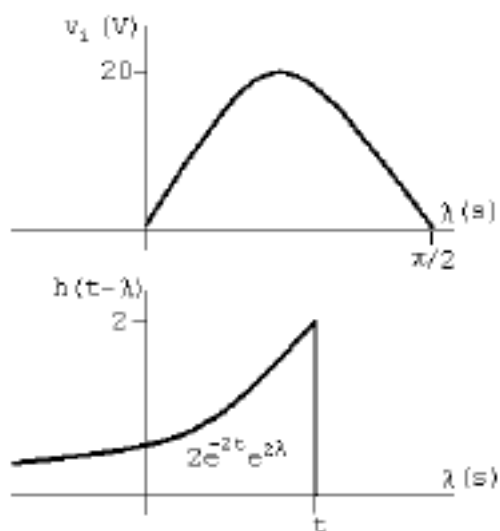
$$v_o(2.2) = 241.41e^{-4.4} = 2.96 \text{ V}$$




P 13.68 [a]  $V_o = \frac{16}{20}V_g$

$$\therefore H(s) = \frac{V_o}{V_g} = \frac{4}{5}$$


$$h(\lambda) = 0.8\delta(\lambda)$$

[b]

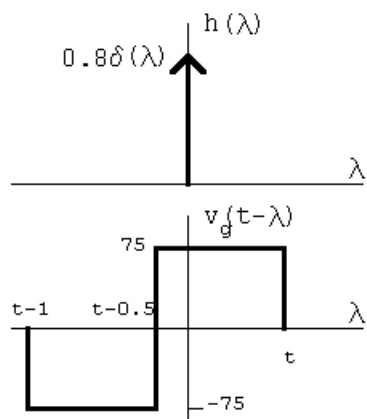

$$0 < t < 0.5 \text{ s} : \quad v_o = \int_0^t 75[0.8\delta(\lambda)] d\lambda = 60 \text{ A}$$

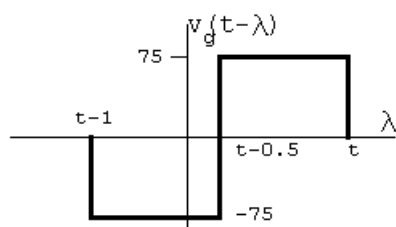
$$0.5 \text{ s} \leq t \leq 1.0 \text{ s}:$$



$$v_o = \int_0^{t-0.5} -75[0.8\delta(\lambda)] d\lambda = -60 \text{ A}$$


$$1 \text{ s} < t < \infty : \quad v_o = 0$$

**[c]**

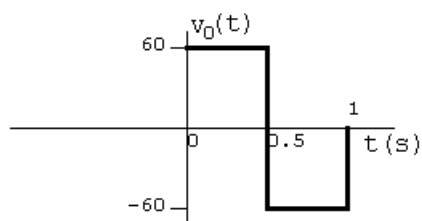

Yes, because the circuit has no memory.


P 13.69 **[a]**

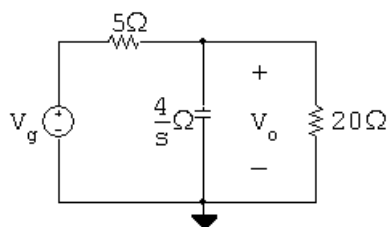

$$\frac{V_o - V_g}{5} + \frac{V_o s}{4} + \frac{V_o}{20} = 0$$

$$(5s + 5)V_o = 4V_g$$

$$H(s) = \frac{V_o}{V_g} = \frac{0.8}{s+1}; \quad h(\lambda) = 0.8e^{-\lambda}u(\lambda)$$

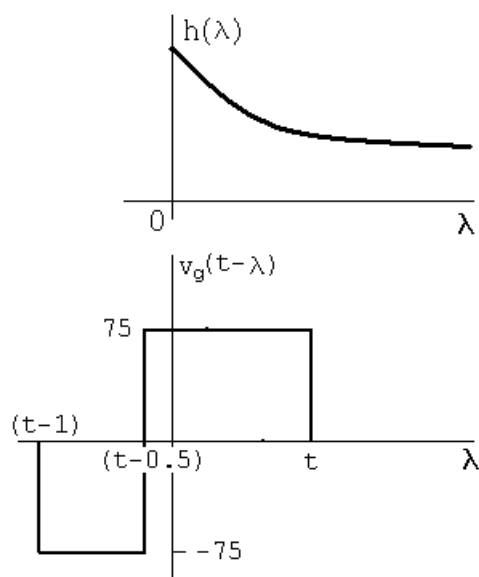
**[b]**

$$0 \leq t \leq 0.5 \text{ s};$$

$$v_o = \int_0^t 75(0.8e^{-\lambda}) d\lambda = 60 \frac{e^{-\lambda}}{-1} \Big|_0^t$$

$$v_o = 60 - 60e^{-t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$
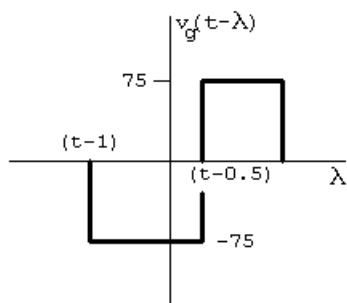
$$0.5 \text{ s} \leq t \leq 1 \text{ s};$$



$$v_o = \int_0^{t-0.5} (-75)(0.8e^{-\lambda}) d\lambda + \int_{t-0.5}^t 75(0.8e^{-\lambda}) d\lambda$$


$$= -60 \frac{e^{-\lambda}}{-1} \Big|_0^{t-0.5} + 60 \frac{e^{-\lambda}}{-1} \Big|_{t-0.5}^t$$

$$= 120e^{-(t-0.5)} - 60e^{-t} - 60 \text{ V}, \quad 0.5 \text{ s} \leq t \leq 1 \text{ s}$$

$$1 \text{ s} \leq t \leq \infty;$$


$$\begin{aligned} v_o &= \int_{t-1}^{t-0.5} (-75)(0.8e^{-\lambda}) d\lambda + \int_{t-0.5}^t 75(0.8e^{-\lambda}) d\lambda \\ &= -60 \frac{e^{-\lambda}}{-1} \Big|_{t-1}^{t-0.5} + 60 \frac{e^{-\lambda}}{-1} \Big|_{t-0.5}^t \\ &= 120e^{-(t-0.5)} - 60e^{-(t-1)} - 60e^{-t} \text{ V}, \quad 1 \text{ s} \leq t \leq \infty \end{aligned}$$

[c]

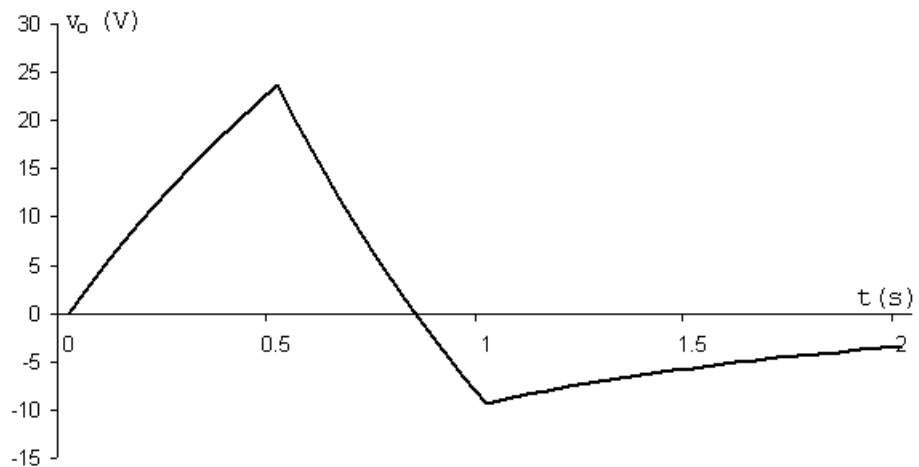

[d] No, the circuit has memory because of the capacitive storage element.

P 13.70

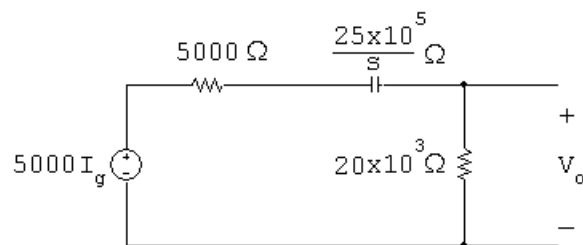

$$V_o = \frac{20 \times 10^3}{5000 + 25 \times 10^5/s + 20 \times 10^3} (5000 I_g)$$

$$\frac{V_o}{I_g} = H(s) = \frac{4000s}{s + 100}$$

$$H(s) = 4000 \left[ 1 - \frac{100}{s + 100} \right] = 4000 - \frac{4 \times 10^5}{s + 100}$$

$$h(\lambda) = 4000\delta(\lambda) - 400,000e^{-100\lambda}u(\lambda)$$



$$\begin{aligned}
v_o &= \int_0^{10^{-3}} (-20 \times 10^{-3}) [4000\delta(\lambda) - 400,000e^{-100\lambda}] d\lambda \\
&\quad + \int_{10^{-3}}^{5 \times 10^{-3}} (10 \times 10^{-3}) [-400,000e^{-100\lambda}] d\lambda \\
&= -80 + 8000 \int_0^{10^{-3}} e^{-100\lambda} d\lambda - \int_{10^{-3}}^{5 \times 10^{-3}} 4000e^{-100\lambda} d\lambda \\
&= -80 - 80(e^{-0.1} - 1) + 40(e^{-0.5} - e^{-0.1}) \\
v_o(5 \times 10^{-3}) &= 40e^{-0.5} - 120e^{-0.1} = 24.26 - 108.58 = -84.32 \text{ V}
\end{aligned}$$

Alternate solution (not using the convolution integral):

$$\begin{aligned}
I_g &= \int_0^{4 \times 10^{-3}} (10 \times 10^{-3}) e^{-st} dt + \int_{4 \times 10^{-3}}^{6 \times 10^{-3}} (-20 \times 10^{-3}) e^{-st} dt \\
&= 10^{-3} \frac{e^{-st}}{-s} \Big|_0^{4 \times 10^{-3}} - 20 \times 10^{-3} \frac{e^{-st}}{-s} \Big|_{4 \times 10^{-3}}^{6 \times 10^{-3}} \\
&= 10 \times 10^{-3} \left[ \frac{1}{s} - \frac{e^{-4 \times 10^{-3}s}}{s} \right] + 20 \times 10^{-3} \left[ \frac{e^{-6 \times 10^{-3}s} - e^{-4 \times 10^{-3}s}}{s} \right] \\
&= \frac{10 \times 10^{-3}}{s} - \frac{30 \times 10^{-3}}{s} e^{-4 \times 10^{-3}s} + \frac{20 \times 10^{-3}}{s} e^{-6 \times 10^{-3}s}
\end{aligned}$$

$$V_o = I_g H(s) = \frac{40}{s + 100} - \frac{120e^{-4 \times 10^{-3}s}}{s + 100} + \frac{80e^{-6 \times 10^{-3}s}}{s + 100}$$

Now use the operational transform  $\mathcal{L}^{-1}\{e^{-as}F(s)\} = f(t-a)u(t-a)$ :


$$\begin{aligned}
v_o &= 40e^{-100t} - 120e^{-100(t-4 \times 10^{-3})}u(t-4 \times 10^{-3}) \\
&\quad + 80e^{-100(t-6 \times 10^{-3})}u(t-6 \times 10^{-3}) \text{ V}
\end{aligned}$$

$$v_o(5 \times 10^{-3}) = 40e^{-0.5} - 120e^{-0.1} + 80(0) = -84.32 \text{ V (Checks)}$$

P 13.71 [a]  $H(s) = \frac{V_o}{V_i} = \frac{1/LC}{s^2 + (R/L)s + (1/LC)}$

$$= \frac{100}{s^2 + 20s + 100} = \frac{100}{(s+10)^2}$$
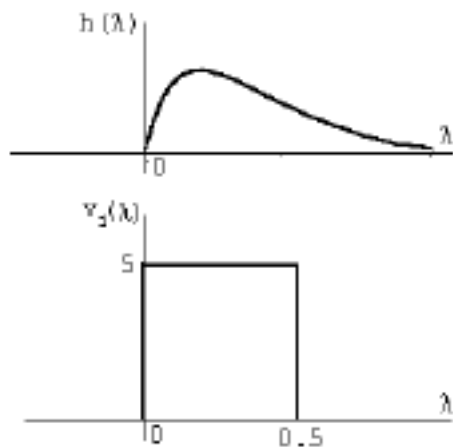
$$h(\lambda) = 100\lambda e^{-10\lambda}u(\lambda)$$




$$0 \leq t \leq 0.5:$$

$$\begin{aligned} v_o &= 500 \int_0^t \lambda e^{-10\lambda} d\lambda \\ &= 500 \left\{ \frac{e^{-10\lambda}}{100} (-10\lambda - 1) \right\} \Big|_0^t \\ &= 5[1 - e^{-10t}(10t + 1)] \end{aligned}$$

$$0.5 \leq t \leq \infty:$$

$$\begin{aligned} v_o &= 500 \int_{t-0.5}^t \lambda e^{-10\lambda} d\lambda \\ &= 500 \left\{ \frac{e^{-10\lambda}}{100} (-10\lambda - 1) \right\} \Big|_{t-0.5}^t \\ &= 5e^{-10t}[e^5(10t - 4) - 10t - 1] \end{aligned}$$

**[b]**

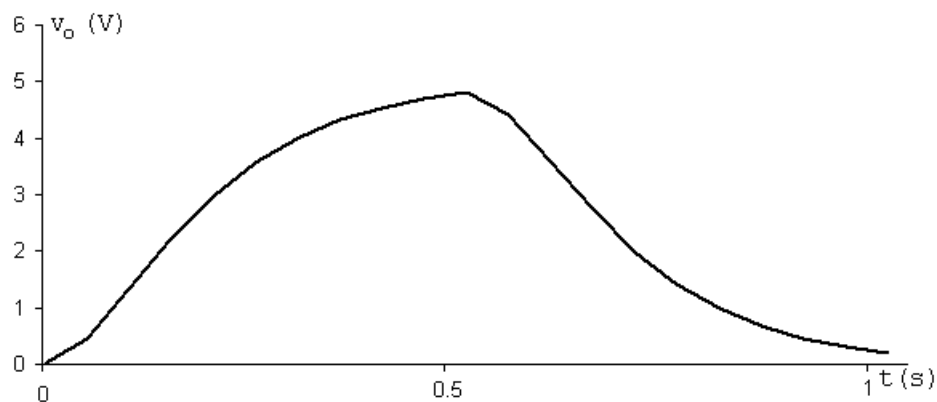

$$\text{P 13.72} \quad H(s) = \frac{16s}{40 + 4s + 16s} = \frac{0.8s}{s + 2} = 0.8 \left( 1 - \frac{2}{s + 2} \right) = 0.8 - \frac{1.6}{s + 2}$$

$$h(\lambda) = 0.8\delta(\lambda) - 1.6e^{-2\lambda}u(\lambda)$$

$$v_o = \int_0^t 75[0.8\delta(\lambda) - 1.6e^{-2\lambda}] d\lambda = \int_0^t 60\delta(\lambda) d\lambda - 120 \int_0^t e^{-2\lambda} d\lambda$$

$$= 60 - 120 \frac{e^{-2\lambda}}{-2} \Big|_0^t = 60 + 60(e^{-2t} - 1)$$

$$= 60e^{-2t}u(t) \text{ V}$$

$$\text{P 13.73} \quad [\mathbf{a}] \quad Y(s) = \int_0^\infty y(t)e^{-st} dt$$

$$Y(s) = \int_0^\infty e^{-st} \left[ \int_0^\infty h(\lambda)x(t - \lambda) d\lambda \right] dt$$

$$= \int_0^\infty \int_0^\infty e^{-st} h(\lambda)x(t - \lambda) d\lambda dt$$

$$= \int_0^\infty h(\lambda) \int_0^\infty e^{-st} x(t - \lambda) dt d\lambda$$

But  $x(t - \lambda) = 0$  when  $t < \lambda$

$$\text{Therefore} \quad Y(s) = \int_0^\infty h(\lambda) \int_\lambda^\infty e^{-st} x(t - \lambda) dt d\lambda$$

Let  $u = t - \lambda$ ;  $du = dt$ ;  $u = 0$ ,  $t = \lambda$ ;  $u = \infty$ ,  $t = \infty$

$$Y(s) = \int_0^\infty h(\lambda) \int_0^\infty e^{-s(u+\lambda)} x(u) du d\lambda$$


$$= \int_0^\infty h(\lambda) e^{-s\lambda} \int_0^\infty e^{-su} x(u) du d\lambda$$

$$= \int_0^\infty h(\lambda) e^{-s\lambda} X(s) d\lambda = H(s) X(s)$$

We are using one-sided Laplace transforms; therefore  $h(t)$  and  $X(t)$  are assumed zero for  $t < 0$ .

$$\text{[b]} \quad F(s) = \frac{a}{s(s+a)^2} = \frac{1}{s} \cdot \frac{a}{(s+a)^2} = H(s)X(s)$$
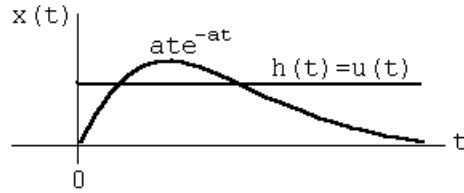
$$\therefore h(t) = u(t), \quad x(t) = ate^{-at}u(t)$$



$$\begin{aligned} \therefore f(t) &= \int_0^t (1)a\lambda e^{-a\lambda} d\lambda = a \left[ \frac{e^{-a\lambda}}{a^2} (-a\lambda - 1) \right] \bigg|_0^t \\ &= \frac{1}{a} [e^{-at}(-at - 1) - 1(-1)] = \frac{1}{a} [1 - e^{-at} - ate^{-at}] \\ &= \left[ \frac{1}{a} - \frac{1}{a}e^{-at} - te^{-at} \right] u(t) \end{aligned}$$


Check:

$$F(s) = \frac{a}{s(s+a)^2} = \frac{K_0}{s} + \frac{K_1}{(s+a)^2} + \frac{K_2}{s+a}$$

$$K_0 = \frac{1}{a}; \quad K_1 = -1; \quad K_2 = \frac{d}{ds} \left( \frac{a}{s} \right)_{s=-a} = -\frac{1}{a}$$

$$f(t) = \left[ \frac{1}{a} - te^{-at} - \frac{1}{a}e^{-at} \right] u(t)$$

P 13.74 [a] The  $s$ -domain circuit is

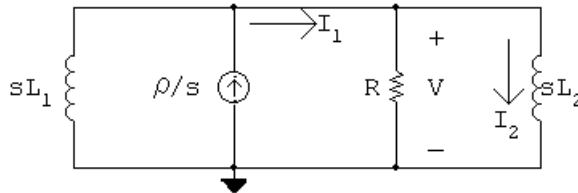

$$\text{The node-voltage equation is } \frac{V}{sL_1} + \frac{V}{R} + \frac{V}{sL_2} = \frac{\rho}{s}$$

$$\text{Therefore } V = \frac{\rho R}{s + (R/L_e)} \quad \text{where } L_e = \frac{L_1 L_2}{L_1 + L_2}$$

$$\text{Therefore } v = \rho R e^{-(R/L_e)t} u(t) \text{ V}$$

$$\textbf{[b]} \quad I_1 = \frac{V}{R} + \frac{V}{sL_2} = \frac{\rho[s + (R/L_2)]}{s[s + (R/L_e)]} = \frac{K_0}{s} + \frac{K_1}{s + (R/L_e)}$$

$$K_0 = \frac{\rho L_1}{L_1 + L_2}; \quad K_1 = \frac{\rho L_2}{L_1 + L_2}$$

$$\text{Thus we have} \quad i_1 = \frac{\rho}{L_1 + L_2} [L_1 + L_2 e^{-(R/L_e)t}] u(t) \quad \mathbf{A}$$

$$\textbf{[c]} \quad I_2 = \frac{V}{sL_2} = \frac{(\rho R/L_2)}{s[s + (R/L_e)]} = \frac{K_2}{s} + \frac{K_3}{s + (R/L_e)}$$

$$K_2 = \frac{\rho L_1}{L_1 + L_2}; \quad K_3 = \frac{-\rho L_1}{L_1 + L_2}$$

$$\text{Therefore} \quad i_2 = \frac{\rho L_1}{L_1 + L_2} [1 - e^{-(R/L_e)t}] u(t)$$


$$\textbf{[d]} \quad \lambda(t) = L_1 i_1 + L_2 i_2 = \rho L_1$$

P 13.75 **[a]** As  $R \rightarrow \infty$ ,  $v(t) \rightarrow \rho L_e \delta(t)$  since the area under the impulse generating function is  $\rho L_e$ .

$$i_1(t) \rightarrow \frac{\rho L_1}{L_1 + L_2} \quad \text{as} \quad R \rightarrow \infty$$

$$i_2(t) \rightarrow \frac{\rho L_1}{L_1 + L_2} \quad \text{as} \quad R \rightarrow \infty$$

**[b]** The  $s$ -domain circuit is

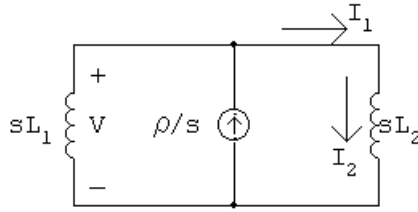

$$\frac{V}{sL_1} + \frac{V}{sL_2} = \frac{\rho}{s}; \quad \text{therefore} \quad V = \frac{\rho L_1 L_2}{L_1 + L_2} = \rho L_e$$

$$\text{Therefore} \quad v(t) = \rho L_e \delta(t)$$

$$I_1 = I_2 = \frac{V}{sL_2} = \left( \frac{\rho L_1}{L_1 + L_2} \right) \left( \frac{1}{s} \right)$$

$$\text{Therefore} \quad i_1 = i_2 = \frac{\rho L_1}{L_1 + L_2} u(t) \text{ A}$$

$$\text{P 13.76} \quad H(j3) = \frac{4(3 + j3)}{-9 + j24 + 41} = 0.42 \angle 8.13^\circ$$

$$\therefore v_o(t) = 16.97 \cos(3t + 8.13^\circ) \text{ V}$$

$$\text{P 13.77} \quad \textbf{[a]} \quad H(s) = \frac{-Z_f}{Z_i}$$

$$Z_f = \frac{(1/C_f)}{s + (1/R_f C_f)} = \frac{10^8}{s + 1000}$$


$$Z_i = \frac{R_i[s + (1/R_i C_i)]}{s} = \frac{10,000(s + 400)}{s}$$

$$H(s) = \frac{-10^4 s}{(s + 400)(s + 1000)}$$

$$\textbf{[b]} \quad H(j400) = \frac{-10^4(j400)}{(400 + j400)(1000 + j400)} = 6.565 \angle -156.8^\circ$$

$$v_o(t) = 13.13 \cos(400t - 156.8^\circ) \text{ V}$$

P 13.78 [a]

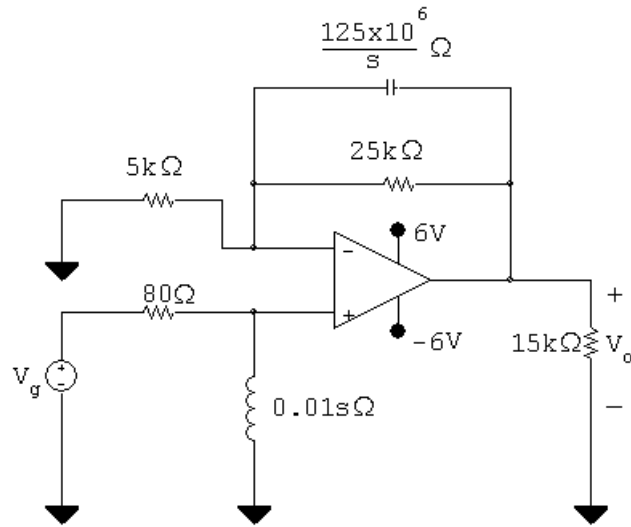

$$V_p = \frac{0.01s}{80 + 0.01s} V_g = \frac{s}{s + 8000} V_g$$

$$\frac{V_n}{5000} + \frac{V_n - V_o}{25,000} + (V_n - V_o)8 \times 10^{-9}s = 0$$

$$5V_n + V_n - V_o + (V_n - V_o)2 \times 10^{-4}s = 0$$

$$6V_n + 2 \times 10^{-4}sV_n = V_o + 2 \times 10^{-4}sV_o$$

$$2 \times 10^{-4}V_n(s + 30,000) = 2 \times 10^{-4}V_o(s + 5000)$$

$$V_n = V_p$$

$$V_o = \frac{s + 30,000}{s + 5000} V_f = \left( \frac{s + 30,000}{s + 5000} \right) \left( \frac{sV_g}{s + 8000} \right)$$

$$H(s) = \frac{V_o}{V_g} = \frac{s(s + 30,000)}{(s + 5000)(s + 8000)}$$

**[b]**  $v_g = 0.6u(t); \quad V_g = \frac{0.6}{s}$

$$V_o = \frac{0.6(s + 30,000)}{(s + 5000)(s + 8000)} = \frac{K_1}{s + 5000} + \frac{K_2}{s + 8000}$$

$$K_1 = \frac{0.6(25,000)}{3000} = 5; \quad K_2 = \frac{0.6(22,000)}{-3000} = -4.4$$

$$\therefore v_o(t) = (5e^{-5000t} - 4.4e^{-8000t})u(t) \text{ V}$$

**[c]**  $V_g = 2 \cos 10,000t \text{ V}$

$$H(j\omega) = \frac{j10,000(30,000 + j10,000)}{(5000 + j10,000)(8000 + j10,000)} = 2.21 \angle -6.34^\circ$$

$$\therefore v_o = 4.42 \cos(10,000t - 6.34^\circ) \text{ V}$$

$$\text{P 13.79 } V_o = \frac{50}{s + 8000} - \frac{20}{s + 5000} = \frac{30(s + 3000)}{(s + 5000)(s + 8000)}$$

$$V_o = H(s)V_g = H(s)\left(\frac{30}{s}\right)$$

$$\therefore H(s) = \frac{s(s + 3000)}{(s + 5000)(s + 8000)}$$

$$H(j6000) = \frac{(j6000)(3000 + j6000)}{(5000 + j6000)(8000 + j6000)} = 0.52 \angle 66.37^\circ$$

$$\therefore v_o(t) = 61.84 \cos(6000t + 66.37^\circ) \text{ V}$$

$$\text{P 13.80 } \text{Original charge on } C_1; \quad q_1 = V_0 C_1$$

$$\text{The charge transferred to } C_2; \quad q_2 = V_0 C_e = \frac{V_0 C_1 C_2}{C_1 + C_2}$$

$$\text{The charge remaining on } C_1; \quad q'_1 = q_1 - q_2 = \frac{V_0 C_1^2}{C_1 + C_2}$$

$$\text{Therefore } V_2 = \frac{q_2}{C_2} = \frac{V_0 C_1}{C_1 + C_2} \quad \text{and} \quad V_1 = \frac{q'_1}{C_1} = \frac{V_0 C_1}{C_1 + C_2}$$

$$\text{P 13.81 [a] } Z_1 = \frac{1/C_1}{s + 1/R_1 C_1} = \frac{25 \times 10^{10}}{s + 20 \times 10^4} \Omega$$

$$Z_2 = \frac{1/C_2}{s + 1/R_2 C_2} = \frac{6.25 \times 10^{10}}{s + 12,500} \Omega$$

$$\frac{V_o}{Z_2} + \frac{V_o - 10/s}{Z_1} = 0$$

$$\frac{V_o(s + 12,500)}{6.25 \times 10^{10}} + \frac{V_o(s + 20 \times 10^4)}{25 \times 10^{10}} = \frac{10}{s} \frac{(s + 20 \times 10^4)}{25 \times 10^{10}}$$

$$V_o = \frac{2(s + 200,000)}{s(s + 50,000)} = \frac{K_1}{s} + \frac{K_2}{s + 50,000}$$

$$K_1 = \frac{2(200,000)}{50,000} = 8$$

$$K_2 = \frac{2(150,000)}{-50,000} = -6$$

$$\therefore v_o = [8 - 6e^{-50,000t}]u(t) \text{ V}$$



$$\begin{aligned}
 \text{[b]} \quad I_0 &= \frac{V_0}{Z_2} = \frac{2(s + 200,000)(s + 12,500)}{s(s + 50,000)6.25 \times 10^{10}} \\
 &= 32 \times 10^{-12} \left[ 1 + \frac{162,500s + 25 \times 10^8}{s(s + 50,000)} \right] \\
 &= 32 \times 10^{-12} \left[ 1 + \frac{K_1}{s} + \frac{K_2}{s + 50,000} \right]
 \end{aligned}$$

$$K_1 = 50,000; \quad K_2 = 112,500$$

$$i_o = 32\delta(t) + [1.6 \times 10^6 + 3.6 \times 10^6 e^{-50,000t}]u(t) \text{ pA}$$

$$\text{[c]} \text{ When } C_1 = 64 \text{ pF}$$

$$Z_1 = \frac{156.25 \times 10^8}{s + 12,500} \Omega$$

$$\frac{V_0(s + 12,500)}{625 \times 10^8} + \frac{V_0(s + 12,500)}{156.25 \times 10^8} = \frac{10}{s} \frac{(s + 12,500)}{156.25 \times 10^8}$$

$$\therefore V_0 + 4V_0 = \frac{40}{s}$$

$$V_0 = \frac{8}{s}$$

$$v_o = 8u(t) \text{ V}$$

$$I_0 = \frac{V_0}{Z_2} = \frac{8}{s} \frac{(s + 12,500)}{6.25 \times 10^{10}} = 128 \times 10^{-12} \left[ 1 + \frac{12,500}{s} \right]$$

$$i_o(t) = 128\delta(t) + 1.6 \times 10^{-6}u(t) \text{ pA}$$

$$\text{P 13.82 Let } a = \frac{1}{R_1 C_1} = \frac{1}{R_2 C_2}$$

$$\text{Then } Z_1 = \frac{1}{C_1(s + a)} \quad \text{and} \quad Z_2 = \frac{1}{C_2(s + a)}$$

$$\frac{V_o}{Z_2} + \frac{V_o}{Z_1} = \frac{10/s}{Z_1}$$

$$V_o C_2(s + a) + V_o C_1(s + a) = (10/s)C_1(s + a)$$

$$V_o = \frac{10}{s} \left( \frac{C_1}{C_1 + C_2} \right)$$

$$\text{Thus, } v_o \text{ is the input scaled by the factor } \frac{C_1}{C_1 + C_2}.$$

P 13.83 [a] For  $t < 0$ ,  $0.5v_1 = 2v_2$ ; therefore  $v_1 = 4v_2$

$$v_1 + v_2 = 100; \quad \text{therefore } v_1(0^-) = 80 \text{ V}$$


[b]  $v_2(0^-) = 20 \text{ V}$

[c]  $v_3(0^-) = 0 \text{ V}$

[d] For  $t > 0$ :

$$I = \frac{100/s}{3.125/s} \times 10^{-6} = 32 \times 10^{-6}$$

$$i(t) = 32\delta(t) \mu\text{A}$$

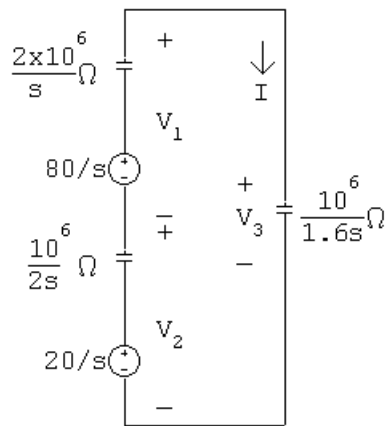

[e]  $v_1(0^+) = -\frac{10^6}{0.5} \int_{0^-}^{0^+} 32 \times 10^{-6} \delta(t) dt + 80 = -64 + 80 = 16 \text{ V}$


[f]  $v_2(0^+) = -\frac{10^6}{2} \int_{0^-}^{0^+} 32 \times 10^{-6} \delta(t) dt + 20 = -16 + 20 = 4 \text{ V}$

[g]  $V_3 = \frac{0.625 \times 10^6}{s} \cdot 32 \times 10^{-6} = \frac{20}{s}$

$$v_3(t) = 20u(t) \text{ V}; \quad v_3(0^+) = 20 \text{ V}$$

Check:  $v_1(0^+) + v_2(0^+) = v_3(0^+)$

P 13.84 [a] For  $t < 0$ :

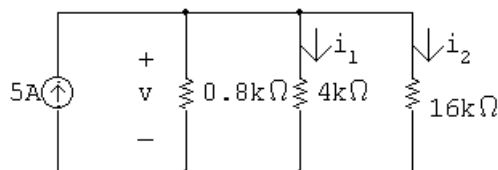

$$R_{\text{eq}} = 0.8 \text{ k}\Omega \parallel 4 \text{ k}\Omega \parallel 16 \text{ k}\Omega = 0.64 \text{ k}\Omega; \quad v = 5(640) = 3200 \text{ V}$$

$$i_1(0^-) = \frac{3200}{4000} = 0.8 \text{ A}; \quad i_2(0^-) = \frac{3200}{16,000} = 0.2 \text{ A}$$

**[b]** For  $t > 0$ :

$$i_1 + i_2 = 0$$

$$8(\Delta i_1) = 2(\Delta i_2)$$


$$i_1(0^-) + \Delta i_1 + i_2(0^-) + \Delta i_2 = 0; \quad \text{therefore} \quad \Delta i_1 = -0.2 \text{ A}$$

$$\Delta i_2 = -0.8 \text{ A}; \quad i_1(0^+) = 0.8 - 0.2 = 0.6 \text{ A}$$

**[c]**  $i_2(0^-) = 0.2 \text{ A}$

**[d]**  $i_2(0^+) = 0.2 - 0.8 = -0.6 \text{ A}$

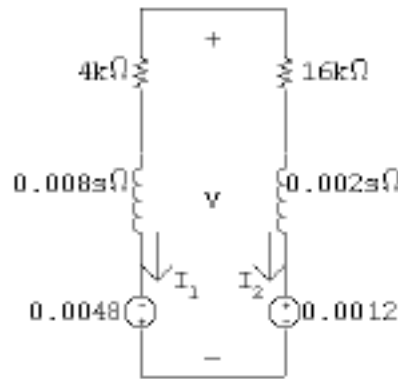**[e]** The  $s$ -domain equivalent circuit for  $t > 0$  is



$$I_1 = \frac{0.006}{0.01s + 20,000} = \frac{0.6}{s + 2 \times 10^6}$$

$$i_1(t) = 0.6e^{-2 \times 10^6 t} u(t) \text{ A}$$


**[f]**  $i_2(t) = -i_1(t) = -0.6e^{-2 \times 10^6 t} u(t) \text{ A}$

$$\textbf{[g]} \quad V = -0.0064 + (0.008s + 4000)I_1 = \frac{-0.0016(s + 6.5 \times 10^6)}{s + 2 \times 10^6}$$

$$= -1.6 \times 10^{-3} - \frac{7200}{s + 2 \times 10^6}$$

$$v(t) = [-1.6 \times 10^{-3} \delta(t)] - [7200e^{-2 \times 10^6 t} u(t)] \text{ V}$$

P 13.85 **[a]**

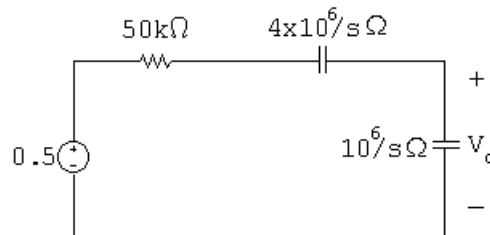

$$V_o = \frac{0.5}{50,000 + 5 \times 10^6/s} \cdot \frac{10^6}{s}$$

$$\frac{500,000}{50,000s + 5 \times 10^6} = \frac{10}{s + 100}$$

$$v_o = 10e^{-100t}u(t) \text{ V}$$

**[b]** At  $t = 0$  the current in the  $1 \mu\text{F}$  capacitor is  $10\delta(t) \mu\text{A}$

$$\therefore v_o(0^+) = 10^6 \int_{0^-}^{0^+} 10 \times 10^{-6} \delta(t) dt = 10 \text{ V}$$


After the impulsive current has charged the  $1 \mu\text{F}$  capacitor to 10 V it discharges through the  $50 \text{ k}\Omega$  resistor.

$$C_e = \frac{C_1 C_2}{C_1 + C_2} = \frac{0.25}{1.25} = 0.2 \mu\text{F}$$

$$\tau = (50,000)(0.2 \times 10^{-6}) = 10^{-2}$$

$$\frac{1}{\tau} = 100 \text{ (Checks)}$$

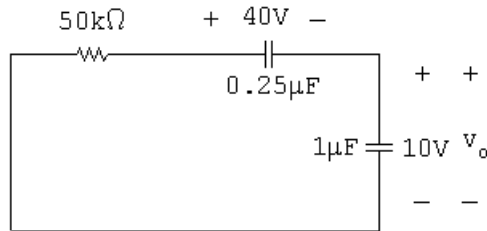
Note – after the impulsive current passes the circuit becomes



The solution for  $v_o$  in this circuit is also

$$v_o = 10e^{-100t}u(t) \text{ V}$$

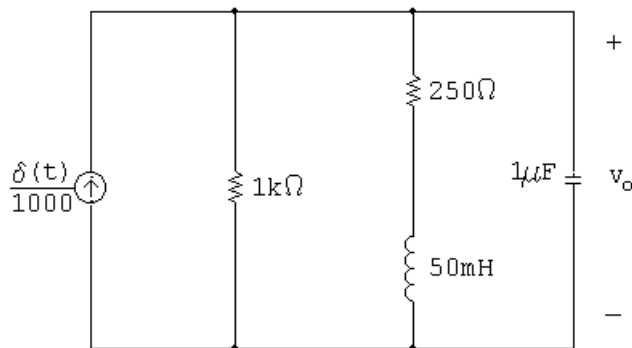P 13.86 **[a]** After making a source transformation, the circuit is as shown. The impulse current will pass through the capacitive branch since it appears as a short circuit to the impulsive current,



$$\text{Therefore } v_o(0^+) = 10^6 \int_{0^-}^{0^+} \left[ \frac{\delta(t)}{1000} \right] dt = 1000 \text{ V}$$

Therefore  $w_C = (0.5)Cv^2 = 0.5 \text{ J}$


**[b]**  $i_L(0^+) = 0$ ; therefore  $w_L = 0 \text{ J}$

**[c]**  $V_o(10^{-6})s + \frac{V_o}{250 + 0.05s} + \frac{V_o}{1000} = 10^{-3}$

Therefore

$$\begin{aligned} V_o &= \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6} \\ &= \frac{K_1}{s + 3000 - j4000} + \frac{K_1^*}{s + 3000 + j4000} \\ K_1 &= 559.02 \angle -26.57^\circ; \quad K_1^* = 559.02 \angle 26.57^\circ \\ v_o &= [1118.03e^{-3000t} \cos(4000t - 26.57^\circ)]u(t) \text{ V} \end{aligned}$$


**[d]** The  $s$ -domain circuit is

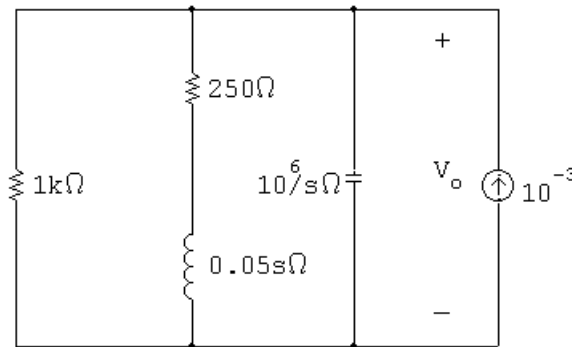

$$\frac{V_o s}{10^6} + \frac{V_o}{250 + 0.05s} + \frac{V_o}{1000} = 10^{-3}$$

Note that this equation is identical to that derived in part [c], therefore the solution for  $V_o$  will be the same.

P 13.87 **[a]**

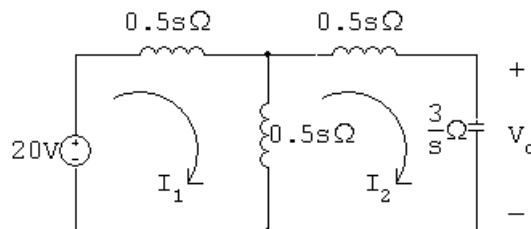

$$20 = sI_1 - 0.5sI_2$$

$$0 = -0.5sI_1 + \left(s + \frac{3}{s}\right)I_2$$

$$\Delta = \begin{vmatrix} s & -0.5s \\ -0.5s & (s + 3/s) \end{vmatrix} = s^2 + 3 - 0.25s^2 = 0.75(s^2 + 4)$$

$$N_1 = \begin{vmatrix} 20 & -0.5s \\ 0 & (s + 3/s) \end{vmatrix} = 20s + \frac{60}{s} = \frac{20s^2 + 60}{s} = \frac{20(s^2 + 3)}{s}$$

$$\begin{aligned} I_1 &= \frac{N_1}{\Delta} = \frac{20(s^2 + 3)}{s(0.75)(s^2 + 4)} = \frac{80}{3} \cdot \frac{s^2 + 3}{s(s^2 + 4)} \\ &= \frac{K_0}{s} + \frac{K_1}{s - j2} + \frac{K_1^*}{s + j2} \end{aligned}$$

$$K_0 = \frac{80}{3} \left( \frac{3}{4} \right) = 20; \quad K_1 = \frac{80}{3} \left[ \frac{-4 + 3}{(j2)(j4)} \right] = \frac{10}{3} \angle 0^\circ$$

$$\therefore i_1 = \left[ 20 + \frac{20}{3} \cos 2t \right] u(t) \text{ A}$$

$$\text{[b]} \quad N_2 = \begin{vmatrix} s & 20 \\ -0.5s & 0 \end{vmatrix} = 10s$$

$$I_2 = \frac{N_2}{\Delta} = \frac{10s}{0.75(s^2 + 4)} = \frac{40}{3} \left( \frac{s}{s^2 + 4} \right) = \frac{K_1}{s - j2} + \frac{K_1^*}{s + j2}$$

$$K_1 = \frac{40}{3} \left( \frac{j2}{j4} \right) = \frac{20}{3} \angle 0^\circ$$

$$i_2 = \frac{40}{3} (\cos 2t) u(t) \text{ A}$$

$$\text{[c]} \quad V_0 = \frac{3}{s} I_2 = \left( \frac{3}{s} \right) \frac{40}{3} \left( \frac{s}{s^2 + 4} \right) = \frac{40}{s^2 + 4} = \frac{K_1}{s - j2} = \frac{K_1^*}{s + j2}$$

$$K_1 = \frac{40}{j4} = -j10 = 10 \angle 90^\circ$$

$$v_o = 20 \cos(2t - 90^\circ) = 20 \sin 2t$$

$$v_o = [20 \sin 2t] u(t) \text{ V}$$

**[d]** Let us begin by noting  $i_1$  jumps from 0 to  $(80/3)$  A between  $0^-$  and  $0^+$  and in this same interval  $i_2$  jumps from 0 to  $(40/3)$  A. Therefore in the derivatives of  $i_1$  and  $i_2$  there will be impulses of  $(80/3)\delta(t)$  and  $(40/3)\delta(t)$ , respectively.

Thus

$$\frac{di_1}{dt} = \frac{80}{3} \delta(t) - \frac{40}{3} \sin 2t \text{ A/s}$$

$$\frac{di_2}{dt} = \frac{40}{3}\delta(t) - \frac{80}{3}\sin 2t \text{ A/s}$$

From the circuit diagram we have

$$\begin{aligned} 20\delta(t) &= 1\frac{di_1}{dt} - 0.5\frac{di_2}{dt} \\ &= \frac{80}{3}\delta(t) - \frac{40}{3}\sin 2t - \frac{20\delta(t)}{3} + \frac{40}{3}\sin 2t \\ &= 20\delta(t) \end{aligned}$$


Thus our solutions for  $i_1$  and  $i_2$  are in agreement with known circuit behavior. Let us also note the impulsive voltage will impart energy into the circuit. Since there is no resistance in the circuit, the energy will not dissipate. Thus the fact that  $i_1$ ,  $i_2$ , and  $v_o$  exist for all time is consistent with known circuit behavior. Also note that although  $i_1$  has a dc component,  $i_2$  does not. This follows from known transformer behavior.

Finally we note the flux linkage prior to the appearance of the impulsive voltage is zero. Now since  $v = d\lambda/dt$ , the impulsive voltage source must be matched to an instantaneous change in flux linkage at  $t = 0^+$  of 20.


For the given polarity dots and reference directions of  $i_1$  and  $i_2$  we have

$$\lambda(0^+) = L_1 i_1(0^+) + M i_1(0^+) - L_2 i_2(0^+) - M i_2(0^+)$$
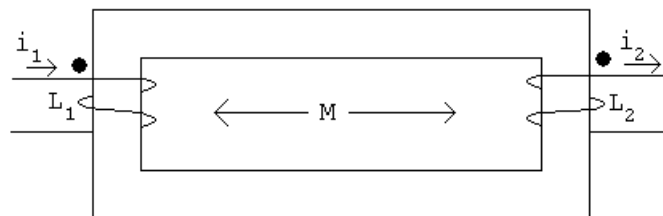
$$\begin{aligned} \lambda(0^+) &= 1\left(\frac{80}{3}\right) + 0.5\left(\frac{80}{3}\right) - 1\left(\frac{40}{3}\right) - 0.5\left(\frac{40}{3}\right) \\ &= \frac{120}{3} - \frac{60}{3} = 20 \quad (\text{Checks}) \end{aligned}$$



P 13.88 [a]

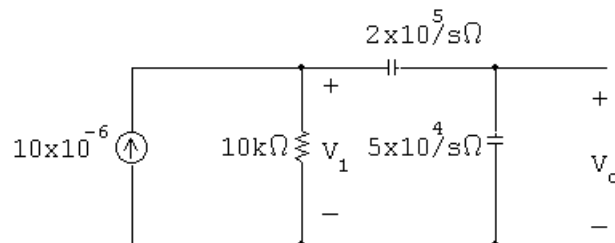

$$\frac{V_1}{10^4} + \frac{V_1}{[(2 \times 10^5)/s] + [(5 \times 10^4)/s]} = 10^{-5}$$

$$\frac{V_1}{10^4} + \frac{sV_1}{25 \times 10^4} = 10^{-5}$$

$$25V_1 + sV_1 = 2.5$$

$$V_1 = \frac{2.5}{s + 25}$$

$$V_o = \left( \frac{sV_1}{25 \times 10^4} \right) \left( \frac{5 \times 10^4}{s} \right) = \frac{1}{5} V_1$$

$$\therefore V_o = \frac{0.5}{s + 25}; \quad v_o = 0.5e^{-25t}u(t) \text{ V}$$

$$\text{[b]} \quad v_o(0^+) = 0.5 \text{ V}$$

$$v_o(0^+) = \frac{10^6}{20} \int_{0^-}^{0^+} 10 \times 10^{-6} \delta(x) dx = 0.5 \text{ V (Checks)}$$

$$C_e = \frac{(5)(20)}{25} = 4 \mu\text{F}$$

$$\tau = RC_e = (10 \times 10^3)(4 \times 10^{-6}) = 4 \times 10^{-2} \text{ s}; \quad \frac{1}{\tau} = \frac{100}{4} = 25 \text{ (Checks)}$$

Yes, the impulsive current establishes an instantaneous charge on each capacitor. After the impulsive current vanishes the capacitors discharge exponentially to zero volts.

P 13.89 [a] The circuit parameters are

$$R_a = \frac{120^2}{1200} = 12 \Omega \quad R_b = \frac{120^2}{1800} = 8 \Omega \quad X_a = \frac{120^2}{350} = \frac{1440}{35} \Omega$$

The branch currents are

$$\mathbf{I}_1 = \frac{120 \angle 0^\circ}{12} = 10 \angle 0^\circ \text{ A(rms)} \quad \mathbf{I}_2 = \frac{120 \angle 0^\circ}{j1440/35} = -j \frac{35}{12} = \frac{35}{12} \angle -90^\circ \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{120 \angle 0^\circ}{8} = 15 \angle 0^\circ \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 25 - j \frac{35}{12} = 25.17 \angle -6.65^\circ \text{ A(rms)}$$

Therefore,

$$i_2 = \left( \frac{35}{12} \right) \sqrt{2} \cos(\omega t - 90^\circ) \text{ A} \quad \text{and} \quad i_L = 25.17 \sqrt{2} \cos(\omega t - 6.65^\circ) \text{ A}$$

Thus,

$$i_2(0^-) = i_2(0^+) = 0 \text{ A} \quad \text{and} \quad i_L(0^-) = i_L(0^+) = 25\sqrt{2} \text{ A}$$



- [b]** Begin by using the  $s$ -domain circuit in Fig. 13.60 to solve for  $V_0$  symbolically. Write a single node voltage equation:

$$\frac{V_0 - (V_g + L_\ell I_0)}{sL_\ell} + \frac{V_0}{R_a} + \frac{V_0}{sL_a} = 0$$

$$\therefore V_0 = \frac{(R_a/L_\ell)V_g + I_0 R_a}{s + [R_a(L_a + L_\ell)]/L_a L_\ell}$$

where  $L_\ell = 1/120\pi$  H,  $L_a = 12/35\pi$  H,  $R_a = 12\ \Omega$ , and  $I_0 R_a = 300\sqrt{2}$  V. Also,

$$V_g = V_0 + I_L(j) = 120 + \left(25 - j\frac{35}{12}\right)j = 122.92 + 25j \text{ V(rms)}$$

$$v_g(t) = 122.92\sqrt{2}\cos\omega t - 25\sqrt{2}\sin\omega t \text{ V, with } \omega = 120\pi \text{ rad/s.}$$

Thus,

$$\begin{aligned} V_0 &= \frac{1440\pi(122.92\sqrt{2}s - 3000\pi\sqrt{2})}{(s + 1475\pi)(s^2 + 14,400\pi^2)} + \frac{300\sqrt{2}}{s + 1475\pi} \\ &= \frac{K_1}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi} + \frac{300\sqrt{2}}{s + 1475\pi} \end{aligned}$$

The coefficients are

$$K_1 = -121.18\sqrt{2} \text{ V} \quad K_2 = 61.03\sqrt{2}/\underline{6.85^\circ} \text{ V} \quad K_2^* = 61.03\sqrt{2}/\underline{-6.85^\circ}$$

Note that  $K_1 + 300\sqrt{2} = 178.82\sqrt{2}$  V. Thus, the inverse transform of  $V_0$  is

$$v_0 = 178.82\sqrt{2}e^{-1475\pi t} + 122.06\sqrt{2}\cos(120\pi t + 6.85^\circ) \text{ V}$$

Initially,

$$v_0(0^+) = 178.82\sqrt{2} + 122.06\sqrt{2}\cos 6.85^\circ = 300\sqrt{2} \text{ V}$$

Note that at  $t = 0^+$  the initial value of  $i_L$ , which is  $25\sqrt{2}$  A, exists in the  $12\ \Omega$  resistor  $R_a$ . Thus, the initial value of  $V_0$  is  $(25\sqrt{2})(12) = 300\sqrt{2}$  V.


- [c]** The phasor domain equivalent circuit has a  $j1\ \Omega$  inductive impedance in series with the parallel combination of a  $12\ \Omega$  resistive impedance and a  $j1440/35\ \Omega$  inductive impedance (remember that  $\omega = 120\pi$  rad/s). Note that  $\mathbf{V}_g = 120\angle 0^\circ + (25.17\angle -6.65^\circ)(j1) = 125.43\angle 11.50^\circ$  V(rms). The node voltage equation in the phasor domain circuit is

$$\frac{\mathbf{V}_0 - 125.43\angle 11.50^\circ}{j1} + \frac{\mathbf{V}_0}{12} + \frac{35\mathbf{V}_0}{j1440} = 0$$


$$\therefore \mathbf{V}_0 = 122.06\angle 6.85^\circ \text{ V(rms)}$$

Therefore,  $v_0 = 122.06\sqrt{2}\cos(120\pi t + 6.85^\circ)$  V, agreeing with the steady-state component of the result in part (b).

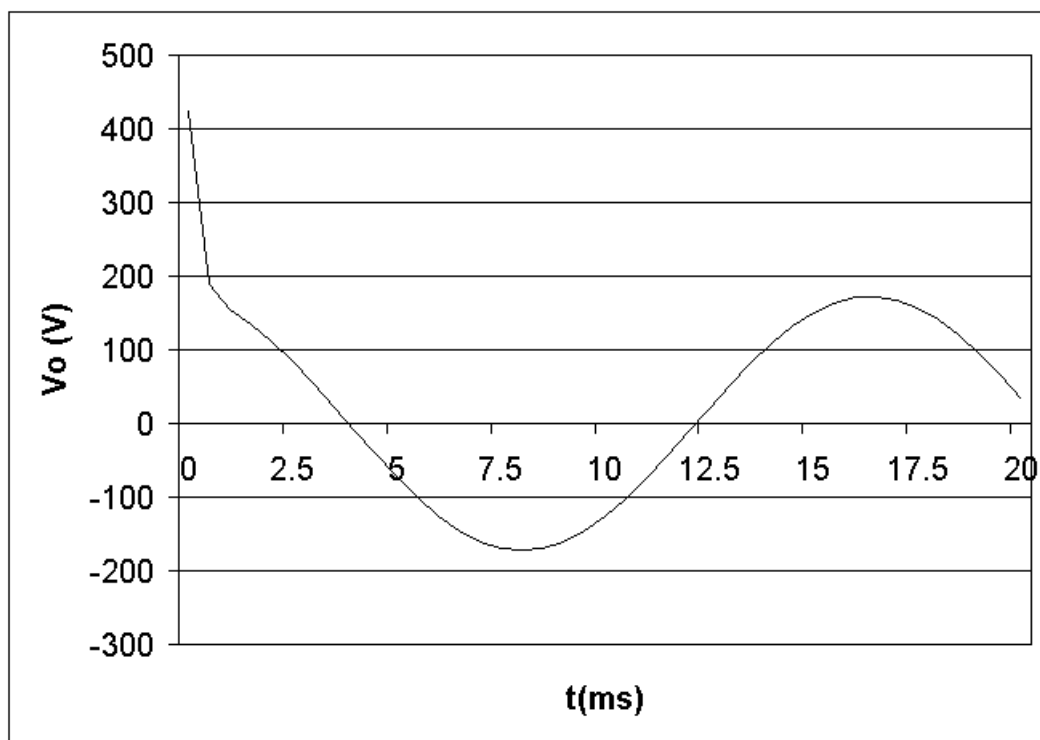[d] A plot of  $v_0$ , generated in Excel, is shown below.



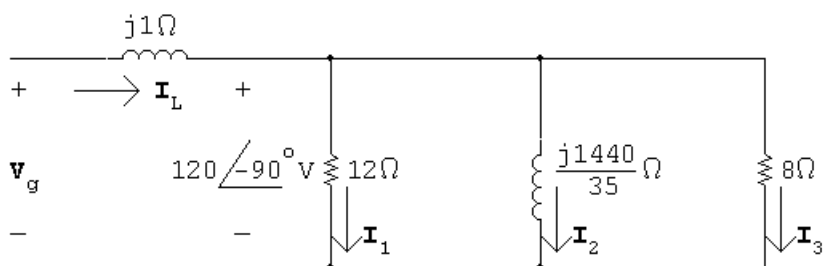P 13.90 [a] At  $t = 0^-$  the phasor domain equivalent circuit is



$$\mathbf{I}_1 = \frac{-j120}{12} = -j10 = 10\angle-90^\circ \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{-j120(35)}{j1440} = -\frac{35}{12} = \frac{35}{12}\angle180^\circ \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{-j120}{8} = -j15 = 15\angle-90^\circ \text{ A (rms)}$$

$$\mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = -\frac{35}{12} - j25 = 25.17\angle-96.65^\circ \text{ A (rms)}$$

$$i_L = 25.17\sqrt{2}\cos(120\pi t - 96.65^\circ) \text{ A}$$

$$i_L(0^-) = i_L(0^+) = -2.92\sqrt{2} \text{ A}$$

$$i_2 = \frac{35}{12}\sqrt{2}\cos(120\pi t + 180^\circ)\text{A}$$

$$i_2(0^-) = i_2(0^+) = -\frac{35}{12}\sqrt{2} = -2.92\sqrt{2}\text{A}$$

$$\mathbf{V}_g = \mathbf{V}_o + j1\mathbf{I}_L$$

$$\begin{aligned}\mathbf{V}_g &= -j120 + 25 - j\frac{35}{12} \\ &= 25 - j122.92\end{aligned}$$

$$v_g = 25\sqrt{2}\cos 120\pi t + 122.92\sqrt{2}\sin 120\pi t$$

$$\therefore V_g = \frac{25\sqrt{2}s + 122.92\sqrt{2}(120\pi)}{s^2 + (120\pi)^2}$$

Use a variation of the  $s$ -domain circuit in Fig.13.60, where

$$L_l = \frac{1}{120\pi}\text{H}; \quad L_a = \frac{12}{35\pi}\text{H}; \quad R_a = 12\Omega$$

$$i_L(0) = -2.92\sqrt{2}\text{A}; \quad i_2(0) = -2.92\sqrt{2}\text{A}$$

The node voltage equation is

$$0 = \frac{V_o - (V_g + i_L(0)L_l)}{sL_l} + \frac{V_o}{R_a} + \frac{V_o + i_2(0)L_a}{sL_a}$$

Solving for  $V_o$  yields

$$V_o = \frac{V_g R_a / L_l}{[s + R_a(L_l + L_a) / L_a L_l]} + \frac{R_a[i_L(0) - i_2(0)]}{[s + R_a(L_l + L_a) / L_l L_a]}$$

$$\frac{R_a}{L_l} = 1440\pi$$

$$\frac{R_a(L_l + L_a)}{L_l L_a} = \frac{12(\frac{1}{120\pi} + \frac{12}{35\pi})}{(\frac{12}{35\pi})(\frac{1}{120\pi})} = 1475\pi$$

$$i_L(0) - i_2(0) = -2.92\sqrt{2} + 2.92\sqrt{2} = 0$$


$$\begin{aligned}\therefore V_o &= \frac{1440\pi[25\sqrt{2}s + 122.92\sqrt{2}(120\pi)]}{(s + 1475\pi)[s^2 + (120\pi)^2]} \\ &= \frac{K_1}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi}\end{aligned}$$


$$K_1 = -14.55\sqrt{2} \quad K_2 = 61.03\sqrt{2}/-83.15^\circ$$

$$\therefore v_o(t) = -14.55\sqrt{2}e^{-1475\pi t} + 122.06\sqrt{2}\cos(120\pi t - 83.15^\circ)\text{V}$$

Check:

$$v_o(0) = (-14.55 + 14.55)\sqrt{2} = 0$$

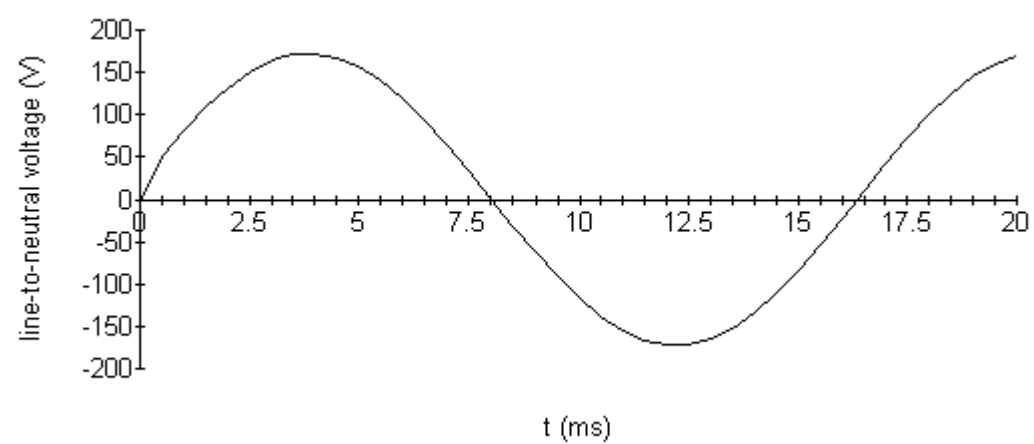**[b]**

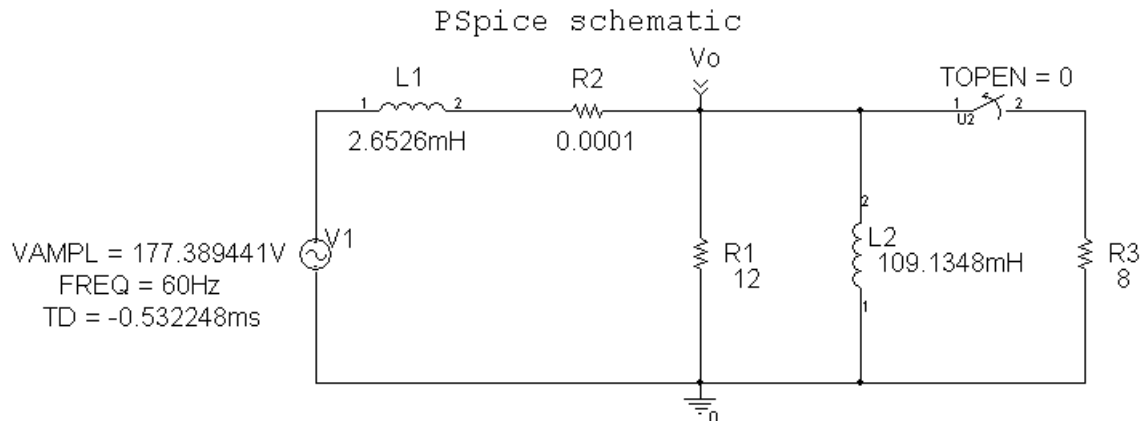

PSpice output file

```

**** 07/15/01 07:40:45 ***** PSpice Lite (Mar 2000) *****

** Profile: "SCHEMATIC1-tran" [ C:\shortcircuits\solutions\p9_76-SCHEMATIC1-tran.sim ]

****      CIRCUIT DESCRIPTION

*****

** Creating circuit file "p9_76-SCHEMATIC1-tran.sim.cir"
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS


*Libraries:
* Local Libraries :
* From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:
.lib "nom.lib"

*Analysis directives:
.TRAN 0 20ms 0
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
.INC ".\p9_76-SCHEMATIC1.net"

**** INCLUDING p9_76-SCHEMATIC1.net ****
* source P9_76
V_V1      N00637 0
+SIN 0 177.389441V 60Hz -0.532248ms 0 0
L_L1      N00637 N01311 2.6526mH IC=0
L_L2      0 VO 109.1348mH IC=0
R_R1      0 VO 12
R_R2      VO N01311 0.0001
R_R3      0 N01959 8
K_U2      VO N01959 Sw_tOpen PARAMS: tOpen=0 ttran=1u Rclosed=0.01
+ Ropen=1Meg


**** RESUMING p9_76-SCHEMATIC1-tran.sim.cir ****
.END

```

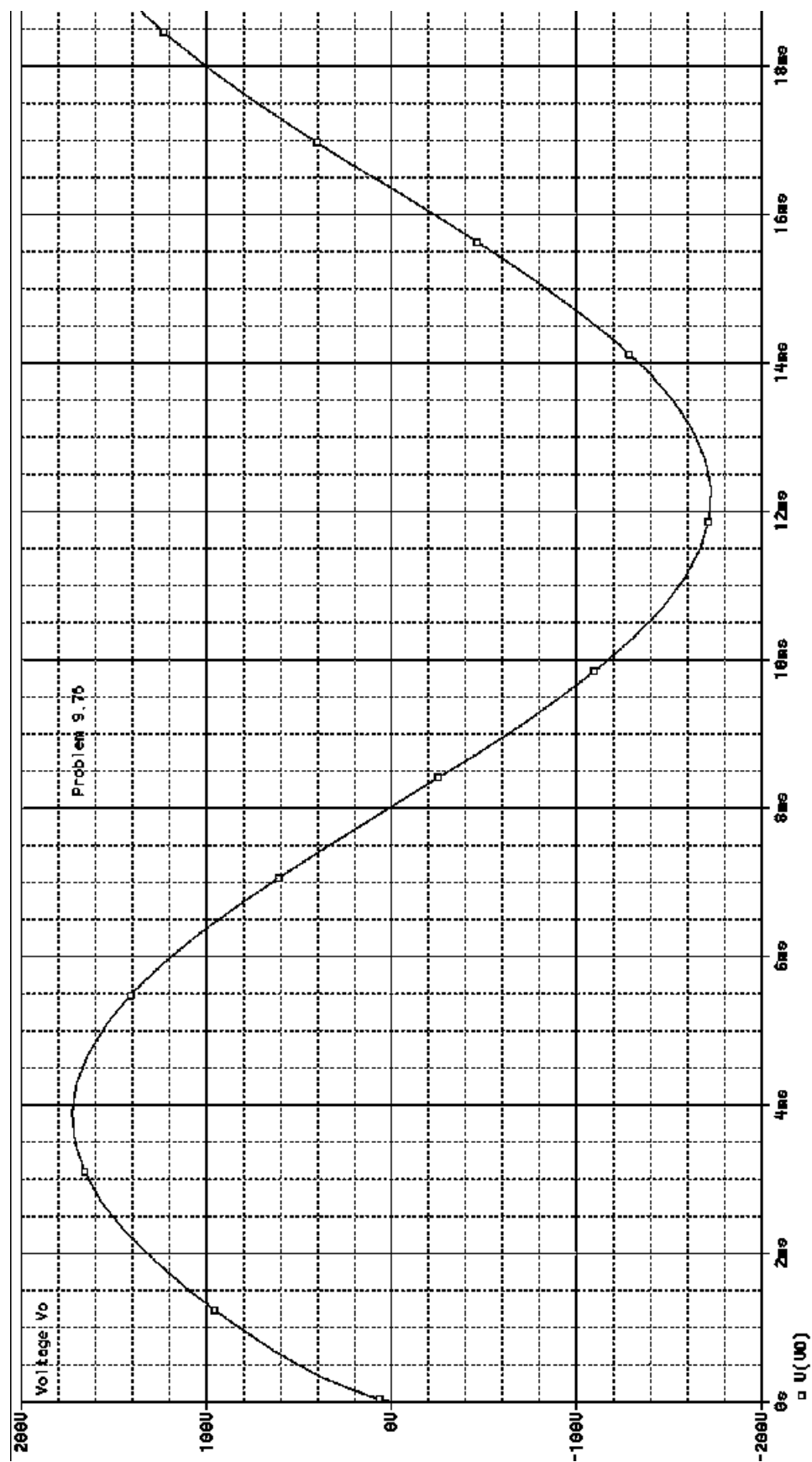

[c] In Prob. 13.89 the line-to-neutral voltage spikes at  $300\sqrt{2}$  V. In part (a) the line-to-neutral voltage has no spike. Thus the amount of voltage disturbance depends on what part of the cycle the sinusoidal steady-state voltage is switched.

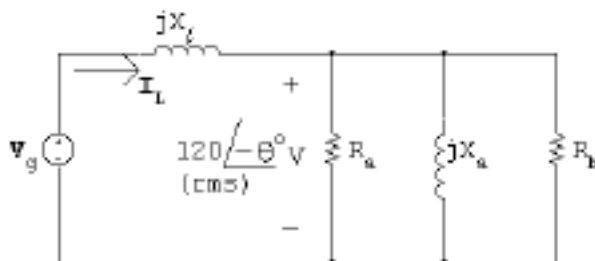P 13.91 [a] First find  $V_g$  before  $R_b$  is disconnected. The phasor domain circuit is



$$\begin{aligned}\mathbf{I}_L &= \frac{120 \angle -\theta^\circ}{R_a} + \frac{120 \angle -\theta^\circ}{R_b} + \frac{120 \angle -\theta^\circ}{jX_a} \\ &= \frac{120 \angle -\theta^\circ}{R_a R_b X_a} [(R_a + R_b)X_a - jR_a R_b]\end{aligned}$$

Since  $X_l = 1 \Omega$  we have

$$\mathbf{V}_g = 120 \angle -\theta^\circ + \frac{120 \angle -\theta^\circ}{R_a R_b X_a} [R_a R_b + j(R_a + R_b)X_a]$$

$$R_a = 12 \Omega; \quad R_b = 8 \Omega; \quad X_a = \frac{1440}{35} \Omega$$

$$\begin{aligned}\mathbf{V}_g &= \frac{120 \angle -\theta^\circ}{1440} (1475 + j300) \\ &= \frac{25}{12} \angle -\theta^\circ (59 + j12) = 125.43 \angle (-\theta + 11.50)^\circ\end{aligned}$$

$$v_g = 125.43\sqrt{2} \cos(120\pi t - \theta + 11.50^\circ) \text{ V}$$


Let  $\beta = -\theta + 11.50^\circ$ . Then

$$v_g = 125.43\sqrt{2} (\cos 120\pi t \cos \beta - \sin 120\pi t \sin \beta) \text{ V}$$

Therefore

$$V_g = \frac{125.43\sqrt{2} (s \cos \beta - 120\pi \sin \beta)}{s^2 + (120\pi)^2}$$

The  $s$ -domain circuit becomes

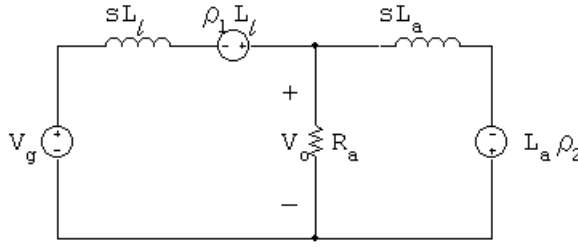

where  $\rho_1 = i_L(0^+)$  and  $\rho_2 = i_2(0^+)$ .

The  $s$ -domain node voltage equation is

$$\frac{V_o - (V_g + \rho_1 L_l)}{sL_l} + \frac{V_o}{R_a} + \frac{V_o + \rho_2 L_a}{sL_a} = 0$$

Solving for  $V_o$  yields

$$V_o = \frac{V_g R_a / L_l + (\rho_1 - \rho_2) R_a}{[s + \frac{(L_a + L_l) R_a}{L_a L_l}]}$$

Substituting the numerical values

$$L_l = \frac{1}{120\pi} \text{ H}; \quad L_a = \frac{12}{35\pi} \text{ H}; \quad R_a = 12 \Omega; \quad R_b = 8 \Omega;$$

gives

$$V_o = \frac{1440\pi V_g + 12(\rho_1 - \rho_2)}{(s + 1475\pi)}$$

Now determine the values of  $\rho_1$  and  $\rho_2$ .

$$\rho_1 = i_L(0^+) \quad \text{and} \quad \rho_2 = i_2(0^+)$$

$$\begin{aligned} \mathbf{I}_L &= \frac{120 \angle -\theta^\circ}{R_a R_b X_a} [(R_a + R_b) X_a - j R_a R_b] \\ &= \frac{120 \angle -\theta^\circ}{96(1440/35)} \left[ \frac{(20)(1440)}{35} - j96 \right] \\ &= 25.17 \angle (-\theta - 6.65)^\circ \text{ A(rms)} \end{aligned}$$

$$\therefore i_L = 25.17\sqrt{2} \cos(120\pi t - \theta - 6.65^\circ) \text{ A}$$

$$i_L(0^+) = \rho_1 = 25.17\sqrt{2} \cos(-\theta - 6.65^\circ) \text{ A}$$

$$\therefore \rho_1 = 25\sqrt{2} \cos \theta - 2.92\sqrt{2} \sin \theta \text{ A}$$

$$\mathbf{I}_2 = \frac{120 \angle -\theta^\circ}{j(1440/35)} = \frac{35}{12} \angle (-\theta - 90)^\circ$$



$$i_2 = \frac{35}{12}\sqrt{2}\cos(120\pi t - \theta - 90^\circ)\text{A}$$

$$\rho_2 = i_2(0^+) = -\frac{35}{12}\sqrt{2}\sin\theta = -2.92\sqrt{2}\sin\theta\text{A}$$

$$\therefore \rho_1 - \rho_2 = 25\sqrt{2}\cos\theta$$

$$(\rho_1 - \rho_2)R_a = 300\sqrt{2}\cos\theta$$

$$\begin{aligned}\therefore V_o &= \frac{1440\pi}{s + 1475\pi} \cdot V_g + \frac{300\sqrt{2}\cos\theta}{s + 1475\pi} \\ &= \frac{1440\pi}{s + 1475\pi} \left[ \frac{125.43\sqrt{2}(s\cos\beta - 120\pi\sin\beta)}{s^2 + 14,400\pi^2} \right] + \frac{300\sqrt{2}\cos\theta}{s + 1475\pi} \\ &= \frac{K_1 + 300\sqrt{2}\cos\theta}{s + 1475\pi} + \frac{K_2}{s - j120\pi} + \frac{K_2^*}{s + j120\pi}\end{aligned}$$

Now

$$\begin{aligned}K_1 &= \frac{(1440\pi)(125.43\sqrt{2})[-1475\pi\cos\beta - 120\pi\sin\beta]}{1475^2\pi^2 + 14,400\pi^2} \\ &= \frac{-1440(125.43\sqrt{2})[1475\cos\beta + 120\sin\beta]}{1475^2 + 14,400}\end{aligned}$$

Since  $\beta = -\theta + 11.50^\circ$ ,  $K_1$  reduces to

$$K_1 = -121.18\sqrt{2}\cos\theta - 14.55\sqrt{2}\sin\theta$$

From the partial fraction expansion for  $V_o$  we see  $v_o(t)$  will go directly into steady state when  $K_1 = -300\sqrt{2}\cos\theta$ . It follows that

$$-14.55\sqrt{2}\sin\theta = -178.82\sqrt{2}\cos\theta$$

$$\text{or} \quad \tan\theta = 12.29$$


$$\text{Therefore,} \quad \theta = 85.35^\circ$$

**[b]** When  $\theta = 85.35^\circ$ ,  $\beta = -73.85^\circ$


$$\begin{aligned}\therefore K_2 &= \frac{1440\pi(125.43\sqrt{2})[-120\pi\sin(-73.85^\circ) + j120\pi\cos(-73.85^\circ)]}{(1475\pi + j120\pi)(j240\pi)} \\ &= \frac{720\sqrt{2}(120.48 + j34.88)}{-120 + j1475} \\ &= 61.03\sqrt{2}/-78.50^\circ \\ \therefore v_o &= 122.06\sqrt{2}\cos(120\pi t - 78.50^\circ)\text{V} \quad t > 0 \\ &= 172.61\cos(120\pi t - 78.50^\circ)\text{V} \quad t > 0\end{aligned}$$

**[c]**  $v_{o1} = 169.71 \cos(120\pi t - 85.35^\circ) \text{ V} \quad t < 0$

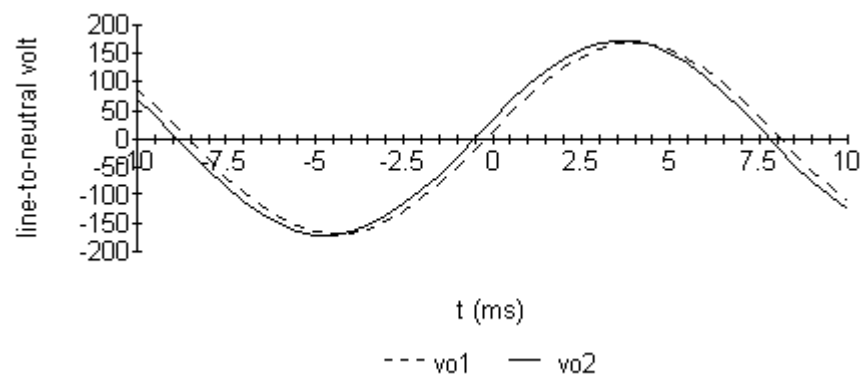$v_{o2} = 172.61 \cos(120\pi t - 78.50^\circ) \text{ V} \quad t > 0$



## PSpice schematic

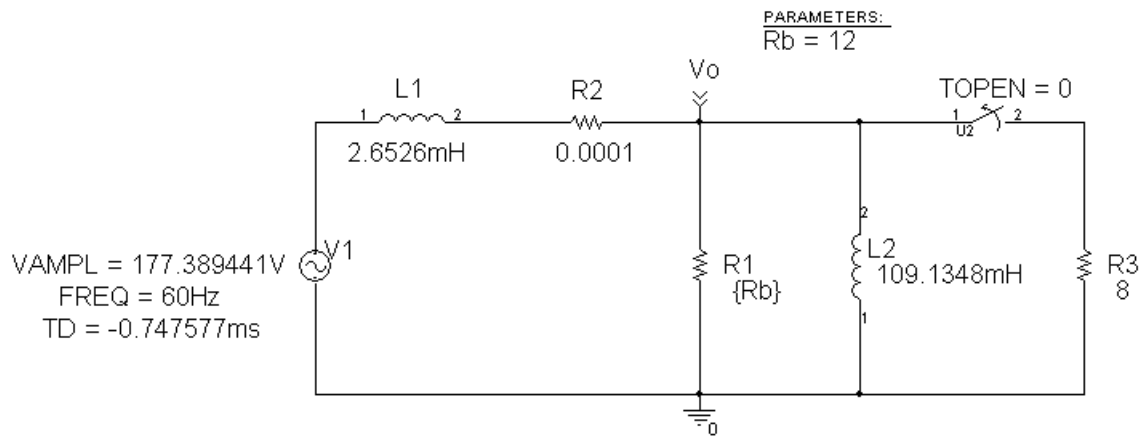

## PSpice output file

```

** Creating circuit file "p9_77-SCHEMATIC1-tran.sim.cir"
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS

*Libraries:
* Local Libraries :
* From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:
.lib "nom.lib"

*Analysis directives:
.TRAN 0 20ms 0
.STEP PARAM Rb LIST 4.8 12
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
.INC ".\p9_77-SCHEMATIC1.net"

**** INCLUDING p9_77-SCHEMATIC1.net ****
* source P9_77
V_V1      N00637 0
+SIN 0 177.389441V 60Hz -0.747577ms 0 0
L_L1      N00637 N01311 2.6526mH IC=0
L_L2      0 VO 109.1348mH IC=0
R_R1      0 VO {Rb}
R_R2      VO N01311 0.0001
R_R3      0 N01959 8
X_U2      VO N01959 Sw_tOpen PARAMS: tOpen=0 ttran=1u Rclosed=0.01
+ Ropen=1Meg
.PARAM Rb=12

**** RESUMING p9_77-SCHEMATIC1-tran.sim.cir ****
.END

```

