

# Sinusoidal Steady State Power Calculations

## Assessment Problems

AP 10.1 [a]  $\mathbf{V} = 100/\underline{-45^\circ} \text{ V}, \quad \mathbf{I} = 20/\underline{15^\circ} \text{ A}$

Therefore

$$P = \frac{1}{2}(100)(20) \cos[-45 - (15)] = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin -60^\circ = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

[b]  $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{165^\circ}$

$$P = 1000 \cos(-210^\circ) = -866.03 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-210^\circ) = 500 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[c]  $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{-105^\circ}$

$$P = 1000 \cos(60^\circ) = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin(60^\circ) = 866.03 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[d]  $\mathbf{V} = 100/\underline{0^\circ}, \quad \mathbf{I} = 20/\underline{120^\circ}$

$$P = 1000 \cos(-120^\circ) = -500 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-120^\circ) = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

AP 10.2  $\text{pf} = \cos(\theta_v - \theta_i) = \cos[15 - (75)] = \cos(-60^\circ) = 0.5 \text{ leading}$

$$\text{rf} = \sin(\theta_v - \theta_i) = \sin(-60^\circ) = -0.866$$

AP 10.3 From Ex. 9.4  $I_{\text{eff}} = \frac{I_{\rho}}{\sqrt{3}} = \frac{0.18}{\sqrt{3}} \text{ A}$

$$P = I_{\text{eff}}^2 R = \left( \frac{0.0324}{3} \right) (5000) = 54 \text{ W}$$

AP 10.4 [a]  $Z = (39 + j26) \parallel (-j52) = 48 - j20 = 52 \angle -22.62^\circ \Omega$

Therefore  $\mathbf{I}_{\ell} = \frac{250 \angle 0^\circ}{48 - j20 + 1 + j4} = 4.85 \angle 18.08^\circ \text{ A(rms)}$

$$\mathbf{V}_L = Z \mathbf{I}_{\ell} = (52 \angle -22.62^\circ)(4.85 \angle 18.08^\circ) = 252.20 \angle -4.54^\circ \text{ V(rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38 \angle -38.23^\circ \text{ A(rms)}$$

[b]  $S_L = \mathbf{V}_L \mathbf{I}_L^* = (252.20 \angle -4.54^\circ)(5.38 \angle +38.23^\circ) = 1357 \angle 33.69^\circ$   
 $= (1129.09 + j752.73) \text{ VA}$

$$P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$$

[c]  $P_{\ell} = |\mathbf{I}_{\ell}|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_{\ell} = |\mathbf{I}_{\ell}|^2 4 = 94.09 \text{ VAR}$

[d]  $S_g(\text{delivering}) = 250 \mathbf{I}_{\ell}^* = (1152.62 - j376.36) \text{ VA}$

Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.

[e]  $Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$

Therefore the capacitor is delivering 1223.18 magnetizing VAR.

Check:  $94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR}$  and

$$1129.09 + 23.52 = 1152.62 \text{ W}$$

AP 10.5 Series circuit derivation:

$$S = 250 \mathbf{I}^* = (40,000 - j30,000)$$

Therefore  $\mathbf{I}^* = 160 - j120 = 200 \angle -36.87^\circ \text{ A(rms)}$

$$\mathbf{I} = 200 \angle 36.87^\circ \text{ A(rms)}$$

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{250}{200 \angle 36.87^\circ} = 1.25 \angle -36.87^\circ = (1 - j0.75) \Omega$$

Therefore  $R = 1 \Omega, \quad X_C = -0.75 \Omega$

Parallel circuit derivation:

$$P = \frac{(250)^2}{R}; \quad \text{therefore} \quad R = \frac{(250)^2}{40,000} = 1.5625 \, \Omega$$

$$Q = \frac{(250)^2}{X_C}; \quad \text{therefore} \quad X_C = \frac{(250)^2}{-30,000} = -2.083 \, \Omega$$

AP 10.6  $S_1 = 15,000(0.6) + j15,000(0.8) = 9000 + j12,000 \, \text{VA}$

$$S_2 = 6000(0.8) + j6000(0.6) = 4800 - j3600 \, \text{VA}$$


$$S_T = S_1 + S_2 = 13,800 + j8400 \, \text{VA}$$

$$S_T = 200\mathbf{I}^*; \quad \text{therefore} \quad \mathbf{I}^* = 69 + j42 \quad \mathbf{I} = 69 - j42 \, \text{A}$$


$$\mathbf{V}_s = 200 + j\mathbf{I} = 200 + j69 + 42 = 242 + j69 = 251.64/\underline{15.91^\circ} \, \text{V(rms)}$$

AP 10.7 [a] The phasor domain equivalent circuit and the Thévenin equivalent are shown below:

Phasor domain equivalent circuit:

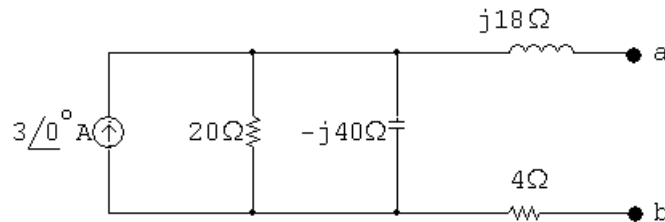

Thévenin equivalent:

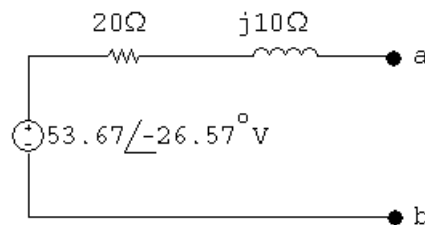

$$\mathbf{V}_{Th} = 3 \frac{-j800}{20 - j40} = 48 - j24 = 53.67/\underline{-26.57^\circ} \, \text{V}$$

$$Z_{Th} = 4 + j18 + \frac{-j800}{20 - j40} = 20 + j10 = 22.36/\underline{26.57^\circ} \, \Omega$$

For maximum power transfer,  $Z_L = (20 - j10) \, \Omega$

$$\text{[b] } \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{40} = 1.34 \angle -26.57^\circ \text{ A}$$


$$\text{Therefore } P = \left( \frac{1.34}{\sqrt{2}} \right)^2 20 = 18 \text{ W}$$

$$\text{[c] } R_L = |Z_{Th}| = 22.36 \Omega$$

$$\text{[d] } \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{42.36 + j10} = 1.23 \angle -39.85^\circ \text{ A}$$

$$\text{Therefore } P = \left( \frac{1.23}{\sqrt{2}} \right)^2 (22.36) = 17 \text{ W}$$

AP 10.8

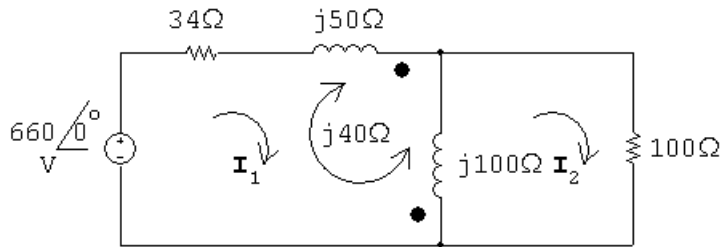

Mesh current equations:

$$660 = (34 + j50)\mathbf{I}_1 + j100(\mathbf{I}_1 - \mathbf{I}_2) + j40\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2)$$


$$0 = j100(\mathbf{I}_2 - \mathbf{I}_1) - j40\mathbf{I}_1 + 100\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 3.536 \angle -45^\circ \text{ A},$$

$$\mathbf{I}_2 = 3.5 \angle 0^\circ \text{ A}; \quad \therefore P = \frac{1}{2}(3.5)^2(100) = 612.50 \text{ W}$$

AP 10.9 [a]

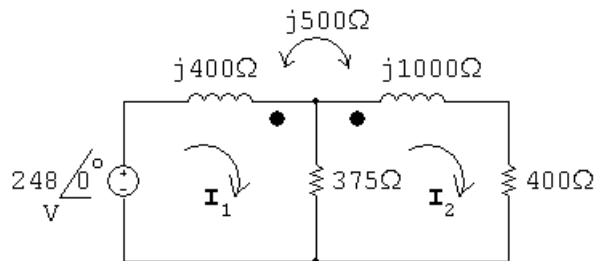

$$248 = j400\mathbf{I}_1 - j500\mathbf{I}_2 + 375(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 375(\mathbf{I}_2 - \mathbf{I}_1) + j1000\mathbf{I}_2 - j500\mathbf{I}_1 + 400\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 0.80 - j0.62 \text{ A}; \quad \mathbf{I}_2 = 0.4 - j0.3 = 0.5 \angle -36.87^\circ \text{ A}$$

$$\therefore P = \frac{1}{2}(0.25)(400) = 50 \text{ W}$$

$$\text{[b]} \quad \mathbf{I}_1 - \mathbf{I}_2 = 0.4 - j0.32 \text{ A}$$

$$P_{375} = \frac{1}{2} |\mathbf{I}_1 - \mathbf{I}_2|^2 (375) = 49.20 \text{ W}$$

$$\text{[c]} \quad P_g = \frac{1}{2} (248)(0.8) = 99.20 \text{ W}$$

$$\sum P_{\text{abs}} = 50 + 49.2 = 99.20 \text{ W} \quad (\text{checks})$$

AP 10.10 **[a]**  $V_{\text{Th}} = 210 \angle 0^\circ \text{ V}; \quad \mathbf{V}_2 = \frac{1}{4} \mathbf{V}_1; \quad \mathbf{I}_1 = \frac{1}{4} \mathbf{I}_2$   
Short circuit equations:

$$840 = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$

$$\therefore \mathbf{I}_2 = 14 \text{ A}; \quad R_{\text{Th}} = \frac{210}{14} = 15 \Omega$$

$$\text{[b]} \quad P_{\text{max}} = \left( \frac{210}{30} \right)^2 15 = 735 \text{ W}$$

AP 10.11 **[a]**  $\mathbf{V}_{\text{Th}} = -4(146 \angle 0^\circ) = -584 \angle 0^\circ \text{ V(rms)} = 584 \angle 180^\circ \text{ V(rms)}$

$$\mathbf{V}_2 = 4\mathbf{V}_1; \quad \mathbf{I}_1 = -4\mathbf{I}_2$$

Short circuit equations:

$$146 \angle 0^\circ = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{V}_2$$

$$\therefore \mathbf{I}_2 = -146/365 = -0.40 \text{ A}; \quad R_{\text{Th}} = \frac{-584}{-0.4} = 1460 \Omega$$

$$\text{[b]} \quad P = \left( \frac{-584}{2920} \right)^2 1460 = 58.40 \text{ W}$$

## Problems

P 10.1 [a]  $P = \frac{1}{2}(100)(10) \cos(50 - 15) = 500 \cos 35^\circ = 409.58 \text{ W} \quad (\text{abs})$

$$Q = 500 \sin 35^\circ = 286.79 \text{ VAR} \quad (\text{abs})$$

[b]  $P = \frac{1}{2}(40)(20) \cos(-15 - 60) = 400 \cos(-75^\circ) = 103.53 \text{ W} \quad (\text{abs})$

$$Q = 400 \sin(-75^\circ) = -386.37 \text{ VAR} \quad (\text{del})$$

[c]  $P = \frac{1}{2}(400)(10) \cos(30 - 150) = 2000 \cos(-120^\circ) = -1000 \text{ W} \quad (\text{del})$


$$Q = 2000 \sin(-120^\circ) = -1732.05 \text{ VAR} \quad (\text{del})$$

[d]  $P = \frac{1}{2}(200)(5) \cos(160 - 40) = 500 \cos(120^\circ) = -250 \text{ W} \quad (\text{del})$

$$Q = 500 \sin(120^\circ) = 433.01 \text{ VAR} \quad (\text{abs})$$

P 10.2  $p = P + P \cos 2\omega t - Q \sin 2\omega t; \quad \frac{dp}{dt} = -2\omega P \sin 2\omega t - 2\omega Q \cos 2\omega t$
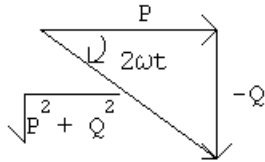
$$\frac{dp}{dt} = 0 \quad \text{when} \quad -2\omega P \sin 2\omega t = 2\omega Q \cos 2\omega t \quad \text{or} \quad \tan 2\omega t = -\frac{Q}{P}$$



$$\cos 2\omega t = \frac{P}{\sqrt{P^2 + Q^2}}; \quad \sin 2\omega t = -\frac{Q}{\sqrt{P^2 + Q^2}}$$

Let  $\theta = \tan^{-1}(-Q/P)$ , then  $p$  is maximum when  $2\omega t = \theta$  and  $p$  is minimum when  $2\omega t = (\theta + \pi)$ .

Therefore  $p_{\max} = P + P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - \frac{Q(-Q)}{\sqrt{P^2 + Q^2}} = P + \sqrt{P^2 + Q^2}$

and  $p_{\min} = P - P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - Q \cdot \frac{Q}{\sqrt{P^2 + Q^2}} = P - \sqrt{P^2 + Q^2}$

P 10.3 [a] hair dryer = 600 W vacuum = 630 W

sun lamp = 279 W air conditioner = 860 W

television = 240 W  $\sum P = 2609$  W

Therefore  $I_{\text{eff}} = \frac{2609}{120} = 21.74$  A

Yes, the breaker will trip.

[b]  $\sum P = 2609 - 909 = 1700$  W;  $I_{\text{eff}} = \frac{1700}{120} = 14.17$  A

Yes, the breaker will not trip if the current is reduced to 14.17 A.

P 10.4 [a]  $I_{\text{eff}} = 40/115 \cong 0.35$  A; [b]  $I_{\text{eff}} = 130/115 \cong 1.13$  A

P 10.5  $W_{\text{dc}} = \frac{V_{\text{dc}}^2}{R}T$ ;  $W_s = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$

$$\therefore \frac{V_{\text{dc}}^2}{R}T = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$V_{\text{dc}}^2 = \frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt$$

$$V_{\text{dc}} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt} = V_{\text{rms}} = V_{\text{eff}}$$

P 10.6 [a] Area under one cycle of  $v_g^2$ :

$$\begin{aligned} A &= (5^2)(2)(30 \times 10^{-6}) + 2^2(2)(37.5 \times 10^{-6}) \\ &= 1800 \times 10^{-6} \end{aligned}$$

Mean value of  $v_g^2$ :

$$\text{M.V.} = \frac{A}{200 \times 10^{-6}} = \frac{1800 \times 10^{-6}}{200 \times 10^{-6}} = 9$$

$$\therefore V_{\text{rms}} = \sqrt{9} = 3 \text{ V(rms)}$$

$$\text{[b]} P = \frac{V_{\text{rms}}^2}{R} = \frac{3^2}{2.25} = 4 \text{ W}$$

P 10.7  $i(t) = 200t$   $0 \leq t \leq 75 \text{ ms}$


$$i(t) = 60 - 600t \quad 75 \text{ ms} \leq t \leq 100 \text{ ms}$$

$$\begin{aligned} I_{\text{rms}} &= \sqrt{\frac{1}{0.1} \left\{ \int_0^{0.075} (200)^2 t^2 dt + \int_{0.075}^{0.1} (60 - 600t)^2 dt \right\}} \\ &= \sqrt{10(5.625) + 10(1.875)} = \sqrt{75} = 8.66 \text{ A(rms)} \end{aligned}$$

P 10.8  $P = I_{\text{rms}}^2 R \quad \therefore R = \frac{3 \times 10^3}{75} = 40 \Omega$

P 10.9  $\mathbf{I}_g = 40 \angle 0^\circ \text{ mA}$
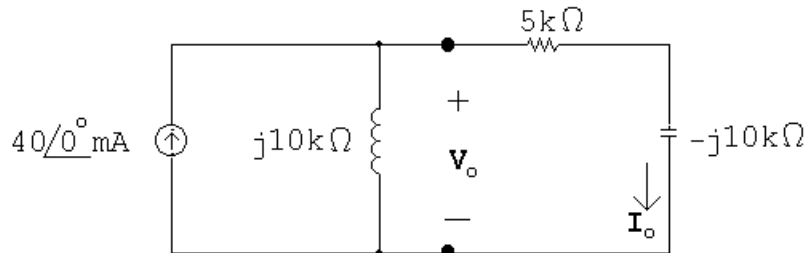
$$j\omega L = j10,000 \Omega; \quad \frac{1}{j\omega C} = -j10,000 \Omega$$



$$\mathbf{I}_o = \frac{j10,000}{5000} (40 \angle 0^\circ) = 80 \angle 90^\circ \text{ mA}$$


$$P = \frac{1}{2} |\mathbf{I}_o|^2 (5000) = \frac{1}{2} (0.08)^2 (5000) = 16 \text{ W}$$

$$Q = \frac{1}{2} |\mathbf{I}_o|^2 (-10,000) = -32 \text{ VAR}$$

$$S = P + jQ = 16 - j32 \text{ VA}$$

$$|S| = 35.78 \text{ VA}$$

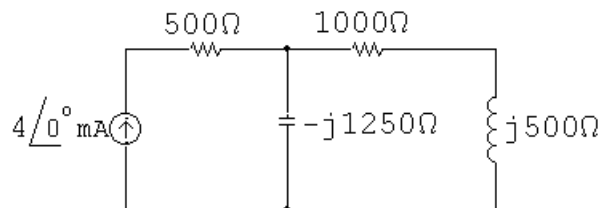P 10.10  $\mathbf{I}_g = 4 \angle 0^\circ \text{ mA}; \quad \frac{1}{j\omega C} = -j1250 \Omega; \quad j\omega L = j500 \Omega$




$$Z_{\text{eq}} = 500 + [-j1250 \parallel (1000 + j500)] = 1500 - j500 \Omega$$

$$P_g = -\frac{1}{2} |I|^2 \text{Re}\{Z_{\text{eq}}\} = -\frac{1}{2} (0.004)^2 (1500) = -12 \text{ mW}$$

The source delivers 12 mW of power to the circuit.



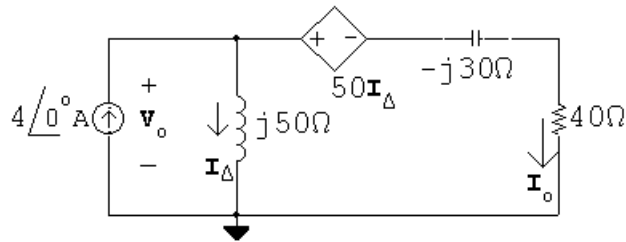P 10.11  $j\omega L = j10^5(0.5 \times 10^{-3}) = j50 \Omega$ ;  $\frac{1}{j\omega C} = \frac{1}{j10^5[(1/3) \times 10^{-6}]} = -j30 \Omega$



$$-4 + \frac{\mathbf{V}_o}{j50} + \frac{\mathbf{V}_o - 50\mathbf{I}_\Delta}{40 - j30} = 0$$

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{j50}$$

Place the equations in standard form:

$$\mathbf{V}_o \left( \frac{1}{j50} + \frac{1}{40 - j30} \right) + \mathbf{I}_\Delta \left( \frac{-50}{40 - j30} \right) = 4$$

$$\mathbf{V}_o \left( \frac{1}{j50} \right) + \mathbf{I}_\Delta(-1) = 0$$

Solving,


$$\mathbf{V}_o = 200 - j400 \text{ V}; \quad \mathbf{I}_\Delta = -8 - j4 \text{ A}$$

$$\mathbf{I}_o = 4 - (-8 - j4) = 12 + j4 \text{ A}$$

$$P_{40\Omega} = \frac{1}{2} |\mathbf{I}_o|^2 (40) = \frac{1}{2} (160)(40) = 3200 \text{ W}$$

P 10.12 [a] line loss = 7500 - 2500 = 5 kW

$$\text{line loss} = |\mathbf{I}_g|^2 20 \quad \therefore |\mathbf{I}_g|^2 = 250$$

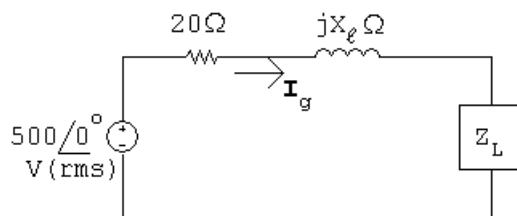


$$|\mathbf{I}_g| = \sqrt{250} \text{ A}$$

$$|\mathbf{I}_g|^2 R_L = 2500 \quad \therefore R_L = 10 \Omega$$

$$|\mathbf{I}_g|^2 X_L = -5000 \quad \therefore X_L = -20 \Omega$$

Thus,

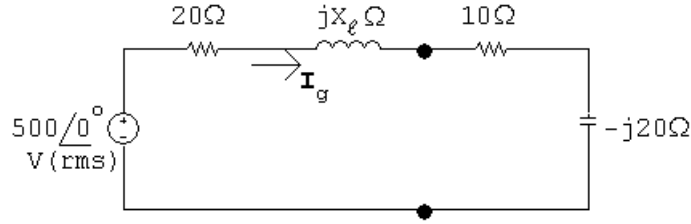

$$|Z| = \sqrt{(30)^2 + (X_\ell - 20)^2} \quad |\mathbf{I}_g| = \frac{500}{\sqrt{900 + (X_\ell - 20)^2}}$$

$$\therefore 900 + (X_\ell - 20)^2 = \frac{25 \times 10^4}{250} = 1000$$

$$\text{Solving,} \quad (X_\ell - 20) = \pm 10.$$

$$\text{Thus, } X_\ell = 10 \Omega \quad \text{or} \quad X_\ell = 30 \Omega$$

**[b]** If  $X_\ell = 30 \Omega$ :

$$\mathbf{I}_g = \frac{500}{30 + j10} = 15 - j5 \text{ A}$$

$$S_g = -500 \mathbf{I}_g^* = -7500 - j2500 \text{ VA}$$

Thus, the voltage source is delivering 7500 W and 2500 magnetizing vars.

$$Q_{j30} = |\mathbf{I}_g|^2 X_\ell = 250(30) = 7500 \text{ VAR}$$

Therefore the line reactance is absorbing 7500 magnetizing vars.

$$Q_{-j20} = |\mathbf{I}_g|^2 X_L = 250(-20) = -5000 \text{ VAR}$$

Therefore the load reactance is generating 5000 magnetizing vars.

$$\sum Q_{\text{gen}} = 7500 \text{ VAR} = \sum Q_{\text{abs}}$$

If  $X_\ell = 10 \Omega$ :

$$\mathbf{I}_g = \frac{500}{30 - j10} = 15 + j5 \text{ A}$$

$$S_g = -500 \mathbf{I}_g^* = -7500 + j2500 \text{ VA}$$

Thus, the voltage source is delivering 7500 W and absorbing 2500 magnetizing vars.

$$Q_{j10} = |\mathbf{I}_g|^2 (10) = 250(10) = 2500 \text{ VAR}$$

Therefore the line reactance is absorbing 2500 magnetizing vars. The load continues to generate 5000 magnetizing vars.

$$\sum Q_{\text{gen}} = 5000 \text{ VAR} = \sum Q_{\text{abs}}$$

P 10.13  $Z_f = -j10,000 \parallel 20,000 = 4000 - j8000 \Omega$

$$Z_i = 2000 - j2000 \Omega$$

$$\therefore \frac{Z_f}{Z_i} = \frac{4000 - j8000}{2000 - j2000} = 3 - j1$$

$$\mathbf{V}_o = -\frac{Z_f}{Z_i} \mathbf{V}_g; \quad \mathbf{V}_g = 1 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_o = (3 - j1)(1) = 3 - j1 = 3.16 \angle -18.43^\circ \text{ V}$$

$$P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \frac{(10)^2}{1000} = 5 \times 10^{-3} = 5 \text{ mW}$$

P 10.14 [a]  $P = \frac{1}{2} \frac{(240)^2}{480} = 60 \text{ W}$

$$-\frac{1}{\omega C} = \frac{-9 \times 10^6}{(5000)(5)} = -360 \Omega$$

$$Q = \frac{1}{2} \frac{(240)^2}{(-360)} = -80 \text{ VAR}$$

$$p_{\max} = P + \sqrt{P^2 + Q^2} = 60 + \sqrt{(60)^2 + (80)^2} = 160 \text{ W (del)}$$

[b]  $p_{\min} = 60 - \sqrt{60^2 + 80^2} = -40 \text{ W (abs)}$

[c]  $P = 60 \text{ W}$  from (a)

[d]  $Q = -80 \text{ VAR}$  from (a)

[e] generate, because  $Q < 0$


[f]  $\text{pf} = \cos(\theta_v - \theta_i)$

$$\mathbf{I} = \frac{240}{480} + \frac{240}{-j360} = 0.5 + j0.67 = 0.83 \angle 53.13^\circ \text{ A}$$

$$\therefore \text{pf} = \cos(0 - 53.13^\circ) = 0.6 \text{ leading}$$

[g]  $\text{rf} = \sin(-53.13^\circ) = -0.8$

P 10.15 [a]

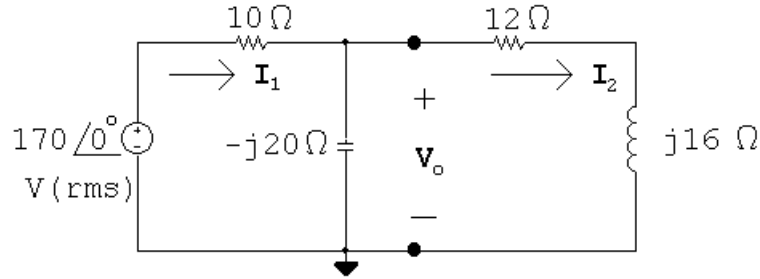

The mesh equations are:

$$(10 - j20)\mathbf{I}_1 + (j20)\mathbf{I}_2 = 170$$

$$(j20)\mathbf{I}_1 + (12 - j4)\mathbf{I}_2 = 0$$

Solving,

$$\mathbf{I}_1 = 4 + j1 \text{ A}; \quad \mathbf{I}_2 = 3.5 - j5.5 \text{ A}$$

$$S = -\mathbf{V}_g \mathbf{I}_1^* = -(170)(4 - j1) = -680 + j170 \text{ VA}$$

**[b]** Source is delivering 680 W.**[c]** Source is absorbing 170 magnetizing VAR.

$$\mathbf{[d]} \quad P_{10\Omega} = (\sqrt{17})^2(10) = 170 \text{ W}$$

$$P_{12\Omega} = (\sqrt{42.5})^2(12) = 510 \text{ W} \quad (\mathbf{I}_1 - \mathbf{I}_2) = 0.5 + j6.5 \text{ A}$$

$$Q_{-j20\Omega} = (\sqrt{42.5})^2(20) = -850 \text{ VAR} \quad |\mathbf{I}_1 - \mathbf{I}_2| = \sqrt{42.5}$$

$$Q_{j16\Omega} = (\sqrt{42.5})^2(16) = 680 \text{ VAR}$$

$$\mathbf{[e]} \quad \sum P_{\text{del}} = 680 \text{ W}$$

$$\sum P_{\text{diss}} = 170 + 510 = 680 \text{ W}$$


$$\therefore \sum P_{\text{del}} = \sum P_{\text{diss}} = 680 \text{ W}$$

$$\mathbf{[f]} \quad \sum Q_{\text{abs}} = 170 + 680 = 850 \text{ VAR}$$

$$\sum Q_{\text{dev}} = 850 \text{ VAR}$$

$$\therefore \sum \text{mag VAR dev} = \sum \text{mag VAR abs} = 850$$

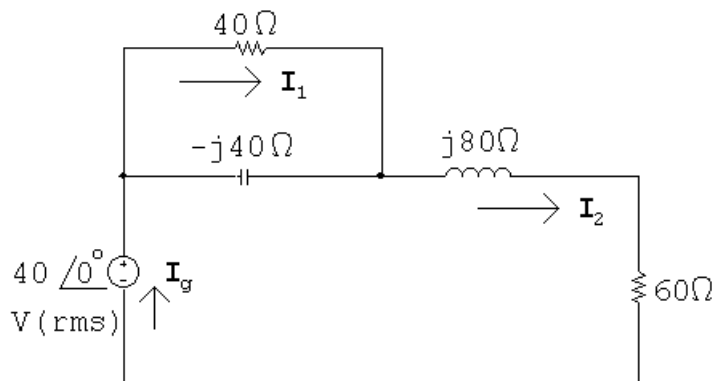P 10.16 [a]  $\frac{1}{j\omega C} = -j40\ \Omega$ ;  $j\omega L = j80\ \Omega$



$$Z_{\text{eq}} = 40 \parallel -j40 + j80 + 60 = 80 + j60\ \Omega$$

$$\mathbf{I}_g = \frac{40\angle 0^\circ}{80 + j60} = 0.32 - j0.24\ \text{A}$$

$$S_g = -\frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = -\frac{1}{2} 40(0.32 + j0.24) = -6.4 - j4.8\ \text{VA}$$

$$P = 6.4\ \text{W}(\text{del}); \quad Q = 4.8\ \text{VAR}(\text{del})$$

$$|S| = |S_g| = 8\ \text{VA}$$

[b]  $\mathbf{I}_1 = \frac{-j40}{40 - j40} \mathbf{I}_g = 0.04 - j0.28\ \text{A}$

$$P_{40\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (40) = 1.6\ \text{W}$$

$$P_{60\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (60) = 4.8\ \text{W}$$

$$\sum P_{\text{diss}} = 1.6 + 4.8 = 6.4\ \text{W} = \sum P_{\text{dev}}$$

[c]  $\mathbf{I}_{-j40\Omega} = \mathbf{I}_g - \mathbf{I}_1 = 0.28 + j0.04\ \text{A}$

$$Q_{-j40\Omega} = \frac{1}{2} |\mathbf{I}_{-j40\Omega}|^2 (-40) = -1.6\ \text{VAR}(\text{del})$$

$$Q_{j80\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (80) = 6.4\ \text{VAR}(\text{abs})$$

$$\sum Q_{\text{abs}} = 6.4 - 1.6 = 4.8\ \text{VAR} = \sum Q_{\text{dev}}$$

P 10.17 [a]  $Z_1 = 240 + j70 = 250\angle 16.26^\circ\ \Omega$

$$\text{pf} = \cos(16.26^\circ) = 0.96\ \text{lagging}$$

$$\text{rf} = \sin(16.26^\circ) = 0.28$$

$$Z_2 = 160 - j120 = 200/\underline{-36.87^\circ} \Omega$$

$$\text{pf} = \cos(-36.87^\circ) = 0.80 \text{ leading}$$

$$\text{rf} = \sin(-36.87^\circ) = -0.60$$

$$Z_3 = 30 - j40 = 50/\underline{-53.13^\circ} \Omega$$

$$\text{pf} = \cos(-53.13^\circ) = 0.6 \text{ leading}$$

$$\text{rf} = \sin(-53.13^\circ) = -0.8$$

$$\text{[b]} Y = Y_1 + Y_2 + Y_3$$

$$Y_1 = \frac{1}{250/\underline{16.26^\circ}}; \quad Y_2 = \frac{1}{200/\underline{-36.87^\circ}}; \quad Y_3 = \frac{1}{50/\underline{-53.13^\circ}}$$

$$Y = 19.84 + j17.88 \text{ mS}$$

$$Z = \frac{1}{Y} = 37.44/\underline{-42.03^\circ} \Omega$$

$$\text{pf} = \cos(-42.03^\circ) = 0.74 \text{ leading}$$

$$\text{rf} = \sin(-42.03^\circ) = -0.67$$

$$\text{P 10.18 [a]} S_1 = 16 + j18 \text{ kVA}; \quad S_2 = 6 - j8 \text{ kVA}; \quad S_3 = 8 + j0 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 30 + j10 \text{ kVA}$$

$$250\mathbf{I}^* = (30 + j10) \times 10^3; \quad \therefore \mathbf{I} = 120 - j40 \text{ A}$$

$$Z = \frac{250}{120 - j40} = 1.875 + j0.625 \Omega = 1.98/\underline{18.43^\circ} \Omega$$

$$\text{[b]} \text{pf} = \cos(18.43^\circ) = 0.9487 \text{ lagging}$$

$$\text{P 10.19 [a]} \text{ From the solution to Problem 10.18 we have}$$

$$\mathbf{I}_L = 120 - j40 \text{ A(rms)}$$

$$\begin{aligned} \therefore \mathbf{V}_s &= 250/\underline{0^\circ} + (120 - j40)(0.01 + j0.08) = 254.4 + j9.2 \\ &= 254.57/\underline{2.07^\circ} \text{ V(rms)} \end{aligned}$$

$$\text{[b]} |\mathbf{I}_L| = \sqrt{16,000}$$

$$P_\ell = (16,000)(0.01) = 160 \text{ W} \quad Q_\ell = (16,000)(0.08) = 1280 \text{ VAR}$$

$$\text{[c]} P_s = 30,000 + 160 = 30.16 \text{ kW} \quad Q_s = 10,000 + 1280 = 11.28 \text{ kVAR}$$

$$\text{[d]} \eta = \frac{30}{30.16}(100) = 99.47\%$$


P 10.20  $S_T = 4500 - j\frac{4500}{0.96}(0.28) = 4500 - j1312.5 \text{ VA}$

$$S_1 = \frac{2700}{0.8}(0.8 + j0.6) = 2700 + j2025 \text{ VA}$$

$$S_2 = S_T - S_1 = 1800 - j3337.5 = 3791.95 \angle -61.66^\circ \text{ VA}$$

$$\text{pf} = \cos(-61.66^\circ) = 0.4747 \text{ leading}$$

P 10.21

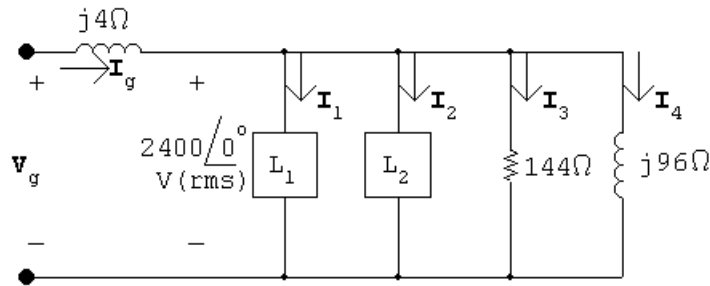

$$2400\mathbf{I}_1^* = 60,000 + j40,000$$

$$\mathbf{I}_1^* = 25 + j16.67; \quad \therefore \mathbf{I}_1 = 25 - j16.67 \text{ A(rms)}$$

$$2400\mathbf{I}_2^* = 20,000 - j10,000$$

$$\mathbf{I}_2^* = 8.33 - j4.167; \quad \therefore \mathbf{I}_2 = 8.33 + j4.167 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{2400\angle 0^\circ}{144} = 16.67 + j0 \text{ A}; \quad \mathbf{I}_4 = \frac{2400\angle 0^\circ}{j96} = 0 - j25 \text{ A}$$

$$\mathbf{I}_g = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 + \mathbf{I}_4 = 50 - j37.5 \text{ A}$$

$$\mathbf{V}_g = 2400 + (j4)(50 - j37.5) = 2550 + j200 = 2557.83 \angle 4.48^\circ \text{ V(rms)}$$

P 10.22 [a]  $S_1 = 60,000 - j70,000 \text{ VA}$

$$S_2 = \frac{|\mathbf{V}_L|^2}{Z_2^*} = \frac{(2500)^2}{24 - j7} = 240,000 + j70,000 \text{ VA}$$

$$S_1 + S_2 = 300,000 \text{ VA}$$


$$2500\mathbf{I}_L^* = 300,000; \quad \therefore \mathbf{I}_L = 120 \angle 0^\circ \text{ A(rms)}$$

$$\begin{aligned} \mathbf{V}_g &= \mathbf{V}_L + \mathbf{I}_L(0.1 + j1) = 2500 + (120)(0.1 + j1) \\ &= 2512 + j120 = 2514.86 \angle 2.735^\circ \text{ V(rms)} \end{aligned}$$


$$\text{[b]} \quad T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

$$\frac{2.735^\circ}{360^\circ} = \frac{t}{16.67 \text{ ms}}; \quad \therefore t = 126.62 \mu\text{s}$$

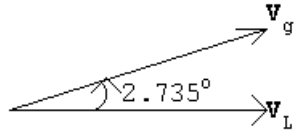**[c]**  $\mathbf{V}_L$  lags  $\mathbf{V}_g$  by  $2.735^\circ$  or  $126.62 \mu\text{s}$



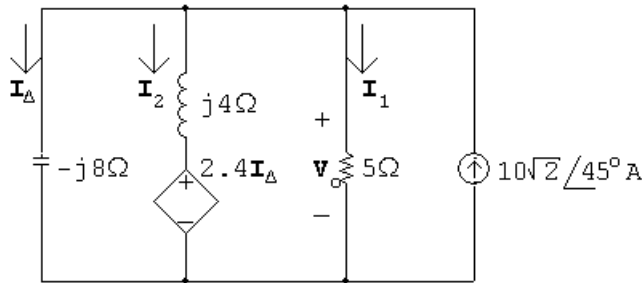P 10.23 **[a]** From the solution to Problem 9.56 we have:



$$\mathbf{V}_o = j80 = 80\angle 90^\circ \text{ V}$$

$$S_g = -\frac{1}{2} \mathbf{V}_o \mathbf{I}_g^* = -\frac{1}{2} (j80)(10 - j10) = -400 - j400 \text{ VA}$$

Therefore, the independent current source is delivering 400 W and 400 magnetizing vars.

$$\mathbf{I}_1 = \frac{\mathbf{V}_o}{5} = j16 \text{ A}$$

$$P_{5\Omega} = \frac{1}{2} (16)^2 (5) = 640 \text{ W}$$

Therefore, the  $8\Omega$  resistor is absorbing 640 W.

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8} = -10 \text{ A}$$

$$Q_{\text{cap}} = \frac{1}{2} (10)^2 (-8) = -400 \text{ VAR}$$

Therefore, the  $-j8\Omega$  capacitor is developing 400 magnetizing vars.

$$2.4\mathbf{I}_\Delta = -24 \text{ V}$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} = \frac{j80 + 24}{j4} \\ &= 20 - j6 \text{ A} = 20.88\angle -16.7^\circ \text{ A} \end{aligned}$$



$$Q_{j4} = \frac{1}{2} |\mathbf{I}_2|^2 (4) = 872 \text{ VAR}$$

Therefore, the  $j4 \Omega$  inductor is absorbing 872 magnetizing vars.


$$\begin{aligned} S_{\text{d.s.}} &= \frac{1}{2} (2.4 \mathbf{I}_\Delta) \mathbf{I}_2^* = \frac{1}{2} (-24)(20 + j6) \\ &= -240 - j72 \text{ VA} \end{aligned}$$

Thus the dependent source is delivering 240 W and 72 magnetizing vars.

$$\text{[b]} \quad \sum P_{\text{gen}} = 400 + 240 = 640 \text{ W} = \sum P_{\text{abs}}$$

$$\text{[c]} \quad \sum Q_{\text{gen}} = 400 + 400 + 72 = 872 \text{ VAR} = \sum Q_{\text{abs}}$$

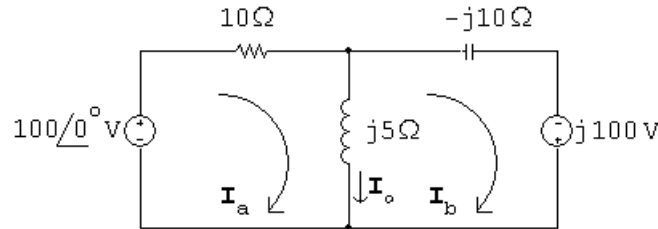P 10.24 [a] From the solution to Problem 9.58 we have



$$\mathbf{I}_a = -j10 \text{ A}; \quad \mathbf{I}_b = -20 + j10 \text{ A}; \quad \mathbf{I}_o = 20 - j20 \text{ A}$$

$$S_{100V} = -\frac{1}{2} (100) \mathbf{I}_a^* = -50(j10) = -j500 \text{ VA}$$

Thus, the 100 V source is developing 500 magnetizing vars.

$$\begin{aligned} S_{j100V} &= -\frac{1}{2} (j100) \mathbf{I}_b^* = -j50(-20 - j10) \\ &= -500 + j1000 \text{ VA} \end{aligned}$$

Thus, the  $j100 \text{ V}$  source is developing 500 W and absorbing 1000 magnetizing vars.

$$P_{10\Omega} = \frac{1}{2} |\mathbf{I}_a|^2 (10) = 500 \text{ W}$$

Thus the  $10 \Omega$  resistor is absorbing 500 W.

$$Q_{-j10\Omega} = \frac{1}{2} |\mathbf{I}_b|^2 (-10) = -2500 \text{ VAR}$$

Thus the  $-j10 \Omega$  capacitor is developing 2500 magnetizing vars.

$$Q_{j5\Omega} = \frac{1}{2} |\mathbf{I}_o|^2 (5) = 2000 \text{ VAR}$$

Thus the  $j5 \Omega$  inductor is absorbing 2000 magnetizing vars.

$$\text{[b]} \quad \sum P_{\text{dev}} = 500 \text{ W} = \sum P_{\text{abs}}$$

$$[c] \sum Q_{\text{dev}} = 500 + 2500 = 3000 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 1000 + 2000 = 3000 \text{ VAR} = \sum Q_{\text{dev}}$$

P 10.25 [a]  $\mathbf{I} = \frac{465 \angle 0^\circ}{124 + j93} = 2.4 - j1.8 = 3 \angle -36.87^\circ \text{ A(rms)}$

$$P = (3)^2(4) = 36 \text{ W}$$

[b]  $Y_L = \frac{1}{120 + j90} = 5.33 - j4 \text{ mS}$

$$\therefore X_C = \frac{1}{-4 \times 10^{-3}} = -250 \Omega$$

[c]  $Z_L = \frac{1}{5.33 \times 10^{-3}} = 187.5 \Omega$


[d]  $\mathbf{I} = \frac{465 \angle 0^\circ}{191.5 + j3} = 2.43 \angle -0.9^\circ \text{ A}$

$$P = (2.43)^2(4) = 23.58 \text{ W}$$

[e]  $\% = \frac{23.58}{36}(100) = 65.5\%$

Thus the power loss after the capacitor is added is 65.6% of the power loss before the capacitor is added.

P 10.26 [a]

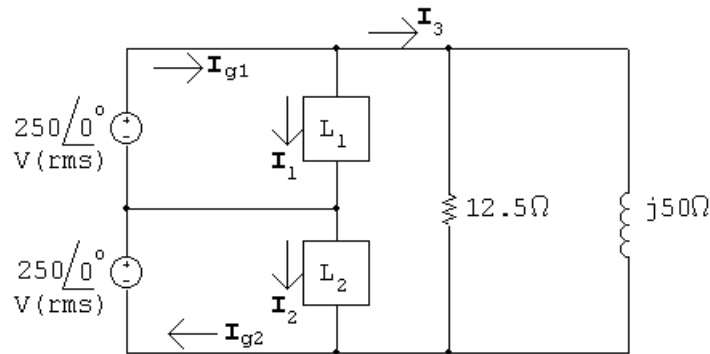

$$250\mathbf{I}_1^* = 7500 + j2500; \quad \therefore \mathbf{I}_1 = 30 - j10 \text{ A(rms)}$$

$$250\mathbf{I}_2^* = 2800 - j9600; \quad \therefore \mathbf{I}_2 = 11.2 + j38.4 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{500}{12.5} + \frac{500}{j50} = 40 - j10 \text{ A(rms)}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 70 - j20 \text{ A}$$

$$S_{g1} = 250(70 + j20) = 17,500 + j5000 \text{ VA}$$

Thus the  $\mathbf{V}_{g1}$  source is delivering 17.5 kW and 5000 magnetizing vars.

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 51.2 + j28.4 \text{ A (rms)}$$

$$S_{g2} = 250(51.2 - j28.4) = 12,800 - j7100 \text{ VA}$$

Thus the  $\mathbf{V}_{g2}$  source is delivering 12.8 kW and absorbing 7100 magnetizing vars.

$$\text{[b]} \quad \sum P_{\text{gen}} = 17.5 + 12.8 = 30.3 \text{ kW}$$

$$\sum P_{\text{abs}} = 7500 + 2800 + \frac{(500)^2}{12.5} = 30.3 \text{ kW} = \sum P_{\text{gen}}$$

$$\sum Q_{\text{del}} = 9600 + 5000 = 14.6 \text{ kVAR}$$

$$\sum Q_{\text{abs}} = 2500 + 7100 + \frac{(500)^2}{50} = 14.6 \text{ kVAR} = \sum Q_{\text{del}}$$

$$\text{P 10.27} \quad S_1 = 1200 + j1196 = 2396 + j0 \text{ VA}$$

$$\therefore \mathbf{I}_1 = \frac{2396}{120} = 19.97 \text{ A}$$

$$S_2 = 860 + j600 + j240 = 1700 + j0 \text{ VA}$$

$$\therefore \mathbf{I}_2 = \frac{1700}{120} = 14.167 \text{ A}$$

$$S_3 = 4474 + j12,200 = 16,674 + j0 \text{ VA}$$


$$\therefore \mathbf{I}_3 = \frac{16,674}{240} = 69.48 \text{ A}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 89.44 \text{ A}$$

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 83.64 \text{ A}$$

Breakers will not trip since both feeder currents are less than 100 A.

P 10.28 [a]

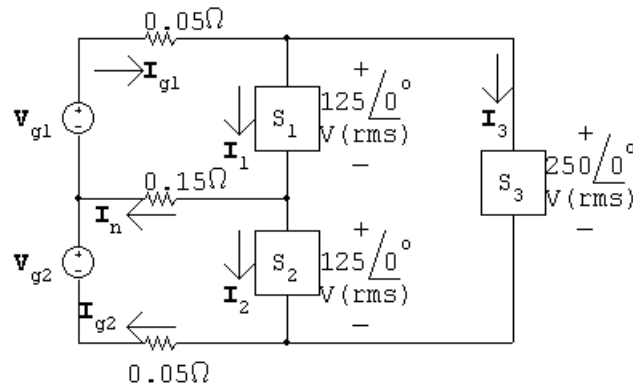

$$\mathbf{I}_1 = \frac{4000 - j1000}{125} = 32 - j8 \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{5000 - j2000}{125} = 40 - j16 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{10,000 + j0}{250} = 40 + j0 \text{ A (rms)}$$

$$\therefore \mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 72 - j8 \text{ A (rms)}$$

$$\mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = -8 + j8 \text{ A (rms)}$$

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 80 - j16 \text{ A (rms)}$$

$$\mathbf{V}_{g1} = 0.05\mathbf{I}_{g1} + 125 + 0.15\mathbf{I}_n = 127.4 + j0.8 \text{ V (rms)}$$

$$\mathbf{V}_{g2} = -0.15\mathbf{I}_n + 125 + 0.05\mathbf{I}_{g2} = 130.2 - j2 \text{ V (rms)}$$

$$S_{g1} = [(127.4 + j0.8)(72 + j8)] = [9166.4 + j1076.8] \text{ VA}$$

$$S_{g2} = [(130.2 - j2)(80 + j16)] = [10,448 + j1923.2] \text{ VA}$$

Note: Both sources are delivering average power and magnetizing VAR to the circuit.

$$\text{[b]} P_{0.05} = |\mathbf{I}_{g1}|^2(0.05) = 262.4 \text{ W}$$

$$P_{0.15} = |\mathbf{I}_n|^2(0.15) = 19.2 \text{ W}$$

$$P_{0.05} = |\mathbf{I}_{g2}|^2(0.05) = 332.8 \text{ W}$$


$$\sum P_{\text{dis}} = 262.4 + 19.2 + 332.8 + 4000 + 5000 + 10,000 = 19,614.4 \text{ W}$$

$$\sum P_{\text{dev}} = 9166.4 + 10,448 = 19,614.4 \text{ W} = \sum P_{\text{dis}}$$

$$\sum Q_{\text{abs}} = 1000 + 2000 = 3000 \text{ VAR}$$

$$\sum Q_{\text{del}} = 1076.8 + 1923.2 = 3000 \text{ VAR} = \sum Q_{\text{abs}}$$

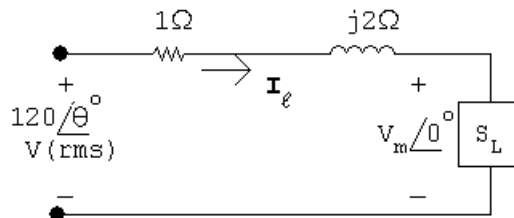P 10.29 [a] Let  $\mathbf{V}_L = V_m \angle 0^\circ$ :



$$S_L = 600(0.8 + j0.6) = 480 + j360 \text{ VA}$$

$$\mathbf{I}_\ell^* = \frac{480}{V_m} + j\frac{360}{V_m}; \quad \mathbf{I}_\ell = \frac{480}{V_m} - j\frac{360}{V_m}$$

$$120/\underline{\theta} = V_m + \left( \frac{480}{V_m} - j\frac{360}{V_m} \right) (1 + j2)$$

$$120V_m/\underline{\theta} = V_m^2 + (480 - j360)(1 + j2) = V_m^2 + 1200 + j600$$

$$120V_m \cos \theta = V_m^2 + 1200; \quad 120V_m \sin \theta = 600$$

$$(120)^2 V_m^2 = (V_m^2 + 1200)^2 + 600^2$$

$$14,400V_m^2 = V_m^4 + 2400V_m^2 + 18 \times 10^5$$

or

$$V_m^4 - 12,000V_m^2 + 18 \times 10^5 = 0$$

Solving,

$$V_m = 108.85 \text{ V and } V_m = 12.326 \text{ V}$$


If  $V_m = 108.85 \text{ V}$ :

$$\sin \theta = \frac{600}{(108.85)(120)} = 0.045935; \quad \therefore \theta = 2.63^\circ$$

If  $V_m = 12.326 \text{ V}$ :

$$\sin \theta = \frac{600}{(12.326)(120)} = 0.405647; \quad \therefore \theta = 23.93^\circ$$

**[b]**

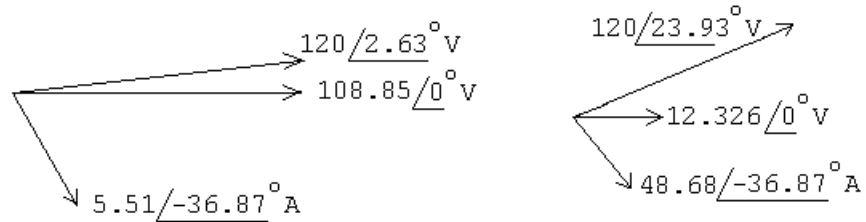

P 10.30 **[a]**  $S_L = 20,000(0.85 + j0.53) = 17,000 + j10,535.65 \text{ VA}$

$$125\mathbf{I}_L^* = (17,000 + j10,535.65); \quad \mathbf{I}_L^* = 136 + j84.29 \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = 136 - j84.29 \text{ A(rms)}$$

$$\begin{aligned} \mathbf{V}_s &= 125 + (136 - j84.29)(0.01 + j0.08) = 133.10 + j10.04 \\ &= 133.48/\underline{4.31^\circ} \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s| = 133.48 \text{ V(rms)}$$

**[b]**  $P_\ell = |\mathbf{I}_\ell|^2(0.01) = (160)^2(0.01) = 256 \text{ W}$

$$\begin{aligned} \text{[c]} \quad \frac{(125)^2}{X_C} &= -10,535.65; & X_C &= -1.483 \, \Omega \\ -\frac{1}{\omega C} &= -1.48; & C &= \frac{1}{(1.48)(120\pi)} = 1788.59 \, \mu\text{F} \end{aligned}$$


$$\text{[d]} \quad \mathbf{I}_\ell = 136 + j0 \, \text{A(rms)}$$

$$\begin{aligned} \mathbf{V}_s &= 125 + 136(0.01 + j0.08) = 126.36 + j10.88 \\ &= 126.83 \angle 4.92^\circ \, \text{V(rms)} \end{aligned}$$

$$|\mathbf{V}_s| = 126.83 \, \text{V(rms)}$$

$$\text{[e]} \quad P_\ell = (136)^2(0.01) = 184.96 \, \text{W}$$

P 10.31

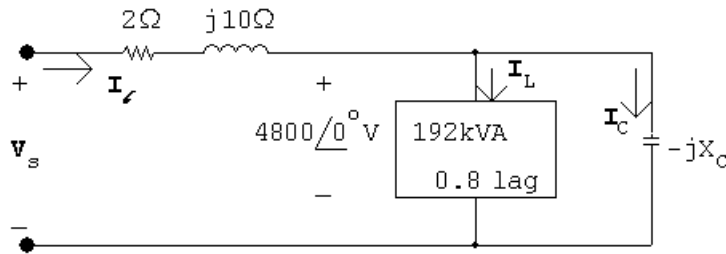

$$\mathbf{I}_L = \frac{153,600 - j115,200}{4800} = 32 - j24 \, \text{A(rms)}$$

$$\mathbf{I}_C = \frac{4800}{-jX_C} = j\frac{4800}{X_C} = jI_C$$

$$\mathbf{I}_\ell = 32 - j24 + jI_C = 32 + j(I_C - 24)$$

$$\begin{aligned} \mathbf{V}_s &= 4800 + (2 + j10)[32 + j(I_C - 24)] \\ &= (5104 - 10I_C) + j(272 + 2I_C) \end{aligned}$$

$$|\mathbf{V}_s|^2 = (5104 - 10I_C)^2 + (272 + 2I_C)^2 = (4800)^2$$

$$\therefore 104I_C^2 - 100,992I_C + 3,084,800 = 0$$

$$\text{Solving, } \mathbf{I}_C = 31.57 \, \text{A(rms); } \mathbf{I}_C = 939.51 \, \text{A(rms)}$$

\*Select the smaller value of  $I_C$  to minimize the magnitude of  $I_\ell$ .

$$\therefore X_C = -\frac{4800}{31.57} = -152.04$$

$$\therefore C = \frac{1}{(152.04)(120\pi)} = 17.45 \, \mu\text{F}$$

P 10.32  $Z_L = |Z_L| \angle \theta^\circ = |Z_L| \cos \theta^\circ + j|Z_L| \sin \theta^\circ$

Thus  $|\mathbf{I}| = \frac{|\mathbf{V}_{Th}|}{\sqrt{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}}$

Therefore  $P = \frac{0.5|\mathbf{V}_{Th}|^2 |Z_L| \cos \theta}{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}$

Let  $D =$  demoninator in the expression for  $P$ , then

$$\frac{dP}{d|Z_L|} = \frac{(0.5|\mathbf{V}_{Th}|^2 \cos \theta)(D \cdot 1 - |Z_L| dD/d|Z_L|)}{D^2}$$

$$\frac{dD}{d|Z_L|} = 2(R_{Th} + |Z_L| \cos \theta) \cos \theta + 2(X_{Th} + |Z_L| \sin \theta) \sin \theta$$


$$\frac{dP}{d|Z_L|} = 0 \quad \text{when} \quad D = |Z_L| \left( \frac{dD}{d|Z_L|} \right)$$

Substituting the expressions for  $D$  and  $(dD/d|Z_L|)$  into this equation gives us the relationship  $R_{Th}^2 + X_{Th}^2 = |Z_L|^2$  or  $|Z_{Th}| = |Z_L|$ .

P 10.33 [a]  $Z_{Th} = j40 \parallel 40 - j40 = 20 - j20$

$$\therefore Z_L = Z_{Th}^* = 20 + j20 \Omega$$

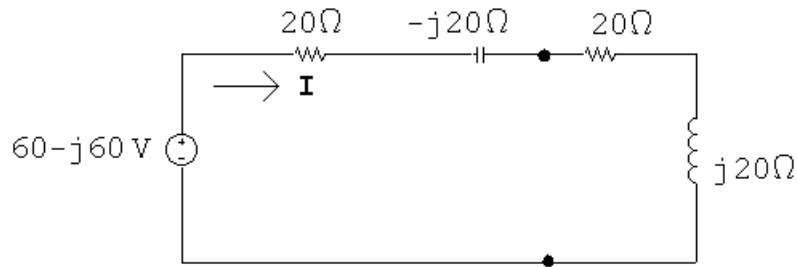[b]  $\mathbf{V}_{Th} = \frac{40}{40 + j40}(120) = 60 - j60 \text{ V}$



$$\mathbf{I} = \frac{60 - j60}{40} = 1.5 - j1.5 \text{ A}$$

$$P_{load} = \frac{1}{2} |\mathbf{I}|^2 (20) = 45 \text{ W}$$

P 10.34 [a]  $\frac{115.2 + j33.6 - 240}{Z_{Th}} + \frac{115.2 + j33.6}{80 - j60} = 0$

$$\therefore Z_{Th} = 40 - j100 \Omega$$

$$\therefore Z_L = 40 + j100 \Omega$$


$$\text{[b] } \mathbf{I} = \frac{240}{80} = 3 \text{ A(rms)}$$

$$P = (3)^2(40) = 360 \text{ W}$$

$$\text{P 10.35 [a] } Z_{\text{Th}} = [(3 + j4) \parallel -j8] + 7.32 - j17.24 = 15 - j15 \Omega$$

$$\therefore R = |Z_{\text{Th}}| = 21.21 \Omega$$

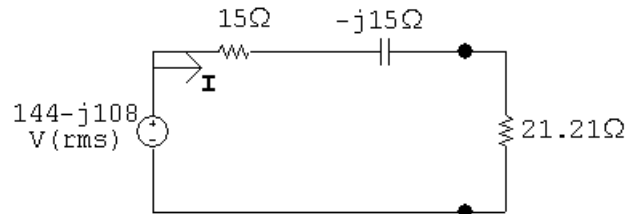
$$\text{[b] } \mathbf{V}_{\text{Th}} = \frac{-j8}{3 - j4}(112.5) = 144 - j108 \text{ V(rms)}$$



$$\mathbf{I} = \frac{144 - j108}{35.21 - j15} = 4.45 - j1.14$$

$$P = |\mathbf{I}|^2(21.21) = 447.35 \text{ W}$$

P 10.36 [a] Open circuit voltage:

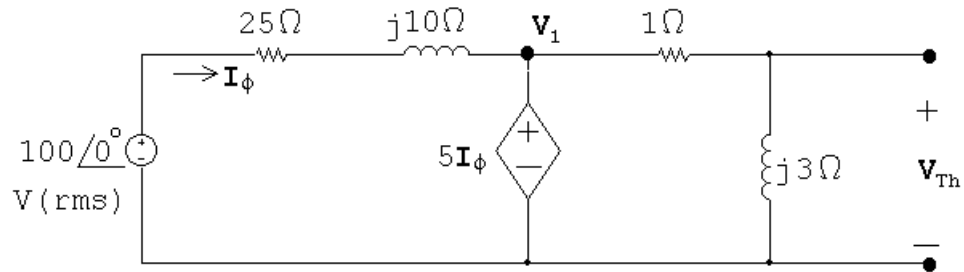

$$\mathbf{V}_1 = 5\mathbf{I}_\phi = 5 \frac{100 - 5\mathbf{I}_\phi}{25 + j10}$$


$$(25 + j10)\mathbf{I}_\phi = 100 - 5\mathbf{I}_\phi$$

$$\mathbf{I}_\phi = \frac{100}{30 + j10} = 3 - j1 \text{ A}$$

$$\mathbf{V}_{\text{Th}} = \frac{j3}{1 + j3}(5\mathbf{I}_\phi) = 15 \angle 0^\circ \text{ V}$$



Short circuit current:

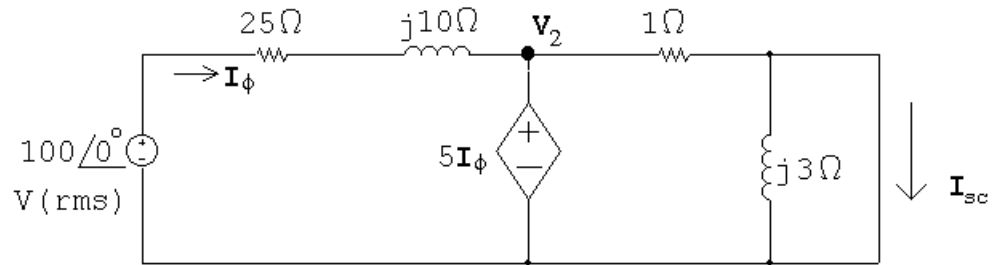


$$\mathbf{V}_2 = 5\mathbf{I}_\phi = \frac{100 - 5\mathbf{I}_\phi}{25 + j10}$$

$$\mathbf{I}_\phi = 3 - j1 \text{ A}$$

$$\mathbf{I}_{sc} = \frac{5\mathbf{I}_\phi}{1} = 15 - j5 \text{ A}$$

$$\mathbf{Z}_{Th} = \frac{15}{15 - j5} = 0.9 + j0.3 \Omega$$

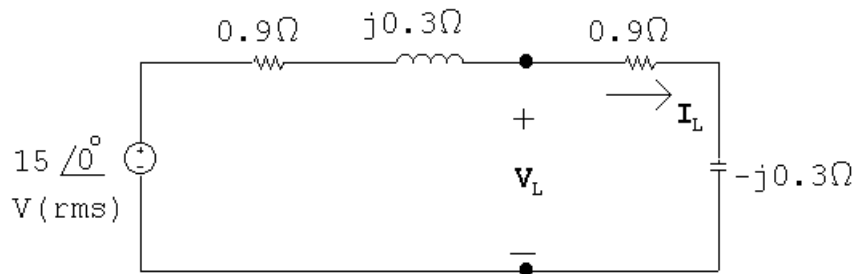
$$\mathbf{Z}_L = \mathbf{Z}_{Th}^* = 0.9 - j0.3 \Omega$$



$$\mathbf{I}_L = \frac{15}{1.8} = 8.33 \text{ A(rms)}$$

$$P = |\mathbf{I}_L|^2(0.9) = 62.5 \text{ W}$$

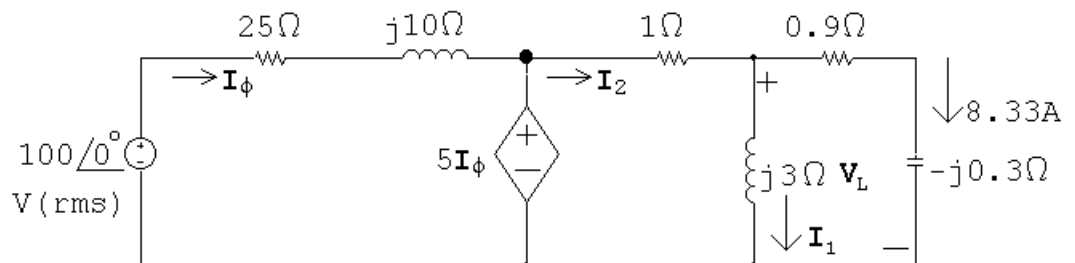**[b]**  $\mathbf{V}_L = (0.9 - j0.3)(8.33) = 7.5 - j2.5 \text{ V(rms)}$



$$\mathbf{I}_1 = \frac{\mathbf{V}_L}{j3} = -0.833 - j2.5 \text{ A(rms)}$$

$$\mathbf{I}_2 = \mathbf{I}_1 + \mathbf{I}_L = 7.5 - j2.5 \text{ A(rms)}$$

$$5\mathbf{I}_\phi = \mathbf{I}_2 + \mathbf{V}_L \quad \therefore \quad \mathbf{I}_\phi = 3 - j1 \text{ A}$$

$$\mathbf{I}_{d.s.} = \mathbf{I}_\phi - \mathbf{I}_2 = -4.5 + j1.5 \text{ A}$$

$$S_g = -100(3 + j1) = -300 - j100 \text{ VA}$$

$$S_{d.s.} = 5(3 - j1)(-4.5 - j1.5) = -75 + j0 \text{ VA}$$

$$P_{dev} = 300 + 75 = 375 \text{ W}$$

$$\% \text{ developed} = \frac{62.5}{375}(100) = 16.67\%$$

Checks:

$$P_{25\Omega} = (10)(25) = 250 \text{ W}$$

$$P_{1\Omega} = (62.5)(1) = 62.5 \text{ W}$$

$$P_{0.9\Omega} = 62.5 \text{ W}$$

$$\sum P_{abs} = 250 + 62.5 + 62.5 = 375 \text{ W} = \sum P_{dev}$$

$$Q_{j10} = (10)(10) = 100 \text{ VAR}$$


$$Q_{j3} = (6.94)(3) = 20.83 \text{ VAR}$$

$$Q_{-j0.3} = (69.4)(-0.3) = -20.83 \text{ VAR}$$

$$Q_{source} = -100 \text{ VAR}$$

$$\sum Q = 100 + 20.83 - 20.83 - 100 = 0$$

P 10.37 [a] Open circuit voltage:

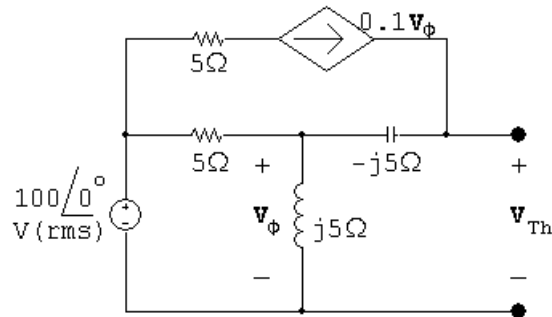


$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} - 0.1\mathbf{V}_\phi = 0$$

$$\therefore \mathbf{V}_\phi = 40 + j80 \text{ V(rms)}$$

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_\phi + 0.1\mathbf{V}_\phi(-j5) = \mathbf{V}_\phi(1 - j0.5) = 80 + j60 \text{ V(rms)}$$

Short circuit current:

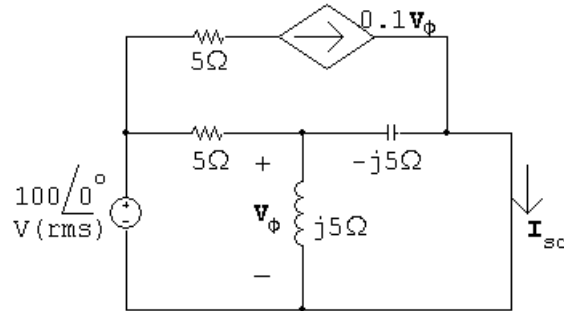

$$\mathbf{I}_{\text{sc}} = 0.1\mathbf{V}_\phi + \frac{\mathbf{V}_\phi}{-j5} = (0.1 + j0.2)\mathbf{V}_\phi$$

$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} + \frac{\mathbf{V}_\phi}{-j5} = 0$$


$$\therefore \mathbf{V}_\phi = 100 \text{ V(rms)}$$

$$\mathbf{I}_{\text{sc}} = (0.1 + j0.2)(100) = 10 + j20 \text{ A(rms)}$$

$$Z_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{80 + j60}{10 + j20} = 4 - j2 \Omega$$

$$\therefore R_o = |Z_{\text{Th}}| = 4.47 \Omega$$


[b]

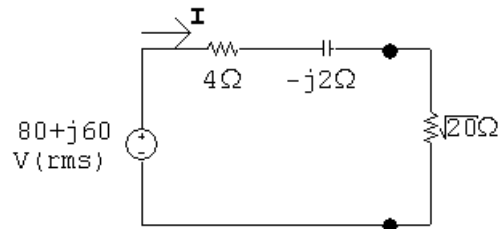

$$\mathbf{I} = \frac{80 + j60}{4 + \sqrt{20} - j2} = 7.36 + j8.82 \text{ A(rms)}$$

$$P = (11.49)^2(\sqrt{20}) = 590.17 \text{ W}$$


[c]

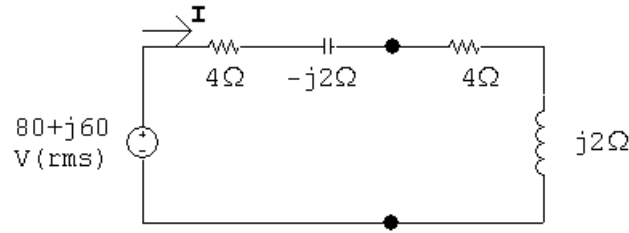

$$\mathbf{I} = \frac{80 + j60}{8} = 10 + j7.5 \text{ A(rms)}$$

$$P = (10^2 + 7.5^2)(4) = 625 \text{ W}$$

[d]

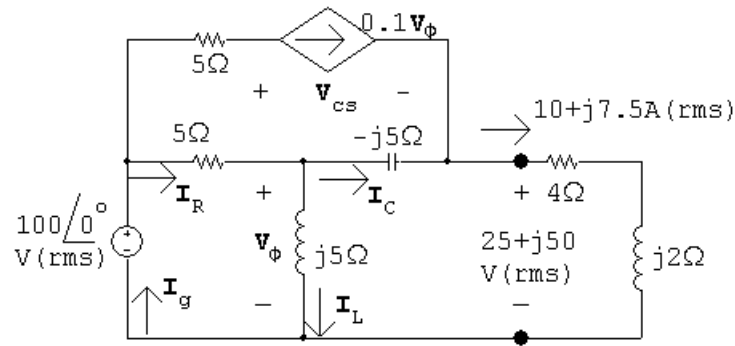

$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} + \frac{\mathbf{V}_\phi - (25 + j50)}{-j5} = 0$$

$$\mathbf{V}_\phi = 50 + j25 \text{ V(rms)}$$

$$0.1\mathbf{V}_\phi = 5 + j2.5$$

$$5 + j2.5 + \mathbf{I}_C = 10 + j7.5$$

$$\mathbf{I}_C = 5 + j5 \text{ A(rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_\phi}{j5} = 5 - j10 \text{ A(rms)}$$

$$\mathbf{I}_R = \mathbf{I}_C + \mathbf{I}_L = 10 - j5 \text{ A(rms)}$$

$$\mathbf{I}_g = \mathbf{I}_R + 0.1\mathbf{V}_\phi = 15 - j2.5 \text{ A(rms)}$$

$$S_g = -100\mathbf{I}_g^* = -1500 - j250 \text{ VA}$$

$$100 = 5(5 + j2.5) + \mathbf{V}_{cs} + 25 + j50 \quad \therefore \quad \mathbf{V}_{cs} = 50 - j62.5 \text{ V(rms)}$$

$$S_{cs} = (50 - j62.5)(5 - j2.5) = 93.75 - j437.5 \text{ VA}$$

Thus,

$$\sum P_{\text{dev}} = 1500$$

$$\% \text{ delivered to } R_o = \frac{625}{1500}(100) = 41.67\%$$


P 10.38 [a] First find the Thévenin equivalent:

$$j\omega L = j3000\ \Omega$$

$$Z_{\text{Th}} = 6000 \parallel 12,000 + j3000 = 4000 + j3000\ \Omega$$

$$\mathbf{V}_{\text{Th}} = \frac{12,000}{6000 + 12,000}(180) = 120\angle 0^\circ\ \text{V}$$

$$\frac{-j}{\omega C} = -j1000\ \Omega$$

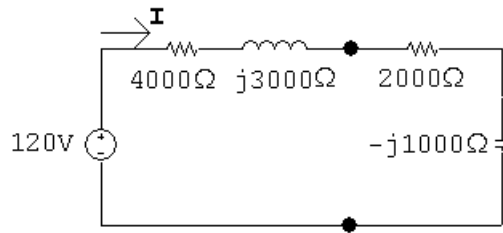

$$\mathbf{I} = \frac{120}{6000 + j2000} = 18 - j6\ \text{mA}$$

$$P = \frac{1}{2}|\mathbf{I}|^2(2000) = 360\ \text{mW}$$

[b] Set  $C_o = 0.1\ \mu\text{F}$  so  $-j/\omega C = -j2000\ \Omega$   $j3000 - j2000 = j1000\ \Omega$   
Set  $R_o$  as close as possible to

$$R_o = \sqrt{4000^2 + 1000^2} = 4123.1\ \Omega$$

$$\therefore R_o = 4000\ \Omega$$

$$\text{[c] } \mathbf{I} = \frac{120}{8000 + j1000} = 14.77 - j1.85\ \text{mA}$$

$$P = \frac{1}{2}|\mathbf{I}|^2(4000) = 443.1\ \text{mW}$$

Yes;  $443.1\ \text{mW} > 360\ \text{mW}$

$$\text{[d] } \mathbf{I} = \frac{120}{8000} = 15\ \text{mA}$$

$$P = \frac{1}{2}(0.015)^2(4000) = 450\ \text{mW}$$

[e]  $R_o = 4000\ \Omega$ ;  $C_o = 66.67\ \text{nF}$

[f] Yes;  $450\ \text{mW} > 443.1\ \text{mW}$

P 10.39 [a] Set  $C_o = 0.1 \mu\text{F}$ , so  $-j/\omega C = -j2000 \Omega$ ; also set  $R_o = 4123.1 \Omega$

$$\mathbf{I} = \frac{120}{8123.1 + j1000} = 14.55 - j1.79 \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 (4123.1) = 443.18 \text{ mW}$$

[b] Yes;  $443.18 \text{ mW} > 360 \text{ mW}$

[c] Yes;  $443.18 \text{ mW} < 450 \text{ mW}$

P 10.40 [a]  $\frac{1}{\omega C} = 100 \Omega$ ;  $C = \frac{1}{(100)(120\pi)} = 26.53 \mu\text{F}$

$$[\text{b}] \mathbf{I}_{\text{wo}} = \frac{13,800}{300} + \frac{13,800}{j100} = 46 - j138 \text{ A(rms)}$$

$$\begin{aligned} \mathbf{V}_{\text{swo}} &= 13,800 + (46 - j138)(1.5 + j12) = 15,525 + j345 \\ &= 15,528.83 / \underline{1.27^\circ} \text{ V(rms)} \end{aligned}$$

$$\mathbf{I}_{\text{w}} = \frac{13,800}{300} = 46 \text{ A(rms)}$$

$$\mathbf{V}_{\text{sw}} = 13,800 + 46(1.5 + j12) = 13,869 + j552 = 13,879.98 / \underline{2.28^\circ} \text{ V(rms)}$$

$$\% \text{ increase} = \left( \frac{15,528.82}{13,879.98} - 1 \right) (100) = 11.88\%$$

$$[\text{c}] P_{\ell\text{wo}} = |46 - j138|^2 1.5 = 31.74 \text{ kW}$$

$$P_{\ell\text{w}} = 46^2 (1.5) = 3174 \text{ W}$$

$$\% \text{ increase} = \left( \frac{31,740}{3174} - 1 \right) (100) = 900\%$$

P 10.41 [a]  $S_o = \text{original load} = 1600 + j \frac{1600}{0.8} (0.6) = 1600 + j1200 \text{ kVA}$

$$S_f = \text{final load} = 1920 + j \frac{1920}{0.96} (0.28) = 1920 + j560 \text{ kVA}$$

$$\therefore Q_{\text{added}} = 560 - 1200 = -640 \text{ kVAR}$$

[b] deliver

$$[\text{c}] S_a = \text{added load} = 320 - j640 = 715.54 / \underline{-63.43^\circ} \text{ kVA}$$

$$\text{pf} = \cos(-63.43) = 0.4472 \text{ leading}$$

$$\text{[d]} \quad \mathbf{I}_L^* = \frac{(1600 + j1200) \times 10^3}{2400} = 666.67 + j500 \text{ A}$$

$$\mathbf{I}_L = 666.67 - j500 = 833.33 \angle -36.87^\circ \text{ A(rms)}$$

$$|\mathbf{I}_L| = 833.33 \text{ A(rms)}$$

$$\text{[e]} \quad \mathbf{I}_L^* = \frac{(1920 + j560) \times 10^3}{2400} = 800 + j233.33$$

$$\mathbf{I}_L = 800 - j233.33 = 833.33 \angle -16.26^\circ \text{ A(rms)}$$

$$|\mathbf{I}_L| = 833.33 \text{ A(rms)}$$

P 10.42 [a]  $P_{\text{before}} = P_{\text{after}} = (833.33)^2(0.05) = 34,722.22 \text{ W}$


$$\begin{aligned} \text{[b]} \quad \mathbf{V}_s(\text{before}) &= 2400 + (666.67 - j500)(0.05 + j0.4) \\ &= 2633.33 + j241.67 = 2644.4 \angle 5.24^\circ \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s(\text{before})| = 2644.4 \text{ V(rms)}$$

$$\begin{aligned} \mathbf{V}_s(\text{after}) &= 2400 + (800 + j233.33)(0.05 + j0.4) \\ &= 2346.67 + j331.67 = 2369.99 \angle 8.04^\circ \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s(\text{after})| = 2369.99 \text{ V(rms)}$$

P 10.43 [a]

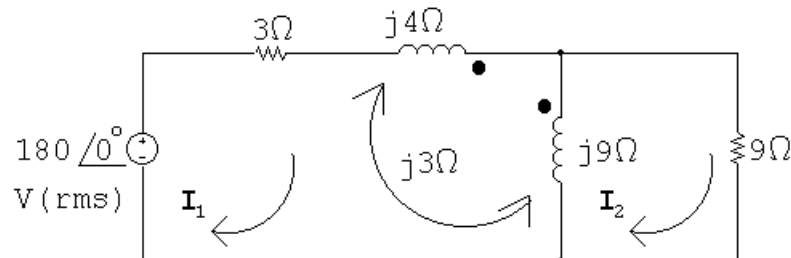

$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_2 - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_2) - j3\mathbf{I}_1$$

$$0 = 9\mathbf{I}_2 + j9(\mathbf{I}_2 - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_1 = 18 - j18 \text{ A(rms)}; \quad \mathbf{I}_2 = 12 \angle 0^\circ \text{ A(rms)}$$


$$\therefore \mathbf{V}_o = (12)(9) = 108 \angle 0^\circ \text{ V(rms)}$$

[b]  $P = (12)^2(9) = 1296 \text{ W}$

[c]  $S_g = -(180)(18 + j18) = -3240 - j3240 \text{ VA} \quad \therefore P_g = -3240 \text{ W}$

$$\% \text{ delivered} = \frac{1296}{3240}(100) = 40\%$$

P 10.44 [a] Open circuit voltage:

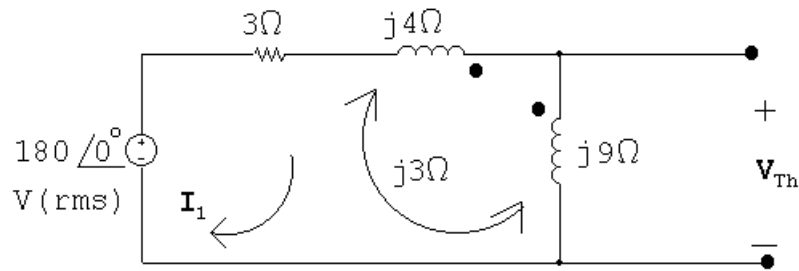


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 - j3\mathbf{I}_1 + j9\mathbf{I}_1 - j3\mathbf{I}_1$$

$$\therefore \mathbf{I}_1 = \frac{180}{3 + j7} = 9.31 - j21.72 \text{ A(rms)}$$

$$\mathbf{V}_{Th} = j9\mathbf{I}_1 - j3\mathbf{I}_1 = j6\mathbf{I}_1 = 130.34 + j55.86 \text{ V} = 141.81 \angle 23.20^\circ \text{ V(rms)}$$

Short circuit current:

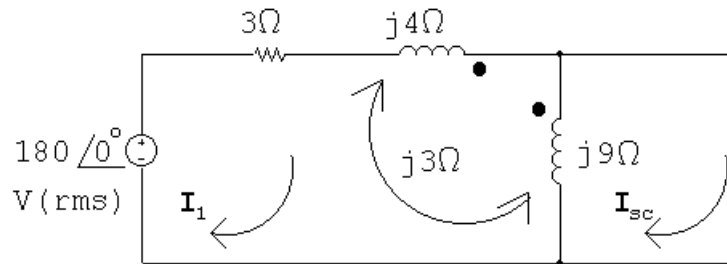


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_{sc} - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_{sc}) - j3\mathbf{I}_1$$

$$0 = j9(\mathbf{I}_{sc} - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_{sc} = 20 - j20 \text{ A} \quad \mathbf{I}_1 = 30 - j20 \text{ A}$$
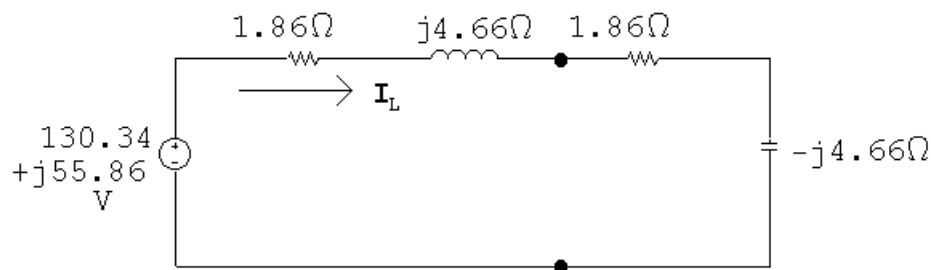
$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{130.34 + j55.86}{20 - j20} = 1.86 + j4.66 \Omega$$



$$\mathbf{I}_L = \frac{130.34 + j55.86}{3.72} = 35 + j15 = 38.08 \angle 23.20^\circ \text{ A}$$




$$P_L = (38.12)^2(1.86) = 2700 \text{ W}$$

$$\text{[b]} \quad \mathbf{I}_1 = \frac{Z_o + j9}{j6} \mathbf{I}_2 = \frac{1.86 - j4.66 + j9}{j6} (35 + j15) = 30 \angle 0^\circ \text{ A(rms)}$$

$$P_{\text{dev}} = (180)(30) = 5400 \text{ W}$$

P 10.45 [a]

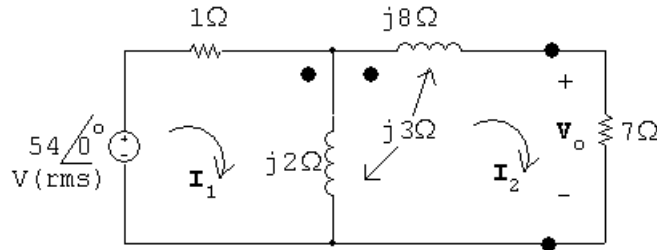

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) + j3\mathbf{I}_2$$

$$0 = 7\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_1) - j3\mathbf{I}_2 + j8\mathbf{I}_2 + j3(\mathbf{I}_1 - \mathbf{I}_2)$$

Solving,

$$\mathbf{I}_1 = 12 - j21 \text{ A(rms)}; \quad \mathbf{I}_2 = -3 \text{ A(rms)}$$


$$\mathbf{V}_o = 7\mathbf{I}_2 = -21 \angle 180^\circ \text{ V(rms)}$$

$$\text{[b]} \quad P = |\mathbf{I}_2|^2(7) = 63 \text{ W}$$

$$\text{[c]} \quad P_g = (54)(12) = 648 \text{ W}$$

$$\% \text{ delivered} = \frac{63}{648}(100) = 9.72\%$$

P 10.46 [a]

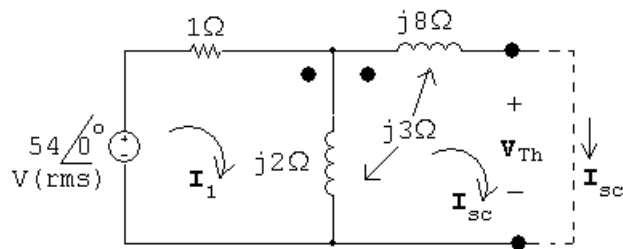

Open circuit:

$$\mathbf{V}_{\text{Th}} = -j3\mathbf{I}_1 + j2\mathbf{I}_1 = -j\mathbf{I}_1$$

$$\mathbf{I}_1 = \frac{54}{1 + j2} = 10.8 - j21.6 \text{ A}$$

$$\mathbf{V}_{\text{Th}} = -21.6 - j10.8 \text{ V}$$

Short circuit:

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_{sc}) + j3\mathbf{I}_{sc}$$

$$0 = j2(\mathbf{I}_{sc} - \mathbf{I}_1) - j3\mathbf{I}_{sc} + j8\mathbf{I}_{sc} + j3(\mathbf{I}_1 - \mathbf{I}_{sc})$$


Solving,

$$\mathbf{I}_{sc} = -3.32 + j5.82$$

$$Z_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{-21.6 - j10.8}{-3.32 + j5.82} = 0.2 + 3.6j = 3.6 \angle 86.82^\circ \Omega$$

$$\therefore R_L = |Z_{Th}| = 3.606 \Omega$$


[b]

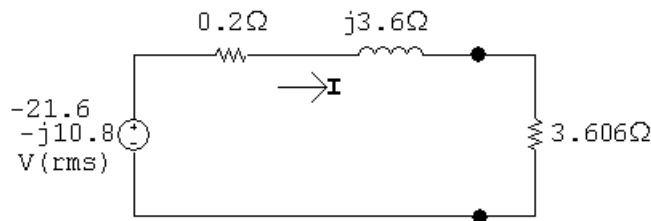

$$\mathbf{I} = \frac{-21.6 - j10.8}{3.806 + j3.6} = 4.610 \angle 163.2^\circ \text{ A}$$

$$P = |\mathbf{I}|^2(3.6) = 76.6 \text{ W, which is greater than when } R_L = 7 \Omega$$

P 10.47 [a]

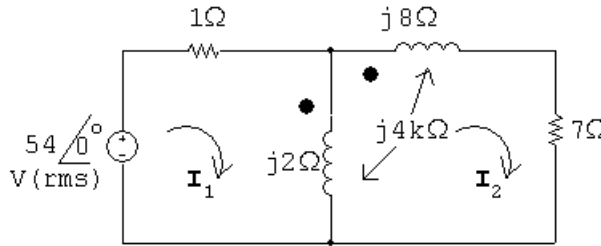

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) + j4k\mathbf{I}_2$$

$$0 = 7\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_1) - j4k\mathbf{I}_2 + j8\mathbf{I}_2 + j4k(\mathbf{I}_1 - \mathbf{I}_2)$$

Place the equations in standard form:

$$54 = (1 + j2)\mathbf{I}_1 + j(4k - 2)\mathbf{I}_2$$

$$0 = j(4k - 2)\mathbf{I}_1 + [7 + j(10 - 8k)]\mathbf{I}_2$$

$$\mathbf{I}_1 = \frac{54 - \mathbf{I}_2 j(4k - 2)}{(1 + j2)}$$

Substituting,

$$\mathbf{I}_2 = -\frac{j54(4k - 2)}{[7 + j(10 - 8k)](1 + j2) + (4k - 2)^2}$$

For  $\mathbf{V}_o = 0$ ,  $\mathbf{I}_2 = 0$ , so if  $4k - 2 = 0$ , then  $k = 0.5$ .

**[b]** When  $\mathbf{I}_2 = 0$


$$\mathbf{I}_1 = \frac{54}{1 + j2} = 10.8 - j21.6 \text{ A(rms)}$$

$$P_g = (54)(10.8) = 583.2 \text{ W}$$


Check:

$$P_{\text{loss}} = |\mathbf{I}_1|^2(1) = 583.2 \text{ W}$$

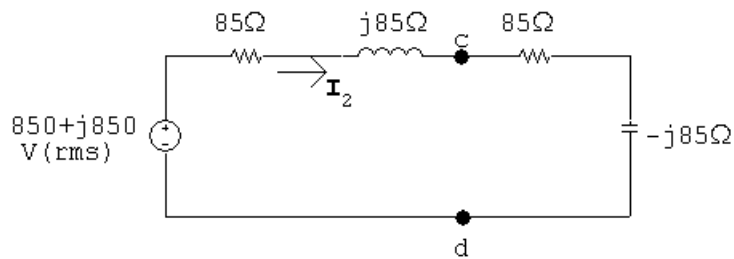P 10.48 **[a]** From Problem 9.67,  $Z_{\text{Th}} = 85 + j85 \Omega$  and  $\mathbf{V}_{\text{Th}} = 850 + j850 \text{ V}$ . Thus, for maximum power transfer,  $Z_L = Z_{\text{Th}}^* = 85 - j85 \Omega$ :


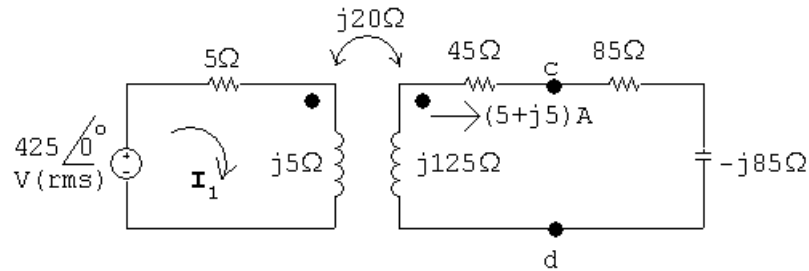
$$\mathbf{I}_2 = \frac{850 + j850}{170} = 5 + j5 \text{ A}$$



$$425\angle 0^\circ = (5 + j5)\mathbf{I}_1 - j20(5 + j5)$$

$$\therefore \mathbf{I}_1 = \frac{325 + j100}{5 + j5} = 42.5 - j22.5 \text{ A}$$

$$S_g(\text{del}) = 425(42.5 + j22.5) = 18,062.5 + j9562.5 \text{ VA}$$

$$P_g = 18,062.5 \text{ W}$$

**[b]**  $P_{\text{loss}} = |\mathbf{I}_1|^2(5) + |\mathbf{I}_2|^2(45) = 11,562.5 + 2250 = 13,812.5 \text{ W}$

$$\% \text{ loss in transformer} = \frac{18,062.5 - 13,812.5}{18,062.5}(100) = 23.53\%$$

P 10.49 [a] From Problem 9.70,

$$Z_{ab} = 100 + j136.26 \quad \text{so}$$

$$\mathbf{I}_1 = \frac{50}{100 + j13.74 + 100 + j136.26} = \frac{50}{200 + j150} = 160 - j120 \text{ mA}$$

$$\mathbf{I}_2 = \frac{j\omega M}{Z_{22}} \mathbf{I}_1 = \frac{j270}{800 + j600} (0.16 - j0.12) = 51.84 + j15.12 \text{ mA}$$

$$\mathbf{V}_L = (300 + j100)(51.84 + j15.12)10^{-3} = 14.04 + j9.72 \text{ V}$$

$$|\mathbf{V}_L| = 17.08 \text{ V}$$


[b]  $P_g(\text{ideal}) = 50(0.16) = 8 \text{ W}$

$$P_g(\text{practical}) = 8 - |\mathbf{I}_1|^2(100) = 4 \text{ W}$$

$$P_L = |\mathbf{I}_2|^2(300) = 874.8 \text{ mW}$$

$$\% \text{ delivered} = \frac{0.8748}{4}(100) = 21.87\%$$

P 10.50 [a]

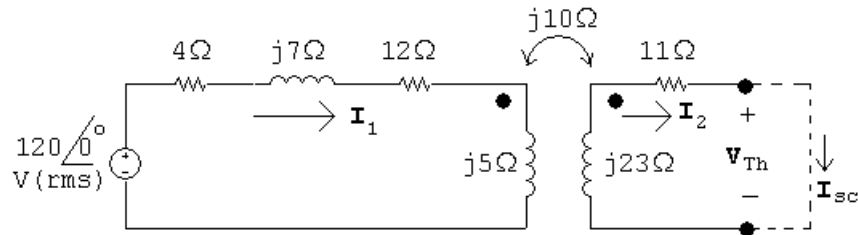

Open circuit:

$$\mathbf{V}_{Th} = \frac{120}{16 + j12}(j10) = 36 + j48 \text{ V}$$

Short circuit:

$$(16 + j12)\mathbf{I}_1 - j10\mathbf{I}_{sc} = 120$$

$$-j10\mathbf{I}_1 + (11 + j23)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 2.4\angle 0^\circ \text{ A}$$

$$Z_{Th} = \frac{36 + j48}{2.4} = 15 + j20 \Omega$$

$$\therefore Z_L = Z_{Th}^* = 15 - j20 \Omega$$

$$\mathbf{I}_L = \frac{\mathbf{V}_{Th}}{Z_{Th} + Z_L} = \frac{36 + j48}{30} = 1.2 + j1.6 \text{ A(rms)} = 2.0\angle 53.13^\circ \text{ A(rms)}$$

$$P_L = |\mathbf{I}_L|^2(15) = 60 \text{ W}$$


$$\text{[b]} \quad \mathbf{I}_1 = \frac{Z_{22}\mathbf{I}_2}{j\omega M} = \frac{26 + j3}{j10}(1.2 + j1.6) = 5.23 \angle -30.29^\circ \text{ A (rms)}$$

$$P_{\text{transformer}} = (120)(5.23) \cos(-30.29^\circ) - (5.23)^2(4) = 432.8 \text{ W}$$

$$\% \text{ delivered} = \frac{60}{432.8}(100) = 13.86\%$$

P 10.51 [a]  $j\omega L_1 = j(10,000)(1 \times 10^{-3}) = j10 \Omega$
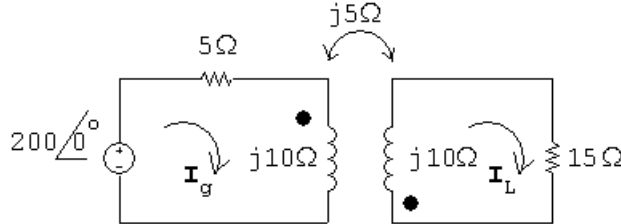
$$j\omega L_2 = j(10,000)(1 \times 10^{-3}) = j10 \Omega$$



$$200 = (5 + j10)\mathbf{I}_g + j5\mathbf{I}_L$$

$$0 = j5\mathbf{I}_g + (15 + j10)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 10 - j15 \text{ A}; \quad \mathbf{I}_L = -5 \text{ A}$$

Thus,

$$i_g = 18.03 \cos(10,000t - 56.31^\circ) \text{ A}$$

$$i_L = 5 \cos(10,000t - 180^\circ) \text{ A}$$

[b]  $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.5}{\sqrt{1}} = 0.5$

[c] When  $t = 50\pi \mu\text{s}$ :

$$10,000t = (10,000)(50\pi) \times 10^{-6} = 0.5\pi \text{ rad} = 90^\circ$$

$$i_g(50\pi \mu\text{s}) = 18.03 \cos(90^\circ - 56.31^\circ) = 15 \text{ A}$$

$$i_L(50\pi \mu\text{s}) = 5 \cos(90^\circ - 180^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(10^{-3})(15)^2 + 0 + 0 = 112.5 \text{ mJ}$$

When  $t = 100\pi \mu\text{s}$ :

$$10,000t = (10^4)(100\pi) \times 10^{-6} = \pi = 180^\circ$$

$$i_g(100\pi \mu\text{s}) = 18.03 \cos(180^\circ - 56.31^\circ) = -10 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 5 \cos(180^\circ - 180^\circ) = 5 \text{ A}$$

$$w = \frac{1}{2}(10^{-3})(10)^2 + \frac{1}{2}(10^{-3})(5)^2 + 0.5 \times 10^{-3}(-10)(5) = 37.5 \text{ mJ}$$

**[d]** From (a),  $I_m = 5$  A,

$$\therefore P = \frac{1}{2}(5)^2(15) = 187.5 \text{ W}$$

**[e]** Open circuit:

$$\mathbf{V}_{\text{Th}} = \frac{200}{5 + j10}(-j5) = -80 - j40 \text{ V}$$

Short circuit:

$$200 = (5 + j10)\mathbf{I}_1 + j5\mathbf{I}_{\text{sc}}$$

$$0 = j10\mathbf{I}_{\text{sc}} + j5\mathbf{I}_1$$


Solving,

$$\mathbf{I}_{\text{sc}} = -11.094/\underline{123.69^\circ} \text{ A}; \quad \mathbf{I}_1 = 22.188/\underline{-56.31^\circ} \text{ A}$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{-80 - j40}{-11.094/\underline{123.69^\circ}} = 1 + j8 \Omega$$

$$\therefore R_L = 8.962 \Omega$$

**[f]**

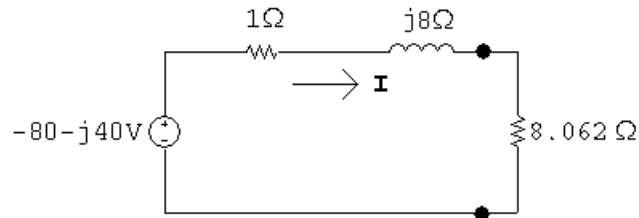

$$\mathbf{I} = \frac{-80 - j40}{9.062 + j8} = 7.399/\underline{165.13^\circ} \text{ A}$$


$$P = \frac{1}{2}(7.399)^2(8.062) = 220.70 \text{ W}$$

**[g]**  $\mathbf{Z}_L = \mathbf{Z}_{\text{Th}}^* = 1 - j8 \Omega$

**[h]**  $\mathbf{I} = \frac{-80 - j40}{2} = 44.72/\underline{-153.43^\circ} \text{ A}$

$$P = \frac{1}{2}(44.72)^2(1) = 1000 \text{ W}$$

P 10.52 [a]

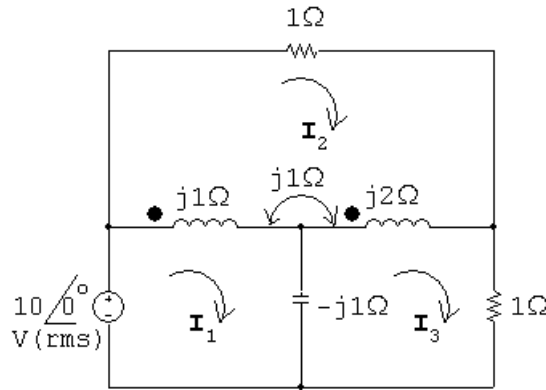

$$10 = j1(\mathbf{I}_1 - \mathbf{I}_2) + j1(\mathbf{I}_3 - \mathbf{I}_2) - j1(\mathbf{I}_1 - \mathbf{I}_3)$$

$$0 = 1\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_3) + j1(\mathbf{I}_2 - \mathbf{I}_1) + j1(\mathbf{I}_2 - \mathbf{I}_1) + j1(\mathbf{I}_2 - \mathbf{I}_3)$$

$$0 = 1\mathbf{I}_3 - j1(\mathbf{I}_3 - \mathbf{I}_1) + j2(\mathbf{I}_3 - \mathbf{I}_2) + j1(\mathbf{I}_1 - \mathbf{I}_2)$$

Solving,


$$\mathbf{I}_1 = 6.25 + j7.5 \text{ A(rms)}; \quad \mathbf{I}_2 = 5 + j2.5 \text{ A(rms)}; \quad \mathbf{I}_3 = 5 - j2.5 \text{ A(rms)}$$

$$\mathbf{I}_a = \mathbf{I}_1 = 6.25 + j7.5 \text{ A} \qquad \mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_2 = 1.25 + j5 \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 = 5 + j2.5 \text{ A} \qquad \mathbf{I}_d = \mathbf{I}_3 - \mathbf{I}_2 = -j5 \text{ A}$$

$$\mathbf{I}_e = \mathbf{I}_1 - \mathbf{I}_3 = 1.25 + j10 \text{ A} \qquad \mathbf{I}_f = \mathbf{I}_3 = 5 - j2.5 \text{ A}$$

[b]

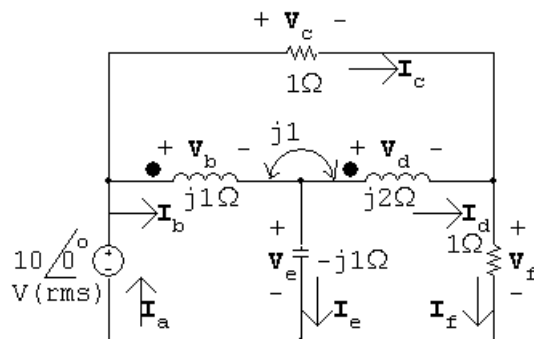

$$\mathbf{V}_a = 10 \text{ V}$$

$$\mathbf{V}_b = j1\mathbf{I}_b + j1\mathbf{I}_d = j1.25 \text{ V}$$

$$\mathbf{V}_c = 1\mathbf{I}_c = 5 + j2.5 \text{ V}$$

$$\mathbf{V}_d = j2\mathbf{I}_d + j1\mathbf{I}_b = 5 + j1.25 \text{ V}$$

$$\mathbf{V}_e = -j1\mathbf{I}_e = 10 - j1.25 \text{ V}$$

$$\mathbf{V}_f = 1\mathbf{I}_f = 5 - j2.5 \text{ V}$$

$$S_a = -10\mathbf{I}_a^* = -62.5 + j75 \text{ VA}$$

$$S_b = \mathbf{V}_b\mathbf{I}_b^* = 6.25 + j1.5625 \text{ VA}$$

$$S_c = \mathbf{V}_c \mathbf{I}_c^* = 31.25 + j0 \text{ VA}$$

$$S_d = \mathbf{V}_d \mathbf{I}_d^* = -6.25 + j25 \text{ VA}$$

$$S_e = \mathbf{V}_e \mathbf{I}_e^* = 0 - j101.5625 \text{ VA}$$

$$S_f = \mathbf{V}_f \mathbf{I}_f^* = 31.25 \text{ VA}$$

**[c]**  $\sum P_{\text{dev}} = 62.5 \text{ W}$

$$\sum P_{\text{abs}} = 6.25 + 31.25 - 6.25 + 31.25 = 62.5 \text{ W}$$

Note that the total power absorbed by the coupled coils is zero:

$$6.25 - 6.25 = 0 = P_b + P_d$$


**[d]**  $\sum Q_{\text{dev}} = 101.5625 \text{ VAR}$

The capacitor is developing magnetizing vars.

$$\sum Q_{\text{abs}} = 75 + 1.5625 + 25 = 101.5625 \text{ VAR}$$

$$\sum Q \text{ absorbed by the coupled coils is } Q_b + Q_d = 26.5625 \text{ VAR}$$


P 10.53 Open circuit voltage:

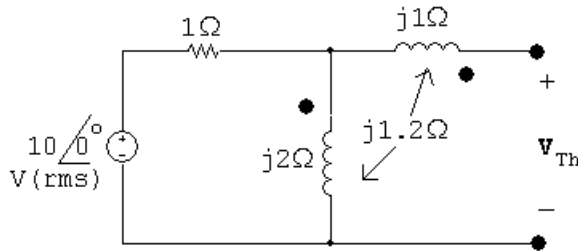

$$\mathbf{I}_1 = \frac{10\angle 0^\circ}{1 + j2} = 2 - j4 \text{ A}$$

$$\mathbf{V}_{\text{Th}} = j2\mathbf{I}_1 + j1.2\mathbf{I}_1 = j3.2\mathbf{I}_1 = 12.8 + j6.4 = 14.31\angle 26.57^\circ \text{ V}$$

Short circuit current:

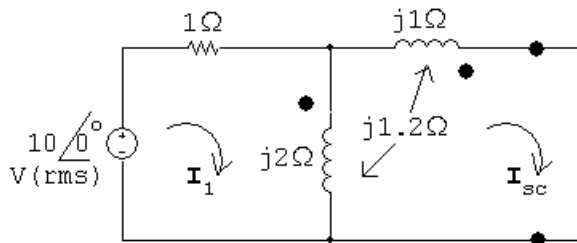

$$10\angle 0^\circ = (1 + j2)\mathbf{I}_1 - j3.2\mathbf{I}_{\text{sc}}$$




$$0 = -j3.2\mathbf{I}_1 + j5.4\mathbf{I}_{\text{sc}}$$

Solving,

$$\mathbf{I}_{\text{sc}} = 5.89 / -5.92^\circ \text{ A}$$

$$Z_{\text{Th}} = \frac{14.31 / 26.57^\circ}{5.89 / -5.92^\circ} = 2.43 / 32.49^\circ = 2.048 + j1.304 \Omega$$
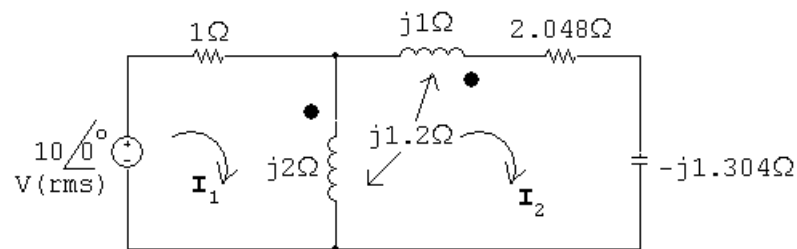
$$\therefore \mathbf{I}_2 = \frac{14.31 / 26.57^\circ}{4.096} = 3.49 / 26.57^\circ \text{ A}$$




$$10\angle 0^\circ = (1 + j2)\mathbf{I}_1 - j3.2\mathbf{I}_2$$

$$\therefore \mathbf{I}_1 = \frac{10 + j3.2\mathbf{I}_2}{1 + j2} = \frac{10 + j3.2(3.49 / 26.57^\circ)}{1 + j2} = 5\angle 0^\circ \text{ A}$$

$$Z_g = \frac{10\angle 0^\circ}{5\angle 0^\circ} = 2 + j0 = 2\angle 0^\circ \Omega$$

P 10.54 [a]

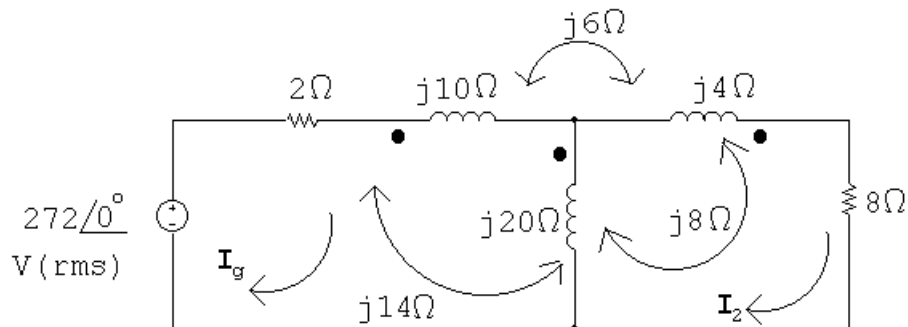

$$272\angle 0^\circ = 2\mathbf{I}_g + j10\mathbf{I}_g + j14(\mathbf{I}_g - \mathbf{I}_2) - j6\mathbf{I}_2$$

$$+ j14\mathbf{I}_g - j8\mathbf{I}_2 + j20(\mathbf{I}_g - \mathbf{I}_2)$$

$$0 = j20(\mathbf{I}_2 - \mathbf{I}_g) - j14\mathbf{I}_g + j8\mathbf{I}_2 + j4\mathbf{I}_2$$

$$+ j8(\mathbf{I}_2 - \mathbf{I}_g) - j6\mathbf{I}_g + 8\mathbf{I}_2$$

Solving,

$$\mathbf{I}_g = 20 - j4 \text{ A(rms)}; \quad \mathbf{I}_2 = 24 \angle 0^\circ \text{ A(rms)}$$

$$P_{8\Omega} = (24)^2(8) = 4608 \text{ W}$$


$$\text{[b]} \quad P_g(\text{developed}) = (272)(20) = 5440 \text{ W}$$

$$\text{[c]} \quad Z_{ab} = \frac{\mathbf{V}_g}{\mathbf{I}_g} - 2 = \frac{272}{20 - j4} - 2 = 11.08 + j2.62 = 11.38 \angle 13.28^\circ \Omega$$

$$\text{[d]} \quad P_{2\Omega} = |\mathbf{I}_g|^2(2) = 832 \text{ W}$$

$$\sum P_{\text{diss}} = 832 + 4608 = 5440 \text{ W} = \sum P_{\text{dev}}$$

P 10.55 [a]

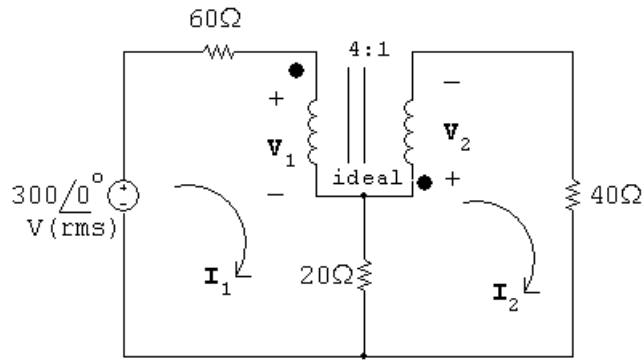

$$300 = 60\mathbf{I}_1 + \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{V}_2 + 40\mathbf{I}_2$$

$$\mathbf{V}_2 = \frac{1}{4}\mathbf{V}_1; \quad \mathbf{I}_2 = -4\mathbf{I}_1$$

Solving,

$$\mathbf{V}_1 = 260 \text{ V(rms)}; \quad \mathbf{V}_2 = 65 \text{ V(rms)}$$

$$\mathbf{I}_1 = 0.25 \text{ A(rms)}; \quad \mathbf{I}_2 = -1.0 \text{ A(rms)}$$

$$\mathbf{V}_{5A} = \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2) = 285 \text{ V(rms)}$$


$$\therefore P = -(285)(5) = -1425 \text{ W}$$

Thus 1425 W is delivered by the current source to the circuit.

$$\text{[b]} \quad \mathbf{I}_{20\Omega} = \mathbf{I}_1 - \mathbf{I}_2 = 1.25 \text{ A(rms)}$$

$$\therefore P_{20\Omega} = (1.25)^2(20) = 31.25 \text{ W}$$

P 10.56

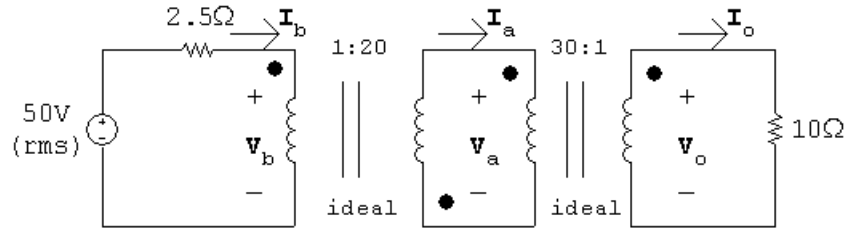

$$30\mathbf{V}_o = \mathbf{V}_a; \quad \frac{\mathbf{I}_o}{30} = \mathbf{I}_a; \quad \mathbf{V}_o = 10\mathbf{I}_o \quad \text{therefore} \quad \frac{\mathbf{V}_a}{\mathbf{I}_a} = 9 \text{ k}\Omega$$

$$\frac{\mathbf{V}_b}{1} = \frac{-\mathbf{V}_a}{20}; \quad \mathbf{I}_b = -20\mathbf{I}_a; \quad \text{therefore} \quad \frac{\mathbf{V}_b}{\mathbf{I}_b} = \frac{9000}{400} = 22.5 \Omega$$

Therefore  $\mathbf{I}_b = [50/(2.5 + 22.5)] = 2 \text{ A (rms)}$ ; since the ideal transformers are lossless,  $P_{10\Omega} = P_{22.5\Omega}$ , and the power delivered to the  $22.5 \Omega$  resistor is  $2^2(22.5)$  or  $90 \text{ W}$ .

P 10.57 [a]  $\frac{\mathbf{V}_b}{\mathbf{I}_b} = \frac{a^2 10}{400} = 2.5 \Omega; \quad \text{therefore} \quad a^2 = 100, \quad a = 10$

[b]  $\mathbf{I}_b = \frac{50}{5} = 10 \text{ A}; \quad P = (100)(2.5) = 250 \text{ W}$

P 10.58 [a]  $Z_{\text{Th}} = 720 + j1500 + \left(\frac{200}{50}\right)^2 (40 - j30) = 1360 + j1020 = 1700/\underline{36.87^\circ} \Omega$


$$\therefore Z_{\text{ab}} = 1700 \Omega$$

$$Z_{\text{ab}} = \frac{Z_{\text{L}}}{(1 + N_1/N_2)^2}$$

$$(1 + N_1/N_2)^2 = 6800/1700 = 4$$

$$\therefore N_1/N_2 = 1 \quad \text{or} \quad N_2 = N_1 = 1000 \text{ turns}$$

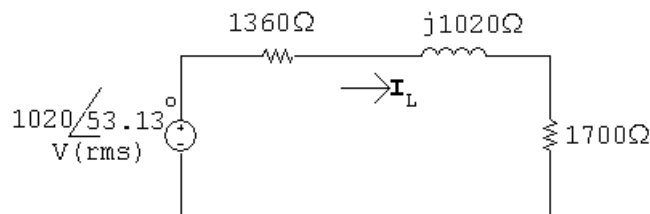[b]  $\mathbf{V}_{\text{Th}} = \frac{255/\underline{0^\circ}}{40 + j30}(j200) = 1020/\underline{53.13^\circ} \text{ V}$




$$\mathbf{I}_L = \frac{1020/\underline{53.13^\circ}}{3060 + j1020} = 0.316/\underline{34.7^\circ} \text{ A(rms)}$$

Since the transformer is ideal,  $P_{6800} = P_{1700}$ .

$$P = |\mathbf{I}_L|^2(1700) = 170 \text{ W}$$

[c]

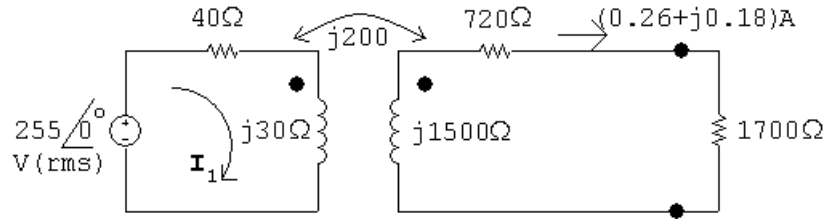

$$255\angle 0^\circ = (40 + j30)\mathbf{I}_1 - j200(0.26 + j0.18)$$


$$\therefore \mathbf{I}_1 = 4.13 - j1.80 \text{ A(rms)}$$

$$P_{\text{gen}} = (255)(4.13) = 1053 \text{ W}$$

$$P_{\text{trans}} = 1053 - 170 = 883 \text{ W}$$

$$\% \text{ transmitted} = \frac{883}{1053}(100) = 83.85\%$$

P 10.59 [a]

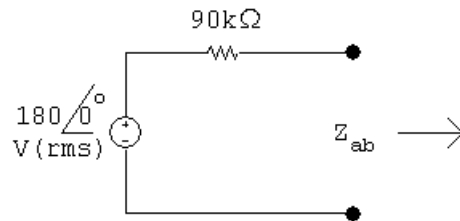

For maximum power transfer,  $Z_{ab} = 90 \text{ k}\Omega$

$$Z_{ab} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L$$


$$\therefore \left(1 + \frac{N_1}{N_2}\right)^2 = \frac{90,000}{400} = 225$$

$$1 + \frac{N_1}{N_2} = \pm 15; \quad \frac{N_1}{N_2} = 15 - 1 = 14$$

[b]  $P = |\mathbf{I}_i|^2 (90,000) = \left(\frac{180}{180,000}\right)^2 (90,000) = 90 \text{ mW}$

[c]  $\mathbf{V}_1 = R_i \mathbf{I}_i = (90,000) \left(\frac{180}{180,000}\right) = 90 \text{ V}$

[d]

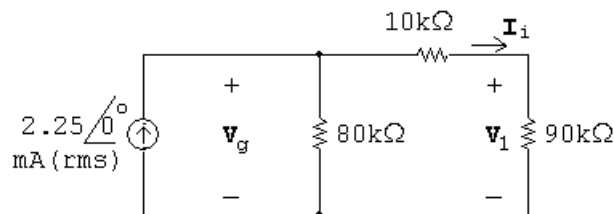

$$\mathbf{V}_g = (2.25 \times 10^{-3})(100,000 \parallel 80,000) = 100 \text{ V}$$

$$P_g(\text{del}) = (2.25 \times 10^{-3})(100) = 225 \text{ mW}$$

$$\% \text{ delivered} = \frac{90}{225}(100) = 40\%$$

P 10.60 [a]  $Z_{ab} = \left(1 + \frac{N_1}{N_2}\right)^2 (1 - j2) = 25 - j50 \Omega$

$$\therefore \mathbf{I}_1 = \frac{100 \angle 0^\circ}{15 + j50 + 25 - j50} = 2.5 \angle 0^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{N_1}{N_2} \mathbf{I}_1 = 10 \angle 0^\circ \text{ A}$$

$$\therefore \mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 = 12.5 \angle 0^\circ \text{ A(rms)}$$

$$P_{1\Omega} = (12.5)^2(1) = 156.25 \text{ W}$$

$$P_{15\Omega} = (2.5)^2(15) = 93.75 \text{ W}$$

[b]  $P_g = -100(2.5 \angle 0^\circ) = -250 \text{ W}$

$$\sum P_{\text{abs}} = 156.25 + 93.75 = 250 \text{ W} = \sum P_{\text{dev}}$$

P 10.61 [a]  $25a_1^2 + 4a_2^2 = 500$

$$\mathbf{I}_{25} = a_1 \mathbf{I}; \quad P_{25} = a_1^2 \mathbf{I}^2(25)$$

$$\mathbf{I}_4 = a_2 \mathbf{I}; \quad P_4 = a_2^2 \mathbf{I}^2(4)$$

$$P_4 = 4P_{25}; \quad a_2^2 \mathbf{I}^2 4 = 100a_1^2 \mathbf{I}^2$$

$$\therefore 100a_1^2 = 4a_2^2$$

$$25a_1^2 + 100a_1^2 = 500; \quad a_1 = 2$$

$$25(4) + 4a_2^2 = 500; \quad a_2 = 10$$

[b]  $\mathbf{I} = \frac{2000 \angle 0^\circ}{500 + 500} = 2 \angle 0^\circ \text{ A(rms)}$


$$\mathbf{I}_{25} = a_1 \mathbf{I} = 4 \text{ A}$$

$$P_{25\Omega} = (16)(25) = 400 \text{ W}$$

[c]  $\mathbf{I}_4 = a_2 \mathbf{I} = 10(2) = 20 \text{ A(rms)}$

$$\mathbf{V}_4 = (20)(4) = 80 \angle 0^\circ \text{ V(rms)}$$

P 10.62 [a] Open circuit voltage:

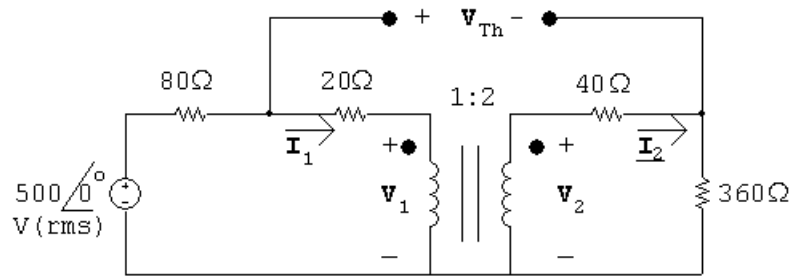

$$500 = 100\mathbf{I}_1 + \mathbf{V}_1$$

$$\mathbf{V}_2 = 400\mathbf{I}_2$$

$$\frac{\mathbf{V}_1}{1} = \frac{\mathbf{V}_2}{2} \quad \therefore \quad \mathbf{V}_2 = 2\mathbf{V}_1$$

$$\mathbf{I}_1 = 2\mathbf{I}_2$$

Substitute and solve:

$$2\mathbf{V}_1 = 400\mathbf{I}_1/2 = 200\mathbf{I}_1 \quad \therefore \quad \mathbf{V}_1 = 100\mathbf{I}_1$$


$$500 = 100\mathbf{I}_1 + 100\mathbf{I}_1 \quad \therefore \quad \mathbf{I}_1 = 500/200 = 2.5 \text{ A}$$

$$\therefore \quad \mathbf{I}_2 = \frac{1}{2}\mathbf{I}_1 = 1.25 \text{ A}$$

$$\mathbf{V}_1 = 100(2.5) = 250 \text{ V}; \quad \mathbf{V}_2 = 2\mathbf{V}_1 = 500 \text{ V}$$

$$\mathbf{V}_{Th} = 20\mathbf{I}_1 + \mathbf{V}_1 - \mathbf{V}_2 + 40\mathbf{I}_2 = -150 \text{ V(rms)}$$

Short circuit current:

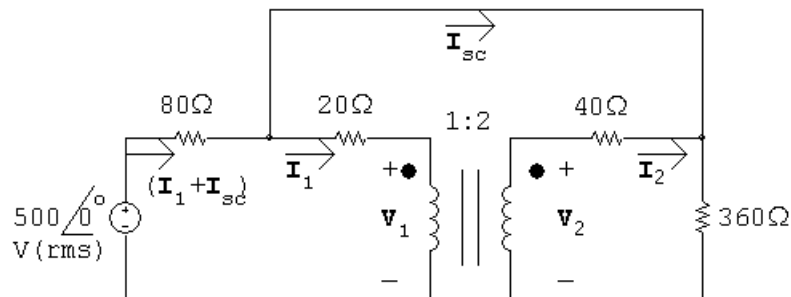

$$500 = 80(\mathbf{I}_{sc} + \mathbf{I}_1) + 360(\mathbf{I}_{sc} + 0.5\mathbf{I}_1)$$


$$2\mathbf{V}_1 = 40\frac{\mathbf{I}_1}{2} + 360(\mathbf{I}_{sc} + 0.5\mathbf{I}_1)$$

$$500 = 80(\mathbf{I}_1 + \mathbf{I}_{sc}) + 20\mathbf{I}_1 + \mathbf{V}_1$$

Solving,


$$\mathbf{I}_{\text{sc}} = -1.47 \text{ A}; \quad \mathbf{I}_1 = 4.41 \text{ A}; \quad \mathbf{V}_1 = 176.47 \text{ V}$$
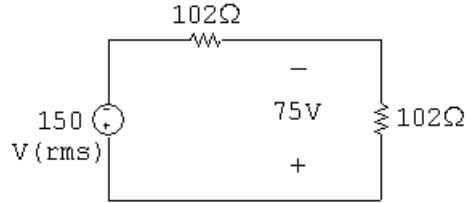
$$R_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{-150}{-1.47} = 102 \Omega$$



$$P = \frac{75^2}{102} = 55.15 \text{ W}$$

**[b]**

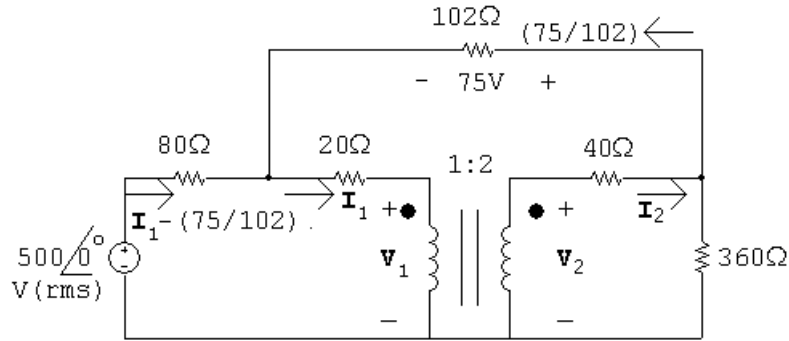

$$500 = 80[\mathbf{I}_1 - (75/102)] - 75 + 360[\mathbf{I}_2 - (75/102)]$$

$$575 + \frac{6000}{102} + \frac{27,000}{102} = 80\mathbf{I}_1 + 180\mathbf{I}_1$$

$$\therefore \quad \mathbf{I}_1 = 3.456 \text{ A}$$

$$P_{\text{source}} = (500)[3.456 - (75/102)] = 1360.29 \text{ W}$$

$$\% \text{ delivered} = \frac{55.15}{1360.29}(100) = 4.05\%$$

**[c]**  $P_{80\Omega} = 80 \left( \mathbf{I}_1 - \frac{75}{102} \right)^2 = 592.13 \text{ W}$

$$P_{20\Omega} = 20\mathbf{I}_1^2 = 238.86 \text{ W}$$


$$P_{40\Omega} = 40\mathbf{I}_2^2 = 119.43 \text{ W}$$

$$P_{102\Omega} = \frac{75^2}{102} = 55.15 \text{ W}$$

$$P_{360\Omega} = 360 \left( \mathbf{I}_2 - \frac{75}{102} \right)^2 = 354.73 \text{ W}$$

$$\sum P_{\text{abs}} = 592.13 + 238.86 + 119.43 + 55.15 + 354.73 = 1360.3 \text{ W} = \sum P_{\text{dev}}$$

P 10.63 [a] Open circuit voltage:

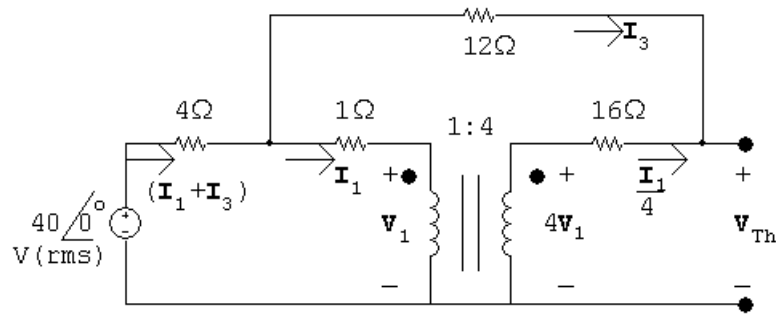


$$40\angle 0^\circ = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3 + \mathbf{V}_{Th}$$

$$\frac{\mathbf{I}_1}{4} = -\mathbf{I}_3; \quad \mathbf{I}_1 = -4\mathbf{I}_3$$

Solving,

$$\mathbf{V}_{Th} = 40\angle 0^\circ \text{ V}$$

Short circuit current:

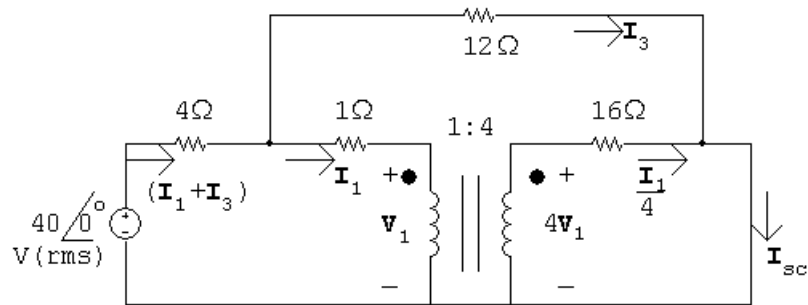

$$40\angle 0^\circ = 4\mathbf{I}_1 + 4\mathbf{I}_3 + \mathbf{I}_1 + \mathbf{V}_1$$

$$4\mathbf{V}_1 = 16(\mathbf{I}_1/4) = 4\mathbf{I}_1; \quad \therefore \mathbf{V}_1 = \mathbf{I}_1$$

$$\therefore 40\angle 0^\circ = 6\mathbf{I}_1 + 4\mathbf{I}_3$$

Also,


$$40\angle 0^\circ = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 6 \text{ A}; \quad \mathbf{I}_3 = 1 \text{ A}; \quad \mathbf{I}_{sc} = \mathbf{I}_1/4 + \mathbf{I}_3 = 2.5 \text{ A}$$
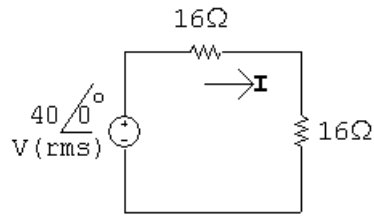
$$R_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{40}{2.5} = 16 \Omega$$






$$\mathbf{I} = \frac{40\angle 0^\circ}{32} = 1.25\angle 0^\circ \text{ A(rms)}$$

$$P = (1.25)^2(16) = 25 \text{ W}$$

[b]

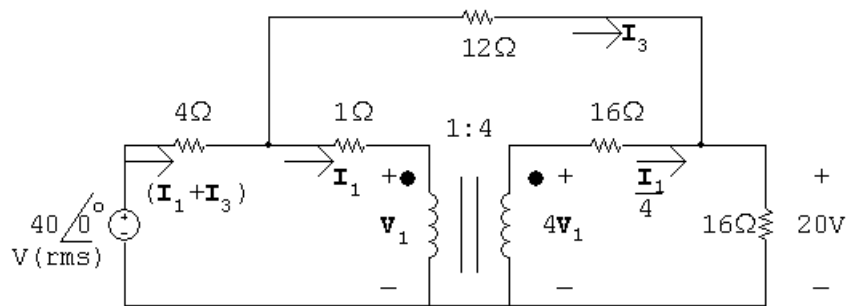

$$40 = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3 + 20$$

$$4\mathbf{V}_1 = 4\mathbf{I}_1 + 16(\mathbf{I}_1/4 + \mathbf{I}_3); \quad \therefore \mathbf{V}_1 = 2\mathbf{I}_1 + 4\mathbf{I}_3$$

$$40 = 4\mathbf{I}_1 + 4\mathbf{I}_3 + \mathbf{I}_1 + \mathbf{V}_1$$

$$\therefore \mathbf{I}_1 = 6 \text{ A}; \quad \mathbf{I}_3 = -0.25 \text{ A}; \quad \mathbf{I}_1 + \mathbf{I}_3 = 5.75\angle 0^\circ \text{ A}; \quad \mathbf{V}_1 = 11\angle 0^\circ \text{ V}$$

$$P_{40V}(\text{developed}) = 40(5.75) = 230 \text{ W}$$

$$\therefore \% \text{ delivered} = \frac{25}{230}(100) = 10.87\%$$

$$[\mathbf{c}] \quad P_{R_L} = 25 \text{ W}; \quad P_{16\Omega} = (1.5)^2(16) = 36 \text{ W}$$

$$P_{4\Omega} = (5.75)^2(4) = 132.25 \text{ W}; \quad P_{1\Omega} = (6)^2(1) = 36 \text{ W}$$

$$P_{12\Omega} = (-0.25)^2(12) = 0.75 \text{ W}$$

$$\sum P_{\text{abs}} = 25 + 36 + 132.25 + 36 + 0.75 = 230 \text{ W} = \sum P_{\text{dev}}$$


P 10.64 [a] Replace the circuit to the left of the primary winding with a Thévenin equivalent:

$$\mathbf{V}_{\text{Th}} = (15)(20 \parallel j10) = 60 + j120 \text{ V}$$

$$\mathbf{Z}_{\text{Th}} = 2 + 20 \parallel j10 = 6 + j8 \Omega$$

Transfer the secondary impedance to the primary side:
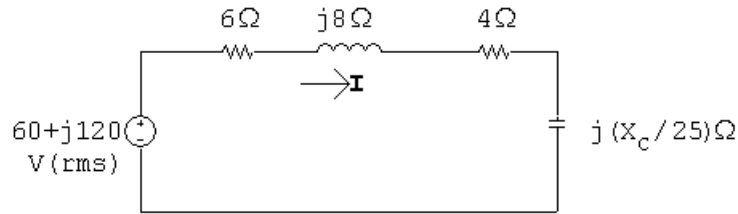
$$Z_p = \frac{1}{25}(100 + jX_C) = 4 + j\frac{X_C}{25} \Omega$$



Now maximize  $\mathbf{I}$  by setting  $(X_C/25) = -8 \Omega$ :

$$\therefore C = \frac{1}{200(20 \times 10^3)} = 0.25 \mu\text{F}$$

$$\text{[b]} \quad \mathbf{I} = \frac{60 + j120}{10} = 6 + j12 \text{ A}$$

$$P = |\mathbf{I}|^2(4) = 720 \text{ W}$$

$$\text{[c]} \quad \frac{R_o}{25} = 6 \Omega; \quad \therefore R_o = 150 \Omega$$


$$\text{[d]} \quad \mathbf{I} = \frac{60 + j120}{12} = 5 + j10 \text{ A}$$

$$P = |\mathbf{I}|^2(6) = 750 \text{ W}$$


$$\text{P 10.65 [a]} \quad Z_{ab} = 50 - j400 = \left(1 - \frac{N_1}{N_2}\right)^2 Z_L = \left(1 - \frac{2800}{700}\right)^2 Z_L = 9Z_L$$

$$\therefore Z_L = \frac{1}{9}(50 - j400) = 5.556 - j44.444 \Omega$$

[b]

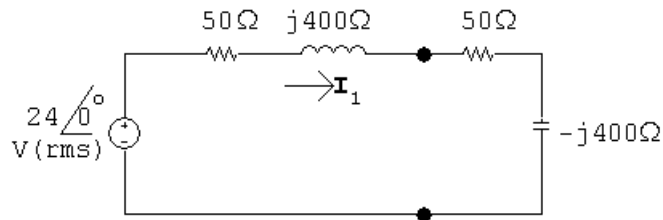
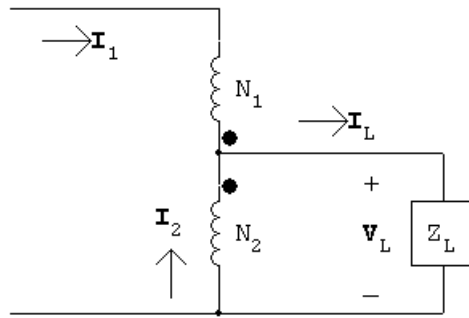
$$\mathbf{I}_1 = \frac{24}{100} = 240/0^\circ \text{ mA}$$



$$N_1 \mathbf{I}_1 = -N_2 \mathbf{I}_2$$

$$\mathbf{I}_2 = -4\mathbf{I}_1 = 960/\underline{180^\circ} \text{ mA}$$

$$\mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 = 720/\underline{180^\circ} \text{ mA(rms)}$$

$$\mathbf{V}_L = (5.556 - j44.444)\mathbf{I}_L = -4 + j32 = 32.25/\underline{97.13^\circ} \text{ V(rms)}$$

P 10.66 [a] Begin with the MEDIUM setting, as shown in Fig. 10.31, as it involves only the resistor  $R_2$ . Then,

$$P_{\text{med}} = 500 \text{ W} = \frac{V^2}{R_2} = \frac{120^2}{R_2}$$

Thus,

$$R_2 = \frac{120^2}{500} = 28.8 \Omega$$

[b] Now move to the LOW setting, as shown in Fig. 10.30, which involves the resistors  $R_1$  and  $R_2$  connected in series:

$$P_{\text{low}} = \frac{V^2}{R_1 + R_2} = \frac{V^2}{R_1 + 28.8} = 250 \text{ W}$$

Thus,

$$R_1 = \frac{120^2}{250} - 28.8 = 28.8 \Omega$$

[c] Note that the HIGH setting has  $R_1$  and  $R_2$  in parallel:

$$P_{\text{high}} = \frac{V^2}{R_1 \parallel R_2} = \frac{120^2}{28.8 \parallel 28.8} = 1000 \text{ W}$$

If the HIGH setting has required power other than 1000 W, this problem could not have been solved. In other words, the HIGH power setting was chosen in such a way that it would be satisfied once the two resistor values were calculated to satisfy the LOW and MEDIUM power settings.

$$\text{P 10.67 [a]} \quad P_L = \frac{V^2}{R_1 + R_2}; \quad R_1 + R_2 = \frac{V^2}{P_L}$$

$$P_M = \frac{V^2}{R_2}; \quad R_2 = \frac{V^2}{P_M}$$

$$P_H = \frac{V^2(R_1 + R_2)}{R_1 R_2}$$

$$R_1 + R_2 = \frac{V^2}{P_L}; \quad R_1 = \frac{V^2}{P_L} - \frac{V^2}{P_M}$$

$$P_H = \frac{V^2 V^2 / P_L}{\left(\frac{V^2}{P_L} - \frac{V^2}{P_M}\right) \left(\frac{V^2}{P_M}\right)} = \frac{P_M P_L P_M}{P_L (P_M - P_L)}$$

$$P_H = \frac{P_M^2}{P_M - P_L}$$

$$\text{[b]} \quad P_H = \frac{(750)^2}{(750 - 250)} = 1125 \text{ W}$$

P 10.68 First solve the expression derived in P10.67 for  $P_M$  as a function of  $P_L$  and  $P_H$ . Thus

$$P_M - P_L = \frac{P_M^2}{P_H} \quad \text{or} \quad \frac{P_M^2}{P_H} - P_M + P_L = 0$$

$$P_M^2 - P_M P_H + P_L P_H = 0$$

$$\begin{aligned} \therefore P_M &= \frac{P_H}{2} \pm \sqrt{\left(\frac{P_H}{2}\right)^2 - P_L P_H} \\ &= \frac{P_H}{2} \pm P_H \sqrt{\frac{1}{4} - \left(\frac{P_L}{P_H}\right)} \end{aligned}$$

For the specified values of  $P_L$  and  $P_H$

$$P_M = 500 \pm 1000\sqrt{0.25 - 0.24} = 500 \pm 100$$

$$\therefore P_{M1} = 600 \text{ W}; \quad P_{M2} = 400 \text{ W}$$

Note in this case we design for two medium power ratings

If  $P_{M1} = 600 \text{ W}$

$$R_2 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_1 + R_2 = \frac{(120)^2}{240} = 60 \, \Omega$$

$$R_1 = 60 - 24 = 36 \, \Omega$$

$$\text{CHECK: } P_H = \frac{(120)^2(60)}{(36)(24)} = 1000 \, \text{W}$$

$$\text{If } P_{M2} = 400 \, \text{W}$$

$$R_2 = \frac{(120)^2}{400} = 36 \, \Omega$$

$$R_1 + R_2 = 60 \, \Omega \quad (\text{as before})$$

$$R_1 = 24 \, \Omega$$

$$\text{CHECK: } P_H = 1000 \, \text{W}$$

$$\text{P 10.69} \quad R_1 + R_2 + R_3 = \frac{(120)^2}{600} = 24 \, \Omega$$

$$R_2 + R_3 = \frac{(120)^2}{900} = 16 \, \Omega$$

$$\therefore R_1 = 24 - 16 = 8 \, \Omega$$

$$R_3 + R_1 \parallel R_2 = \frac{(120)^2}{1200} = 12 \, \Omega$$

$$\therefore 16 - R_2 + \frac{8R_2}{8 + R_2} = 12$$

$$R_2 - \frac{8R_2}{8 + R_2} = 4$$

$$8R_2 + R_2^2 - 8R_2 = 32 + 4R_2$$

$$R_2^2 - 4R_2 - 32 = 0$$

$$R_2 = 2 \pm \sqrt{4 + 32} = 2 \pm 6$$

$$\therefore R_2 = 8 \, \Omega; \quad \therefore R_3 = 8 \, \Omega$$

$$\text{P 10.70} \quad R_2 = \frac{(220)^2}{500} = 96.8 \, \Omega$$

$$R_1 + R_2 = \frac{(220)^2}{250} = 193.6 \, \Omega$$

$$\therefore R_1 = 96.8 \, \Omega$$

$$\text{CHECK: } R_1 \parallel R_2 = 48.4 \, \Omega$$

$$P_H = \frac{(220)^2}{48.4} = 1000 \, \text{W}$$