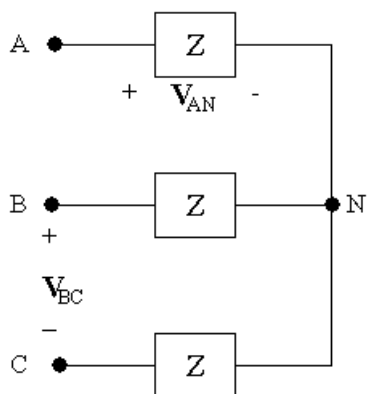


## Balanced Three-Phase Circuits

### Assessment Problems

AP 11.1 Make a sketch:



We know  $\mathbf{V}_{AN}$  and wish to find  $\mathbf{V}_{BC}$ . To do this, write a KVL equation to find  $\mathbf{V}_{AB}$ , and use the known phase angle relationship between  $\mathbf{V}_{AB}$  and  $\mathbf{V}_{BC}$  to find  $\mathbf{V}_{BC}$ .

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} + \mathbf{V}_{NB} = \mathbf{V}_{AN} - \mathbf{V}_{BN}$$

Since  $\mathbf{V}_{AN}$ ,  $\mathbf{V}_{BN}$ , and  $\mathbf{V}_{CN}$  form a balanced set, and  $\mathbf{V}_{AN} = 240\angle -30^\circ \text{ V}$ , and the phase sequence is positive,

$$\mathbf{V}_{BN} = |\mathbf{V}_{AN}| \angle (\angle \mathbf{V}_{AN} - 120^\circ) = 240\angle -30^\circ - 120^\circ = 240\angle -150^\circ \text{ V}$$

Then,

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} = (240\angle -30^\circ) - (240\angle -150^\circ) = 415.46\angle 0^\circ \text{ V}$$


Since  $\mathbf{V}_{AB}$ ,  $\mathbf{V}_{BC}$ , and  $\mathbf{V}_{CA}$  form a balanced set with a positive phase sequence, we can find  $\mathbf{V}_{BC}$  from  $\mathbf{V}_{AB}$ :

$$\mathbf{V}_{BC} = |\mathbf{V}_{AB}| \angle (\angle \mathbf{V}_{AB} - 120^\circ) = 415.69\angle 0^\circ - 120^\circ = 415.69\angle -120^\circ \text{ V}$$

Thus,

$$\mathbf{V}_{BC} = 415.69\angle -120^\circ \text{ V}$$

AP 11.2 Make a sketch:

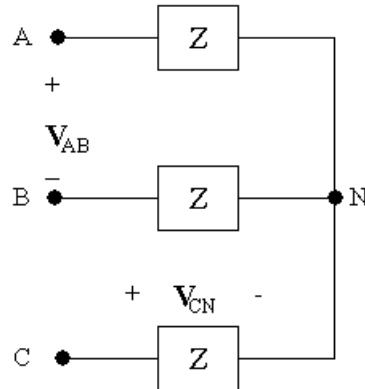

We know  $V_{CN}$  and wish to find  $V_{AB}$ . To do this, write a KVL equation to find  $V_{BC}$ , and use the known phase angle relationship between  $V_{AB}$  and  $V_{BC}$  to find  $V_{AB}$ .

$$V_{BC} = V_{BN} + V_{NC} = V_{BN} - V_{CN}$$

Since  $V_{AN}$ ,  $V_{BN}$ , and  $V_{CN}$  form a balanced set, and  $V_{CN} = 450 \angle -25^\circ$  V, and the phase sequence is negative,

$$V_{BN} = |V_{CN}| \angle \angle V_{CN} - 120^\circ = 450 \angle -25^\circ - 120^\circ = 450 \angle -145^\circ \text{ V}$$

Then,

$$V_{BC} = V_{BN} - V_{CN} = (450 \angle -145^\circ) - (450 \angle -25^\circ) = 779.42 \angle -175^\circ \text{ V}$$


Since  $V_{AB}$ ,  $V_{BC}$ , and  $V_{CA}$  form a balanced set with a negative phase sequence, we can find  $V_{AB}$  from  $V_{BC}$ :

$$V_{AB} = |V_{BC}| \angle \angle V_{BC} - 120^\circ = 779.42 \angle -295^\circ \text{ V}$$

But we normally want phase angle values between  $+180^\circ$  and  $-180^\circ$ . We add  $360^\circ$  to the phase angle computed above. Thus,

$$V_{AB} = 779.42 \angle 65^\circ \text{ V}$$

AP 11.3 Sketch the a-phase circuit:

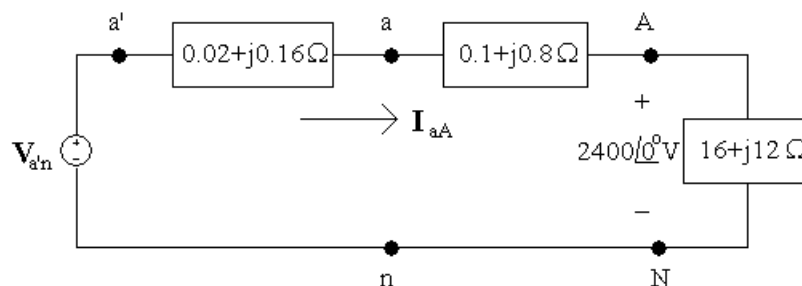

- [a] We can find the line current using Ohm's law, since the a-phase line current is the current in the a-phase load. Then we can use the fact that  $\mathbf{I}_{aA}$ ,  $\mathbf{I}_{bB}$ , and  $\mathbf{I}_{cC}$  form a balanced set to find the remaining line currents. Note that since we were not given any phase angles in the problem statement, we can assume that the phase voltage given,  $\mathbf{V}_{AN}$ , has a phase angle of  $0^\circ$ .

$$2400\angle 0^\circ = \mathbf{I}_{aA}(16 + j12)$$

so

$$\mathbf{I}_{aA} = \frac{2400\angle 0^\circ}{16 + j12} = 96 - j72 = 120\angle -36.87^\circ \text{ A}$$

With an acb phase sequence,

$$\angle \mathbf{I}_{bB} = \angle \mathbf{I}_{aA} + 120^\circ \quad \text{and} \quad \angle \mathbf{I}_{cC} = \angle \mathbf{I}_{aA} - 120^\circ$$

so

$$\mathbf{I}_{aA} = 120\angle -36.87^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 120\angle 83.13^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 120\angle -156.87^\circ \text{ A}$$

- [b] The line voltages at the source are  $\mathbf{V}_{ab}$ ,  $\mathbf{V}_{bc}$ , and  $\mathbf{V}_{ca}$ . They form a balanced set. To find  $\mathbf{V}_{ab}$ , use the a-phase circuit to find  $\mathbf{V}_{AN}$ , and use the relationship between phase voltages and line voltages for a y-connection (see Fig. 11.9[b]). From the a-phase circuit, use KVL:

$$\begin{aligned} \mathbf{V}_{an} &= \mathbf{V}_{aA} + \mathbf{V}_{AN} = (0.1 + j0.8)\mathbf{I}_{aA} + 2400\angle 0^\circ \\ &= (0.1 + j0.8)(96 - j72) + 2400\angle 0^\circ = 2467.2 + j69.6 \\ &= 2468.18\angle 1.62^\circ \text{ V} \end{aligned}$$

From Fig. 11.9(b),

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3}\angle -30^\circ) = 4275.02\angle -28.38^\circ \text{ V}$$

With an acb phase sequence,

$$\angle \mathbf{V}_{bc} = \angle \mathbf{V}_{ab} + 120^\circ \quad \text{and} \quad \angle \mathbf{V}_{ca} = \angle \mathbf{V}_{ab} - 120^\circ$$

so

$$\mathbf{V}_{ab} = 4275.02\angle -28.38^\circ \text{ V}$$

$$\mathbf{V}_{bc} = 4275.02\angle 91.62^\circ \text{ V}$$

$$\mathbf{V}_{ca} = 4275.02\angle -148.38^\circ \text{ V}$$

[c] Using KVL on the a-phase circuit

$$\begin{aligned}\mathbf{V}_{a'n} &= \mathbf{V}_{a'a} + \mathbf{V}_{an} = (0.2 + j0.16)\mathbf{I}_{aA} + \mathbf{V}_{an} \\ &= (0.02 + j0.16)(96 - j72) + (2467.2 + j69.9) \\ &= 2480.64 + j83.52 = 2482.05 \angle 1.93^\circ \text{ V}\end{aligned}$$

With an acb phase sequence,

$$\angle \mathbf{V}_{b'n} = \angle \mathbf{V}_{a'n} + 120^\circ \quad \text{and} \quad \angle \mathbf{V}_{c'n} = \angle \mathbf{V}_{a'n} - 120^\circ$$

so

$$\mathbf{V}_{a'n} = 2482.05 \angle 1.93^\circ \text{ V}$$

$$\mathbf{V}_{b'n} = 2482.05 \angle 121.93^\circ \text{ V}$$

$$\mathbf{V}_{c'n} = 2482.05 \angle -118.07^\circ \text{ V}$$

$$\text{AP 11.4 } \mathbf{I}_{cC} = (\sqrt{3} \angle -30^\circ) \mathbf{I}_{CA} = (\sqrt{3} \angle -30^\circ) \cdot 8 \angle -15^\circ = 13.86 \angle -45^\circ \text{ A}$$

$$\text{AP 11.5 } \mathbf{I}_{aA} = 12 \angle (65^\circ - 120^\circ) = 12 \angle -55^\circ$$

$$\begin{aligned}\mathbf{I}_{AB} &= \left[ \left( \frac{1}{\sqrt{3}} \right) \angle -30^\circ \right] \mathbf{I}_{aA} = \left( \frac{\angle -30^\circ}{\sqrt{3}} \right) \cdot 12 \angle -55^\circ \\ &= 6.93 \angle -85^\circ \text{ A}\end{aligned}$$

$$\text{AP 11.6 [a] } \mathbf{I}_{AB} = \left[ \left( \frac{1}{\sqrt{3}} \right) \angle 30^\circ \right] [69.28 \angle -10^\circ] = 40 \angle 20^\circ \text{ A}$$

$$\text{Therefore } Z_\phi = \frac{4160 \angle 0^\circ}{40 \angle 20^\circ} = 104 \angle -20^\circ \Omega$$

$$\text{[b] } \mathbf{I}_{AB} = \left[ \left( \frac{1}{\sqrt{3}} \right) \angle -30^\circ \right] [69.28 \angle -10^\circ] = 40 \angle -40^\circ \text{ A}$$

$$\text{Therefore } Z_\phi = 104 \angle 40^\circ \Omega$$

$$\text{AP 11.7 } \mathbf{I}_\phi = \frac{110}{3.667} + \frac{110}{j2.75} = 30 - j40 = 50 \angle -53.13^\circ \text{ A}$$

$$\text{Therefore } |\mathbf{I}_{aA}| = \sqrt{3} \mathbf{I}_\phi = \sqrt{3}(50) = 86.60 \text{ A}$$

AP 11.8 [a]  $|S| = \sqrt{3}(208)(73.8) = 26,587.67 \text{ VA}$

$$Q = \sqrt{(26,587.67)^2 - (22,659)^2} = 13,909.50 \text{ VAR}$$

[b]  $\text{pf} = \frac{22,659}{26,587.67} = 0.8522 \quad \text{lagging}$

AP 11.9 [a]  $\mathbf{V}_{\text{AN}} = \left( \frac{2450}{\sqrt{3}} \right) \angle 0^\circ \text{ V}; \quad \mathbf{V}_{\text{AN}} \mathbf{I}_{\text{aA}}^* = S_\phi = 144 + j192 \text{ kVA}$

Therefore

$$\mathbf{I}_{\text{aA}}^* = \frac{(144 + j192)1000}{2450/\sqrt{3}} = (101.8 + j135.7) \text{ A}$$

$$\mathbf{I}_{\text{aA}} = 101.8 - j135.7 = 169.67 \angle -53.13^\circ \text{ A}$$

$$|\mathbf{I}_{\text{aA}}| = 169.67 \text{ A}$$

[b]  $P = \frac{(2450)^2}{R}; \quad \text{therefore} \quad R = \frac{(2450)^2}{144,000} = 41.68 \Omega$

$$Q = \frac{(2450)^2}{X}; \quad \text{therefore} \quad X = \frac{(2450)^2}{192,000} = 31.26 \Omega$$

[c]  $Z_\phi = \frac{\mathbf{V}_{\text{AN}}}{\mathbf{I}_{\text{aA}}} = \frac{2450/\sqrt{3}}{169.67 \angle -53.13^\circ} = 8.34 \angle 53.13^\circ = (5 + j6.67) \Omega$

$$\therefore R = 5 \Omega, \quad X = 6.67 \Omega$$

## Problems

P 11.1 [a] First, convert the cosine waveforms to phasors:

$$\mathbf{V}_a = 208 \angle 27^\circ; \quad \mathbf{V}_b = 208 \angle 147^\circ; \quad \mathbf{V}_c = 208 \angle -93^\circ$$

Subtract the phase angle of the a-phase from all phase angles:

$$\angle \mathbf{V}'_a = 27^\circ - 27^\circ = 0^\circ$$

$$\angle \mathbf{V}'_b = 147^\circ - 27^\circ = 120^\circ$$

$$\angle \mathbf{V}'_c = -93^\circ - 27^\circ = -120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore acb

[b] First, convert the cosine waveforms to phasors:

$$\mathbf{V}_a = 4160 \angle -18^\circ; \quad \mathbf{V}_b = 4160 \angle -138^\circ; \quad \mathbf{V}_c = 4160 \angle +102^\circ$$

Subtract the phase angle of the a-phase from all phase angles:

$$\angle \mathbf{V}'_a = -18^\circ + 18^\circ = 0^\circ$$

$$\angle \mathbf{V}'_b = -138^\circ + 18^\circ = -120^\circ$$

$$\angle \mathbf{V}'_c = 102^\circ + 18^\circ = 120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore abc

P 11.2 [a]  $\mathbf{V}_a = 180 \angle 0^\circ \text{ V}$

$$\mathbf{V}_b = 180 \angle -120^\circ \text{ V}$$

$$\mathbf{V}_c = 180 \angle -240^\circ = 180 \angle 120^\circ \text{ V}$$

Balanced, positive phase sequence

[b]  $\mathbf{V}_a = 180 \angle -90^\circ \text{ V}$

$$\mathbf{V}_b = 180 \angle 30^\circ \text{ V}$$

$$\mathbf{V}_c = 180 \angle -210^\circ \text{ V} = 180 \angle 150^\circ \text{ V}$$

Balanced, negative phase sequence

[c]  $\mathbf{V}_a = 400 \angle -270^\circ \text{ V} = 400 \angle 90^\circ \text{ V}$

$$\mathbf{V}_b = 400 \angle 120^\circ \text{ V}$$

$$\mathbf{V}_c = 400 \angle -30^\circ \text{ V}$$

Unbalanced, phase angle in b-phase

**[d]**  $\mathbf{V}_a = 200/\underline{30^\circ} \text{ V}$

$$\mathbf{V}_b = 201/\underline{150^\circ} \text{ V}$$

$$\mathbf{V}_c = 200/\underline{270^\circ} \text{ V} = 200/\underline{-90^\circ} \text{ V}$$

Unbalanced, unequal amplitude in the b-phase

**[e]**  $\mathbf{V}_a = 208/\underline{42^\circ} \text{ V}$

$$\mathbf{V}_b = 208/\underline{-78^\circ} \text{ V}$$

$$\mathbf{V}_c = 208/\underline{-201^\circ} \text{ V} = 208/\underline{159^\circ} \text{ V}$$

Unbalanced, phase angle in the c-phase

**[f]** Unbalanced; the frequencies of the waveforms are not the same for the positive sequence of Eq. 11.1

P 11.3  $\mathbf{V}_a = V_m/\underline{0^\circ} = V_m + j0$

$$\mathbf{V}_b = V_m/\underline{-120^\circ} = -V_m(0.5 + j0.866)$$

$$\mathbf{V}_c = V_m/\underline{120^\circ} = V_m(-0.5 + j0.866)$$

$$\begin{aligned} \mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c &= (V_m)(1 + j0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= V_m(0) = 0 \end{aligned}$$

For the negative sequences of Eq. 11.2,  $\mathbf{V}_b$  and  $\mathbf{V}_c$  are interchanged, but the sum is still zero.

P 11.4  $\mathbf{I} = \frac{\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c}{3(R_W + jX_W)} = 0$

P 11.5 **[a]**  $\mathbf{I}_{aA} = \frac{200}{25} = 8/\underline{0^\circ} \text{ A}$

$$\mathbf{I}_{bB} = \frac{200/\underline{-120^\circ}}{30 - j40} = 4/\underline{-66.87^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = \frac{200/\underline{120^\circ}}{80 + j60} = 2/\underline{83.13^\circ} \text{ A}$$

The magnitudes are unequal and the phase angles are not  $120^\circ$  apart.

**b]**  $\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 9.96/\underline{-9.79^\circ} \text{ A}$

P 11.6 [a]  $\mathbf{I}_{aA} = \frac{277\angle 0^\circ}{80 + j60} = 2.77\angle -36.87^\circ \text{ A}$

$$\mathbf{I}_{bB} = \frac{277\angle -120^\circ}{80 + j60} = 2.77\angle -156.87^\circ \text{ A}$$

$$\mathbf{I}_{cC} = \frac{277\angle 120^\circ}{80 + j60} = 2.77\angle 83.13^\circ \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 0$$

[b]  $\mathbf{V}_{AN} = (78 + j54)\mathbf{I}_{aA} = 262.79\angle -2.17^\circ \text{ V}$

[c]  $\mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN}$

$$\mathbf{V}_{BN} = (77 + j56)\mathbf{I}_{bB} = 263.73\angle -120.84^\circ \text{ V}$$

$$\mathbf{V}_{AB} = 262.79\angle -2.17^\circ - 263.73\angle -120.84^\circ = 452.89\angle 28.55^\circ \text{ V}$$

[d] Unbalanced — see conditions for a balanced circuit on p. 504 of the text!

P 11.7  $Z_{ga} + Z_{la} + Z_{La} = 60 + j80 \Omega$

$$Z_{gb} + Z_{lb} + Z_{Lb} = 40 + j30 \Omega$$

$$Z_{gc} + Z_{lc} + Z_{Lc} = 20 + j15 \Omega$$


$$\frac{\mathbf{V}_N - 240}{60 + j80} + \frac{\mathbf{V}_N - 240\angle 120^\circ}{40 + j30} + \frac{\mathbf{V}_N - 240\angle -120^\circ}{20 + j15} + \frac{\mathbf{V}_N}{10} = 0$$

Solving for  $\mathbf{V}_N$  yields

$$\mathbf{V}_N = 42.94\angle -156.32^\circ \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_N}{10} = 4.29\angle -156.32^\circ \text{ A}$$

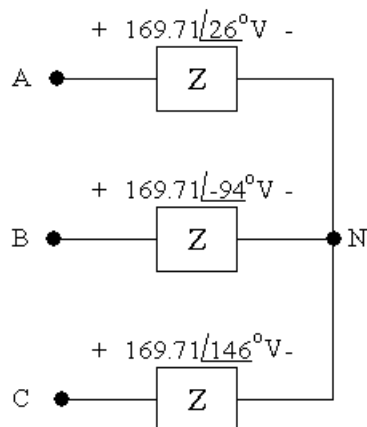P 11.8 Make a sketch of the load in the frequency domain. Note that we convert the time domain line-to-neutral voltages to phasors:



Note that these three voltages form a balanced set with an abc phase sequence. First, use KVL to find  $\mathbf{V}_{AB}$ :

$$\begin{aligned}\mathbf{V}_{AB} &= \mathbf{V}_{AN} + \mathbf{V}_{NB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} \\ &= (169.71 \angle 26^\circ) - (169.71 \angle -94^\circ) = 293.95 \angle 56^\circ \text{ V}\end{aligned}$$

With an abc phase sequence,

$$\angle \mathbf{V}_{BC} = \angle \mathbf{V}_{AB} - 120^\circ \quad \text{and} \quad \angle \mathbf{V}_{CA} = \angle \mathbf{V}_{AB} + 120^\circ$$

so

$$\mathbf{V}_{AB} = 293.95 \angle 56^\circ \text{ V}$$

$$\mathbf{V}_{BC} = 293.95 \angle -64^\circ \text{ V}$$

$$\mathbf{V}_{CA} = 293.95 \angle 176^\circ \text{ V}$$


To get back to the time domain, perform an inverse phasor transform of the three line voltages, using a frequency of  $\omega$ :

$$v_{AB}(t) = 293.95 \cos(\omega t + 56^\circ) \text{ V}$$

$$v_{BC}(t) = 293.95 \cos(\omega t - 64^\circ) \text{ V}$$

$$v_{CA}(t) = 293.95 \cos(\omega t + 176^\circ) \text{ V}$$

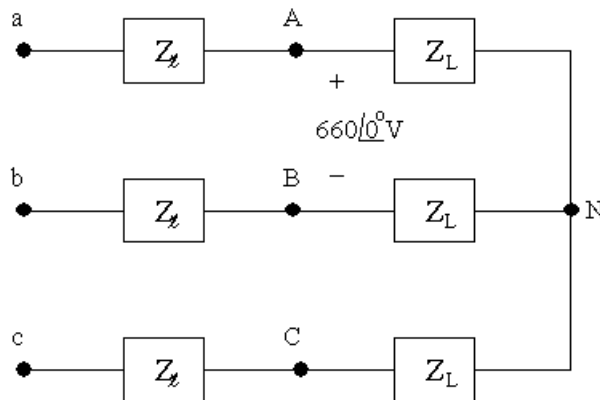P 11.9 Make a sketch of the three-phase line and load:



$$Z_\ell = 0.25 + j2 \Omega/\phi$$

$$Z_L = 30.48 + j22.86 \Omega/\phi$$

- [a] The line currents are  $\mathbf{I}_{aA}$ ,  $\mathbf{I}_{bB}$ , and  $\mathbf{I}_{cC}$ . To find  $\mathbf{I}_{aA}$ , first find  $\mathbf{V}_{AN}$  and use Ohm's law for the a-phase load impedance. Since we are only concerned with finding voltage and current magnitudes, the phase sequence doesn't matter and we arbitrarily assume a positive phase sequence. Since we are not given any phase angles in the problem statement, we can assume the angle of  $\mathbf{V}_{AB}$  is  $0^\circ$ . Use Fig. 11.9(a) to find  $\mathbf{V}_{AN}$  from  $\mathbf{V}_{AB}$ .

$$\mathbf{V}_{AN} = \frac{660}{\sqrt{3}} \angle (0 - 30^\circ) = 381.05 \angle -30^\circ \text{ V}$$

Now find  $\mathbf{I}_{aA}$  using Ohm's law:

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{AN}}{Z_L} = \frac{381.05 \angle -30^\circ}{30.48 + j22.86} = 3.993 - j9.20 = 10 \angle -66.87^\circ \text{ V}$$

Thus, the magnitude of the line current is

$$|\mathbf{I}_{aA}| = 10 \text{ A}$$


- [b] The line voltage at the source is  $\mathbf{V}_{ab}$ . From KVL on the top loop of the three-phase circuit,

$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_{aA} + \mathbf{V}_{AB} + \mathbf{V}_{Bb} \\ &= Z_\ell \mathbf{I}_{aA} + \mathbf{V}_{AB} + Z_\ell \mathbf{I}_{Bb} \\ &= Z_\ell \mathbf{I}_{aA} + \mathbf{V}_{AB} - Z_\ell \mathbf{I}_{bB} \\ &= (0.25 + j2)(10 \angle -66.87^\circ) + 660 \angle 0^\circ - (0.25 + j2)(10 \angle -173.13^\circ) \\ &= 684.71 \angle 2.10^\circ \text{ V} \end{aligned}$$

Thus, the magnitude of the line voltage at the source is

$$|\mathbf{V}_{ab}| = 684.71 \text{ V}$$

P 11.10 Make a sketch of the a-phase:

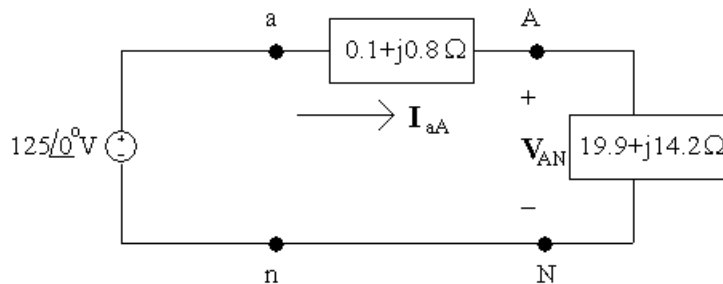

- [a] Find the a-phase line current from the a-phase circuit:

$$\begin{aligned} \mathbf{I}_{aA} &= \frac{125 \angle 0^\circ}{0.1 + j0.8 + 19.9 + j14.2} = \frac{125 \angle 0^\circ}{20 + j15} \\ &= 4 - j3 = 5 \angle -36.87^\circ \text{ A} \end{aligned}$$

Find the other line currents using the acb phase sequence:

$$\mathbf{I}_{bB} = 5 / \underline{-36.87^\circ + 120^\circ} = 5 / \underline{83.13^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = 5 / \underline{-36.87^\circ - 120^\circ} = 5 / \underline{-156.87^\circ} \text{ A}$$

- [b]** The phase voltage at the source is  $\mathbf{V}_{an} = 125 / \underline{0^\circ}$  V. Use Fig. 11.9(b) to find the line voltage,  $\mathbf{V}_{ab}$ , from the phase voltage:

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3} / \underline{-30^\circ}) = 216.51 / \underline{-30^\circ} \text{ V}$$

Find the other line voltages using the acb phase sequence:

$$\mathbf{V}_{bc} = 216.51 / \underline{-30^\circ + 120^\circ} = 216.51 / \underline{90^\circ} \text{ V}$$

$$\mathbf{V}_{ca} = 216.51 / \underline{-30^\circ - 120^\circ} = 216.51 / \underline{-150^\circ} \text{ V}$$

- [c]** The phase voltage at the load in the a-phase is  $\mathbf{V}_{AN}$ . Calculate its value using  $\mathbf{I}_{aA}$  and the load impedance:

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} Z_L = (4 - j3)(19.9 + j14.2) = 122.2 - j2.9 = 122.23 / \underline{-1.36^\circ} \text{ V}$$

Find the phase voltage at the load for the b- and c-phases using the acb sequence:

$$\mathbf{V}_{BN} = 122.23 / \underline{-1.36^\circ + 120^\circ} = 122.23 / \underline{118.64^\circ} \text{ V}$$

$$\mathbf{V}_{CN} = 122.23 / \underline{-1.36^\circ - 120^\circ} = 122.23 / \underline{-121.36^\circ} \text{ V}$$

- [d]** The line voltage at the load in the a-phase is  $\mathbf{V}_{AB}$ . Find this line voltage from the phase voltage at the load in the a-phase,  $\mathbf{V}_{AN}$ , using Fig. 11.9(b):

$$\mathbf{V}_{AB} = \mathbf{V}_{AN}(\sqrt{3} / \underline{-30^\circ}) = 211.71 / \underline{-31.36^\circ} \text{ V}$$

Find the line voltage at the load for the b- and c-phases using the acb sequence:

$$\mathbf{V}_{BC} = 211.71 / \underline{-31.36^\circ + 120^\circ} = 211.71 / \underline{88.69^\circ} \text{ V}$$

$$\mathbf{V}_{CA} = 211.71 / \underline{-31.36^\circ - 120^\circ} = 211.71 / \underline{-151.36^\circ} \text{ V}$$

**P 11.11 [a]**  $\mathbf{I}_{AB} = \frac{480}{60 + j45} = 6.4 / \underline{-36.87^\circ} \text{ A}$

$$\mathbf{I}_{BC} = 6.4 / \underline{-156.87^\circ} \text{ A}$$

$$\mathbf{I}_{CA} = 6.4 / \underline{83.13^\circ} \text{ A}$$

**[b]**  $\mathbf{I}_{aA} = \sqrt{3} / \underline{-30^\circ} \mathbf{I}_{AB} = 11.09 / \underline{-66.87^\circ} \text{ A}$


$$\mathbf{I}_{bB} = 11.09 / \underline{173.13^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = 11.09 / \underline{53.13^\circ} \text{ A}$$

[c] Transform the  $\Delta$ -connected load to a Y-connected load:

$$Z_Y = \frac{Z_\Delta}{3} = \frac{60 + j45}{3} = 20 + j15 \Omega$$

The single-phase equivalent circuit is:

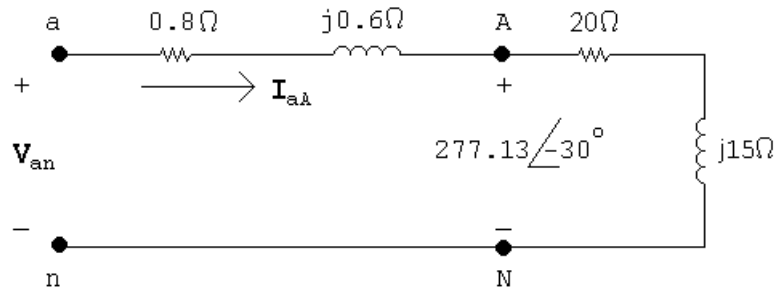


$$\begin{aligned} \mathbf{V}_{an} &= 277.13 \angle -30^\circ + (0.8 + j0.6)(11.09 \angle -66.87^\circ) \\ &= 288.21 \angle -30^\circ \text{ V} \end{aligned}$$

$$\mathbf{V}_{ab} = \sqrt{3} \angle 30^\circ \mathbf{V}_{an} = 499.20 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_{bc} = 499.20 \angle -120^\circ \text{ V}$$

$$\mathbf{V}_{ca} = 499.20 \angle 120^\circ \text{ V}$$

P 11.12 [a]

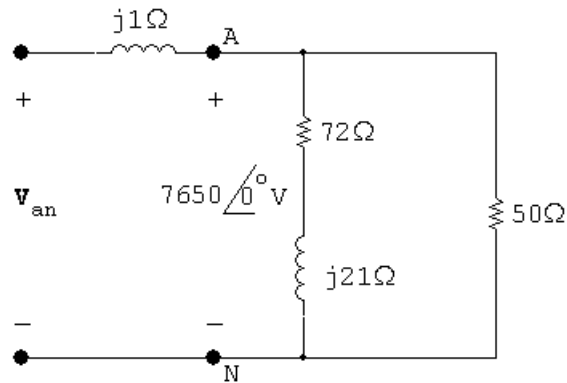

$$\mathbf{I}_{aA} = \frac{7650}{72 + j21} + \frac{7650}{50} = 252.54 \angle -6.49^\circ \text{ A}$$

$$|\mathbf{I}_{aA}| = 252.54 \text{ A}$$

[b]  $\mathbf{I}_{AB} = \frac{7650\sqrt{3} \angle 30^\circ}{150} = 88.33 \angle 30^\circ \text{ A}$

$$|\mathbf{I}_{AB}| = 88.33 \text{ A}$$

$$[\mathbf{c}] \mathbf{I}_{\text{AN}} = \frac{7650 \angle 0^\circ}{72 + j21} = 102 \angle -16.26^\circ \text{ A}$$

$$|\mathbf{I}_{\text{AN}}| = 102 \text{ A}$$

$$[\mathbf{d}] \mathbf{V}_{\text{an}} = (252.54 \angle -6.49^\circ)(j1) + 7650 \angle 0^\circ = 7682.66 \angle 1.87^\circ \text{ V}$$

$$|\mathbf{V}_{\text{ab}}| = \sqrt{3}(7682.66) = 13,306.76 \text{ V}$$


P 11.13 [a] Since the phase sequence is acb (negative) we have:

$$\mathbf{V}_{\text{an}} = 2399.47 \angle 30^\circ \text{ V}$$

$$\mathbf{V}_{\text{bn}} = 2399.47 \angle 150^\circ \text{ V}$$

$$\mathbf{V}_{\text{cn}} = 2399.47 \angle -90^\circ \text{ V}$$
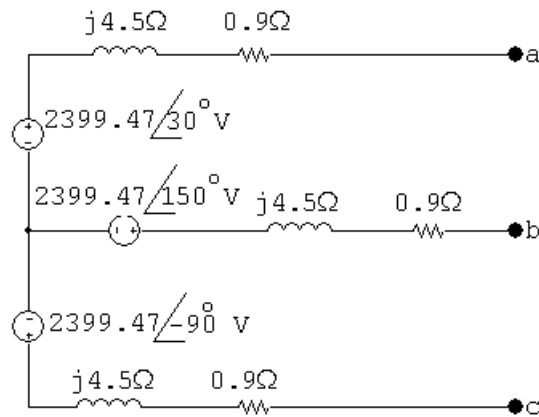
$$\mathbf{Z}_Y = \frac{1}{3} \mathbf{Z}_\Delta = 0.9 + j4.5 \Omega / \phi$$




$$[\mathbf{b}] \mathbf{V}_{\text{ab}} = 2399.47 \angle 30^\circ - 2399.47 \angle 150^\circ = 2399.47 \sqrt{3} \angle 0^\circ = 4156 \angle 0^\circ \text{ V}$$

Since the phase sequence is negative, it follows that

$$\mathbf{V}_{\text{bc}} = 4156 \angle 120^\circ \text{ V}$$

$$\mathbf{V}_{\text{ca}} = 4156 \angle -120^\circ \text{ V}$$

[c]

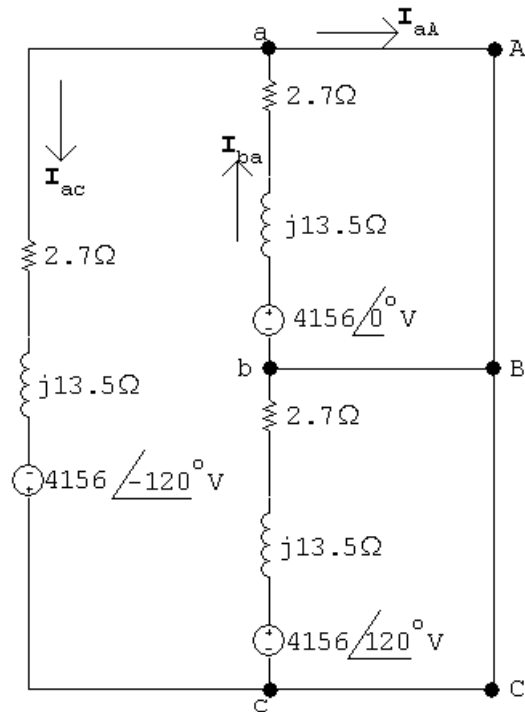

$$\mathbf{I}_{ba} = \frac{4156}{2.7 + j13.5} = 301.87 \angle -78.69^\circ \text{ A}$$


$$\mathbf{I}_{ac} = 301.87 \angle -198.69^\circ \text{ A}$$

$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = 522.86 \angle -48.69^\circ \text{ A}$$

Since we have a balanced three-phase circuit and a negative phase sequence we have:

$$\mathbf{I}_{bB} = 522.86 \angle 71.31^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 522.86 \angle -168.69^\circ \text{ A}$$

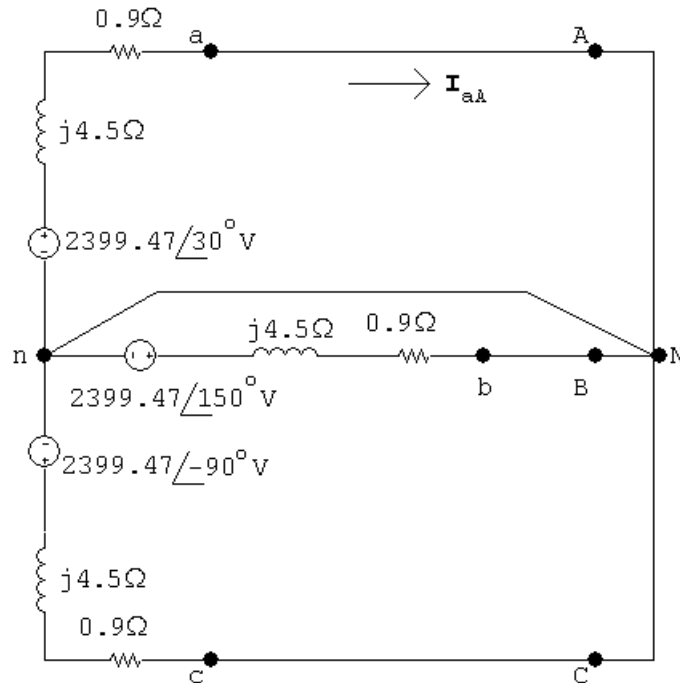
**[d]**

$$\mathbf{I}_{aA} = \frac{2399.47/30^\circ}{0.9 + j4.5} = 522.86/-48.69^\circ \text{ A}$$

Since we have a balanced three-phase circuit and a negative phase sequence we have:

$$\mathbf{I}_{bB} = 522.86/71.31^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 522.86/-168.69^\circ \text{ A}$$

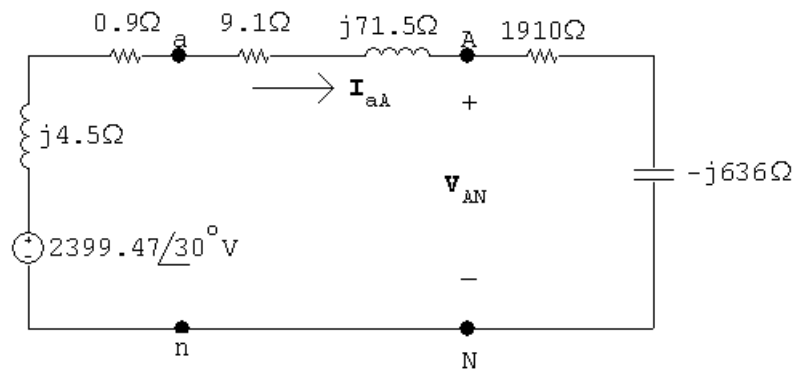**P 11.14 [a]**

$$\mathbf{I}_{aA} = \frac{2399.47/30^\circ}{1920 - j560} = 1.2/46.26^\circ \text{ A}$$

$$\mathbf{V}_{AN} = (1910 - j636)(1.2/46.26^\circ) = 2415.19/27.84^\circ \text{ V}$$


$$|\mathbf{V}_{AB}| = \sqrt{3}(2415.19) = 4183.23 \text{ V}$$

$$[c] \quad |I_{ab}| = \frac{1.2}{\sqrt{3}} = 0.69 \text{ A}$$

$$[d] \quad V_{an} = (1919.1 - j564.5)(1.2/\underline{46.26^\circ}) = 2400/\underline{29.87^\circ} \text{ V}$$

$$|V_{ab}| = \sqrt{3}(2400) = 4156.92 \text{ V}$$

P 11.15 [a]

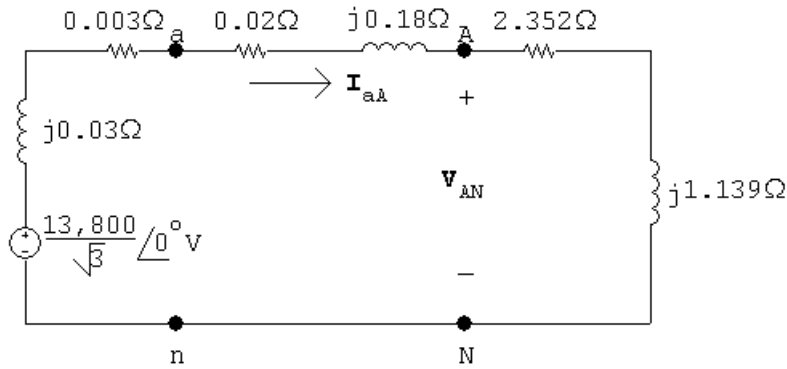

$$[b] \quad I_{aA} = \frac{13,800}{\sqrt{3}(2.375 + j1.349)} = 2917/\underline{-29.6^\circ} \text{ A}$$

$$|I_{aA}| = 2917 \text{ A}$$

$$[c] \quad V_{AN} = (2.352 + j1.139)(2917/\underline{-29.6^\circ}) = 7622.94/\underline{-3.76^\circ} \text{ V}$$

$$|V_{AB}| = \sqrt{3}|V_{AN}| = 13,203.31 \text{ V}$$

$$[d] \quad V_{an} = (2.372 + j1.319)(2917/\underline{-29.6^\circ}) = 7616.93/\underline{-0.52^\circ} \text{ V}$$

$$|V_{ab}| = \sqrt{3}|V_{an}| = 13,712.52 \text{ V}$$

$$[e] \quad |I_{AB}| = \frac{|I_{aA}|}{\sqrt{3}} = 1684.13 \text{ A}$$

$$[f] \quad |I_{ab}| = |I_{AB}| = 1684.13 \text{ A}$$

P 11.16 [a]  $I_{AB} = \frac{4160/\underline{0^\circ}}{160 + j120} = 20.8/\underline{-36.87^\circ} \text{ A}$

$$I_{BC} = 20.8/\underline{83.13^\circ} \text{ A}$$

$$I_{CA} = 20.8/\underline{-156.87^\circ} \text{ A}$$

[b]  $I_{aA} = \sqrt{3}/\underline{30^\circ} I_{AB} = 36.03/\underline{-6.87^\circ} \text{ A}$

$$I_{bB} = 36.03/\underline{113.13^\circ} \text{ A}$$

$$I_{cC} = 36.03/\underline{-126.87^\circ} \text{ A}$$

[c]  $I_{ba} = I_{AB} = 20.8/\underline{-36.87^\circ} \text{ A};$

$$I_{cb} = I_{BC} = 20.8/\underline{83.13^\circ} \text{ A};$$

$$I_{ac} = I_{CA} = 20.8/\underline{-156.87^\circ} \text{ A};$$

P 11.17 [a]  $\mathbf{I}_{AB} = \frac{480/0^\circ}{2.4 - j0.7} = 192/\underline{16.26^\circ} \text{ A}$

$$\mathbf{I}_{BC} = \frac{480/120^\circ}{8 + j6} = 48/\underline{83.13^\circ} \text{ A}$$

$$\mathbf{I}_{CA} = \frac{480/-120^\circ}{20} = 24/\underline{-120^\circ} \text{ A}$$

[b]  $\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$   
 $= 210/\underline{20.79^\circ} \text{ A}$

$$\mathbf{I}_{bB} = \mathbf{I}_{BC} - \mathbf{I}_{AB}$$

$$= 178.68/\underline{-178.04^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$


$$= 70.7/\underline{-104.53^\circ} \text{ A}$$

P 11.18 From the solution to Problem 11.17 we have:

$$S_{AB} = (480/0^\circ)(192/\underline{-16.26^\circ}) = 88,473.6 - j25,804.8 \text{ VA}$$

$$S_{BC} = (480/120^\circ)(48/\underline{-83.13^\circ}) = 18,432.0 + j13,824.0 \text{ VA}$$
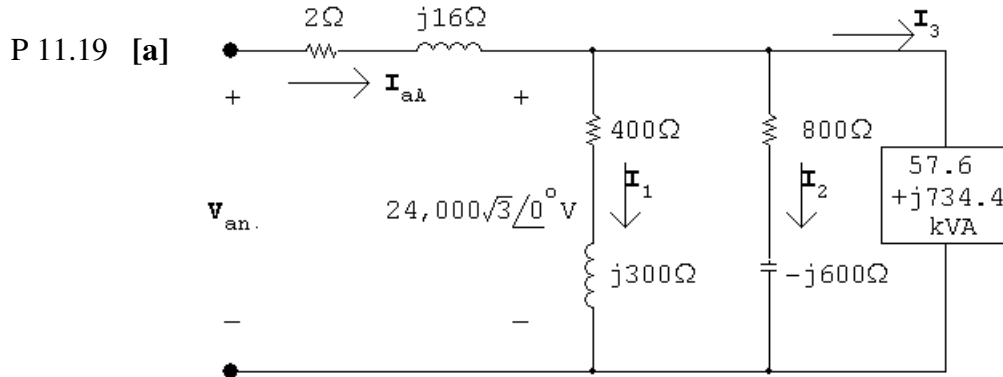
$$S_{CA} = (480/-120^\circ)(24/\underline{120^\circ}) = 11,520 + j0 \text{ VA}$$



$$\mathbf{I}_1 = \frac{24,000\sqrt{3}/0^\circ}{400 + j300} = 66.5 - j49.9 \text{ A}$$

$$\mathbf{I}_2 = \frac{24,000\sqrt{3}/0^\circ}{800 - j600} = 33.3 + j24.9 \text{ A}$$

$$\mathbf{I}_3^* = \frac{57,600 + j734,400}{24,000\sqrt{3}} = 1.4 + j17.7$$

$$\mathbf{I}_3 = 1.4 - j17.7 \text{ A}$$

$$\mathbf{I}_{aA} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 101.2 - j42.7 \text{ A} = 109.8 \angle -22.8^\circ \text{ A}$$

$$\mathbf{V}_{an} = (2 + j16)(101.2 - j42.7) + 24,000\sqrt{3} = 42,456.2 + j1533.2 \text{ V}$$

$$\begin{aligned} S_\phi &= \mathbf{V}_{an} \mathbf{I}_{aA}^* = (42,456.2 + j1533.8)(101.2 + j42.7) \\ &= 4,229.2 + j1964.0 \text{ kVA} \end{aligned}$$

$$S_T = 3S_\phi = 12,687.7 + j9892.1 \text{ kVA}$$

$$\text{[b]} \quad S_{1/\phi} = 24,000\sqrt{3}(66.5 + j49.9) = 2765.0 + j2073.8 \text{ kVA}$$


$$S_{2/\phi} = 24,000\sqrt{3}(33.3 - j24.9) = 1382.5 - j1036.9 \text{ kVA}$$

$$S_{3/\phi} = 57.6 + j734.4 \text{ kVA}$$

$$S_\phi(\text{load}) = 4205.1 + j1771.3 \text{ kVA}$$

$$\% \text{ delivered} = \left( \frac{4205.1}{4229.2} \right) (100) = 99.4\%$$

P 11.20 [a]

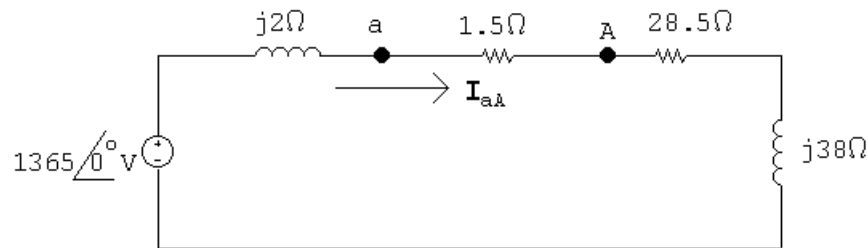

$$\mathbf{I}_{aA} = \frac{1365 \angle 0^\circ}{30 + j40} = 27.3 \angle -53.13^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{I}_{aA}}{\sqrt{3}} \angle 150^\circ = 15.76 \angle 96.87^\circ \text{ A}$$

$$\text{[b]} \quad S_{g/\phi} = -1365 \mathbf{I}_{aA}^* = -22,358.7 - j29,811.6 \text{ VA}$$

$$\therefore P_{\text{developed/phase}} = 22.359 \text{ kW}$$

$$P_{\text{absorbed/phase}} = |\mathbf{I}_{aA}|^2 28.5 = 21.241 \text{ kW}$$

$$\% \text{ delivered} = \frac{21.241}{22.359} (100) = 95\%$$

P 11.21 Let  $p_a$ ,  $p_b$ , and  $p_c$  represent the instantaneous power of phases a, b, and c, respectively. Then assuming a positive phase sequence, we have

$$p_a = v_{an} i_{aA} = [V_m \cos \omega t][I_m \cos(\omega t - \theta_\phi)]$$

$$p_b = v_{bn} i_{bB} = [V_m \cos(\omega t - 120^\circ)][I_m \cos(\omega t - \theta_\phi - 120^\circ)]$$

$$p_c = v_{cn} i_{cC} = [V_m \cos(\omega t + 120^\circ)][I_m \cos(\omega t - \theta_\phi + 120^\circ)]$$

The total instantaneous power is  $p_T = p_a + p_b + p_c$ , so

$$p_T = V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \cos(\omega t - 120^\circ) \cos(\omega t - \theta_\phi - 120^\circ) \\ + \cos(\omega t + 120^\circ) \cos(\omega t - \theta_\phi + 120^\circ)]$$

Now simplify using trigonometric identities. In simplifying, collect the coefficients of  $\cos(\omega t - \theta_\phi)$  and  $\sin(\omega t - \theta_\phi)$ . We get


$$p_T = V_m I_m [\cos \omega t (1 + 2 \cos^2 120^\circ) \cos(\omega t - \theta_\phi) \\ + 2 \sin \omega t \sin^2 120^\circ \sin(\omega t - \theta_\phi)] \\ = 1.5 V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \sin \omega t \sin(\omega t - \theta_\phi)] \\ = 1.5 V_m I_m \cos \theta_\phi$$

P 11.22 [a]  $S_{1/\phi} = 40,000(0.96) - j40,000(0.28) = 38,400 - j11,200 \text{ VA}$

$$S_{2/\phi} = 60,000(0.8) + j60,000(0.6) = 48,000 + j36,000 \text{ VA}$$

$$S_{3/\phi} = 33,600 + j5200 \text{ VA}$$
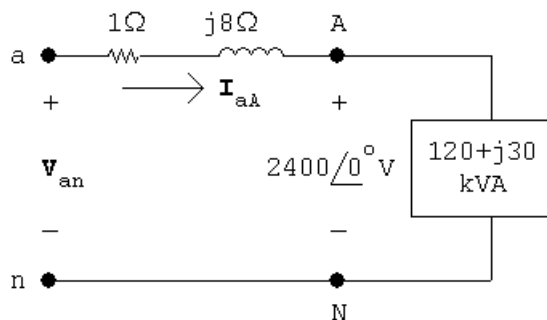
$$S_{T/\phi} = S_1 + S_2 + S_3 = 120,000 + j30,000 \text{ VA}$$



$$\therefore \mathbf{I}_{aA}^* = \frac{120,000 + j30,000}{2400} = 50 + j12.5$$

$$\therefore \mathbf{I}_{aA} = 50 - j12.5 \text{ A}$$

$$\mathbf{V}_{an} = 2400 + (50 - j12.5)(1 + j8) = 2550 + j387.5 = 2579.27 \angle 8.64^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(2579.27) = 4467.43 \text{ V}$$

$$\text{[b]} S_{g/\phi} = (2550 + j387.5)(50 + j12.5) = 122,656.25 + j51,250 \text{ VA}$$

$$\% \text{ efficiency} = \frac{120,000}{122,656.25}(100) = 97.83\%$$

$$\text{P 11.23 [a]} S_1 = (4.864 + j3.775) \text{ kVA}$$

$$S_2 = 17.636(0.96) + j17.636(0.28) = (16.931 + j4.938) \text{ kVA}$$

$$\sqrt{3}V_L I_L \sin \theta_3 = 13,853; \quad \sin \theta_3 = \frac{13,853}{\sqrt{3}(208)(73.8)} = 0.521$$

$$\text{Therefore } \cos \theta_3 = 0.854$$

Therefore

$$P_3 = \frac{13,853}{0.521} \times 0.854 = 22,693.58 \text{ W}$$

$$S_3 = 22.694 + j13.853 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 44.49 + j22.57 \text{ kVA}$$


$$S_{T/\phi} = \frac{1}{3}S_T = 14.83 + j7.52 \text{ kVA}$$

$$\frac{208}{\sqrt{3}}\mathbf{I}_{aA}^* = (14.83 + j7.52)10^3; \quad \mathbf{I}_{aA}^* = 123.49 + j62.64 \text{ A}$$

$$\mathbf{I}_{aA} = 123.49 - j62.64 = 138.46 \angle -26.90^\circ \text{ A (rms)}$$

$$\text{[b]} \text{ pf} = \cos(-26.90^\circ) = 0.892 \text{ lagging}$$

P 11.24

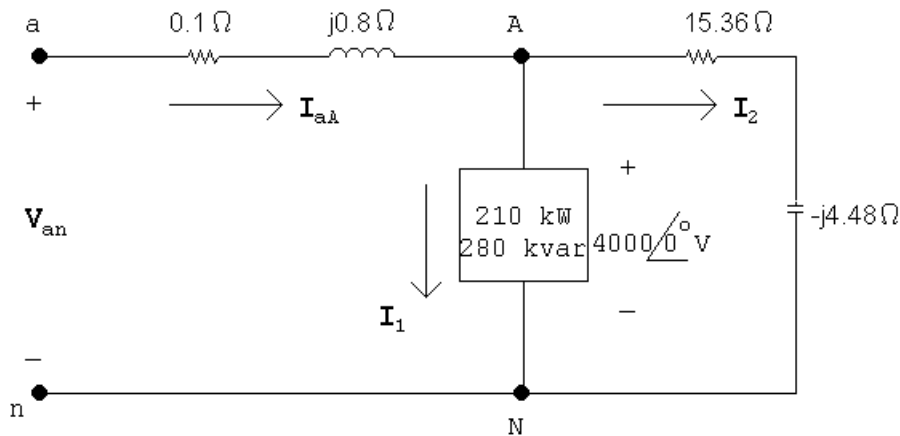

$$4000\mathbf{I}_1^* = (210 + j280)10^3$$

$$\mathbf{I}_1^* = \frac{210}{4} + j\frac{280}{4} = 52.5 + j70 \text{ A}$$

$$\mathbf{I}_1 = 52.5 - j70 \text{ A}$$

$$\mathbf{I}_2 = \frac{4000/\underline{0^\circ}}{15.36 - j4.48} = 240 + j70 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = \mathbf{I}_1 + \mathbf{I}_2 = 292.5 + j0 \text{ A}$$

$$\mathbf{V}_{an} = 4000 + j0 + 292.5(0.1 + j0.8) = 4036.04/\underline{3.32^\circ} \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}|\mathbf{V}_{an}| = 6990.62 \text{ V}$$

P 11.25 [a]  $P_{\text{OUT}} = 746 \times 100 = 74,600 \text{ W}$

$$P_{\text{IN}} = 74,600/(0.97) = 76,907.22 \text{ W}$$

$$\sqrt{3}V_L I_L \cos \theta = 76,907.22$$


$$I_L = \frac{76,907.22}{\sqrt{3}(208)(0.88)} = 242.58 \text{ A}$$

[b]  $Q = \sqrt{3}V_L I_L \sin \phi = \sqrt{3}(208)(242.58)(0.475) = 41,510.12 \text{ VAR}$

P 11.26 [a]  $\mathbf{I}_{aA}^* = \frac{(160 + j46.67)10^3}{1200} = 133.3 + j38.9$

$$\mathbf{I}_{aA} = 133.3 - j38.9 \text{ A}$$
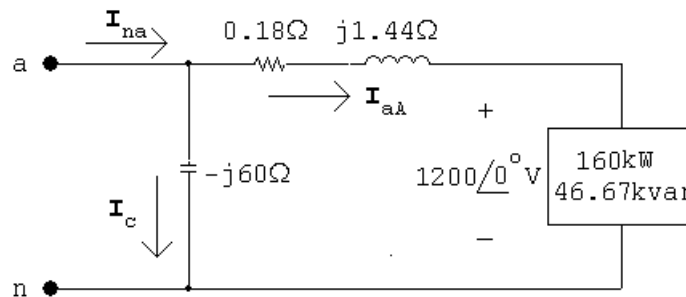
$$\mathbf{V}_{an} = 1200 + (133.3 - j38.9)(0.18 + j1.44) = 1280 + j185 \text{ V}$$



$$\mathbf{I}_C = \frac{1280 + j185}{-j60} = -3.1 + j21.3 \text{ A}$$

$$\mathbf{I}_{na} = (\mathbf{I}_{aA} + \mathbf{I}_C) = -130.3 - j17.6 = 131.4/\underline{7.7^\circ} \text{ A}$$

$$[b] S_{g/\phi} = (1280 + j185)(-130.3 - j17.6) = -163,472 - j46,567.4 \text{ VA}$$

$$S_{gT} = 3S_{g/\phi} = -490.4 - j139.7 \text{ kVA}$$

Therefore, the source is delivering 490.4 kW and 139.7 kvars.


$$[c] P_{\text{del}} = 490.4 \text{ kW}$$

$$P_{\text{abs}} = 3(160,000) + 3|\mathbf{I}_{\text{aA}}|^2(0.18) \\ = 490.4 \text{ kW} = P_{\text{del}}$$

$$[d] Q_{\text{del}} = 3|\mathbf{I}_C|^2(60) + 139.7 \times 10^3 = 223.3 \text{ kVAR}$$

$$Q_{\text{abs}} = 3(46,666) + 3|\mathbf{I}_{\text{aA}}|^2(1.44) \\ = 223.3 \text{ kVAR} = Q_{\text{del}}$$

P 11.27 [a]

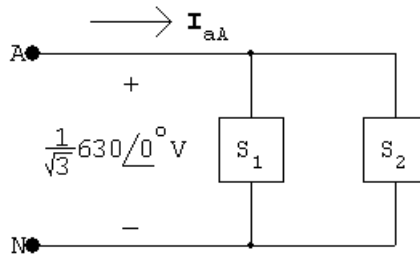

$$S_{s/\phi} = \frac{1}{3}(60)(0.96 - j0.28) \times 10^3 = 19.2 - j5.6 \text{ kVA}$$

$$S_{1/\phi} = 15 \text{ kVA}$$


$$S_{2/\phi} = S_{s/\phi} - S_{1/\phi} = 4.2 - j5.6 \text{ kVA}$$

$$\therefore \mathbf{I}_2^* = \frac{4200 - j5600}{630/\sqrt{3}} = 11.547 - j15.396 \text{ A}$$

$$\mathbf{I}_2 = 11.547 + j15.396 \text{ A}$$


$$Z_y = \frac{630\angle 0^\circ / \sqrt{3}}{\mathbf{I}_2} = 11.34 - j15.12 \Omega$$
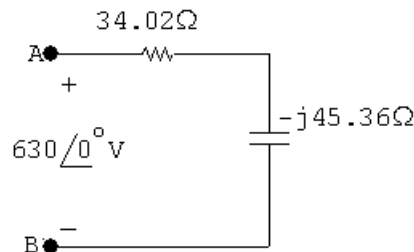
$$Z_\Delta = 3Z_y = 34.02 - j45.36 \Omega$$



$$\text{[b]} \quad R = \frac{(630/\sqrt{3})^2}{4200} = 31.5 \, \Omega; \quad R_{\Delta} = 3R = 94.5 \, \Omega$$
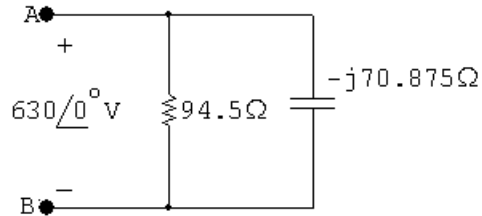
$$X_L = \frac{(630/\sqrt{3})^2}{-5600} = -23.625 \, \Omega; \quad X_{\Delta} = 3X_L = -70.875 \, \Omega$$




P 11.28 Assume a  $\Delta$ -connect load (series):

$$S_{\phi} = \frac{1}{3}(96 \times 10^3)(0.8 + j0.6) = 25,600 + j19,200 \text{ VA}$$


$$Z_{\Delta\phi}^* = \frac{|480|^2}{25,600 + j19,200} = 5.76 - j4.32 \, \Omega$$
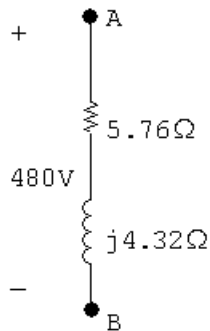
$$Z_{\Delta\phi} = 5.76 + j4.32 \, \Omega$$



Now assume a Y-connected load (series):
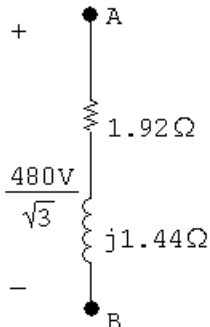
$$Z_{Y\phi} = \frac{1}{3}Z_{\Delta\phi} = 1.92 + j1.44 \, \Omega$$




Now assume a  $\Delta$ -connected load (parallel):

$$P_{\phi} = \frac{|480|^2}{R_{\Delta}}$$

$$R_{\Delta\phi} = \frac{|480|^2}{25,600} = 9\ \Omega$$

$$Q_{\phi} = \frac{|480|^2}{X_{\Delta}}$$


$$X_{\Delta\phi} = \frac{|480|^2}{19,200} = 12\ \Omega$$

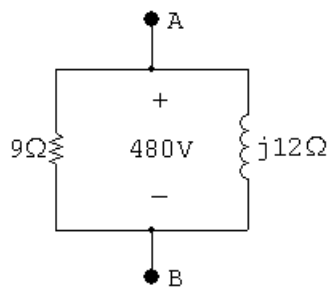

Now assume a Y-connected load (parallel):

$$R_{Y\phi} = \frac{1}{3}R_{\Delta\phi} = 3\ \Omega$$

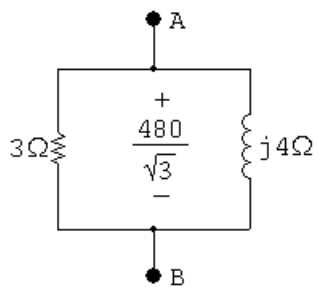
$$X_{Y\phi} = \frac{1}{3}X_{\Delta\phi} = 4\ \Omega$$



$$\text{P 11.29 } S_{g/\phi} = \frac{1}{3}(41.6)(0.707 + j0.707) \times 10^3 = 9803.73 + j9806.69 \text{ VA}$$

$$\mathbf{I}_{aA}^* = \frac{9803.73 + j9803.73}{240/\sqrt{3}} = 70.75 + j70.77 \text{ A}$$
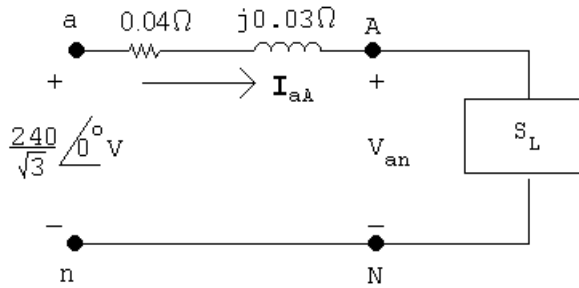
$$\mathbf{I}_{aA} = 70.75 - j70.77 \text{ A}$$



$$\begin{aligned} \mathbf{V}_{AN} &= \frac{240}{\sqrt{3}} - (0.04 + j0.03)(70.75 - j70.77) \\ &= 133.61 + j0.71 = 133.61 \angle 0.30^\circ \text{ V} \end{aligned}$$

$$|\mathbf{V}_{AB}| = \sqrt{3}(133.61) = 231.42 \text{ V}$$

$$[\text{b}] S_{L/\phi} = (133.61 + j0.71)(70.76 + j70.76) = 9403.1 + j9506.3 \text{ VA}$$

$$S_L = 3S_{L/\phi} = 28,209 + j28,519 \text{ VA}$$

Check:

$$S_g = 41,600(0.707 + j0.707) = 29,411 + j29,420 \text{ VA}$$


$$P_\ell = 3|\mathbf{I}_{aA}|^2(0.04) = 1202 \text{ W}$$

$$P_g = P_L + P_\ell = 28,209 + 1202 = 29,411 \text{ W} \quad (\text{checks})$$

$$Q_\ell = 3|\mathbf{I}_{aA}|^2(0.03) = 901 \text{ VAR}$$

$$Q_g = Q_L + Q_\ell = 28,519 + 901 = 29,420 \text{ VAR} \quad (\text{checks})$$

P 11.30 [a]

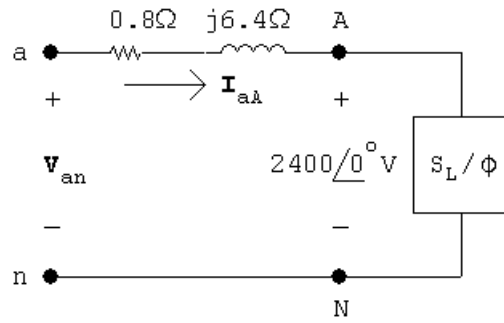

$$S_{L/\phi} = \frac{1}{3} \left[ 720 + j \frac{720}{0.8} (0.6) \right] 10^3 = 240,000 + j180,000 \text{ VA}$$


$$\mathbf{I}_{aA}^* = \frac{240,000 + j180,000}{2400} = 100 + j75 \text{ A}$$

$$\mathbf{I}_{aA} = 100 - j75 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= 2400 + (0.8 + j6.4)(100 - j75) \\ &= 2960 + j580 = 3016.29 \angle 11.09^\circ \text{ V} \end{aligned}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(3016.29) = 5224.37 \text{ V}$$

[b]

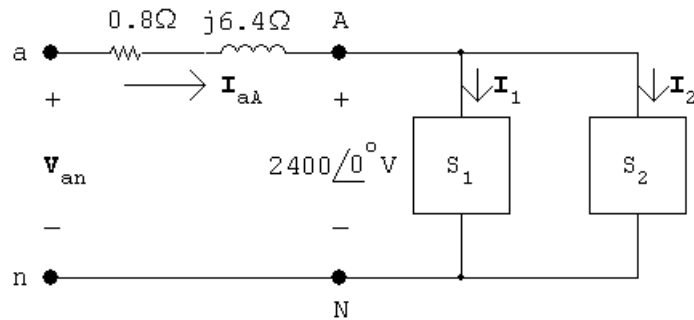

$$\mathbf{I}_1 = 100 - j75 \text{ A} \quad (\text{from part [a]})$$

$$S_2 = 0 - j \frac{1}{3} (576) \times 10^3 = -j192,000 \text{ VAR}$$

$$\mathbf{I}_2^* = \frac{-j192,000}{2400} = -j80 \text{ A}$$

$$\therefore \mathbf{I}_2 = j80 \text{ A}$$

$$\mathbf{I}_{aA} = 100 - j75 + j80 = 100 + j5 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= 2400 + (100 + j5)(0.8 + j6.4) \\ &= 2448 + j644 = 2531.29 \angle 14.74^\circ \text{ V} \end{aligned}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(2531.29) = 4384.33 \text{ V}$$

**[c]**  $|\mathbf{I}_{aA}| = 125 \text{ A}$

$$P_{\text{loss}/\phi} = (125)^2(0.8) = 12,500 \text{ W}$$

$$P_{g/\phi} = 240,000 + 12,500 = 252.5 \text{ kW}$$

$$\% \eta = \frac{240}{252.5}(100) = 95.05\%$$

**[d]**  $|\mathbf{I}_{aA}| = 100.125 \text{ A}$

$$P_{\ell/\phi} = (100.125)^2(0.8) = 8020 \text{ W}$$

$$\% \eta = \frac{240,000}{248,200}(100) = 96.77\%$$

**[e]**  $Z_{\text{cap}/Y} = -j \frac{2400^2}{-192,000} = -j30 \Omega$

$$Z_{\text{cap}/\Delta} = 3Z_{\text{cap}/Y} = -j90 \Omega$$

$$\therefore \frac{1}{\omega C} = 90; \quad C = \frac{1}{(90)(120\pi)} = 29.47 \mu\text{F}$$

P 11.31 **[a]** From Assessment Problem 11.9,  $\mathbf{I}_{aA} = (101.8 - j135.7) \text{ A}$

Therefore  $\mathbf{I}_{\text{cap}} = j135.7 \text{ A}$

Therefore  $Z_{CY} = \frac{2450/\sqrt{3}}{j135.7} = -j10.42 \Omega$

Therefore  $C_Y = \frac{1}{(10.42)(2\pi)(60)} = 254.5 \mu\text{F}$

$$Z_{C\Delta} = (-j10.42)(3) = -j31.26 \Omega$$

Therefore  $C_{\Delta} = \frac{254.5}{3} = 84.84 \mu\text{F}$

**[b]**  $C_Y = 254.5 \mu\text{F}$

**[c]**  $|\mathbf{I}_{aA}| = 101.8 \text{ A}$

$$\text{P 11.32 } Z_\phi = |Z|/\theta = \frac{\mathbf{V}_{\text{AN}}}{\mathbf{I}_{\text{aA}}}$$

$$\theta = \angle \mathbf{V}_{\text{AN}} - \angle \mathbf{I}_{\text{aA}}$$

$$\theta_1 = \angle \mathbf{V}_{\text{AB}} - \angle \mathbf{I}_{\text{aA}}$$

For a positive phase sequence,

$$\angle \mathbf{V}_{\text{AB}} = \angle \mathbf{V}_{\text{AN}} + 30^\circ$$

Thus,

$$\theta_1 = \angle \mathbf{V}_{\text{AN}} + 30^\circ - \angle \mathbf{I}_{\text{aA}} = \theta + 30^\circ$$

Similarly,

$$Z_\phi = |Z|/\theta = \frac{\mathbf{V}_{\text{CN}}}{\mathbf{I}_{\text{cC}}}$$

$$\theta = \angle \mathbf{V}_{\text{CN}} - \angle \mathbf{I}_{\text{cC}}$$

$$\theta_2 = \angle \mathbf{V}_{\text{CB}} - \angle \mathbf{I}_{\text{cC}}$$

For a positive phase sequence,

$$\angle \mathbf{V}_{\text{CB}} = \angle \mathbf{V}_{\text{BA}} - 120^\circ = \angle \mathbf{V}_{\text{AB}} + 60^\circ$$

$$\angle \mathbf{I}_{\text{cC}} = \angle \mathbf{I}_{\text{aA}} + 120^\circ$$

Thus,

$$\begin{aligned} \theta_2 &= \angle \mathbf{V}_{\text{AB}} + 60^\circ - \angle \mathbf{I}_{\text{aA}} - 120^\circ = \theta_1 - 60^\circ \\ &= \theta + 30^\circ - 60^\circ = \theta - 30^\circ \end{aligned}$$

P 11.33 Use values from the negative sequence part of Example 11.1 — part (g):

$$\mathbf{V}_{\text{AB}} = 199.58/\underline{-31.19^\circ} \text{ V}$$

$$\mathbf{I}_{\text{aA}} = 2.5/\underline{-36.87^\circ} \text{ A}$$

$$W_{m1} = |\mathbf{V}_{\text{AB}}||\mathbf{I}_{\text{aA}}| \cos(\angle \mathbf{V}_{\text{AB}} - \angle \mathbf{I}_{\text{aA}}) = (199.58)(2.4) \cos(5.68^\circ) = 476.63 \text{ W}$$

$$W_{m2} = |\mathbf{V}_{\text{CB}}||\mathbf{I}_{\text{cC}}| \cos(\angle \mathbf{V}_{\text{CB}} - \angle \mathbf{I}_{\text{cC}}) = (199.58)(2.4) \cos(65.68^\circ) = 197.29 \text{ W}$$

$$\text{CHECK: } W_1 + W_2 = 673.9 = (2.4)^2(39)(3) = 673.9 \text{ W}$$

$$\begin{aligned}
\text{P 11.34 [a]} \quad W_2 - W_1 &= V_L I_L [\cos(\theta - 30^\circ) - \cos(\theta + 30^\circ)] \\
&= V_L I_L [\cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ \\
&\quad - \cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ] \\
&= 2V_L I_L \sin \theta \sin 30^\circ = V_L I_L \sin \theta,
\end{aligned}$$

$$\text{therefore } \sqrt{3}(W_2 - W_1) = \sqrt{3}V_L I_L \sin \theta = Q_T$$

$$\text{[b]} \quad Z_\phi = (8 + j6) \Omega$$

$$Q_T = \sqrt{3}[2476.25 - 979.75] = 2592 \text{ VAR},$$

$$Q_T = 3(12)^2(6) = 2592 \text{ VAR};$$

$$Z_\phi = (8 - j6) \Omega$$

$$Q_T = \sqrt{3}[979.75 - 2476.25] = -2592 \text{ VAR},$$

$$Q_T = 3(12)^2(-6) = -2592 \text{ VAR};$$

$$Z_\phi = 5(1 + j\sqrt{3}) \Omega$$

$$Q_T = \sqrt{3}[2160 - 0] = 3741.23 \text{ VAR},$$

$$Q_T = 3(12)^2(5\sqrt{3}) = 3741.23 \text{ VAR};$$

$$Z_\phi = 10 \angle -75^\circ \Omega$$

$$Q_T = \sqrt{3}[-645.53 - 1763.63] = -4172.80 \text{ VAR},$$

$$Q_T = 3(12)^2[-10 \sin 75^\circ] = -4172.80 \text{ VAR}$$

$$\text{P 11.35} \quad \mathbf{I}_{aA} = (\mathbf{V}_{AN}/Z_\phi) = |\mathbf{I}_L| \angle -\theta_\phi \mathbf{A},$$

$$Z_\phi = |Z| \angle \theta_\phi, \quad \mathbf{V}_{BC} = |\mathbf{V}_L| \angle -90^\circ \mathbf{V},$$

$$W_m = |\mathbf{V}_L| |\mathbf{I}_L| \cos[-90^\circ - (-\theta_\phi)]$$

$$= |\mathbf{V}_L| |\mathbf{I}_L| \cos(\theta_\phi - 90^\circ)$$

$$= |\mathbf{V}_L| |\mathbf{I}_L| \sin \theta_\phi,$$

$$\text{therefore } \sqrt{3}W_m = \sqrt{3}|\mathbf{V}_L| |\mathbf{I}_L| \sin \theta_\phi = Q_{\text{total}}$$

P 11.36 [a]  $Z = 16 - j12 = 20/\underline{-36.87^\circ} \Omega$

$$\mathbf{V}_{AN} = 680/\underline{0^\circ} \text{ V}; \quad \therefore \mathbf{I}_{aA} = 34/\underline{36.87^\circ} \text{ A}$$

$$\mathbf{V}_{BC} = \mathbf{V}_{BN} - \mathbf{V}_{CN} = 680\sqrt{3}/\underline{-90^\circ} \text{ V}$$

$$W_m = (680\sqrt{3})(34) \cos(-90 - 36.87^\circ) = -24,027.0 \text{ W}$$

$$\sqrt{3}W_m = -41,616.0 \text{ VAR}$$

[b]  $Q_\phi = (34^2)(-12) = -13,872 \text{ VAR}$

$$Q_T = 3Q_\phi = -41,616 \text{ VAR} = \sqrt{3}W_m$$

P 11.37 [a]  $Z_\phi = 160 + j120 = 200/\underline{36.87^\circ} \Omega$

$$S_\phi = \frac{4160^2}{160 - j120} = 69,222.4 + j51,916.8 \text{ VA}$$

$$S_T = 3S_\phi = 207,667.2 + j155,750.4 \text{ VA}$$

[b]  $W_{m1} = (4160)(36.03) \cos(0 + 6.87^\circ) = 148,808.64 \text{ W}$

$$W_{m2} = (4160)(36.03) \cos(-60^\circ + 126.87^\circ) = 58,877.55 \text{ W}$$

Check:  $P_T = 207.7 \text{ kW} = W_{m1} + W_{m2}.$

P 11.38 [a]  $\mathbf{I}_{aA}^* = \frac{144(0.96 - j0.28)10^3}{7200} = 20/\underline{-16.26^\circ} \text{ A}$

$$\mathbf{V}_{BN} = 7200/\underline{-120^\circ} \text{ V}; \quad \mathbf{V}_{CN} = 7200/\underline{120^\circ} \text{ V}$$

$$\mathbf{V}_{BC} = \mathbf{V}_{BN} - \mathbf{V}_{CN} = 7200\sqrt{3}/\underline{-90^\circ} \text{ V}$$

$$\mathbf{I}_{bB} = 20/\underline{-103.74^\circ} \text{ A}$$

$$W_{m1} = (7200\sqrt{3})(20) \cos(-90^\circ + 103.74^\circ) = 242,278.14 \text{ W}$$

[b] Current coil in line aA, measure  $\mathbf{I}_{aA}$ .

Voltage coil across AC, measure  $\mathbf{V}_{AC}$ .

[c]  $I_{aA} = 20/\underline{16.76^\circ} \text{ A}$

$$\mathbf{V}_{AC} = \mathbf{V}_{AN} - \mathbf{V}_{CN} = 7200\sqrt{3}/\underline{-30^\circ} \text{ V}$$

$$W_{m2} = (7200\sqrt{3})(20) \cos(-30^\circ - 16.26^\circ) = 172,441.86 \text{ W}$$

[d]  $W_{m1} + W_{m2} = 414.72 \text{ kW}$

$$P_T = 432,000(0.96) = 414.72 \text{ kW} = W_{m1} + W_{m2}$$

P 11.39 [a]  $W_1 = |\mathbf{V}_{BA}| |\mathbf{I}_{bB}| \cos \theta_1$

Negative phase sequence:

$$\mathbf{V}_{BA} = 240\sqrt{3}/\underline{150^\circ} \text{ V}$$

$$\mathbf{I}_{aA} = \frac{240/\underline{0^\circ}}{13.33/\underline{-30^\circ}} = 18/\underline{30^\circ} \text{ A}$$

$$\mathbf{I}_{bB} = 18/\underline{150^\circ} \text{ A}$$

$$W_1 = (18)(240)\sqrt{3} \cos 0^\circ = 7482.46 \text{ W}$$

$$W_2 = |\mathbf{V}_{CA}| |\mathbf{I}_{cC}| \cos \theta_2$$

$$\mathbf{V}_{CA} = 240\sqrt{3}/\underline{-150^\circ} \text{ V}$$

$$\mathbf{I}_{cC} = 18/\underline{-90^\circ} \text{ A}$$

$$W_2 = (18)(240)\sqrt{3} \cos(-60^\circ) = 3741.23 \text{ W}$$

[b]  $P_\phi = (18)^2(40/3) \cos(-30^\circ) = 3741.23 \text{ W}$

$$P_T = 3P_\phi = 11,223.69 \text{ W}$$

$$W_1 + W_2 = 7482.46 + 3741.23 = 11,223.69 \text{ W}$$

$$\therefore W_1 + W_2 = P_T \quad (\text{checks})$$

P 11.40 [a] Negative phase sequence:

$$\mathbf{V}_{AB} = 240\sqrt{3}/\underline{-30^\circ} \text{ V}$$

$$\mathbf{V}_{BC} = 240\sqrt{3}/\underline{90^\circ} \text{ V}$$

$$\mathbf{V}_{CA} = 240\sqrt{3}/\underline{-150^\circ} \text{ V}$$

$$\mathbf{I}_{AB} = \frac{240\sqrt{3}/\underline{-30^\circ}}{20/\underline{30^\circ}} = 20.78/\underline{-60^\circ} \text{ A}$$

$$\mathbf{I}_{BC} = \frac{240\sqrt{3}/\underline{90^\circ}}{60/\underline{0^\circ}} = 6.93/\underline{90^\circ} \text{ A}$$

$$\mathbf{I}_{CA} = \frac{240\sqrt{3}/\underline{-150^\circ}}{40/\underline{-30^\circ}} = 10.39/\underline{-120^\circ} \text{ A}$$

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} + \mathbf{I}_{AC} = 18/\underline{-30^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CB} + \mathbf{I}_{CA} = \mathbf{I}_{CA} - \mathbf{I}_{BC} = 16.75/\underline{-108.06^\circ} \text{ A}$$

$$W_{m1} = 240\sqrt{3}(18) \cos(-30 + 30^\circ) = 7482.46 \text{ W}$$

$$W_{m2} = 240\sqrt{3}(16.75) \cos(-90 + 108.07^\circ) = 6621.23 \text{ W}$$

$$\textbf{[b]} \quad W_{m1} + W_{m2} = 14,103.69 \text{ W}$$

$$P_A = (12\sqrt{3})^2(20 \cos 30^\circ) = 7482.46 \text{ W}$$

$$P_B = (4\sqrt{3})^2(60) = 2880 \text{ W}$$

$$P_C = (6\sqrt{3})^2[40 \cos(-30^\circ)] = 3741.23 \text{ W}$$

$$P_A + P_B + P_C = 14,103.69 = W_{m1} + W_{m2}$$

$$\text{P 11.41} \quad \tan \phi = \frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2} = 0.7498$$

$$\therefore \phi = 36.86^\circ$$

$$\therefore 2400|\mathbf{I}_L| \cos 66.87^\circ = 40,823.09$$

$$|\mathbf{I}_L| = 43.3 \text{ A}$$

$$|Z_\phi| = \frac{2400/\sqrt{3}}{43.3} = 32 \Omega \quad \therefore Z_\phi = 32 \angle 36.87^\circ \Omega$$

$$\text{P 11.42} \quad \textbf{[a]} \quad Z = \frac{1}{3}Z_\Delta = 4.48 + j15.36 = 16 \angle 73.74^\circ \Omega$$

$$\mathbf{I}_{aA} = \frac{600 \angle 0^\circ}{16 \angle 73.74^\circ} = 37.5 \angle -73.74^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 37.5 \angle -193.74^\circ \text{ A}$$

$$\mathbf{V}_{AC} = 600\sqrt{3} \angle -30^\circ \text{ V}$$

$$\mathbf{V}_{BC} = 600\sqrt{3} \angle -90^\circ \text{ V}$$

$$W_1 = (600\sqrt{3})(37.5) \cos(-30 + 73.74^\circ) = 28,156.15 \text{ W}$$

$$W_2 = (600\sqrt{3})(37.5) \cos(-90 + 193.74^\circ) = -9256.15 \text{ W}$$

$$\textbf{[b]} \quad W_1 + W_2 = 18,900 \text{ W}$$

$$P_T = 3(37.5)^2(13.44/3) = 18,900 \text{ W}$$

$$\textbf{[c]} \quad \sqrt{3}(W_1 - W_2) = 64,800 \text{ VAR}$$

$$Q_T = 3(37.5)^2(46.08/3) = 64,800 \text{ VAR}$$

P 11.43 From the solution to Prob. 11.17 we have

$$\mathbf{I}_{aA} = 210 \angle 20.79^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_{bB} = 178.68 \angle -178.04^\circ \text{ A}$$

$$\begin{aligned} \text{[a]} \quad W_1 &= |\mathbf{V}_{ac}| |\mathbf{I}_{aA}| \cos(\theta_{ac} - \theta_{aA}) \\ &= 480(210) \cos(60^\circ - 20.79^\circ) = 78,103.2 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad W_2 &= |\mathbf{V}_{bc}| |\mathbf{I}_{bB}| \cos(\theta_{bc} - \theta_{bB}) \\ &= 480(178.68) \cos(120^\circ + 178.04^\circ) = 40,317.7 \text{ W} \end{aligned}$$

$$\text{[c]} \quad W_1 + W_2 = 118,421 \text{ W}$$

$$P_{AB} = (192)^2(2.4) = 88,473.6 \text{ W}$$


$$P_{BC} = (48)^2(8) = 18,432 \text{ W}$$

$$P_{CA} = (24)^2(20) = 11,520 \text{ W}$$


$$P_{AB} + P_{BC} + P_{CA} = 118,425.7$$

$$\text{therefore } W_1 + W_2 \approx P_{\text{total}} \quad (\text{round-off differences})$$


P 11.44 [a] For one phase,

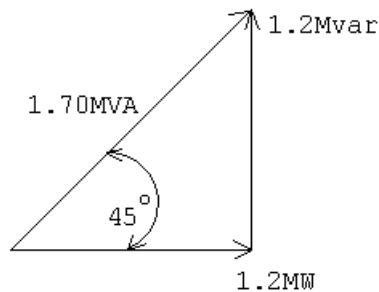


[b]

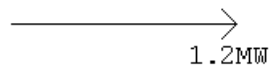

[c]

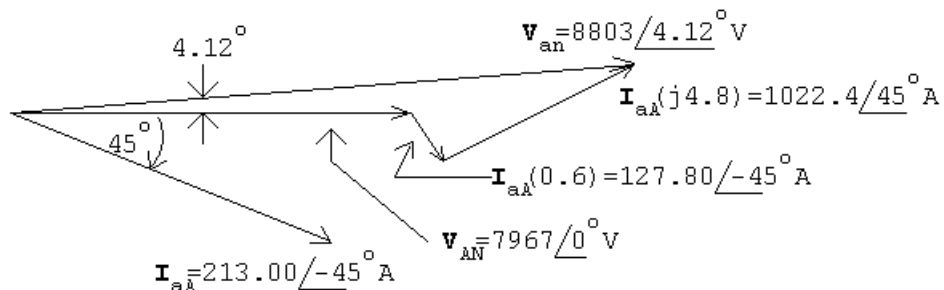

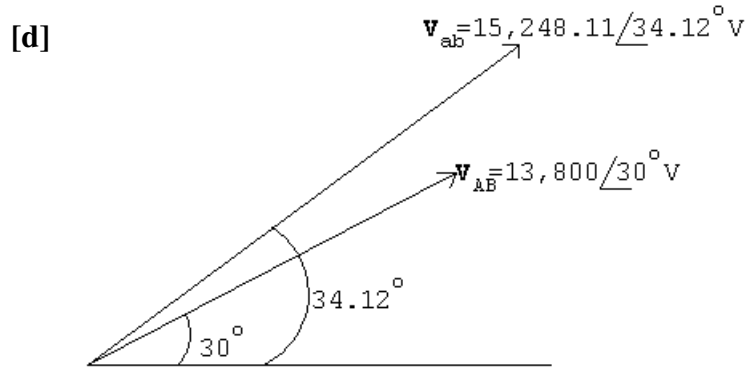

P 11.45 [a]  $Q = \frac{|\mathbf{V}|^2}{X_C}$

$$\therefore |X_C| = \frac{(13,800)^2}{1.2 \times 10^6} = 158.70 \Omega$$

$$\therefore \frac{1}{\omega C} = 158.70; \quad C = \frac{1}{2\pi(60)(158.70)} = 16.71 \mu\text{F}$$

[b]  $|X_C| = \frac{(13,800/\sqrt{3})^2}{1.2 \times 10^6} = \frac{1}{3}(158.70)$

$$\therefore C = 3(16.71) = 50.14 \mu\text{F}$$

P 11.46 If the capacitors remain connected when the substation drops its load, the expression for the line current becomes

$$\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = -j1.2 \times 10^6$$

or  $\mathbf{I}_{aA}^* = -j150.61 \text{ A}$

Hence  $\mathbf{I}_{aA} = j150.61 \text{ A}$

Now,

$$\mathbf{V}_{an} = \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(j150.61) = 7244.49 + j90.37 = 7245.05 \angle 0.71^\circ \text{ V}$$

The magnitude of the line-to-line voltage at the generating plant is

$$|\mathbf{V}_{ab}| = \sqrt{3}(7245.05) = 12,548.80 \text{ V}.$$

This is a problem because the voltage is below the acceptable minimum of 13 kV. Thus when the load at the substation drops off, the capacitors must be switched off.

P 11.47 Before the capacitors are added the total line loss is

$$P_L = 3|150.61 + j150.61|^2(0.6) = 81.66 \text{ kW}$$

After the capacitors are added the total line loss is

$$P_L = 3|150.61|^2(0.6) = 40.83 \text{ kW}$$

Note that adding the capacitors to control the voltage level also reduces the amount of power loss in the lines, which in this example is cut in half.

P 11.48 [a]  $\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = 80 \times 10^3 + j200 \times 10^3 - j1200 \times 10^3$

$$\mathbf{I}_{aA}^* = \frac{80\sqrt{3} - j1000\sqrt{3}}{13.8} = 10.04 - j125.51 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = 10.04 + j125.51 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(10.04 + j125.51) \\ &= 7371.01 + j123.50 = 7372.04 \angle 0.96^\circ \text{ V} \end{aligned}$$

$$\therefore |\mathbf{V}_{ab}| = \sqrt{3}(7372.04) = 12,768.75 \text{ V}$$

[b] Yes, the magnitude of the line-to-line voltage at the power plant is less than the allowable minimum of 13 kV.

P 11.49 [a]  $\frac{13,800}{\sqrt{3}} \mathbf{I}_{aA}^* = (80 + j200) \times 10^3$

$$\mathbf{I}_{aA}^* = \frac{80\sqrt{3} + j200\sqrt{3}}{13.8} = 10.04 + j25.1 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = 10.04 - j25.1 \text{ A}$$

$$\begin{aligned} \mathbf{V}_{an} &= \frac{13,800}{\sqrt{3}} \angle 0^\circ + (0.6 + j4.8)(10.04 - j25.1) \\ &= 8093.95 + j33.13 = 8094.02 \angle 0.23^\circ \text{ V} \end{aligned}$$

$$\therefore |\mathbf{V}_{ab}| = \sqrt{3}(8094.02) = 14,019.25 \text{ V}$$

[b] Yes:  $13 \text{ kV} < 14,019.25 < 14.6 \text{ kV}$

[c]  $P_{\text{loss}} = 3|10.04 + j125.51|^2(0.6) = 28.54 \text{ kW}$

[d]  $P_{\text{loss}} = 3|10.04 + j25.1|^2(0.6) = 1.32 \text{ kW}$

[e] Yes, the voltage at the generating plant is at an acceptable level and the line loss is greatly reduced.