

Sinusoidal Steady State Analysis

Assessment Problems

AP 9.1 [a] $\mathbf{V} = 170\angle -40^\circ \text{ V}$

[b] $10 \sin(1000t + 20^\circ) = 10 \cos(1000t - 70^\circ)$

$\therefore \mathbf{I} = 10\angle -70^\circ \text{ A}$

[c] $\mathbf{I} = 5\angle 36.87^\circ + 10\angle -53.13^\circ$

$= 4 + j3 + 6 - j8 = 10 - j5 = 11.18\angle -26.57^\circ \text{ A}$

[d] $\sin(20,000\pi t + 30^\circ) = \cos(20,000\pi t - 60^\circ)$

Thus,

$\mathbf{V} = 300\angle 45^\circ - 100\angle -60^\circ = 212.13 + j212.13 - (50 - j86.60)$

$= 162.13 + j298.73 = 339.90\angle 61.51^\circ \text{ mV}$

AP 9.2 [a] $v = 18.6 \cos(\omega t - 54^\circ) \text{ V}$

[b] $\mathbf{I} = 20\angle 45^\circ - 50\angle -30^\circ = 14.14 + j14.14 - 43.3 + j25$

$= -29.16 + j39.14 = 48.81\angle 126.68^\circ$

Therefore $i = 48.81 \cos(\omega t + 126.68^\circ) \text{ mA}$

[c] $\mathbf{V} = 20 + j80 - 30\angle 15^\circ = 20 + j80 - 28.98 - j7.76$

$= -8.98 + j72.24 = 72.79\angle 97.08^\circ$

$v = 72.79 \cos(\omega t + 97.08^\circ) \text{ V}$

AP 9.3 [a] $\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$

[b] $Z_L = j\omega L = j200 \Omega$

$$\text{[c]} \quad \mathbf{V}_L = \mathbf{I}Z_L = (10\angle 30^\circ)(200\angle 90^\circ) \times 10^{-3} = 2\angle 120^\circ \text{ V}$$

$$\text{[d]} \quad v_L = 2 \cos(10,000t + 120^\circ) \text{ V}$$

$$\text{AP 9.4 [a]} \quad X_C = \frac{-1}{\omega C} = \frac{-1}{4000(5 \times 10^{-6})} = -50 \Omega$$

$$\text{[b]} \quad Z_C = jX_C = -j50 \Omega$$

$$\text{[c]} \quad \mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{30\angle 25^\circ}{50\angle -90^\circ} = 0.6\angle 115^\circ \text{ A}$$

$$\text{[d]} \quad i = 0.6 \cos(4000t + 115^\circ) \text{ A}$$

$$\text{AP 9.5} \quad \mathbf{I}_1 = 100\angle 25^\circ = 90.63 + j42.26$$

$$\mathbf{I}_2 = 100\angle 145^\circ = -81.92 + j57.36$$

$$\mathbf{I}_3 = 100\angle -95^\circ = -8.72 - j99.62$$

$$\mathbf{I}_4 = -(\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3) = (0 + j0) \text{ A}, \quad \text{therefore} \quad i_4 = 0 \text{ A}$$

$$\text{AP 9.6 [a]} \quad \mathbf{I} = \frac{125\angle -60^\circ}{|Z|\angle \theta_z} = \frac{125}{|Z|}\angle (-60 - \theta_z)^\circ$$

$$\text{But } -60 - \theta_z = -105^\circ \quad \therefore \quad \theta_z = 45^\circ$$


$$Z = 90 + j160 + jX_C$$

$$\therefore X_C = -70 \Omega; \quad X_C = -\frac{1}{\omega C} = -70$$

$$\therefore C = \frac{1}{(70)(5000)} = 2.86 \mu\text{F}$$

$$\text{[b]} \quad \mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{125\angle -60^\circ}{(90 + j90)} = 0.982\angle -105^\circ \text{ A}; \quad \therefore \quad |\mathbf{I}| = 0.982 \text{ A}$$

AP 9.7 [a]

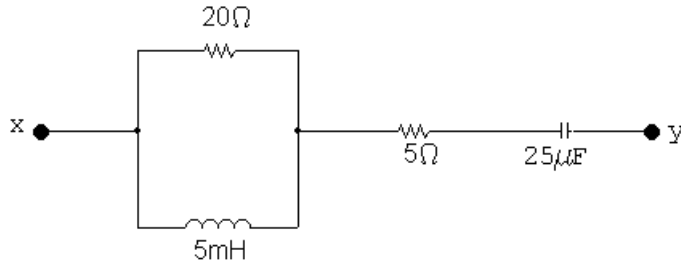

$$\omega = 2000 \text{ rad/s}$$

$$\omega L = 10 \Omega, \quad \frac{-1}{\omega C} = -20 \Omega$$

$$Z_{xy} = 20 \parallel j10 + 5 + j20 = \frac{20(j10)}{(20 + j10)} + 5 - j20$$

$$= 4 + j8 + 5 - j20 = (9 - j12) \Omega$$

[b] $\omega L = 40 \Omega, \quad \frac{-1}{\omega C} = -5 \Omega$

$$Z_{xy} = 5 - j5 + 20 \parallel j40 = 5 - j5 + \left[\frac{(20)(j40)}{20 + j40} \right]$$

$$= 5 - j5 + 16 + j8 = (21 + j3) \Omega$$

[c] $Z_{xy} = \left[\frac{20(j\omega L)}{20 + j\omega L} \right] + \left(5 - \frac{j10^6}{25\omega} \right)$

$$= \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j400\omega L}{400 + \omega^2 L^2} + 5 - \frac{j10^6}{25\omega}$$

The impedance will be purely resistive when the j terms cancel, i.e.,

$$\frac{400\omega L}{400 + \omega^2 L^2} = \frac{10^6}{25\omega}$$

Solving for ω yields $\omega = 4000$ rad/s.

[d] $Z_{xy} = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + 5 = 10 + 5 = 15 \Omega$

AP 9.8 The frequency 4000 rad/s was found to give $Z_{xy} = 15 \Omega$ in Assessment Problem 9.7. Thus,


$$\mathbf{V} = 150 \angle 0^\circ, \quad \mathbf{I}_s = \frac{\mathbf{V}}{Z_{xy}} = \frac{150 \angle 0^\circ}{15} = 10 \angle 0^\circ \text{ A}$$

Using current division,

$$\mathbf{I}_L = \frac{20}{20 + j20}(10) = 5 - j5 = 7.07 \angle -45^\circ \text{ A}$$

$$i_L = 7.07 \cos(4000t - 45^\circ) \text{ A}, \quad I_m = 7.07 \text{ A}$$

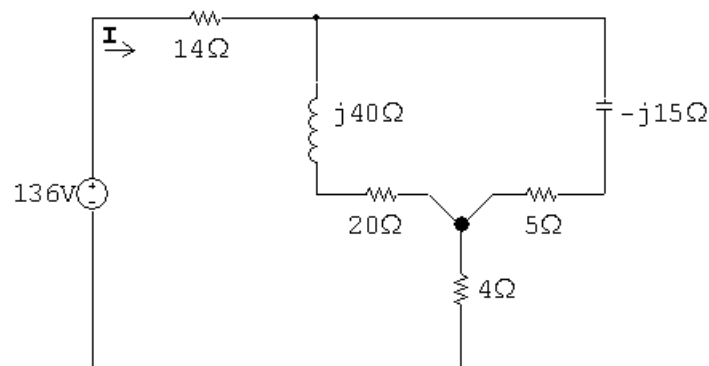AP 9.9 After replacing the delta made up of the 50Ω , 40Ω , and 10Ω resistors with its equivalent wye, the circuit becomes



The circuit is further simplified by combining the parallel branches,

$$(20 + j40) \parallel (5 - j15) = (12 - j16) \Omega$$

$$\text{Therefore } \mathbf{I} = \frac{136 \angle 0^\circ}{14 + 12 - j16 + 4} = 4 \angle 28.07^\circ \text{ A}$$

$$\text{AP 9.10 } \mathbf{V}_1 = 240 \angle 53.13^\circ = 144 + j192 \text{ V}$$

$$\mathbf{V}_2 = 96 \angle -90^\circ = -j96 \text{ V}$$


$$j\omega L = j(4000)(15 \times 10^{-3}) = j60 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60 \Omega$$

Perform source transformations:

$$\frac{\mathbf{V}_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4 \text{ A}$$

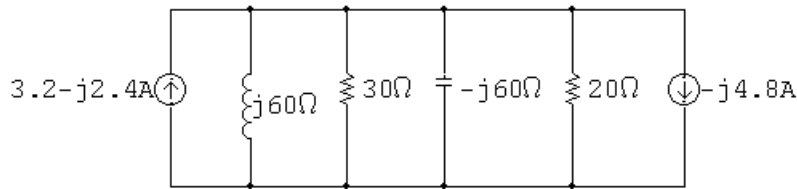
$$\frac{\mathbf{V}_2}{20} = -j \frac{96}{20} = -j4.8 \text{ A}$$



Combine the parallel impedances:

$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$

$$Z = \frac{1}{Y} = 12 \Omega$$

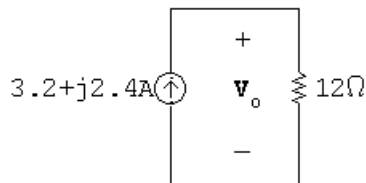

$$\mathbf{V}_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48 \angle 36.87^\circ \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$


AP 9.11 Use the lower node as the reference node. Let \mathbf{V}_1 = node voltage across the $20\ \Omega$ resistor and \mathbf{V}_{Th} = node voltage across the capacitor. Writing the node voltage equations gives us

$$\frac{\mathbf{V}_1}{20} - 2\angle 45^\circ + \frac{\mathbf{V}_1 - 10\mathbf{I}_x}{j10} = 0 \quad \text{and} \quad \mathbf{V}_{Th} = \frac{-j10}{10 - j10}(10\mathbf{I}_x)$$

We also have

$$\mathbf{I}_x = \frac{\mathbf{V}_1}{20}$$

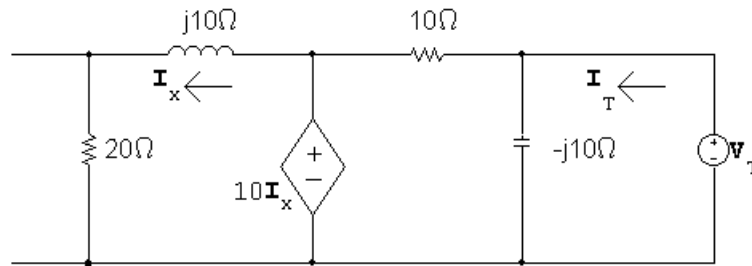Solving these equations for \mathbf{V}_{Th} gives $\mathbf{V}_{Th} = 10\angle 45^\circ \text{ V}$. To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus



It follows from the circuit that


$$10\mathbf{I}_x = (20 + j10)\mathbf{I}_x$$

Therefore

$$\mathbf{I}_x = 0 \quad \text{and} \quad \mathbf{I}_T = \frac{\mathbf{V}_T}{-j10} + \frac{\mathbf{V}_T}{10}$$

$$Z_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T}, \quad \text{therefore} \quad Z_{Th} = (5 - j5)\ \Omega$$

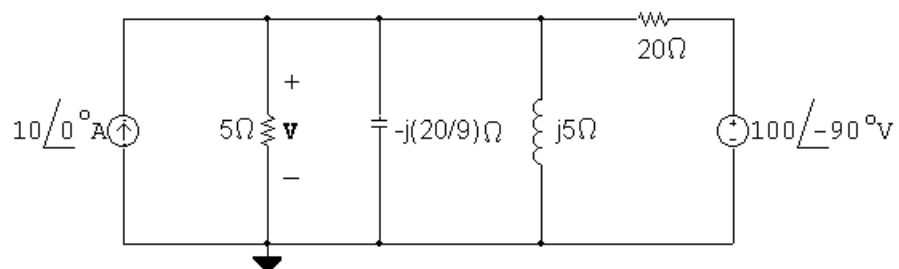AP 9.12 The phasor domain circuit is as shown in the following diagram:



The node voltage equation is

$$-10 + \frac{\mathbf{V}}{5} + \frac{\mathbf{V}}{-j(20/9)} + \frac{\mathbf{V}}{j5} + \frac{\mathbf{V} - 100\angle -90^\circ}{20} = 0$$

Therefore $\mathbf{V} = 10 - j30 = 31.62\angle -71.57^\circ$

Therefore $v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$

AP 9.13 Let \mathbf{I}_a , \mathbf{I}_b , and \mathbf{I}_c be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

Solving for $\mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07\angle 3.95^\circ \text{ A}$.

AP 9.14 [a] $M = 0.4\sqrt{0.0625} = 0.1 \text{ H}, \quad \omega M = 80 \Omega$

$$Z_{22} = 40 + j800(0.125) + 360 + j800(0.25) = (400 + j300) \Omega$$

Therefore $|Z_{22}| = 500 \Omega, \quad Z_{22}^* = (400 - j300) \Omega$

$$Z_r = \left(\frac{80}{500}\right)^2 (400 - j300) = (10.24 - j7.68) \Omega$$

[b] $\mathbf{I}_1 = \frac{245.20}{184 + 100 + j400 + Z_r} = 0.50\angle -53.13^\circ \text{ A}$

$$i_1 = 0.5 \cos(800t - 53.13^\circ) \text{ A}$$

[c] $\mathbf{I}_2 = \left(\frac{j\omega M}{Z_{22}}\right) \mathbf{I}_1 = \frac{j80}{500\angle 36.87^\circ} (0.5\angle -53.13^\circ) = 0.08\angle 0^\circ \text{ A}$

$$i_2 = 80 \cos 800t \text{ mA}$$

$$\begin{aligned}\text{AP 9.15 } \mathbf{I}_1 &= \frac{\mathbf{V}_s}{Z_1 + Z_2/a^2} = \frac{25 \times 10^3 \angle 0^\circ}{1500 + j6000 + (25)^2(4 - j14.4)} \\ &= 4 + j3 = 5 \angle 36.87^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\mathbf{V}_1 &= \mathbf{V}_s - Z_1 \mathbf{I}_1 = 25,000 \angle 0^\circ - (4 + j3)(1500 + j6000) \\ &= 37,000 - j28,500\end{aligned}$$

$$\mathbf{V}_2 = -\frac{1}{25} \mathbf{V}_1 = -1480 + j1140 = 1868.15 \angle 142.39^\circ \text{ V}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{Z_2} = \frac{1868.15 \angle 142.39^\circ}{4 - j14.4} = 125 \angle -143.13^\circ \text{ A}$$

$$\text{Also, } I_2 = -25I_1$$

Problems

P 9.1 [a] $\omega = 2\pi f = 3769.91 \text{ rad/s}$, $f = \frac{\omega}{2\pi} = 600 \text{ Hz}$

[b] $T = 1/f = 1.67 \text{ ms}$

[c] $V_m = 10 \text{ V}$

[d] $v(0) = 10 \cos(-53.13^\circ) = 6 \text{ V}$

[e] $\phi = -53.13^\circ$; $\phi = \frac{-53.13^\circ(2\pi)}{360^\circ} = -0.9273 \text{ rad}$

[f] $V = 0$ when $3769.91t - 53.13^\circ = 90^\circ$. Now resolve the units:

$$(3769.91 \text{ rad/s})t = \frac{143.13^\circ}{(180^\circ/\pi)} = 2.498 \text{ rad}, \quad t = 662.64 \mu\text{s}$$

[g] $(dv/dt) = (-10)3769.91 \sin(3769.91t - 53.13^\circ)$

$$(dv/dt) = 0 \quad \text{when} \quad 3769.91t - 53.13^\circ = 0^\circ$$

$$\text{or} \quad 3769.91t = \frac{53.13^\circ}{57.3^\circ/\text{rad}} = 0.9273 \text{ rad}$$

Therefore $t = 245.97 \mu\text{s}$

P 9.2 $V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

Therefore $V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$

P 9.3 [a] 40 V

[b] $2\pi f = 100\pi$; $f = 50 \text{ Hz}$

[c] $\omega = 100\pi = 314.159 \text{ rad/s}$

[d] $\theta(\text{rad}) = \frac{2\pi}{360^\circ}(60^\circ) = \frac{\pi}{3} = 1.05 \text{ rad}$

[e] $\theta = 60^\circ$

[f] $T = \frac{1}{f} = \frac{1}{50} = 20 \text{ ms}$

[g] $v = -40$ when


$$100\pi t + \frac{\pi}{3} = \pi; \quad \therefore t = 6.67 \text{ ms}$$

$$\begin{aligned}
 \text{[h]} \quad v &= 40 \cos \left[100\pi \left(t - \frac{0.01}{3} \right) + \frac{\pi}{3} \right] \\
 &= 40 \cos [100\pi t - (\pi/3) + (\pi/3)] \\
 &= 40 \cos 100\pi t \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[i]} \quad 100\pi(t - t_o) + (\pi/3) &= 100\pi t - (\pi/2) \\
 \therefore 100\pi t_o &= \frac{5\pi}{6}; \quad t_o = 8.33 \text{ ms}
 \end{aligned}$$

$$\begin{aligned}
 \text{[j]} \quad 100\pi(t + t_o) + (\pi/3) &= 100\pi t + 2\pi \\
 \therefore 100\pi t_o &= \frac{5\pi}{3}; \quad t_o = 16.67 \text{ ms} \\
 &16.67 \text{ ms to the left}
 \end{aligned}$$

P 9.4

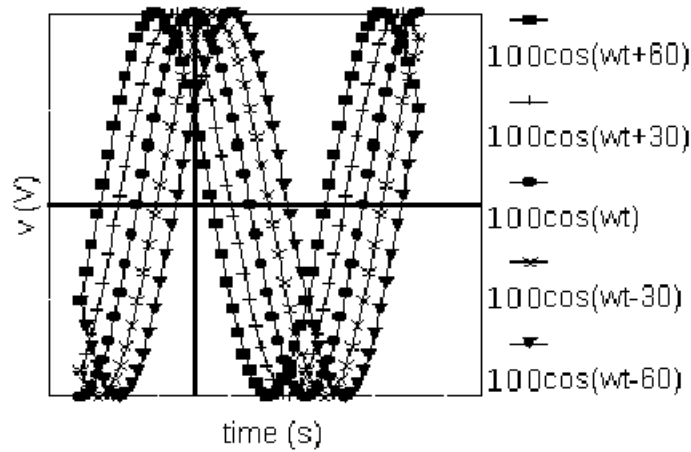[a] Left as ϕ becomes more positive

[b] Left

P 9.5 [a] By hypothesis

$$v = 80 \cos(\omega t + \theta)$$

$$\frac{dv}{dt} = -80\omega \sin(\omega t + \theta)$$

$$\therefore 80\omega = 80,000; \quad \omega = 1000 \text{ rad/s}$$

$$\text{[b]} \quad f = \frac{\omega}{2\pi} = 159.155 \text{ Hz}; \quad T = \frac{1}{f} = 6.28 \text{ ms}$$

$$\frac{-2\pi/3}{6.28} = -0.3333, \quad \therefore \theta = -90 - (-0.3333)(360) = 30^\circ$$

$$\therefore v = 80 \cos(1000t + 30^\circ) \text{ V}$$

P 9.6 [a] $\frac{T}{2} = 8 + 2 = 10 \text{ ms}; \quad T = 20 \text{ ms}$

$$f = \frac{1}{T} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz}$$

[b] $v = V_m \sin(\omega t + \theta)$

$$\omega = 2\pi f = 100\pi \text{ rad/s}$$

$$100\pi(-2 \times 10^{-3}) + \theta = 0; \quad \therefore \theta = \frac{\pi}{5} \text{ rad} = 36^\circ$$

$$v = V_m \sin[100\pi t + 36^\circ]$$

$$80.9 = V_m \sin 36^\circ; \quad V_m = 137.64 \text{ V}$$

$$v = 137.64 \sin[100\pi t + 36^\circ] = 137.64 \cos[100\pi t - 54^\circ] \text{ V}$$

P 9.7
$$\begin{aligned} u &= \int_{t_o}^{t_o+T} V_m^2 \cos^2(\omega t + \phi) dt \\ &= V_m^2 \int_{t_o}^{t_o+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt \\ &= \frac{V_m^2}{2} \left\{ \int_{t_o}^{t_o+T} dt + \int_{t_o}^{t_o+T} \cos(2\omega t + 2\phi) dt \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_o}^{t_o+T} \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_o + 4\pi + 2\phi) - \sin(2\omega t_o + 2\phi)] \right\} \\ &= V_m^2 \left(\frac{T}{2} \right) + \frac{1}{2\omega} (0) = V_m^2 \left(\frac{T}{2} \right) \end{aligned}$$

P 9.8 $V_m = \sqrt{2}V_{\text{rms}} = \sqrt{2}(120) = 169.71 \text{ V}$

P 9.9 [a] The numerical values of the terms in Eq. 9.8 are

$$V_m = 20, \quad R/L = 1066.67, \quad \omega L = 60$$

$$\sqrt{R^2 + \omega^2 L^2} = 100$$

$$\phi = 25^\circ, \quad \theta = \tan^{-1} 60/80, \quad \theta = 36.87^\circ$$

Substitute these values into Equation 9.9:

$$i = [-195.72e^{-1066.67t} + 200 \cos(800t - 11.87^\circ)] \text{ mA}, \quad t \geq 0$$

[b] Transient component $= -195.72e^{-1066.67t} \text{ mA}$

Steady-state component $= 200 \cos(800t - 11.87^\circ) \text{ mA}$

[c] By direct substitution into Eq 9.9 in part (a), $i(1.875 \text{ ms}) = 28.39 \text{ mA}$

[d] $200 \text{ mA}, \quad 800 \text{ rad/s}, \quad -11.87^\circ$

[e] The current lags the voltage by 36.87° .

P 9.10 **[a]** From Eq. 9.9 we have

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

But

$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to

$$V_m \cos(\omega t + \phi)$$

At $t = 0$, Eq. 9.9 reduces to

$$i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

$$\mathbf{[b]} \quad i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

Therefore

$$L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta)$$

and

$$Ri_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$L \frac{di_{ss}}{dt} + Ri_{ss} = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$= V_m \cos(\omega t + \phi)$$

P 9.11 **[a]** $\mathbf{Y} = 50/\underline{60^\circ} + 100/\underline{-30^\circ} = 111.8/\underline{-3.43^\circ}$

$$y = 111.8 \cos(500t - 3.43^\circ)$$

[b] $\mathbf{Y} = 200/\underline{50^\circ} - 100/\underline{60^\circ} = 102.99/\underline{40.29^\circ}$

$$y = 102.99 \cos(377t + 40.29^\circ)$$

[c] $\mathbf{Y} = 80/\underline{30^\circ} - 100/\underline{-225^\circ} + 50/\underline{-90^\circ} = 161.59/\underline{-29.96^\circ}$

$$y = 161.59 \cos(100t - 29.96^\circ)$$

$$[\mathbf{d}] \mathbf{Y} = 250/\underline{0^\circ} + 250/\underline{120^\circ} + 250/\underline{-120^\circ} = 0$$

$$y = 0$$

$$\text{P 9.12} \quad [\mathbf{a}] \quad 1000\text{Hz}$$

$$[\mathbf{b}] \quad \theta_v = 0^\circ$$

$$[\mathbf{c}] \quad \mathbf{I} = \frac{200/\underline{0^\circ}}{j\omega L} = \frac{200}{\omega L} \underline{-90^\circ} = 25 \underline{-90^\circ}; \quad \theta_i = -90^\circ$$

$$[\mathbf{d}] \quad \frac{200}{\omega L} = 25; \quad \omega L = \frac{200}{25} = 8 \Omega$$

$$[\mathbf{e}] \quad L = \frac{8}{2\pi(1000)} = 1.27 \text{ mH}$$

$$[\mathbf{f}] \quad Z_L = j\omega L = j8 \Omega$$

$$\text{P 9.13} \quad [\mathbf{a}] \quad \omega = 2\pi f = 314,159.27 \text{ rad/s}$$

$$[\mathbf{b}] \quad \mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{10 \times 10^{-3} \underline{0^\circ}}{1/j\omega C} = j\omega C(10 \times 10^{-3}) \underline{0^\circ} = 10 \times 10^{-3} \omega C \underline{90^\circ}$$

$$\therefore \theta_i = 90^\circ$$

$$[\mathbf{c}] \quad 628.32 \times 10^{-6} = 10 \times 10^{-3} \omega C$$

$$\frac{1}{\omega C} = \frac{10 \times 10^{-3}}{628.32 \times 10^{-6}} = 15.92 \Omega, \quad \therefore X_C = -15.92 \Omega$$


$$[\mathbf{d}] \quad C = \frac{1}{15.92(\omega)} = \frac{1}{(15.92)(100\pi \times 10^3)}$$

$$C = 0.2 \mu\text{F}$$

$$[\mathbf{e}] \quad Z_c = j \left(\frac{-1}{\omega C} \right) = -j15.92 \Omega$$

$$\text{P 9.14} \quad [\mathbf{a}] \quad j\omega L = j(2 \times 10^4)(300 \times 10^{-6}) = j6 \Omega$$
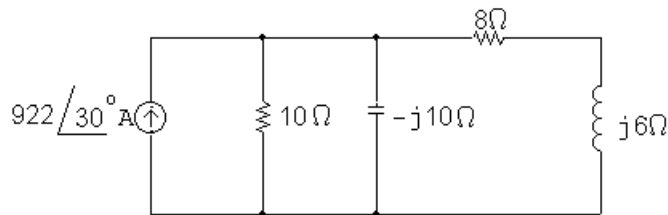
$$\frac{1}{j\omega C} = -j \frac{1}{(2 \times 10^4)(5 \times 10^{-6})} = -j10 \Omega; \quad \mathbf{I}_g = 922 \underline{30^\circ} \text{ A}$$



[b] $\mathbf{V}_o = 922\angle 30^\circ Z_e$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{10} + j\frac{1}{10} + \frac{1}{8 + j6}$$

$$Y_e = 0.18 + j0.04 \text{ S}$$


$$Z_e = \frac{1}{0.18 + j0.04} = 5.42\angle -12.53^\circ \Omega$$

$$\mathbf{V}_o = (922\angle 30^\circ)(5.42\angle -12.53^\circ) = 5000.25\angle 17.47^\circ \text{ V}$$

[c] $v_o = 5000.25 \cos(2 \times 10^4 t + 17.47^\circ) \text{ V}$

P 9.15 **[a]** $Z_L = j(8000)(5 \times 10^{-3}) = j40 \Omega$
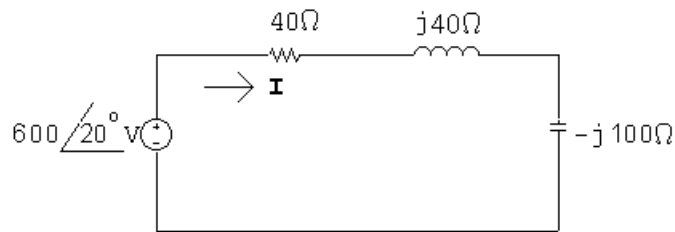
$$Z_C = \frac{-j}{(8000)(1.25 \times 10^{-6})} = -j100 \Omega$$



[b] $\mathbf{I} = \frac{600\angle 20^\circ}{40 + j40 - j100} = 8.32\angle 76.31^\circ \text{ A}$

[c] $i = 8.32 \cos(8000t + 76.31^\circ) \text{ A}$

P 9.16 $Z = 4 + j(50)(0.24) - j\frac{1}{(50)(0.0025)} = 4 + j4 = 5.66\angle 45^\circ \Omega$

$$\mathbf{I}_o = \frac{\mathbf{V}}{Z} = \frac{0.1\angle -90^\circ}{5.66\angle 45^\circ} = 17.68\angle -135^\circ \text{ mA}$$

$$i_o(t) = 17.68 \cos(50t - 135^\circ) \text{ mA}$$

P 9.17 **[a]** $Y = \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4}$

$$= 0.12 - j0.16 + 0.04 + j0.03 + j0.25$$

$$= 0.16 + j0.12 = 200\angle 36.87^\circ \text{ mS}$$

[b] $G = 160 \text{ mS}$

[c] $B = 120 \text{ mS}$

$$[\mathbf{d}] \quad \mathbf{I} = 8\angle 0^\circ \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{8}{0.2\angle 36.87^\circ} = 40\angle -36.87^\circ \text{ V}$$


$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{40\angle -36.87^\circ}{4\angle -90^\circ} = 10\angle 53.13^\circ \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

P 9.18 $Z_L = j(2000)(60 \times 10^{-3}) = j120 \Omega$

$$Z_C = \frac{-j}{(2000)(12.5 \times 10^{-6})} = -j40 \Omega$$

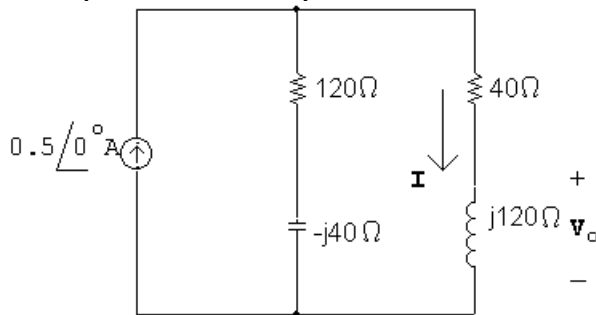Construct the phasor domain equivalent circuit:



Using current division:

$$\mathbf{I} = \frac{(120 - j40)}{120 - j40 + 40 + j120}(0.5) = 0.25 - j0.25 \text{ A}$$

$$\mathbf{V}_o = j120\mathbf{I} = 30 + j30 = 42.43\angle 45^\circ \text{ V}$$

$$v_o = 42.43 \cos(2000t + 45^\circ) \text{ V}$$

P 9.19 [a] $\mathbf{V}_g = 300\angle 78^\circ$; $\mathbf{I}_g = 6\angle 33^\circ$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = \frac{300\angle 78^\circ}{6\angle 33^\circ} = 50\angle 45^\circ \Omega$$

[b] i_g lags v_g by 45° :


$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ}(400 \mu\text{s}) = 50 \mu\text{s}$$

$$\text{P 9.20} \quad \frac{1}{j\omega C} = \frac{1}{(1 \times 10^{-6})(50 \times 10^3)} = -j20 \Omega$$

$$j\omega L = j50 \times 10^3(1.2 \times 10^{-3}) = j60 \Omega$$
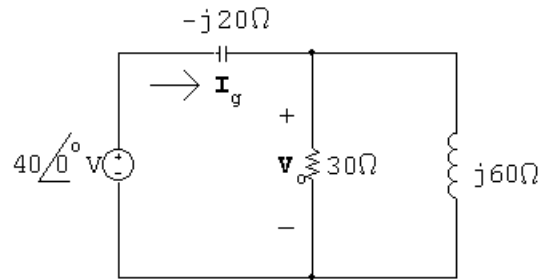
$$\mathbf{V}_g = 40\angle 0^\circ \text{ V}$$



$$Z_e = -j20 + 30\|j60 = 24 - j8 \Omega$$

$$\mathbf{I}_g = \frac{40\angle 0^\circ}{24 - j8} = 1.5 + j0.5 \text{ mA}$$

$$\mathbf{V}_o = (30\|j60)\mathbf{I}_g = \frac{30(j60)}{30 + j60}(1.5 + j0.5) = 30 + j30 = 42.43\angle 45^\circ \text{ V}$$

$$v_o = 42.43 \cos(50,000t + 45^\circ) \text{ V}$$

$$\text{P 9.21} \quad [\mathbf{a}] \quad Z_1 = R_1 - j\frac{1}{\omega C_1}$$

$$Z_2 = \frac{R_2/j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and}$$

$$\frac{1}{\omega C_1} = \frac{\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}$$

$$[\mathbf{b}] \quad R_1 = \frac{1000}{1 + (40 \times 10^3)^2(1000)^2(50 \times 10^{-9})^2} = 200 \Omega$$

$$C_1 = \frac{1 + (40 \times 10^3)^2(1000)^2(50 \times 10^{-9})^2}{(40 \times 10^3)^2(1000)^2(50 \times 10^{-9})} = 62.5 \text{ nF}$$

P 9.22 [a] $Y_2 = \frac{1}{R_2} + j\omega C_2$

$$Y_1 = \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2}$$

Therefore $Y_1 = Y_2$ when

$$R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2}$$

[b] $R_2 = \frac{1 + (50 \times 10^3)^2 (1000)^2 (40 \times 10^{-9})^2}{(50 \times 10^3)^2 (1000)^2 (40 \times 10^{-9})^2} = 1250 \, \Omega$

$$C_2 = \frac{40 \times 10^{-9}}{1 + (50 \times 10^3)^2 (1000)^2 (40 \times 10^{-9})^2} = 8 \, \text{nF}$$

P 9.23 [a] $Z_1 = R_1 + j\omega L_1$

$$Z_2 = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

[b] $R_1 = \frac{(4000)^2 (1.25)^2 (5000)}{5000^2 + 4000^2 (1.25)^2} = 2500 \, \Omega$

$$L_1 = \frac{(5000)^2 (1.25)}{5000^2 + 4000^2 (1.25)^2} = 625 \, \text{mH}$$

P 9.24 [a] $Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

Therefore $Y_2 = Y_1$ when

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$

[b] $R_2 = \frac{8000^2 + 1000^2 (4)^2}{8000} = 10 \, \text{k}\Omega$

$$L_2 = \frac{8000^2 + 1000^2 (4)^2}{1000^2 (4)} = 20 \, \text{H}$$

P 9.25 $\mathbf{V}_g = 500\angle 30^\circ \text{ V}; \quad \mathbf{I}_g = 0.1\angle 83.13^\circ \text{ mA}$

$$Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 5000\angle -53.13^\circ \Omega = 3000 - j4000 \Omega$$

$$z = 3000 + j\left(\omega - \frac{32 \times 10^3}{\omega}\right)$$

$$\omega - \frac{32 \times 10^3}{\omega} = -4000$$

$$\omega^2 + 4000\omega - 32 \times 10^3 = 0$$

$$\omega = 7.984 \text{ rad/s}$$

P 9.26 [a] $Z_{\text{eq}} = \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \parallel (1200 + j0.2\omega)$

$$= \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \frac{(1200 + j0.2\omega)}{1200 + j[0.2\omega - \frac{20 \times 10^6}{\omega}]}$$

$$= \frac{50,000}{3} + \frac{\frac{-j20 \times 10^6}{\omega}(1200 + j0.2\omega) \left[1200 - j\left(0.2\omega - \frac{20 \times 10^6}{\omega}\right)\right]}{1200^2 + \left(0.2\omega - \frac{20 \times 10^6}{\omega}\right)^2}$$

$$\text{Im}(Z_{\text{eq}}) = -\frac{20 \times 10^6}{\omega}(1200)^2 - \frac{20 \times 10^6}{\omega} \left[0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega}\right)\right] = 0$$

$$-20 \times 10^6(1200)^2 - 20 \times 10^6 \left[0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega}\right)\right] = 0$$

$$-(1200)^2 = 0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega}\right)$$

$$0.2^2\omega^2 - 0.2(20 \times 10^6) + 1200^2 = 0$$

$$\omega^2 = 64 \times 10^6 \quad \therefore \quad \omega = 8000 \text{ rad/s}$$

$$\therefore \quad f = 1273.24 \text{ Hz}$$

[b] $Z_{\text{eq}} = \frac{50,000}{3} + -j2500 \parallel (1200 + j1600)$

$$= \frac{50,000}{3} + \frac{(-j2500)(1200 + j1600)}{1200 - j900} = 20,000 \Omega$$

$$\mathbf{I}_g = \frac{30\angle 0^\circ}{20,000} = 1.5\angle 0^\circ \text{ mA}$$

$$i_g(t) = 1.5 \cos 8000t \text{ mA}$$

- P 9.27 [a] Find the equivalent impedance seen by the source, as a function of L , and set the imaginary part of the equivalent impedance to 0, solving for L :

$$Z_C = \frac{-j}{(500)(2 \times 10^{-6})} = -j1000 \Omega$$

$$\begin{aligned} Z_{eq} &= -j1000 + j500L \parallel 2000 = -j1000 + \frac{2000(j500L)}{2000 + j500L} \\ &= -j1000 + \frac{2000(j500L)(2000 - j500L)}{2000^2 + (500L)^2} \end{aligned}$$

$$\text{Im}(Z_{eq}) = -1000 + \frac{2000^2(500L)}{2000^2 + (500L)^2} = 0$$

$$\therefore \frac{2000^2(500L)}{2000^2 + (500L)^2} = 1000$$

$$\therefore 500^2 L^2 - \frac{1}{2} 2000^2 L + 2000^2 = 0$$

Solving the quadratic equation, $L = 4 \text{ H}$

$$[\text{b}] \mathbf{I}_g = \frac{100 \angle 0^\circ}{-j1000 + j2000 \parallel 2000} = \frac{100 \angle 0^\circ}{1000} = 0.1 \angle 0^\circ \text{ A}$$

$$i_g(t) = 0.1 \cos 500t \text{ A}$$

- P 9.28 [a] $j\omega L + R \parallel (-j/\omega C) = j\omega L + \frac{-jR/\omega C}{R - j/\omega C}$

$$= j\omega L + \frac{-jR}{\omega C R - j1}$$

$$= j\omega L + \frac{-jR(\omega C R + j1)}{\omega^2 C^2 R^2 + 1}$$

$$\text{Im}(Z_{ab}) = \omega L - \frac{\omega C R^2}{\omega^2 C^2 R^2 + 1} = 0$$

$$\therefore L = \frac{C R^2}{\omega^2 C^2 R^2 + 1}$$

$$\therefore \omega^2 C^2 R^2 + 1 = \frac{C R^2}{L}$$


$$\therefore \omega^2 = \frac{(C R^2 / L) - 1}{C^2 R^2} = \frac{\frac{(25 \times 10^{-9})(100)^2}{160 \times 10^{-6}} - 1}{(25 \times 10^{-9})^2 (100)^2} = 900 \times 10^8$$

$$\omega = 300 \text{ krad/s}$$

$$\text{[b]} \quad Z_{ab}(300 \times 10^3) = j48 + \frac{(100)(-j133.33)}{100 - j133.33} = 64 \Omega$$

$$\text{P 9.29} \quad j\omega L = j100 \times 10^3(0.6 \times 10^{-3}) = j60 \Omega$$
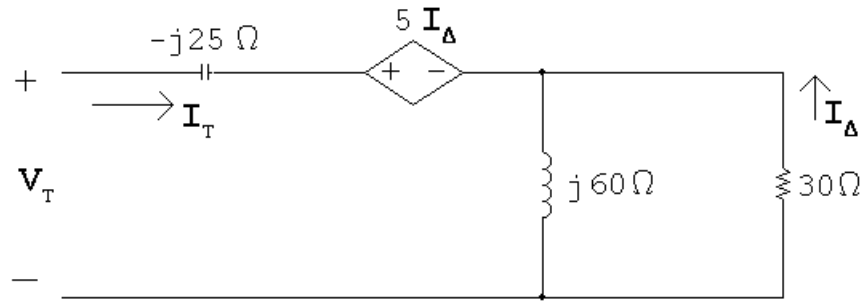
$$\frac{1}{j\omega C} = \frac{-j}{(100 \times 10^3)(0.4 \times 10^{-6})} = -j25 \Omega$$



$$\mathbf{V}_T = -j25\mathbf{I}_T + 5\mathbf{I}_\Delta - 30\mathbf{I}_\Delta$$

$$\mathbf{I}_\Delta = \frac{-j60}{30 + j60}\mathbf{I}_T$$

$$\mathbf{V}_T = -j25\mathbf{I}_T + 25\frac{j60}{30 + j60}\mathbf{I}_T$$

$$\frac{\mathbf{V}_T}{\mathbf{I}_T} = Z_{ab} = 20 - j15 = 25\angle -36.87^\circ \Omega$$

$$\text{P 9.30} \quad \text{[a]} \quad Z_1 = 400 - j\frac{10^6}{500(2.5)} = 400 - j800 \Omega$$

$$Z_2 = 2000 \parallel j500L = \frac{j10^6 L}{2000 + j500L}$$

$$Z_T = Z_1 + Z_2 = 400 - j800 + \frac{j10^6 L}{2000 + j500L}$$

$$= 400 + \frac{500 \times 10^6 L^2}{2000^2 + 500^2 L^2} - j800 + j\frac{2 \times 10^9 L}{2000^2 + 500^2 L^2}$$

Z_T is resistive when

$$\frac{2 \times 10^9 L}{2000^2 + 500^2 L^2} = 800 \quad \text{or} \quad 500^2 L^2 - 25 \times 10^5 L + 2000^2 = 0$$

Solving, $L_1 = 8 \text{ H}$ and $L_2 = 2 \text{ H}$.

[b] When $L = 8 \text{ H}$:

$$Z_T = 400 + \frac{500 \times 10^6 (8)^2}{2000^2 + 500^2 (8)^2} = 2000 \Omega$$

$$\mathbf{I}_g = \frac{200 \angle 0^\circ}{2000} = 100 \angle 0^\circ \text{ mA}$$

$$i_g = 100 \cos 500t \text{ mA}$$

When $L = 2 \text{ H}$:

$$Z_T = 400 + \frac{500 \times 10^6 (2)^2}{2000^2 + 500^2 (2)^2} = 800 \Omega$$

$$\mathbf{I}_g = \frac{200 \angle 0^\circ}{800} = 250 \angle 0^\circ \text{ mA}$$

$$i_g = 250 \cos 500t \text{ mA}$$

P 9.31 **[a]** $Y_1 = \frac{11}{2500 \times 10^3} = 4.4 \times 10^{-6} \text{ S}$

$$\begin{aligned} Y_2 &= \frac{1}{14,000 + j5\omega} \\ &= \frac{14,000}{196 \times 10^6 + 25\omega^2} - j \frac{5\omega}{196 \times 10^6 + 25\omega^2} \end{aligned}$$

$$Y_3 = j\omega 2 \times 10^{-9}$$

$$Y_T = Y_1 + Y_2 + Y_3$$

For i_g and v_o to be in phase the j component of Y_T must be zero; thus,

$$\omega 2 \times 10^{-9} = \frac{5\omega}{196 \times 10^6 + 25\omega^2}$$

or

$$25\omega^2 + 196 \times 10^6 = \frac{5}{2 \times 10^{-9}}$$

$$\therefore 25\omega^2 = 2304 \times 10^6 \quad \therefore \omega = 9600 \text{ rad/s}$$

[b] $Y_T = 4.4 \times 10^{-6} + \frac{14,000}{196 \times 10^6 + 25(9600)^2} = 10 \times 10^{-6} \text{ S}$

$$\therefore Z_T = 100 \text{ k}\Omega$$

$$\mathbf{V}_o = (0.25 \times 10^{-3} \angle 0^\circ)(100 \times 10^3) = 25 \angle 0^\circ \text{ V}$$

$$v_o = 25 \cos 9600t \text{ V}$$

P 9.32 [a] $Z_g = 500 - j\frac{10^6}{\omega} + \frac{10^3(j0.5\omega)}{10^3 + j0.5\omega}$

$$= 500 - j\frac{10^6}{\omega} + \frac{500j\omega(1000 - j0.5\omega)}{10^6 + 0.25\omega^2}$$

$$= 500 - j\frac{10^6}{\omega} + \frac{250\omega^2}{10^6 + 0.25\omega^2} + j\frac{5 \times 10^5\omega}{10^6 + 0.25\omega^2}$$

\therefore If Z_g is purely real, $\frac{10^6}{\omega} = \frac{5 \times 10^5\omega}{10^6 + 0.25\omega^2}$

$$2(10^6 + 0.25\omega^2) = \omega^2 \quad \therefore \quad 4 \times 10^6 = \omega^2$$

$\therefore \quad \omega = 2000 \text{ rad/s}$

[b] When $\omega = 2000 \text{ rad/s}$

$$Z_g = 500 - j500 + (j1000 \parallel 1000) = 1000 \Omega$$

$$\therefore \mathbf{I}_g = \frac{20\angle 0^\circ}{1000} = 20\angle 0^\circ \text{ mA}$$

$$\mathbf{V}_o = \mathbf{V}_g - \mathbf{I}_g Z_1$$

$$Z_1 = 500 - j500 \Omega$$

$$\mathbf{V}_o = 20\angle 0^\circ - (0.02\angle 0^\circ)(500 - j500) = 10 + j10 = 14.14\angle 45^\circ \text{ V}$$

$$v_o = 14.14 \cos(2000t + 45^\circ) \text{ V}$$

P 9.33 $Z_{ab} = 1 - j8 + (2 + j4) \parallel (10 - j20) + (40 \parallel j20)$

$$= 1 - j8 + 3 + j4 + 8 + j16 = 12 + j12 \Omega = 16.971\angle 45^\circ \Omega$$

P 9.34 First find the admittance of the parallel branches

$$Y_p = \frac{1}{2 - j6} + \frac{1}{12 + j4} + \frac{1}{2} + \frac{1}{j0.5} = 0.625 - j1.875 \text{ S}$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.625 - j1.875} = 0.16 + j0.48 \Omega$$

$$Z_{ab} = -j4.48 + 0.16 + j0.48 + 2.84 = 3 - j4 \Omega$$


$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{3 - j4} = 120 + j160 \text{ mS}$$

$$= 200\angle 53.13^\circ \text{ mS}$$

P 9.35 Simplify the top triangle using series and parallel combinations:

$$(1 + j1) \parallel (1 - j1) = 1 \Omega$$

Convert the lower left delta to a wye:

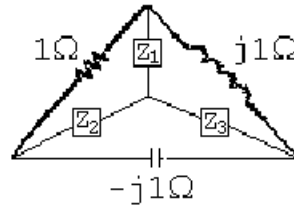


$$Z_1 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

$$Z_2 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_3 = \frac{(j1)(-j1)}{1 + j1 - j1} = 1 \Omega$$

Convert the lower right delta to a wye:

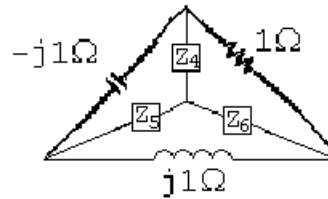


$$Z_4 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_5 = \frac{(-j1)(j1)}{1 + j1 - j1} = 1 \Omega$$

$$Z_6 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

The resulting circuit is shown below:

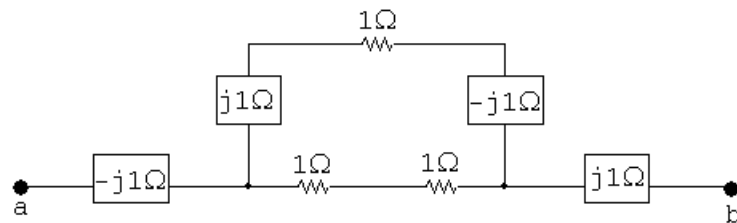

Simplify the middle portion of the circuit by making series and parallel combinations:

$$(1 + j1 - j1) \parallel (1 + 1) = 1 \parallel 2 = 2/3 \Omega$$

$$Z_{ab} = -j1 + 2/3 + j1 = 2/3 \Omega$$

$$\text{P 9.36} \quad \mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{500 - j1000}{300 + j1600 + 500 - j1000} (100 \angle 0^\circ) = 111.8 \angle -100.3^\circ \text{ V}$$

$$v_o = 111.8 \cos(8000t - 100.3^\circ) \text{ V}$$

$$\text{P 9.37} \quad \frac{1}{j\omega C} = -j400 \Omega$$

$$j\omega L = j1200 \Omega$$

$$\text{Let } Z_1 = 200 - j400 \Omega; \quad Z_2 = 600 + j1200 \Omega$$


$$\mathbf{I}_g = 400 \angle 0^\circ \text{ mA}$$

$$\mathbf{I}_o = \frac{Z_2}{Z_1 + Z_2} \mathbf{I}_g = \frac{600 + j1200}{800 + j800} (0.4 \angle 0^\circ)$$

$$= 450 + j150 \text{ mA} = 474.34 \angle 18.43^\circ \text{ mA}$$

$$i_o = 474.34 \cos(20,000t + 18.43^\circ) \text{ mA}$$

P 9.38

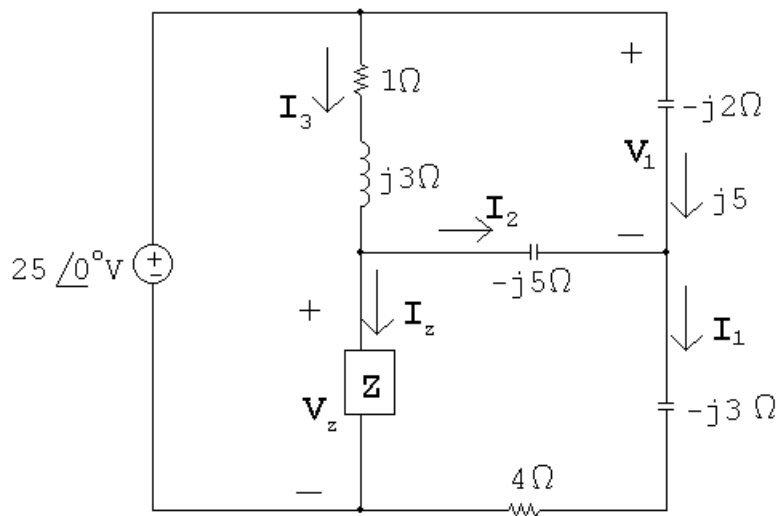

$$\mathbf{V}_1 = j5(-j2) = 10 \text{ V}$$

$$-25 + 10 + (4 - j3)\mathbf{I}_1 = 0 \quad \therefore \quad \mathbf{I}_1 = \frac{15}{4 - j3} = 2.4 + j1.8 \text{ A}$$

$$\mathbf{I}_2 = \mathbf{I}_1 - j5 = (2.4 + j1.8) - j5 = 2.4 - j3.2 \text{ A}$$

$$\mathbf{V}_Z = -j5\mathbf{I}_2 + (4 - j3)\mathbf{I}_1 = -j5(2.4 - j3.2) + (4 - j3)(2.4 + j1.8) = -1 - j12 \text{ V}$$

$$-25 + (1 + j3)\mathbf{I}_3 + (-1 - j12) = 0 \quad \therefore \quad \mathbf{I}_3 = 6.2 - j6.6 \text{ A}$$

$$\mathbf{I}_Z = \mathbf{I}_3 - \mathbf{I}_2 = (6.2 - j6.6) - (2.4 - j3.2) = 3.8 - j3.4 \text{ A}$$


$$Z = \frac{\mathbf{V}_Z}{\mathbf{I}_Z} = \frac{-1 - j12}{3.8 - j3.4} = 1.42 - j1.88 \Omega$$

P 9.39 $\mathbf{I}_s = 3\angle 0^\circ \text{ mA}$

$$\frac{1}{j\omega C} = -j0.4 \Omega$$

$$j\omega L = j0.4 \Omega$$


After source transformation we have

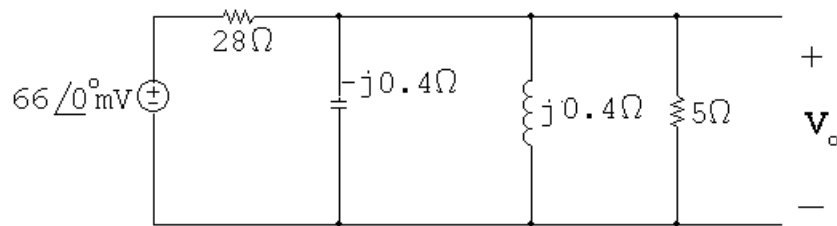

$$\mathbf{V}_o = \frac{-j0.4 \parallel j0.4 \parallel 5}{28 + -j0.4 \parallel j0.4 \parallel 5} (66 \times 10^{-3}) = 10 \text{ mV}$$

$$v_o = 10 \cos 200t \text{ mV}$$

P 9.40 [a]

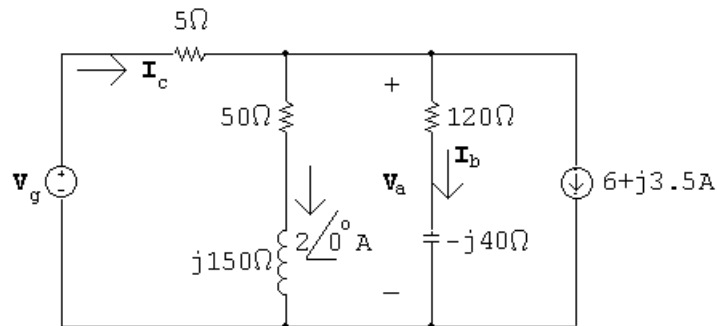

$$\mathbf{V}_a = (50 + j150)(2\angle 0^\circ) = 100 + j300 \text{ V}$$

$$\mathbf{I}_b = \frac{100 + j300}{120 - j40} = j2.5 \text{ A} = 2.5\angle 90^\circ \text{ A}$$

$$\mathbf{I}_c = 2\angle 0^\circ + j2.5 + 6 + j3.5 = 8 + j6 \text{ A} = 10\angle 36.87^\circ \text{ A}$$

$$\mathbf{V}_g = 5\mathbf{I}_c + \mathbf{V}_a = 5(8 + j6) + 100 + j300 = 140 + j330 \text{ V} = 358.47\angle 67.01^\circ \text{ V}$$


[b] $i_b = 2.5 \cos(800t + 90^\circ) \text{ A}$

$$i_c = 10 \cos(800t + 36.87^\circ) \text{ A}$$

$$v_g = 358.47 \cos(800t + 67.01^\circ) \text{ V}$$

P 9.41 [a] $j\omega L = j(1000)(100) \times 10^{-3} = j100 \Omega$
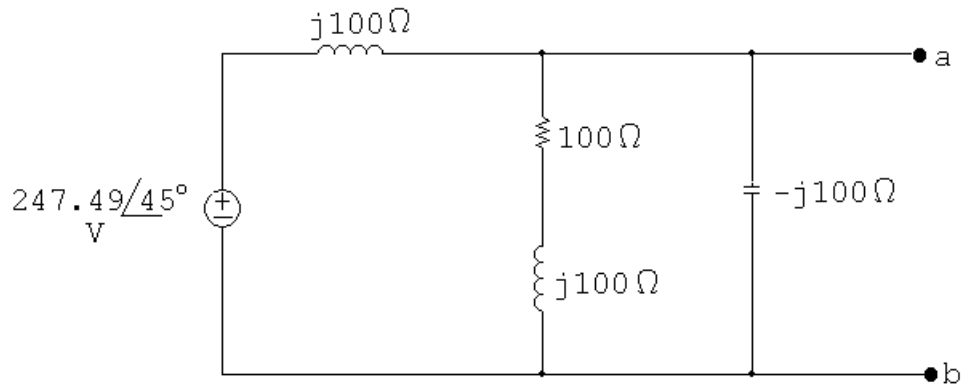
$$\frac{1}{j\omega C} = -j \frac{10^6}{(1000)(10)} = -j100 \Omega$$



Using voltage division,

$$\mathbf{V}_{ab} = \frac{(100 + j100) \parallel (-j100)}{j100 + (100 + j100) \parallel (-j100)} (247.49 \angle 45^\circ) = 350 \angle 0^\circ$$

$$\mathbf{V}_{Th} = \mathbf{V}_{ab} = 350 \angle 0^\circ \text{ V}$$


[b] Remove the voltage source and combine impedances in parallel to find

$$Z_{Th} = Z_{ab}:$$

$$Y_{ab} = \frac{1}{j100} + \frac{1}{100 + j100} + \frac{1}{-j100} = 5 - j5 \text{ mS}$$

$$Z_{Th} = Z_{ab} = \frac{1}{Y_{ab}} = 100 + j100 \Omega$$

[c]

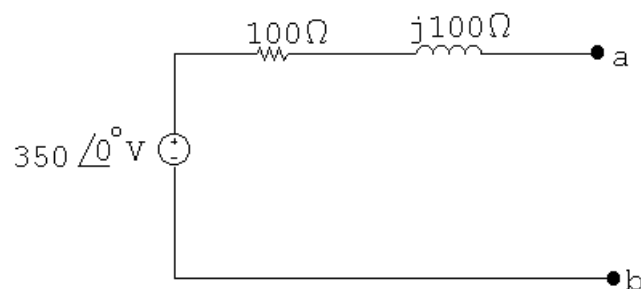


P 9.42 Using voltage division:

$$\mathbf{V}_{\text{Th}} = \frac{36}{36 + j60 - j48}(240) = 216 - j72 = 227.68 \angle -18.43^\circ \text{ V}$$

Remove the source and combine impedances in series and in parallel:

$$\mathbf{Z}_{\text{Th}} = 36 \parallel (j60 - j48) = 3.6 + j10.8 \Omega$$

P 9.43 Open circuit voltage:

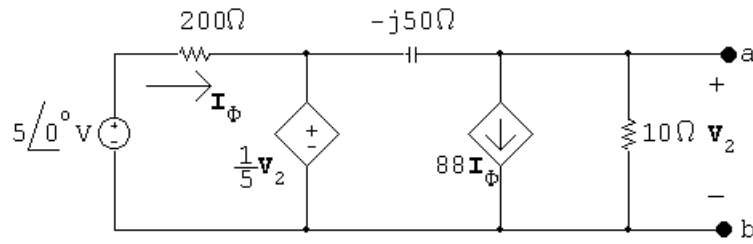


$$\frac{\mathbf{V}_2}{10} + 88\mathbf{I}_\phi + \frac{\mathbf{V}_2 - \frac{1}{5}\mathbf{V}_2}{-j50} = 0$$

$$\mathbf{I}_\phi = \frac{5 - (\mathbf{V}_2/5)}{200}$$

Solving,

$$\mathbf{V}_2 = -66 + j88 = 110 \angle 126.87^\circ \text{ V} = \mathbf{V}_{\text{Th}}$$

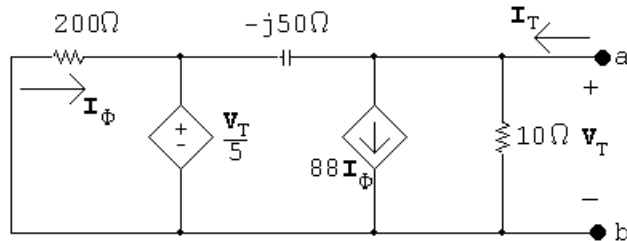Find the Thévenin equivalent impedance using a test source:



$$\mathbf{I}_T = \frac{\mathbf{V}_T}{10} + 88\mathbf{I}_\phi + \frac{0.8\mathbf{V}_t}{-j50}$$


$$\mathbf{I}_\phi = \frac{-\mathbf{V}_T/5}{200}$$

$$\mathbf{I}_T = \mathbf{V}_T \left(\frac{1}{10} - 88 \frac{1/5}{200} + \frac{0.8}{-j50} \right)$$


$$\therefore \frac{\mathbf{V}_T}{\mathbf{I}_T} = 30 - j40 = Z_{Th}$$

$$\mathbf{I}_N = \frac{\mathbf{V}_{Th}}{Z_{Th}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A} = 2.2 \angle 180^\circ \text{ A}$$

The Norton equivalent circuit:

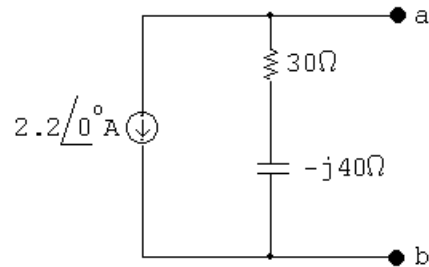

P 9.44 Short circuit current

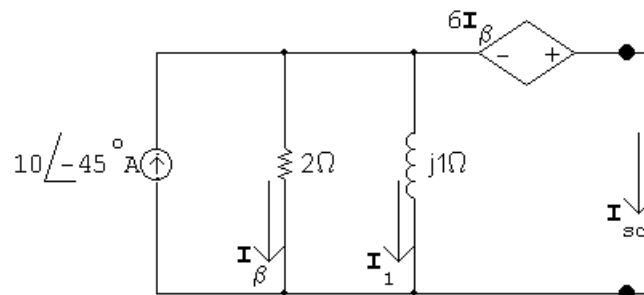


$$\mathbf{I}_\beta = \frac{-6\mathbf{I}_\beta}{2}$$

$$2\mathbf{I}_\beta = -6\mathbf{I}_\beta; \quad \therefore \mathbf{I}_\beta = 0$$

$$\mathbf{I}_1 = 0; \quad \therefore \mathbf{I}_{sc} = 10 \angle -45^\circ \text{ A} = \mathbf{I}_N$$

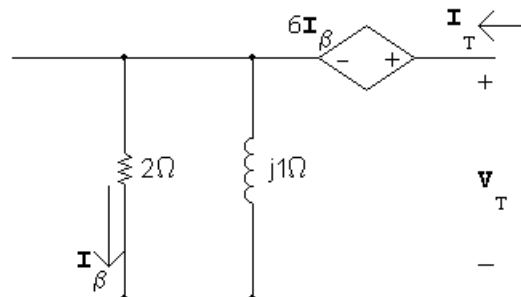The Norton impedance is the same as the Thévenin impedance. Find it using a test source



$$\mathbf{V}_T = 6\mathbf{I}_\beta + 2\mathbf{I}_\beta = 8\mathbf{I}_\beta, \quad \mathbf{I}_\beta = \frac{j1}{2 + j1} \mathbf{I}_T$$


$$Z_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = \frac{8\mathbf{I}_\beta}{[(2+j1)/j1]\mathbf{I}_\beta} = \frac{j8}{2+j1} = 1.6 + j3.2\Omega$$

P 9.45 Using current division:

$$\mathbf{I}_N = \mathbf{I}_{sc} = \frac{50}{80 + j60}(4) = 1.6 - j1.2 = 2/\underline{-36.87^\circ} \text{ A}$$


$$Z_N = -j100 \parallel (80 + j60) = 100 - j50\Omega$$

The Norton equivalent circuit:

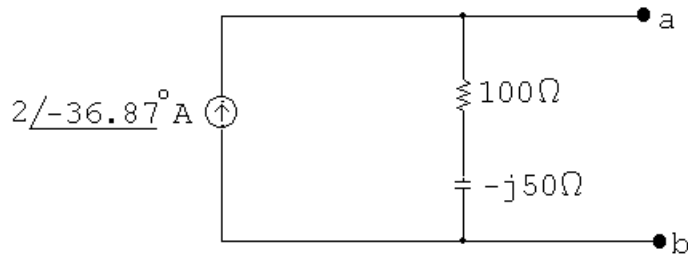

P 9.46 $\omega = 2\pi(200/\pi) = 400 \text{ rad/s}$

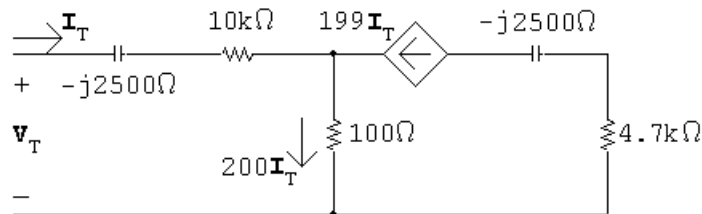
$$Z_c = \frac{-j}{400(10^{-6})} = -j2500\Omega$$




$$\mathbf{V}_T = (10,000 - j2500)\mathbf{I}_T + 100(200)\mathbf{I}_T$$

$$Z_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = 30 - j2.5\text{ k}\Omega$$

P 9.47

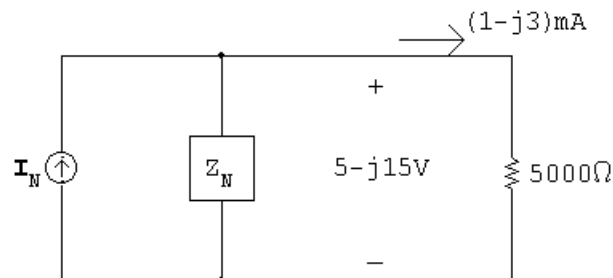
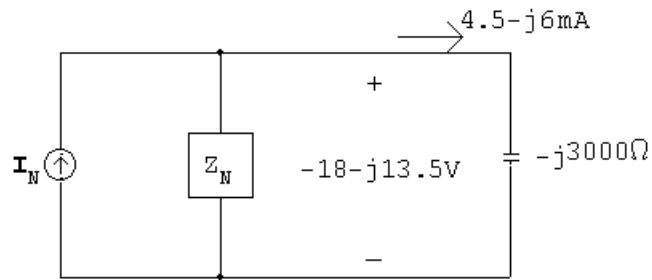
$$\mathbf{I}_N = \frac{5 - j15}{Z_N} + (1 - j3) \text{ mA}, \quad Z_N \text{ in k}\Omega$$




$$\mathbf{I}_N = \frac{-18 - j13.5}{Z_N} + 4.5 - j6 \text{ mA}, \quad Z_N \text{ in } \text{k}\Omega$$


$$\frac{5 - j15}{Z_N} + 1 - j3 = \frac{-18 - j13.5}{Z_N} + (4.5 - j6)$$

$$\frac{23 - j1.5}{Z_N} = 3.5 - j3 \quad \therefore \quad Z_N = 4 + j3 \text{ k}\Omega$$
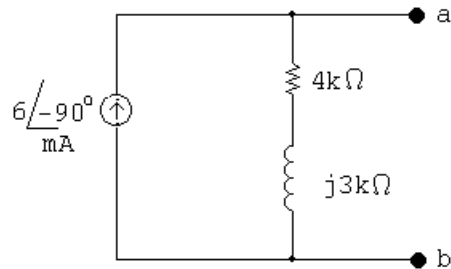
$$\mathbf{I}_N = \frac{5 - j15}{4 + j3} + 1 - j3 = -j6 \text{ mA} = 6 \angle -90^\circ \text{ mA}$$



P 9.48 Open circuit voltage:

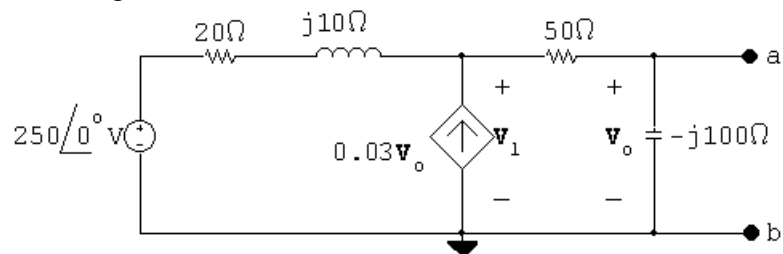


$$\frac{\mathbf{V}_1 - 250}{20 + j10} - 0.03\mathbf{V}_o + \frac{\mathbf{V}_1}{50 - j100} = 0$$

$$\therefore \mathbf{V}_o = \frac{-j100}{50 - j100} \mathbf{V}_1$$

$$\frac{\mathbf{V}_1}{20 + j10} + \frac{j3\mathbf{V}_1}{50 - j100} + \frac{\mathbf{V}_1}{50 - j100} = \frac{250}{20 + j10}$$

$$\mathbf{V}_1 = 500 - j250 \text{ V}; \quad \mathbf{V}_o = 300 - j400 \text{ V} = \mathbf{V}_{\text{Th}} = 500 \angle -53.13^\circ \text{ V}$$


Short circuit current:

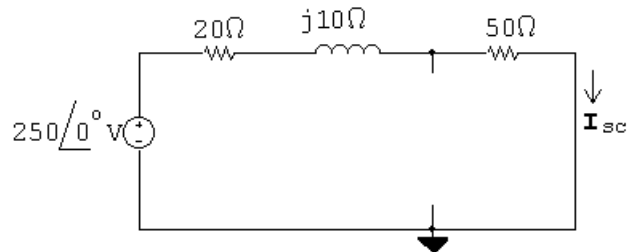


$$\mathbf{I}_{\text{sc}} = \frac{250 \angle 0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

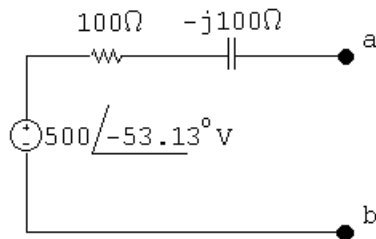

P 9.49 Open circuit voltage:

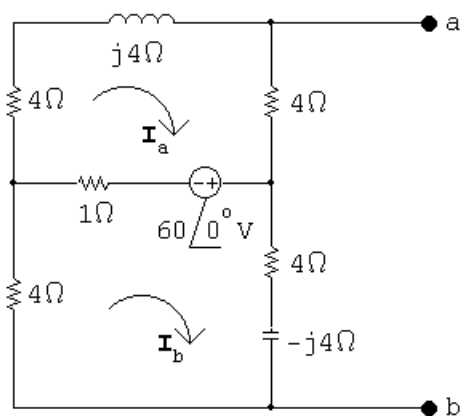

$$(9 + j4)\mathbf{I}_a - \mathbf{I}_b = -60 \angle 0^\circ$$


$$-\mathbf{I}_a + (9 - j4)\mathbf{I}_b = 60\angle 0^\circ$$

Solving,

$$\mathbf{I}_a = -5 + j2.5 \text{ A}; \quad \mathbf{I}_b = 5 + j2.5 \text{ A}$$

$$\mathbf{V}_{\text{Th}} = 4\mathbf{I}_a + (4 - j4)\mathbf{I}_b = 10\angle 0^\circ \text{ V}$$

Short circuit current:

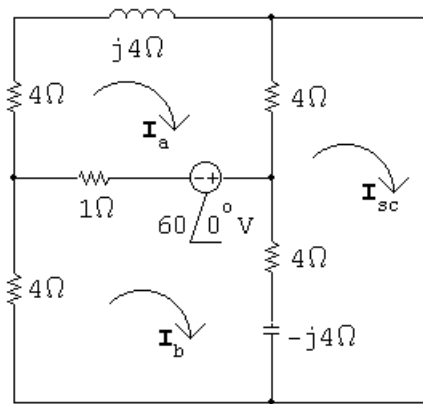

$$(9 + j4)\mathbf{I}_a - 1\mathbf{I}_b - 4\mathbf{I}_{\text{sc}} = -60$$

$$-1\mathbf{I}_a + (9 - j4)\mathbf{I}_b - (4 - j4)\mathbf{I}_{\text{sc}} = 60$$


$$-4\mathbf{I}_a - (4 - j4)\mathbf{I}_b + (8 - j4)\mathbf{I}_{\text{sc}} = 0$$

Solving,

$$\mathbf{I}_{\text{sc}} = 2.07\angle 0^\circ$$

$$Z_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{10\angle 0^\circ}{2.07\angle 0^\circ} = 4.83 \Omega$$

Alternate calculation for Z_{Th} :

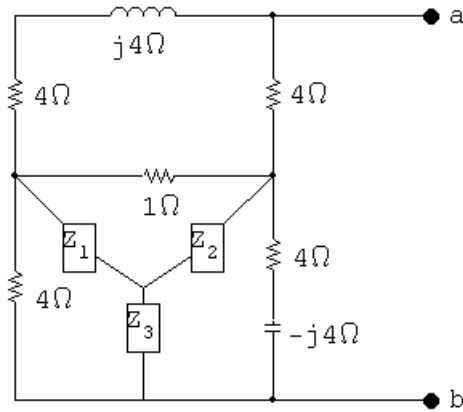


$$\sum Z = 4 + 1 + 4 - j4 = 9 - j4$$

$$Z_1 = \frac{4}{9 - j4}$$

$$Z_2 = \frac{4 - j4}{9 - j4}$$

$$Z_3 = \frac{16 - j16}{9 - j4}$$

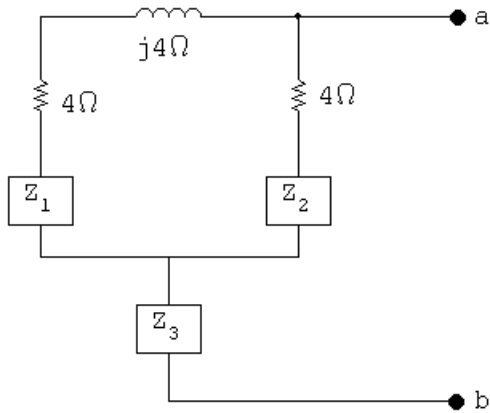


$$Z_a = 4 + j4 + \frac{4}{9 - j4} = \frac{56 + j20}{9 - j4}$$

$$Z_b = 4 + \frac{4 - j4}{9 - j4} = \frac{40 - j20}{9 - j4}$$

$$Z_a \parallel Z_b = \frac{2640 - j320}{864 - j384}$$

$$Z_3 + Z_a \parallel Z_b = \frac{16 - j16}{9 - j4} + \frac{2640 - j320}{864 - j384} = \frac{4176 - j1856}{864 - j384} = 4.83 \Omega$$

P 9.50 [a]

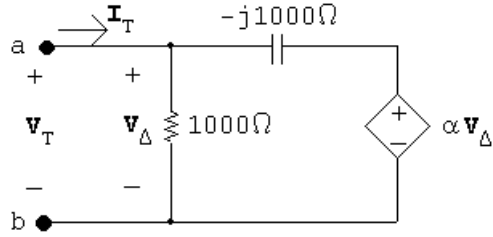

$$\mathbf{I}_T = \frac{\mathbf{V}_T}{1000} + \frac{\mathbf{V}_T - \alpha \mathbf{V}_T}{-j1000}$$

$$\frac{\mathbf{I}_T}{\mathbf{V}_T} = \frac{1}{1000} - \frac{(1 - \alpha)}{j1000} = \frac{j - 1 + \alpha}{j1000}$$

$$\therefore Z_{\text{Th}} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = \frac{j1000}{\alpha - 1 + j}$$

Z_{Th} is real when $\alpha = 1$.

[b] $Z_{\text{Th}} = 1000 \Omega$

[c] $Z_{\text{Th}} = 500 - j500 = \frac{j1000}{\alpha - 1 + j}$

$$= \frac{1000}{(\alpha - 1)^2 + 1} + j \frac{1000(\alpha - 1)}{(\alpha - 1)^2 + 1}$$

Equate the real parts:

$$\frac{1000}{(\alpha - 1)^2 + 1} = 500 \quad \therefore (\alpha - 1)^2 + 1 = 2$$

$$\therefore (\alpha - 1)^2 = 1 \quad \text{so} \quad \alpha = 0$$

Check the imaginary parts:


$$\left. \frac{(\alpha - 1)1000}{(\alpha - 1)^2 + 1} \right|_{\alpha=1} = -500$$

Thus, $\alpha = 0$.

[d] $Z_{\text{Th}} = \frac{1000}{(\alpha - 1)^2 + 1} + j \frac{1000(\alpha - 1)}{(\alpha - 1)^2 + 1}$

For $\text{Im}(Z_{\text{Th}}) > 0$, α must be greater than 1. So Z_{Th} is inductive for $1 < \alpha \leq 10$.

P 9.51

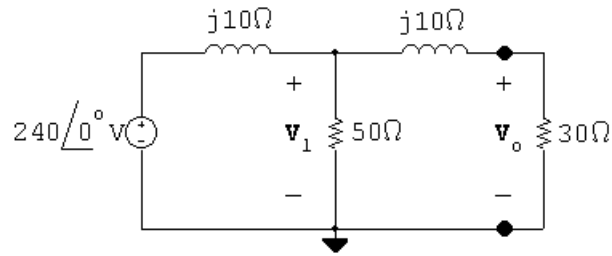

$$\frac{\mathbf{V}_1 - 240}{j10} + \frac{\mathbf{V}_1}{50} + \frac{\mathbf{V}_1}{30 + j10} = 0$$

 Solving for \mathbf{V}_1 yields

$$\mathbf{V}_1 = 198.63 \angle -24.44^\circ \text{ V}$$


$$\mathbf{V}_o = \frac{30}{30 + j10}(\mathbf{V}_1) = 188.43 \angle -42.88^\circ \text{ V}$$

 P 9.52 $j\omega L = j(2000)(1 \times 10^{-3}) = j2 \Omega$

$$\frac{1}{j\omega C} = -j \frac{10^6}{(2000)(100)} = -j5 \Omega$$

$$\mathbf{V}_{g1} = 20 \angle -36.87^\circ = 16 - j12 \text{ V}$$
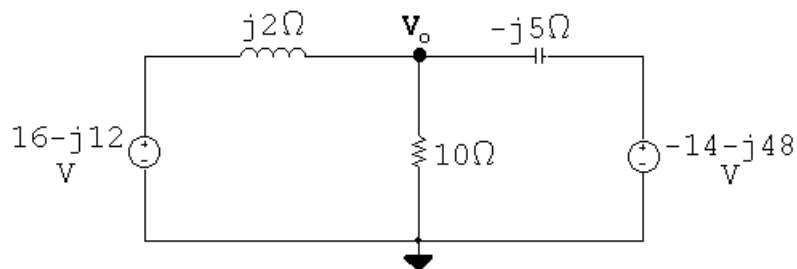
$$\mathbf{V}_{g2} = 50 \angle -106.26^\circ = -14 - j48 \text{ V}$$




$$\frac{\mathbf{V}_o - (16 - j12)}{j2} + \frac{\mathbf{V}_o}{10} + \frac{\mathbf{V}_o - (-14 - j48)}{-j5} = 0$$

Solving,


$$\mathbf{V}_o = 36 \angle 0^\circ \text{ V}$$

$$v_o(t) = 36 \cos 2000t \text{ V}$$

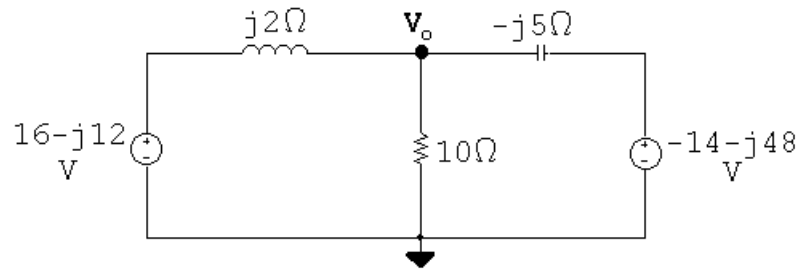P 9.53 From the solution to Problem 9.52 the phasor-domain circuit is



Making two source transformations yields

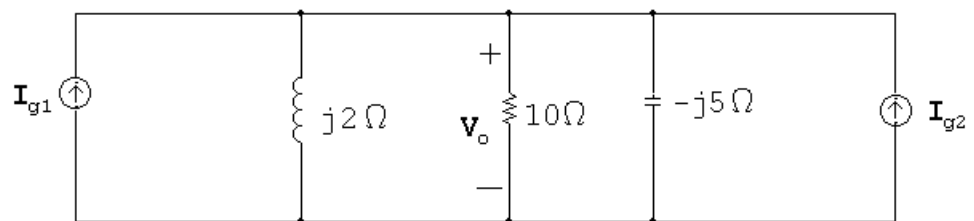

$$\mathbf{I}_{g1} = \frac{16 - j12}{j2} = -6 - j8 \text{ A}$$


$$\mathbf{I}_{g2} = \frac{-14 - j48}{-j5} = 9.6 - j2.8 \text{ A}$$

$$Y = \frac{1}{j2} + \frac{1}{10} + \frac{1}{-j5} = (0.1 - j0.3) \text{ S}$$

$$Z = \frac{1}{Y} = 1 + j3 \Omega$$

$$\mathbf{I}_e = \mathbf{I}_{g1} + \mathbf{I}_{g2} = 3.6 - j10.8 \text{ A}$$


Hence the circuit reduces to

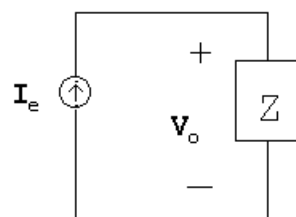

$$\mathbf{V}_o = Z\mathbf{I}_e = (1 + j3)(3.6 - j10.8) = 36\angle 0^\circ \text{ V}$$

$$\therefore v_o(t) = 36 \cos 2000t \text{ V}$$

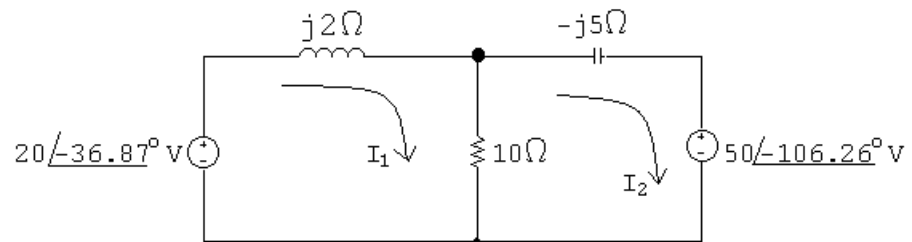P 9.54 The circuit with the mesh currents identified is shown below:



The mesh current equations are:

$$-20\angle-36.87^\circ + j2\mathbf{I}_1 + 10(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$50\angle-106.26^\circ + 10(\mathbf{I}_2 - \mathbf{I}_1) - j5\mathbf{I}_2 = 0$$

In standard form:

$$\mathbf{I}_1(10 + j2) + \mathbf{I}_2(-10) = 20\angle-36.87^\circ$$

$$\mathbf{I}_1(-10) + \mathbf{I}_2(10 - j5) = -50\angle-106.26^\circ = 50\angle73.74^\circ$$

Solving on a calculator yields:

$$\mathbf{I}_1 = -6 + j10\text{A}; \quad \mathbf{I}_2 = -9.6 + j10\text{A}$$


Thus,

$$\mathbf{V}_o = 10(\mathbf{I}_1 - \mathbf{I}_2) = 36\text{V}$$

and


$$v_o(t) = 36 \cos 2000t\text{V}$$

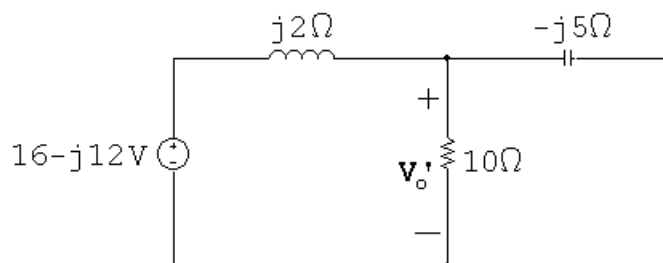P 9.55 From the solution to Problem 9.52 the phasor-domain circuit with the right-hand source removed is



$$\mathbf{V}_o' = \frac{10\parallel -j5}{j2 + 10\parallel -j5}(16 - j12) = 18 - j26\text{ V}$$

With the left hand source removed

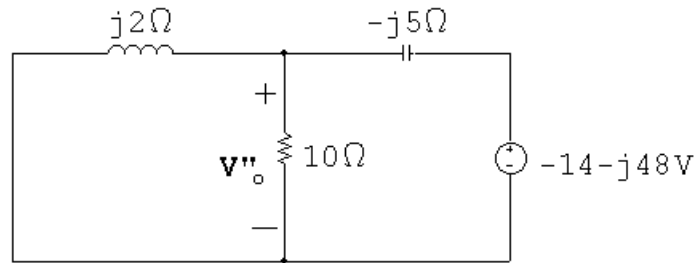

$$\mathbf{V}_o'' = \frac{10 \parallel j2}{-j5 + 10 \parallel j2} (-14 - j48) = 18 + j26 \text{ V}$$

$$\mathbf{V}_o = \mathbf{V}_o' + \mathbf{V}_o'' = 18 - j26 + 18 + j26 = 36 \text{ V}$$

$$v_o(t) = 36 \cos 2000t \text{ V}$$

P 9.56 Write a KCL equation at the top node:

$$\frac{\mathbf{V}_o}{-j8} + \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} + \frac{\mathbf{V}_o}{5} - (10 + j10) = 0$$


The constraint equation is:

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8}$$

Solving,

$$\mathbf{V}_o = j80 = 80 \angle 90^\circ \text{ V}$$

P 9.57

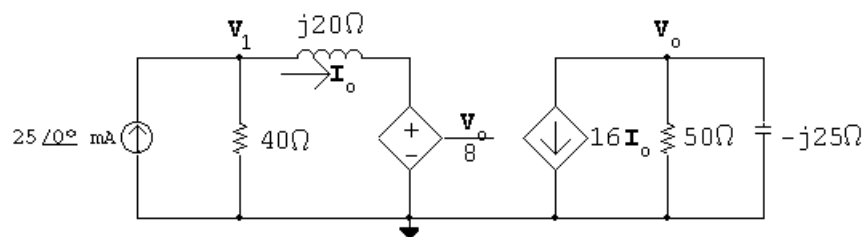

Write node voltage equations:

Left Node:

$$\frac{\mathbf{V}_1}{40} + \frac{\mathbf{V}_1 - \mathbf{V}_o/8}{j20} = 0.025 \angle 0^\circ$$

Right Node:

$$\frac{\mathbf{V}_o}{50} + \frac{\mathbf{V}_o}{j25} + 16\mathbf{I}_o = 0$$

The constraint equation is

$$\mathbf{I}_o = \frac{\mathbf{V}_1 - \mathbf{V}_o/8}{j20}$$


Solution:

$$\mathbf{V}_o = (4 + j4) = 5.66/\underline{45^\circ} \text{ V}$$

$$\mathbf{V}_1 = (0.8 + j0.6) = 1.0/\underline{36.87^\circ} \text{ V}$$

$$\mathbf{I}_o = (5 - j15) = 15.81/\underline{-71.57^\circ} \text{ mA}$$

P 9.58

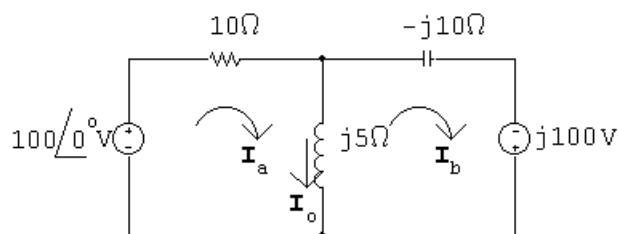

$$(10 + j5)\mathbf{I}_a - j5\mathbf{I}_b = 100\angle 0^\circ$$

$$-j5\mathbf{I}_a - j5\mathbf{I}_b = j100$$


Solving,

$$\mathbf{I}_a = -j10 \text{ A}; \quad \mathbf{I}_b = -20 + j10 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_a - \mathbf{I}_b = 20 - j20 = 28.28/\underline{-45^\circ} \text{ A}$$

$$i_o(t) = 28.28 \cos(50,000t - 45^\circ) \text{ A}$$

P 9.59

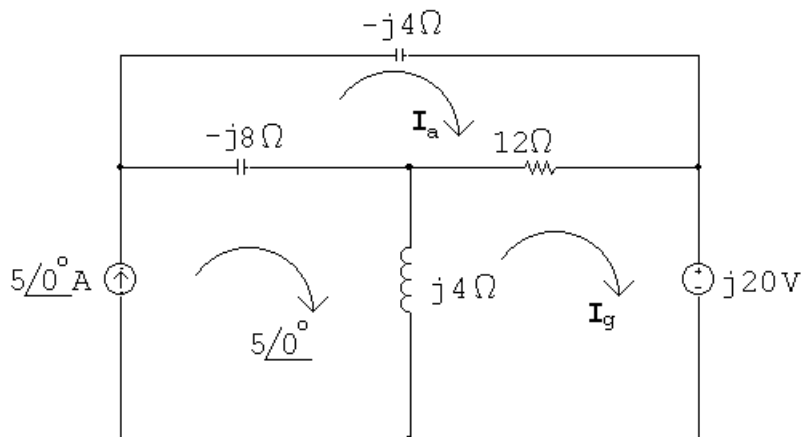


$$(12 - j12)\mathbf{I}_a - 12\mathbf{I}_g - 5(-j8) = 0$$

$$-12\mathbf{I}_a + (12 + j4)\mathbf{I}_g + j20 - 5(j4) = 0$$

Solving,

$$\mathbf{I}_g = 4 - j2 = 4.47/\underline{-26.57^\circ} \text{ A}$$

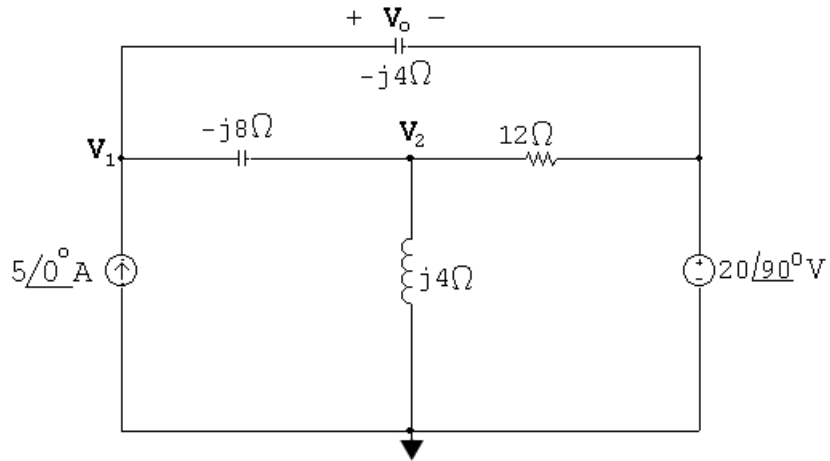P 9.60 Set up the frequency domain circuit to use the node voltage method:



$$\text{At } \mathbf{V}_1: \quad -5\angle 0^\circ + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j8} + \frac{\mathbf{V}_1 - 20\angle 90^\circ}{-j4} = 0$$

$$\text{At } \mathbf{V}_2: \quad \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j8} + \frac{\mathbf{V}_2}{j4} + \frac{\mathbf{V}_2 - 20\angle 90^\circ}{12} = 0$$

In standard form:

$$\mathbf{V}_1 \left(\frac{1}{-j8} + \frac{1}{-j4} \right) + \mathbf{V}_2 \left(-\frac{1}{-j8} \right) = 5\angle 0^\circ + \frac{20\angle 90^\circ}{-j4}$$

$$\mathbf{V}_1 \left(-\frac{1}{-j8} \right) + \mathbf{V}_2 \left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20\angle 90^\circ}{12}$$

Solving on a calculator:


$$\mathbf{V}_1 = -\frac{8}{3} + j\frac{4}{3} \text{ V} \qquad \mathbf{V}_2 = -8 + j4 \text{ V}$$

Thus

$$\mathbf{V}_0 = \mathbf{V}_1 - 20\angle 90^\circ = -\frac{8}{3} - j\frac{56}{3} = 18.86/\underline{-98.13^\circ} \text{ V}$$

P 9.61 $j\omega L = j5000(60 \times 10^{-3}) = j300 \Omega$
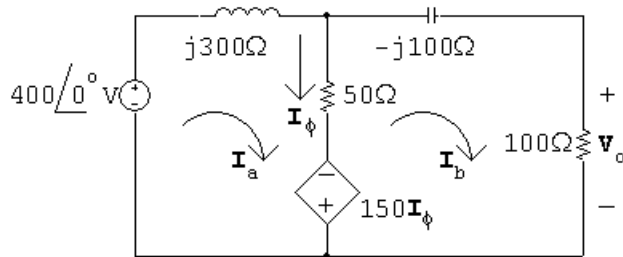
$$\frac{1}{j\omega C} = \frac{-j}{(5000)(2 \times 10^{-6})} = -j100 \Omega$$



$$-400\angle 0^\circ + (50 + j300)\mathbf{I}_a - 50\mathbf{I}_b - 150(\mathbf{I}_a - \mathbf{I}_b) = 0$$

$$(150 - j100)\mathbf{I}_b - 50\mathbf{I}_a + 150(\mathbf{I}_a - \mathbf{I}_b) = 0$$


Solving,

$$\mathbf{I}_a = -0.8 - j1.6 \text{ A}; \quad \mathbf{I}_b = -1.6 + j0.8 \text{ A}$$

$$\mathbf{V}_o = 100\mathbf{I}_b = -160 + j80 = 178.89\angle 153.43^\circ \text{ V}$$

$$v_o = 178.89 \cos(5000t + 153.43^\circ) \text{ V}$$

P 9.62

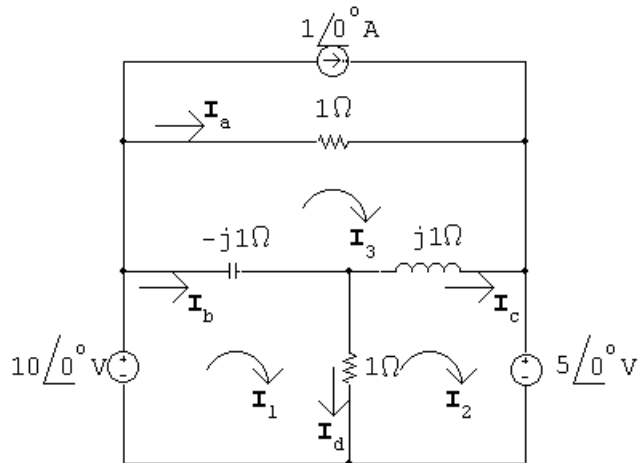

$$10\angle 0^\circ = (1 - j1)\mathbf{I}_1 - 1\mathbf{I}_2 + j1\mathbf{I}_3$$

$$-5\angle 0^\circ = -1\mathbf{I}_1 + (1 + j1)\mathbf{I}_2 - j1\mathbf{I}_3$$

$$1 = j1\mathbf{I}_1 - j1\mathbf{I}_2 + \mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 11 + j10 \text{ A}; \quad \mathbf{I}_2 = 11 + j5 \text{ A}; \quad \mathbf{I}_3 = 6 \text{ A}$$


$$\mathbf{I}_a = \mathbf{I}_3 - 1 = 5 \text{ A} = 5\angle 0^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_3 = 5 + j10 \text{ A} = 11.18\angle 63.43^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 - \mathbf{I}_3 = 5 + j5 \text{ A} = 7.07\angle 45^\circ \text{ A}$$

$$\mathbf{I}_d = \mathbf{I}_1 - \mathbf{I}_2 = j5 \text{ A} = 5\angle 90^\circ \text{ A}$$

P 9.63

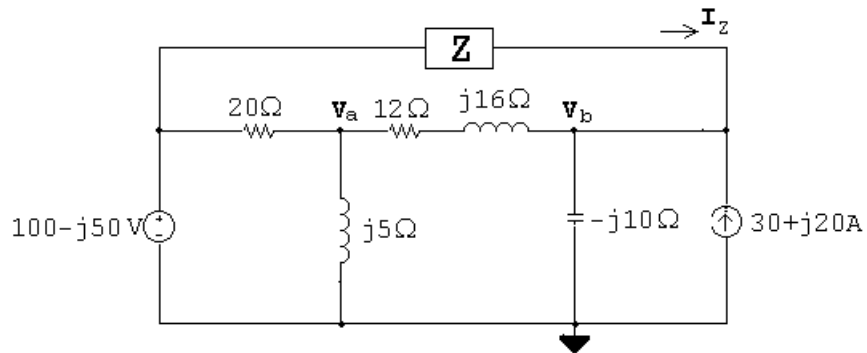

$$\frac{\mathbf{V}_a - (100 - j50)}{20} + \frac{\mathbf{V}_a}{j5} + \frac{\mathbf{V}_a - (140 + j30)}{12 + j16} = 0$$

Solving,

$$\mathbf{V}_a = 40 + j30 \text{ V}$$

$$\mathbf{I}_Z + (30 + j20) - \frac{140 + j30}{-j10} + \frac{(40 + j30) - (140 + j30)}{12 + j16} = 0$$

Solving,

$$\mathbf{I}_Z = -30 - j10 \text{ A}$$

$$Z = \frac{(100 - j50) - (140 + j30)}{-30 - j10} = 2 + j2 \Omega$$


P 9.64 [a] $\frac{1}{j\omega C} = -j50 \Omega$

$$j\omega L = j120 \Omega$$

$$Z_e = 100 \parallel -j50 = 20 - j40 \Omega$$

$$\mathbf{I}_g = 2 \angle 0^\circ$$
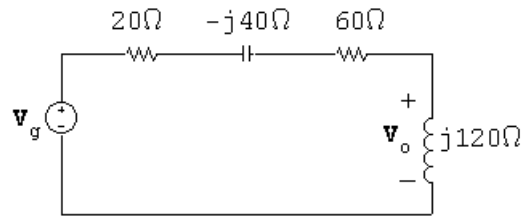
$$\mathbf{V}_g = \mathbf{I}_g Z_e = 2(20 - j40) = 40 - j80 \text{ V}$$



$$\mathbf{V}_o = \frac{j120}{80 + j80}(40 - j80) = 90 - j30 = 94.87 \angle -18.43^\circ \text{ V}$$

$$v_o = 94.87 \cos(16 \times 10^5 t - 18.43^\circ) \text{ V}$$

[b] $\omega = 2\pi f = 16 \times 10^5$; $f = \frac{8 \times 10^5}{\pi}$

$$T = \frac{1}{f} = \frac{\pi}{8 \times 10^5} = 1.25\pi \mu\text{s}$$

$$\therefore \frac{18.43}{360}(1.25\pi \mu\text{s}) = 201.09 \text{ ns}$$


$$\therefore v_o \text{ lags } i_g \text{ by } 201.09 \text{ ns}$$

P 9.65 $j\omega L = j10^6(10 \times 10^{-6}) = j10 \Omega$

$$\frac{1}{j\omega C} = \frac{-j}{(10^6)(0.1 \times 10^{-6})} = -j10 \Omega$$

$$\mathbf{V}_a = 50 \angle -90^\circ = -j50 \text{ V}$$
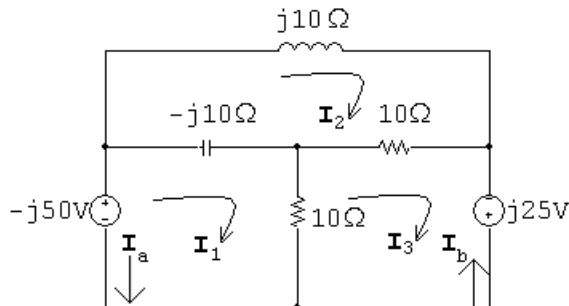
$$\mathbf{V}_b = 25 \angle 90^\circ = j25 \text{ V}$$



$$(10 - j10)\mathbf{I}_1 + j10\mathbf{I}_2 - 10\mathbf{I}_3 = -j50$$

$$j10\mathbf{I}_1 + 10\mathbf{I}_2 - 10\mathbf{I}_3 = 0$$

$$-10\mathbf{I}_1 - 10\mathbf{I}_2 + 20\mathbf{I}_3 = j25$$

Solving,

$$\mathbf{I}_1 = 0.5 - j1.5 \text{ A}; \quad \mathbf{I}_3 = -1 + j0.5 \text{ A} \quad \mathbf{I}_2 = -2.5 \text{ A}$$

$$\mathbf{I}_a = -\mathbf{I}_1 = -0.5 + j1.5 = 1.58/\underline{108.43^\circ} \text{ A}$$

$$\mathbf{I}_b = -\mathbf{I}_3 = 1 - j0.5 = 1.12/\underline{-26.57^\circ} \text{ A}$$


$$i_a = 1.58 \cos(10^6 t + 108.43^\circ) \text{ A}$$

$$i_b = 1.12 \cos(10^6 t - 26.57^\circ) \text{ A}$$

P 9.66 [a] $j\omega L_1 = j(5000)(2 \times 10^{-3}) = j10 \Omega$

$$j\omega L_2 = j(5000)(8 \times 10^{-3}) = j40 \Omega$$

$$j\omega M = j10 \Omega$$

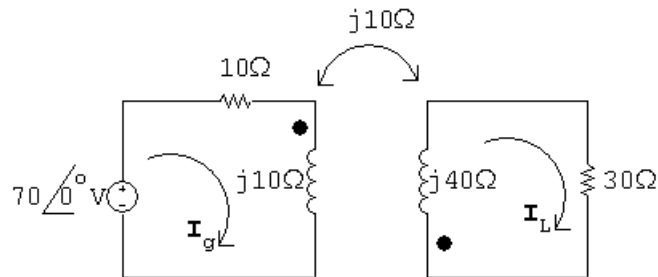

$$70 = (10 + j10)\mathbf{I}_g + j10\mathbf{I}_L$$

$$0 = j10\mathbf{I}_g + (30 + j40)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 4 - j3 \text{ A}; \quad \mathbf{I}_L = -1 \text{ A}$$

$$i_g = 5 \cos(5000t - 36.87^\circ) \text{ A}$$

$$i_L = 1 \cos(5000t - 180^\circ) \text{ A}$$

[b] $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{\sqrt{16}} = 0.5$

[c] When $t = 100\pi \mu\text{s}$,

$$5000t = (5000)(100\pi) \times 10^{-6} = 0.5\pi = \pi/2 \text{ rad} = 90^\circ$$

$$i_g(100\pi \mu\text{s}) = 5 \cos(53.13^\circ) = 3 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 1 \cos(-90^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(2 \times 10^{-3})(9) + 0 + 0 = 9 \text{ mJ}$$

When $t = 200\pi \mu\text{s}$,

$$5000t = \pi \text{ rad} = 180^\circ$$

$$i_g(200\pi \mu\text{s}) = 5 \cos(180^\circ - 36.87^\circ) = -4 \text{ A}$$

$$i_L(200\pi \mu\text{s}) = 1 \cos(180^\circ - 180^\circ) = 1 \text{ A}$$


$$w = \frac{1}{2}(2 \times 10^{-3})(16) + \frac{1}{2}(8 \times 10^{-3})(1) + 2 \times 10^{-3}(-4)(1) = 12 \text{ mJ}$$

P 9.67 Remove the voltage source to find the equivalent impedance:

$$Z_{\text{Th}} = 45 + j125 + \left(\frac{20}{|5 + j5|} \right)^2 (5 - j5) = 85 + j85 \Omega$$

Using voltage division:
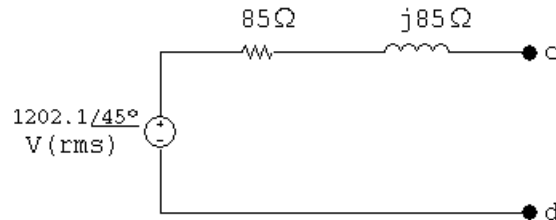
$$\mathbf{V}_{\text{Th}} = \mathbf{V}_{\text{cd}} = j20\mathbf{I}_1 = j20 \left(\frac{425}{5 + j5} \right) = 850 + j850 \text{ V} = 1202.1 \angle 45^\circ \text{ V}$$



P 9.68 [a] $j\omega L_1 = j(200 \times 10^3)(10^{-3}) = j200 \Omega$

$$j\omega L_2 = j(200 \times 10^3)(4 \times 10^{-3}) = j800 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{(200 \times 10^3)(12.5 \times 10^{-9})} = -j400 \Omega$$

$$\therefore Z_{22} = 100 + 200 + j800 - j400 = 300 + j400 \Omega$$

$$\therefore Z_{22}^* = 300 - j400 \Omega$$

$$M = k\sqrt{L_1 L_2} = 2k \times 10^{-3}$$

$$\omega M = (200 \times 10^3)(2k \times 10^{-3}) = 400k$$

$$Z_r = \left[\frac{400k}{500} \right]^2 (300 - j400) = k^2(192 - j256) \Omega$$

$$Z_{\text{in}} = 200 + j200 + 192k^2 - j256k^2$$

$$|Z_{\text{in}}| = [(200 + 192k^2)^2 + (200 - 256k^2)^2]^{\frac{1}{2}}$$

$$\frac{d|Z_{\text{in}}|}{dk} = \frac{1}{2}[(200 + 192k^2)^2 + (200 - 256k^2)^2]^{-\frac{1}{2}} \times$$

$$[2(200 + 192k^2)384k + 2(200 - 256k^2)(-512k)]$$

$$\frac{d|Z_{\text{in}}|}{dk} = 0 \text{ when}$$

$$768k(200 + 192k^2) - 1024k(200 - 256k^2) = 0$$

$$\therefore k^2 = 0.125; \quad \therefore k = \sqrt{0.125} = 0.3536$$

$$\begin{aligned} \text{[b]} \quad Z_{\text{in}}(\text{min}) &= 200 + 192(0.125) + j[200 - 0.125(256)] \\ &= 224 + j168 = 280/\underline{36.87^\circ} \Omega \end{aligned}$$

$$\mathbf{I}_1(\text{max}) = \frac{560/\underline{0^\circ}}{224 + j168} = 2/\underline{-36.87^\circ} \text{ A}$$

$$\therefore i_1(\text{peak}) = 2 \text{ A}$$

Note — You can test that the k value obtained from setting $d|Z_{\text{in}}|/dk = 0$ leads to a minimum by noting $0 \leq k \leq 1$. If $k = 1$,

$$Z_{\text{in}} = 392 - j56 = 395.98/\underline{-8.13^\circ} \Omega$$

Thus,

$$|Z_{\text{in}}|_{k=1} > |Z_{\text{in}}|_{k=\sqrt{0.125}}$$

If $k = 0$,

$$Z_{\text{in}} = 200 + j200 = 282.84/\underline{45^\circ} \Omega$$

Thus,

$$|Z_{\text{in}}|_{k=0} > |Z_{\text{in}}|_{k=\sqrt{0.125}}$$

P 9.69 $j\omega L_1 = j50 \Omega$

$$j\omega L_2 = j32 \Omega$$

$$\frac{1}{j\omega C} = -j20\ \Omega$$

$$j\omega M = j(4 \times 10^3)k\sqrt{(12.5)(8)} \times 10^{-3} = j40k\ \Omega$$

$$Z_{22} = 5 + j32 - j20 = 5 + j12\ \Omega$$

$$Z_{22}^* = 5 - j12\ \Omega$$

$$Z_r = \left[\frac{40k}{|5 + j12|} \right]^2 (5 - j12) = 47.337k^2 - j113.609k^2$$

$$Z_{ab} = 20 + j50 + 47.337k^2 - j113.609k^2 = (20 + 47.337k^2) + j(50 - 113.609k^2)$$

Z_{ab} is resistive when

$$50 - 113.609k^2 = 0 \quad \text{or} \quad k^2 = 0.44 \quad \text{so} \quad k = 0.66$$

$$\therefore Z_{ab} = 20 + (47.337)(0.44) = 40.83\ \Omega$$

P 9.70 [a] $j\omega L_L = j100\ \Omega$

$$j\omega L_2 = j500\ \Omega$$

$$Z_{22} = 300 + 500 + j100 + j500 = 800 + j600\ \Omega$$


$$Z_{22}^* = 800 - j600\ \Omega$$

$$\omega M = 270\ \Omega$$

$$Z_r = \left(\frac{270}{1000} \right)^2 [800 - j600] = 58.32 - j43.74\ \Omega$$

[b] $Z_{ab} = R_1 + j\omega L_1 + Z_r = 41.68 + j180 + 58.32 - j43.74 = 100 + j136.26\ \Omega$

P 9.71

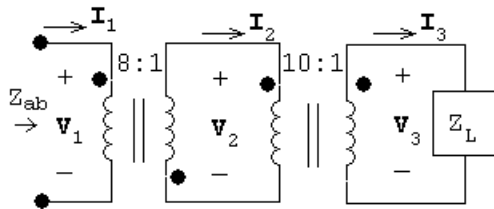

$$Z_L = \frac{\mathbf{V}_3}{\mathbf{I}_3} = 80\angle 60^\circ\ \Omega$$

$$\frac{\mathbf{V}_2}{10} = \frac{\mathbf{V}_3}{1}; \quad 10\mathbf{I}_2 = 1\mathbf{I}_3$$

$$\frac{\mathbf{V}_1}{8} = -\frac{\mathbf{V}_2}{1}; \quad 8\mathbf{I}_1 = -1\mathbf{I}_2$$

$$Z_{ab} = \frac{\mathbf{V}_1}{\mathbf{I}_1}$$

Substituting,

$$\begin{aligned} Z_{ab} &= \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{-8\mathbf{V}_2}{-\mathbf{I}_2/8} = \frac{8^2\mathbf{V}_2}{\mathbf{I}_2} \\ &= \frac{8^2(10\mathbf{V}_3)}{\mathbf{I}_3/10} = \frac{(8)^2(10)^2\mathbf{V}_3}{\mathbf{I}_3} = (8)^2(10)^2 Z_L = 512,000 \underline{60^\circ} \Omega \end{aligned}$$

P 9.72 In Eq. 9.69 replace $\omega^2 M^2$ with $k^2 \omega^2 L_1 L_2$ and then write X_{ab} as

$$\begin{aligned} X_{ab} &= \omega L_1 - \frac{k^2 \omega^2 L_1 L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \\ &= \omega L_1 \left\{ 1 - \frac{k^2 \omega L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \right\} \end{aligned}$$

For X_{ab} to be negative requires

$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 < k^2 \omega L_2 (\omega L_2 + \omega L_L)$$

or


$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 - k^2 \omega L_2 (\omega L_2 + \omega L_L) < 0$$

which reduces to

$$R_{22}^2 + \omega^2 L_2^2 (1 - k^2) + \omega L_2 \omega L_L (2 - k^2) + \omega^2 L_L^2 < 0$$

But $k \leq 1$ hence it is impossible to satisfy the inequality. Therefore X_{ab} can never be negative if X_L is an inductive reactance.

P 9.73 [a]

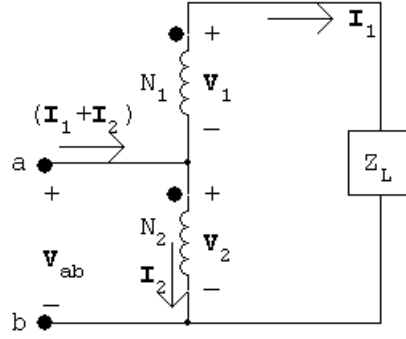

$$Z_{ab} = \frac{V_{ab}}{I_1 + I_2} = \frac{V_2}{I_1 + I_2} = \frac{V_2}{(1 + N_1/N_2)I_1}$$

$$N_1 I_1 = N_2 I_2, \quad I_2 = \frac{N_1}{N_2} I_1$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}, \quad V_1 = \frac{N_1}{N_2} V_2$$

$$V_1 + V_2 = Z_L I_1 = \left(\frac{N_1}{N_2} + 1 \right) V_2$$

$$Z_{ab} = \frac{I_1 Z_L}{(N_1/N_2 + 1)(1 + N_1/N_2)I_1}$$

$$\therefore Z_{ab} = \frac{Z_L}{[1 + (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

[b] Assume dot on the \$N_2\$ coil is moved to the lower terminal. Then

$$V_1 = -\frac{N_1}{N_2} V_2 \quad \text{and} \quad I_2 = -\frac{N_1}{N_2} I_1$$


As before

$$Z_{ab} = \frac{V_2}{I_1 + I_2} \quad \text{and} \quad V_1 + V_2 = Z_L I_1$$

$$\therefore Z_{ab} = \frac{V_2}{(1 - N_1/N_2)I_1} = \frac{Z_L I_1}{[1 - (N_1/N_2)]^2 I_1}$$

$$Z_{ab} = \frac{Z_L}{[1 - (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

P 9.74 [a]

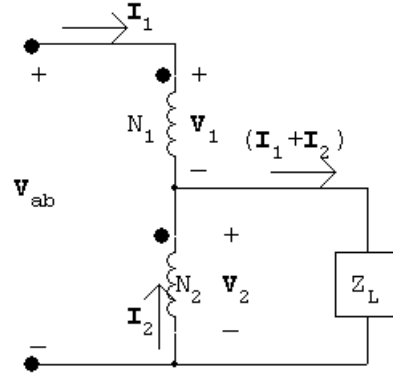

$$Z_{ab} = \frac{V_{ab}}{I_1} = \frac{V_1 + V_2}{I_1}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}, \quad V_2 = \frac{N_2}{N_1} V_1$$

$$N_1 I_1 = N_2 I_2, \quad I_2 = \frac{N_1}{N_2} I_1$$

$$V_2 = (I_1 + I_2) Z_L = I_1 \left(1 + \frac{N_1}{N_2} \right) Z_L$$

$$V_1 + V_2 = \left(\frac{N_1}{N_2} + 1 \right) V_2 = \left(1 + \frac{N_1}{N_2} \right)^2 Z_L I_1$$

$$\therefore Z_{ab} = \frac{(1 + N_1/N_2)^2 Z_L I_1}{I_1}$$

$$Z_{ab} = \left(1 + \frac{N_1}{N_2} \right)^2 Z_L \quad \text{Q.E.D.}$$

[b] Assume dot on N_2 is moved to the lower terminal, then

$$\frac{V_1}{N_1} = \frac{-V_2}{N_2}, \quad V_1 = \frac{-N_1}{N_2} V_2$$

$$N_1 I_1 = -N_2 I_2, \quad I_2 = \frac{-N_1}{N_2} I_1$$

As in part [a]

$$V_2 = (I_2 + I_1) Z_L \quad \text{and} \quad Z_{ab} = \frac{V_1 + V_2}{I_1}$$

$$Z_{ab} = \frac{(1 - N_1/N_2) V_2}{I_1} = \frac{(1 - N_1/N_2)(1 - N_1/N_2) Z_L I_1}{I_1}$$

$$Z_{ab} = [1 - (N_1/N_2)]^2 Z_L \quad \text{Q.E.D.}$$

P 9.75 [a] $\mathbf{I} = \frac{240}{24} + \frac{240}{j32} = (10 - j7.5) \text{ A}$

$$\mathbf{V}_s = 240\angle 0^\circ + (0.1 + j0.8)(10 - j7.5) = 247 + j7.25 = 247.11\angle 1.68^\circ \text{ V}$$

[b] Use the capacitor to eliminate the j component of \mathbf{I} , therefore

$$\mathbf{I}_c = j7.5 \text{ A}, \quad Z_c = \frac{240}{j7.5} = -j32 \Omega$$

$$\mathbf{V}_s = 240 + (0.1 + j0.8)10 = 241 + j8 = 241.13\angle 1.90^\circ \text{ V}$$

[c] Let \mathbf{I}_c denote the magnitude of the current in the capacitor branch. Then

$$\mathbf{I} = (10 - j7.5 + j\mathbf{I}_c) = 10 + j(\mathbf{I}_c - 7.5) \text{ A}$$

$$\begin{aligned} \mathbf{V}_s &= 240\angle \alpha = 240 + (0.1 + j0.8)[10 + j(\mathbf{I}_c - 7.5)] \\ &= (247 - 0.8\mathbf{I}_c) + j(7.25 + 0.1\mathbf{I}_c) \end{aligned}$$

It follows that

$$240 \cos \alpha = (247 - 0.8\mathbf{I}_c) \quad \text{and} \quad 240 \sin \alpha = (7.25 + 0.1\mathbf{I}_c)$$


Now square each term and then add to generate the quadratic equation

$$\mathbf{I}_c^2 - 605.77\mathbf{I}_c + 5325.48 = 0; \quad \mathbf{I}_c = 302.88 \pm 293.96$$

Therefore


$$\mathbf{I}_c = 8.92 \text{ A (smallest value) and } Z_c = 240/j8.92 = -j26.90 \Omega.$$

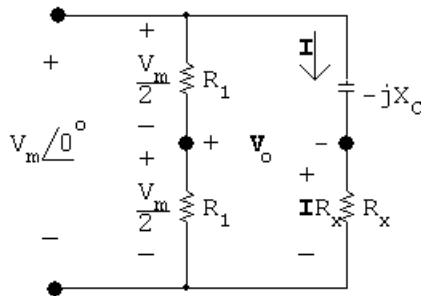P 9.76 The phasor domain equivalent circuit is




$$V_o = \frac{V_m\angle 0^\circ}{2} - \mathbf{I}R_x; \quad \mathbf{I} = \frac{V_m\angle 0^\circ}{R_x - jX_C}$$

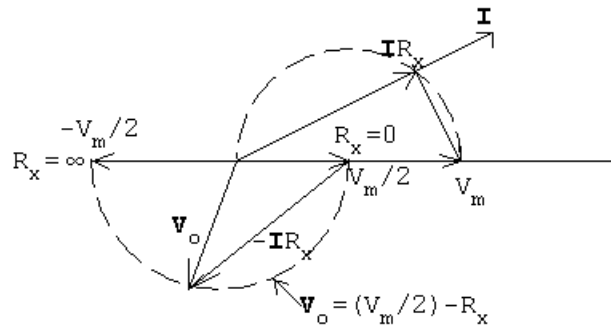As R_x varies from 0 to ∞ , the amplitude of v_o remains constant and its phase angle decreases from 0° to -180° , as shown in the following phasor diagram:



P 9.77 [a]

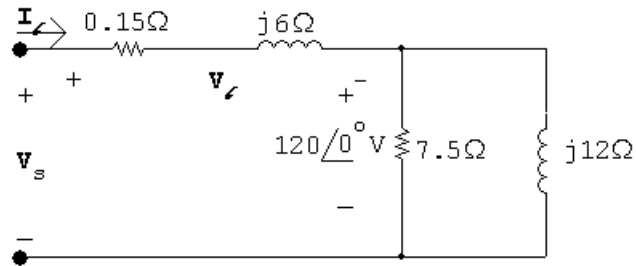


$$\mathbf{I}_\ell = \frac{120}{7.5} + \frac{120}{j12} = 16 - j10 \text{ A}$$

$$\mathbf{V}_\ell = (0.15 + j6)(16 - j10) = 62.4 + j94.5 = 113.24 \angle 56.56^\circ \text{ V}$$

$$\mathbf{V}_s = 120 \angle 0^\circ + \mathbf{V}_\ell = 205.43 \angle 27.39^\circ \text{ V}$$


[b]

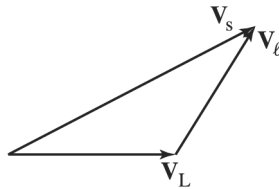

$$\text{[c] } \mathbf{I}_\ell = \frac{120}{2.5} + \frac{120}{j4} = 48 - j30 \text{ A}$$

$$\mathbf{V}_\ell = (0.15 + j6)(48 - j30) = 339.73 \angle 56.56^\circ \text{ V}$$
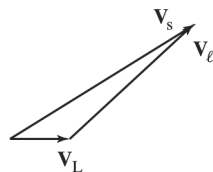
$$\mathbf{V}_s = 120 + \mathbf{V}_\ell = 418.02 \angle 42.7^\circ \text{ V}$$




The amplitude of \mathbf{V}_s must be increased from 205.43 V to 418.02 V (more than doubled) to maintain the load voltage at 120 V.

$$[\mathbf{d}] \quad \mathbf{I}_\ell = \frac{120}{2.5} + \frac{120}{j4} + \frac{120}{-j2} = 48 + j30 \text{ A}$$

$$\mathbf{V}_\ell = (0.15 + j6)(48 + j30) = 339.73/120.57^\circ \text{ V}$$
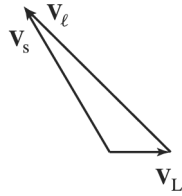
$$\mathbf{V}_s = 120 + \mathbf{V}_\ell = 297.23/100.23^\circ \text{ V}$$



The amplitude of \mathbf{V}_s must be increased from 205.43 V to 297.23 V to maintain the load voltage at 120 V.

$$\text{P 9.78} \quad \mathbf{V}_g = 4/0^\circ \text{ V}; \quad \frac{1}{j\omega C} = -j20 \text{ k}\Omega$$

Let \mathbf{V}_a = voltage across the capacitor, positive at upper terminal
Then:


$$\frac{\mathbf{V}_a - 4/0^\circ}{20,000} + \frac{\mathbf{V}_a}{-j20,000} + \frac{\mathbf{V}_a}{20,000} = 0; \quad \therefore \mathbf{V}_a = (1.6 - j0.8) \text{ V}$$

$$\frac{0 - \mathbf{V}_a}{20,000} + \frac{0 - \mathbf{V}_o}{10,000} = 0; \quad \mathbf{V}_o = -\frac{\mathbf{V}_a}{2}$$

$$\therefore \mathbf{V}_o = -0.8 + j0.4 = 0.89/153.43^\circ \text{ V}$$

$$v_o = 0.89 \cos(200t + 153.43^\circ) \text{ V}$$

P 9.79 [a]

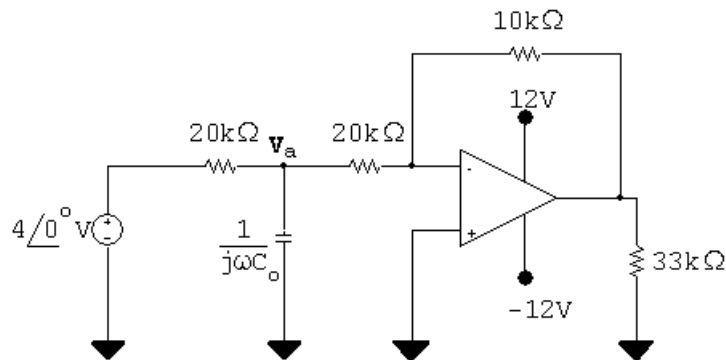

$$\frac{\mathbf{V}_a - 4/0^\circ}{20,000} + j\omega C_o \mathbf{V}_a + \frac{\mathbf{V}_a}{20,000} = 0$$

$$\mathbf{V}_a = \frac{4}{2 + j20,000\omega C_o}$$

$$\mathbf{V}_o = -\frac{\mathbf{V}_a}{2} \quad (\text{see solution to Prob. 9.78})$$

$$\mathbf{V}_o = \frac{-2}{2 + j4 \times 10^6 C_o} = \frac{2/\underline{180^\circ}}{2 + j4 \times 10^6 C_o}$$

$$\therefore \text{denominator angle} = 45^\circ$$


$$\text{so } 4 \times 10^6 C_o = 2 \quad \therefore \quad C_o = 0.5 \mu\text{F}$$

$$\text{[b]} \quad \mathbf{V}_o = \frac{2/\underline{180^\circ}}{2 + j2} = 0.707/\underline{135^\circ} \text{ V}$$

$$v_o = 0.707 \cos(200t + 135^\circ) \text{ V}$$

$$\text{P 9.80} \quad \frac{1}{j\omega C_1} = -j10 \text{ k}\Omega$$
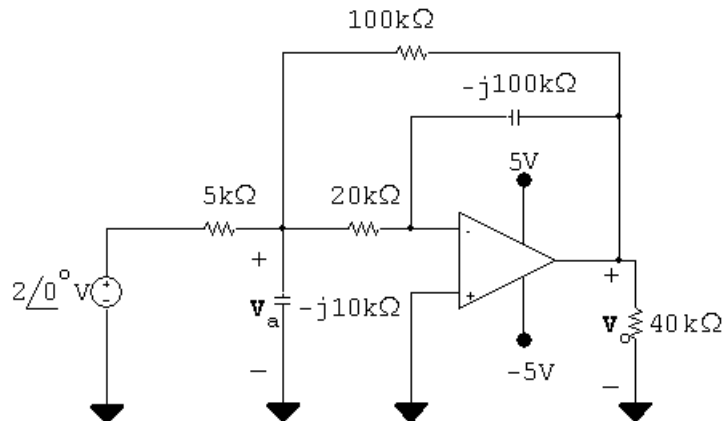
$$\frac{1}{j\omega C_2} = -j100 \text{ k}\Omega$$



$$\frac{\mathbf{V}_a - 2}{5000} + \frac{\mathbf{V}_a}{-j10,000} + \frac{\mathbf{V}_a}{20,000} + \frac{\mathbf{V}_a - \mathbf{V}_o}{100,000} = 0$$

$$20\mathbf{V}_a - 40 + j10\mathbf{V}_a + 5\mathbf{V}_a + \mathbf{V}_a - \mathbf{V}_o = 0$$

$$\therefore (26 + j10)\mathbf{V}_a - \mathbf{V}_o = 40$$

$$\frac{0 - \mathbf{V}_a}{20,000} + \frac{0 - \mathbf{V}_o}{-j100,000} = 0$$

$$j5\mathbf{V}_a - \mathbf{V}_o = 0$$

Solving,

$$\mathbf{V}_o = 1.43 + j7.42 = 7.55/\underline{79.11^\circ} \text{ V}$$

$$v_o(t) = 7.55 \cos(10^6 t + 79.11^\circ) \text{ V}$$

P 9.81 [a] $\mathbf{V}_g = 25\angle 0^\circ \text{ V}$

$$\mathbf{V}_p = \frac{20}{100} \mathbf{V}_g = 5\angle 0^\circ; \quad \mathbf{V}_n = \mathbf{V}_p = 5\angle 0^\circ \text{ V}$$

$$\frac{5}{80,000} + \frac{5 - \mathbf{V}_o}{Z_p} = 0$$

$$Z_p = -j80,000 \parallel 40,000 = 32,000 - j16,000 \Omega$$

$$\mathbf{V}_o = \frac{5Z_p}{80,000} + 5 = 7 - j1 = 7.07\angle -8.13^\circ \text{ V}$$

$$v_o = 7.07 \cos(50,000t - 8.13^\circ) \text{ V}$$

[b] $\mathbf{V}_p = 0.2V_m\angle 0^\circ; \quad \mathbf{V}_n = \mathbf{V}_p = 0.2V_m\angle 0^\circ$

$$\frac{0.2V_m}{80,000} + \frac{0.2V_m - \mathbf{V}_o}{32,000 - j16,000} = 0$$

$$\therefore \mathbf{V}_o = 0.2V_m + \frac{32,000 - j16,000}{80,000} V_m(0.2) = 0.2V_m(1.4 - j0.2)$$

$$\therefore |0.2V_m(1.4 - j0.2)| \leq 10$$

$$\therefore V_m \leq 35.36 \text{ V}$$

P 9.82 [a] $\frac{1}{j\omega C} = -j20 \Omega$

$$\frac{\mathbf{V}_n}{20} + \frac{\mathbf{V}_n - \mathbf{V}_o}{-j20} = 0$$

$$\frac{\mathbf{V}_o}{-j20} = \frac{\mathbf{V}_n}{20} + \frac{\mathbf{V}_n}{-j20}$$

$$\mathbf{V}_o = -j1\mathbf{V}_n + \mathbf{V}_n = (1 - j1)\mathbf{V}_n$$

$$\mathbf{V}_p = \frac{\mathbf{V}_g(1/j\omega C_o)}{5 + (1/j\omega C_o)} = \frac{\mathbf{V}_g}{1 + j(5)(10^5)C_o}$$

$$\mathbf{V}_g = 6\angle 0^\circ \text{ V}$$

$$\mathbf{V}_p = \frac{6\angle 0^\circ}{1 + j5 \times 10^5 C_o} = \mathbf{V}_n$$

$$\therefore \mathbf{V}_o = \frac{(1 - j1)6\angle 0^\circ}{1 + j5 \times 10^5 C_o}$$

$$|\mathbf{V}_o| = \frac{\sqrt{2}(6)}{\sqrt{1 + 25 \times 10^{10} C_o^2}} = 6$$


Solving,

$$C_o = 2 \mu\text{F}$$

$$\text{[b]} \quad \mathbf{V}_o = \frac{6(1-j1)}{1+j1} = -j6 \text{ V}$$

$$v_o = 6 \cos(10^5 t - 90^\circ) \text{ V}$$

P 9.83 [a]

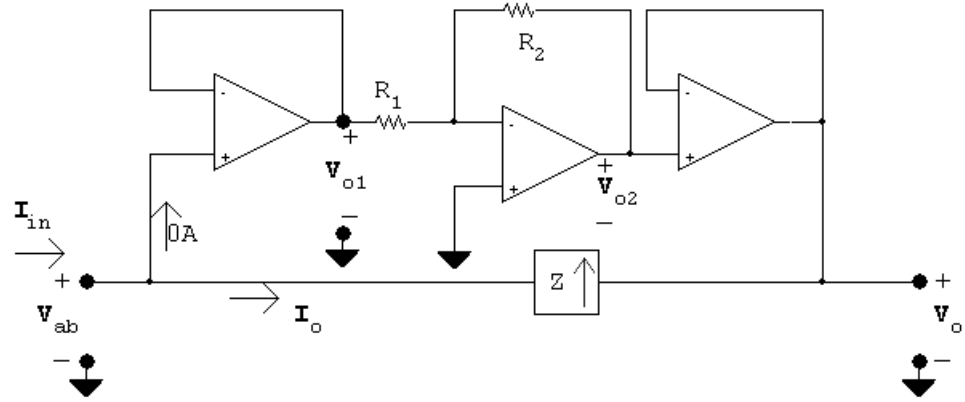

Because the op-amps are ideal $\mathbf{I}_{\text{in}} = \mathbf{I}_o$, thus

$$Z_{\text{ab}} = \frac{\mathbf{V}_{\text{ab}}}{\mathbf{I}_{\text{in}}} = \frac{\mathbf{V}_{\text{ab}}}{\mathbf{I}_o}; \quad \mathbf{I}_o = \frac{\mathbf{V}_{\text{ab}} - \mathbf{V}_o}{Z}$$

$$\mathbf{V}_{o1} = \mathbf{V}_{\text{ab}}; \quad \mathbf{V}_{o2} = -\left(\frac{R_2}{R_1}\right) \mathbf{V}_{o1} = -K \mathbf{V}_{o1} = -K \mathbf{V}_{\text{ab}}$$

$$\mathbf{V}_o = \mathbf{V}_{o2} = -K \mathbf{V}_{\text{ab}}$$

$$\therefore \mathbf{I}_o = \frac{\mathbf{V}_{\text{ab}} - (-K \mathbf{V}_{\text{ab}})}{Z} = \frac{(1+K) \mathbf{V}_{\text{ab}}}{Z}$$

$$\therefore Z_{\text{ab}} = \frac{\mathbf{V}_{\text{ab}}}{(1+K) \mathbf{V}_{\text{ab}}} Z = \frac{Z}{(1+K)}$$

$$\text{[b]} \quad Z = \frac{1}{j\omega C}; \quad Z_{\text{ab}} = \frac{1}{j\omega C(1+K)}; \quad \therefore C_{\text{ab}} = C(1+K)$$

P 9.84 [a] $\mathbf{I}_1 = \frac{120}{24} + \frac{240}{8.4 + j6.3} = 23.29 - j13.71 = 27.02 \angle -30.5^\circ \text{ A}$

$$\mathbf{I}_2 = \frac{120}{12} - \frac{120}{24} = 5 \angle 0^\circ \text{ A}$$

$$\mathbf{I}_3 = \frac{120}{12} + \frac{240}{8.4 + j6} = 28.29 - j13.71 = 31.44 \angle -25.87^\circ \text{ A}$$

$$\mathbf{I}_4 = \frac{120}{24} = 5 \angle 0^\circ \text{ A}; \quad \mathbf{I}_5 = \frac{120}{12} = 10 \angle 0^\circ \text{ A}$$

$$\mathbf{I}_6 = \frac{240}{8.4 + j6.3} = 18.29 - j13.71 = 22.86 \angle -36.87^\circ \text{ A}$$


[b] $\mathbf{I}_1 = 0$ $\mathbf{I}_3 = 15 \text{ A}$ $\mathbf{I}_5 = 10 \text{ A}$
 $\mathbf{I}_2 = 10 + 5 = 15 \text{ A}$ $\mathbf{I}_4 = -5 \text{ A}$ $\mathbf{I}_6 = 5 \text{ A}$

[c] The clock and television set were fed from the uninterrupted side of the circuit, that is, the 12Ω load includes the clock and the TV set.

[d] No, the motor current drops to 5 A, well below its normal running value of 22.86 A.

[e] After fuse A opens, the current in fuse B is only 15 A.

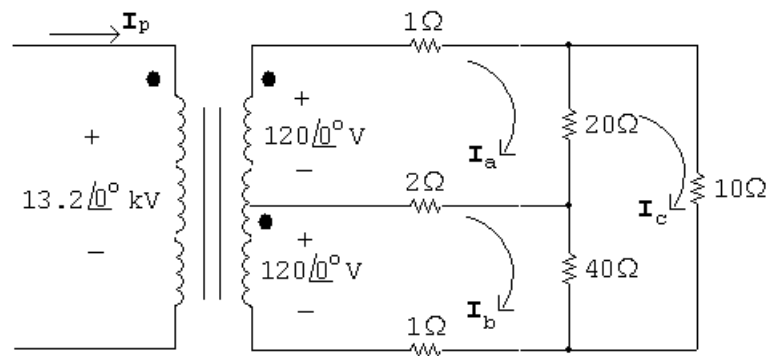P 9.85 [a] The circuit is redrawn, with mesh currents identified:



The mesh current equations are:

$$120\angle 0^\circ = 23\mathbf{I}_a - 2\mathbf{I}_b - 20\mathbf{I}_c$$

$$120\angle 0^\circ = -2\mathbf{I}_a + 43\mathbf{I}_b - 40\mathbf{I}_c$$

$$0 = -20\mathbf{I}_a - 40\mathbf{I}_b + 70\mathbf{I}_c$$

Solving,

$$\mathbf{I}_a = 24\angle 0^\circ \text{ A} \quad \mathbf{I}_b = 21.96\angle 0^\circ \text{ A} \quad \mathbf{I}_c = 19.40\angle 0^\circ \text{ A}$$

The branch currents are:

$$\mathbf{I}_1 = \mathbf{I}_a = 24\angle 0^\circ \text{ A}$$

$$\mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 2.04\angle 0^\circ \text{ A}$$

$$\mathbf{I}_3 = \mathbf{I}_b = 21.96\angle 0^\circ \text{ A}$$

$$\mathbf{I}_4 = \mathbf{I}_c = 19.40\angle 0^\circ \text{ A}$$

$$\mathbf{I}_5 = \mathbf{I}_a - \mathbf{I}_c = 4.6\angle 0^\circ \text{ A}$$

$$\mathbf{I}_6 = \mathbf{I}_b - \mathbf{I}_c = 2.55\angle 0^\circ \text{ A}$$

[b] Let N_1 be the number of turns on the primary winding; because the secondary winding is center-tapped, let $2N_2$ be the total turns on the secondary. From Fig. 9.58,

$$\frac{13,200}{N_1} = \frac{240}{2N_2} \quad \text{or} \quad \frac{N_2}{N_1} = \frac{1}{110}$$

The ampere turn balance requires

$$N_1 \mathbf{I}_p = N_2 \mathbf{I}_1 + N_2 \mathbf{I}_3$$

Therefore,

$$\mathbf{I}_p = \frac{N_2}{N_1} (\mathbf{I}_1 + \mathbf{I}_3) = \frac{1}{110} (24 + 21.96) = 0.42 \angle 0^\circ \text{ A}$$

Check voltages —


$$\mathbf{V}_4 = 10 \mathbf{I}_4 = 194 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_5 = 20 \mathbf{I}_5 = 92 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_6 = 40 \mathbf{I}_6 = 102 \angle 0^\circ \text{ V}$$

All of these voltages are low for a reasonable distribution circuit.

P 9.86 [a]

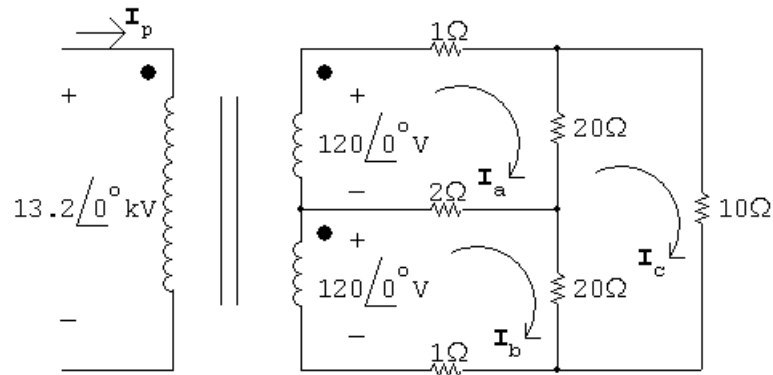

The three mesh current equations are

$$120 \angle 0^\circ = 23 \mathbf{I}_a - 2 \mathbf{I}_b - 20 \mathbf{I}_c$$

$$120 \angle 0^\circ = -2 \mathbf{I}_a + 23 \mathbf{I}_b - 20 \mathbf{I}_c$$

$$0 = -20 \mathbf{I}_a - 20 \mathbf{I}_b + 50 \mathbf{I}_c$$

Solving,

$$\mathbf{I}_a = 24 \angle 0^\circ \text{ A}; \quad \mathbf{I}_b = 24 \angle 0^\circ \text{ A}; \quad \mathbf{I}_c = 19.2 \angle 0^\circ \text{ A}$$

$$\therefore \mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 0 \text{ A}$$

$$\begin{aligned} \text{[b]} \quad \mathbf{I}_p &= \frac{N_2}{N_1} (\mathbf{I}_1 + \mathbf{I}_3) = \frac{N_2}{N_1} (\mathbf{I}_a + \mathbf{I}_b) \\ &= \frac{1}{110} (24 + 24) = 0.436 \angle 0^\circ \text{ A} \end{aligned}$$

[c] Check voltages —


$$\mathbf{V}_4 = 10\mathbf{I}_4 = 10\mathbf{I}_c = 192\angle 0^\circ \text{ V}$$

$$\mathbf{V}_5 = 20\mathbf{I}_5 = 20(\mathbf{I}_a - \mathbf{I}_c) = 96\angle 0^\circ \text{ V}$$

$$\mathbf{V}_6 = 40\mathbf{I}_6 = 20(\mathbf{I}_b - \mathbf{I}_c) = 96\angle 0^\circ \text{ V}$$

Where the two loads are equal, the current in the neutral conductor (\mathbf{I}_2) is zero, and the voltages \mathbf{V}_5 and \mathbf{V}_6 are equal. The voltages \mathbf{V}_4 , \mathbf{V}_5 , and \mathbf{V}_6 are too low for a reasonable distribution circuit.

P 9.87 [a]

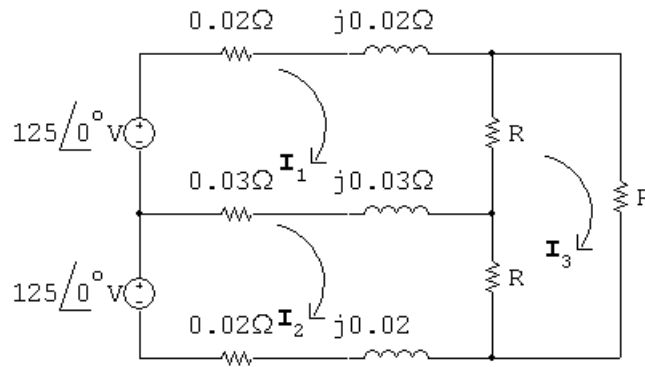

$$125 = (R + 0.05 + j0.05)\mathbf{I}_1 - (0.03 + j0.03)\mathbf{I}_2 - R\mathbf{I}_3$$

$$125 = -(0.03 + j0.03)\mathbf{I}_1 + (R + 0.05 + j0.05)\mathbf{I}_2 - R\mathbf{I}_3$$

Subtracting the above two equations gives


$$0 = (R + 0.08 + j0.08)\mathbf{I}_1 - (R + 0.08 + j0.08)\mathbf{I}_2$$

$$\therefore \mathbf{I}_1 = \mathbf{I}_2 \quad \text{so} \quad \mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = 0 \text{ A}$$

[b] $\mathbf{V}_1 = R(\mathbf{I}_1 - \mathbf{I}_3); \quad \mathbf{V}_2 = R(\mathbf{I}_2 - \mathbf{I}_3)$

Since $\mathbf{I}_1 = \mathbf{I}_2$ (from part [a]) $\mathbf{V}_1 = \mathbf{V}_2$

[c]

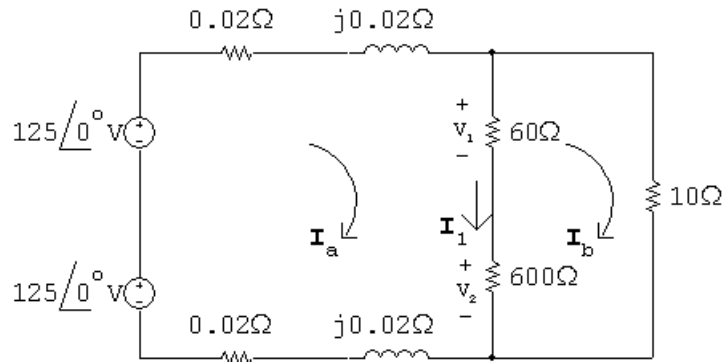

$$250 = (660.04 + j0.04)\mathbf{I}_a - 660\mathbf{I}_b$$

$$0 = -660\mathbf{I}_a + 670\mathbf{I}_b$$

Solving,

$$\mathbf{I}_a = 25.28 \angle -0.23^\circ = 25.28 - j0.10 \text{ A}$$


$$\mathbf{I}_b = 24.90 \angle -0.23^\circ = 24.90 - j0.10 \text{ A}$$

$$\mathbf{I}_1 = \mathbf{I}_a - \mathbf{I}_b = 0.377 - j0.00153 \text{ A}$$

$$\mathbf{V}_1 = 60\mathbf{I}_1 = 22.63 - j0.0195 = 22.64 \angle -0.23^\circ \text{ V}$$

$$\mathbf{V}_2 = 600\mathbf{I}_1 = 226.3 - j0.915 = 226.4 \angle -0.23^\circ \text{ V}$$

[d]

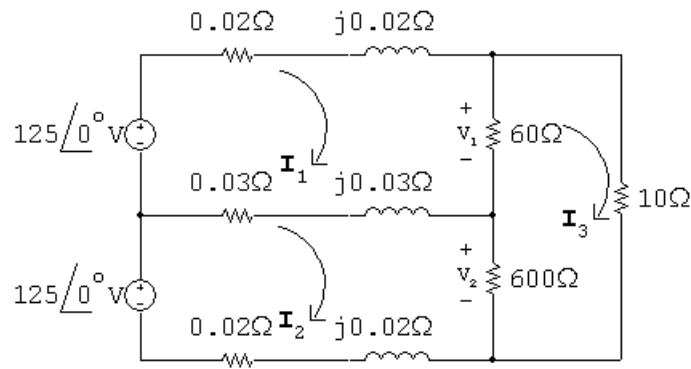

$$125 = (60.05 + j0.05)\mathbf{I}_1 - (0.03 + j0.03)\mathbf{I}_2 - 60\mathbf{I}_3$$

$$125 = -(0.03 + j0.03)\mathbf{I}_1 + (600.05 + j0.05)\mathbf{I}_2 - 600\mathbf{I}_3$$

$$0 = -60\mathbf{I}_1 - 600\mathbf{I}_2 + 670\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 26.97 \angle -0.24^\circ = 26.97 - j0.113 \text{ A}$$

$$\mathbf{I}_2 = 25.10 \angle -0.24^\circ = 25.10 - j0.104 \text{ A}$$

$$\mathbf{I}_3 = 24.90 \angle -0.24^\circ = 24.90 - j0.104 \text{ A}$$

$$\mathbf{V}_1 = 60(\mathbf{I}_1 - \mathbf{I}_3) = 124.4 \angle -0.27^\circ \text{ V}$$

$$\mathbf{V}_2 = 600(\mathbf{I}_2 - \mathbf{I}_3) = 124.6 \angle -0.20^\circ \text{ V}$$

[e] Because an open neutral can result in severely unbalanced voltages across the 125 V loads.

P 9.88 [a] Let N_1 = primary winding turns and $2N_2$ = secondary winding turns. Then

$$\frac{14,000}{N_1} = \frac{250}{2N_2}; \quad \therefore \frac{N_2}{N_1} = \frac{1}{112} = a$$

In part c),

$$\mathbf{I}_p = 2a\mathbf{I}_a$$

$$\begin{aligned} \therefore \mathbf{I}_p &= \frac{2N_2\mathbf{I}_a}{N_1} = \frac{1}{56}\mathbf{I}_a \\ &= \frac{1}{56}(25.28 - j0.10) \end{aligned}$$

$$\mathbf{I}_p = 451.4 - j1.8 \text{ mA} = 451.4/\underline{-0.23^\circ} \text{ mA}$$

In part d),

$$\mathbf{I}_p N_1 = \mathbf{I}_1 N_2 + \mathbf{I}_2 N_2$$

$$\begin{aligned} \therefore \mathbf{I}_p &= \frac{N_2}{N_1}(\mathbf{I}_1 + \mathbf{I}_2) \\ &= \frac{1}{112}(26.97 - j0.11 + 25.10 - j0.10) \\ &= \frac{1}{112}(52.07 - j0.22) \end{aligned}$$

$$\mathbf{I}_p = 464.9 - j1.9 \text{ mA} = 464.9/\underline{-0.24^\circ} \text{ mA}$$

[b] Yes, because the neutral conductor carries non-zero current whenever the load is not balanced.