
Active Filter Circuits

Assessment Problems

$$\text{AP 15.1 } H(s) = \frac{-(R_2/R_1)s}{s + (1/R_1C)}$$

$$\frac{1}{R_1C} = 1 \text{ rad/s}; \quad R_1 = 1 \Omega, \quad \therefore C = 1 \text{ F}$$

$$\frac{R_2}{R_1} = 1, \quad \therefore R_2 = R_1 = 1 \Omega$$

$$\therefore H_{\text{prototype}}(s) = \frac{-s}{s + 1}$$

$$\text{AP 15.2 } H(s) = \frac{-(1/R_1C)}{s + (1/R_2C)} = \frac{-20,000}{s + 5000}$$

$$\frac{1}{R_1C} = 20,000; \quad C = 5 \mu\text{F}$$

$$\therefore R_1 = \frac{1}{(20,000)(5 \times 10^{-6})} = 10 \Omega$$

$$\frac{1}{R_2C} = 5000$$

$$\therefore R_2 = \frac{1}{(5000)(5 \times 10^{-6})} = 40 \Omega$$

AP 15.3 $\omega_c = 2\pi f_c = 2\pi \times 10^4 = 20,000\pi \text{ rad/s}$

$$\therefore k_f = 20,000\pi = 62,831.85$$

$$C' = \frac{C}{k_f k_m} \quad \therefore \quad 0.5 \times 10^{-6} = \frac{1}{k_f k_m}$$

$$\therefore k_m = \frac{1}{(0.5 \times 10^{-6})(62,831.85)} = 31.83$$

AP 15.4 For a 2nd order prototype Butterworth high pass filter

$$H(s) = \frac{s^2}{s^2 + \sqrt{2}s + 1}$$

For the circuit in Fig. 15.25

$$H(s) = \frac{s^2}{s^2 + \left(\frac{2}{R_2 C}\right)s + \left(\frac{1}{R_1 R_2 C^2}\right)}$$

Equate the transfer functions. For $C = 1\text{F}$,

$$\frac{2}{R_2 C} = \sqrt{2}, \quad \therefore R_2 = \sqrt{2} = 1.414 \Omega$$

$$\frac{1}{R_1 R_2 C^2} = 1, \quad \therefore R_1 = \frac{1}{\sqrt{2}} = 0.707 \Omega$$

AP 15.5 $Q = 8, K = 5, \omega_o = 1000 \text{ rad/s}, C = 1 \mu\text{F}$

For the circuit in Fig 15.26

$$\begin{aligned} H(s) &= \frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}\right)} \\ &= \frac{K\beta s}{s^2 + \beta s + \omega_o^2} \end{aligned}$$

$$\beta = \frac{2}{R_3 C}, \quad \therefore R_3 = \frac{2}{\beta C}$$

$$\beta = \frac{\omega_o}{Q} = \frac{1000}{8} = 125 \text{ rad/s}$$

$$\therefore R_3 = \frac{2 \times 10^6}{(125)(1)} = 16 \text{ k}\Omega$$

$$K\beta = \frac{1}{R_1 C}$$

$$\therefore R_1 = \frac{1}{K\beta C} = \frac{1}{5(125)(1 \times 10^{-6})} = 1.6 \text{ k}\Omega$$

$$\omega_o^2 = \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}$$

$$10^6 = \frac{(1600 + R_2)}{(1600)(R_2)(16,000)(10^{-6})^2}$$

Solving for R_2 ,

$$R_2 = \frac{(1600 + R_2)10^6}{256 \times 10^5}, \quad 246R_2 = 16,000, \quad R_2 = 65.04 \Omega$$

AP 15.6 $\omega_o = 1000 \text{ rad/s}; \quad Q = 4;$

$$C = 2 \mu\text{F}$$

$$\begin{aligned} H(s) &= \frac{s^2 + (1/R^2 C^2)}{s^2 + \left[\frac{4(1-\sigma)}{RC} \right] s + \left(\frac{1}{R^2 C^2} \right)} \\ &= \frac{s^2 + \omega_o^2}{s^2 + \beta s + \omega_o^2}; \quad \omega_o = \frac{1}{RC}; \quad \beta = \frac{4(1-\sigma)}{RC} \end{aligned}$$

$$R = \frac{1}{\omega_o C} = \frac{1}{(1000)(2 \times 10^{-6})} = 500 \Omega$$

$$\beta = \frac{\omega_o}{Q} = \frac{1000}{4} = 250$$

$$\therefore \frac{4(1-\sigma)}{RC} = 250$$

$$4(1-\sigma) = 250RC = 250(500)(2 \times 10^{-6}) = 0.25$$

$$1-\sigma = \frac{0.25}{4} = 0.0625; \quad \therefore \sigma = 0.9375$$

Problems

P 15.1 Summing the currents at the inverting input node yields

$$\frac{0 - V_i}{Z_i} + \frac{0 - V_o}{Z_f} = 0$$

$$\therefore \frac{V_o}{Z_f} = -\frac{V_i}{Z_i}$$

$$\therefore H(s) = \frac{V_o}{V_i} = -\frac{Z_f}{Z_i}$$

P 15.2 [a]
$$Z_f = \frac{R_2(1/sC_2)}{[R_2 + (1/sC_2)]} = \frac{R_2}{R_2C_2s + 1}$$

$$= \frac{(1/C_2)}{s + (1/R_2C_2)}$$

Likewise

$$Z_i = \frac{(1/C_1)}{s + (1/R_1C_1)}$$

$$\therefore H(s) = \frac{-(1/C_2)[s + (1/R_1C_1)]}{[s + (1/R_2C_2)](1/C_1)}$$

$$= -\frac{C_1 [s + (1/R_1C_1)]}{C_2 [s + (1/R_2C_2)]}$$

[b]
$$H(j\omega) = \frac{-C_1}{C_2} \left[\frac{j\omega + (1/R_1C_1)}{j\omega + (1/R_2C_2)} \right]$$

$$H(j0) = \frac{-C_1}{C_2} \left(\frac{R_2C_2}{R_1C_1} \right) = \frac{-R_2}{R_1}$$

[c]
$$H(j\infty) = -\frac{C_1}{C_2} \left(\frac{j}{j} \right) = \frac{-C_1}{C_2}$$

[d] As $\omega \rightarrow 0$ the two capacitor branches become open and the circuit reduces to a resistive inverting amplifier having a gain of $-R_2/R_1$.

As $\omega \rightarrow \infty$ the two capacitor branches approach a short circuit and in this case we encounter an indeterminate situation; namely $v_n \rightarrow v_i$ but $v_n = 0$ because of the ideal op amp. At the same time the gain of the ideal op amp is infinite so we have the indeterminate form $0 \cdot \infty$. Although $\omega = \infty$ is indeterminate we can reason that for finite large values of ω $H(j\omega)$ will approach $-C_1/C_2$ in value. In other words, the circuit approaches a purely capacitive inverting amplifier with a gain of $(-1/j\omega C_2)/(1/j\omega C_1)$ or $-C_1/C_2$.

P 15.3 [a] $Z_f = \frac{(1/C_2)}{s + (1/R_2C_2)}$

$$Z_i = R_1 + \frac{1}{sC_1} = \frac{R_1}{s} [s + (1/R_1C_1)]$$

$$\begin{aligned} H(s) &= -\frac{(1/C_2)}{[s + (1/R_2C_2)]} \cdot \frac{s}{R_1[s + (1/R_1C_1)]} \\ &= -\frac{1}{R_1C_2} \frac{s}{[s + (1/R_1C_1)][s + (1/R_2C_2)]} \end{aligned}$$

[b] $H(j\omega) = -\frac{1}{R_1C_2} \frac{j\omega}{\left(j\omega + \frac{1}{R_1C_1}\right) \left(j\omega + \frac{1}{R_2C_2}\right)}$

$$H(j0) = 0$$

[c] $H(j\infty) = 0$

[d] As $\omega \rightarrow 0$ the capacitor C_1 disconnects v_i from the circuit. Therefore

$$v_o = v_n = 0.$$


As $\omega \rightarrow \infty$ the capacitor short circuits the feedback network, thus $Z_f = 0$ and therefore $v_o = 0$.

P 15.4 [a] $K = 10^{(10/20)} = 3.16 = \frac{R_2}{R_1}$

$$R_2 = \frac{1}{\omega_c C} = \frac{1}{(2\pi)(10^3)(750 \times 10^{-9})} = 212.21 \Omega$$

$$R_1 = \frac{R_2}{K} = \frac{212.21}{3.16} = 67.11 \Omega$$

[b]

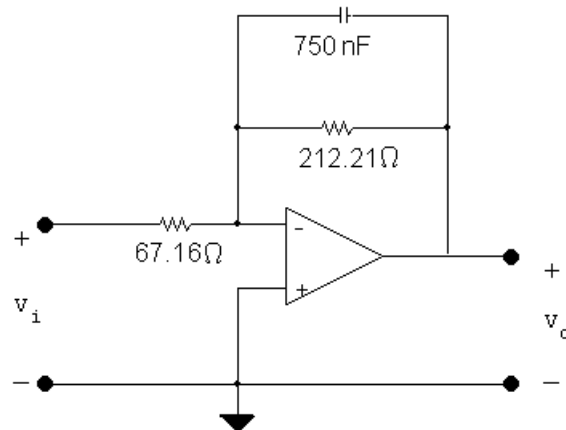


P 15.5 [a] $R_1 = \frac{1}{\omega_c C} = \frac{1}{(2\pi)(8 \times 10^3)(3.9 \times 10^{-9})} = 5.10 \text{ k}\Omega$

$$K = 10^{(14/20)} = 5.01 = \frac{R_2}{R_1}$$

$$\therefore R_2 = 5.01R_1 = 25.57 \text{ k}\Omega$$

[b]

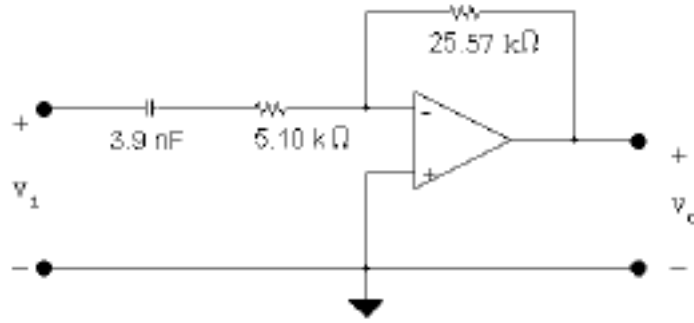P 15.6 For the RC circuit

$$H(s) = \frac{V_o}{V_i} = \frac{(1/RC)}{s + (1/RC)}$$

$$R' = k_m R; \quad C' = \frac{C}{k_m k_f}$$

$$\therefore R'C' = k_m R \frac{C}{k_m k_f} = \frac{1}{k_f} RC = \frac{1}{k_f}$$

$$\frac{1}{R'C'} = k_f$$

$$H'(s) = \frac{(1/R'C')}{s + (1/R'C')} = \frac{k_f}{s + k_f}$$

$$H'(s) = \frac{1}{(s/k_f) + 1}$$

For the RL circuit

$$H(s) = \frac{V_o}{V_i} = \frac{R/L}{s + (R/L)}$$

$$R' = k_m R; \quad L' = \frac{k_m}{k_f} L$$

$$\frac{R'}{L'} = \frac{k_m R}{\frac{k_m}{k_f} L} = k_f \left(\frac{R}{L} \right) = k_f$$

$$H'(s) = \frac{(R'/L')}{s + (R'/L')} = \frac{k_f}{s + k_f}$$

$$H'(s) = \frac{1}{(s/k_f) + 1}$$

P 15.7 For the RC circuit

$$H(s) = \frac{V_o}{V_i} = \frac{s}{s + (1/RC)}$$

$$R' = k_m R; \quad C' = \frac{C}{k_m k_f}$$

$$\therefore R'C' = \frac{RC}{k_f} = \frac{1}{k_f}; \quad \frac{1}{R'C'} = k_f$$

$$H'(s) = \frac{s}{s + (1/R'C')} = \frac{s}{s + k_f} = \frac{(s/k_f)}{(s/k_f) + 1}$$

For the RL circuit

$$H(s) = \frac{s}{s + (R/L)}$$

$$R' = k_m R; \quad L' = \frac{k_m L}{k_f}$$

$$\frac{R'}{L'} = k_f \left(\frac{R}{L} \right) = k_f$$

$$H'(s) = \frac{s}{s + (R'/L')} = \frac{s}{s + k_f} = \frac{(s/k_f)}{(s/k_f) + 1}$$

P 15.8 $H(s) = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)} = \frac{\beta s}{s^2 \beta s + \omega_o^2}$

For the prototype circuit $\omega_o = 1$ and $\beta = \omega_o/Q = 1/Q$.

For the scaled circuit

$$H'(s) = \frac{(R'/L')s}{s^2 + (R'/L')s + (1/L'C')}$$

where $R' = k_m R$; $L' = \frac{k_m}{k_f} L$; and $C' = \frac{C}{k_f k_m}$

$$\therefore \frac{R'}{L'} = \frac{k_m R}{\frac{k_m}{k_f} L} = k_f \left(\frac{R}{L} \right) = k_f \beta$$

$$\frac{1}{L'C'} = \frac{k_f k_m}{\frac{k_m}{k_f} LC} = \frac{k_f^2}{LC} = k_f^2$$

$$Q' = \frac{\omega'_o}{\beta'} = \frac{k_f \omega_o}{k_f \beta} = Q$$

therefore the Q of the scaled circuit is the same as the Q of the unscaled circuit.
Also note $\beta' = k_f \beta$.

$$\therefore H'(s) = \frac{\left(\frac{k_f}{Q}\right)s}{s^2 + \left(\frac{k_f}{Q}\right)s + k_f^2}$$

$$H'(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_f}\right)}{\left[\left(\frac{s}{k_f}\right)^2 + \frac{1}{Q}\left(\frac{s}{k_f}\right) + 1\right]}$$

P 15.9 [a] $L = 1 \text{ H}; \quad C = 1 \text{ F}$

$$R = \frac{1}{Q} = \frac{1}{20} = 0.05 \Omega$$


[b] $k_f = \frac{\omega'_o}{\omega_o} = 40,000; \quad k_m = \frac{R'}{R} = \frac{5000}{0.05} = 100,000$

Thus,

$$R' = k_m R = (0.05)(100,000) = 5 \text{ k}\Omega$$

$$L' = \frac{k_m}{k_f} L = \frac{100,000}{40,000}(1) = 2.5 \text{ H}$$
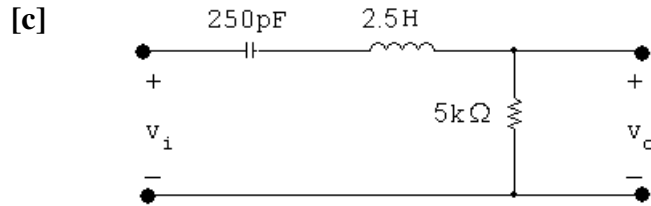
$$C' = \frac{C}{k_m k_f} = \frac{1}{(40,000)(100,000)} = 250 \text{ pF}$$



P 15.10 [a] Since $\omega_o^2 = 1/LC$ and $\omega_o = 1 \text{ rad/s}$,

$$C = \frac{1}{L} = \frac{1}{Q}$$

[b] $H(s) = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}$

$$H(s) = \frac{(1/Q)s}{s^2 + (1/Q)s + 1}$$

[c] In the prototype circuit

$$R = 1 \Omega; \quad L = 16 \text{ H}; \quad C = \frac{1}{L} = 0.0625 \text{ F}$$

$$\therefore k_m = \frac{R'}{R} = 10,000; \quad k_f = \frac{\omega'_o}{\omega_o} = 25,000$$


Thus

$$R' = k_m R = 10 \text{ k}\Omega$$

$$L' = \frac{k_m}{k_f} L = \frac{10,000}{25,000} (16) = 6.4 \text{ H}$$

$$C' = \frac{C}{k_m k_f} = \frac{0.0625}{(10,000)(25,000)} = 250 \text{ pF}$$

[d]

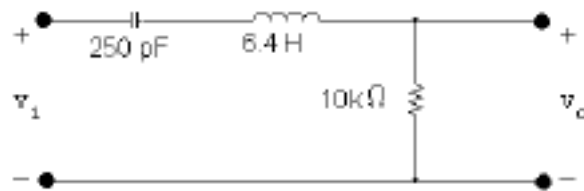

$$[e] \quad H'(s) = \frac{\frac{1}{16} \left(\frac{s}{25,000} \right)}{\left(\frac{s}{25,000} \right)^2 + \frac{1}{16} \left(\frac{s}{25,000} \right) + 1}$$

$$H'(s) = \frac{1562.5s}{s^2 + 1562.5s + 625 \times 10^6}$$

P 15.11 [a] Using the first prototype

$$\omega_o = 1 \text{ rad/s}; \quad C = 1 \text{ F}; \quad L = 1 \text{ H}; \quad R = 25 \Omega$$

$$k_m = \frac{R'}{R} = \frac{40,000}{25} = 1600; \quad k_f = \frac{\omega'_o}{\omega_o} = 50,000$$

Thus,

$$R' = k_m R = 40 \text{ k}\Omega; \quad L' = \frac{k_m}{k_f} L = \frac{1600}{50,000} (1) = 32 \text{ mH};$$

$$C' = \frac{C}{k_m k_f} = \frac{1}{(1600)(50,000)} = 12.5 \text{ nF}$$

Using the second prototype

$$\omega_o = 1 \text{ rad/s}; \quad C = 25 \text{ F}$$


$$L = \frac{1}{25} = 40 \text{ mH}; \quad R = 1 \Omega$$

$$k_m = \frac{R'}{R} = 40,000; \quad k_f = \frac{\omega'_o}{\omega_o} = 50,000$$

Thus,

$$R' = k_m R = 40 \text{ k}\Omega; \quad L' = \frac{k_m}{k_f} L = \frac{40,000}{50,000} (0.04) = 32 \text{ mH};$$
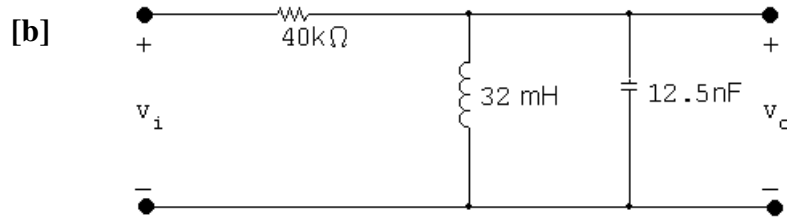
$$C' = \frac{C}{k_m k_f} = \frac{25}{(40,000)(50,000)} = 12.5 \text{ nF}$$



P 15.12 For the scaled circuit

$$H'(s) = \frac{s^2 + \left(\frac{1}{L'C'}\right)}{s^2 + \left(\frac{R'}{L'}\right)s + \left(\frac{1}{L'C'}\right)}$$

$$L' = \frac{k_m}{k_f} L; \quad C' = \frac{C}{k_m k_f}$$

$$\therefore \frac{1}{L'C'} = \frac{k_f^2}{LC}; \quad R' = k_m R$$

$$\therefore \frac{R'}{L'} = k_f \left(\frac{R}{L}\right)$$

It follows then that

$$\begin{aligned} H'(s) &= \frac{s^2 + \left(\frac{k_f^2}{LC}\right)}{s^2 + \left(\frac{R}{L}\right)k_f s + \frac{k_f^2}{LC}} \\ &= \frac{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{LC}\right)}{\left[\left(\frac{s}{k_f}\right)^2 + \left(\frac{R}{L}\right)\left(\frac{s}{k_f}\right) + \left(\frac{1}{LC}\right)\right]} \\ &= H(s)|_{s=s/k_f} \end{aligned}$$

P 15.13 For the circuit in Fig. 15.31

$$H(s) = \frac{s^2 + \left(\frac{1}{LC}\right)}{s^2 + \frac{s}{RC} + \left(\frac{1}{LC}\right)}$$

It follows that

$$H'(s) = \frac{s^2 + \frac{1}{L'C'}}{s^2 + \frac{s}{R'C'} + \frac{1}{L'C'}}$$

$$\text{where } R' = k_m R; \quad L' = \frac{k_m}{k_f} L;$$

$$C' = \frac{C}{k_m k_f}$$

$$\therefore \frac{1}{L'C'} = \frac{k_f^2}{LC}$$

$$\frac{1}{R'C'} = \frac{k_f}{RC}$$

$$\begin{aligned} H'(s) &= \frac{s^2 + \left(\frac{k_f^2}{LC}\right)}{s^2 + \left(\frac{k_f}{RC}\right)s + \frac{k_f^2}{LC}} \\ &= \frac{\left(\frac{s}{k_f}\right)^2 + \frac{1}{LC}}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{RC}\right)\left(\frac{s}{k_f}\right) + \frac{1}{LC}} \\ &= H(s)|_{s=s/k_f} \end{aligned}$$

P 15.14 [a] For the circuit in Fig. P15.14(a)

$$H(s) = \frac{V_o}{V_i} = \frac{s + \frac{1}{s}}{\frac{1}{Q} + s + \frac{1}{s}} = \frac{s^2 + 1}{s^2 + \left(\frac{1}{Q}\right)s + 1}$$

For the circuit in Fig. P15.14(b)

$$\begin{aligned} H(s) &= \frac{V_o}{V_i} = \frac{Qs + \frac{Q}{s}}{1 + Qs + \frac{Q}{s}} \\ &= \frac{Q(s^2 + 1)}{Qs^2 + s + Q} \\ H(s) &= \frac{s^2 + 1}{s^2 + \left(\frac{1}{Q}\right)s + 1} \end{aligned}$$

[b] $k_f \frac{\omega'_o}{\omega_o} = 10^4; \quad Q = 8;$

Replace s with s/k_f .

$$\begin{aligned} H'(s) &= \frac{\left(\frac{s}{10^4}\right)^2 + 1}{\left(\frac{s}{10^4}\right)^2 + \frac{1}{8}\left(\frac{s}{10^4}\right) + 1} \\ &= \frac{s^2 + 10^8}{s^2 + 1250s + 10^8} \end{aligned}$$

P 15.15 For prototype circuit (a):

$$\begin{aligned} H(s) &= \frac{V_o}{V_i} = \frac{Q}{Q + \frac{1}{s+1}} = \frac{Q}{Q + \frac{s}{s^2+1}} \\ H(s) &= \frac{Q(s^2+1)}{Q(s^2+1) + s} = \frac{s^2+1}{s^2 + \left(\frac{1}{Q}\right)s + 1} \end{aligned}$$

For prototype circuit (b):

$$\begin{aligned} H(s) &= \frac{V_o}{V_i} = \frac{1}{1 + \frac{(s/Q)}{(s^2+1)}} \\ &= \frac{s^2+1}{s^2 + \left(\frac{1}{Q}\right)s + 1} \end{aligned}$$

P 15.16 From the solution to Problem 14.15, $\omega_o = 100$ krad/s and $\beta = 12.5$ krad/s. Compute the two scale factors:

$$k_f = \frac{\omega'_o}{\omega_o} = \frac{2\pi(200 \times 10^3)}{100 \times 10^3} = 4\pi$$

$$k_m = \frac{1}{k_f} \frac{C}{C'} = \frac{1}{4\pi} \frac{10 \times 10^{-9}}{2.5 \times 10^{-9}} = \frac{1}{\pi}$$

Thus,

$$R' = k_m R = \frac{8000}{\pi} = 2546.48 \, \Omega \qquad L' = \frac{k_m}{k_f} L = \frac{1/\pi}{4\pi} (10 \times 10^{-3}) = 253.303 \, \mu\text{H}$$

Calculate the cutoff frequencies:

$$\omega'_{c1} = k_f \omega_{c1} = 4\pi(93.95 \times 10^3) = 1180.6 \text{ krad/s}$$

$$\omega'_{c2} = k_f \omega_{c2} = 4\pi(106.45 \times 10^3) = 1337.7 \text{ krad/s}$$

To check, calculate the bandwidth:

$$\beta' = \omega'_{c2} - \omega'_{c1} = 157.1 \text{ krad/s} = 4\pi\beta \text{ (Checks!)}$$

P 15.17 From the solution to Problem 14.24, $\omega_o = 10^6$ rad/s and $\beta = 2\pi(10.61)$ krad/s. Calculate the scale factors:

$$k_f = \frac{\omega'_o}{\omega_o} = \frac{50 \times 10^3}{10^6} = 0.05$$

$$k_m = \frac{k_f L'}{L} = \frac{0.05(200 \times 10^{-6})}{50 \times 10^{-6}} = 0.2$$

Thus,

$$R' = k_m R = (0.2)(750) = 150 \, \Omega \qquad C' = \frac{C}{k_m k_f} = \frac{20 \times 10^{-9}}{(0.2)(0.05)} = 2 \, \mu\text{F}$$

Calculate the bandwidth:

$$\beta' = k_f \beta = (0.05)[2\pi(10.61 \times 10^3)] = 3333 \text{ rad/s}$$


To check, calculate the quality factor:

$$Q = \frac{\omega_o}{\beta} = \frac{10^6}{2\pi(10.61 \times 10^3)} = 15$$

$$Q' = \frac{\omega'_o}{\beta'} = \frac{50 \times 10^3}{3333} = 15 \text{ (Checks)}$$

P 15.18 [a] $k_m = \frac{R'}{R} = \frac{1000}{1} = 1000$; $k_f = \frac{C}{k_m C'} = \frac{1}{(1000)(200 \times 10^{-9})} = 5000$
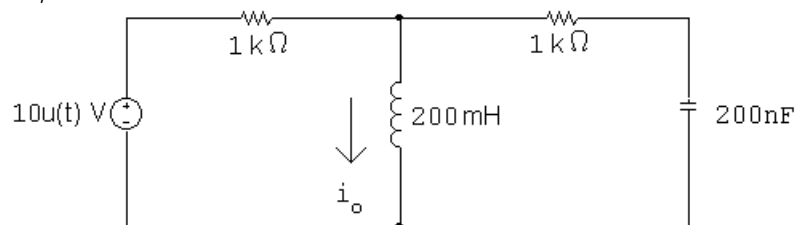
$$L' = \frac{k_m}{k_f}(L) = \frac{1000}{5000}(1) = 200 \text{ mH}$$



[b] $\frac{V - 10/s}{1000} + \frac{V}{0.2s} + \frac{V}{1000 + (5 \times 10^6/s)} = 0$

$$V \left(\frac{1}{1000} + \frac{5}{s} + \frac{s}{1000s + 5 \times 10^6} \right) = \frac{1}{100s}$$

$$V = \frac{10(s + 5000)}{2s^2 + 10,000s + 25 \times 10^6} = \frac{5(s + 5000)}{s^2 + 5000s + 12.5 \times 10^6}$$

$$\begin{aligned}
 I_o &= \frac{V}{0.2s} = \frac{25(s + 5000)}{s(s^2 + 5000s + 12.5 \times 10^6)} \\
 &= \frac{K_1}{s} + \frac{K_2}{s + 2500 - j2500} + \frac{K_2^*}{s + 2500 + j2500}
 \end{aligned}$$

$$K_1 = 0.01; \quad K_2 = -0.005$$

$$i_o(t) = 10 - 10e^{-2500t} \cos 2500t \text{ mA}$$

Since $k_m = 1000$ and the source voltage didn't change, the amplitude of the current is reduced by a factor of 1000. Since $k_f = 5000$ the coefficients of t are multiplied by 5000.

$$\text{P 15.19} \quad k_m = \frac{R'}{R} = \frac{5000}{50} = 100; \quad k_f = \frac{\omega'_o}{\omega_o} = 5000$$

$$C' = \frac{C}{k_m k_f} = \frac{4 \times 10^{-3}}{(100)(5000)} = 8 \text{ nF}$$

$$50 \Omega \rightarrow 5 \text{ k}\Omega; \quad 700 \Omega \rightarrow 70 \text{ k}\Omega$$

$$L' = \frac{k_m}{k_f} L = \frac{100}{5000} (20) = 0.4 \text{ H}$$

$$0.05v_\phi \rightarrow \frac{0.05}{100} v_\phi = 5 \times 10^{-4} v_\phi$$

The original expression for the current:

$$i_o(t) = 1728 + 2880e^{-20t} \cos(15t + 126.87^\circ) \text{ mA}$$

The frequency components will be multiplied by $k_f = 5000$:

$$20 \rightarrow 20(5000) = 10^5; \quad 15 \rightarrow 15(5000) = 75,000$$

The magnitudes will be reduced by $k_m = 100$:

$$1728 \rightarrow 1728/100 = 17.28; \quad 2880 \rightarrow 2880/100 = 28.80$$

The expression for the current in the scaled circuit is thus,

$$i_o(t) = 17.28 + 28.80e^{-10^5 t} \cos(75,000t + 126.87^\circ) \text{ mA}$$

P 15.20 [a] From Eq 15.1 we have

$$H(s) = \frac{-K\omega_c}{s + \omega_c}$$

$$\text{where } K = \frac{R_2}{R_1}, \quad \omega_c = \frac{1}{R_2 C}$$

$$\therefore H'(s) = \frac{-K'\omega'_c}{s + \omega'_c}$$

$$\text{where } K' = \frac{R'_2}{R'_1}, \quad \omega'_c = \frac{1}{R'_2 C'}$$

$$\text{By hypothesis } R'_1 = k_m R_1; \quad R'_2 = k_m R_2,$$

$$\text{and } C' = \frac{C}{k_f k_m}. \text{ It follows that}$$

$$K' = K \text{ and } \omega'_c = k_f \omega_c, \text{ therefore}$$

$$H'(s) = \frac{-K k_f \omega_c}{s + k_f \omega_c} = \frac{-K \omega_c}{\left(\frac{s}{k_f}\right) + \omega_c}$$

$$\text{[b]} H(s) = \frac{-K}{(s + 1)}$$

$$\text{[c]} H'(s) = \frac{-K}{\left(\frac{s}{k_f}\right) + 1} = \frac{-K k_f}{s + k_f}$$

P 15.21 [a] From Eq. 15.4

$$H(s) = \frac{-Ks}{s + \omega_c} \text{ where } K = \frac{R_2}{R_1} \text{ and}$$

$$\omega_c = \frac{1}{R_1 C}$$

$$\therefore H'(s) = \frac{-K's}{s + \omega'_c} \text{ where } K' = \frac{R'_2}{R'_1}$$

$$\text{and } \omega'_c = \frac{1}{R'_1 C'}$$

By hypothesis

$$R'_1 = k_m R_1; \quad R'_2 = k_m R_2; \quad C' = \frac{C}{k_m k_f}$$

It follows that

$$K' = K \text{ and } \omega'_c = k_f \omega_c$$

$$\therefore H'(s) = \frac{-Ks}{s + k_f \omega_c} = \frac{-K(s/k_f)}{\left(\frac{s}{k_f}\right) + \omega_c}$$

$$\text{[b]} \quad H(s) = \frac{-Ks}{(s+1)}$$

$$\text{[c]} \quad H'(s) = \frac{-K(s/k_f)}{\left(\frac{s}{k_f} + 1\right)} = \frac{-Ks}{(s+k_f)}$$

$$\text{P 15.22 [a]} \quad H_{\text{hp}} = \frac{-s}{s+1}; \quad k_f = \frac{\omega'_o}{\omega} = \frac{1000(2\pi)}{1} = 2000\pi$$


$$\therefore H'_{\text{hp}} = \frac{-s}{s+2000\pi}$$

$$\frac{1}{R_H C_H} = 2000\pi; \quad \therefore R_H = \frac{1}{(2000\pi)(0.1 \times 10^{-6})} = 1.59 \text{ k}\Omega$$

$$H_{\text{lp}} = \frac{-1}{s+1}; \quad k_f = \frac{\omega'_o}{\omega} = \frac{5000(2\pi)}{1} = 10,000\pi$$

$$\therefore H'_{\text{lp}} = \frac{-10,000\pi}{s+10,000\pi}$$
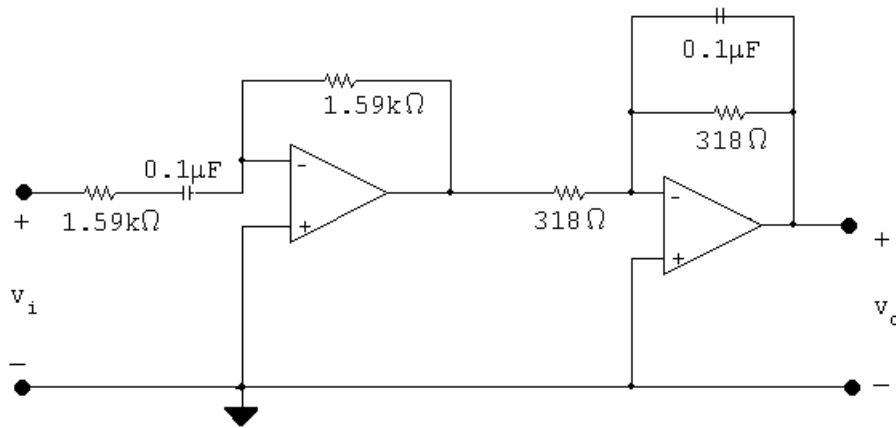
$$\frac{1}{R_L C_L} = 10,000\pi; \quad \therefore R_L = \frac{1}{(10,000\pi)(0.1 \times 10^{-6})} = 318.3 \Omega$$




$$\begin{aligned} \text{[b]} \quad H'(s) &= \frac{-s}{s+2000\pi} \cdot \frac{-10,000\pi}{s+10,000\pi} \\ &= \frac{10,000\pi s}{(s+2000\pi)(s+10,000\pi)} \end{aligned}$$

$$\text{[c]} \quad \omega_o = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{(2000\pi)(10,000\pi)} = 1000\pi\sqrt{20} \text{ rad/s}$$

$$\begin{aligned} H'(j\omega_o) &= \frac{(10,000\pi)(j1000\pi\sqrt{20})}{(2000\pi + j1000\pi\sqrt{20})(10,000\pi + j1000\pi\sqrt{20})} \\ &= \frac{j10\sqrt{20}}{(2 + j\sqrt{20})(10 + j\sqrt{20})} = 0.8333 \angle 0^\circ \end{aligned}$$

[d] $G = 20 \log_{10}(0.8333) = -1.58 \text{ dB}$

[e]

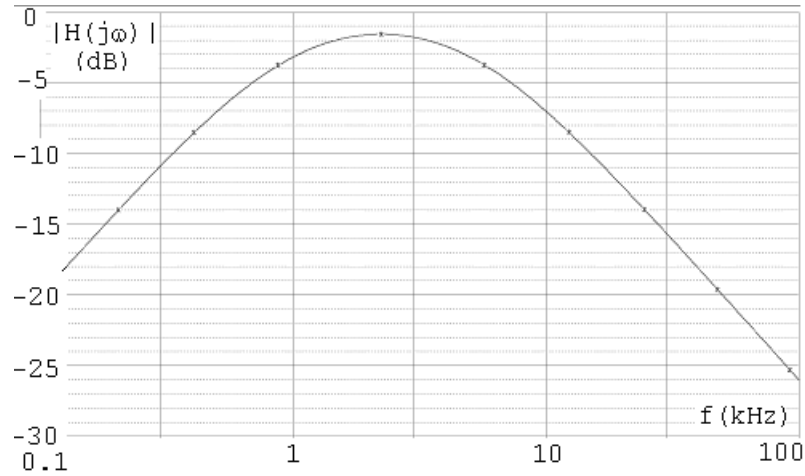

P 15.23 **[a]** For the high-pass section:

$$k_f = \frac{\omega'_o}{\omega} = \frac{4000(2\pi)}{1} = 8000\pi$$

$$H'(s) = \frac{-s}{s + 8000\pi}$$

$$\therefore \frac{1}{R_1(10 \times 10^{-9})} = 8000\pi; \quad R_1 = 3.98 \text{ k}\Omega \quad \therefore \quad R_2 = 3.98 \text{ k}\Omega$$

For the low-pass section:


$$k_f = \frac{\omega'_o}{\omega} = \frac{400(2\pi)}{1} = 800\pi$$

$$H'(s) = \frac{-800\pi}{s + 800\pi}$$

$$\therefore \frac{1}{R_2(10 \times 10^{-9})} = 800\pi; \quad R_2 = 39.8 \text{ k}\Omega \quad \therefore \quad R_1 = 39.8 \text{ k}\Omega$$

0 dB gain corresponds to $K = 1$. In the summing amplifier we are free to choose R_f and R_i so long as $R_f/R_i = 1$. To keep from having many different resistance values in the circuit we opt for $R_f = R_i = 39.8 \text{ k}\Omega$.

[b]

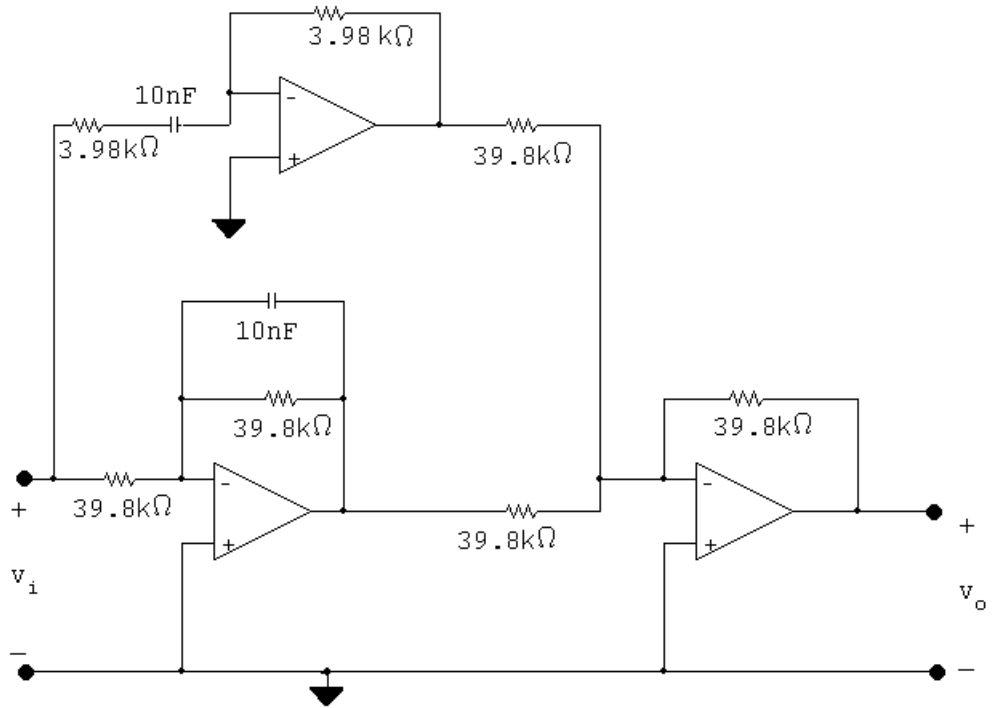


$$\begin{aligned} \text{[c]} \quad H'(s) &= \frac{s}{s + 8000\pi} + \frac{800\pi}{s + 800\pi} \\ &= \frac{s^2 + 1600\pi s + 64 \times 10^5 \pi^2}{(s + 800\pi)(s + 8000\pi)} \end{aligned}$$

$$\text{[d]} \quad \omega_o = \sqrt{(8000\pi)(800\pi)} = 800\pi\sqrt{10}$$

$$\begin{aligned} H'(j800\pi\sqrt{10}) &= \frac{-(800\pi\sqrt{10})^2 + 1600\pi(j800\pi\sqrt{10}) + 64 \times 10^5 \pi^2}{(800\pi + j800\pi\sqrt{10})(8000\pi + j800\pi\sqrt{10})} \\ &= \frac{j128 \times 10^4 \sqrt{10} \pi^2}{(800\pi)^2 (1 + j\sqrt{10})(10 + j\sqrt{10})} \\ &= \frac{j2\sqrt{10}}{(1 + j\sqrt{10})(10 + j\sqrt{10})} \\ &= 0.1818 \angle 0^\circ \end{aligned}$$

$$\text{[e]} \quad G = 20 \log_{10} 0.1818 = -14.81 \text{ dB}$$

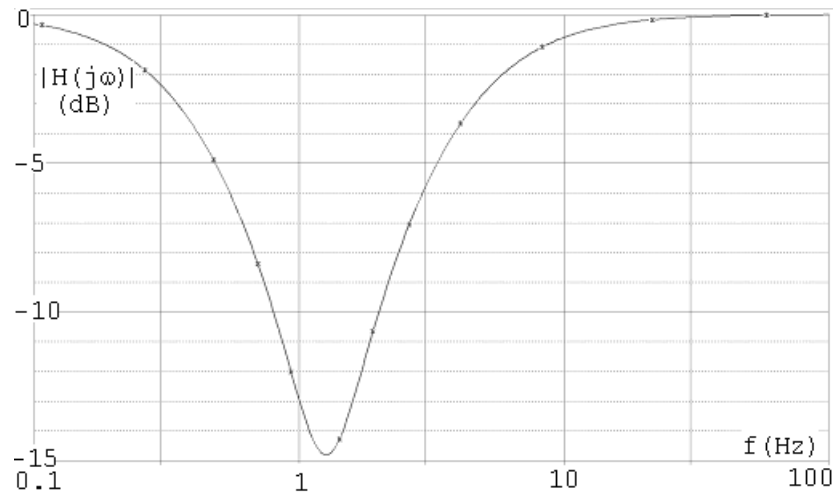[f]

P 15.24 **[a]** $H(s) = \frac{(1/sC)}{R + (1/sC)} = \frac{(1/RC)}{s + (1/RC)}$

$$H(j\omega) = \frac{(1/RC)}{j\omega + (1/RC)}$$

$$|H(j\omega)| = \frac{(1/RC)}{\sqrt{\omega^2 + (1/RC)^2}}$$

$$|H(j\omega)|^2 = \frac{(1/RC)^2}{\omega^2 + (1/RC)^2}$$

[b] Let V_a be the voltage across the capacitor, positive at the upper terminal. Then

$$\frac{V_a - V_i}{R_1} + sCV_a + \frac{V_a}{R_2 + sL} = 0$$

Solving for V_a yields

$$V_a = \frac{(R_2 + sL)V_i}{R_1LCs^2 + (R_1R_2C + L)s + (R_1 + R_2)}$$

But

$$V_o = \frac{sLV_a}{R_2 + sL}$$

Therefore

$$V_o = \frac{sLV_i}{R_1LCs^2 + (L + R_1R_2C)s + (R_1 + R_2)}$$

$$H(s) = \frac{sL}{R_1LCs^2 + (L + R_1R_2C)s + (R_1 + R_2)}$$

$$H(j\omega) = \frac{j\omega L}{[(R_1 + R_2) - R_1LC\omega^2] + j\omega(L + R_1R_2C)}$$

$$|H(j\omega)| = \frac{\omega L}{\sqrt{[R_1 + R_2 - R_1 LC\omega^2]^2 + \omega^2(L + R_1 R_2 C)^2}}$$

$$\begin{aligned} |H(j\omega)|^2 &= \frac{\omega^2 L^2}{(R_1 + R_2 - R_1 LC\omega^2)^2 + \omega^2(L + R_1 R_2 C)^2} \\ &= \frac{\omega^2 L^2}{R_1^2 L^2 C^2 \omega^4 + (L^2 + R_1^2 R_2^2 C^2 - 2R_1^2 LC + 2R_1 R_2 LC)\omega^2 + (R_1 + R_2)^2} \end{aligned}$$

[c] Let V_a be the voltage across R_2 positive at the upper terminal. Then

$$\frac{V_a - V_i}{R_1} + \frac{V_a}{R_2} + V_a sC + V_a sC = 0$$

$$(0 - V_a)sC + (0 - V_a)sC + \frac{0 - V_o}{R_3} = 0$$

$$\therefore V_a = \frac{R_2 V_i}{2R_1 R_2 C s + R_1 + R_2}$$

$$\text{and } V_a = -\frac{V_o}{2R_3 C s}$$

It follows directly that

$$H(s) = \frac{V_o}{V_i} = \frac{-2R_2 R_3 C s}{2R_1 R_2 C s + (R_1 + R_2)}$$

$$\therefore H(j\omega) = \frac{-2R_2 R_3 C(j\omega)}{(R_1 + R_2) + j\omega(2R_1 R_2 C)}$$

$$|H(j\omega)| = \frac{2R_2 R_3 C \omega}{\sqrt{(R_1 + R_2)^2 + \omega^2 4R_1^2 R_2^2 C^2}}$$

$$|H(j\omega)|^2 = \frac{4R_2^2 R_3^2 C^2 \omega^2}{(R_1 + R_2)^2 + 4R_1^2 R_2^2 C^2 \omega^2}$$

P 15.25 $\omega_o = 2\pi f_o = 400\pi \text{ rad/s}$

$$\beta = 2\pi(1000) = 2000\pi \text{ rad/s}$$

$$\therefore \omega_{c2} - \omega_{c1} = 2000\pi$$

$$\sqrt{\omega_{c1}\omega_{c2}} = \omega_o = 400\pi$$

Solve for the cutoff frequencies:

$$\omega_{c1}\omega_{c2} = 16 \times 10^4 \pi^2$$

$$\omega_{c_2} = \frac{16 \times 10^4 \pi^2}{\omega_{c_1}}$$

$$\therefore \frac{16 \times 10^4 \pi^2}{\omega_{c_1}} - \omega_{c_1} = 2000\pi$$

$$\text{or } \omega_{c_1}^2 + 2000\pi\omega_{c_1} - 16 \times 10^4 \pi^2 = 0$$

$$\omega_{c_1} = -1000\pi \pm \sqrt{10^6 \pi^2 + 0.16 \times 10^6 \pi^2}$$

$$\omega_{c_1} = 1000\pi(-1 \pm \sqrt{1.16}) = 242.01 \text{ rad/s}$$

$$\therefore \omega_{c_2} = 2000\pi + 242.01 = 6525.19 \text{ rad/s}$$

$$\text{Thus, } f_{c_1} = 38.52 \text{ Hz} \quad \text{and} \quad f_{c_2} = 1038.52 \text{ Hz}$$

$$\text{Check: } \beta = f_{c_2} - f_{c_1} = 1000 \text{ Hz}$$

$$\omega_{c_2} = \frac{1}{R_L C_L} = 6525.19$$

$$R_L = \frac{1}{(6525.19)(5 \times 10^{-6})} = 30.65 \Omega$$

$$\omega_{c_1} = \frac{1}{R_H C_H} = 242.01$$

$$R_H = \frac{1}{(242.01)(5 \times 10^{-6})} = 826.43 \Omega$$

P 15.26 $\omega_o = 1000 \text{ rad/s}; \quad \text{GAIN} = 6$

$$\beta = 4000 \text{ rad/s}; \quad C = 0.2 \mu\text{F}$$

$$\beta = \omega_{c_2} - \omega_{c_1} = 4000$$

$$\omega_o = \sqrt{\omega_{c_1} \omega_{c_2}} = 1000$$

Solve for the cutoff frequencies:

$$\therefore \omega_{c_1}^2 + 4000\omega_{c_1} - 10^6 = 0$$

$$\omega_{c_1} = -2000 \pm 1000\sqrt{5} = 236.07 \text{ rad/s}$$

$$\omega_{c_2} = 4000 + \omega_{c_1} = 4236.07 \text{ rad/s}$$

$$\text{Check: } \beta = \omega_{c_2} - \omega_{c_1} = 4000 \text{ rad/s}$$

$$\omega_{c_1} = \frac{1}{R_L C_L}$$

$$\therefore R_L = \frac{1}{(0.2 \times 10^{-6})(236.07)} = 21.81 \text{ k}\Omega$$

$$\frac{1}{R_H C_H} = 4236.07$$

$$R_H = \frac{1}{(0.2 \times 10^{-6})(4236.07)} = 1.18 \text{ k}\Omega$$

$$\frac{R_f}{R_i} = 6$$

$$\text{If } R_i = 1 \text{ k}\Omega \quad R_f = 6R_i = 6 \text{ k}\Omega$$

P 15.27 [a] $y = 20 \log_{10} \frac{1}{\sqrt{1 + \omega^{2n}}} = -10 \log_{10}(1 + \omega^{2n})$

From the laws of logarithms we have

$$y = \left(\frac{-10}{\ln 10} \right) \ln(1 + \omega^{2n})$$

Thus

$$\frac{dy}{d\omega} = \left(\frac{-10}{\ln 10} \right) \frac{2n\omega^{2n-1}}{(1 + \omega^{2n})}$$

$$x = \log_{10} \omega = \frac{\ln \omega}{\ln 10}$$

$$\therefore \ln \omega = x \ln 10$$

$$\frac{1}{\omega} \frac{d\omega}{dx} = \ln 10, \quad \frac{d\omega}{dx} = \omega \ln 10$$

$$\frac{dy}{dx} = \left(\frac{dy}{d\omega} \right) \left(\frac{d\omega}{dx} \right) = \frac{-20n\omega^{2n}}{1 + \omega^{2n}} \text{ dB/decade}$$

$$\text{at } \omega = \omega_c = 1 \text{ rad/s}$$

$$\frac{dy}{dx} = -10n \text{ dB/decade.}$$

$$\text{[b]} \quad y = 20 \log_{10} \frac{1}{[\sqrt{1 + \omega^2}]^n} = -10n \log_{10}(1 + \omega^2)$$

$$= \frac{-10n}{\ln 10} \ln(1 + \omega^2)$$

$$\frac{dy}{d\omega} = \frac{-10n}{\ln 10} \left(\frac{1}{1 + \omega^2} \right) 2\omega = \frac{-20n\omega}{(\ln 10)(1 + \omega^2)}$$

As before

$$\frac{d\omega}{dx} = \omega(\ln 10); \quad \therefore \quad \frac{dy}{dx} = \frac{-20n\omega^2}{(1 + \omega^2)}$$

$$\text{At the corner } \omega_c = \sqrt{2^{1/n} - 1} \quad \therefore \quad \omega_c^2 = 2^{1/n} - 1$$

$$\frac{dy}{dx} = \frac{-20n[2^{1/n} - 1]}{2^{1/n}} \text{ dB/decade.}$$

[c] For the Butterworth Filter		For the cascade of identical sections	
n	dy/dx (dB/decade)	n	dy/dx (dB/decade)
1	-10	1	-10
2	-20	2	-11.72
3	-30	3	-12.38
4	-40	4	-12.73
∞	$-\infty$	∞	-13.86

[d] It is apparent from the calculations in part (c) that as n increases the amplitude characteristic at the cutoff frequency decreases at a much faster rate for the Butterworth filter.

Hence the transition region of the Butterworth filter will be much narrower than that of the cascaded sections.

$$\text{P 15.28 [a]} \quad n \cong \frac{(-0.05)(-30)}{\log_{10}(7000/2000)} \cong 2.76$$

$$\therefore n = 3$$

$$\text{[b]} \quad \text{Gain} = 20 \log_{10} \frac{1}{\sqrt{1 + (7000/2000)^6}} = -32.65 \text{ dB}$$

P 15.29 [a] For the scaled circuit

$$H'(s) = \frac{1/(R')^2 C'_1 C'_2}{s^2 + \frac{2}{R' C'_1} s + \frac{1}{(R')^2 C'_1 C'_2}}$$

where

$$R' = k_m R; \quad C'_1 = C_1/k_f k_m; \quad C'_2 = C_2/k_f k_m$$

It follows that

$$\frac{1}{(R')^2 C'_1 C'_2} = \frac{k_f^2}{R^2 C_1 C_2}$$

$$\frac{2}{R' C'_1} = \frac{2k_f}{RC_1}$$

$$\begin{aligned} \therefore H'(s) &= \frac{k_f^2 / R^2 C_1 C_2}{s^2 + \frac{2k_f}{RC_1} s + \frac{k_f^2}{R^2 C_1 C_2}} \\ &= \frac{1/R^2 C_1 C_2}{\left(\frac{s}{k_f}\right)^2 + \frac{2}{RC_1} \left(\frac{s}{k_f}\right) + \frac{1}{R^2 C_1 C_2}} \end{aligned}$$

P 15.30 [a] $H(s) = \frac{1}{(s+1)(s^2+s+1)}$

[b] $f_c = 2000 \text{ Hz}; \quad \omega_c = 4000\pi \text{ rad/s}; \quad k_f = 4000\pi$

$$\begin{aligned} H'(s) &= \frac{1}{\left(\frac{s}{k_f} + 1\right)\left[\left(\frac{s}{k_f}\right)^2 + \frac{s}{k_f} + 1\right]} \\ &= \frac{k_f^3}{(s + k_f)(s^2 + k_f s + k_f^2)} \\ &= \frac{(4000\pi)^3}{(s + 4000\pi)[s^2 + 4000\pi s + (4000\pi)^2]} \end{aligned}$$

[c] $H'(j14,000\pi) = \frac{64}{(4 + j14)(-180 + j56)}$
 $= 0.02332 / -236.77^\circ$

Gain = $20 \log_{10}(0.02332) = -32.65 \text{ dB}$

P 15.31 [a] In the first-order circuit $R = 1 \Omega$ and $C = 1 \text{ F}$.


$$k_m = \frac{R'}{R} = \frac{1000}{1} = 1000; \quad k_f = \frac{\omega'_o}{\omega_o} = \frac{2\pi(2000)}{1} = 4000\pi$$

$$R' = k_m R = 1000 \Omega; \quad C' = \frac{C}{k_m k_f} = \frac{1}{(1000)(4000\pi)} = 79.58 \text{ nF}$$

In the second-order circuit $R = 1 \Omega$, $2/C_1 = 1$ so $C_1 = 2 \text{ F}$, and $C_2 = 1/C_1 = 0.5 \text{ F}$. Therefore in the scaled second-order circuit

$$R' = k_m R = 1000 \Omega; \quad C'_1 = \frac{C_1}{k_m k_f} = \frac{2}{(1000)(4000\pi)} = 159.15 \text{ nF}$$

$$C'_2 = \frac{C_2}{k_m k_f} = \frac{0.5}{(1000)(4000\pi)} = 39.79 \text{ nF}$$

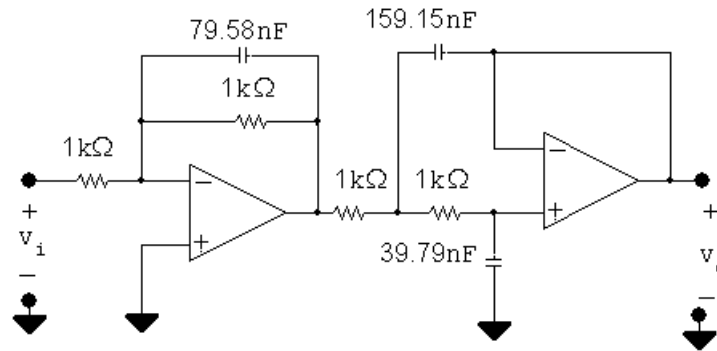[b]

P 15.32 **[a]** $n = \frac{(-0.05)(-48)}{\log_{10}(2000/500)} = 3.99 \quad \therefore n = 4$

From Table 15.1 the transfer function of the first section is

$$H_1(s) = \frac{s^2}{s^2 + 0.765s + 1}$$

For the prototype circuit

$$\frac{2}{R_2} = 0.765; \quad R_2 = 2.61 \Omega; \quad R_1 = \frac{1}{R_2} = 0.383 \Omega$$

The transfer function of the second section is

$$H_2(s) = \frac{s^2}{s^2 + 1.848s + 1}$$

For the prototype circuit

$$\frac{2}{R_2} = 1.848; \quad R_2 = 1.082 \Omega; \quad R_1 = \frac{1}{R_2} = 0.9240 \Omega$$

The scaling factors are:

$$k_f = \frac{\omega'_o}{\omega_o} = \frac{2\pi(2000)}{1} = 4000\pi$$

$$C' = \frac{C}{k_m k_f} \quad \therefore \quad 10 \times 10^{-9} = \frac{1}{4000\pi k_m}$$


$$\therefore k_m = \frac{1}{4000\pi(10 \times 10^{-9})} = 7957.75$$

Therefore in the first section

$$R'_1 = k_m R_1 = 3.04 \text{ k}\Omega; \quad R'_2 = k_m R_2 = 20.80 \text{ k}\Omega$$

In the second section


$$R'_1 = k_m R_1 = 7.35 \text{ k}\Omega; \quad R'_2 = k_m R_2 = 8.61 \text{ k}\Omega$$

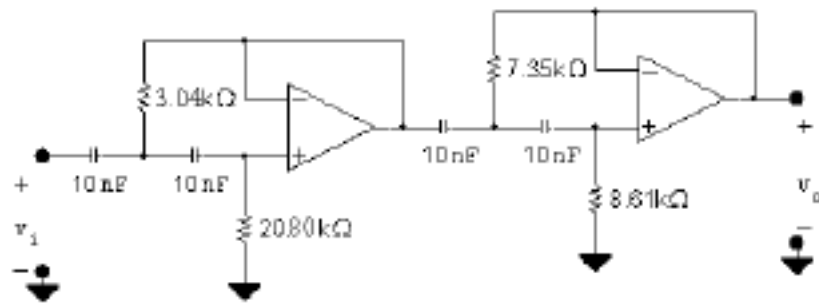[b]

P 15.33 $n = 5: 1 + (-1)^5 s^{10} = 0; \quad s^{10} = 1$

$$s^{10} = 1/0 + 36^\circ k$$

k	s_{k+1}
0	$1/0^\circ$
1	$1/36^\circ$
2	$1/72^\circ$
3	$1/108^\circ$
4	$1/144^\circ$
5	$1/180^\circ$
6	$1/216^\circ$
7	$1/252^\circ$
8	$1/288^\circ$
9	$1/324^\circ$

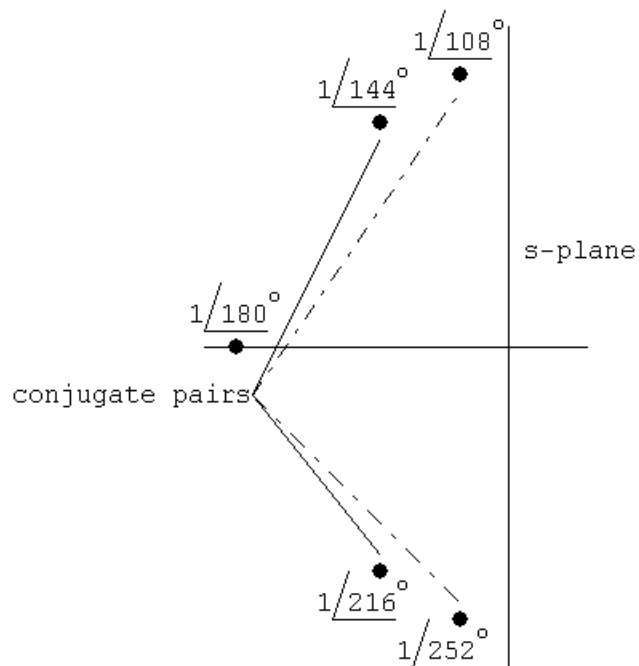

Group by conjugate pairs to form denominator polynomial.

$$(s + 1)[s - (\cos 108^\circ + j \sin 108^\circ)][s - (\cos 252^\circ + j \sin 252^\circ)]$$

$$\cdot [s - (\cos 144^\circ + j \sin 144^\circ)][s - (\cos 216^\circ + j \sin 216^\circ)]$$

$$= (s + 1)(s + 0.309 - j0.951)(s + 0.309 + j0.951) \cdot$$

$$(s + 0.809 - j0.588)(s + 0.809 + j0.588)$$

which reduces to

$$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$$

$$n = 6: 1 + (-1)^6 s^{12} = 0 \quad s^{12} = -1$$

$$s^{12} = 1/\underline{15^\circ + 36^\circ k}$$

$$k \quad s_{k+1}$$

$$0 \quad 1/\underline{15^\circ}$$

$$1 \quad 1/\underline{45^\circ}$$

$$2 \quad 1/\underline{75^\circ}$$

$$3 \quad 1/\underline{105^\circ}$$

$$4 \quad 1/\underline{135^\circ}$$

$$5 \quad 1/\underline{165^\circ}$$

$$6 \quad 1/\underline{195^\circ}$$


$$7 \quad 1/\underline{225^\circ}$$

$$8 \quad 1/\underline{255^\circ}$$

$$9 \quad 1/\underline{285^\circ}$$

$$10 \quad 1/\underline{315^\circ}$$

$$11 \quad 1/\underline{345^\circ}$$

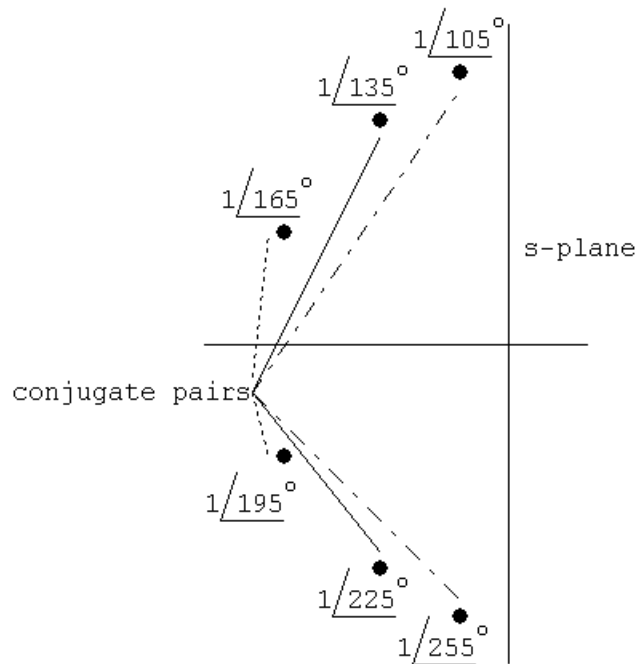

Grouping by conjugate pairs yields

$$(s + 0.2588 - j0.9659)(s + 0.2588 + j0.9659) \times$$

$$(s + 0.7071 - j0.7071)(s + 0.7071 + j0.7071) \times$$

$$(s + 0.9659 - j0.2588)(s + 0.9659 + j0.2588)$$

$$\text{or } (s^2 + 0.518s + 1)(s^2 + 1.414s + 1)(s^2 + 1.932s + 1)$$

$$\text{P 15.34 } H'(s) = \frac{s^2}{s^2 + \frac{2}{k_m R_2 (C/k_m k_f)} s + \frac{1}{k_m R_1 k_m R_2 (C^2/k_m^2 k_f^2)}}$$

$$\begin{aligned} H'(s) &= \frac{s^2}{s^2 + \frac{2k_f}{R_2 C} s + \frac{k_f^2}{R_1 R_2 C^2}} \\ &= \frac{(s/k_f)^2}{(s/k_f)^2 + \frac{2}{R_2 C} \left(\frac{s}{k_f}\right) + \frac{1}{R_1 R_2 C^2}} \end{aligned}$$

P 15.35 [a] $n = \frac{(-0.05)(-48)}{\log_{10}(32/8)} = 3.99 \quad \therefore \quad n = 4$

From Table 15.1 the transfer function is

$$H(s) = \frac{1}{(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)}$$

The capacitor values for the first stage prototype circuit are

$$\frac{2}{C_1} = 0.765 \quad \therefore \quad C_1 = 2.61 \text{ F}$$

$$C_2 = \frac{1}{C_1} = 0.38 \text{ F}$$

The values for the second stage prototype circuit are

$$\frac{2}{C_1} = 1.848 \quad \therefore \quad C_1 = 1.08 \text{ F}$$

$$C_2 = \frac{1}{C_1} = 0.92 \text{ F}$$

The scaling factors are

$$k_m = \frac{R'}{R} = 1000; \quad k_f = \frac{\omega'_o}{\omega_o} = 16,000\pi$$

Therefore the scaled values for the components in the first stage are

$$R_1 = R_2 = R = 1000 \Omega$$

$$C_1 = \frac{2.61}{(16,000\pi)(1000)} = 52.01 \text{ nF}$$


$$C_2 = \frac{0.38}{(16,000\pi)(1000)} = 7.61 \text{ nF}$$

The scaled values for the second stage are

$$R_1 = R_2 = R = 1000 \Omega$$

$$C_1 = \frac{1.08}{(16,000\pi)(1000)} = 21.53 \text{ nF}$$

$$C_2 = \frac{0.92}{(16,000\pi)(1000)} = 18.38 \text{ nF}$$

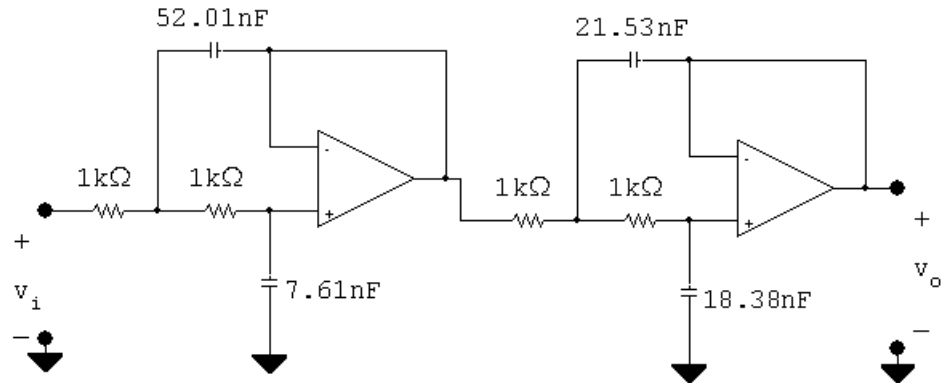[b]

P 15.36 **[a]** The cascade connection is a bandpass filter.

[b] The cutoff frequencies are 2 kHz and 8 kHz.

The center frequency is $\sqrt{(2)(8)} = 4$ kHz.

The Q is $4/(8 - 2) = 2/3 = 0.67$

[c] For the high pass section $k_f = 4000\pi$. The prototype transfer function is

$$H_{\text{hp}}(s) = \frac{s^4}{(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)}$$

$$\therefore H'_{\text{hp}}(s) = \frac{(s/4000\pi)^4}{[(s/4000\pi)^2 + 0.765(s/4000\pi) + 1]} \cdot \frac{1}{[(s/4000\pi)^2 + 1.848(s/4000\pi) + 1]}$$

$$= \frac{s^4}{(s^2 + 3060\pi s + 16 \times 10^6\pi^2)(s^2 + 7392\pi s + 16 \times 10^6\pi^2)}$$

For the low pass section $k_f = 16,000\pi$

$$H_{\text{lp}}(s) = \frac{1}{(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)}$$

$$\therefore H'_{\text{lp}}(s) = \frac{1}{[(s/16,000\pi)^2 + 0.765(s/16,000\pi) + 1]} \cdot \frac{1}{[(s/16,000\pi)^2 + 1.848(s/16,000\pi) + 1]}$$

$$= \frac{(16,000\pi)^4}{([s^2 + 12,240\pi s + (16,000\pi)^2])[s^2 + 29,568\pi s + (16,000\pi)^2]}$$

The cascaded transfer function is

$$H'(s) = H'_{\text{hp}}(s)H'_{\text{lp}}(s)$$

For convenience let

$$D_1 = s^2 + 3060\pi s + 16 \times 10^6 \pi^2$$

$$D_2 = s^2 + 7392\pi s + 16 \times 10^6 \pi^2$$

$$D_3 = s^2 + 12,240\pi s + 256 \times 10^6 \pi^2$$

$$D_4 = s^2 + 29,568\pi s + 256 \times 10^6 \pi^2$$

Then

$$H'(s) = \frac{65,536 \times 10^{12} \pi^4 s^4}{D_1 D_2 D_3 D_4}$$

[d] $\omega_o = 2\pi(4000) = 8000\pi \text{ rad/s}$

$$s = j8000\pi$$

$$s^4 = 4096 \times 10^{12} \pi^4$$

$$\begin{aligned} D_1 &= (16 \times 10^6 \pi^2 - 64 \times 10^6 \pi^2) + j(8000\pi)(3060\pi) \\ &= 10^6 \pi^2(-48 + j24.48) = 10^6 \pi^2(53.88/\underline{152.98^\circ}) \end{aligned}$$

$$\begin{aligned} D_2 &= (16 \times 10^6 \pi^2 - 64 \times 10^6 \pi^2) + j(8000\pi)(7392\pi) \\ &= 10^6 \pi^2(-48 + j59.136) = 10^6 \pi^2(76.16/\underline{129.07^\circ}) \end{aligned}$$

$$\begin{aligned} D_3 &= (256 \times 10^6 \pi^2 - 64 \times 10^6 \pi^2) + j(8000\pi)(12,240\pi) \\ &= 10^6 \pi^2(192 + j97.92) = 10^6 \pi^2(215.53/\underline{27.02^\circ}) \end{aligned}$$

$$\begin{aligned} D_4 &= (256 \times 10^6 \pi^2 - 64 \times 10^6 \pi^2) + j(8000\pi)(29,568\pi) \\ &= 10^6 \pi^2(192 + j236.544) = 10^6 \pi^2(304.66/\underline{50.93^\circ}) \end{aligned}$$

$$\begin{aligned} H'(j\omega_o) &= \frac{(65,536)(4096)\pi^8 \times 10^{24}}{(\pi^8 \times 10^{24})[(53.88)(76.16)(215.53)(304.66)/\underline{360^\circ}]} \\ &= 0.996/\underline{-360^\circ} = 0.996/\underline{0^\circ} \end{aligned}$$

P 15.37 **[a]** From the statement of the problem, $K = 10$ ($= 20 \text{ dB}$). Therefore for the prototype bandpass circuit

$$R_1 = \frac{Q}{K} = \frac{16}{10} = 1.6 \Omega$$

$$R_2 = \frac{Q}{2Q^2 - K} = \frac{16}{502} \Omega$$

$$R_3 = 2Q = 32 \Omega$$

The scaling factors are

$$k_f = \frac{\omega'_o}{\omega_o} = 2\pi(6400) = 12,800\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(20 \times 10^{-9})(12,800\pi)} = 1243.40$$


Therefore,

$$R'_1 = k_m R_1 = (1.6)(1243.40) = 1.99 \text{ k}\Omega$$

$$R'_2 = k_m R_2 = (16/502)(1243.40) = 39.63 \Omega$$

$$R'_3 = k_m R_3 = 32(1243.40) = 39.79 \text{ k}\Omega$$

[b]

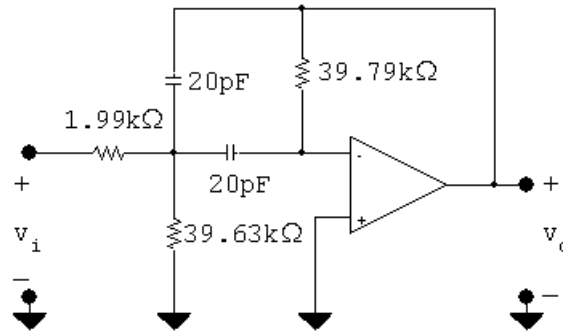

P 15.38 From Eq 15.58 we can write

$$H(s) = \frac{-\left(\frac{2}{R_3 C}\right)\left(\frac{R_3 C}{2}\right)\left(\frac{1}{R_1 C}\right)s}{s^2 + \frac{2}{R_3 C}s + \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}}$$

or

$$H(s) = \frac{-\left(\frac{R_3}{2R_1}\right)\left(\frac{2}{R_3 C}s\right)}{s^2 + \frac{2}{R_3 C}s + \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}}$$

Therefore

$$\frac{2}{R_3 C} = \beta = \frac{\omega_o}{Q}; \quad \frac{R_1 + R_2}{R_1 R_2 R_3 C^2} = \omega_o^2;$$

$$\text{and } K = \frac{R_3}{2R_1}$$

By hypothesis $C = 1 \text{ F}$ and $\omega_o = 1 \text{ rad/s}$

$$\therefore \frac{2}{R_3} = \frac{1}{Q} \text{ or } R_3 = 2Q$$

$$R_1 = \frac{R_3}{2K} = \frac{Q}{K}$$

$$\frac{R_1 + R_2}{R_1 R_2 R_3} = 1$$

$$\frac{Q}{K} + R_2 = \left(\frac{Q}{K}\right) (2Q) R_2$$

$$\therefore R_2 = \frac{Q}{2Q^2 - K}$$

P 15.39 [a] First we will design a unity gain filter and then provide the passband gain with an inverting amplifier. For the high pass section the cut-off frequency is 500 Hz. The order of the Butterworth is

$$n = \frac{(-0.05)(-20)}{\log_{10}(500/200)} = 2.51$$

$$\therefore n = 3$$

$$H_{\text{hp}}(s) = \frac{s^3}{(s+1)(s^2+s+1)}$$

For the prototype first-order section

$$R_1 = R_2 = 1 \Omega, \quad C = 1 \text{ F}$$

For the prototype second-order section

$$R_1 = 0.5 \Omega, \quad R_2 = 2 \Omega, \quad C = 1 \text{ F}$$

The scaling factors are

$$k_f = \frac{\omega'_o}{\omega_o} = 2\pi(500) = 1000\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(15 \times 10^{-9})(1000\pi)} = \frac{10^6}{15\pi}$$

In the scaled first-order section

$$R'_1 = R'_2 = k_m R_1 = \frac{10^6}{15\pi}(1) = 21.22 \text{ k}\Omega$$

$$C' = 15 \text{ nF}$$

In the scaled second-order section

$$R'_1 = 0.5k_m = 10.61 \text{ k}\Omega$$

$$R'_2 = 2k_m = 42.44 \text{ k}\Omega$$

$$C' = 15 \text{ nF}$$

For the low-pass section the cut-off frequency is 4500 Hz. The order of the Butterworth filter is

$$n = \frac{(-0.05)(-20)}{\log_{10}(11,250/4500)} = 2.51; \quad \therefore n = 3$$

$$H_{lp}(s) = \frac{1}{(s+1)(s^2+s+1)}$$

For the prototype first-order section

$$R_1 = R_2 = 1 \Omega, \quad C = 1 \text{ F}$$

For the prototype second-order section

$$R_1 = R_2 = 1 \Omega; \quad C_1 = 2 \text{ F}; \quad C_2 = 0.5 \text{ F}$$

The low-pass scaling factors are

$$k_m = \frac{R'}{R} = 10^4; \quad k_f = \frac{\omega'_o}{\omega_o} = (4500)(2\pi) = 9000\pi$$

For the scaled first-order section

$$R'_1 = R'_2 = 10 \text{ k}\Omega; \quad C' = \frac{C}{k_f k_m} = \frac{1}{(9000\pi)(10^4)} = 3.54 \text{ nF}$$

For the scaled second-order section

$$R'_1 = R'_2 = 10 \text{ k}\Omega$$


$$C'_1 = \frac{C_1}{k_f k_m} = \frac{2}{(9000\pi)(10^4)} = 7.07 \text{ nF}$$

$$C'_2 = \frac{C_2}{k_f k_m} = \frac{0.5}{(9000\pi)(10^4)} = 1.77 \text{ nF}$$

GAIN AMPLIFIER

$$20 \log_{10} K = 20 \text{ dB}, \quad \therefore K = 10$$

Since we are using 10 k Ω resistors in the low-pass stage, we will use $R_f = 100 \text{ k}\Omega$ and $R_i = 10 \text{ k}\Omega$ in the inverting amplifier stage.

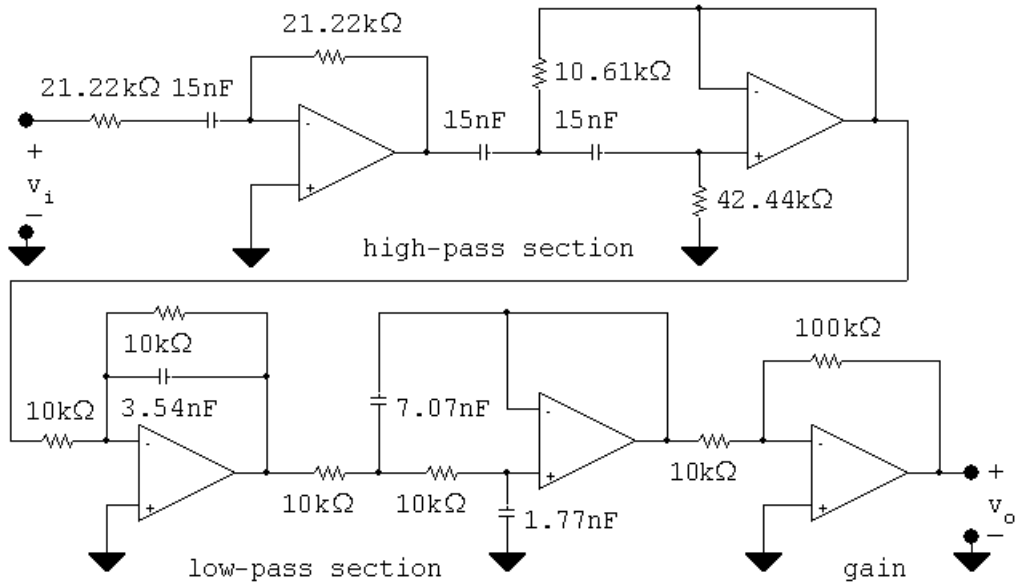[b]P 15.40 **[a]** Unscaled high-pass stage

$$H_{hp}(s) = \frac{s^3}{(s+1)(s^2+s+1)}$$

The frequency scaling factor is $k_f = (\omega'_o/\omega_o) = 1000\pi$. Therefore the scaled transfer function is

$$\begin{aligned} H'_{hp}(s) &= \frac{(s/1000\pi)^3}{\left(\frac{s}{1000\pi} + 1\right) \left[\left(\frac{s}{1000\pi}\right)^2 + \frac{s}{1000\pi} + 1\right]} \\ &= \frac{s^3}{(s+1000\pi)[s^2+1000\pi s+10^6\pi^2]} \end{aligned}$$

Unscaled low-pass stage

$$H_{lp}(s) = \frac{1}{(s+1)(s^2+s+1)}$$

The frequency scaling factor is $k_f = (\omega'_o/\omega_o) = 9000\pi$. Therefore the scaled transfer function is

$$\begin{aligned} H'_{lp}(s) &= \frac{1}{\left(\frac{s}{9000\pi} + 1\right) \left[\left(\frac{s}{9000\pi}\right)^2 + \left(\frac{s}{9000\pi}\right) + 1\right]} \\ &= \frac{1}{(s+9000\pi)(s^2+9000\pi s+81 \times 10^6\pi^2)} \end{aligned}$$

Thus the transfer function for the filter is

$$H'(s) = 10H'_{hp}(s)H'_{lp}(s) = \frac{729 \times 10^{10}\pi^3 s^3}{D_1 D_2 D_3 D_4}$$

where

$$D_1 = s + 1000\pi$$

$$D_2 = s + 9000\pi$$

$$D_3 = s^2 + 1000\pi s + 10^6\pi^2$$

$$D_4 = s^2 + 9000\pi s + 81 \times 10^6\pi^2$$

[b] At $f = 200$ Hz $\omega = 400\pi$ rad/s

$$D_1(j400\pi) = 400\pi(2.5 + j1)$$

$$D_2(j400\pi) = 400\pi(22.5 + j1)$$

$$D_3(j400\pi) = 4 \times 10^5\pi^2(2.1 + j1.0)$$

$$D_4(j400\pi) = 4 \times 10^5\pi^2(202.1 + j9)$$

Therefore

$$D_1 D_2 D_3 D_4(j400\pi) = 256\pi^6 10^{14}(28,534.82/\underline{52.36^\circ})$$

$$\begin{aligned} H'(j400\pi) &= \frac{(729\pi^3 \times 10^{10})(64 \times 10^6\pi^3)}{256\pi^6 \times 10^{14}(28,534.82/\underline{52.36^\circ})} \\ &= 0.639/\underline{-52.36^\circ} \end{aligned}$$

$$\therefore 20 \log_{10} |H'(j400\pi)| = 20 \log_{10}(0.639) = -3.89 \text{ dB}$$

At $f = 1500$ Hz, $\omega = 3000\pi$ rad/s

Then

$$D_1(j3000\pi) = 1000\pi(1 + j3)$$

$$D_2(j3000\pi) = 3000\pi(3 + j1)$$

$$D_3(j3000\pi) = 10^6\pi^2(-8 + j3)$$

$$D_4(j3000\pi) = 9 \times 10^6\pi^2(8 + j3)$$

$$\begin{aligned} H'(j3000\pi) &= \frac{(729 \times \pi^3 \times 10^{10})(27 \times 10^9\pi^3)}{27 \times 10^{18}\pi^6(730/\underline{270^\circ})} \\ &= 9.99/\underline{90^\circ} \end{aligned}$$

$$\therefore 20 \log_{10} |H'(j3000\pi)| = 19.99 \text{ dB}$$

- [c]** From the transfer function the gain is down $19.99 + 3.89$ or 23.88 dB at 200 Hz. Because the upper cut-off frequency is nine times the lower cut-off frequency we would expect the high-pass stage of the filter to predict the loss in gain at 200 Hz. For a 3rd order Butterworth

$$\text{GAIN} = 20 \log_{10} \frac{1}{\sqrt{1 + (500/200)^6}} = -23.89 \text{ dB.}$$

1500 Hz is in the passband for this bandpass filter, and is in fact the center frequency. Hence we expect the gain at 1500 Hz to equal, or nearly equal, 20 dB as specified in Problem 15.39. Thus our scaled transfer function confirms that the filter meets the specifications.

P 15.41 **[a]** From Table 15.1

$$H_{lp}(s) = \frac{1}{(s^2 + 0.518s + 1)(s^2 + \sqrt{2}s + 1)(s^2 + 1.932s + 1)}$$

$$H_{hp}(s) = \frac{1}{\left(\frac{1}{s^2} + 0.518\left(\frac{1}{s}\right) + 1\right)\left(\frac{1}{s^2} + \sqrt{2}\left(\frac{1}{s}\right) + 1\right)\left(\frac{1}{s^2} + 1.932\left(\frac{1}{s}\right) + 1\right)}$$

$$H_{hp}(s) = \frac{s^6}{(s^2 + 0.518s + 1)(s^2 + \sqrt{2}s + 1)(s^2 + 1.932s + 1)}$$

P 15.42 **[a]** $k_f = 25,000$

$$H'_{hp}(s) = \frac{(s/25,000)^6}{[(s/25,000)^2 + 0.518(s/25,000) + 1]}$$

$$\cdot \frac{1}{[(s/25,000)^2 + 1.414s/25,000 + 1][(s/25,000)^2 + 1.932s/25,000 + 1]}$$

$$= \frac{s^6}{(s^2 + 12,950s + 625 \times 10^6)(s^2 + 35,350s + 625 \times 10^6)}$$

$$\cdot \frac{1}{(s^2 + 48,300s + 625 \times 10^6)}$$

[b] $H'(j25,000) = \frac{-(25,000)^6}{[12,950(j25,000)][35,350(j25,000)][48,300(j25,000)]}$

$$= \frac{-(25,000)^3}{(12,950)(25,350)(48,300)j^3}$$

$$= 0.7067 / -90^\circ$$

$$20 \log_{10} |H'(j25,000)| = -3.02 \text{ dB}$$

P 15.43 [a] At very low frequencies the two capacitor branches are open and because the op amp is ideal the current in R_3 is zero. Therefore at low frequencies the circuit behaves as an inverting amplifier with a gain of R_2/R_1 . At very high frequencies the capacitor branches are short circuits and hence the output voltage is zero.

[b] Let the node where R_1 , R_2 , R_3 , and C_2 join be denoted as a , then

$$(V_a - V_i)G_1 + V_a sC_2 + (V_a - V_o)G_2 + V_a G_3 = 0$$

$$-V_a G_3 - V_o sC_1 = 0$$

or

$$(G_1 + G_2 + G_3 + sC_2)V_a - G_2 V_o = G_1 V_i$$

$$V_a = \frac{-sC_1}{G_3} V_o$$

Solving for V_o/V_i yields

$$\begin{aligned} H(s) &= \frac{-G_1 G_3}{(G_1 + G_2 + G_3 + sC_2)sC_1 + G_2 G_3} \\ &= \frac{-G_1 G_3}{s^2 C_1 C_2 + (G_1 + G_2 + G_3)C_1 s + G_2 G_3} \\ &= \frac{-G_1 G_3 / C_1 C_2}{s^2 + \left[\frac{(G_1 + G_2 + G_3)}{C_2} \right] s + \frac{G_2 G_3}{C_1 C_2}} \\ &= \frac{-\frac{G_1 G_2 G_3}{G_2 C_1 C_2}}{s^2 + \left[\frac{(G_1 + G_2 + G_3)}{C_2} \right] s + \frac{G_2 G_3}{C_1 C_2}} \\ &= \frac{-K b_o}{s^2 + b_1 s + b_o} \end{aligned}$$

$$\text{where } K = \frac{G_1}{G_2}; \quad b_o = \frac{G_2 G_3}{C_1 C_2}$$

$$\text{and } b_1 = \frac{G_1 + G_2 + G_3}{C_2}$$

[c] Equating coefficients we see that

$$G_1 = K G_2$$

$$G_3 = \frac{b_o C_1 C_2}{G_2} = \frac{b_o C_1}{G_2}$$

since by hypothesis $C_2 = 1 \text{ F}$

$$b_1 = \frac{G_1 + G_2 + G_3}{C_2} = G_1 + G_2 + G_3$$

$$\therefore b_1 = KG_2 + G_2 + \frac{b_o C_1}{G_2}$$

$$b_1 = G_2(1 + K) + \frac{b_o C_1}{G_2}$$

Solving this quadratic equation for G_2 we get

$$\begin{aligned} G_2 &= \frac{b_1}{2(1 + K)} \pm \sqrt{\frac{b_1^2 - b_o C_1 4(1 + K)}{4(1 + K)^2}} \\ &= \frac{b_1 \pm \sqrt{b_1^2 - 4b_o(1 + K)C_1}}{2(1 + K)} \end{aligned}$$

For G_2 to be realizable

$$C_1 < \frac{b_1^2}{4b_o(1 + K)}$$

[d] 1. Select $C_2 = 1 \text{ F}$

2. Select C_1 such that $C_1 < \frac{b_1^2}{4b_o(1 + K)}$

3. Calculate G_2 (R_2)

4. Calculate G_1 (R_1); $G_1 = KG_2$

5. Calculate G_3 (R_3); $G_3 = b_o C_1 / G_2$

P 15.44 **[a]** In the second order section of a third order Butterworth filter $b_o = b_1 = 1$
Therefore,

$$C_1 \leq \frac{b_1^2}{4b_o(1 + K)} = \frac{1}{(4)(1)(5)} = 0.05 \text{ F}$$

$$\therefore C_1 = 0.05 \text{ F} \quad (\text{limiting value})$$

$$\textbf{[b]} \quad G_2 = \frac{1}{2(1 + 4)} = 0.1 \text{ S}$$

$$G_3 = \frac{1}{0.1}(0.05) = 0.5 \text{ S}$$

$$G_1 = 4(0.1) = 0.4 \text{ S}$$

Therefore,

$$R_1 = \frac{1}{G_1} = 2.5 \Omega; \quad R_2 = \frac{1}{G_2} = 10 \Omega; \quad R_3 = \frac{1}{G_3} = 2 \Omega$$

$$[c] \quad k_f = \frac{\omega'_o}{\omega_o} = 2\pi(2500) = 5000\pi$$

$$k_m = \frac{C_2}{C'_2 k_f} = \frac{1}{(10 \times 10^{-9})k_f} = 6366.2$$

$$C'_1 = \frac{0.05}{k_f k_m} = 0.5 \times 10^{-9} = 500 \text{ pF}$$

$$R'_1 = (2.5)(6366.2) = 15.92 \text{ k}\Omega$$


$$R'_2 = (10)(6366.2) = 63.66 \text{ k}\Omega$$

$$R'_3 = (2)(6366.2) = 12.73 \text{ k}\Omega$$


$$[d] \quad R'_1 = R'_2 = (6366.2)(1) = 6.37 \text{ k}\Omega$$

$$C' = \frac{C}{k_f k_m} = \frac{1}{10^8} = 10 \text{ nF}$$

[e]

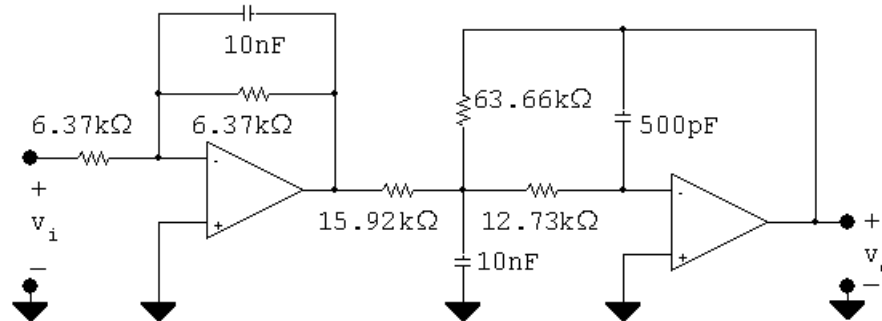

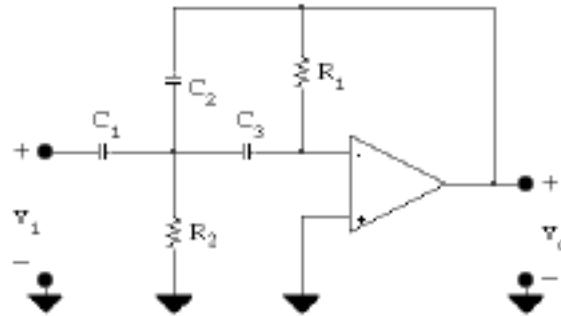P 15.45 [a] By hypothesis the circuit becomes:



For very small frequencies the capacitors behave as open circuits and therefore v_o is zero. As the frequency increases, the capacitive branch impedances become small compared to the resistive branches. When this happens the circuit becomes an inverting amplifier with the capacitor C_2 dominating the feedback path. Hence the gain of the amplifier approaches $(1/j\omega C_2)/(1/j\omega C_1)$ or C_1/C_2 . Therefore the circuit behaves like a high-pass filter with a passband gain of C_1/C_2 .

[b] Summing the currents away from the upper terminal of R_2 yields

$$V_a G_2 + (V_a - V_i) s C_1 + (V_a - V_o) s C_2 + V_a s C_3 = 0$$

or

$$V_a [G_2 + s(C_1 + C_2 + C_3)] - V_o s C_2 = s C_1 V_i$$

Summing the currents away from the inverting input terminal gives

$$(0 - V_a) s C_3 + (0 - V_o) G_1 = 0$$

or

$$s C_3 V_a = -G_1 V_o; \quad V_a = \frac{-G_1 V_o}{s C_3}$$

Therefore we can write

$$\frac{-G_1 V_o}{s C_3} [G_2 + s(C_1 + C_2 + C_3)] - s C_2 V_o = s C_1 V_i$$

Solving for V_o/V_i gives

$$\begin{aligned} H(s) = \frac{V_o}{V_i} &= \frac{-C_1 C_3 s^2}{[C_2 C_3 s^2 + G_1 (C_1 + C_2 + C_3) s + G_1 G_2]} \\ &= \frac{\frac{-C_1}{C_2} s^2}{\left[s^2 + \frac{G_1}{C_2 C_3} (C_1 + C_2 + C_3) s + \frac{G_1 G_2}{C_2 C_3} \right]} \\ &= \frac{-K s^2}{s^2 + b_1 s + b_o} \end{aligned}$$

Therefore the circuit implements a second-order high-pass filter with a passband gain of C_1/C_2 .

[c] $C_1 = K$:

$$b_1 = \frac{G_1}{(1)(1)} (K + 2) = G_1 (K + 2)$$

$$\therefore G_1 = \frac{b_1}{K + 2}; \quad R_1 = \left(\frac{K + 2}{b_1} \right)$$

$$b_o = \frac{G_1 G_2}{(1)(1)} = G_1 G_2$$

$$\therefore G_2 = \frac{b_o}{G_1} = \frac{b_o}{b_1} (K + 2)$$

$$\therefore R_2 = \frac{b_1}{b_o (K + 2)}$$

[d] From Table 15.1 the transfer function of the second-order section of a third-order high-pass Butterworth filter is

$$H(s) = \frac{Ks^2}{s^2 + s + 1}$$

Therefore $b_1 = b_o = 1$

Thus

$$C_1 = K = 8 \text{ F}$$

$$R_1 = \frac{8+2}{1} = 10 \Omega$$

$$R_2 = \frac{1}{1(8+2)} = 0.10 \Omega$$

P 15.46 [a] Low-pass filter:

$$n = \frac{(-0.05)(-30)}{\log_{10}(1000/400)} = 3.77; \quad \therefore n = 4$$

In the first prototype second-order section: $b_1 = 0.765$, $b_o = 1$, $C_2 = 1 \text{ F}$

$$C_1 \leq \frac{b_1^2}{4b_o(1+K)} \leq \frac{(0.765)^2}{(4)(2)} \leq 0.0732$$

choose $C_1 = 0.03 \text{ F}$

$$G_2 = \frac{0.765 \pm \sqrt{(0.765)^2 - 4(2)(0.03)}}{4} = \frac{0.765 \pm 0.588}{4}$$

Arbitrarily select the larger value for G_2 , then

$$G_2 = 0.338 \text{ S}; \quad \therefore R_2 = \frac{1}{G_2} = 2.96 \Omega$$

$$G_1 = KG_2 = 0.338 \text{ S}; \quad \therefore R_1 = \frac{1}{G_1} = 2.96 \Omega$$

$$G_3 = \frac{b_o C_1}{G_2} = \frac{(1)(0.03)}{0.338} = 0.089 \quad \therefore R_3 = 1/G_3 = 11.3 \Omega$$

Therefore in the first second-order prototype circuit

$$R_1 = R_2 = 2.96 \Omega; \quad R_3 = 11.3 \Omega$$

$$C_1 = 0.03 \text{ F}; \quad C_2 = 1 \text{ F}$$

In the second second-order prototype circuit: $b_1 = 1.848$, $b_o = 1$, $C_2 = 1 \text{ F}$

$$\therefore C_1 \leq \frac{(1.848)^2}{8} \leq 0.427$$

choose $C_1 = 0.30 \text{ F}$

$$G_2 = \frac{1.848 \pm \sqrt{(1.848)^2 - 8(0.3)}}{4} = \frac{1.848 \pm 1.008}{4}$$

Arbitrarily select the larger value, then

$$G_2 = 0.7139 \text{ S}; \quad \therefore \quad R_2 = \frac{1}{G_2} = 1.4008 \Omega$$

$$G_1 = KG_2 = 0.7139 \text{ S}; \quad \therefore \quad R_1 = \frac{1}{G_1} = 1.4008 \Omega$$

$$G_3 = \frac{b_o C_1}{G_2} = \frac{(1)(0.30)}{0.7139} = 0.4202 \text{ S} \quad \therefore \quad R_3 = 1/G_3 = 2.3796 \Omega$$

In the low-pass section of the filter

$$k_f = \frac{\omega'_o}{\omega_o} = 2\pi(400) = 800\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(10 \times 10^{-9})k_f} = \frac{125,000}{\pi}$$

Therefore in the first scaled second-order section

$$R'_1 = R'_2 = 2.96k_m = 118 \text{ k}\Omega$$

$$R'_3 = 11.3k_m = 450 \text{ k}\Omega$$

$$C'_1 = \frac{0.03}{k_f k_m} = 300 \text{ pF}$$

$$C'_2 = 10 \text{ nF}$$

In the second scaled second-order section

$$R'_1 = R'_2 = 1.4008k_m = 55.74 \text{ k}\Omega$$

$$R'_3 = 2.3796k_m = 94.68 \text{ k}\Omega$$

$$C'_1 = \frac{0.3}{k_f k_m} = 3 \text{ nF}$$

$$C'_2 = 10 \text{ nF}$$

High-pass filter section

$$n = \frac{(-0.05)(-30)}{\log_{10}(6400/2560)} = 3.77; \quad n = 4.$$

In the first prototype second-order section: $b_1 = 0.765$; $b_o = 1$; $C_2 = C_3 = 1 \text{ F}$

$$C_1 = K = 1 \text{ F}$$

$$R_1 = \frac{K + 2}{b_1} = \frac{3}{0.765} = 3.92 \Omega$$

$$R_2 = \frac{b_1}{b_o(K + 2)} = \frac{0.765}{3} = 0.255 \Omega$$

In the second prototype second-order section: $b_1 = 1.848$; $b_o = 1$;
 $C_2 = C_3 = 1 \text{ F}$

$$C_1 = K = 1 \text{ F}$$

$$R_1 = \frac{K + 2}{b_1} = \frac{3}{1.848} = 1.623 \Omega$$

$$R_2 = \frac{b_1}{b_o(K + 2)} = \frac{1.848}{3} = 0.616 \Omega$$

In the high-pass section of the filter

$$k_f = \frac{\omega'_o}{\omega_o} = 2\pi(6400) = 12,800\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(10 \times 10^{-9})(12,800\pi)} = \frac{7812.5}{\pi}$$

In the first scaled second-order section

$$R'_1 = 3.92k_m = 9.75 \text{ k}\Omega$$

$$R'_2 = 0.255k_m = 634 \Omega$$

$$C'_1 = C'_2 = C'_3 = 10 \text{ nF}$$

In the second scaled second-order section

$$R'_1 = 1.623k_m = 4.04 \text{ k}\Omega$$

$$R'_2 = 0.616k_m = 1.53 \text{ k}\Omega$$

$$C'_1 = C'_2 = C'_3 = 10 \text{ nF}$$

In the gain section, let $R_i = 10 \text{ k}\Omega$ and $R_f = 10 \text{ k}\Omega$.

The scaled transfer function for the high-pass filter is

$$\begin{aligned} H'_{hp}(s) &= \frac{(s/12,800\pi)^4}{\left[\left(\frac{s}{12,800\pi}\right)^2 + \frac{0.765s}{12,800\pi} + 1\right] \left[\left(\frac{s}{12,800\pi}\right)^2 + \frac{1.848s}{12,800\pi} + 1\right]} \\ &= \frac{s^4}{[s^2 + 9792\pi s + (12,800\pi)^2][s^2 + 23,654.4\pi s + (12,800\pi)^2]} \end{aligned}$$

The transfer function for the filter is

$$H'(s) = [H'_{lp}(s) + H'_{hp}(s)]$$

[b] $f_o = \sqrt{f_{c1}f_{c2}} = \sqrt{(400)(6400)} = 1600 \text{ Hz}$

$$\omega_o = 2\pi f_o = 3200\pi \text{ rad/s}$$

$$(j\omega_o)^2 = -1024 \times 10^4 \pi^2$$

$$(j\omega_o)^4 = 1,048,576 \times 10^8 \pi^4$$

$$\begin{aligned} H'_{lp}(j\omega_o) &= \frac{4096 \times 10^8 \pi^4}{[-960 \times 10^4 \pi^2 + j612(3200\pi^2)]} \times \\ &\quad \frac{1}{[-960 \times 10^4 \pi^2 + j1478.4(3200\pi^2)]} \\ &= \frac{40,000}{(-3000 + j612)(-3000 + j1478.4)} \\ &= 3906.2 \times 10^{-6} / 37.76^\circ \\ H'_{hp}(j\omega_o) &= \frac{1,048,576 \times 10^8 \pi^4}{[15,360 \times 10^4 \pi^2 + j9792(3200\pi^2)]} \\ &\quad \frac{1}{[15,360 \times 10^4 \pi^2 + j23,654.4(3200\pi^2)]} \\ &= \frac{10.24 \times 10^6}{(48,000 + j9792)(48,000 + j23,654.4)} \\ &= 3906.2 \times 10^{-6} / -37.76^\circ \end{aligned}$$

$$\therefore H'(j\omega_o) = -3906.2 \times 10^{-6} (1/37.76^\circ + 1/-37.76^\circ)$$

$$= -3906.2 \times 10^{-6} (1.58/0^\circ) = -6176.35 \times 10^{-6} / 0^\circ$$

$$G = 20 \log_{10} |H'(j\omega_o)| = 20 \log_{10} (6176.35 \times 10^{-6}) = -44.19 \text{ dB}$$

P 15.48 [a] At low frequencies the capacitor branches are open; $v_o = v_i$. At high frequencies the capacitor branches are short circuits and the output voltage is zero. Hence the circuit behaves like a unity-gain low-pass filter.

- [b]** Let v_a represent the voltage-to-ground at the right-hand terminal of R_1 . Observe this will also be the voltage at the left-hand terminal of R_2 . The s -domain equations are

$$(V_a - V_i)G_1 + (V_a - V_o)sC_1 = 0$$

$$(V_o - V_a)G_2 + sC_2V_o = 0$$

or

$$(G_1 + sC_1)V_a - sC_1V_o = G_1V_i$$

$$-G_2V_a + (G_2 + sC_2)V_o = 0$$

$$\therefore V_a = \frac{G_2 + sC_2V_o}{G_2}$$

$$\therefore \left[(G_1 + sC_1) \frac{(G_2 + sC_2)}{G_2} - sC_1 \right] V_o = G_1V_i$$

$$\therefore \frac{V_o}{V_i} = \frac{G_1G_2}{(G_1 + sC_1)(G_2 + sC_2) - C_1G_2s}$$

which reduces to

$$\frac{V_o}{V_i} = \frac{G_1G_2/C_1C_2}{s^2 + \frac{G_1}{C_1}s + \frac{G_1G_2}{C_1C_2}} = \frac{b_o}{s^2 + b_1s + b_o}$$

- [c]** There are four circuit components and two restraints imposed by $H(s)$; therefore there are two free choices.

[d] $b_1 = \frac{G_1}{C_1} \therefore G_1 = b_1C_1$

$$b_o = \frac{G_1G_2}{C_1C_2} \therefore G_2 = \frac{b_o}{b_1}C_2$$

- [e]** No, all physically realizeable capacitors will yield physically realizeable resistors.

- [f]** From Table 15.1 we know the transfer function of the prototype 4th order Butterworth filter is

$$H(s) = \frac{1}{(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)}$$

$$\text{In the first section } b_o = 1, \quad b_1 = 0.765$$

$$\therefore G_1 = (0.765)(1) = 0.765 \text{ S}$$

$$R_1 = 1/G_1 = 1.307 \Omega$$

$$G_2 = \frac{1}{0.765}(1) = 1.307 \text{ S}$$

$$R_2 = 1/G_2 = 0.765 \Omega$$


In the second section $b_o = 1$, $b_1 = 1.848$

$$\therefore G_1 = 1.848 \text{ S}$$

$$R_1 = 1/G_1 = 0.541 \Omega$$

$$G_2 = \left(\frac{1}{1.848} \right) (1) = 0.541 \text{ S}$$

$$R_2 = 1/G_2 = 1.848 \Omega$$

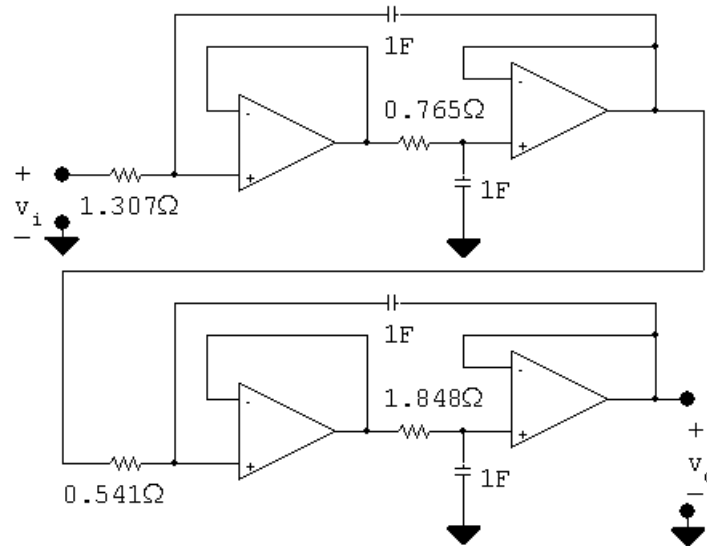

P 15.49 [a] $k_f = \frac{\omega'_o}{\omega_o} = 2\pi(3000) = 6000\pi$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(4.7 \times 10^{-9})(6000\pi)} = \frac{10^6}{28.2\pi}$$

In the first section


$$R'_1 = 1.307k_m = 14.75 \text{ k}\Omega$$

$$R'_2 = 0.765k_m = 8.64 \text{ k}\Omega$$


In the second section

$$R'_1 = 0.541k_m = 6.11 \text{ k}\Omega$$

$$R'_2 = 1.848k_m = 20.86 \text{ k}\Omega$$

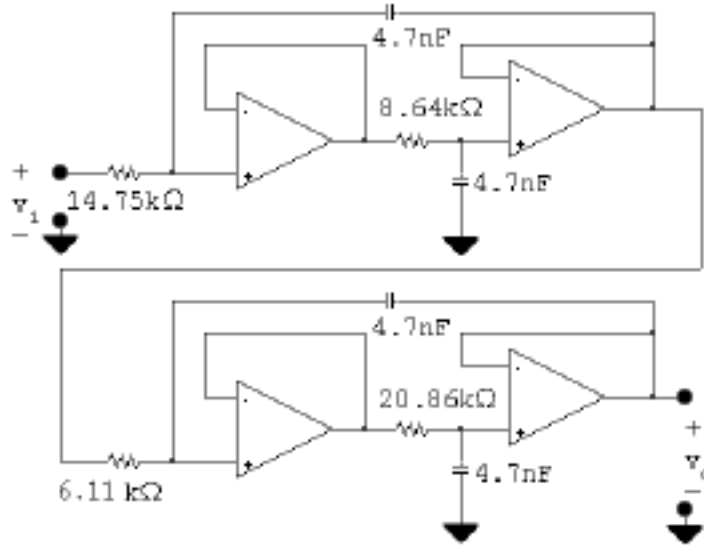[b]

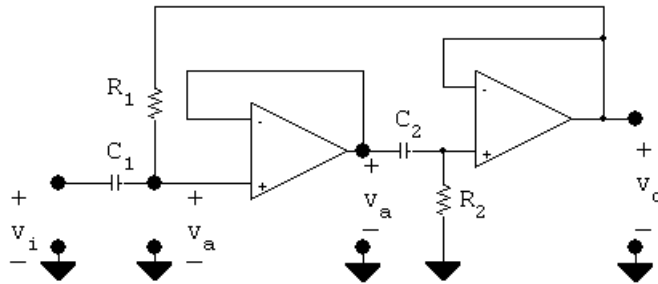P 15.50 **[a]** Interchanging the R s and C 's yields the following circuit.



At low frequencies the capacitors appear as open circuits and hence the output voltage is zero. As the frequency increases the capacitor branches approach short circuits and $v_a = v_i = v_o$. Thus the circuit is a unity-gain, high-pass filter.

[b] The s -domain equations are

$$(V_a - V_i)sC_1 + (V_a - V_o)G_1 = 0$$

$$(V_o - V_a)sC_2 + V_oG_2 = 0$$

It follows that

$$V_a(G_1 + sC_1) - G_1V_o = sC_1V_i$$

$$\text{and } V_a = \frac{(G_2 + sC_2)V_o}{sC_2}$$

Thus

$$\left\{ \left[\frac{(G_2 + sC_2)}{sC_2} \right] (G_1 + sC_1) - G_1 \right\} V_o = sC_1V_i$$

$$V_o\{s^2C_1C_2 + sC_1G_2 + G_1G_2\} = s^2C_1C_2V_i$$

$$\begin{aligned}
 H(s) &= \frac{V_o}{V_i} = \frac{s^2}{\left(s^2 + \frac{G_2}{C_2}s + \frac{G_1G_2}{C_1C_2}\right)} \\
 &= \frac{V_o}{V_i} = \frac{s^2}{s^2 + b_1s + b_o}
 \end{aligned}$$

- [c]** There are 4 circuit components: R_1 , R_2 , C_1 and C_2 .
 There are two transfer function constraints: b_1 and b_o .
 Therefore there are two free choices.

[d] $b_o = \frac{G_1G_2}{C_1C_2}; \quad b_1 = \frac{G_2}{C_2}$

$$\therefore G_2 = b_1C_2; \quad R_2 = \frac{1}{b_1C_2}$$

$$G_1 = \frac{b_o}{b_1}C_1 \therefore R_1 = \frac{b_1}{b_oC_1}$$

- [e]** No, all realizeable capacitors will produce realizeable resistors.

- [f]** The second-order section in a 3rd-order Butterworth high-pass filter is $s^2/(s^2 + s + 1)$. Therefore $b_o = b_1 = 1$ and

$$R_1 = \frac{1}{(1)(1)} = 1 \Omega.$$


$$R_2 = \frac{1}{(1)(1)} = 1 \Omega.$$

P 15.51 **[a]** $k_f = \frac{\omega'_o}{\omega_o} = 10^4\pi$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(75 \times 10^{-9})(10^4\pi)} = \frac{10^5}{75\pi}$$

$$C_1 = C_2 = 75 \text{ nF}; \quad R'_1 = R'_2 = k_m R = 424.4 \Omega$$

[b] $R = 424.4 \Omega; \quad C = 75 \text{ nF}$

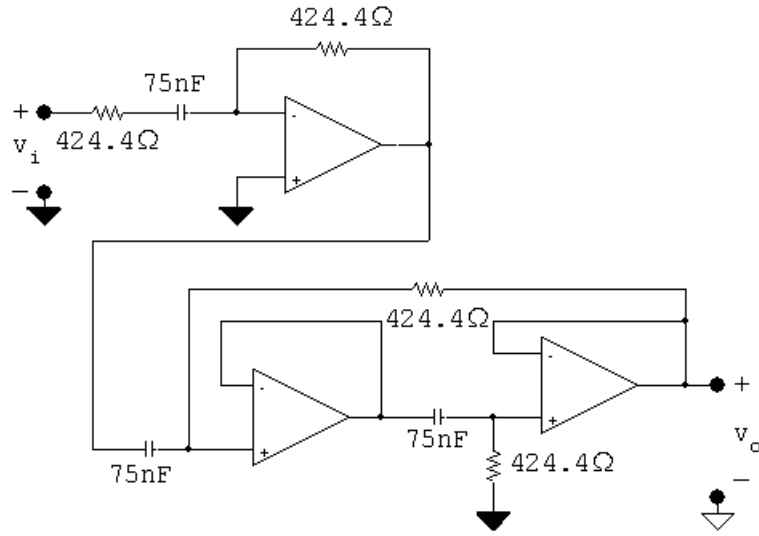[c]

$$\text{[d]} \quad H_{\text{hp}}(s) = \frac{s^3}{(s+1)(s^2+s+1)}$$

$$H'_{\text{hp}}(s) = \frac{(s/10^4\pi)^3}{[(s/10^4\pi) + 1][(s/10^4\pi)^2 + (s/10^4\pi) + 1]}$$

$$= \frac{s^3}{(s + 10^4\pi)(s^2 + 10^4\pi s + 10^8\pi^2)}$$

$$\text{[e]} \quad H'_{\text{hp}}(j10^4\pi) = \frac{(j10^4\pi)^3}{(j10^4\pi + 10^4\pi)[(j10^4\pi)^2 + 10^4\pi(j10^4\pi) + 10^8\pi^2]} = 0.7071 \angle 135^\circ$$

$$\therefore |H'_{\text{hp}}| = 0.7071 = -3 \text{ dB}$$

P 15.52 **[a]** It follows directly from Eq 15.64 that

$$H(s) = \frac{s^2 + 1}{s^2 + 4(1 - \sigma)s + 1}$$

Now note from Eq 15.69 that $(1 - \sigma)$ equals $1/4Q$, hence

$$H(s) = \frac{s^2 + 1}{s^2 + \frac{1}{Q}s + 1}$$

[b] For Example 15.13, $\omega_o = 5000 \text{ rad/s}$ and $Q = 5$. Therefore $k_f = 5000$ and

$$H'(s) = \frac{(s/5000)^2 + 1}{(s/5000)^2 + \frac{1}{5} \left(\frac{s}{5000} \right) + 1}$$

$$= \frac{s^2 + 25 \times 10^6}{s^2 + 1000s + 25 \times 10^6}$$

P 15.53 **[a]** $\omega_o = 2000\pi \text{ rad/s}$

$$\therefore k_f = \frac{\omega'_o}{\omega_o} = 2000\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(15 \times 10^{-9})(2000\pi)} = \frac{10^5}{3\pi}$$

$$R' = k_m R = \frac{10^5}{3\pi}(1) = 10,610 \Omega$$

$$\frac{R'}{2} = 5,305 \Omega$$


$$\sigma = 1 - \frac{1}{4Q} = 1 - \frac{1}{4(20)} = 0.9875$$

$$\sigma R' = 10,478 \Omega; \quad (1 - \sigma)R' = 133 \Omega$$

$$C' = 15 \text{ nF}$$

$$2C' = 30 \text{ nF}$$

[b]

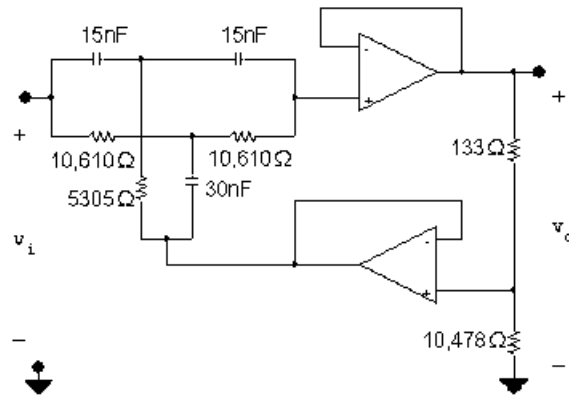

[c] $k_f = 2000\pi$

$$\begin{aligned} H(s) &= \frac{(s/2000\pi)^2 + 1}{(s/2000\pi)^2 + \frac{1}{20}(s/2000\pi) + 1} \\ &= \frac{s^2 + 4 \times 10^6 \pi^2}{s^2 + 100\pi s + 4 \times 10^6 \pi^2} \end{aligned}$$

P 15.54 To satisfy the gain specification of 20 dB at $\omega = 0$ and $\alpha = 1$ requires

$$\frac{R_1 + R_2}{R_1} = 10 \quad \text{or} \quad R_2 = 9R_1$$

Choose a standard resistor of 11.1 k Ω for R_1 and a 100 k Ω potentiometer for R_2 . Since $(R_1 + R_2)/R_1 \gg 1$ the value of C_1 is

$$C_1 = \frac{1}{2\pi(40)(10^5)} = 39.79 \text{ nF}$$

Choose a standard capacitor value of 39 nF. Using the selected values of R_1 and R_2 the maximum gain for $\alpha = 1$ is

$$20 \log_{10} \left(\frac{111.1}{11.1} \right)_{\alpha=1} = 20.01 \text{ dB}$$

When $C_1 = 39 \text{ nF}$ the frequency $1/R_2 C_1$ is

$$\frac{1}{R_2 C_1} = \frac{10^9}{10^5(39)} = 256.41 \text{ rad/s} = 40.81 \text{ Hz}$$

The magnitude of the transfer function at 256.41 rad/s is

$$|H(j256.41)|_{\alpha=1} = \frac{|111.1 \times 10^3 + j256.41(11.1)(100)(39)10^{-3}|}{|11.1 \times 10^3 + j256.41(11.1)(100)(39)10^{-3}|} = 7.11$$

Therefore the gain at 40.81 Hz is

$$20 \log_{10}(7.11)_{\alpha=1} = 17.04 \text{ dB}$$


P 15.55 $20 \log_{10} \left(\frac{R_1 + R_2}{R_1} \right) = 13.98$

$$\therefore \frac{R_1 + R_2}{R_1} = 5; \quad \therefore R_2 = 4R_1$$

Choose $R_1 = 100 \text{ k}\Omega$. Then $R_2 = 400 \text{ k}\Omega$

$$\frac{1}{R_2 C_1} = 100\pi \text{ rad/s}; \quad \therefore C_1 = \frac{1}{(100\pi)(400 \times 10^3)} = 7.96 \text{ nF}$$

P 15.56 [a] 

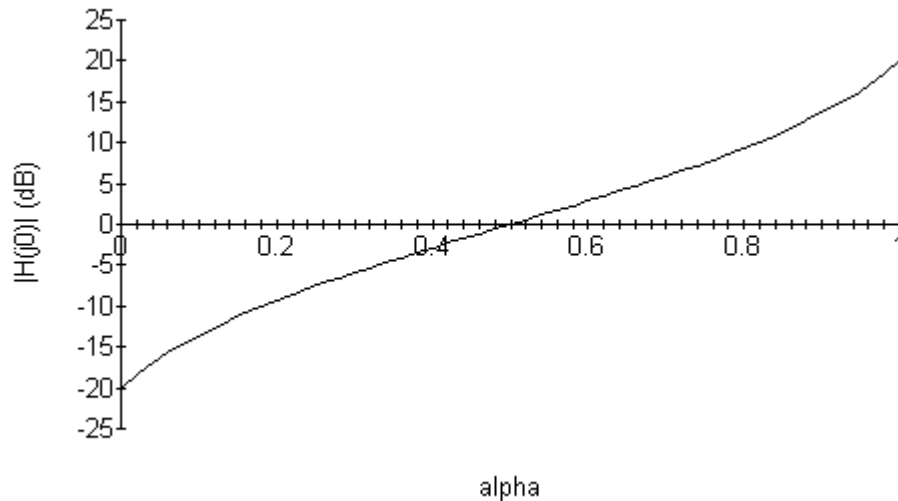


P 15.57 [a] Combine the impedances of the capacitors in series in Fig. P15.53(b) to get

$$C_{\text{eq}} = \frac{1-\alpha}{sC_1} + \frac{\alpha}{sC_1} = \frac{1}{sC_1}$$

which is identical to the impedance of the capacitor in Fig. P15.53(a).

[b]

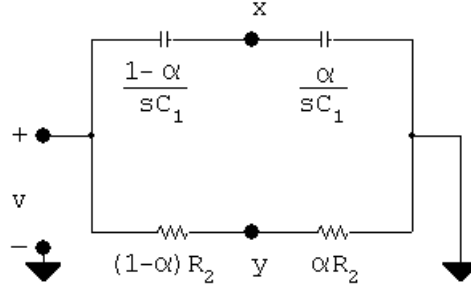

$$V_x = \frac{\alpha/sC_1}{(1-\alpha)/sC_1 + \alpha/sC_1} V = \alpha$$

$$V_y = \frac{\alpha R_2}{(1-\alpha)R_2 + \alpha R_2} = \alpha = V_x$$

[c] Since x and y are both at the same potential, they can be shorted together, and the circuit in Fig. 15.34 can thus be drawn as shown in Fig. 15.53(c).

[d] The feedback path between V_o and V_s containing the resistance $R_4 + 2R_3$ has no effect on the ratio V_o/V_s , as this feedback path is not involved in the nodal equation that defines the voltage ratio. Thus, the circuit in Fig. 15.53(c) can be simplified into the form of Fig. 15.2, where the input impedance is the equivalent impedance of R_1 in series with the parallel combination of $(1-\alpha)/sC_1$ and $(1-\alpha)R_2$, and the feedback impedance is the equivalent impedance of R_1 in series with the parallel combination of α/sC_1 and αR_2 :

$$\begin{aligned} Z_i &= R_1 + \frac{\frac{(1-\alpha)}{sC_1} \cdot (1-\alpha)R_2}{(1-\alpha)R_2 + \frac{(1-\alpha)}{sC_1}} \\ &= \frac{R_1 + (1-\alpha)R_2 + R_1 R_2 C_1 s}{1 + R_2 C_1 s} \end{aligned}$$

$$\begin{aligned} Z_f &= R_1 + \frac{\frac{\alpha}{sC_1} \cdot \alpha R_2}{\alpha R_2 + \frac{\alpha}{sC_1}} \\ &= \frac{R_1 + \alpha R_2 + R_1 R_2 C_1 s}{1 + R_2 C_1 s} \end{aligned}$$

P 15.58 As $\omega \rightarrow 0$

$$|H(i\omega)| \rightarrow \frac{2R_3 + R_4}{2R_3 + R_4} = 1$$

Therefore the circuit would have no effect on low frequency signals. As $\omega \rightarrow \infty$

$$|H(j\omega)| \rightarrow \frac{[(1 - \beta)R_4 + R_o](\beta R_4 + R_3)}{[(1 - \beta)R_4 + R_3](\beta R_4 + R_o)}$$

When $\beta = 1$

$$|H(j\infty)|_{\beta=1} = \frac{R_o(R_4 + R_3)}{R_3(R_4 + R_o)}$$

If $R_4 \gg R_o$

$$|H(j\infty)|_{\beta=1} \cong \frac{R_o}{R_3} > 1$$

Thus, when $\beta = 1$ we have amplification or “boost”. When $\beta = 0$

$$|H(j\infty)|_{\beta=0} = \frac{R_3(R_4 + R_3)}{R_o(R_4 + R_o)}$$

If $R_4 \gg R_o$

$$|H(j\infty)|_{\beta=0} \cong \frac{R_3}{R_o} < 1$$

Thus, when $\beta = 0$ we have attenuation or “cut”.

Also note that when $\beta = 0.5$

$$|H(j\omega)|_{\beta=0.5} = \frac{(0.5R_4 + R_o)(0.5R_4 + R_3)}{(0.5R_4 + R_3)(0.5R_4 + R_o)} = 1$$

Thus, the transition from amplification to attenuation occurs at $\beta = 0.5$. If $\beta > 0.5$ we have amplification, and if $\beta < 0.5$ we have attenuation.

Also note the amplification and attenuation are symmetric about $\beta = 0.5$. i.e.

$$|H(j\omega)|_{\beta=0.6} = \frac{1}{|H(j\omega)|_{\beta=0.4}}$$

Yes, the circuit can be used as a treble volume control because

- The circuit has no effect on low frequency signals
- Depending on β the circuit can either amplify ($\beta > 0.5$) or attenuate ($\beta < 0.5$) signals in the treble range
- The amplification (boost) and attenuation (cut) are symmetric around $\beta = 0.5$. When $\beta = 0.5$ the circuit has no effect on signals in the treble frequency range.

P 15.59 [a] $|H(j\infty)|_{\beta=1} = \frac{R_o(R_4 + R_3)}{R_3(R_4 + R_o)} = \frac{(65.9)(505.9)}{(5.9)(565.9)} = 9.99$

\therefore maximum boost $= 20 \log_{10} 9.99 = 19.99$ dB

[b] $|H(j\infty)|_{\beta=0} = \frac{R_3(R_4 + R_3)}{R_o(R_4 + R_o)}$

\therefore maximum cut $= -21.93$ dB

[c] $R_4 = 500 \text{ k}\Omega$; $R_o = R_1 + R_3 + 2R_5 = 65.9 \text{ k}\Omega$

$\therefore R_4 = 7.59 R_o$

Yes, R_4 is significantly greater than R_o .

[d] $|H(j/R_3 C_2)|_{\beta=1} = \left| \frac{(2R_3 + R_4) + j\frac{R_o}{R_3}(R_4 + R_3)}{(2R_3 + R_4) + j(R_4 + R_o)} \right|$

$$= \left| \frac{511.8 + j\frac{65.9}{5.9}(505.9)}{511.8 + j565.9} \right|$$

$$= 7.44$$

$20 \log_{10} |H(j/R_3 C_2)|_{\beta=1} = 20 \log_{10} 7.44 = 17.43$ dB

[e] When $\beta = 0$

$$|H(j/R_3 C_2)|_{\beta=0} = \frac{(2R_3 + R_4) + j(R_4 + R_o)}{(2R_3 + R_4) + j\frac{R_o}{R_3}(R_4 + R_3)}$$

Note this is the reciprocal of $|H(j/R_3 C_2)|_{\beta=1}$.

$\therefore 20 \log_{10} |H(j/R_3 C_2)|_{\beta=0} = -17.43$ dB

[f] The frequency $1/R_3 C_2$ is very nearly where the gain is 3 dB off from its maximum boost or cut. Therefore for frequencies higher than $1/R_3 C_2$ the circuit designer knows that gain or cut will be within 3 dB of the maximum.

$$\text{P 15.60} \quad |H(j\infty)| = \frac{[(1 - \beta)R_4 + R_o][\beta R_4 + R_3]}{[1 - \beta R_4 + R_3][\beta R_4 + R_o]}$$

