

55. (a) At $t = 0$ the capacitor is completely uncharged and the current in the capacitor branch is as it would be if the capacitor were replaced by a wire. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is downward. Let i_3 be the current in R_3 and take it to be positive if it is downward. The junction rule produces

$$i_1 = i_2 + i_3 ,$$

the loop rule applied to the left-hand loop produces

$$\mathcal{E} - i_1 R_1 - i_2 R_2 = 0 ,$$

and the loop rule applied to the right-hand loop produces

$$i_2 R_2 - i_3 R_3 = 0 .$$

Since the resistances are all the same we can simplify the mathematics by replacing R_1 , R_2 , and R_3 with R . The solution to the three simultaneous equations is

$$i_1 = \frac{2\mathcal{E}}{3R} = \frac{2(1.2 \times 10^3 \text{ V})}{3(0.73 \times 10^6 \Omega)} = 1.1 \times 10^{-3} \text{ A}$$

and

$$i_2 = i_3 = \frac{\mathcal{E}}{3R} = \frac{1.2 \times 10^3 \text{ V}}{3(0.73 \times 10^6 \Omega)} = 5.5 \times 10^{-4} \text{ A} .$$

At $t = \infty$ the capacitor is fully charged and the current in the capacitor branch is 0. Thus, $i_1 = i_2$, and the loop rule yields

$$\mathcal{E} - i_1 R_1 - i_1 R_2 = 0 .$$

The solution is

$$i_1 = i_2 = \frac{\mathcal{E}}{2R} = \frac{1.2 \times 10^3 \text{ V}}{2(0.73 \times 10^6 \Omega)} = 8.2 \times 10^{-4} \text{ A} .$$

- (b) We take the upper plate of the capacitor to be positive. This is consistent with current flowing into that plate. The junction equation is $i_1 = i_2 + i_3$, and the loop equations are

$$\mathcal{E} - i_1 R - i_2 R = 0 \quad \text{and} \quad -\frac{q}{C} - i_3 R + i_2 R = 0 .$$

We use the first equation to substitute for i_1 in the second and obtain $\mathcal{E} - 2i_2 R - i_3 R = 0$. Thus $i_2 = (\mathcal{E} - i_3 R)/2R$. We substitute this expression into the third equation above to obtain $-(q/C) - (i_3 R) + (\mathcal{E}/2) - (i_3 R/2) = 0$. Now we replace i_3 with dq/dt to obtain

$$\frac{3R}{2} \frac{dq}{dt} + \frac{q}{C} = \frac{\mathcal{E}}{2} .$$

This is just like the equation for an RC series circuit, except that the time constant is $\tau = 3RC/2$ and the impressed potential difference is $\mathcal{E}/2$. The solution is

$$q = \frac{C\mathcal{E}}{2} \left(1 - e^{-2t/3RC} \right) .$$

The current in the capacitor branch is

$$i_3 = \frac{dq}{dt} = \frac{\mathcal{E}}{3R} e^{-2t/3RC} .$$

The current in the center branch is

$$\begin{aligned} i_2 &= \frac{\mathcal{E}}{2R} - \frac{i_3}{2} = \frac{\mathcal{E}}{2R} - \frac{\mathcal{E}}{6R} e^{-2t/3RC} \\ &= \frac{\mathcal{E}}{6R} \left(3 - e^{-2t/3RC} \right) \end{aligned}$$