

16. (a) The potential difference across C_1 is $V_1 = 10\text{ V}$. Thus, $q_1 = C_1 V_1 = (10\text{ }\mu\text{F})(10\text{ V}) = 1.0 \times 10^{-4}\text{ C}$.
(b) Let $C = 10\text{ }\mu\text{F}$. We first consider the three-capacitor combination consisting of C_2 and its two closest neighbors, each of capacitance C . The equivalent capacitance of this combination is

$$C_{\text{eq}} = C + \frac{C_2 C}{C + C_2} = 1.5C .$$

Also, the voltage drop across this combination is

$$V = \frac{C V_1}{C + C_{\text{eq}}} = \frac{C V_1}{C + 1.5C} = \frac{2}{5} V_1 .$$

Since this voltage difference is divided equally between C_2 and the one connected in series with it, the voltage difference across C_2 satisfies $V_2 = V/2 = V_1/5$. Thus

$$q_2 = C_2 V_2 = (10\text{ }\mu\text{F}) \left(\frac{10\text{ V}}{5} \right) = 2.0 \times 10^{-5}\text{ V} .$$