

9. (a) If i is the current and ΔV is the potential difference, then the power absorbed is given by $P = i \Delta V$. Thus,

$$\Delta V = \frac{P}{i} = \frac{50 \text{ W}}{1.0 \text{ A}} = 50 \text{ V} .$$

Since the energy of the charge decreases, point A is at a higher potential than point B; that is, $V_A - V_B = 50 \text{ V}$.

- (b) The end-to-end potential difference is given by $V_A - V_B = +iR + \mathcal{E}$, where \mathcal{E} is the emf of element C and is taken to be positive if it is to the left in the diagram. Thus, $\mathcal{E} = V_A - V_B - iR = 50 \text{ V} - (1.0 \text{ A})(2.0 \Omega) = 48 \text{ V}$.
- (c) A positive value was obtained for \mathcal{E} , so it is toward the left. The negative terminal is at B.