

55. (a) We assume i is from left to right through the closed switch. We let i_1 be the current in the resistor and take it to be downward. Let i_2 be the current in the inductor, also assumed downward. The junction rule gives $i = i_1 + i_2$ and the loop rule gives $i_1 R - L(di_2/dt) = 0$. According to the junction rule, $(di_1/dt) = -(di_2/dt)$. We substitute into the loop equation to obtain

$$L \frac{di_1}{dt} + i_1 R = 0 .$$

This equation is similar to Eq. 31-48, and its solution is the function given as Eq. 31-49:

$$i_1 = i_0 e^{-Rt/L} ,$$

where i_0 is the current through the resistor at $t = 0$, just after the switch is closed. Now just after the switch is closed, the inductor prevents the rapid build-up of current in its branch, so at that moment $i_2 = 0$ and $i_1 = i$. Thus $i_0 = i$, so

$$i_1 = i e^{-Rt/L} \quad \text{and} \quad i_2 = i - i_1 = i \left(1 - e^{-Rt/L} \right) .$$

- (b) When $i_2 = i_1$,

$$e^{-Rt/L} = 1 - e^{-Rt/L} \implies e^{-Rt/L} = \frac{1}{2} .$$

Taking the natural logarithm of both sides (and using $\ln(1/2) = -\ln 2$) we obtain

$$\left(\frac{Rt}{L} \right) = \ln 2 \implies t = \frac{L}{R} \ln 2 .$$