

70. (a) The rms current in the cable is $I_{\text{rms}} = P/V_t = 250 \times 10^3 \text{ W}/(80 \times 10^3 \text{ V}) = 3.125 \text{ A}$. The rms voltage drop is then $\Delta V = I_{\text{rms}}R = (3.125 \text{ A})(2)(0.30 \Omega) = 1.9 \text{ V}$, and the rate of energy dissipation is $P_d = I_{\text{rms}}^2 R = (3.125 \text{ A})^2(0.60 \Omega) = 5.9 \text{ W}$.
- (b) Now $I_{\text{rms}} = 250 \times 10^3 \text{ W}/(8.0 \times 10^3 \text{ V}) = 31.25 \text{ A}$, so $\Delta V = (31.25 \text{ A})(0.60 \Omega) = 19 \text{ V}$ and $P_d = (31.25 \text{ A})^2(0.60 \Omega) = 5.9 \times 10^2 \text{ W}$.
- (c) Now $I_{\text{rms}} = 250 \times 10^3 \text{ W}/(0.80 \times 10^3 \text{ V}) = 312.5 \text{ A}$, so $\Delta V = (312.5 \text{ A})(0.60 \Omega) = 1.9 \times 10^2 \text{ V}$ and $P_d = (312.5 \text{ A})^2(0.60 \Omega) = 5.9 \times 10^4 \text{ W}$. Both the rate of energy dissipation and the voltage drop increase as V_t decreases. Therefore, to minimize these effects the best choice among the three V_t 's above is $V_t = 80 \text{ kV}$.