

89. (a) The six resistors to the left of $\mathcal{E}_1 = 16 \text{ V}$ battery can be reduced to a single resistor $R = 8.0 \, \Omega$, through which the current must be $i_R = \mathcal{E}_1/R = 2.0 \text{ A}$. Now, by the loop rule, the current through the $3.0 \, \Omega$ and $1.0 \, \Omega$ resistors at the upper right corner is

$$i' = \frac{16.0 \text{ V} - 8.0 \text{ V}}{3.0 \, \Omega + 1.0 \, \Omega} = 2.0 \text{ A}$$

in a direction that is “backward” relative to the $\mathcal{E}_2 = 8.0 \text{ V}$ battery. Thus, by the junction rule,

$$i_1 = i_R + i' = 4.0 \text{ A}$$

and is upward (that is, in the “forward” direction relative to \mathcal{E}_1).

- (b) The current i_2 derives from a succession of symmetric splittings of i_R (reversing the procedure of reducing those six resistors to find R in part (a)). We find

$$i_2 = \frac{1}{2} \left(\frac{1}{2} i_R \right) = 0.50 \text{ A}$$

and is clearly downward.

- (c) Using our conclusions from part (a) in Eq. 28-14, we obtain $P = i_1 \mathcal{E}_1 = (4)(16) = 64 \text{ W}$ supplied.
 (d) Using results calculated in part (a) in Eq. 28-14, we obtain $P = i' \mathcal{E}_2 = (2)(8) = 16 \text{ W}$ absorbed.