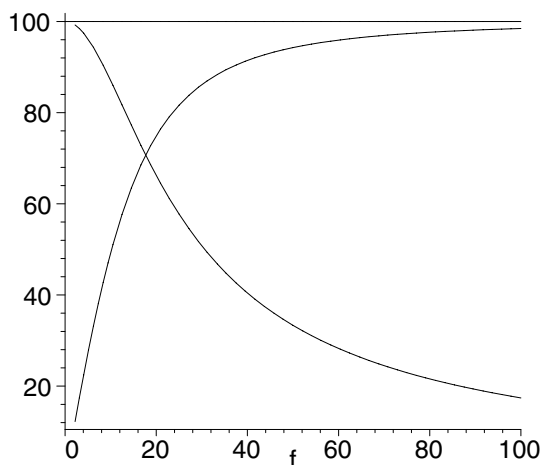


78. (a) The voltage amplitude for the source is $V_s = 100 \text{ V} = IZ = I\sqrt{R^2 + X_C^2}$, from which we can determine the current at each frequency (the explicit dependence of X_C on frequency is stated in the solution to part (a) of problem 77). This leads to the voltage amplitude across the resistor $V_R = IR$ and the voltage amplitude across the capacitor

$$V_C = IX_C = \left(\frac{V_s}{\sqrt{R^2 + X_C^2}} \right) X_C \quad \text{where} \quad X_C = \frac{1}{2\pi C f}$$

using the values $R = 200 \, \Omega$ and $C = 45 \times 10^{-6} \text{ F}$ given in problem 77. We show, below, the graphs of V_s , V_R and V_C over the range $0 < f < 100 \text{ Hz}$. The falling curve is V_C and the rising curve is V_R .



- (b) The graph indicates that V_C and V_R are equal at roughly 18 Hz. More careful considerations lead to $f = 17.7 \text{ Hz}$ as the frequency for which $V_C = V_R$.