

5. (a) Let  $i$  be the current in the circuit and take it to be positive if it is to the left in  $R_1$ . We use Kirchhoff's loop rule:  $\mathcal{E}_1 - iR_2 - iR_1 - \mathcal{E}_2 = 0$ . We solve for  $i$ :

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{12\text{ V} - 6.0\text{ V}}{4.0\,\Omega + 8.0\,\Omega} = 0.50\text{ A} .$$

A positive value is obtained, so the current is counterclockwise around the circuit.

- (b) If  $i$  is the current in a resistor  $R$ , then the power dissipated by that resistor is given by  $P = i^2R$ . For  $R_1$ ,  $P_1 = (0.50\text{ A})^2(4.0\,\Omega) = 1.0\text{ W}$  and for  $R_2$ ,  $P_2 = (0.50\text{ A})^2(8.0\,\Omega) = 2.0\text{ W}$ .
- (c) If  $i$  is the current in a battery with emf  $\mathcal{E}$ , then the battery supplies energy at the rate  $P = i\mathcal{E}$  provided the current and emf are in the same direction. The battery absorbs energy at the rate  $P = i\mathcal{E}$  if the current and emf are in opposite directions. For  $\mathcal{E}_1$ ,  $P_1 = (0.50\text{ A})(12\text{ V}) = 6.0\text{ W}$  and for  $\mathcal{E}_2$ ,  $P_2 = (0.50\text{ A})(6.0\text{ V}) = 3.0\text{ W}$ . In battery 1 the current is in the same direction as the emf. Therefore, this battery supplies energy to the circuit; the battery is discharging. The current in battery 2 is opposite the direction of the emf, so this battery absorbs energy from the circuit. It is charging.