

28. (a) R_2 , R_3 and R_4 are in parallel. By finding a common denominator and simplifying, the equation $1/R = 1/R_2 + 1/R_3 + 1/R_4$ gives an equivalent resistance of

$$R = \frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} = \frac{(50\ \Omega)(50\ \Omega)(75\ \Omega)}{(50\ \Omega)(50\ \Omega) + (50\ \Omega)(75\ \Omega) + (50\ \Omega)(75\ \Omega)} = 19\ \Omega .$$

Thus, considering the series contribution of resistor R_1 , the equivalent resistance for the network is $R_{\text{eq}} = R_1 + R = 100\ \Omega + 19\ \Omega = 1.2 \times 10^2\ \Omega$.

- (b) $i_1 = \mathcal{E}/R_{\text{eq}} = 6.0\ \text{V}/(1.1875 \times 10^2\ \Omega) = 5.1 \times 10^{-2}\ \text{A}$; $i_2 = (\mathcal{E} - V_1)/R_2 = (\mathcal{E} - i_1 R_1)/R_2 = [6.0\ \text{V} - (5.05 \times 10^{-2}\ \text{A})(100\ \Omega)]/50\ \Omega = 1.9 \times 10^{-2}\ \text{A}$; $i_3 = (\mathcal{E} - V_1)/R_3 = i_2 R_2/R_3 = (1.9 \times 10^{-2}\ \text{A})(50\ \Omega/50\ \Omega) = 1.9 \times 10^{-2}\ \text{A}$; $i_4 = i_1 - i_2 - i_3 = 5.0 \times 10^{-2}\ \text{A} - 2(1.895 \times 10^{-2}\ \text{A}) = 1.2 \times 10^{-2}\ \text{A}$.