

39. The current in  $R_2$  is  $i$ . Let  $i_1$  be the current in  $R_1$  and take it to be downward. According to the junction rule the current in the voltmeter is  $i - i_1$  and it is downward. We apply the loop rule to the left-hand loop to obtain

$$\mathcal{E} - iR_2 - i_1R_1 - ir = 0 .$$

We apply the loop rule to the right-hand loop to obtain

$$i_1R_1 - (i - i_1)R_V = 0 .$$

The second equation yields

$$i = \frac{R_1 + R_V}{R_V} i_1 .$$

We substitute this into the first equation to obtain

$$\mathcal{E} - \frac{(R_2 + r)(R_1 + R_V)}{R_V} i_1 + R_1 i_1 = 0 .$$

This has the solution

$$i_1 = \frac{\mathcal{E}R_V}{(R_2 + r)(R_1 + R_V) + R_1R_V} .$$

The reading on the voltmeter is

$$\begin{aligned} i_1R_1 &= \frac{\mathcal{E}R_VR_1}{(R_2 + r)(R_1 + R_V) + R_1R_V} \\ &= \frac{(3.0\text{ V})(5.0 \times 10^3\ \Omega)(250\ \Omega)}{(300\ \Omega + 100\ \Omega)(250\ \Omega + 5.0 \times 10^3\ \Omega) + (250\ \Omega)(5.0 \times 10^3\ \Omega)} = 1.12\text{ V} . \end{aligned}$$

The current in the absence of the voltmeter can be obtained by taking the limit as  $R_V$  becomes infinitely large. Then

$$i_1R_1 = \frac{\mathcal{E}R_1}{R_1 + R_2 + r} = \frac{(3.0\text{ V})(250\ \Omega)}{250\ \Omega + 300\ \Omega + 100\ \Omega} = 1.15\text{ V} .$$

The fractional error is  $(1.12 - 1.15)/(1.15) = -0.030$ , or  $-3.0\%$ .