

44. (a) The capacitive reactance is

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(400 \text{ Hz})(24.0 \times 10^{-6} \text{ F})} = 16.6 \, \Omega .$$

- (b) The impedance is

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (2\pi fL - X_C)^2} \\ &= \sqrt{(220 \, \Omega)^2 + [2\pi(400 \text{ Hz})(150 \times 10^{-3} \text{ H}) - 16.6 \, \Omega]^2} = 422 \, \Omega . \end{aligned}$$

- (c) The current amplitude is

$$I = \frac{\mathcal{E}_m}{Z} = \frac{220 \text{ V}}{422 \, \Omega} = 0.521 \text{ A} .$$

- (d) Now  $X_C \propto C_{\text{eq}}^{-1}$ . Thus,  $X_C$  increases as  $C_{\text{eq}}$  decreases.

- (e) Now  $C_{\text{eq}} = C/2$ , and the new impedance is

$$Z = \sqrt{(220 \, \Omega)^2 + [2\pi(400 \text{ Hz})(150 \times 10^{-3} \text{ H}) - 2(16.6 \, \Omega)]^2} = 408 \, \Omega < 422 \, \Omega .$$

Therefore, the impedance decreases.

- (f) Since  $I \propto Z^{-1}$ , it increases.