

52. (a) We do not employ energy conservation since, in reaching equilibrium, some energy is dissipated either as heat or radio waves. Charge is conserved; therefore, if  $Q = C_1 V_{\text{bat}} = 40 \mu\text{C}$ , and  $q_1$  and  $q_2$  are the charges on  $C_1$  and  $C_2$  after the switch is thrown to the right and equilibrium is reached, then

$$Q = q_1 + q_2 \quad .$$

Reducing the right portion of the circuit (the  $C_3$ ,  $C_4$  parallel pair which are in series with  $C_2$ ) we have an equivalent capacitance of  $C' = 8.0 \mu\text{F}$  which has charge  $q' = q_2$  and potential difference equal to that of  $C_1$ . Thus,

$$\begin{aligned} V_1 &= V' \\ \frac{q_1}{C_1} &= \frac{q_2}{C'} \end{aligned}$$

which yields  $4q_1 = q_2$ . Therefore,

$$Q = q_1 + 4q_1$$

leads to  $q_1 = 8.0 \mu\text{C}$  and consequently to  $q_2 = 32 \mu\text{C}$ .

- (b) From Eq. 26-1, we have  $V_2 = (32 \mu\text{C})(16 \mu\text{F}) = 2.0 \text{ V}$ .