

54. (a) When switch S is just closed (case I), $V_1 = \mathcal{E}$ and $i_1 = \mathcal{E}/R_1 = 10\text{ V}/5.0\ \Omega = 2.0\text{ A}$. After a long time (case II) we still have $V_1 = \mathcal{E}$, so $i_1 = 2.0\text{ A}$.
- (b) Case I: since now $\mathcal{E}_L = \mathcal{E}$, $i_2 = 0$; case II: since now $\mathcal{E}_L = 0$, $i_2 = \mathcal{E}/R_2 = 10\text{ V}/10\ \Omega = 1.0\text{ A}$.
- (c) Case I: $i = i_1 + i_2 = 2.0\text{ A} + 0 = 2.0\text{ A}$; case II: $i = i_1 + i_2 = 2.0\text{ A} + 1.0\text{ A} = 3.0\text{ A}$.
- (d) Case I: since $\mathcal{E}_L = \mathcal{E}$, $V_2 = \mathcal{E} - \mathcal{E}_L = 0$; case II: since $\mathcal{E}_L = 0$, $V_2 = \mathcal{E} - \mathcal{E}_L = \mathcal{E} = 10\text{ V}$.
- (e) Case I: $\mathcal{E}_L = \mathcal{E} = 10\text{ V}$; case II: $\mathcal{E}_L = 0$.
- (f) Case I: $di_2/dt = \mathcal{E}_L/L = \mathcal{E}/L = 10\text{ V}/5.0\text{ H} = 2.0\text{ A/s}$; case II: $di_2/dt = \mathcal{E}_L/L = 0$.