

37. (a) Now $X_C = 0$, while $R = 160\ \Omega$ and $X_L = 86.7\ \Omega$ remain unchanged. Therefore, the impedance is

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(160\ \Omega)^2 + (86.7\ \Omega)^2} = 182\ \Omega .$$

The current amplitude is now found to be

$$I = \frac{\mathcal{E}_m}{Z} = \frac{36.0\ \text{V}}{182\ \Omega} = 0.198\ \text{A} .$$

The phase angle is, from Eq. 33-65,

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{86.7\ \Omega - 0}{160\ \Omega} \right) = 28.5^\circ .$$

- (b) We first find the voltage amplitudes across the circuit elements:

$$V_R = IR = (0.198\ \text{A})(160\ \Omega) \approx 32\ \text{V}$$

$$V_L = IX_L = (0.198\ \text{A})(86.7\ \Omega) \approx 17\ \text{V}$$

This is an inductive circuit, so \mathcal{E}_m leads I . The phasor diagram is drawn to scale below.

