

41. Let the current in the ammeter be i' . We have $V = i'(R + R_A)$, or $R = V/i' - R_A = R' - R_A$, where $R' = V/i'$ is the apparent reading of the resistance.