

60. (a) The power consumed by the light bulb is  $P = I^2 R/2$ . So we must let  $P_{\max}/P_{\min} = (I/I_{\min})^2 = 5$ , or

$$\left(\frac{I}{I_{\min}}\right)^2 = \left(\frac{\mathcal{E}_m/Z_{\min}}{\mathcal{E}_m/Z_{\max}}\right)^2 = \left(\frac{Z_{\max}}{Z_{\min}}\right)^2 = \left(\frac{\sqrt{R^2 + (\omega L_{\max})^2}}{R}\right)^2 = 5 .$$

We solve for  $L_{\max}$ :

$$L_{\max} = \frac{2R}{\omega} = \frac{2(120 \text{ V})^2/1000 \text{ W}}{2\pi(60.0 \text{ Hz})} = 7.64 \times 10^{-2} \text{ H} .$$

- (b) Now we must let

$$\left(\frac{R_{\max} + R_{\text{bulb}}}{R_{\text{bulb}}}\right)^2 = 5 ,$$

or

$$R_{\max} = (\sqrt{5} - 1)R_{\text{bulb}} = (\sqrt{5} - 1)\frac{(120 \text{ V})^2}{1000 \text{ W}} = 17.8 \Omega .$$

This is not done because the resistors would consume, rather than temporarily store, electromagnetic energy.