

36. (a) Since $i = \mathcal{E}/(r + R_{\text{ext}})$ and $i_{\text{max}} = \mathcal{E}/r$, we have $R_{\text{ext}} = R(i_{\text{max}}/i - 1)$ where $r = 1.50 \text{ V}/1.00 \text{ mA} = 1.50 \times 10^3 \Omega$. Thus, $R_{\text{ext}} = (1.5 \times 10^3 \Omega)(1/0.10 - 1) = 1.35 \times 10^4 \Omega$;
- (b) $R_{\text{ext}} = (1.5 \times 10^3 \Omega)(1/0.50 - 1) = 1.50 \times 10^3 \Omega$;
- (c) $R_{\text{ext}} = (1.5 \times 10^3 \Omega)(1/0.90 - 1) = 167 \Omega$.
- (d) Since $r = 20.0 \Omega + R$, $R = 1.50 \times 10^3 \Omega - 20.0 \Omega = 1.48 \times 10^3 \Omega$.