

69. (a) The energy stored in the capacitor is given by $U_E = q^2/2C$. Since q is a periodic function of t with period T , so must be U_E . Consequently, U_E will not be changed over one complete cycle. Actually, U_E has period $T/2$, which does not alter our conclusion.
- (b) Similarly, the energy stored in the inductor is $U_B = \frac{1}{2}i^2L$. Since i is a periodic function of t with period T , so must be U_B .
- (c) The energy supplied by the generator is

$$P_{\text{avg}}T = (I_{\text{rms}}\mathcal{E}_{\text{rms}} \cos \phi)T = \left(\frac{1}{2}T\right) \mathcal{E}_m I \cos \phi$$

where we substitute $I_{\text{rms}} = I/\sqrt{2}$ and $\mathcal{E}_{\text{rms}} = \mathcal{E}_m/\sqrt{2}$.

- (d) The energy dissipated by the resistor is

$$P_{\text{avg, resistor}} T = (I_{\text{rms}} V_R)T = I_{\text{rms}}(I_{\text{rms}} R)T = \left(\frac{1}{2}T\right) I^2 R .$$

- (e) Since $\mathcal{E}_m I \cos \phi = \mathcal{E}_m I (V_R/\mathcal{E}_m) = \mathcal{E}_m I (IR/\mathcal{E}_m) = I^2 R$, the two quantities are indeed the same.