

47. (a) The voltage difference V across the capacitor varies with time as $V(t) = \mathcal{E}(1 - e^{-t/RC})$. At $t = 1.30 \mu\text{s}$ we have $V(t) = 5.00 \text{ V}$, so $5.00 \text{ V} = (12.0 \text{ V})(1 - e^{-1.30 \mu\text{s}/RC})$, which gives $\tau = (1.30 \mu\text{s})/\ln(12/7) = 2.41 \mu\text{s}$.
- (b) $C = \tau/R = 2.41 \mu\text{s}/15.0 \text{ k}\Omega = 161 \text{ pF}$.