

38. (a) $\mathcal{E} = V + ir = 12\text{ V} + (10\text{ A})(0.050\text{ }\Omega) = 12.5\text{ V}.$

(b) Now $\mathcal{E} = V' + (i_{\text{motor}} + 8.0\text{ A})r$, where $V' = i'_A R_{\text{light}} = (8.0\text{ A})(12\text{ V}/10\text{ A}) = 9.6\text{ V}.$ Therefore,

$$i_{\text{motor}} = \frac{\mathcal{E} - V'}{r} - 8.0\text{ A} = \frac{12.5\text{ V} - 9.6\text{ V}}{0.050\text{ }\Omega} - 8.0\text{ A} = 50\text{ A} .$$