

23. The energy needed to charge the  $100\text{ }\mu\text{F}$  capacitor to  $300\text{ V}$  is

$$\frac{1}{2}C_2V^2 = \frac{1}{2}(100 \times 10^{-6}\text{ F})(300\text{ V})^2 = 4.50\text{ J} .$$

The energy initially in the  $900\text{ }\mu\text{F}$  capacitor is

$$\frac{1}{2}C_1V^2 = \frac{1}{2}(900 \times 10^{-6}\text{ F})(100\text{ V})^2 = 4.50\text{ J} .$$

All the energy originally in the  $900\text{ }\mu\text{F}$  capacitor must be transferred to the  $100\text{ }\mu\text{F}$  capacitor. The plan is to store it temporarily in the inductor. We do this by leaving switch  $S_1$  open and closing switch  $S_2$ . We wait until the  $900\text{ }\mu\text{F}$  capacitor is completely discharged and the current in the circuit is at maximum (this occurs at  $t = T_1/4$ , one quarter of the relevant period). Since

$$T_1 = 2\pi\sqrt{LC_1} = 2\pi\sqrt{(10.0\text{ H})(900 \times 10^{-6}\text{ F})} = 0.596\text{ s} ,$$

we wait until  $t = (0.596\text{ s})/4 = 0.149\text{ s}$ . Now, we close switch  $S_1$  while simultaneously opening switch  $S_2$ . Next, we wait for one-fourth of the  $T_2$  period to elapse and open switch  $S_1$ . The  $100\text{ }\mu\text{F}$  capacitor then has maximum charge, and all the energy resides in it. Since

$$T_2 = 2\pi\sqrt{LC_2} = 2\pi\sqrt{(10.0\text{ H})(100 \times 10^{-6}\text{ F})} = 0.199\text{ s} ,$$

we must keep  $S_1$  closed for  $(0.199\text{ s})/4 = 0.0497\text{ s}$ . It is helpful to refer to Figure 23-1 to appreciate the emphasis on “quarter-periods” in this solution.