

39. (a) The capacitive reactance is

$$X_C = \frac{1}{\omega_d C} = \frac{1}{2\pi f_d C} = \frac{1}{2\pi(60.0 \text{ Hz})(70.0 \times 10^{-6} \text{ F})} = 37.9 \, \Omega .$$

The inductive reactance  $86.7 \, \Omega$  is unchanged. The new impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(160 \, \Omega)^2 + (37.9 \, \Omega - 86.7 \, \Omega)^2} = 167 \, \Omega .$$

The current amplitude is

$$I = \frac{\mathcal{E}_m}{Z} = \frac{36.0 \text{ V}}{167 \, \Omega} = 0.216 \text{ A} .$$

The phase angle is

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{86.7 \, \Omega - 37.9 \, \Omega}{160 \, \Omega} \right) = 17.0^\circ .$$

(b) We first find the voltage amplitudes across the circuit elements:

$$V_R = IR = (0.216 \text{ A})(160 \, \Omega) = 34.6 \text{ V}$$

$$V_L = IX_L = (0.216 \text{ A})(86.7 \, \Omega) = 18.7 \text{ V}$$

$$V_C = IX_C = (0.216 \text{ A})(37.9 \, \Omega) = 8.19 \text{ V}$$

Note that  $X_L > X_C$ , so that  $\mathcal{E}_m$  leads  $I$ . The phasor diagram is drawn to scale below.

